

1	INTRODUCTION TO SMALL-SIGNAL MODELING.....	1
1.1	LINEAR SYSTEMS.....	1
1.1.1	Linearization by Perturbation	2
1.1.2	Gain and Slope.....	5
1.1.3	The Importance of the Bias Point	8
1.1.4	A Small-Signal Model	10
1.1.5	Partial Differentiation	14
1.2	SWITCHING CONVERTERS—BASIC CELLS	16
1.2.1	Input and Output Ripple.....	18
1.2.2	Conduction Modes	19
1.2.3	Indirect Energy Transfer.....	25
1.2.4	Reversing Output Voltage Polarity.....	31
1.2.5	Inductive and Capacitive Equilibrium.....	35
1.2.6	Conversion Ratios of Switching Converters	41
1.2.7	Considering Losses in Conversion Ratios	43
1.2.8	Isolated Versions.....	49
1.2.9	Generating the Duty Ratio—The PWM Block	51
1.2.10	Frequency Response of the PWM Block.....	53
1.2.11	From a Static to a Quasi-Static Transfer Function	56
1.2.12	Adding Feedforward to the PWM Block.....	59
1.2.13	Voltage-Mode and Current-Mode Control.....	61
1.2.14	Quasi-Square-Wave Resonant Converters	69
1.2.15	Hysteretic Converters	72
1.3	THE PWM SWITCH MODEL IN VOLTAGE MODE CONTROL	76
1.3.1	Small-Signal Model in CCM.....	82
1.3.2	The PWM Switch Operated in DCM	82
1.3.3	Small-Signal Model in DCM	87
1.3.4	Dc Operating Points with the PWM Switch Model.....	90
1.3.5	Quasi-Resonant Operation	97
1.4	THE PWM SWITCH MODEL IN CURRENT MODE CONTROL.....	102
1.4.1	Small-Signal Model in CCM.....	112
1.4.2	Small-Signal Model in DCM	115
1.4.3	Small-Signal Model in QR.....	121
1.4.4	Constant On-Time Valley Current Control.....	125
1.4.5	Constant Off-Time Peak Current Control.....	130
1.5	WHAT SHOULD I RETAIN FROM THIS CHAPTER?.....	135
1.6	REFERENCES	136
2	THE BUCK CONVERTER AND ITS DERIVATIVES.....	137
2.1	BUCK TRANSFER FUNCTIONS IN CCM — FIXED-FREQUENCY VOLTAGE-MODE CONTROL.....	137
2.1.1	Input to Output	147
2.1.2	Output Impedance	149
2.1.3	Input Impedance	153

2.2	BUCK TRANSFER FUNCTIONS IN DCM—FIXED-FREQUENCY VOLTAGE-MODE CONTROL.....	159
2.2.1	<i>Input to Output</i>	171
2.2.2	<i>Output Impedance</i>	175
2.2.3	<i>Input Impedance</i>	180
2.3	BUCK TRANSFER FUNCTIONS IN CCM—PEAK-CURRENT-MODE CONTROL	189
2.3.1	<i>Input to Output</i>	198
2.3.2	<i>Output Impedance</i>	202
2.3.3	<i>Input Impedance</i>	205
2.4	BUCK TRANSFER FUNCTIONS IN DCM—PEAK-CURRENT-MODE CONTROL	214
2.4.1	<i>Input to Output</i>	223
2.4.2	<i>Output Impedance</i>	225
2.4.3	<i>Input Impedance</i>	230
2.5	TAPPED BUCK TRANSFER FUNCTION IN CCM—VOLTAGE-MODE CONTROL	236
2.6	QUASI-RESONANT BUCK TRANSFER FUNCTION—CURRENT-MODE CONTROL.....	243
2.7	CONSTANT ON-TIME BUCK TRANSFER FUNCTION—CURRENT-MODE CONTROL	249
2.8	FIXED OFF-TIME BUCK TRANSFER FUNCTION—CURRENT-MODE CONTROL	236
2.9	FIXED FREQUENCY MULTIPHASE BUCK TRANSFER FUNCTION—VOLTAGE- AND CURRENT-MODE CONTROL	255
2.10	ISOLATED BUCK-DERIVED CONVERTERS: THE FORWARD CONVERTER IN VOLTAGE-MODE CONTROL	260
2.11	ISOLATED BUCK-DERIVED CONVERTERS: THE FORWARD CONVERTER IN CURRENT-MODE CONTROL	263
2.12	ISOLATED BUCK-DERIVED CONVERTERS: THE FORWARD CONVERTER WITH ACTIVE CLAMP IN VOLTAGE-MODE CONTROL	270
2.13	ISOLATED BUCK-DERIVED CONVERTERS: THE PUSH-PULL CONVERTER IN CURRENT- AND VOLTAGE-MODE CONTROL.....	273
2.14	ISOLATED BUCK-DERIVED CONVERTERS: THE HALF- AND FULL- BRIDGE CONVERTERS	276
2.15	ISOLATED BUCK-DERIVED CONVERTERS: THE PHASE-SHIFTED FULL-BRIDGE CONVERTER IN VOLTAGE-MODE CONTROL.....	279
2.16	ISOLATED BUCK-DERIVED CONVERTERS: THE PHASE-SHIFTED FULL-BRIDGE CONVERTER IN CURRENT-MODE CONTROL.....	282
2.17	WHAT SHOULD I RETAIN FROM THIS CHAPTER?.....	284
2.18	REFERENCES	285
3	THE BOOST CONVERTER AND ITS DERIVATIVES.....	286
3.1	BOOST TRANSFER FUNCTIONS IN CCM—FIXED-FREQUENCY VOLTAGE-MODE CONTROL	286
3.1.1	<i>Input to Output</i>	299
3.1.2	<i>Output Impedance</i>	302
3.1.3	<i>Input Impedance</i>	306
3.2	BOOST TRANSFER FUNCTIONS IN DCM—FIXED-FREQUENCY VOLTAGE-MODE CONTROL.....	312
3.2.1	<i>Input to Output</i>	324
3.2.2	<i>Output Impedance</i>	327
3.2.3	<i>Input Impedance</i>	332
3.3	BOOST TRANSFER FUNCTIONS IN CCM—FIXED-FREQUENCY CURRENT-MODE CONTROL.....	338
3.3.1	<i>Input to Output</i>	357

3.3.2	<i>Output Impedance</i>	362
3.3.3	<i>Input Impedance</i>	367
3.4	BOOST TRANSFER FUNCTIONS IN DCM—FIXED-FREQUENCY CURRENT-MODE CONTROL	376
3.4.1	<i>Input to Output</i>	389
3.4.2	<i>Output Impedance</i>	394
3.4.3	<i>Input Impedance</i>	398
3.5	TAPPED BOOST TRANSFER FUNCTIONS IN CCM—VOLTAGE-MODE CONTROL	405
3.6	FIXED-FREQUENCY MULTIPHASE BOOST TRANSFER FUNCTION—VOLTAGE- AND CURRENT-MODE CONTROL	411
3.7	QUASI-RESONANT BOOST TRANSFER FUNCTION—CURRENT-MODE CONTROL	416
3.8	BOOST IN POWER FACTOR CORRECTION—BOUNDARY MODE VOLTAGE-MODE CONTROL	424
3.9	BOOST IN POWER FACTOR CORRECTION—BOUNDARY MODE CURRENT-MODE CONTROL	435
3.10	WHAT SHOULD I RETAIN FROM THIS CHAPTER?.....	442
3.11	REFERENCES	442
4	THE BUCK-BOOST CONVERTER AND ITS DERIVATIVES	443
4.1	BUCK-BOOST TRANSFER FUNCTIONS IN CCM—FIXED-FREQUENCY VOLTAGE-MODE CONTROL	443
4.1.1	<i>Input to Output</i>	454
4.1.2	<i>Output Impedance</i>	457
4.1.3	<i>Input Impedance</i>	461
4.5	BUCK-BOOST TRANSFER FUNCTIONS IN DCM—FIXED-FREQUENCY VOLTAGE-MODE CONTROL	468
4.2.1	<i>Input to Output</i>	476
4.2.2	<i>Output Impedance</i>	479
4.2.3	<i>Input Impedance</i>	484
4.9	BUCK-BOOST TRANSFER FUNCTIONS IN CCM—FIXED-FREQUENCY CURRENT-MODE CONTROL	493
4.3.1	<i>Input to Output</i>	511
4.3.2	<i>Output Impedance</i>	516
4.3.3	<i>Input Impedance</i>	522
4.13	BUCK-BOOST TRANSFER FUNCTIONS IN DCM—FIXED-FREQUENCY CURRENT-MODE CONTROL	535
4.4.1	<i>Input to Output</i>	548
4.4.2	<i>Output Impedance</i>	554
4.4.3	<i>Input Impedance</i>	560
4.17	THE FLYBACK CONVERTER OPERATED IN VOLTAGE-MODE CONTROL	567
4.18	THE FLYBACK CONVERTER OPERATED IN CURRENT-MODE CONTROL.....	572
4.19	THE FLYBACK CONVERTER OPERATED IN QUASI-SQUARE-WAVE RESONANT MODE	580
4.20	THE FLYBACK IN SINGLE-STAGE POWER FACTOR CORRECTION—CURRENT MODE	585
4.21	THE FLYBACK IN SINGLE-STAGE POWER FACTOR CORRECTION—VOLTAGE MODE	594
4.22	WHAT SHOULD I RETAIN FROM THIS CHAPTER?.....	603
4.23	REFERENCES	604
5	HIGH-ORDER CONVERTERS	605
5.1	THE ĆUK CONVERTER.....	605
5.1.1	<i>Coupled Inductors</i>	610
5.1.2	<i>Isolated Version</i>	616
5.2	THE SEPIC.....	622

5.2.1	<i>Coupled Inductors</i>	629
5.2.2	<i>Current Mode Control</i>	635
5.2.3	<i>Coupled Inductors</i>	638
5.3	THE ZETA	641
5.3.1	<i>Coupled Inductors</i>	646
5.3.2	<i>Current Mode Control</i>	649
5.4	THE LLC CONVERTER	652
5.4.1	<i>Current Mode Control</i>	659
5.5	WHAT SHOULD I RETAIN FROM THIS CHAPTER?.....	662
5.6	REFERENCES	663
5.7	CONCLUSION	663

APPENDIX A—FAST ANALYTICAL CIRCUITS TECHNIQUES OR FACTS665

1	A QUICK INTRODUCTION TO FAST ANALYTICAL TECHNIQUES.....	665
2	ZEROES OF THE NETWORK	666
3	POLES IN THE NETWORK.....	670
4	A COMMON DENOMINATOR	675
5	THE FACTS APPLIED TO A SECOND-ORDER SYSTEM.....	681
6	REFERENCES	685