

Table of Content

• The Subcircuits	3
• The Compensators	4
• Introduction	5
• Working with the Templates	54
• Buck Converter in Voltage-Mode Control – AC Analysis	57
• Buck Converter in Current-Mode Control – AC Analysis	58
• The Frequency-Response Analyzer (FRA)	59
• A Simple Buck with the Frequency Response Analyzer	61
• A Cycle-by-Cycle Buck in Voltage-Mode Control	64
• A Cycle-by-Cycle Buck in Current-Mode Control	65
• A Constant On-Time Buck Converter	66
• Forward Converter in Current-Mode Control – AC Analysis	71
• Single-Switch Forward Cycle-by-Cycle – Current-Mode Control	73
• Two-Switch Forward Converter with UC3845	75
• Multi-Output Forward Converter Cycle-by-Cycle	76
• Forward Converter Active-Clamp Voltage-Mode Control	77
• Full-Bridge Converter in Current-Mode Control	78
• Phase-Shifted Full-Bridge in Voltage-Mode Control	79
• Dual-Active-Bridge Converter	80
• Boost Converter in Voltage-Mode Control – AC Analysis	81
• Boost Converter in Current-Mode Control – AC Analysis	82
• A Simple Boost with the Frequency Response Analyzer	83
• Monte Carlo Analysis of the Averaged Boost Converter	85
• A Cycle-by-Cycle Boost in Voltage-Mode Control	87
• A Cycle-by-Cycle Boost in Current-Mode Control	88
• Power Factor Corrector in Borderline Conduction Mode	89
• Power Factor Corrector in Continuous Conduction Mode	92
• Totem-Pole Power Factor Correction	94

Table of Content

• A Three-Phase Vienna Rectifier	95
• Buck-Boost Converter in Voltage-Mode Control – AC Analysis	97
• Buck-Boost Converter in Current-Mode Control – AC Analysis	98
• A Simple Buck-Boost with the Frequency Response Analyzer	99
• A Cycle-by-Cycle Buck-Boost in Voltage-Mode Control	101
• A Cycle-by-Cycle Buck-Boost in Current-Mode Control	102
• The Flyback Converter in Current-Mode Control – AC Analysis	103
• Flyback Converter operated from the AC Mains	105
• A Cycle-by-Cycle Flyback Converter with Frequency Foldback	106
• Two-Switch Flyback Converter in Current-Mode Control	108
• Flyback Converter Active-Clamp Current-Mode Control	109
• Flyback Converter Asymmetrical Half-Bridge	110
• Flyback Converter in QR Current-Mode Control	111
• A Multi-Output Flyback Converter in Current-Mode Control	112
• Coupled-Inductor SEPIC in Current-Mode Control – AC Analysis	116
• A Cycle-by-Cycle SEPIC in Current-Mode Control	117
• Coupled-Inductor Ćuk in Voltage-Mode Control – AC Analysis	118
• Coupled-Inductor Zeta in Current-Mode Control – AC Analysis	119
• A Cycle-by-Cycle Zeta in Current-Mode Control	121
• DC-Transfer Characteristic of the LLC Converter	122
• LLC Converter in Direct-Frequency Control – Open Loop	124
• LLC Converter in Direct-Frequency Control – FRA Analysis	125
• A Cycle-by-Cycle LLC Converter with Bootstrap	126
• LLC Converter in Bang-Bang Charge-Control	128
• LLC Converter in Current-Mode Control – A CC-CV Charger	129
• References and Books	130

The Subcircuits

• The Op-Amp Generic Model	6
• Testing the Op-Amp	7
• Improving the Op-Amp Model	9
• A Simple Transformer Model	11
• A Dual-Winding Version	12
• A Push-Pull Transformer	14
• A Simple SR Latch Circuit	15
• A D Flip-Flop	16
• A Basic Comparator	17
• Adding Dead Time	18
• Small-Pulse Generator	19
• A Digital Delay	20
• Optocoupler Models	21
• The TL431 Generic Model	23
• Voltage-Controlled Oscillator	24
• Voltage-Mode Controller	25
• Current-Mode Controller	26
• Quasi-Resonant Controller	27
• An Asymmetrical Half-Bridge Controller	28
• Push-Pull Controllers	29
• Phase-Shift Controllers	30
• A Dual Active Bridge Controller	31
• A Voltage-Mode LLC Controller	32
• A Current-Mode LLC Controller	33
• A Bang-Bang Charge-Controlled LLC Controller	34
• The UC34X Controllers	35
• Operating Parameters for the Subcircuits	36

The Compensators

• Type 1 with an Operational-Amplifier	37
• Type 2 with an Operational-Amplifier	38
• Type 3 with an Operational-Amplifier	39
• Type 1 with an Operational Transconductance Amplifier	40
• Type 2 with an Operational Transconductance Amplifier	41
• Type 1 with a TL431 and an Optocoupler	42
• Type 2 with a TL431 and an Optocoupler	43
• Type 2 with a TL431 – no Fast Lane	44
• Type 3 with a TL431 and an Optocoupler	45
• Type 3 with a TL431 – no Fast Lane	46
• A Simple Filtered PID Compensator	47
• PID to Type 3 Compensator	48
• A Digital Type 2 Compensator	49
• A Digital Type 3 Compensator	50
• A Digital Filtered PID	52
• A Digital PI	53