



ON Semiconductor®

Small-Signal Modeling of the Boost Converter Operated in CM

Christophe Basso

IEEE Senior Member

Course Agenda

- ❑ The PWW Switch Concept
- ❑ Small-Analysis in Continuous Conduction Mode
- ❑ Small-Signal Response in Discontinuous Mode
- ❑ EMI Filter Output Impedance
- ❑ Cascaded Converters Operation





Course Agenda

- The PWW Switch Concept**
- Small-Analysis in Continuous Conduction Mode
- Small-Signal Response in Discontinuous Mode
- EMI Filter Output Impedance
- Cascaded Converters Operation




Non-Linearity in a Switching Converter

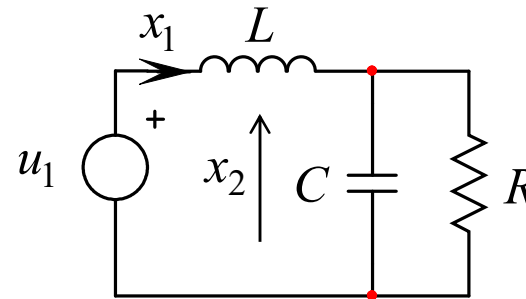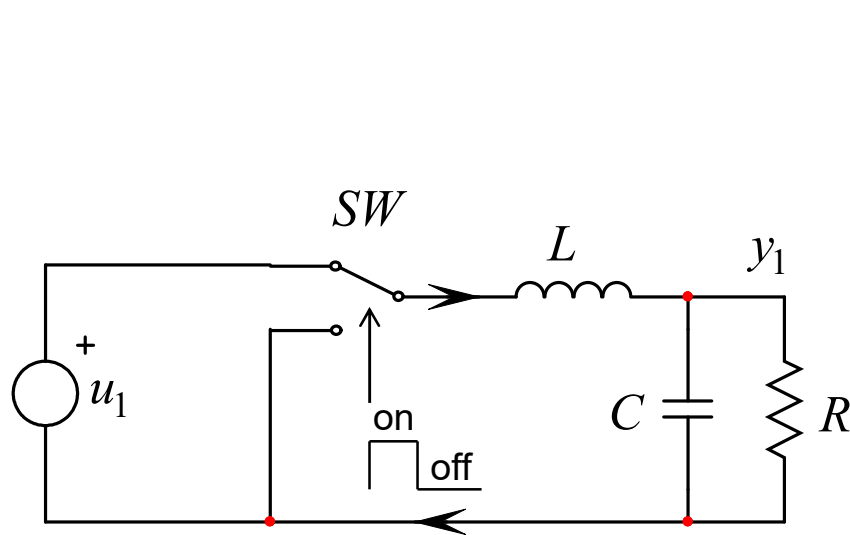□ A switching converter is ruled by linear equations...



during
 DT_{sw}

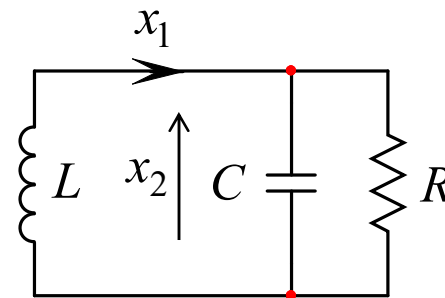


during
 $(1-D)T_{sw}$

□ ...combining so-called state variables

State Variables

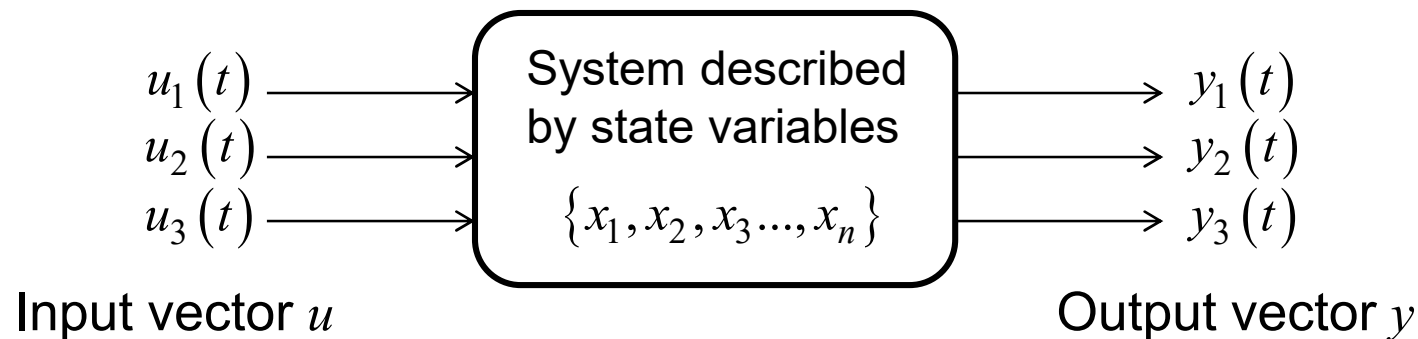- ❑ State variables describe the mathematical state of a system
- ❑ n state variables for n independent storage elements
- ❑ knowing variables state at t_0 helps compute outputs for $t > t_0$




- ❑ x_1 is the inductor current and x_2 is the capacitor voltage
- ❑ Differentiation gives the state variable rate of change

$$x_1 = i_L(t) \quad \dot{x}_1 = \frac{di_L(t)}{dt} \quad \text{Predict future system state} \quad x_2 = v_C(t) \quad \dot{x}_2 = \frac{dv_C(t)}{dt}$$

Describe the System During the On-Time

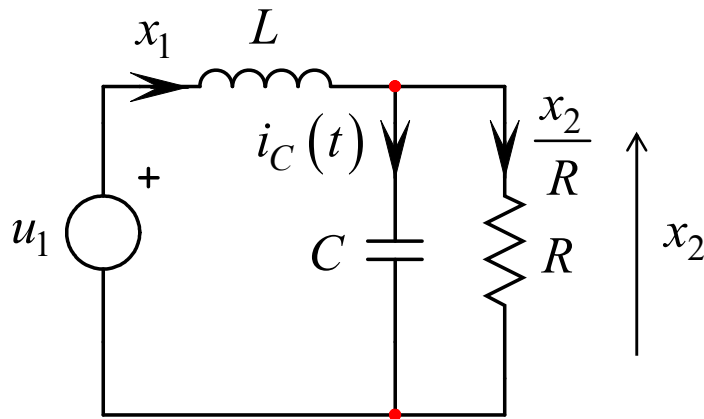- Observe the system during the on-time duration or dT_{SW} :



$$i_C(t) = C \frac{dv_C(t)}{dt} = C\dot{x}_2 = x_1 - \frac{1}{R}x_2$$

$$u_1 = L \frac{di_L(t)}{dt} + v_C(t) = L\dot{x}_1 + x_2$$


$$\left. \begin{aligned} \dot{x}_1 &= -\frac{1}{L}x_2 + \frac{1}{L}u_1 \\ \dot{x}_2 &= \frac{1}{C}x_1 - \frac{1}{RC}x_2 \end{aligned} \right\} \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 1/L & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix}$$

State coefficients Source coefficients



Describe the System During the Off-Time

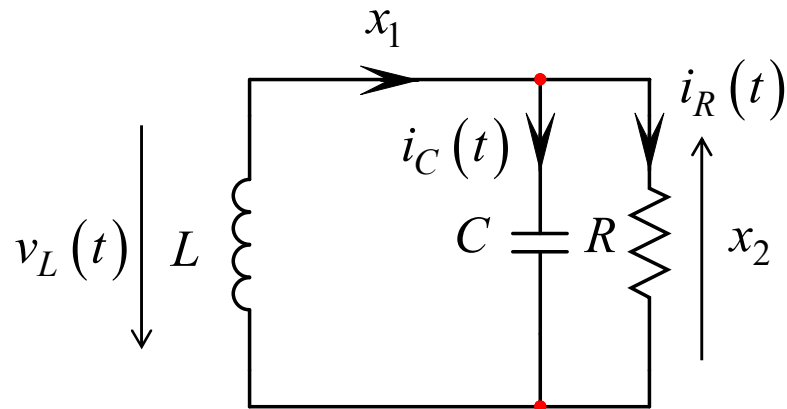- Repeat the exercise during the off-time duration or $1-dT_{SW}$



$$v_L(t) = -x_2 \quad v_L(t) = L\dot{x}_1$$

$$\Rightarrow x_2 = -L\dot{x}_1$$

$$i_R(t) = x_1 - i_C(t) = x_1 - C\dot{x}_2$$

$$x_2 = i_R(t)R$$

$$\Rightarrow x_2 = R(x_1 - C\dot{x}_2)$$

$$\Rightarrow \left. \begin{aligned} \dot{x}_1 &= 0 - \frac{1}{L}x_2 \\ \dot{x}_2 &= \frac{1}{C}x_1 - \frac{1}{RC}x_2 \end{aligned} \right\}$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix}$$

State coefficients

Source coefficients

Make it Fit the State Equation Format

- Arrange expressions to make them fit the format:

$$\dot{x} = \mathbf{A}x(t) + \mathbf{B}u(t) \quad \text{State equation}$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \overset{\text{on-time network}}{\begin{bmatrix} 1/L & 0 \\ 0 & 0 \end{bmatrix}} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} \Rightarrow \mathbf{A}_1 = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \mathbf{B}_1 = \begin{bmatrix} 1/L & 0 \\ 0 & 0 \end{bmatrix}$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \overset{\text{off-time network}}{\begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} \Rightarrow \mathbf{A}_2 = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \mathbf{B}_2 = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$$

- How do we link matrixes \mathbf{A}_1 and \mathbf{A}_2 , \mathbf{B}_1 and \mathbf{B}_2 ?
- We smooth the discontinuity by weighting them by D and $1-D$

$$\dot{x} = \left[\mathbf{A}_1 D + \mathbf{A}_2 (1-D) \right] x(t) + \left[\mathbf{B}_1 D + \mathbf{B}_2 (1-D) \right] u(t)$$


The State-Space Averaging Method (SSA)

- We now have a continuous large-signal equation
- We need to linearize it via perturbations

$$D = D_0 + \hat{d} \quad x = x_0 + \hat{x} \quad u = u_0 + \hat{u}$$


$$\dot{x} = \left[\mathbf{A}_1 D + \mathbf{A}_2 (1 - D) \right] x(t) + \left[\mathbf{B}_1 d + \mathbf{B}_2 (1 - D) \right] u(t)$$
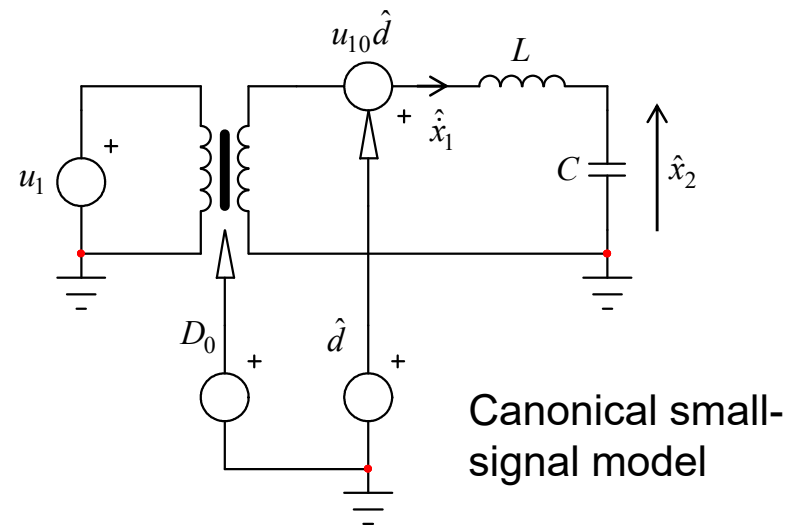
$$\begin{aligned} \hat{\dot{x}}_1 &= \frac{1}{L} \hat{x}_2 + \frac{D_0}{L} \hat{u}_1 + \frac{\hat{d}}{L} u_{10} \\ \hat{\dot{x}}_2 &= \frac{1}{C} \hat{x}_1 - \frac{1}{RC} \hat{x}_2 \end{aligned}$$



The State-Space Averaging Method (SSA)

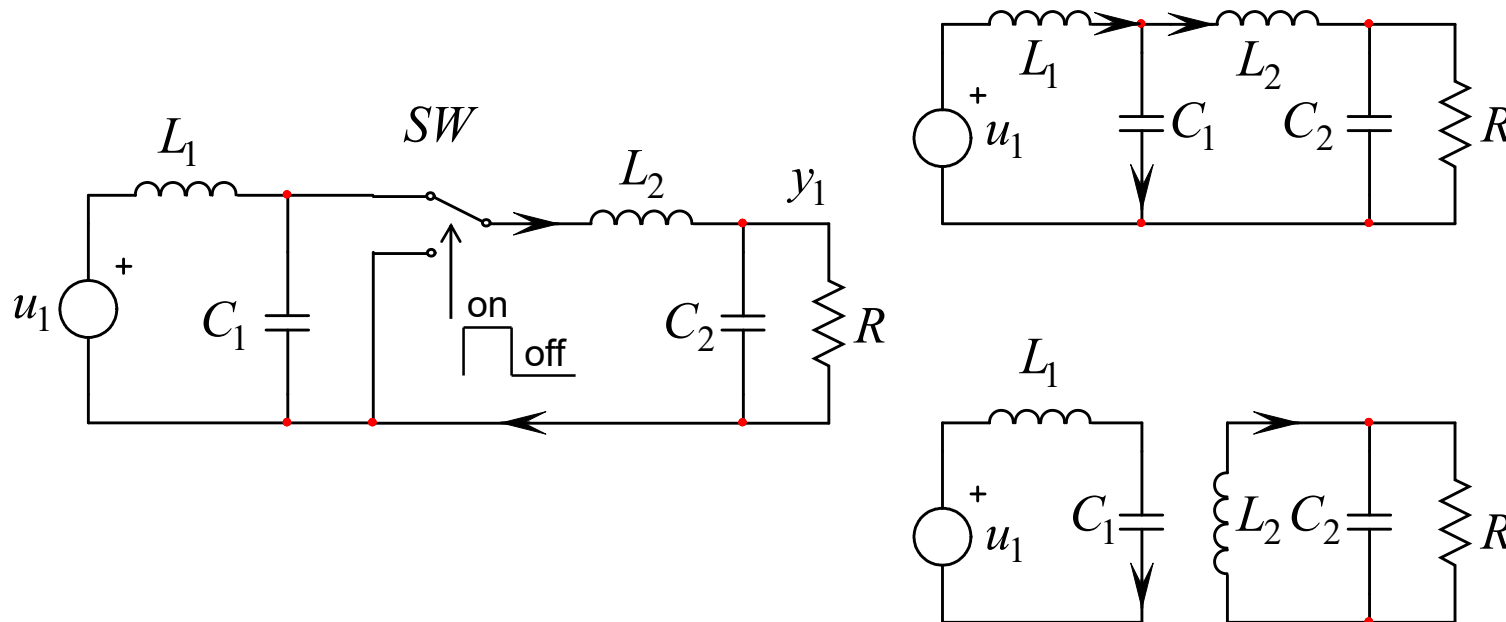
- ❑ SSA was applied to switching converters by Dr Ćuk in 1976
- ❑ It is a long, painful process, manipulating numerous terms
- ❑ What if you add an EMI filter for instance?




- ❑ 4 state variables and you have to re-derive all equations!

The PWM Switch Model in Voltage Mode

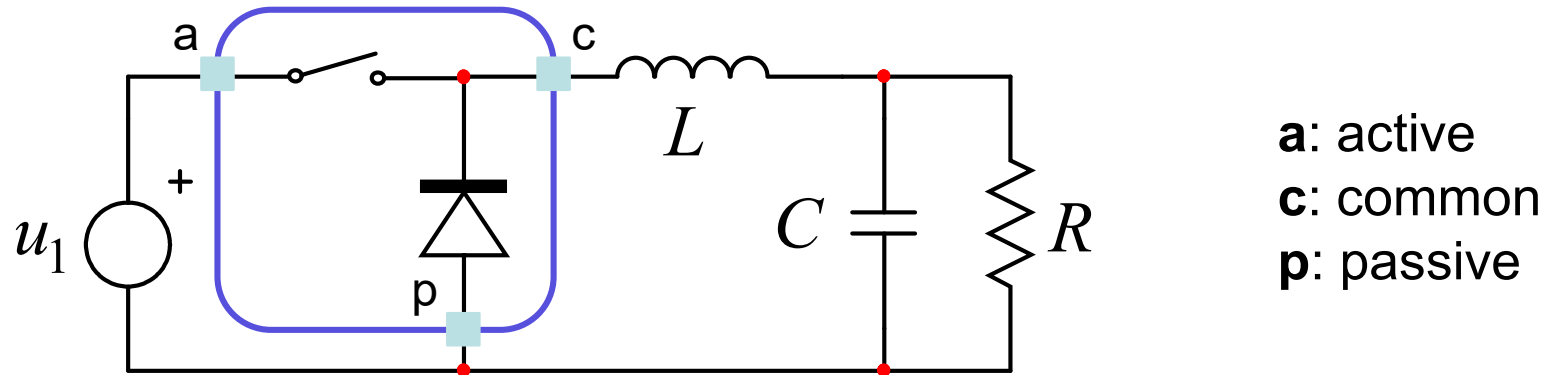- We know that non-linearity is brought by the switching cell




- Why don't we linearize the cell alone?

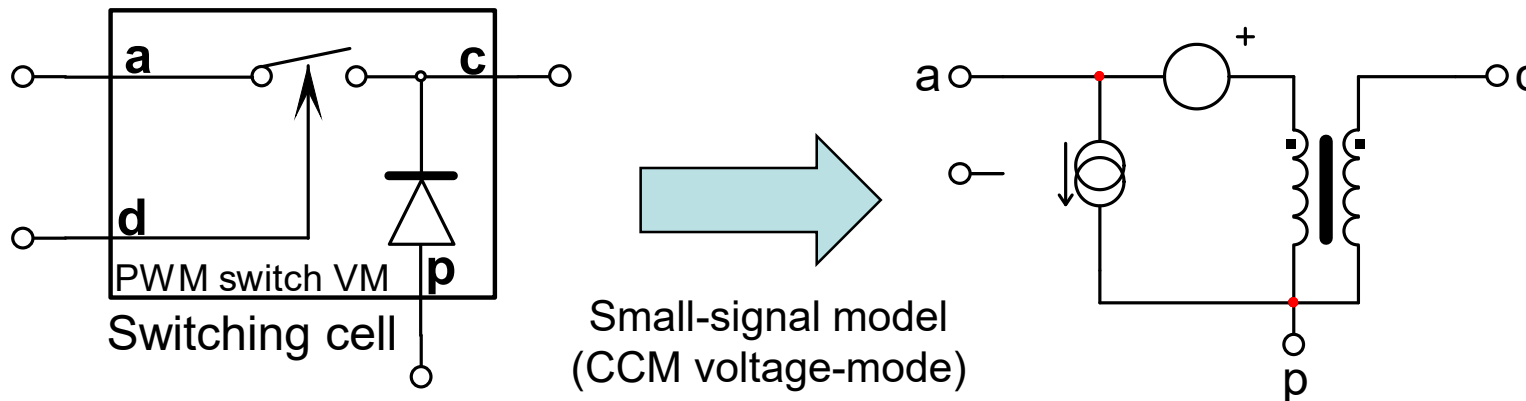

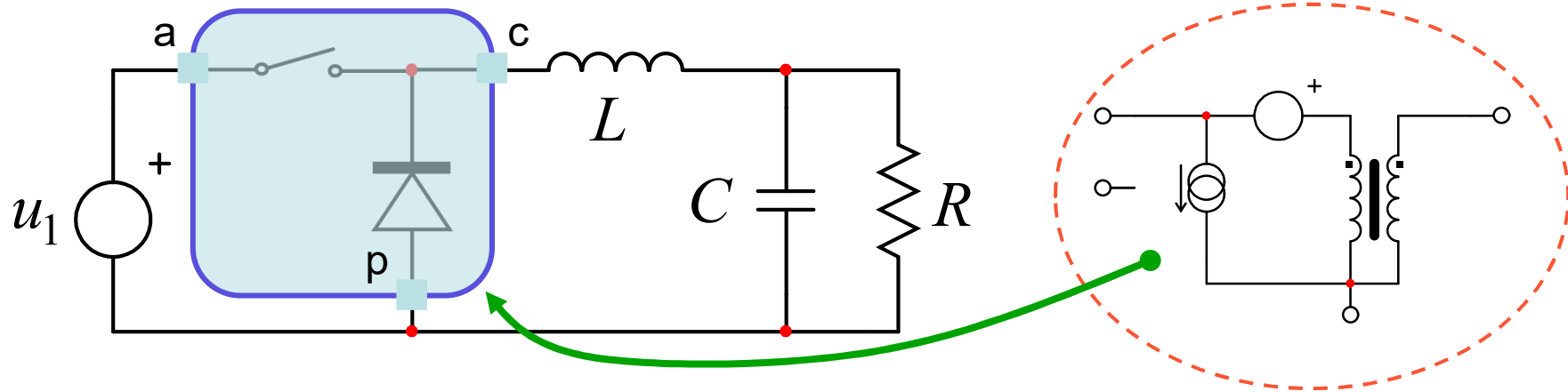
V. Vorperian, "Simplified Analysis of PWM Converters using Model of PWM Switch, parts I and II" IEEE Transactions on Aerospace and Electronic Systems, Vol. 26, NO. 3, 1990

Replace the Switches by the Model

- Like in the bipolar circuit, replace the switching cell...




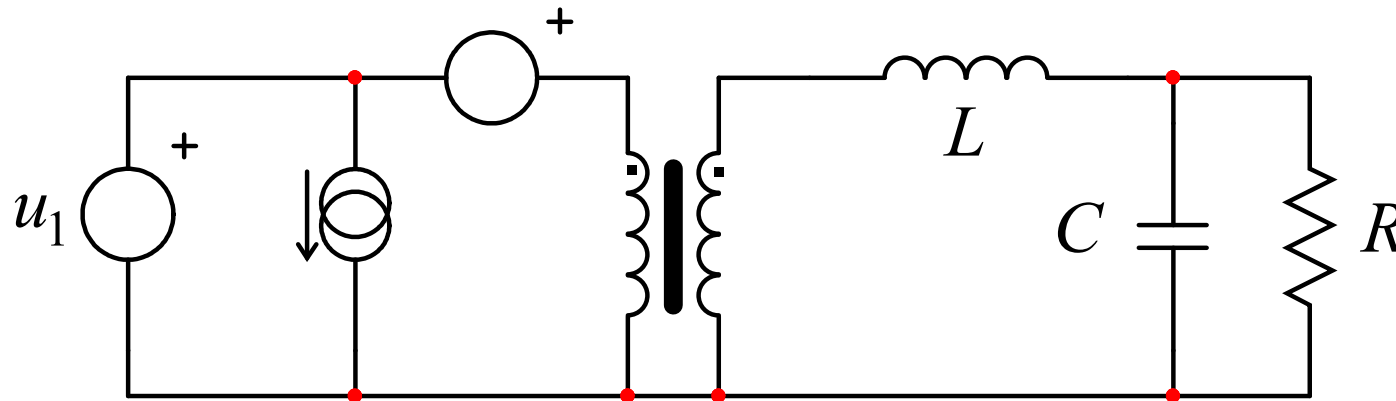- ...and solve a set of linear equations!




An Invariant Model

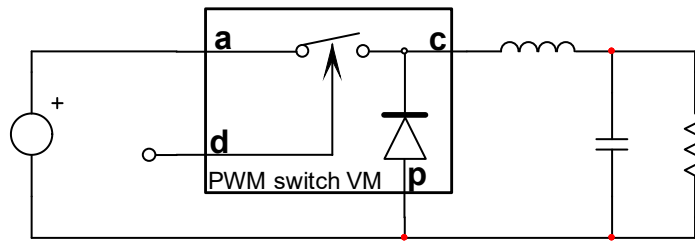
- The switching cell made of two switches is everywhere!




buck

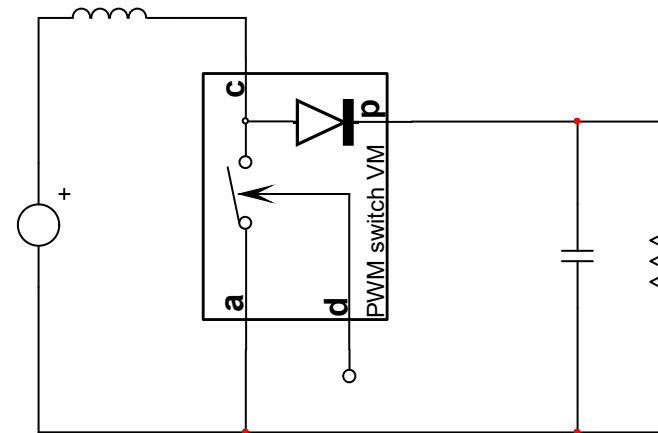

boost

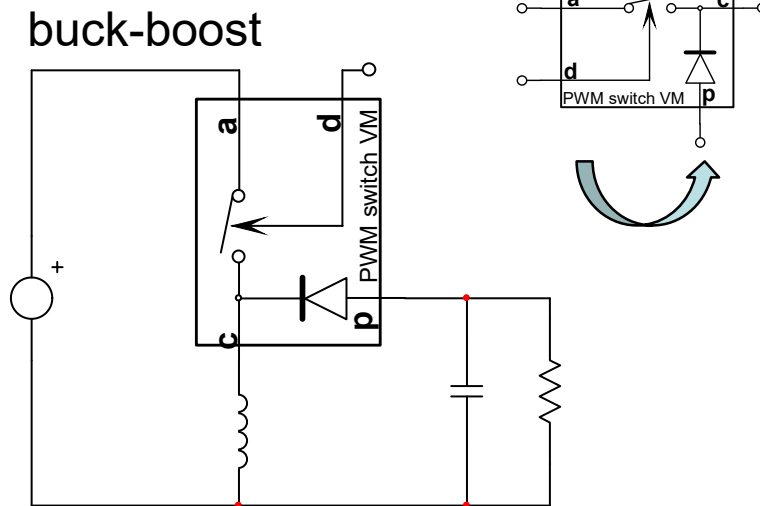

buck-boost

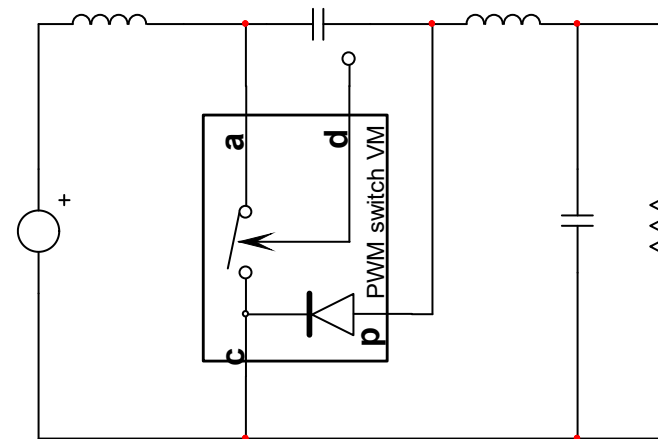


Ćuk



Smoothing the Discontinuity

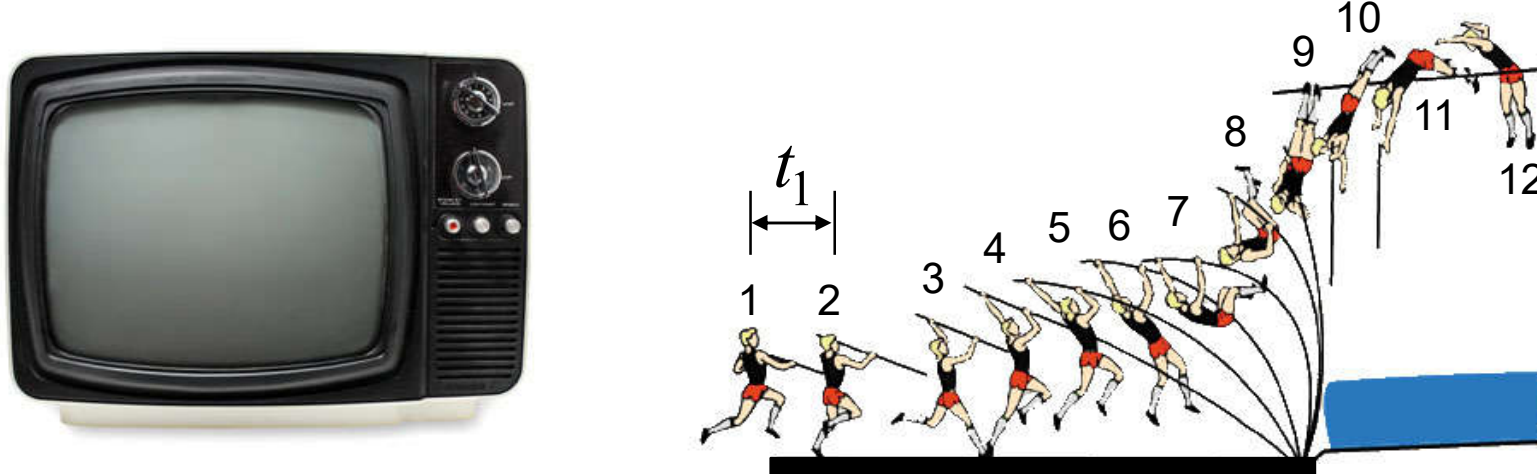- A CRT TV displays frames at a certain rate, 50 per second



- The optic nerve time constant is larger than an interval
- A succession of discrete events is seen as continuous


Low-frequency filtering
Integration



See "phi phenomena", www.wikipedia.org

Averaging Waveforms

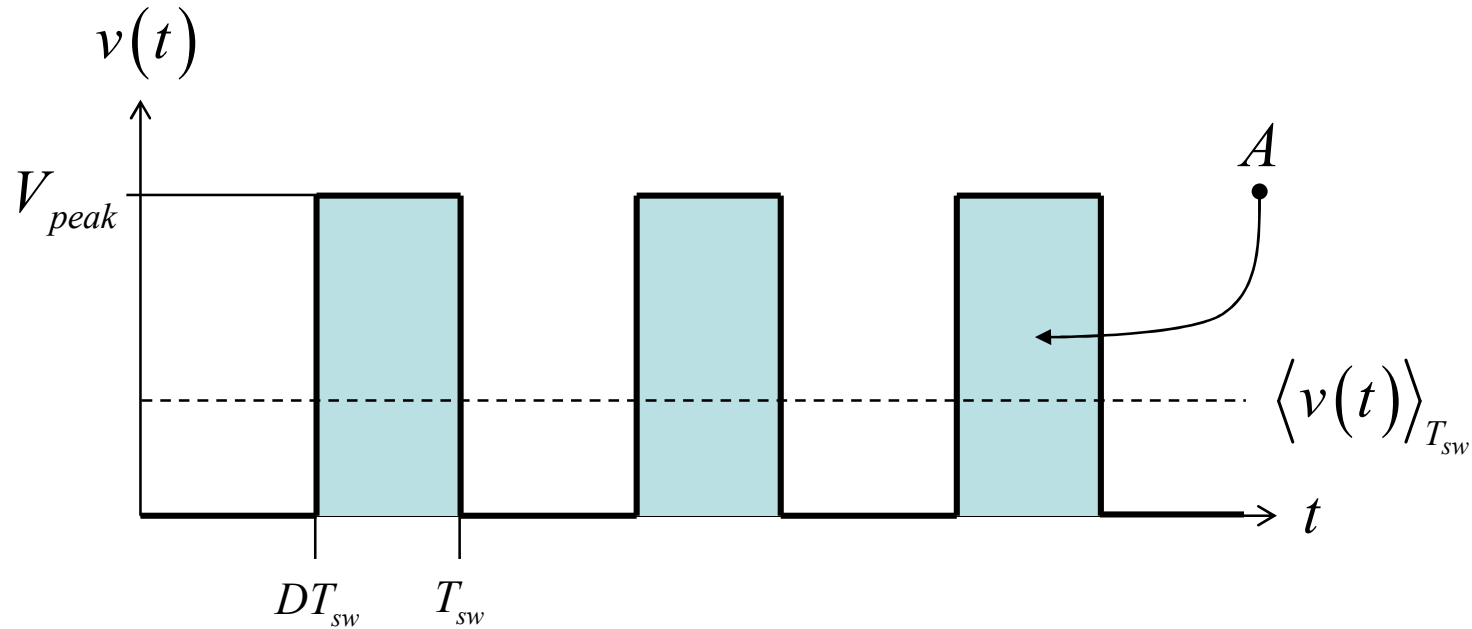- The keyword in the PWM switch is *averaging*




$$\langle v(t) \rangle_{T_{sw}} = \frac{1}{T_{sw}} \int_0^{T_{sw}} v(t) \cdot dt = \frac{1}{T_{sw}} \int_{DT_{sw}}^{T_{sw}} V_{peak} \cdot dt = V_{peak} (1 - D) = V_{peak} D'$$

- The resulting function is continuous in time

From Steps to a Continuous Function

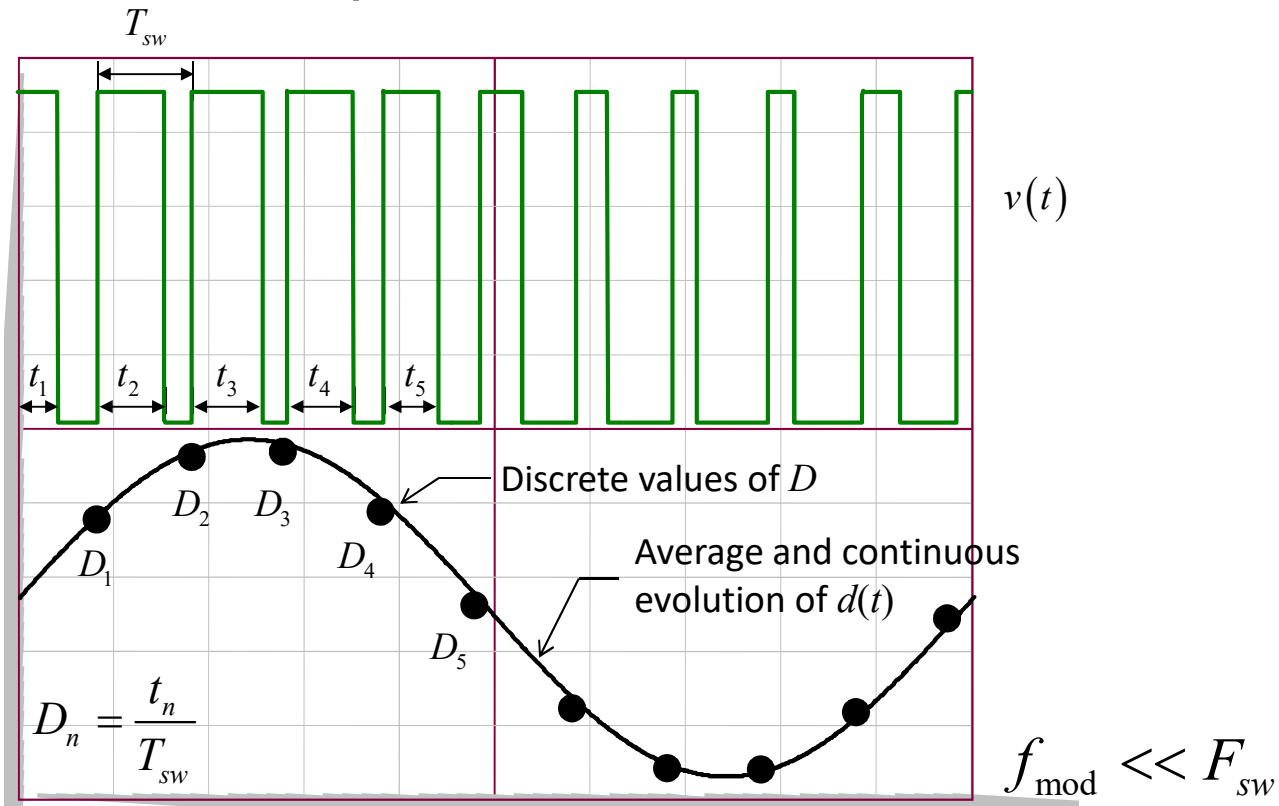
- ❑ Some functions require mathematical abstraction: duty ratio




- ❑ At the modulation frequency scale, points look contiguous
- ❑ Link them through a continuous-time ripple-free function $d(t)$

The Common Passive Configuration

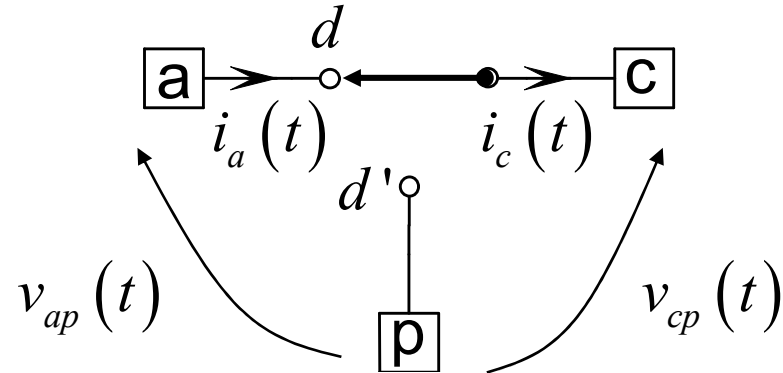- The PWM switch is a single-pole double-throw model




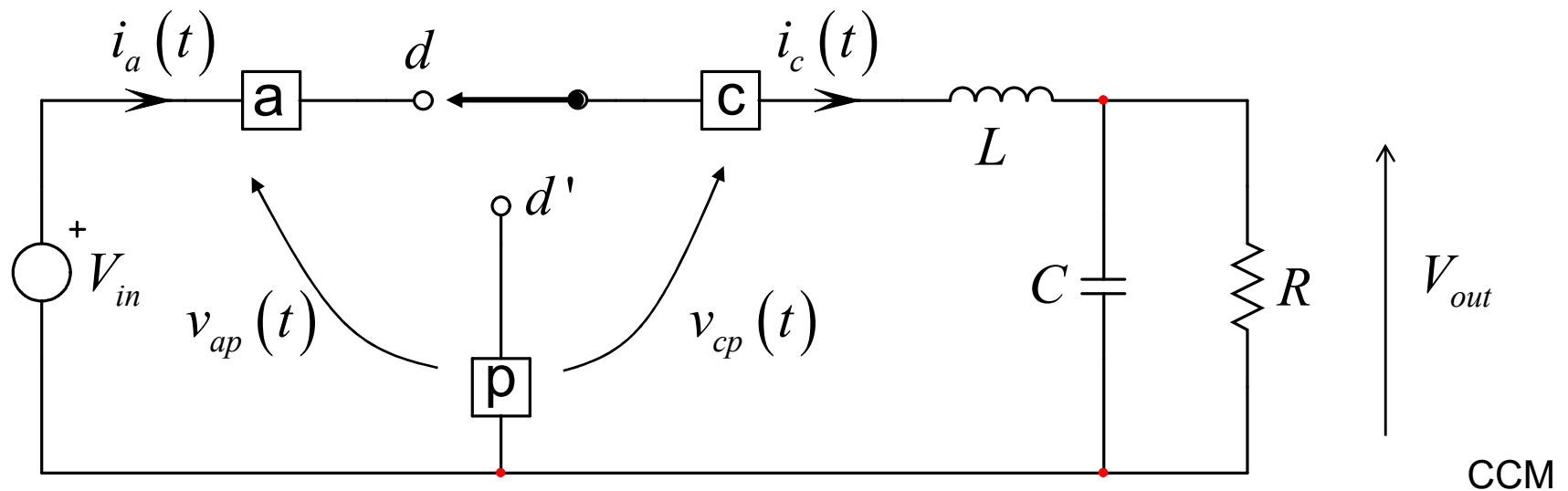- Install it in a buck converter and draw the waveforms



The Common Passive Configuration

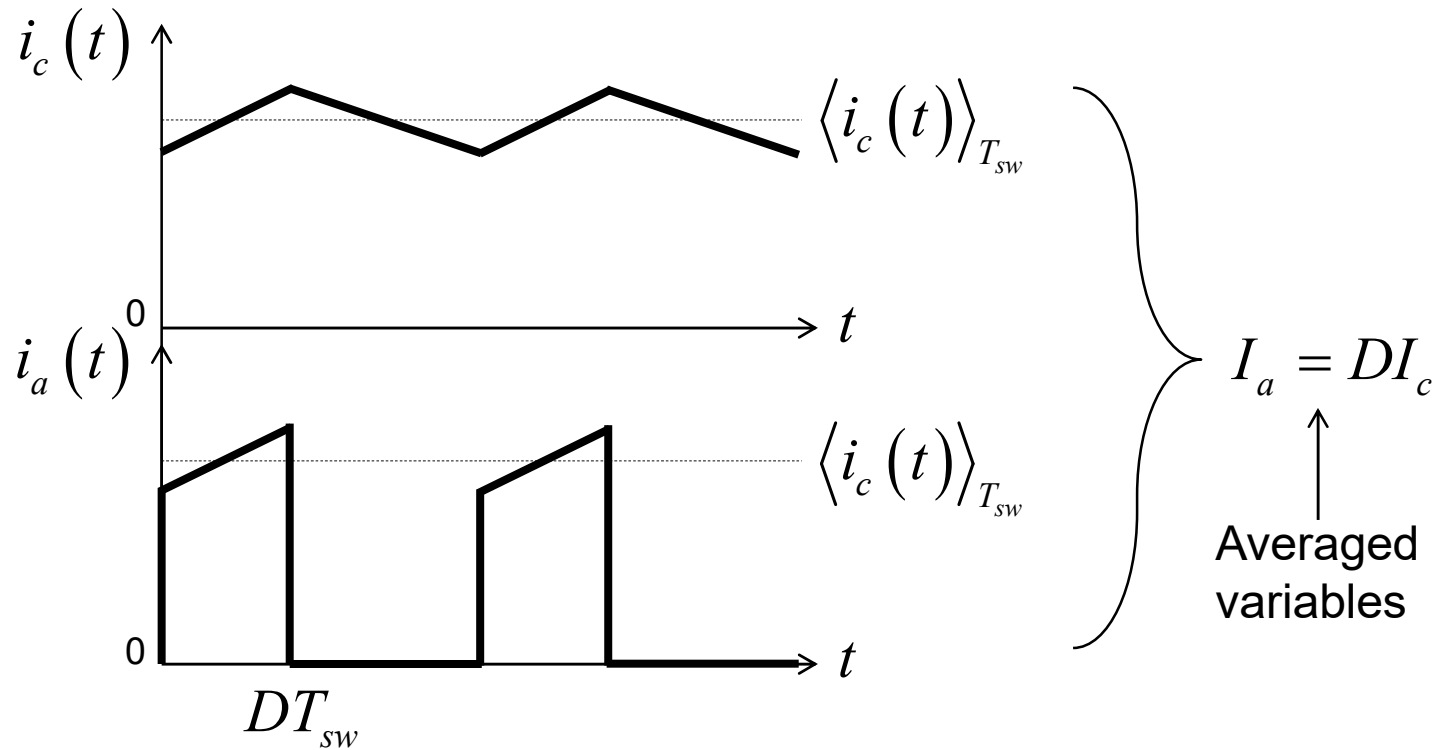- Average the current waveforms across the PWM switch




$$\langle i_a(t) \rangle_{T_{sw}} = I_a = \frac{1}{T_{sw}} \int_0^{dT_{sw}} i_a(t) dt = D \langle i_c(t) \rangle_{T_{sw}} = DI_c$$

CCM



The Common Passive Configuration

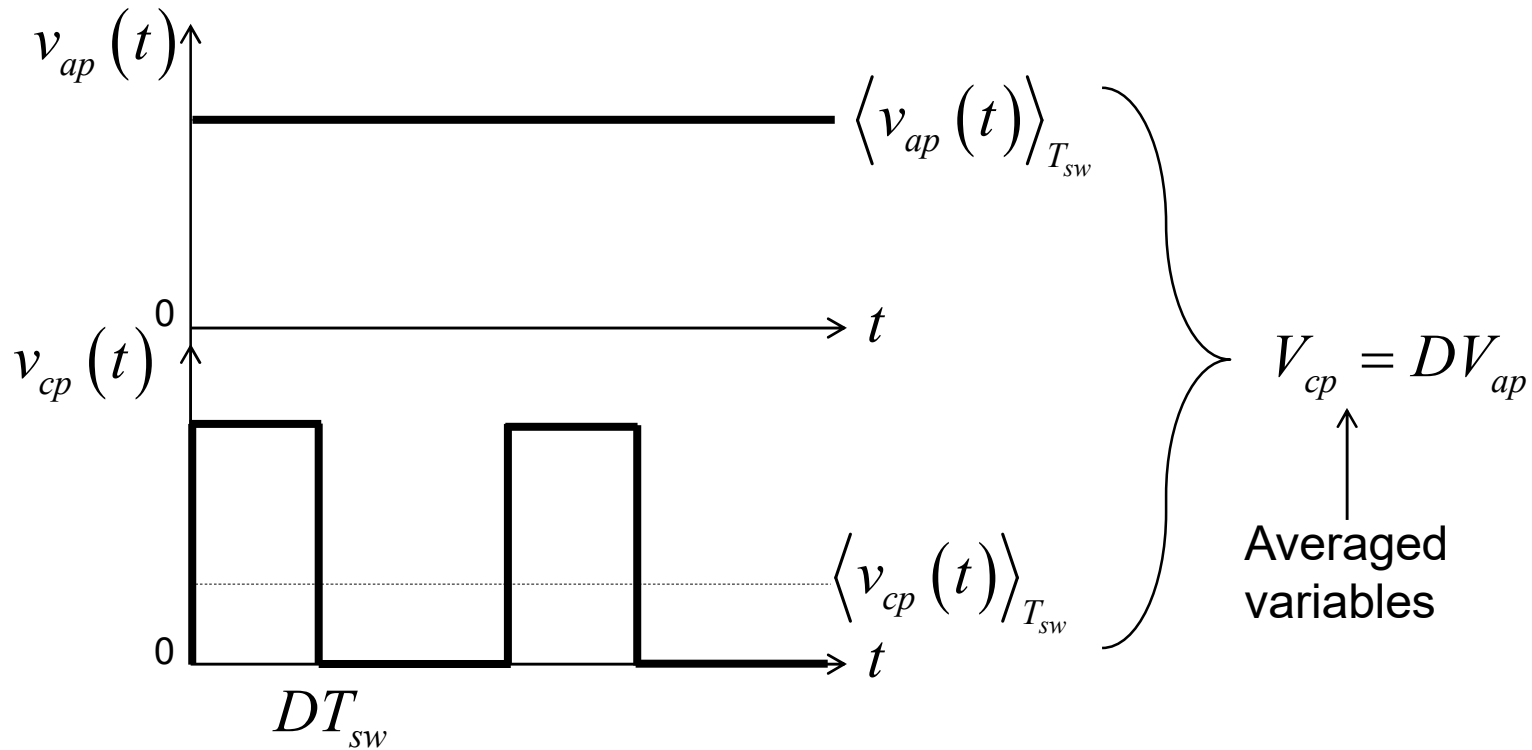- Average the voltage waveforms across the PWM switch




$$\langle v_{cp}(t) \rangle_{T_{sw}} = V_{cp} = \frac{1}{T_{sw}} \int_0^{DT_{sw}} v_{cp}(t) dt = D \langle v_{ap}(t) \rangle_{T_{sw}} = DV_{ap}$$

CCM




A Two-Port Representation

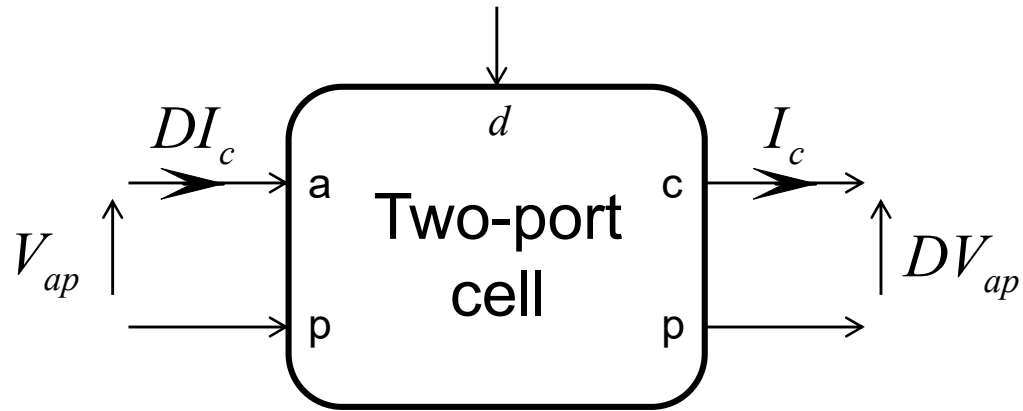- We have a link between input and output variables



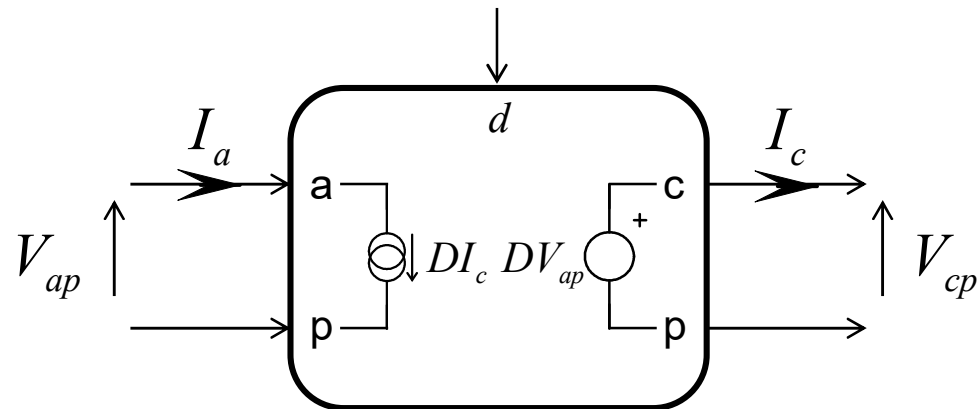- It can further be illustrated with current and voltage sources




CCM




A Transformer Representation

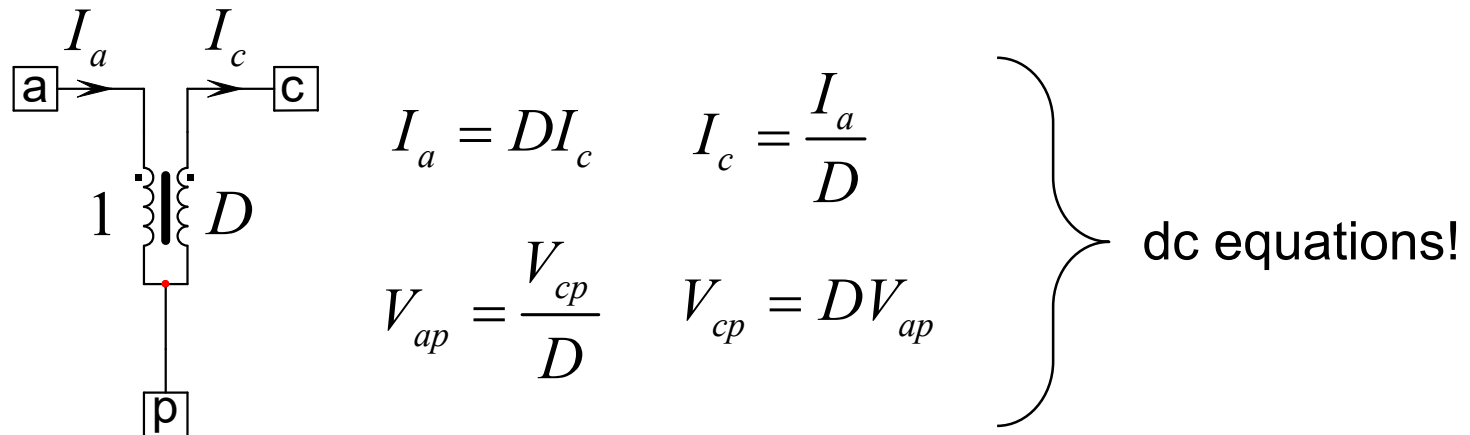- The PWM switch large-signal model is a dc "transformer"!



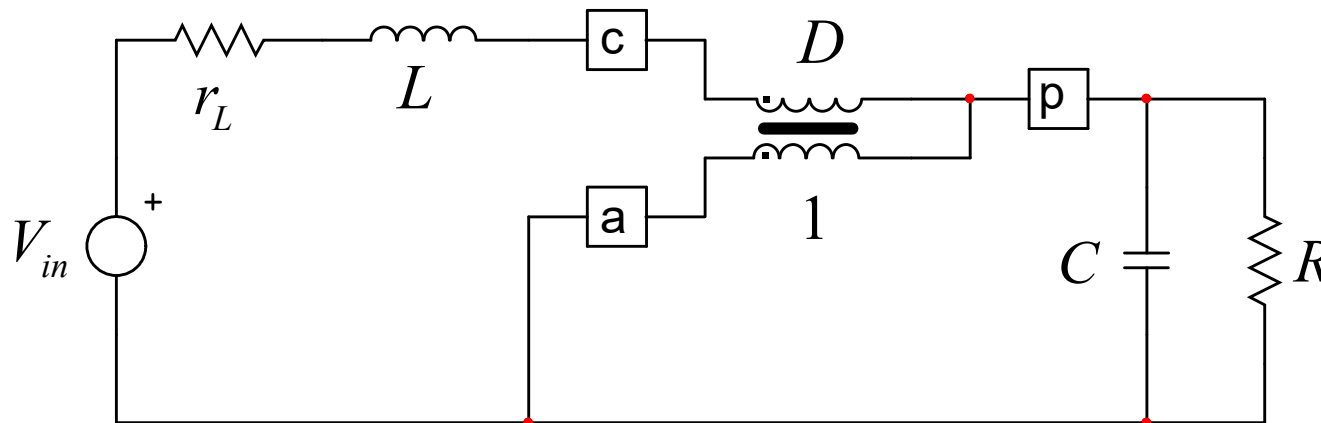- It can be immediately plugged into any 2-switch converter




CCM




Simulate Immediately with this Model

- SPICE can get you the dc bias point

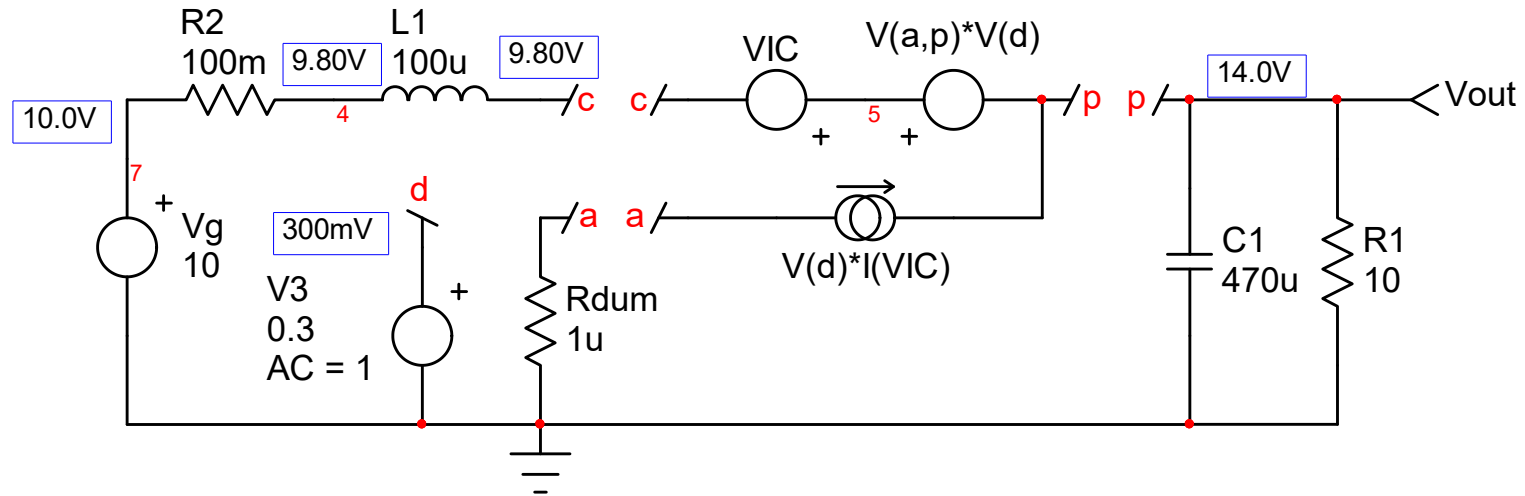

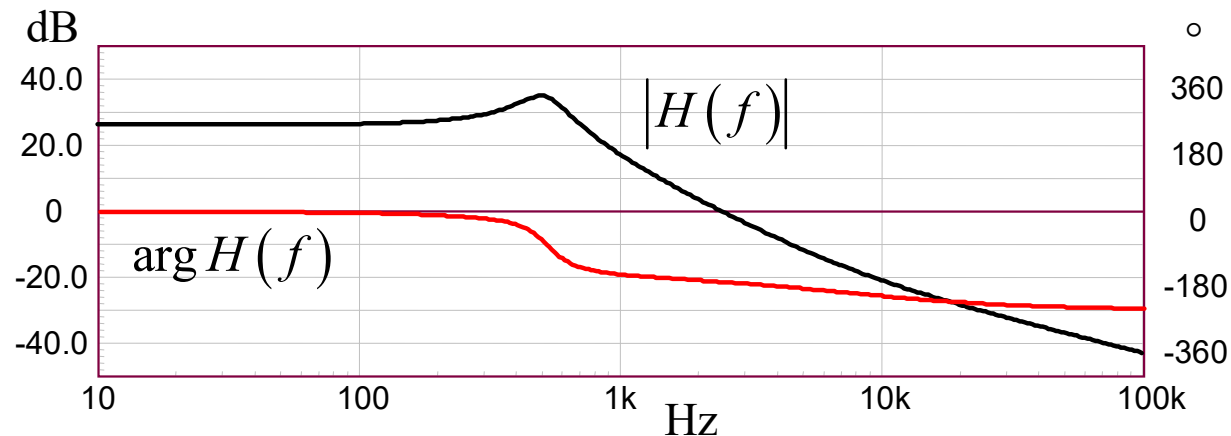- ...but also the ac response as it linearizes the circuit




CCM



We Want Transfer Functions

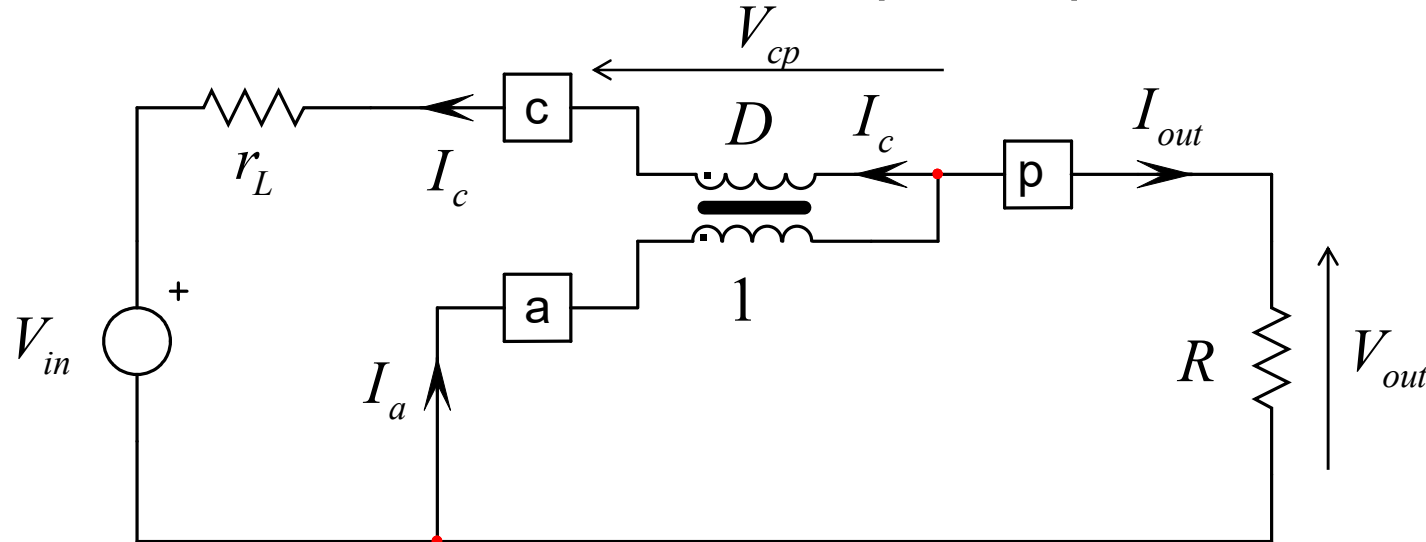- Derive the dc transfer function: open caps., short inductors



$$V_{out} = I_{out} R$$

$$V_{out} = (I_a - I_c) R$$

$$I_a = DI_c$$

$$V_{out} = I_c (D-1) R$$

$$V_{in} + r_L I_c - V_{cp} = V_{out}$$

$$V_{in} + r_L I_c + DV_{out} = V_{out}$$

$$I_c = \frac{V_{out} (1-D) - V_{in}}{r_L}$$


$$\frac{V_{out}}{V_{in}} = \frac{1}{(1-D) - \frac{r_L}{(D-1)R}}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{D'} \frac{1}{1 + \frac{r_L}{RD'^2}}$$

CCM

Plotting Transfer Functions

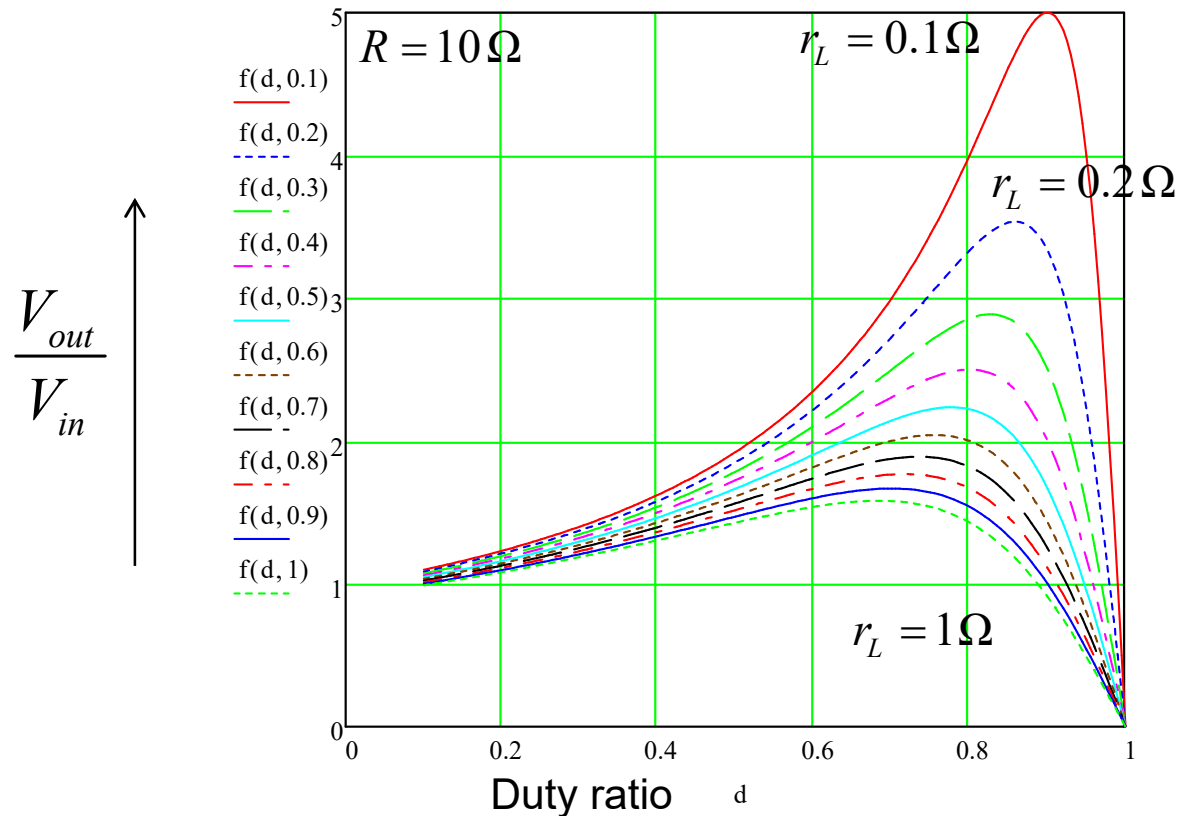- Plot the lossy boost transfer function in a snapshot



- Above a certain conversion ratio, latch-up occurs

CCM


Course Agenda

- The PWW Switch Concept
- Small-Signal Analysis in Continuous Conduction Mode**
- Small-Signal Response in Discontinuous Mode
- EMI Filter Output Impedance
- Cascaded Converters Operation



A Boost Converter in Current Mode

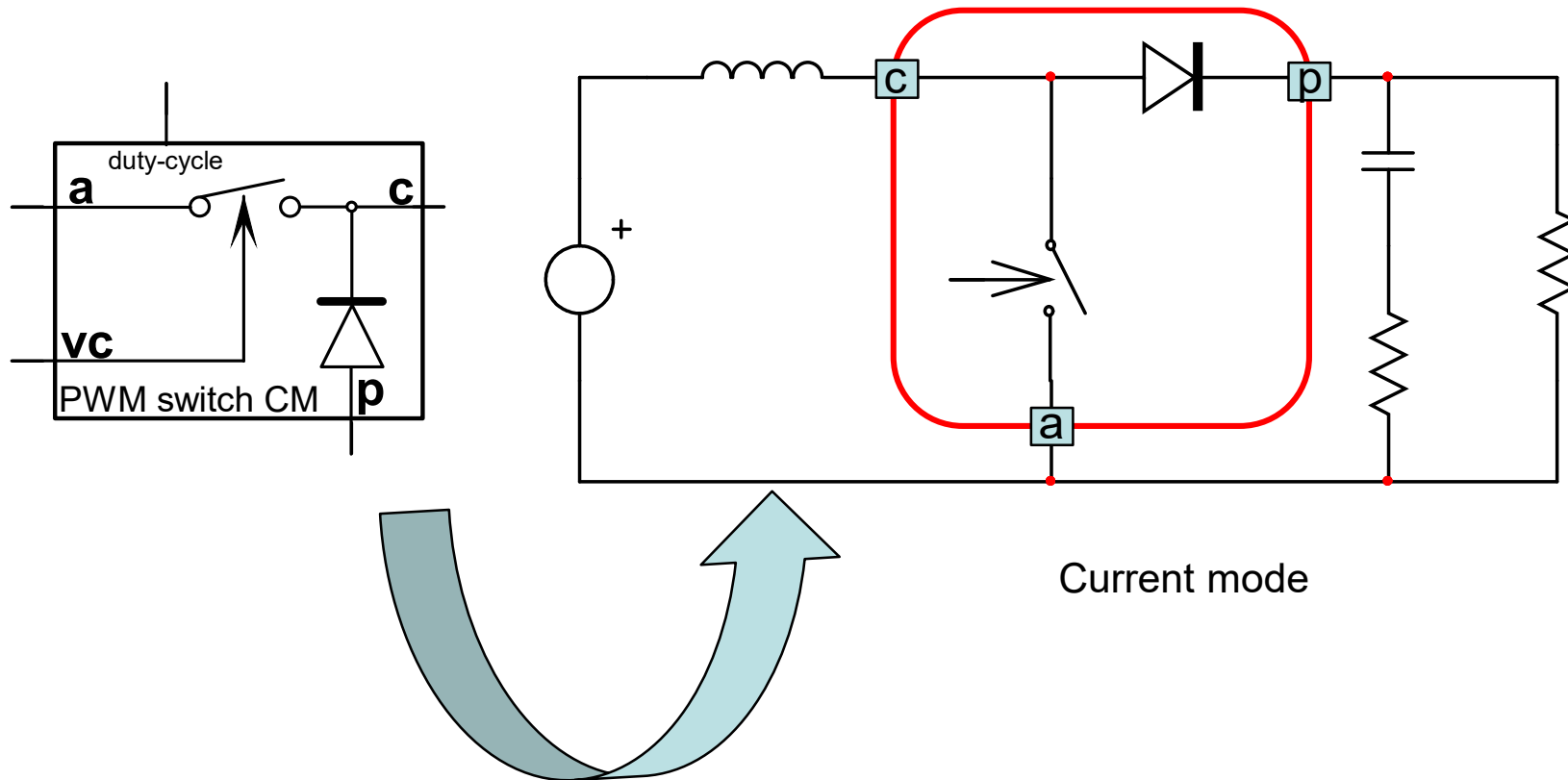
- Identify the diode and switch position in a boost CM



- Replace switches by the small-signal PWM switch model

A Small Signal Model

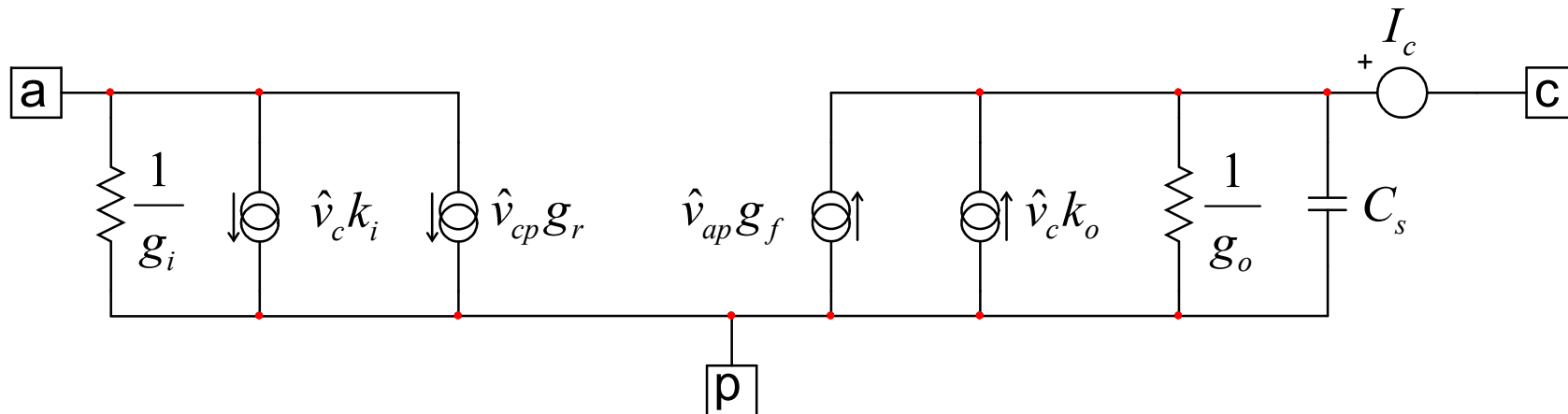- The model includes current sources and conductances



$$k_o = \frac{1}{R_i} \quad g_f = Dg_o - \frac{DD'T_{sw}}{2L} \quad g_o = -\frac{T_{sw}}{L} \left(D' \frac{S_a}{S_n} + \frac{1}{2} - D \right)$$


$$k_i = \frac{D}{R_i} \quad g_i = D \left(g_f - \frac{I_c}{V_{ap}} \right) \quad g_r = \frac{I_c}{V_{ap}} - g_o D$$

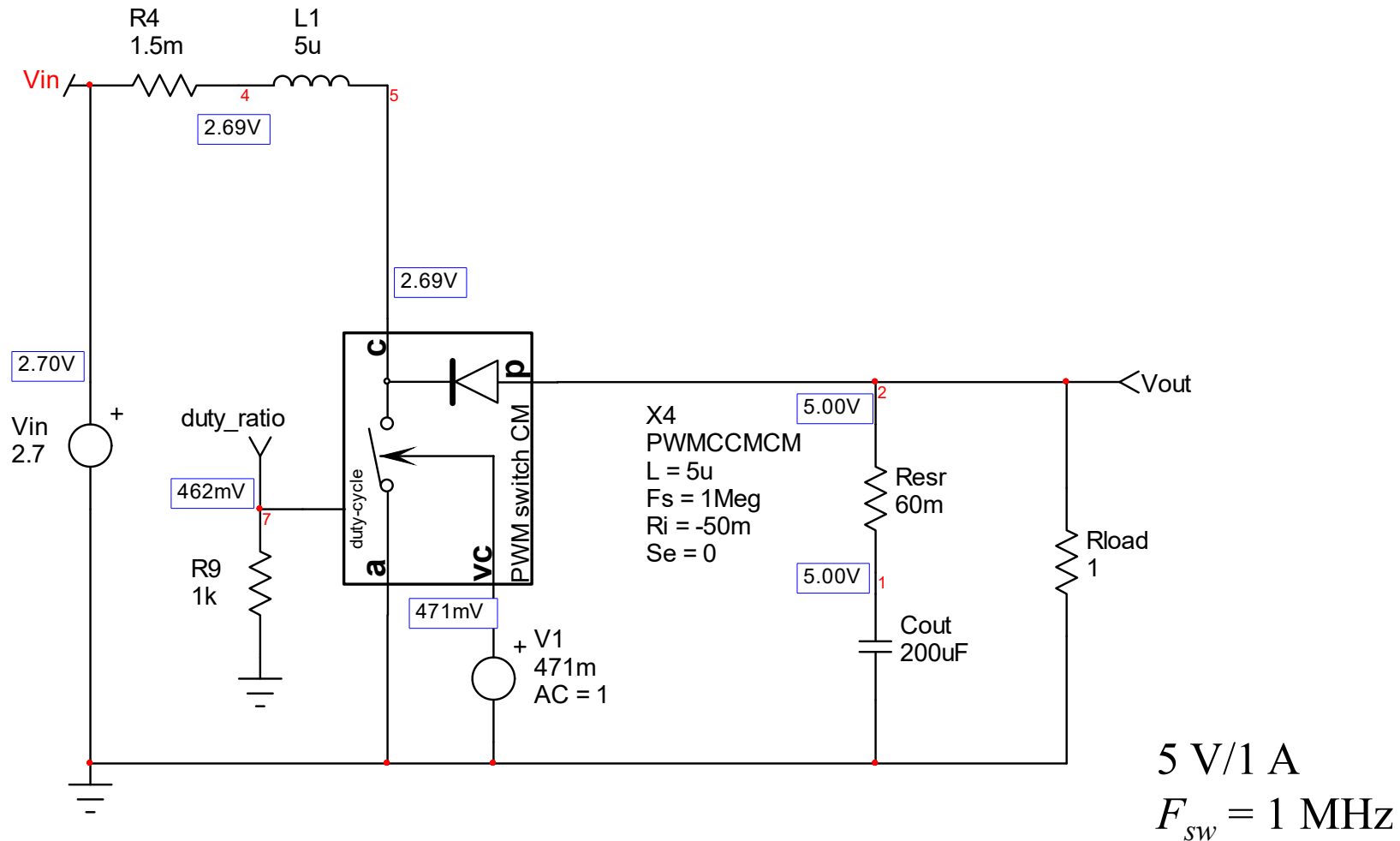V. Vorpérian, "Analysis of Current-Controlled PWM Converters using the Model of the PWM Switch", PCIM Conference, 1990




Start with a Large Signal Response

- Use the original large-signal (nonlinear) PWMCM model





Frequency Response of the CM Boost

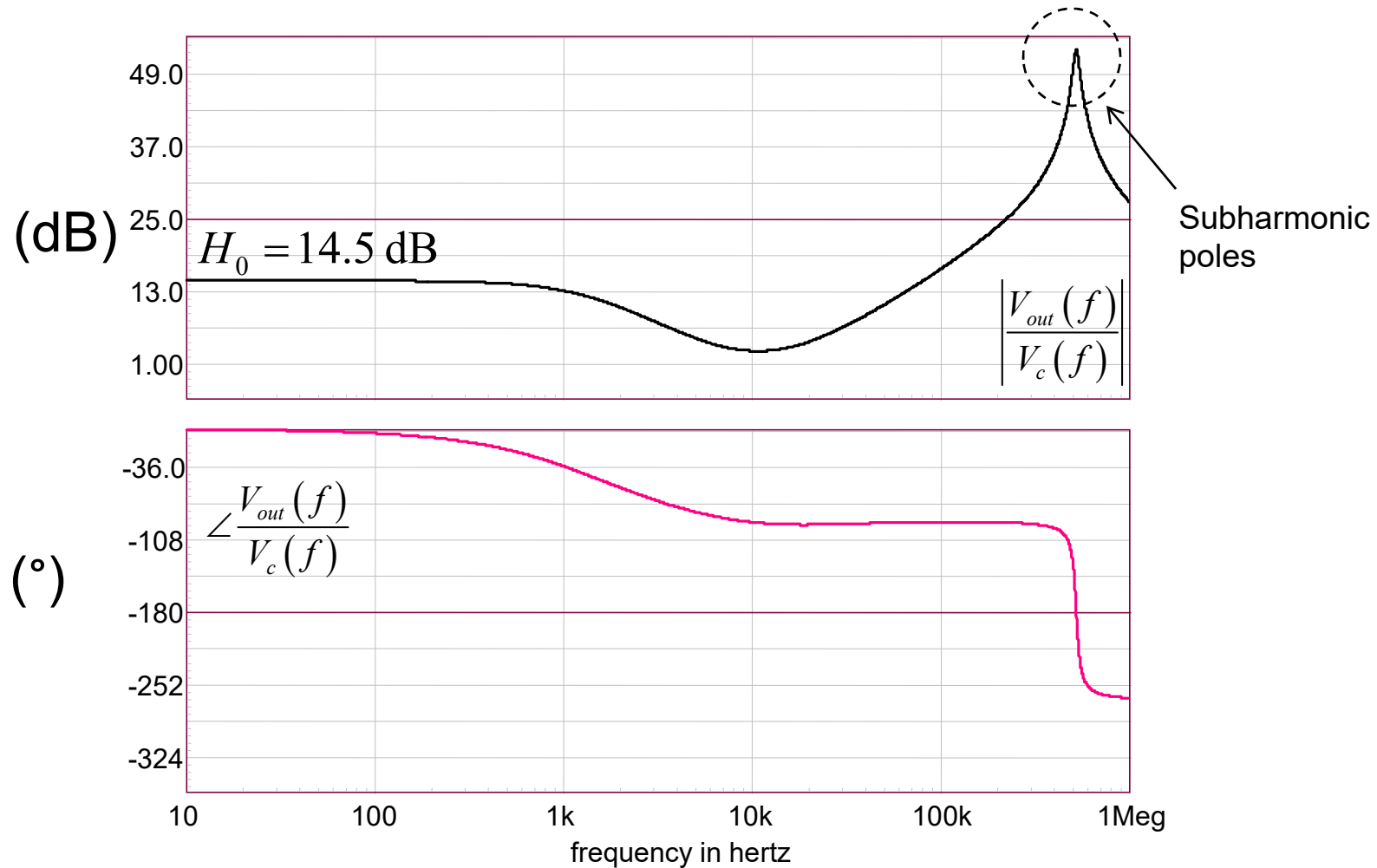- This frequency response becomes the reference



Plug the Linearized Small-Signal Model

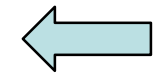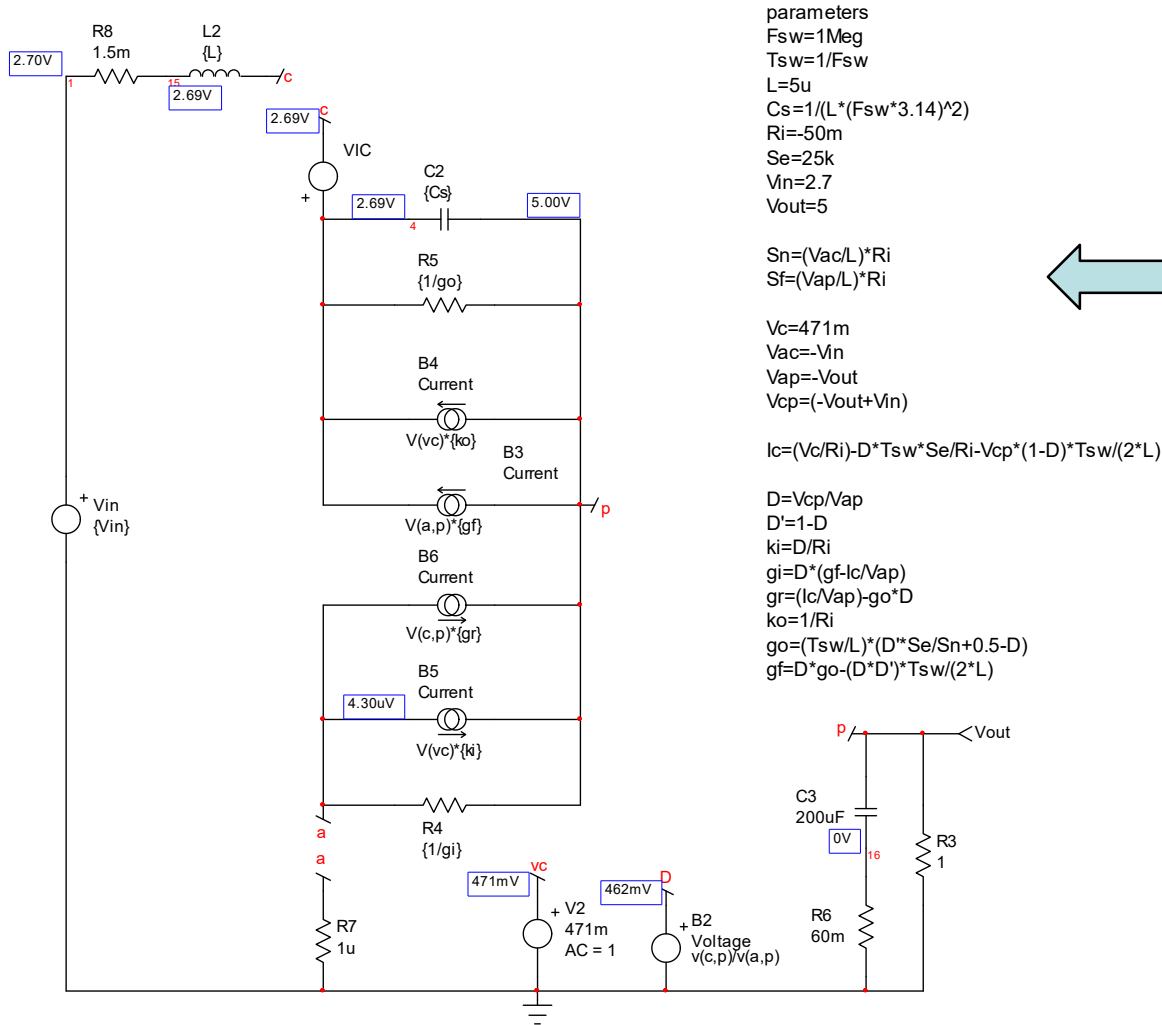- Use the linearized model to check coefficients and response




These coefficients are computed by the macro



Small-Signal Response and Original Model

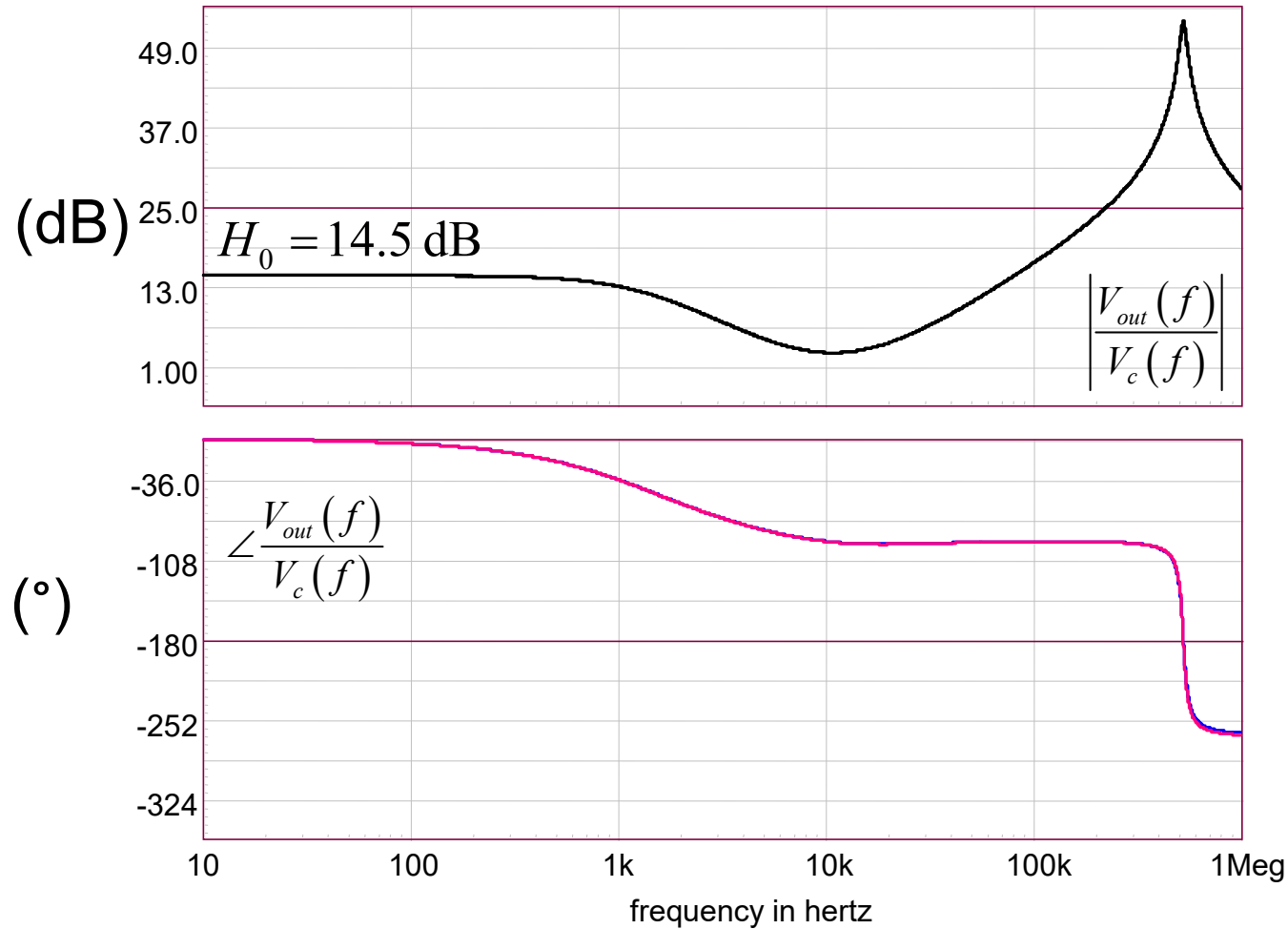- Validate the small-signal approach by comparing responses




Good to go!



Rearrange Sources to Improve Readability

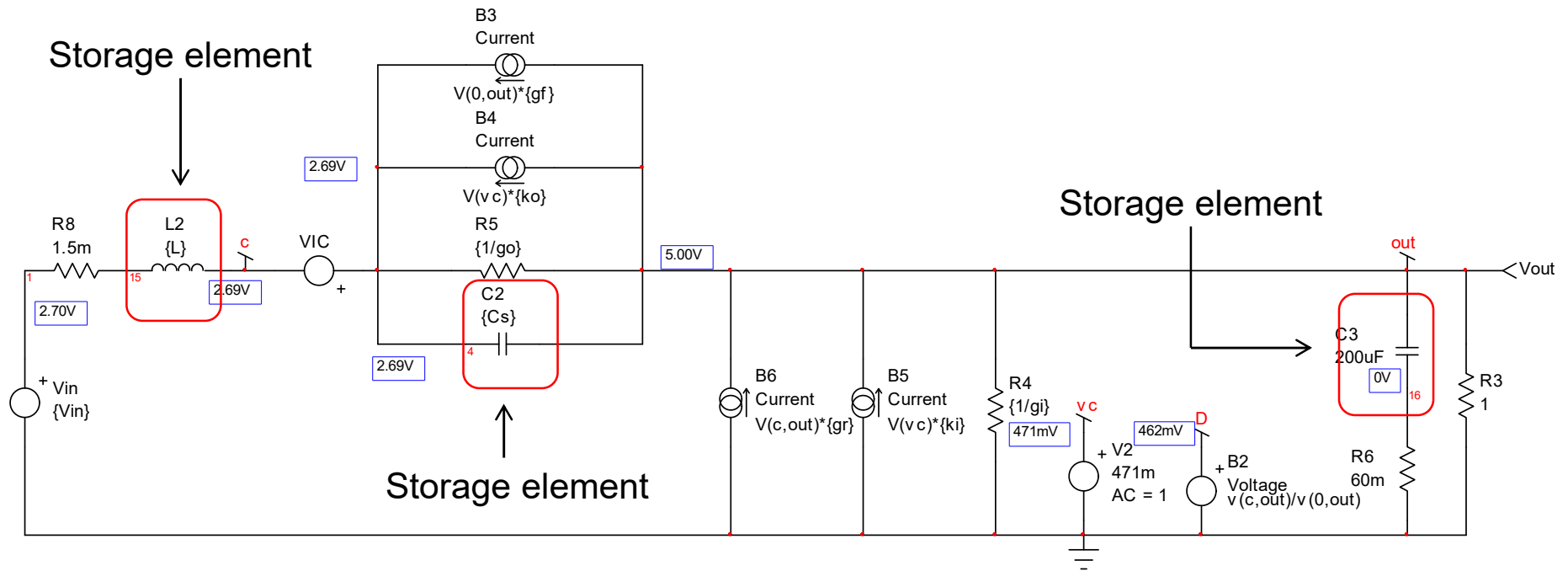- It is important to lay the network out properly



- Make sure the frequency response remains unchanged

What is the Converter Order?

- Count storage elements: L and two C
- The denominator of the transfer function is of 3rd order

$$H(s) = H_0 \frac{\left(1 + \frac{s}{s_{z_1}}\right) \left(1 + \frac{s}{s_{z_2}}\right)}{\left(1 + \frac{s}{s_{p_1}}\right) \left(1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2\right)}$$

Dc gain
Zeros

↓
←

H_0
1

s_{z_1}
 s_{z_2}

s_{p_1}
 $\omega_0 Q$
 ω_0

↑

Subharmonic poles



Start with the Static Analysis

□ For $s = 0$, short inductors and open capacitors


parameters
 $F_{sw}=1\text{Meg}$
 $T_{sw}=1/F_{sw}$
 $L=5\mu$
 $C_s=1/(L*(F_{sw}*3.14)^2)$
 $R_i=-50\text{m}$
 $S_e=0$
 $V_{in}=2.7$
 $V_{out}=5$

$S_n=(V_{ac}/L)*R_i$
 $S_f=(V_{ap}/L)*R_i$

$V_c=471\text{m}$
 $V_{ac}=-V_{in}$
 $V_{ap}=-V_{out}$
 $V_{cp}=(-V_{out}+V_{in})$


$I_c=(V_c/R_i)-D*T_{sw}*S_e-V_{cp}*(1-D)*T_{sw}/(2*L)$

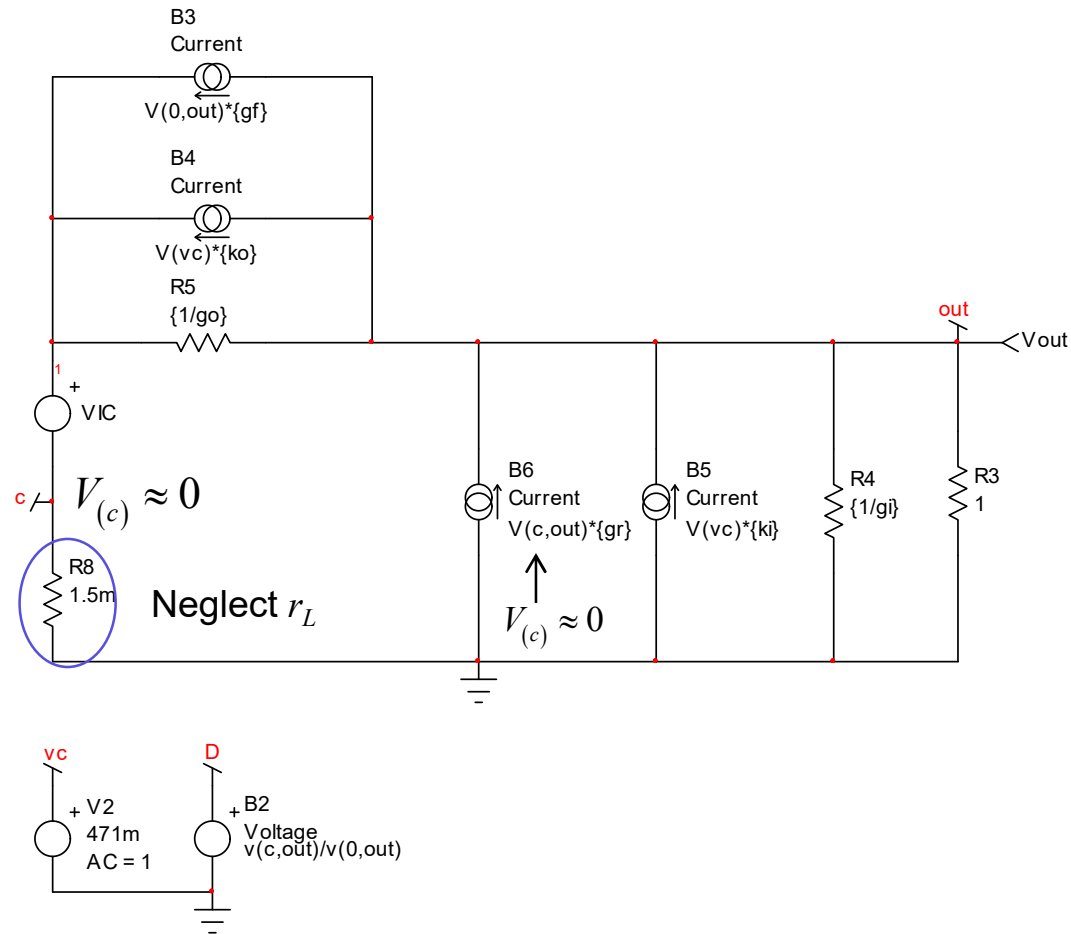$D=V_{cp}/V_{ap}$
 $D'=1-D$
 $k_i=D/R_i$
 $g_i=D*(g_f-I_c/V_{ap})$
 $g_r=(I_c/V_{ap})-g_o*D$
 $k_o=1/R_i$
 $g_o=(T_{sw}/L)*(D'*S_e/S_n+0.5-D)$
 $g_f=D*g_o-(D*D')*T_{sw}/(2*L)$




Simplify and Rearrange

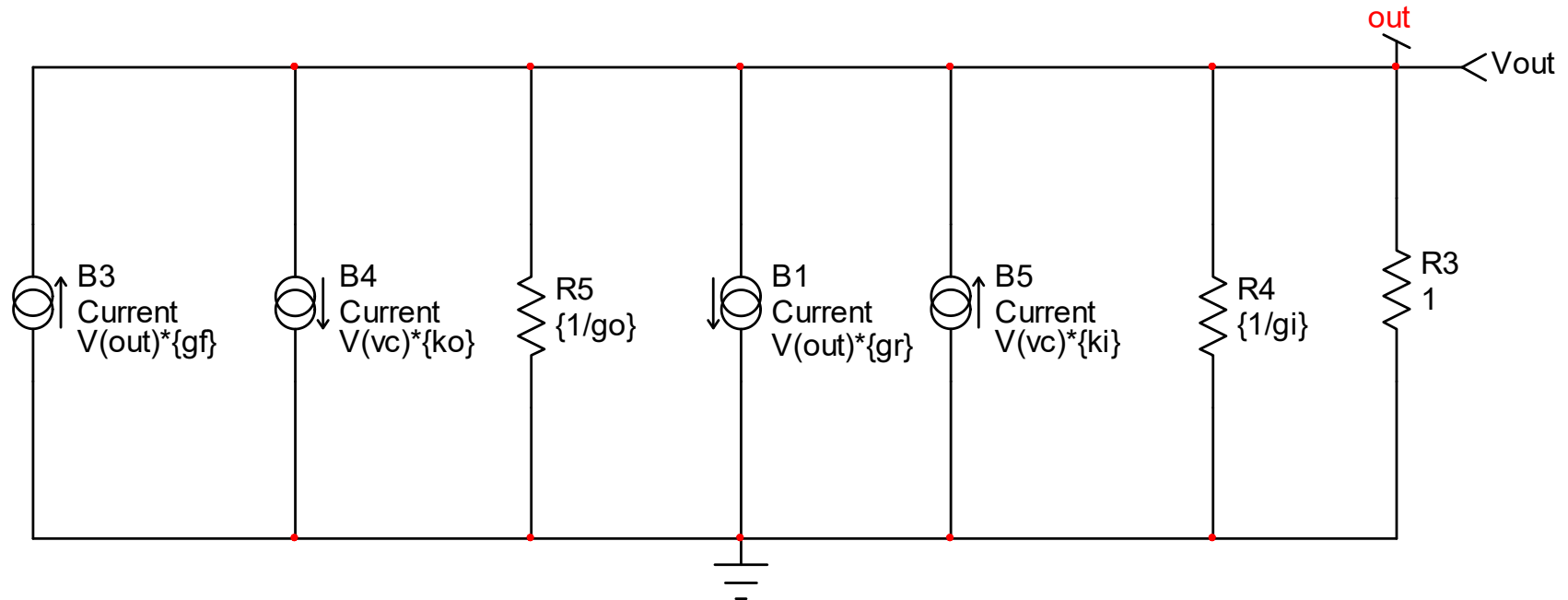- Rearrange sources to make the circuit look simpler


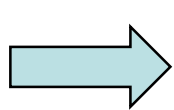
$$V_{out} g_f - V_c k_o - V_{out} (g_o + g_i) - V_{out} g_r + V_c k_i = \frac{V_{out}}{R_1}$$



$$H_0 = \frac{k_o - k_i}{g_f - (g_o + g_i) - g_r - \frac{1}{R_1}}$$


Mathcad® calculations

$$H_0 := 20 \cdot \log \left[\frac{k_o - k_i}{g_f - (g_o + g_i) - g_r - \frac{1}{R_L}} \right] = 14.563 \text{ dB}$$



Put Storage Elements Back in Place

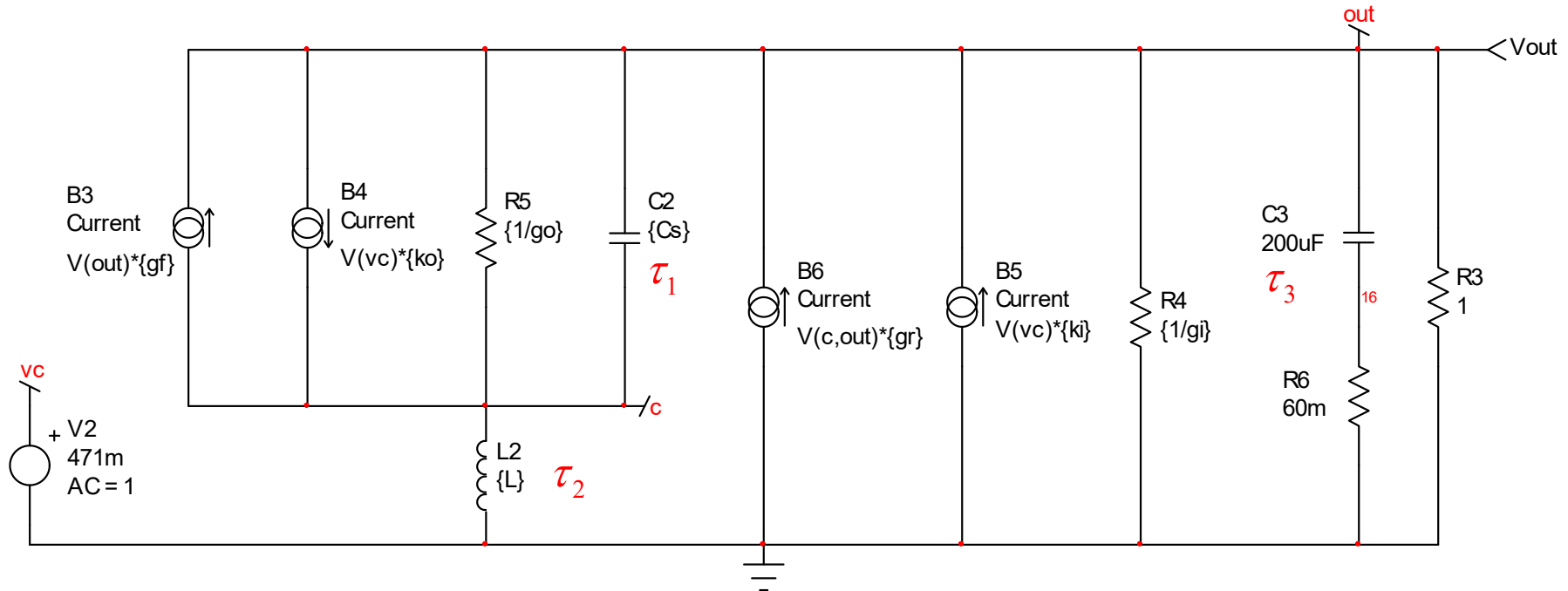- Rearrange sources to make the circuit look simpler



- Label each storage element with a time constant τ
- Time to call the FACTs! Set excitation to 0, $V_c = 0$

FACTS: Fast Analytical Circuit Techniques


Polynomial Form of a 3rd Function

- A transfer function is made of a numerator and a denominator

$$H(s) = \frac{N(s)}{D(s)} \begin{array}{l} \longleftarrow \text{zeros} \\ \longleftarrow \text{poles} \end{array}$$

- The denominator combines the circuit time constants
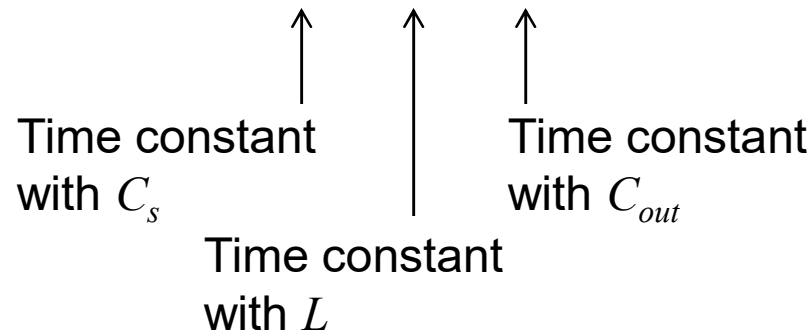
$$D(s) = 1 + (\tau_1 + \tau_2 + \tau_3)s + (\tau_1\tau_2^1 + \tau_1\tau_3^1 + \tau_2\tau_3^2)s^2 + (\tau_1\tau_2^1\tau_3^{12})s^3$$




- To calculate time constants, suppress the excitation, all is dc



Calculate the First Time Constant



- What resistance does C_s « see » ?

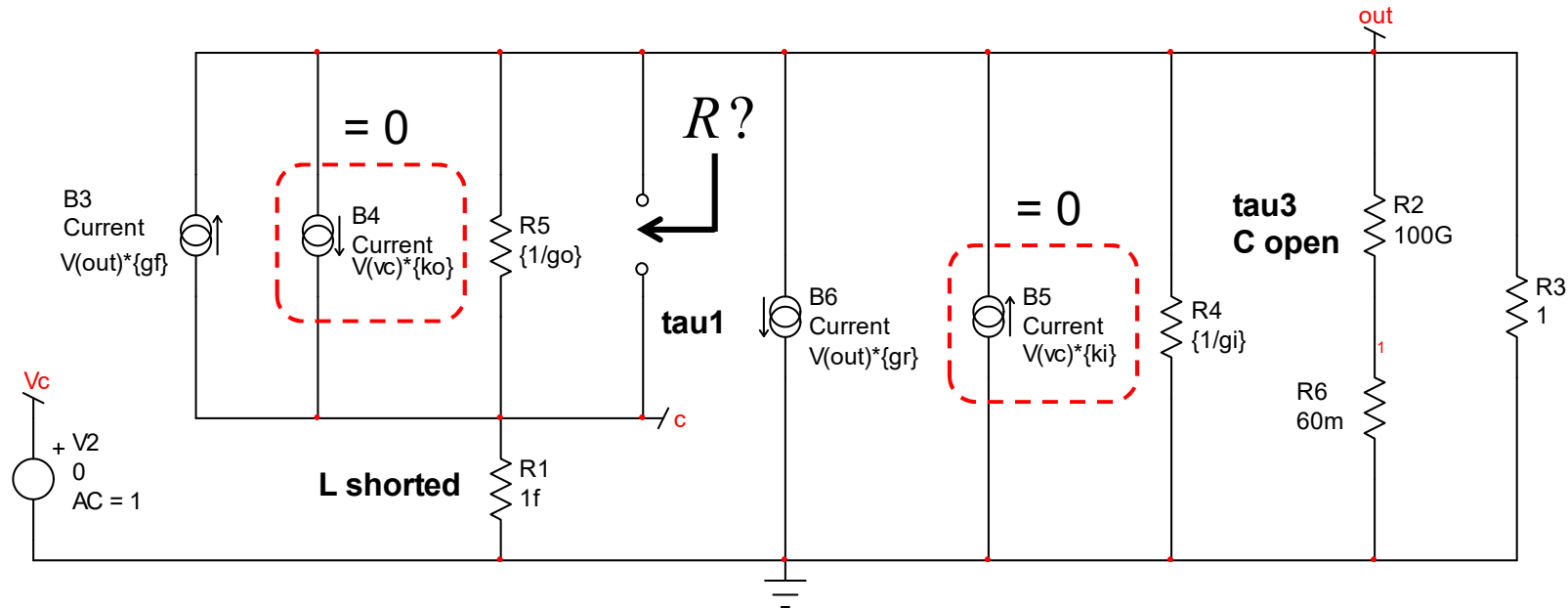

- The excitation is 0 so several sources go away
- You can further simplify the circuit and test it in SPICE

Calculate the First Time Constant

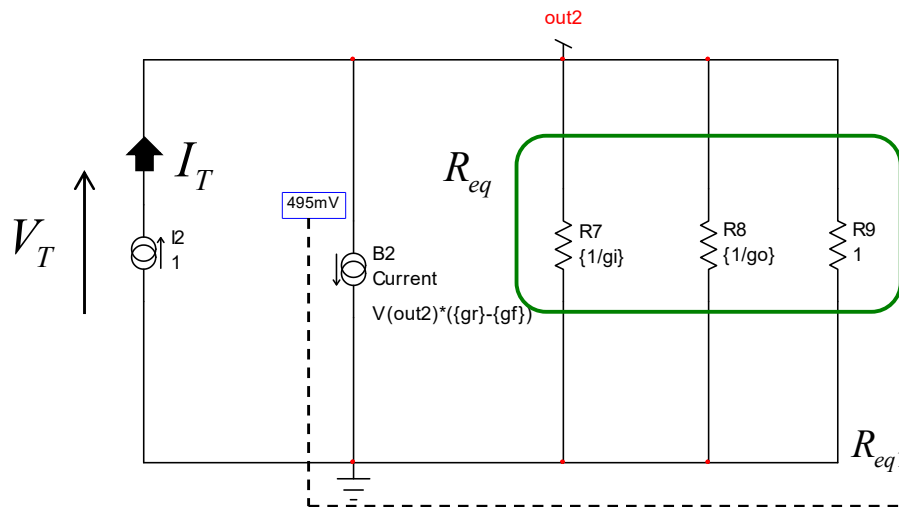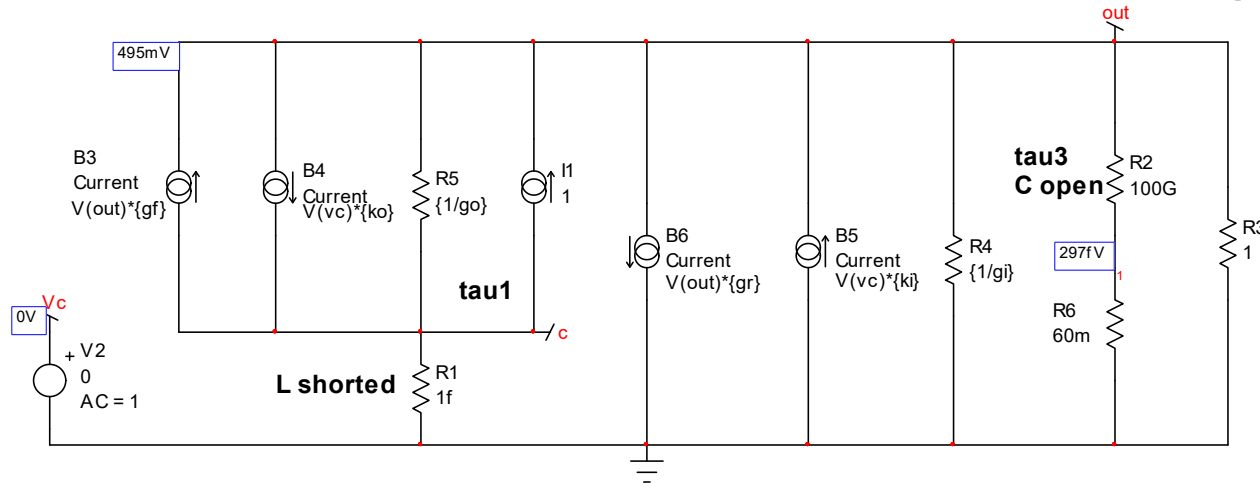□ Check the result with a simple dc operating point calculation



$$I_T = V_{out} (g_r - g_f) + \frac{V_{out}}{R_{eq}}$$

$$R = \frac{V_T}{I_T} = \frac{V_{out}}{I_T} = \frac{1}{g_r - g_f + \frac{1}{R_{eq}}}$$

$$R_{eq1} = R_L \parallel \frac{1}{g_i} \parallel \frac{1}{g_o}$$


$$\frac{1}{\frac{1}{R_{eq}} + g_r - g_f} = 0.495\Omega$$

$$\tau_1 = RC_s$$




Calculate the Second Time Constant

□ What resistance does L « see » ?

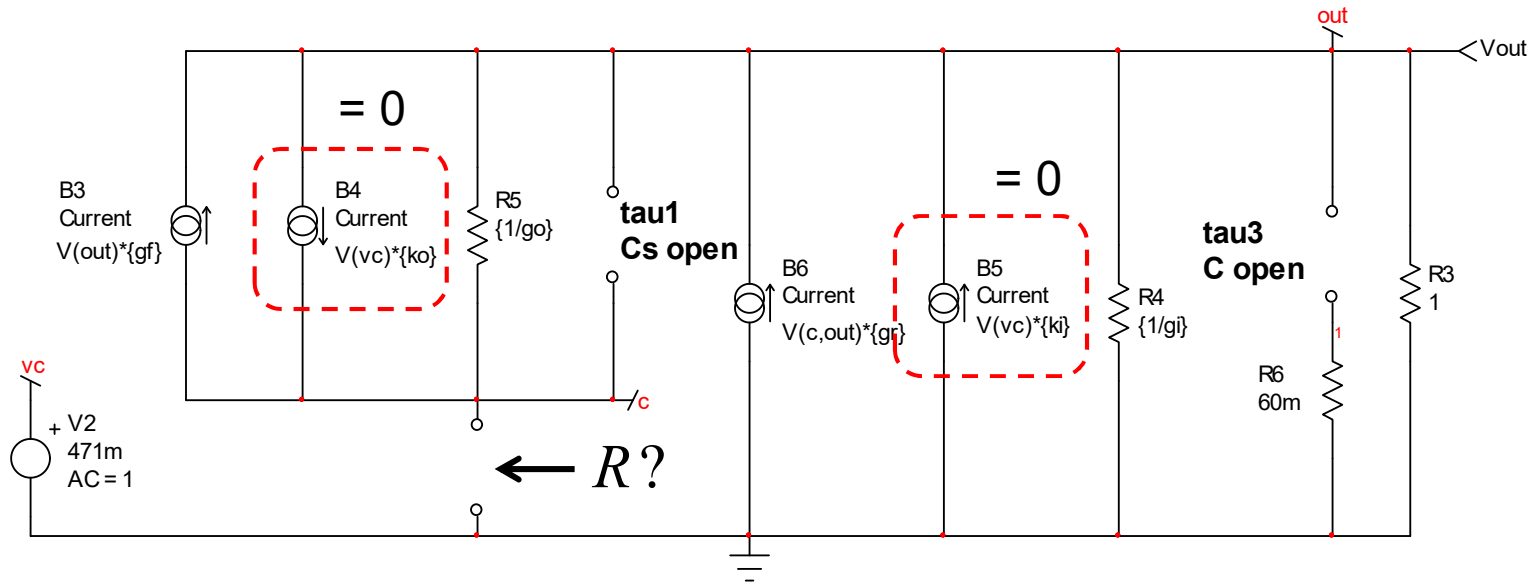

- The excitation V_c is 0 so simplify the circuit
- Rearrange the network and test it in SPICE

Calculate the Second Time Constant

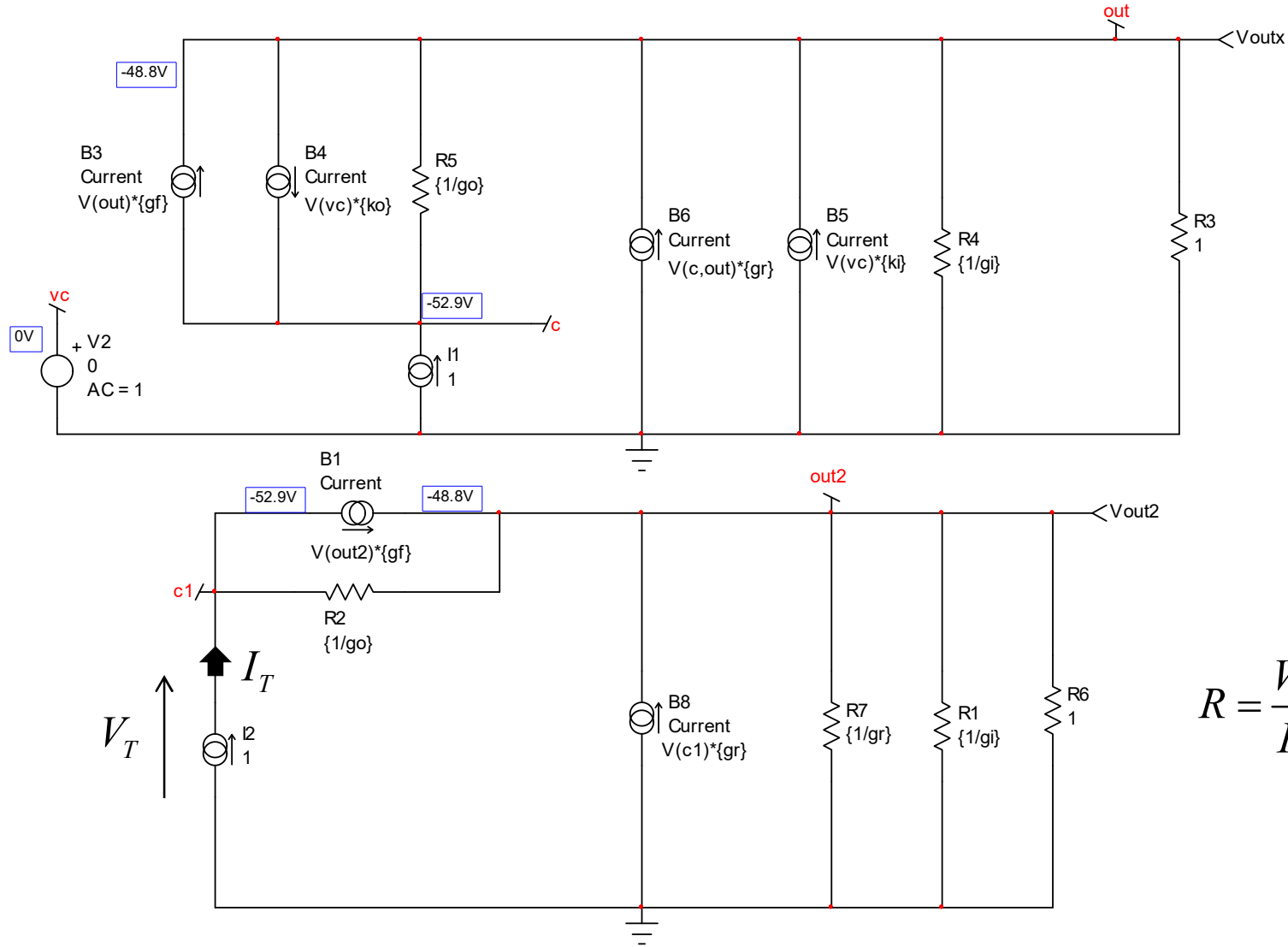

Calculate the Second Time Constant

□ Express I_T and V_{out} then rearrange to unveil V_T/I_T


$$I_T = V_{out}g_f + \frac{V_T - V_{out}}{\frac{1}{g_o}} \quad V_{out} = (I_T + V_Tg_r)R_{eq} \quad R_{eq2} = R_L \parallel \frac{1}{g_i} \parallel \frac{1}{g_r}$$

$$\Rightarrow R = \frac{V_T}{I_T} = \frac{1 - R_{eq}(g_f - g_o)}{g_o + R_{eq}g_r(g_f - g_o)} \quad \Rightarrow \tau_2 = \frac{L}{\frac{1 - R_{eq}(g_f - g_o)}{g_o + R_{eq}g_r(g_f - g_o)}}$$

$$\frac{[1 - R_{eq2} \cdot (g_f - g_o)]}{[g_o + R_{eq2} \cdot g_r \cdot (g_f - g_o)]} = -52.897\Omega \quad \text{Same result as dc point simulation}$$

Calculate the Third Time Constant


- What resistance does C_{out} « see » ?

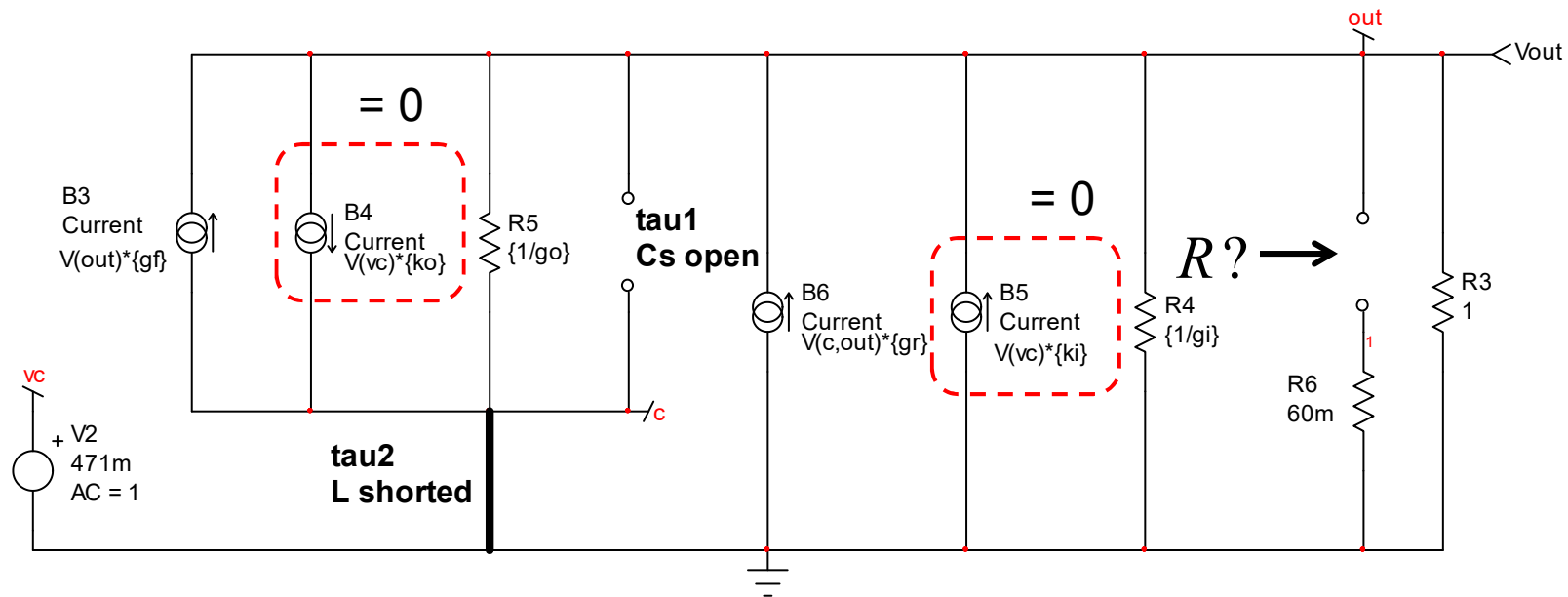

- The circuit is very close to that of τ_1
- Rearrange the network and test it in SPICE

Calculate the Third Time Constant

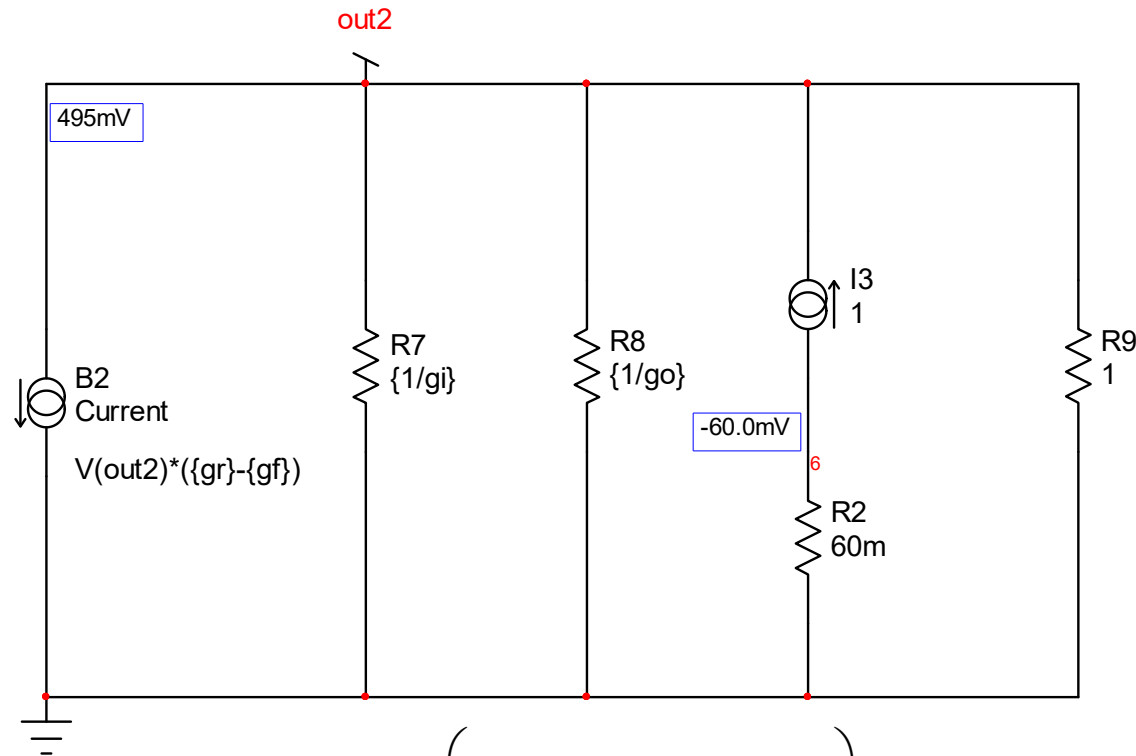- Same resistance as for τ_1 plus r_C in series



$$\tau_3 = \left(\frac{1}{g_r - g_f + \frac{1}{R_{eq1}}} + r_C \right) C_{out}$$

$$R_{eq1} = R_L \parallel \frac{1}{g_i} \parallel \frac{1}{g_o}$$



First Coefficients a_1 and a_2


- FACTs tell us that a_1 sums up all time constants

$$a_1 = \tau_1 + \tau_2 + \tau_3 \longrightarrow \text{Dimension is time}$$

- For a_2 , we multiply combined-time constants

$$a_2 = \tau_1\tau_2^1 + \tau_1\tau_3^1 + \tau_2\tau_3^2 \longrightarrow \text{Dimension is time}^2$$

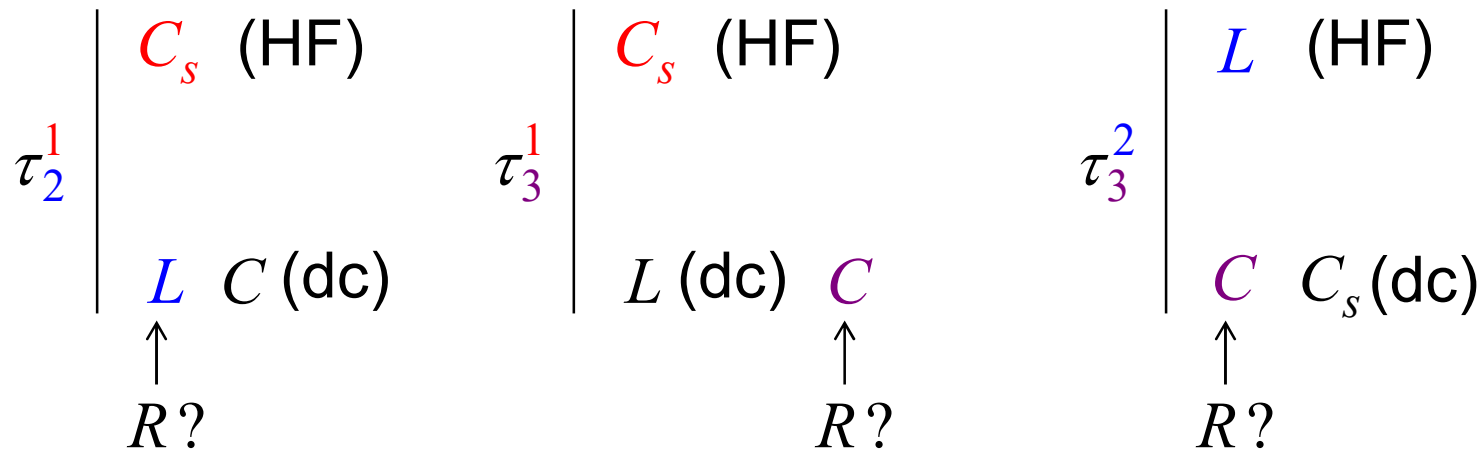- What is this new time constants definition, τ_2^1 ?




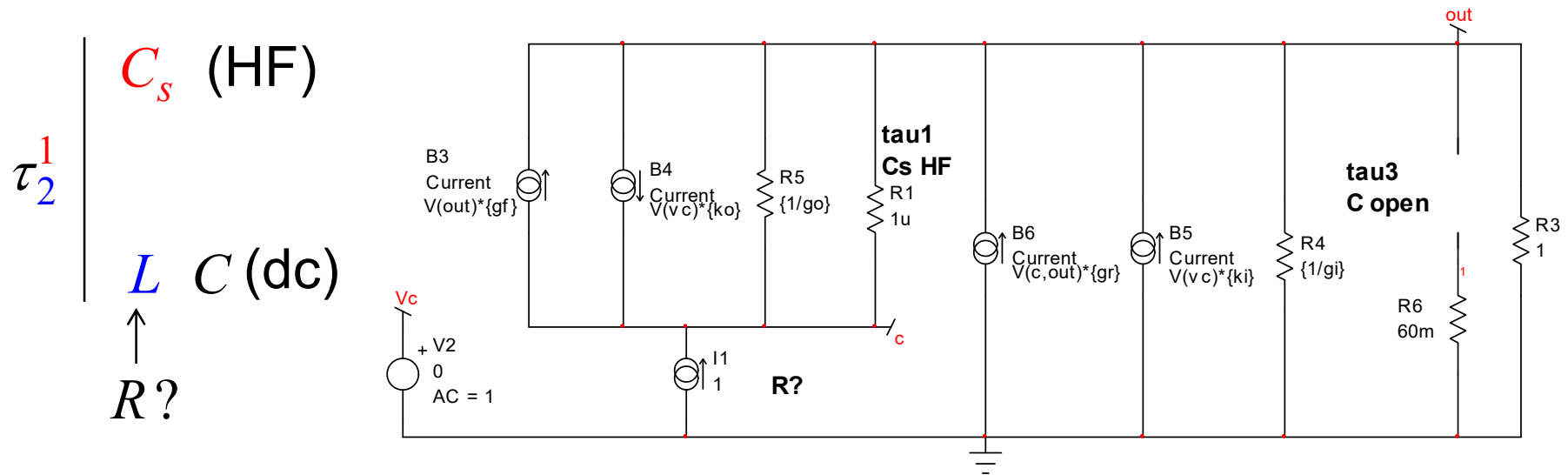V. Vorpérian, "Fast Analytical Techniques for Electrical and Electronic Circuits", Cambridge Press, 2002



Calculate the Terms for a_2

□ What resistance does L while C_s is a short and C_{out} is open?



τ_2^1 C_s (HF)

L C (dc)

$R?$




Go for an intermediate step



A Simplified Drawing for a Simple Answer

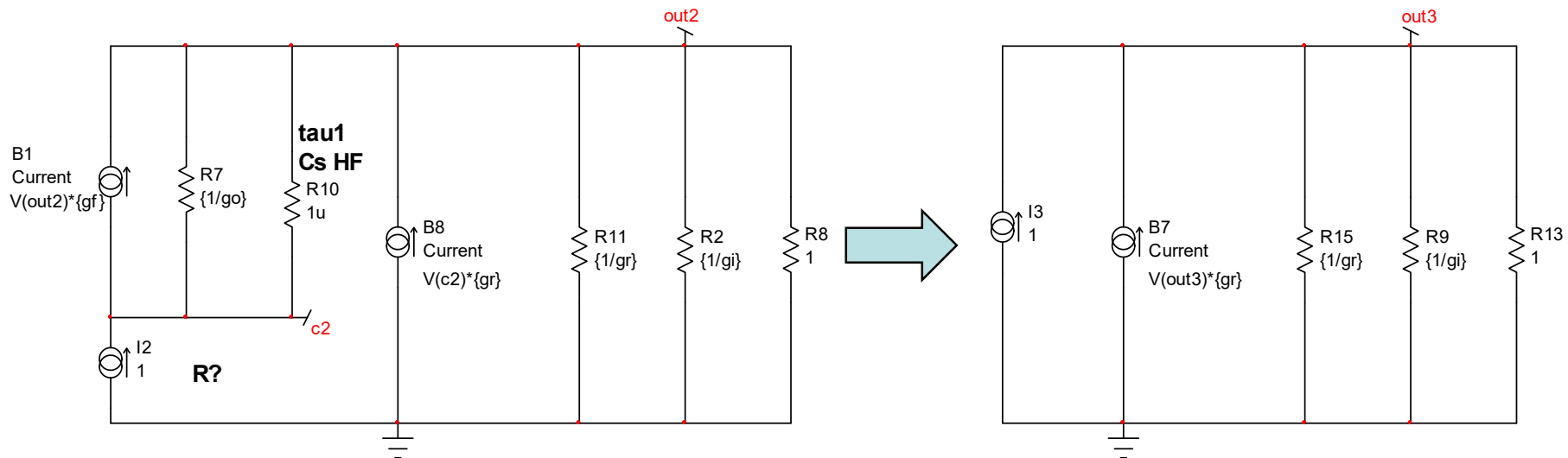□ What $R?$ does L see while C_s is a short and C_{out} is open?




$$\tau_2^1 = \frac{L}{\frac{1}{R_1 \parallel \frac{1}{g_r} \parallel \frac{1}{g_i}} - g_r}$$




The Mid Term is Easy to Get

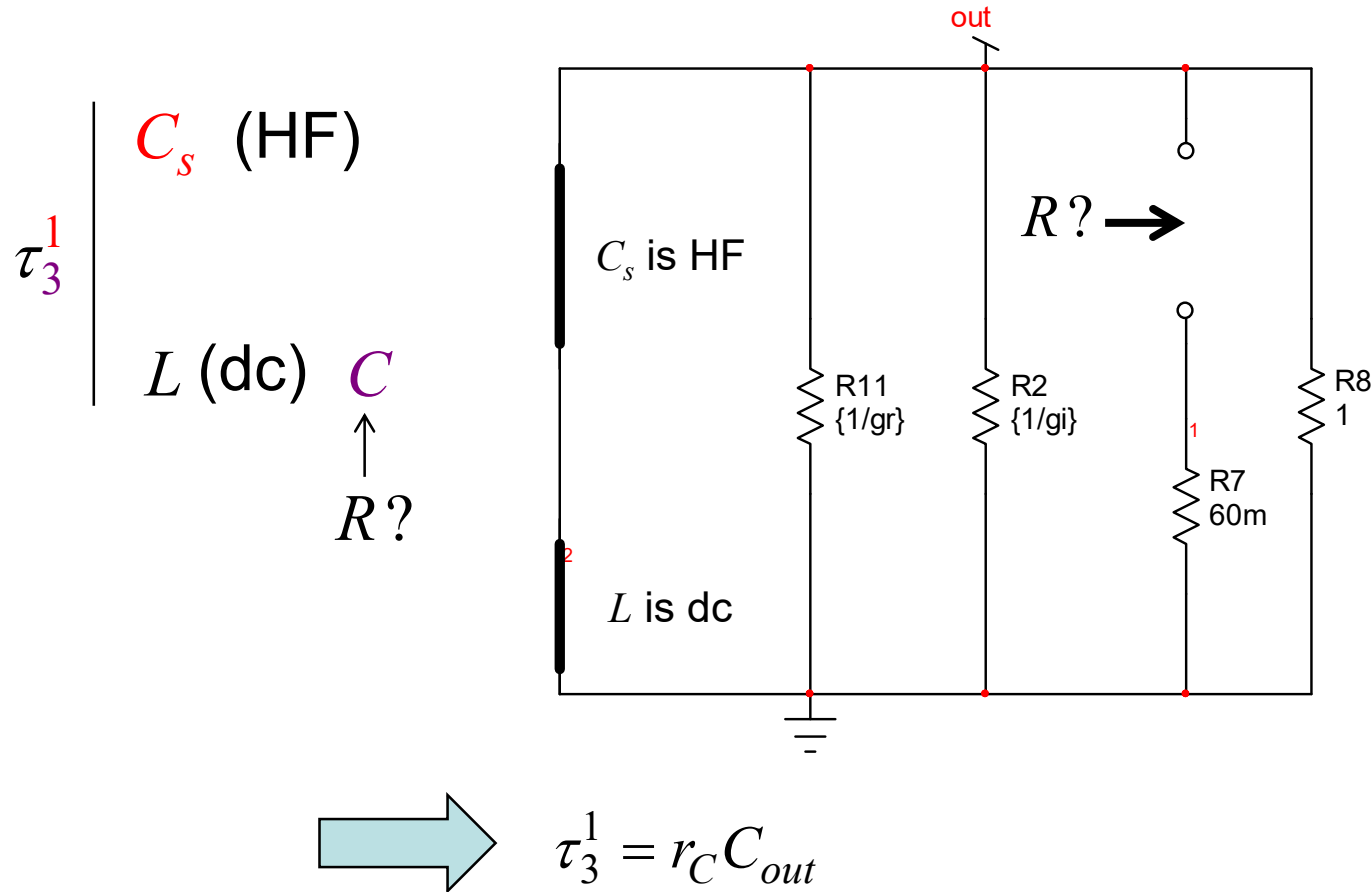- L and C_s ensure a complete short over R_L



For the Last Term, L is open

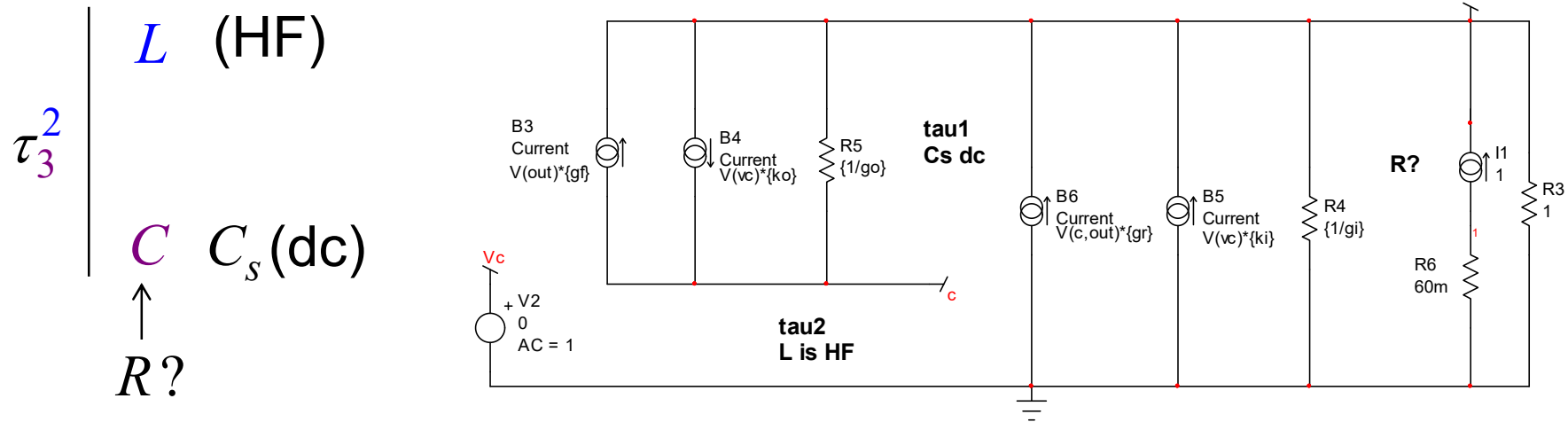□ What resistance does C_{out} see when C_s and L are open?





Too complex! Go for another combination.

$$\tau_2 \tau_3^2 \rightarrow \tau_3 \tau_2^3$$




Reorder Time Constants for Simpler Sketch

□ The schematic now looks simpler...

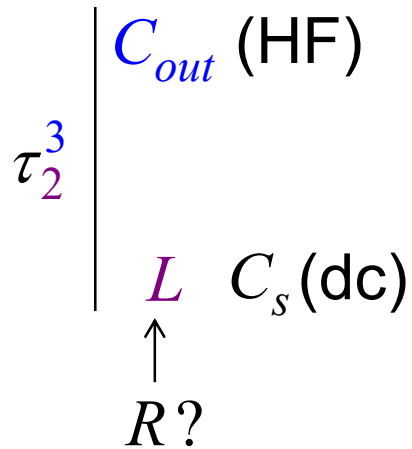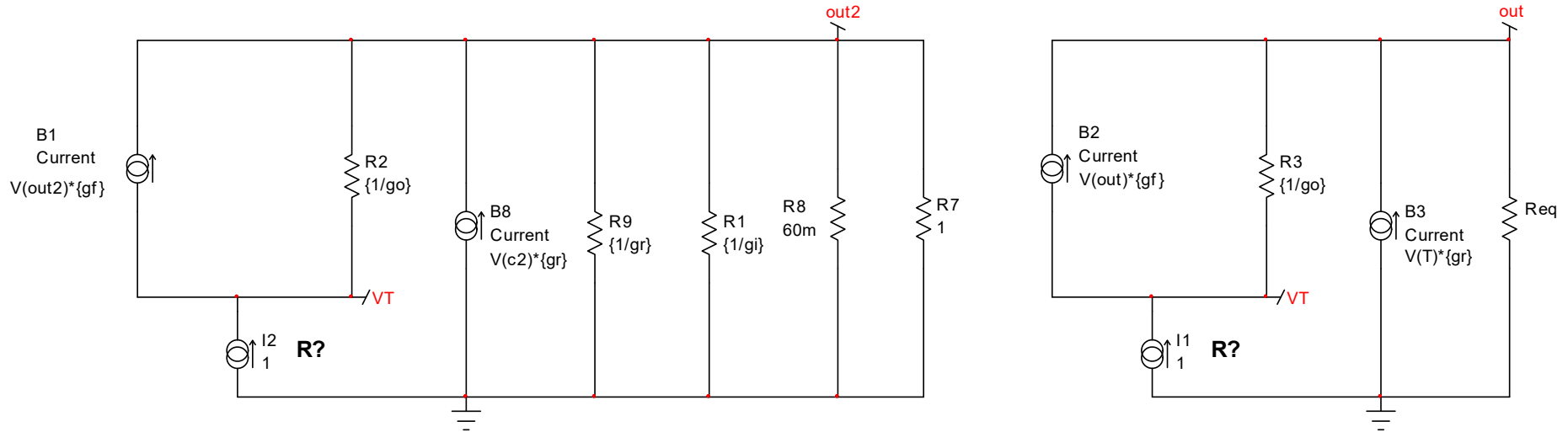

Extract the New Time Constant Definition

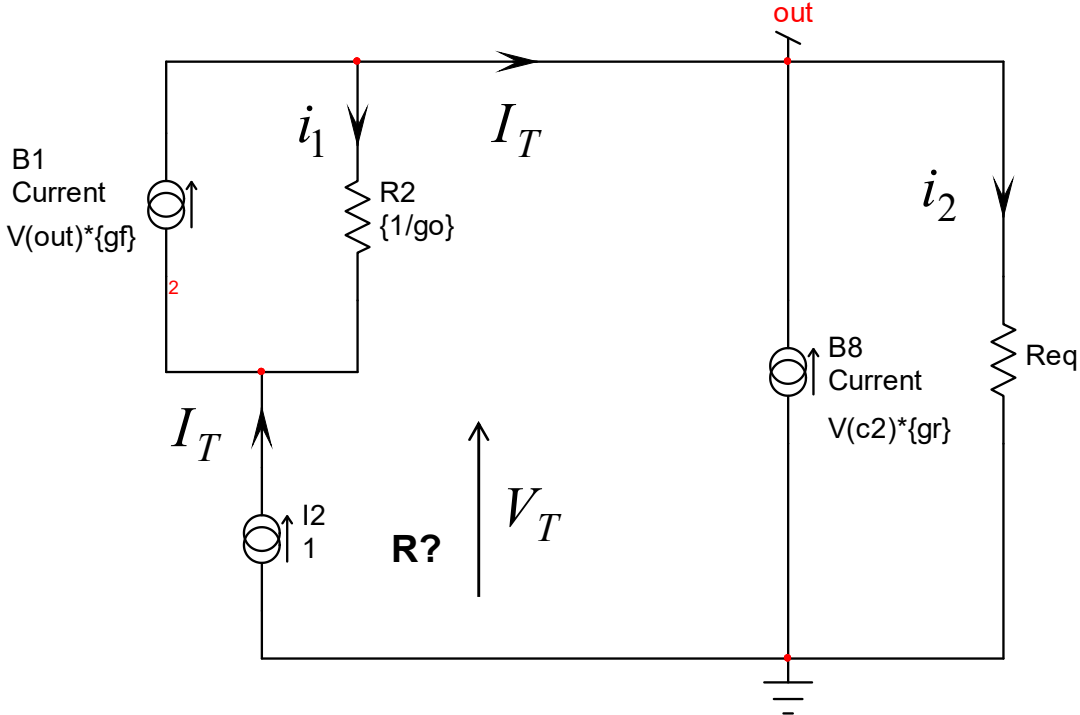

$$R_{eq} = r_C \parallel R_L \parallel \frac{1}{g_i} \parallel \frac{1}{g_r}$$

$$i_2 = I_T + V_T g_r$$

$$I_T = i_1 + V_{out} g_f$$

$$i_1 = \frac{V_T - V_{out}}{\frac{1}{g_o}}$$

$$V_{out} = R_{eq} (I_T + V_T g_r)$$

substitute


$$I_T = \frac{V_T - V_{out}}{\frac{1}{g_o}} + V_{out} g_f \quad \longrightarrow \quad R = \frac{1 - R_{eq} (g_f - g_o)}{g_o + R_{eq} g_r (g_f - g_o)} \quad \tau_2^3 = \frac{L}{R}$$

...And a_3 is ?

- For a_3 , we multiply by a third time-constant

$$a_3 = \tau_1 \tau_2 \tau_3^{1,2} \longrightarrow \text{Dimension is time}^3$$

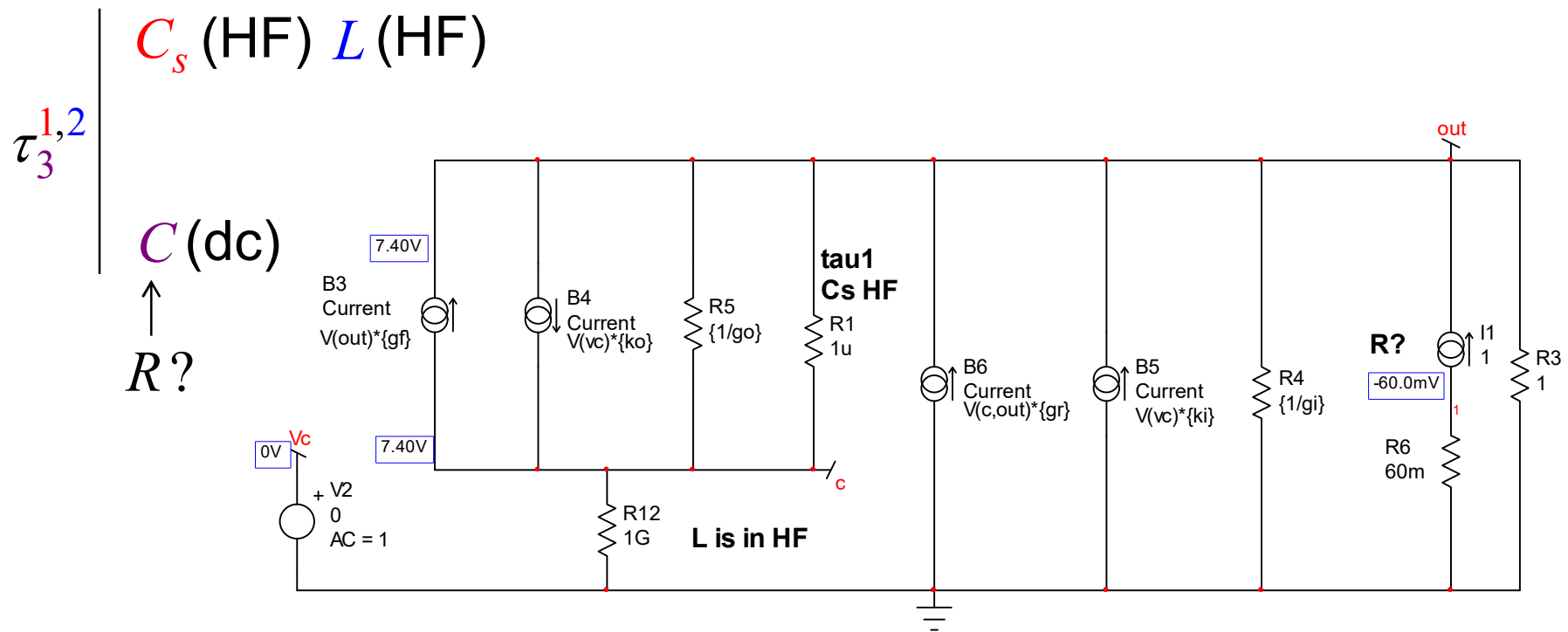- What is this new time constant definition?



Rearrange and Simplify

parameters

Fsw = 1Meg

Tsw = 1/Fsw

L = 5u

Cs = 1/(L*(Fsw*3.14)^2)

Ri = 50m

Se = 0

Vin = 2.7

Vout = 5

Sn = (Vac/L)*Ri

Sf = (Vap/L)*Ri

Vc = 471m

Vac = -Vin

Vap = -Vout

Vcp = (-Vout+Vin)

lc = (Vc/Ri) - D*Tsw*Se - Vcp*(1-D)*Tsw/(2*L)

D = Vcp/Vap

D' = 1-D

ki = D/Ri



gi = D*(gf - lc/Vap)

gr = (lc/Vap) - go*D

ko = 1/Ri

go = (Tsw/L)*(D*Se/Sn + 0.5 - D)

gf = D*go - (D*D)*Tsw/(2*L)

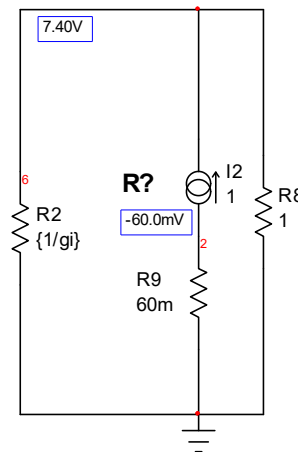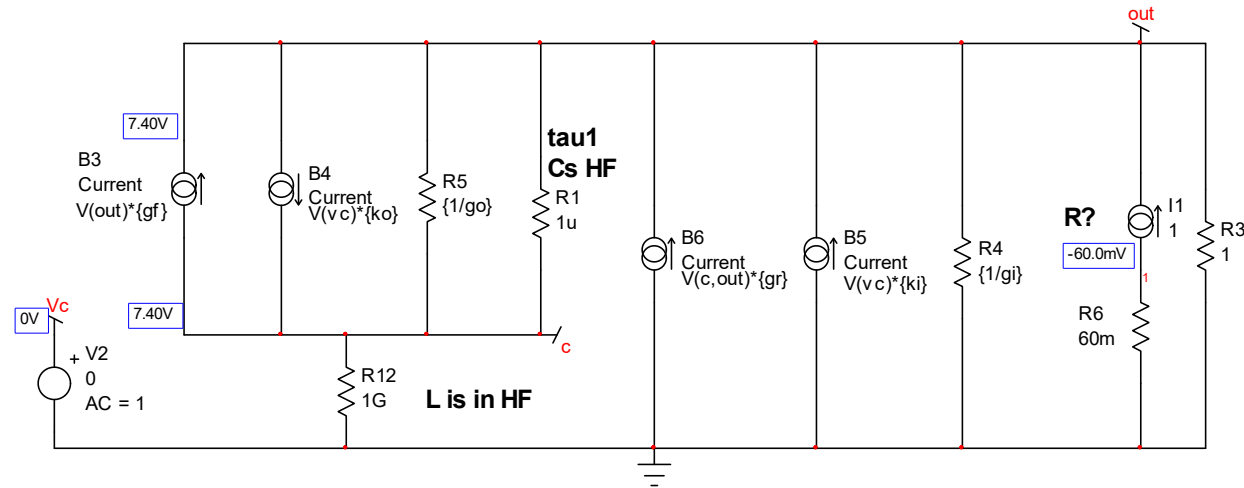

$$\tau_{3,2}^{1,2} = \left(\frac{1}{g_i} \parallel r_L + r_C \right) C_{out}$$

Final Denominator Expression

$$a_1 = \tau_1 + \tau_2 + \tau_3$$

$$a_1 = \left(\frac{1}{g_r - g_f + \frac{1}{R_{eq1}}} \right) C_s + \frac{L}{\frac{1 - R_{eq2}(g_f - g_o)}{g_o + R_{eq2}g_r(g_f - g_o)}} + \left(\frac{1}{g_r - g_f + \frac{1}{R_{eq1}}} + r_C \right) C_{out}$$

$$a_2 = \tau_1\tau_2^1 + \tau_1\tau_3^1 + \tau_2\tau_3^2 \rightarrow \tau_1\tau_2^1 + \tau_1\tau_3^1 + \tau_3\tau_2^3$$


$$a_2 = \left(\frac{1}{g_r - g_f + \frac{1}{R_{eq1}}} \right) C_s \frac{L}{\frac{1}{R_1 \parallel \frac{1}{g_r} \parallel \frac{1}{g_i}} - g_r} + \left(\frac{1}{g_r - g_f + \frac{1}{R_{eq1}}} \right) C_s r_C C_{out} + \left(\frac{1}{g_r - g_f + \frac{1}{R_{eq1}}} + r_C \right) C_{out} \frac{L}{\frac{1 - R_{eq2}(g_f - g_o)}{g_o + R_{eq2}g_r(g_f - g_o)}}$$

$$a_3 = \tau_1\tau_2^1\tau_3^{12} \quad a_3 = \left(\frac{1}{g_r - g_f + \frac{1}{R_{eq1}}} \right) C_s \frac{L}{\frac{1}{R_1 \parallel \frac{1}{g_r} \parallel \frac{1}{g_i}} - g_r} \left(\frac{1}{g_i} \parallel r_L + r_C \right) C_{out}$$



Find the Zeros

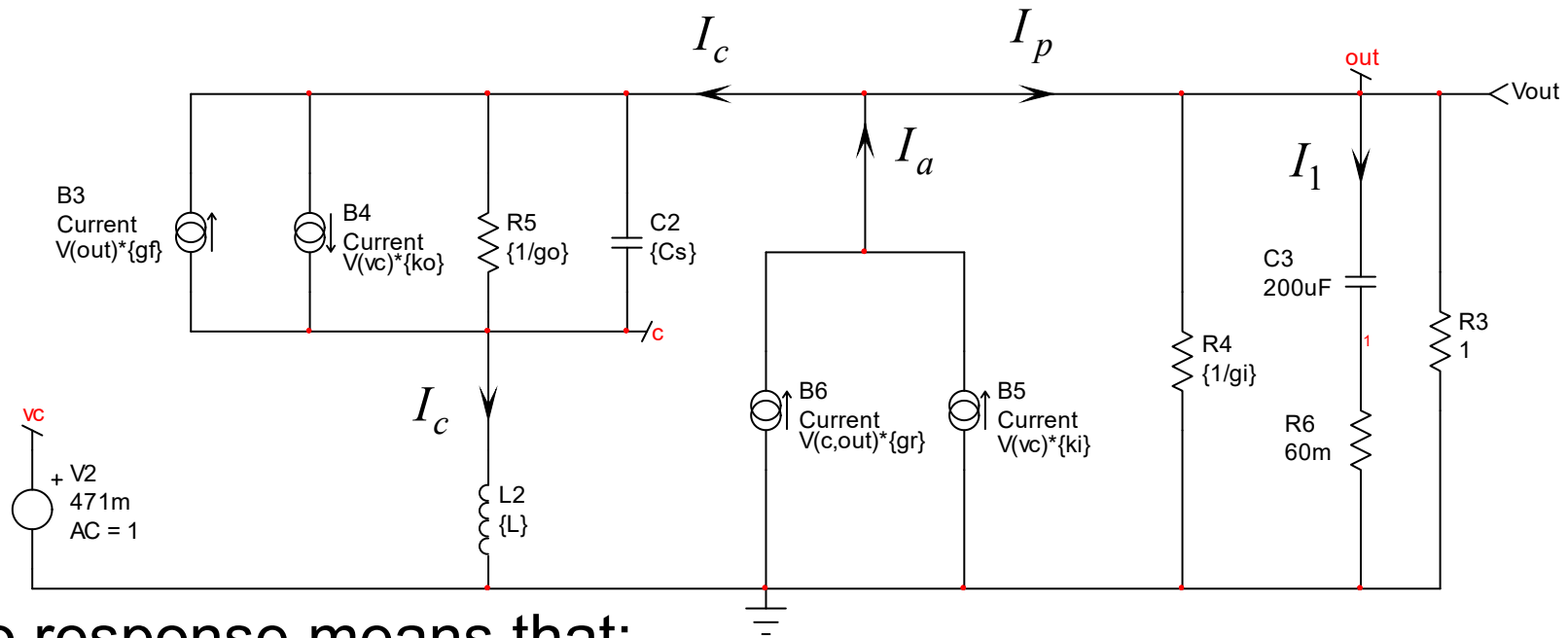- A zero means the *excitation* does not generate a *response*




No response means that:

$$I_p = 0 \left\{ \begin{array}{l} I_p = I_1 \longrightarrow \text{Short circuit} \longrightarrow r_C + sC_{out} = 0 \longrightarrow s_{z_1} = -\frac{1}{r_C C_{out}} \\ I_p = 0 \longrightarrow V_{out} = 0 \end{array} \right.$$



Find the Zeros

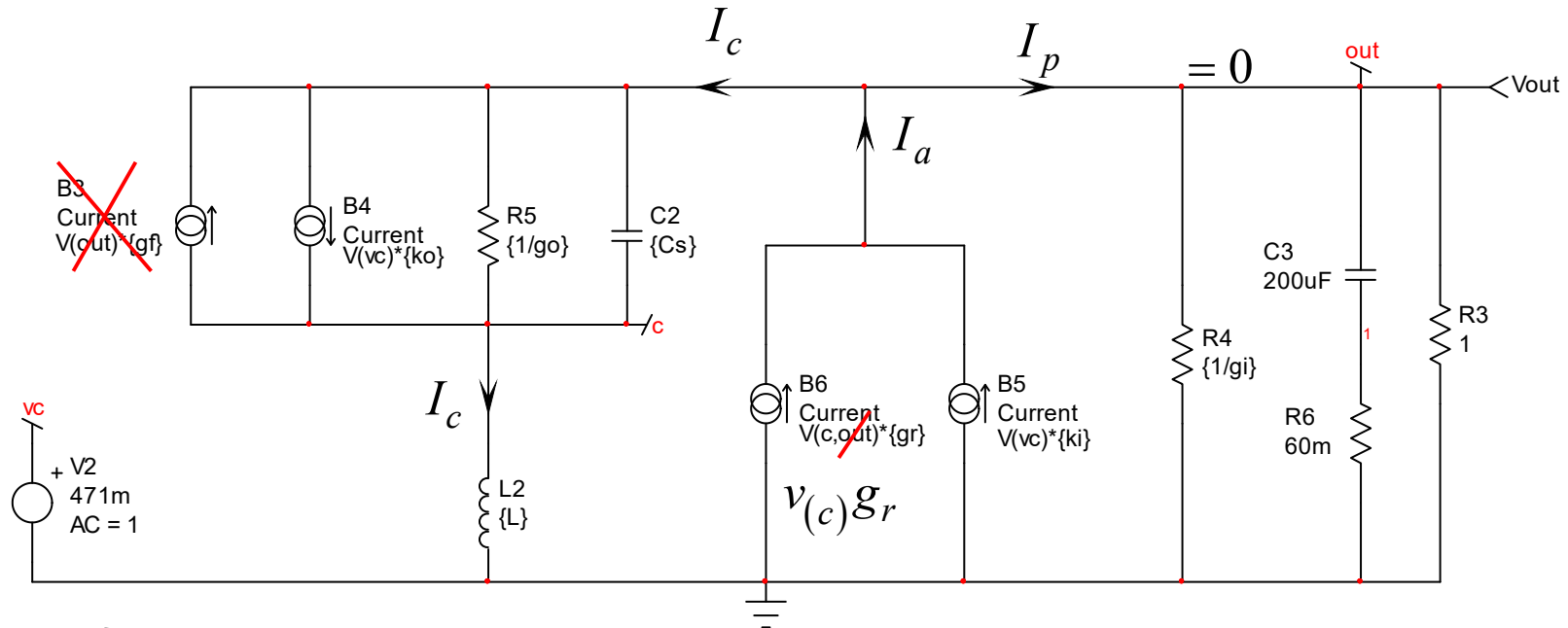- A Capitalize on the 0-V response to remove sources



$$\left. \begin{aligned} I_a = I_p \end{aligned} \right\} \begin{aligned} v_{(c)}g_r + V_c k_i &= I_c \\ I_c &= V_c k_o - v_{(c)}g_o - v_{(c)}sC_s \\ v_{(c)}g_r + V_c k_i &= V_c k_o - v_{(c)}g_o - v_{(c)}sC_s \end{aligned}$$

$$\frac{v_{(c)}}{sL} = V_c k_o - v_{(c)}g_o - v_{(c)}sC_s$$

$$v_{(c)} = \frac{V_c k_o}{\frac{1}{sL} + g_o + sC_s}$$



Find The Zeros

□ After substituting $v_{(c)}$ into the equation rearrange it

$$\frac{V_c (k_i + Lg_o k_i s + Lg_r k_o s + C_s L k_i s^2)}{1 + sLg_o + s^2 C_s L} = \frac{V_c k_o}{1 + sLg_o + s^2 C_s L}$$

➔ $k_i + Lg_o k_i s + Lg_r k_o s + C_s L k_i s^2 = k_o$

$$(k_i - k_o) \left(1 + sL \left(\frac{g_o k_i + g_r k_o}{k_i - k_o} \right) + s^2 \frac{C_s L k_i}{k_i - k_o} \right) = 0$$

➔ $1 + sL \left(\frac{g_o k_i + g_r k_o}{k_i - k_o} \right) + s^2 \frac{C_s L k_i}{k_i - k_o} = 0$

For low Q values, the 2nd order polynomial can be expressed as

$$1 + a_1 s + a_2 s^2 \approx (1 + a_1 s) \left(1 + \frac{a_2}{a_1} s \right)$$

Find the Zeros – Final Lap!

- The first zero is a right half-plane zero

$$1 + sL \left(\frac{g_o k_i + g_r k_o}{k_i - k_o} \right) = 1 - \frac{s}{s_{z_1}} \quad s_{z_1} = \frac{k_i - k_o}{L(g_o k_i + g_r k_o)} \quad \Rightarrow \quad \omega_{z_1} \approx \frac{(1-D)^2 R_L}{L}$$

Negative value!

- The second zero is given by the capacitor ESR

$$1 + sr_C C_{out} = 0 \quad \Rightarrow \quad \omega_{z_2} \approx \frac{(1-D)^2 R_L}{L}$$

- The third zero is located at high frequency

$$1 + s \frac{C_s k_i}{g_o k_i + g_r k_o} = 1 + \frac{s}{s_{z_3}} \quad s_{z_3} = \frac{g_o k_i + g_r k_o}{C_s k_i} \quad \Rightarrow \quad \text{Neglect it}$$

$$\longrightarrow f_{z2} := \frac{\omega_{z2}}{2\pi} = 3.16 \times 10^4 \text{ kHz}$$

V. Vorpérian, "Analytical Methods in Power Electronics", 3-day course in Toulouse, 2004



Arranging the Transfer Function

- The denominator has to be rearranged a little bit...

$$D(s) = 1 + b_1s + b_2s^2 + b_3s^3$$

- The term $1 + b_1s$ dominates at low frequency

$$1 + b_1s + b_2s^2 + b_3s^3 \approx (1 + b_1s) \left(1 + \frac{b_2}{b_1}s + \frac{b_3}{b_1}s^2 \right)$$

$$(1 + b_1s) \left(1 + \frac{b_2}{b_1}s + \frac{b_3}{b_1}s^2 \right) \approx \left(1 + \frac{s}{\omega_{p1}} \right) \frac{1}{1 + \frac{s}{\omega_n Q_p} + \left(\frac{s}{\omega_n} \right)^2}$$

$$\omega_{p1} \approx \frac{\frac{2}{R_L} + \frac{T_{sw}}{LM^3} \left(1 + \frac{S_a}{S_n} \right)}{C_{out}}$$

$$Q_p = \frac{1}{\pi(m_c D' - 0.5)} \quad \omega_n = \frac{\pi}{T_{sw}} \quad m_c = 1 + \frac{S_a}{S_n}$$

Dc gain H_0



$$H_0 \approx \frac{R_L}{R_i} \frac{1}{2M + \frac{R_L T_{sw}}{LM^2} \left(\frac{1}{2} + \frac{S_a}{S_n} \right)}$$



Final Expression

□ The transfer function of a CCM Boost Converter in CM is


$$\frac{V_{out}(s)}{V_c(s)} \approx \frac{R_L}{R_i} \frac{1}{2M + \frac{R_L T_{sw}}{LM^2} \left(\frac{1}{2} + \frac{S_a}{S_n} \right)} \frac{\left(1 - s \frac{L}{(1-D)^2 R_L} \right) (1 + sr_C C_{out})}{1 + s \frac{C_{out}}{\frac{2}{R_L} + \frac{T_{sw}}{LM^3} \left(1 + \frac{S_a}{S_n} \right)}} \frac{1}{1 + \frac{s}{\omega_n Q_p} + \left(\frac{s}{\omega_n} \right)^2}$$

S_a is the external ramp compensation to damp subharmonic oscillations




Check SPICE Versus Mathcad

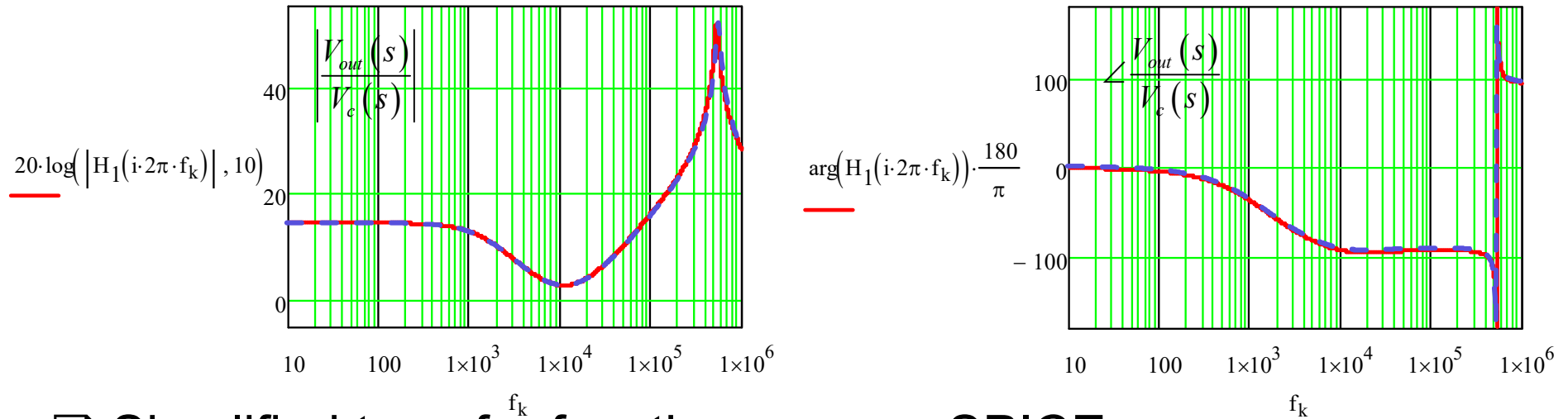□ Full-featured transfer functions versus SPICE



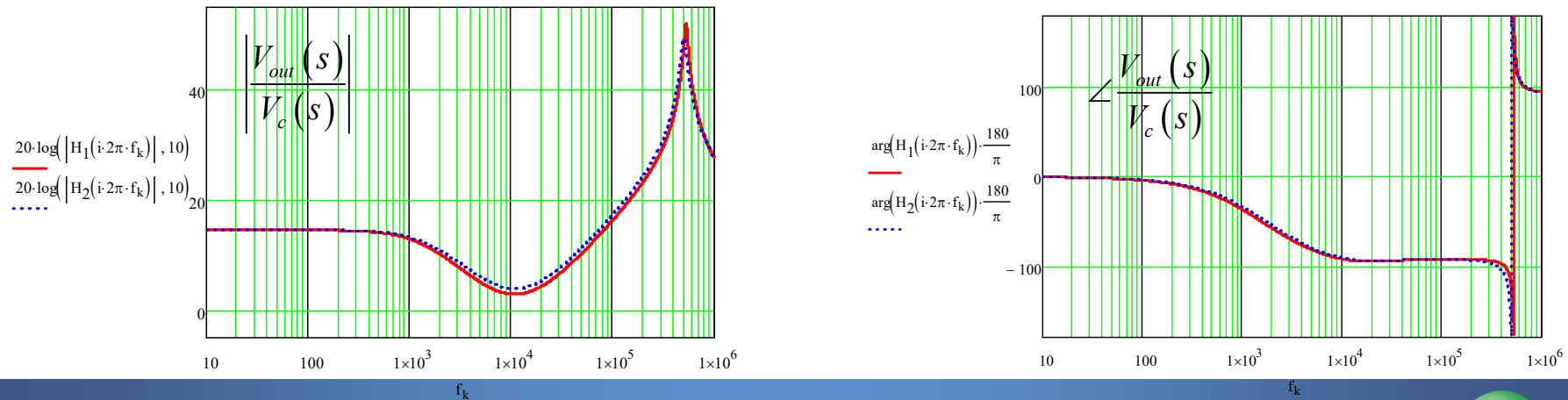□ Simplified transfer functions versus SPICE



Course Agenda

- ❑ The PWW Switch Concept
- ❑ Small-Analysis in Continuous Conduction Mode
- ❑ **Small-Signal Response in Discontinuous Mode**
- ❑ EMI Filter Output Impedance
- ❑ Cascaded Converters Operation



The CM Boost Converter in DCM

□ To check the operating mode, calculate the critical load

$$R_{crit} = \frac{2F_{sw}LV_{out}^2}{V_{in}^2 \left(1 - \frac{V_{in}}{V_{out}}\right)}$$


$$F_{sw} = 1 \text{ MHz}$$

$$L = 5 \mu\text{H}$$

$$V_{in} = 2.7 \text{ V}$$

$$V_{out} = 5 \text{ V}$$
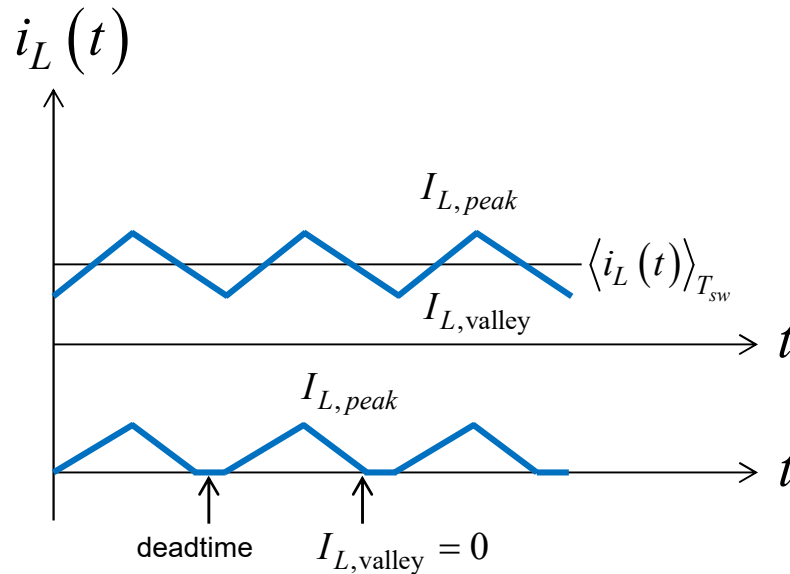
$$\longrightarrow R_{crit} = 74.7 \Omega$$



CCM, $R_L < R_{crit}$

DCM, $R_L > R_{crit}$



Transfer Function of DCM CM Boost

- The converter is a first-order converter at low frequency

$$H(s) = \frac{1}{S_n m_c T_{sw}} \frac{2V_{out}}{D} \frac{M-1}{2M-1} \frac{\left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 - \frac{s}{\omega_{z_2}}\right)}{\left(1 + \frac{s}{\omega_{p_1}}\right) \left(1 + \frac{s}{\omega_{p_2}}\right)}$$



$$S_n = \frac{V_{in}}{L} R_i \quad \omega_{z_1} = \frac{1}{r_C C_{out}} \quad \omega_{z_2} = \frac{R_{load}}{M^2 L} \quad \omega_{p_1} = \frac{1}{R_L C_{out}} \frac{2M-1}{M-1}$$

$$\omega_{p_2} = 2F_{sw} \left(\frac{1 - \frac{1}{M}}{D} \right)^2 \quad m_c = 1 + \frac{S_a}{S_n}$$



The Ac Response of the DCM CM Boost

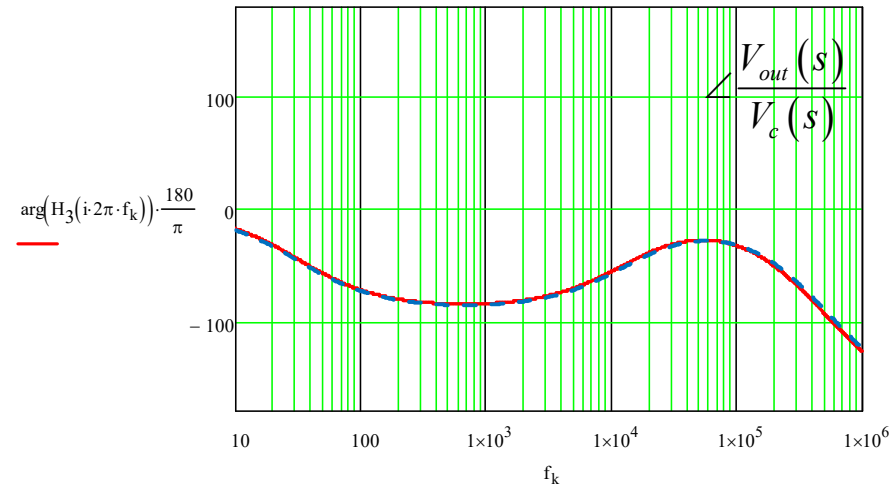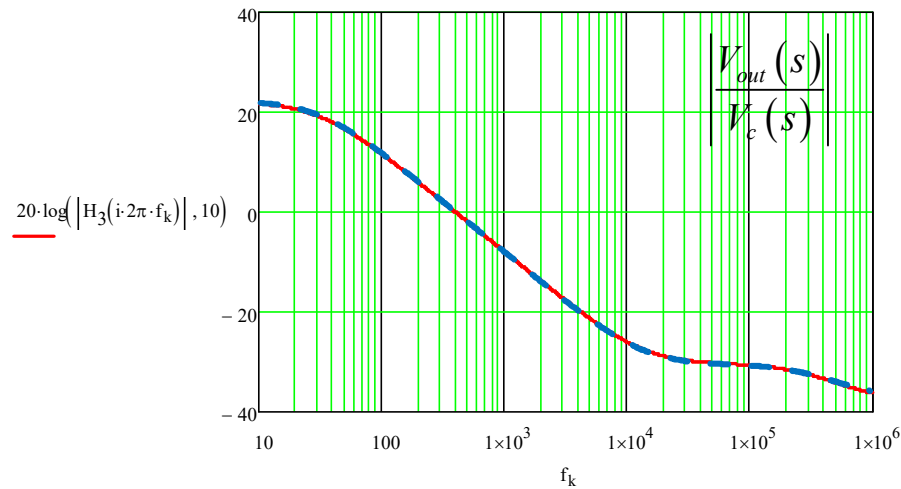- A RHPZ is still present in DCM with a high-frequency pole




SPICE simulation versus Mathcad



Why a RHP Zero in DCM?

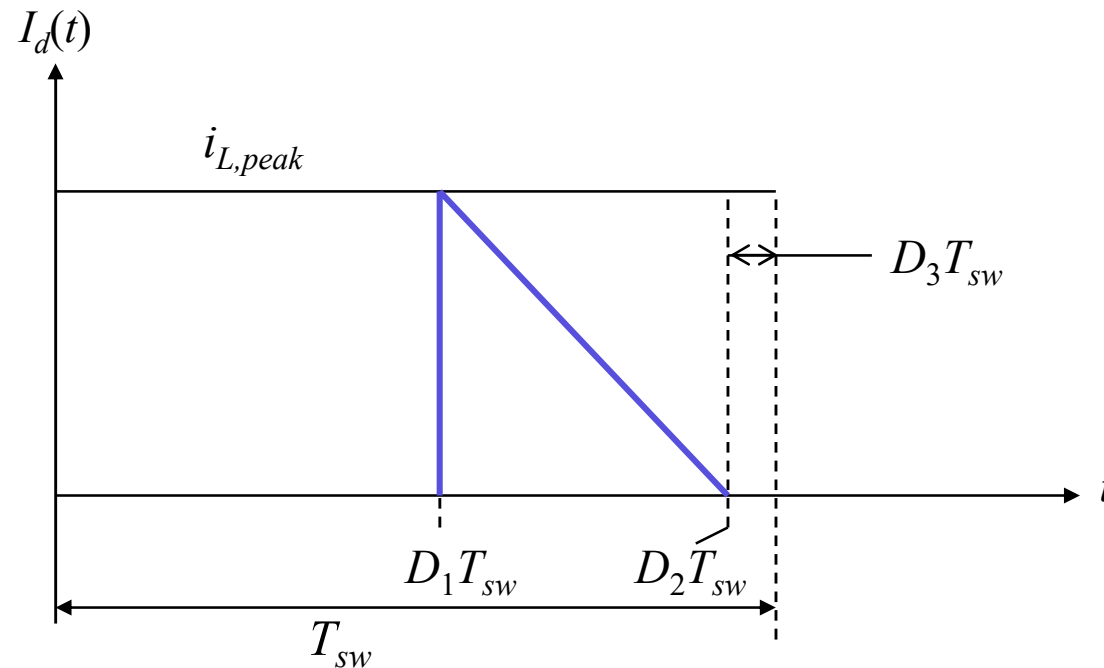
- The RHP Zero is present in CCM and is still there in DCM!



- When D_1 increases, $[D_1, D_2]$ stays constant but D_3 shrinks

Why a RHP Zero in DCM?

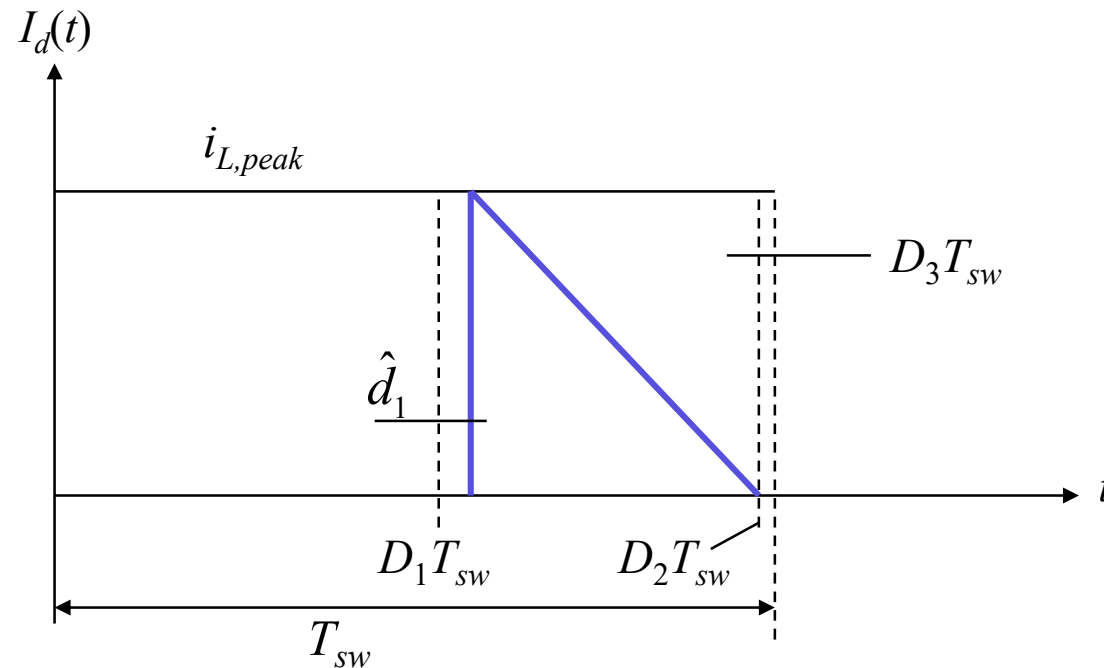
- The triangle is simply shifted to the right by \hat{d}_1



- The capacitor refueling time is delayed and a drop occurs

The Refueling Time is Shifted

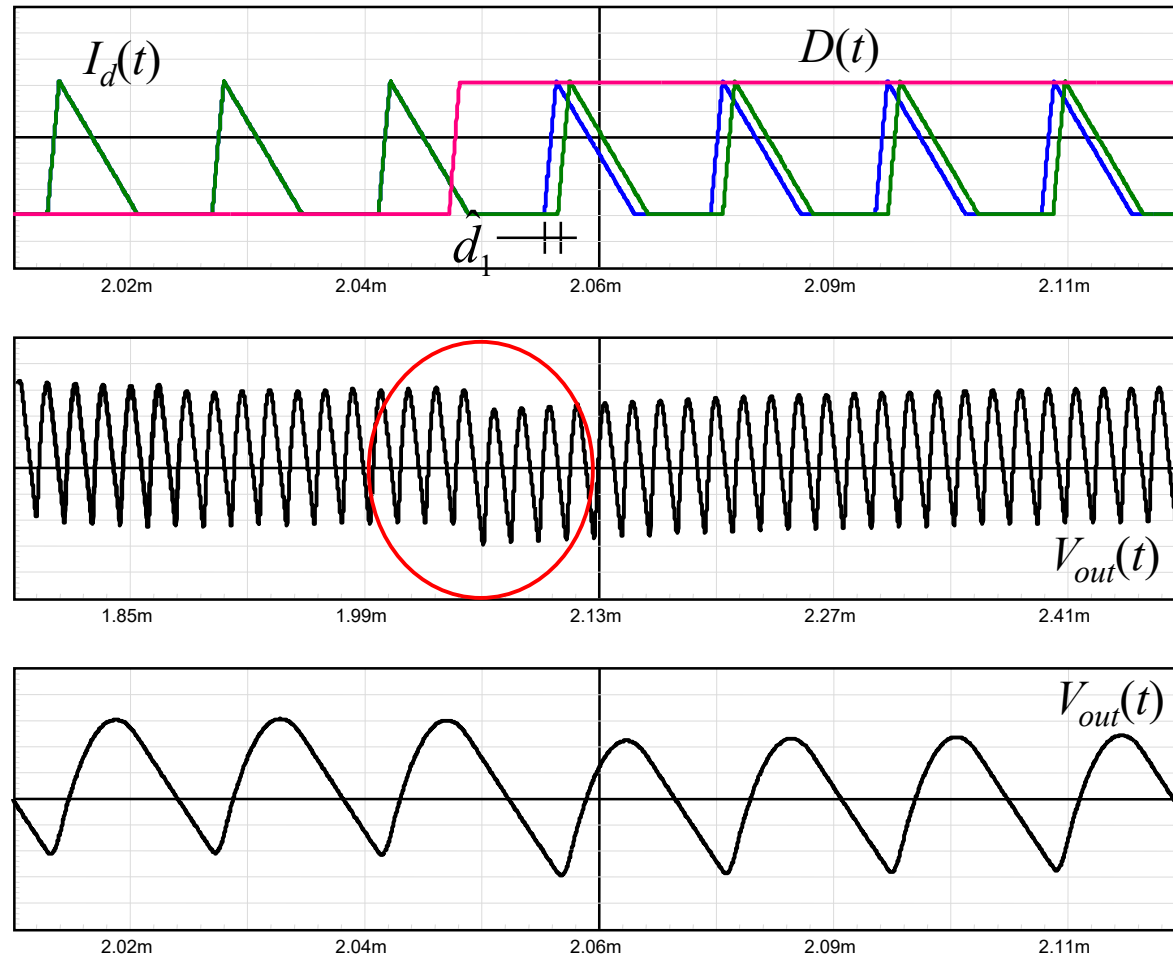- If D increases, the diode current is delayed by \hat{d}_1



Simulation, no peak increase


Course Agenda

- ❑ The PWW Switch Concept
- ❑ Small-Analysis in Continuous Conduction Mode
- ❑ Small-Signal Response in Discontinuous Mode
- ❑ **EMI Filter Output Impedance**
- ❑ Cascaded Converters Operation



EMI Filter Interaction

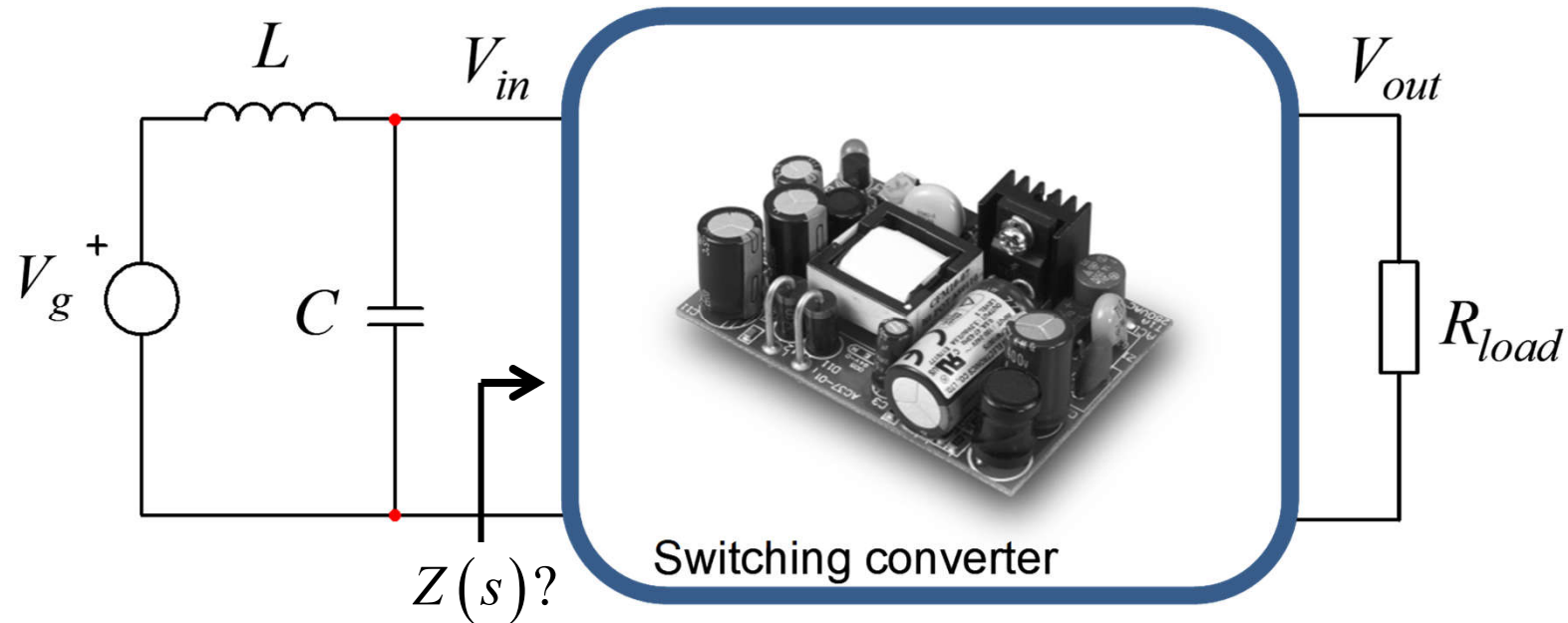- A LC filter is included to prevent the dc line pollution



- What load does the converter offer?

C. Basso, "Designing Control Loops for Linear and Switching Power Supplies", Artech House, 2012

A Negative Incremental Resistance


- Assume a 100%-efficient converter:

$$P_{out} = P_{in} \longrightarrow I_{in}V_{in} = I_{out}V_{out}$$

- In closed-loop operation, P_{out} is constant

$$\longrightarrow I_{in}(V_{in}) = \frac{P_{out}}{V_{in}}$$

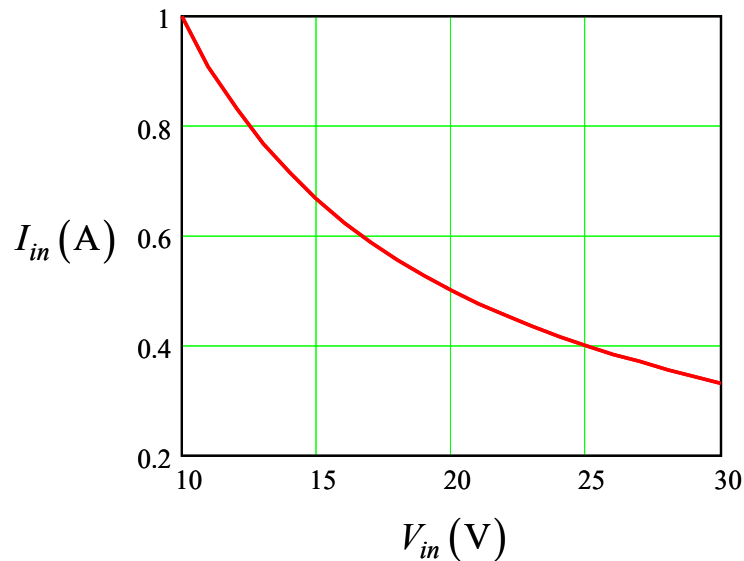- For a constant P_{out} , if V_{in} increases, I_{in} drops




$$\frac{dI_{in}(V_{in})}{dV_{in}} = \frac{d\left(\frac{P_{out}}{V_{in}}\right)}{dV_{in}} = -\frac{P_{out}}{V_{in}^2}$$

The incremental input resistance is negative

A Simple LC Filter

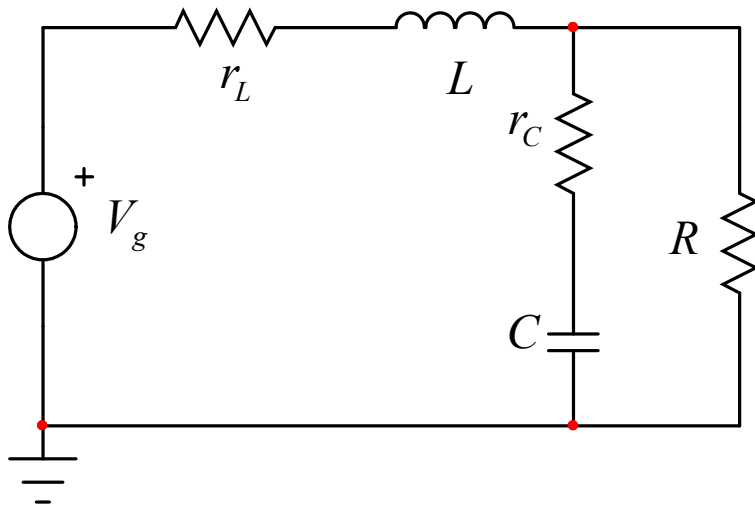□ The low-pass filter is built with a L and C components:



$$T(s) = \frac{1 + s/\omega_{z_1}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

$$\omega_{z_1} = \frac{1}{r_C C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{r_L + R}{r_C + R}}$$

$$Q = \frac{LC\omega_0(r_C + R)}{L + C(r_L r_C + r_L R + r_C R)} \approx R_{load} \sqrt{\frac{C}{L}}$$

If R is || with $-R$



$$Q = \frac{R \cdot (-R)}{R - R} \sqrt{\frac{C}{L}} \rightarrow \infty$$

A negative resistance cancels losses: poles become imaginary





A Negative Impedance Oscillator

- If losses are compensated, the damping factor is zero


$$T(s) = \frac{1}{\frac{s^2}{\omega_0^2} + \frac{s}{\omega_0 Q} + 1} \quad Q = \frac{1}{2\zeta} \rightarrow \text{If ohmic losses are gone, the damping factor is zero, } Q \text{ is infinite.}$$

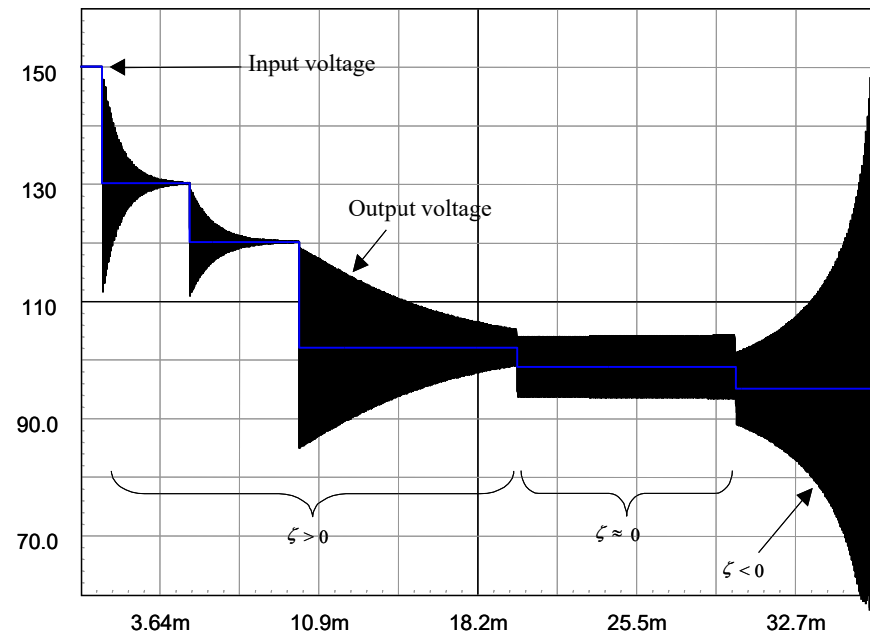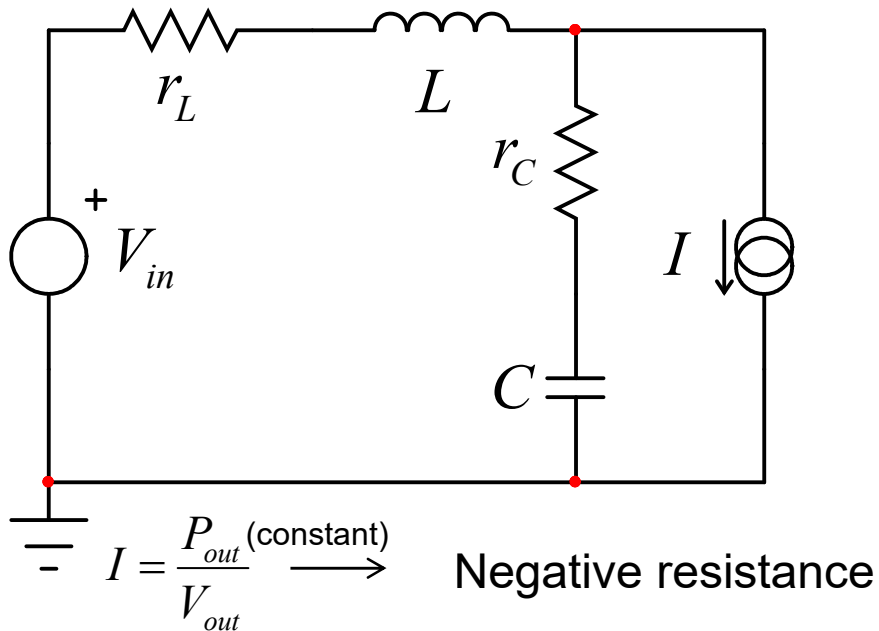- Without precautions, instability can happen!



Filter Output Impedance

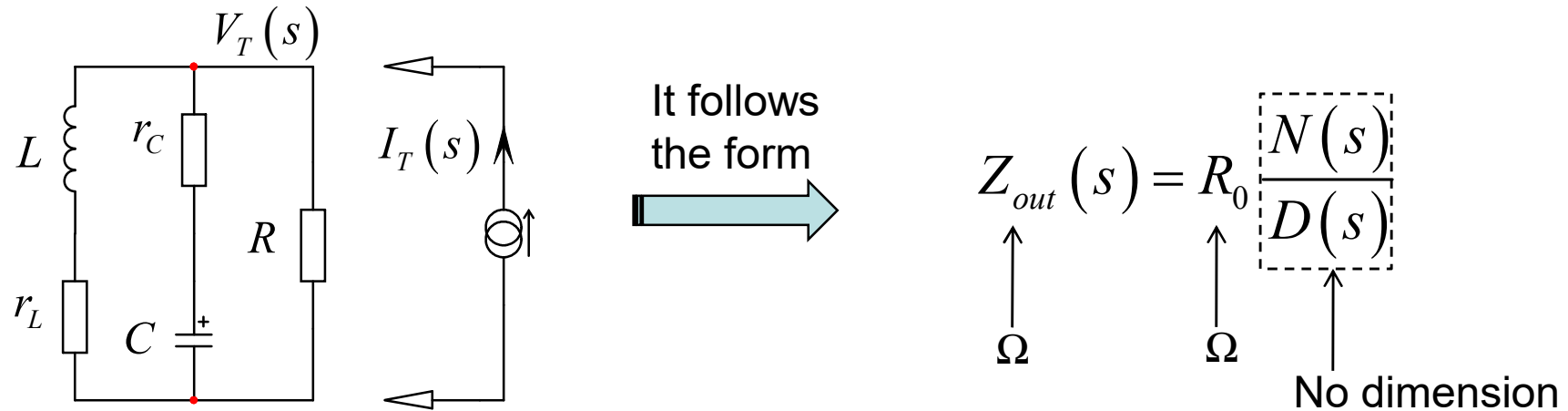
□ What is the output impedance of an LC filter?



$$Z_{out}(s) = (r_L \parallel R_{load}) \frac{\left(1 + s \frac{L}{r_L}\right) (1 + sr_C C_{out})}{1 + s \left(\frac{L}{r_L + R_{load}} + C [(r_L \parallel R_{load}) + r_C] \right) + s^2 \left(LC \frac{r_C + R_{load}}{r_L + R_{load}} \right)}$$

Negative Resistance at Low Frequency

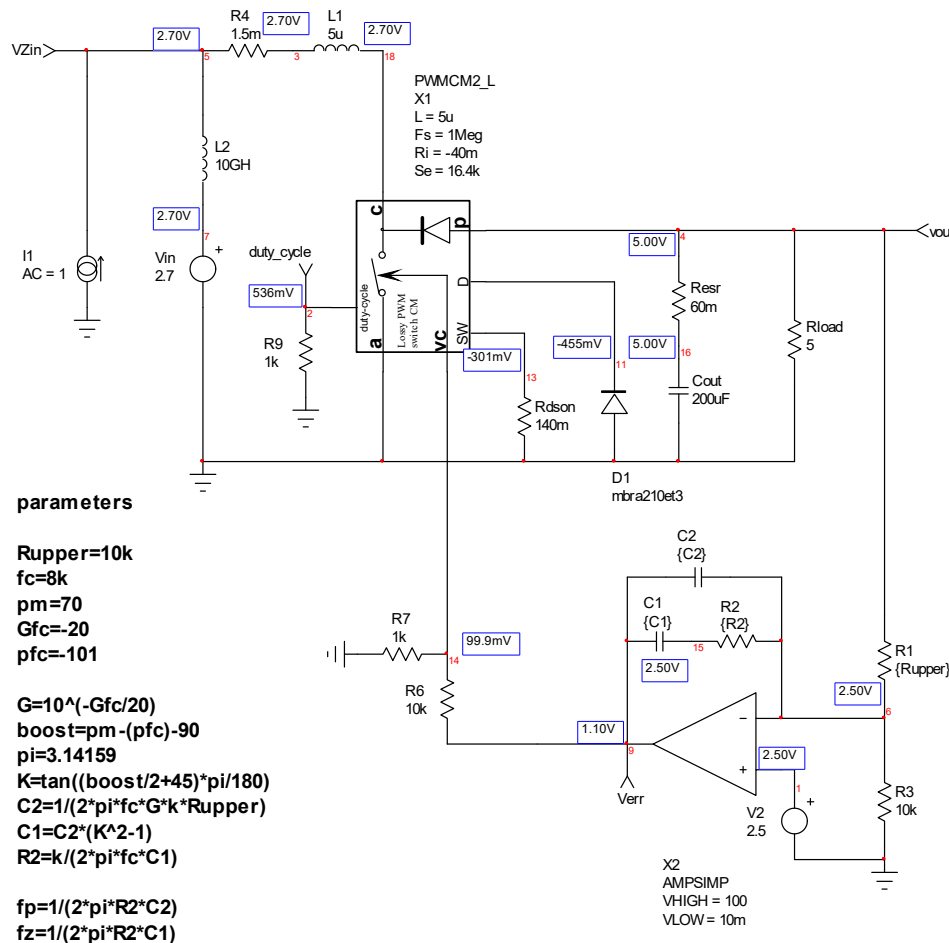□ Neg. resistance exists because of feedback ($P_{out} = \text{constant}$)




SwitchMode Power Supplies: SPICE Simulations and Practical Designs
 Christophe Basso - McGraw-Hill, 2014




Negative Resistance at Low Frequency

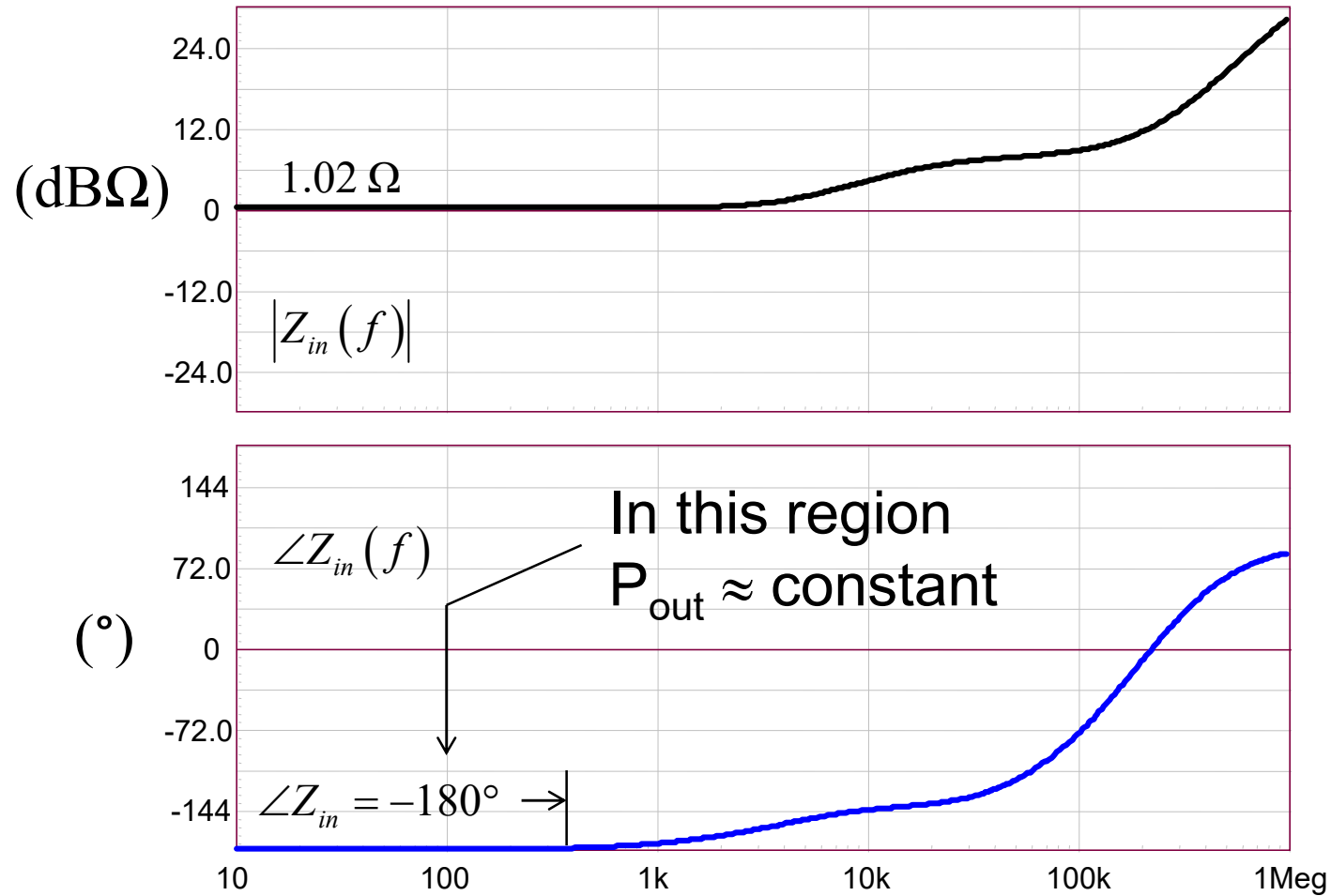- The resistance is truly negative up to 200 Hz




Negative Resistance is One Part Only

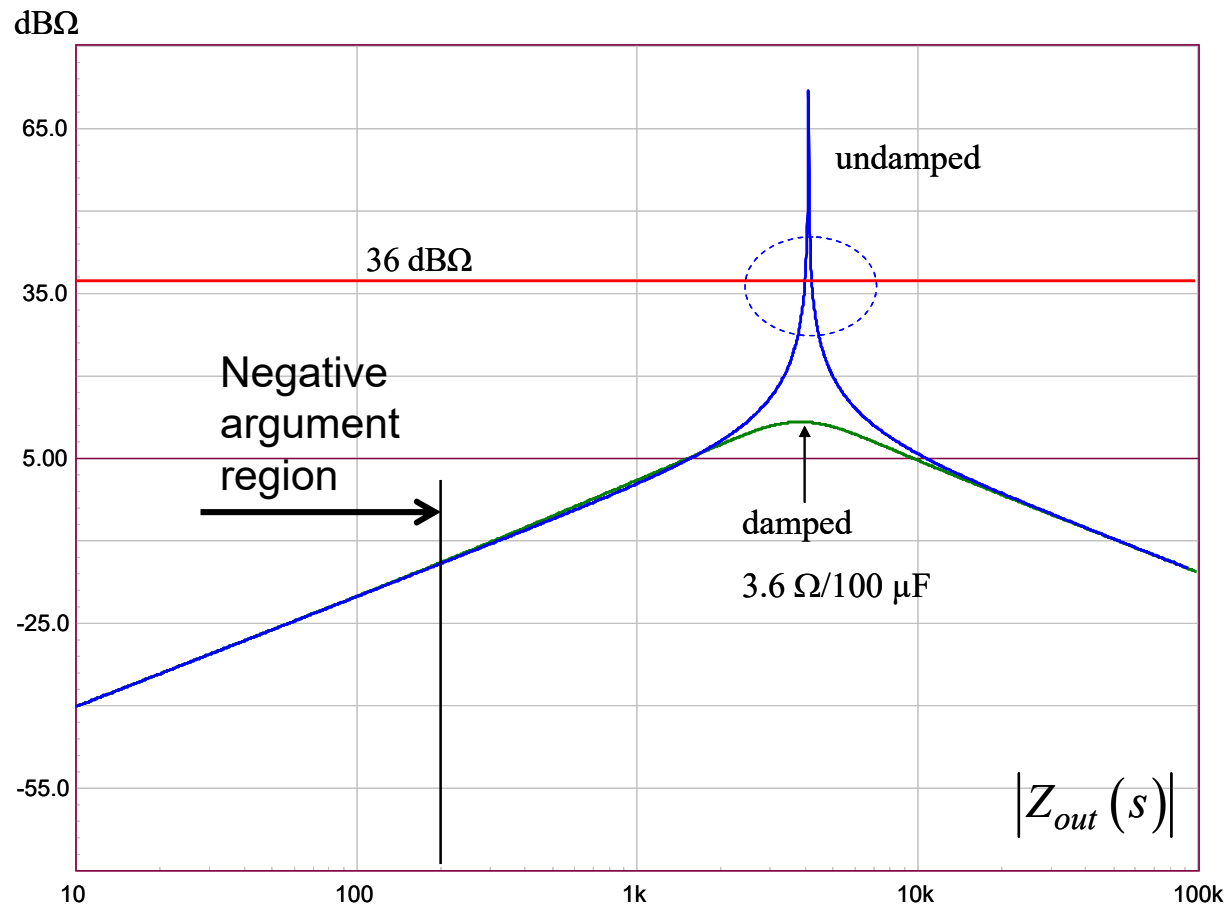- ❑ Negative resistance problems occur only when $\angle Z_{in} = -180^\circ$
- ❑ Beyond this region, instability is linked to gain degradation




Open-Loop Gain Degradation

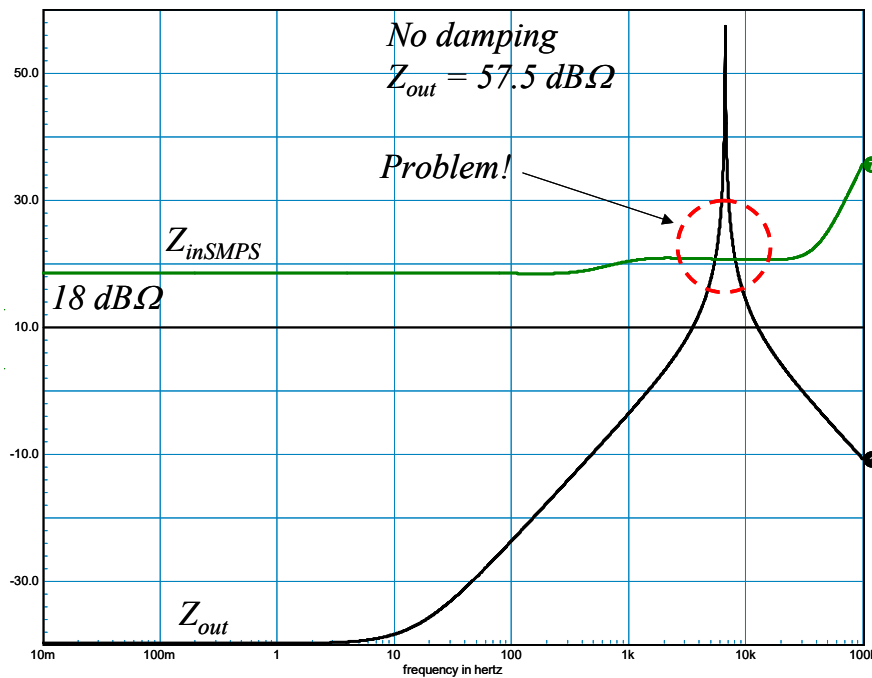- ❑ Here the EMI filter peaks at high frequency
- ❑ The open-loop is severely affected and stability is at stake



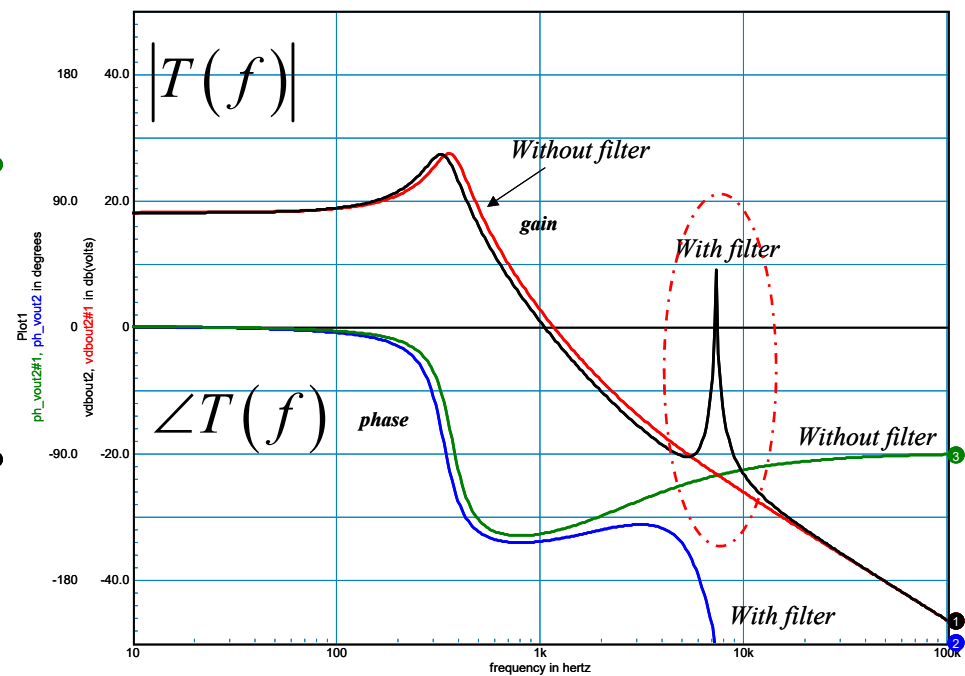Filter output impedance versus closed-loop buck input impedance.




Buck open-loop gain with and without input filter.



Evaluating How Loop Gain is Modified

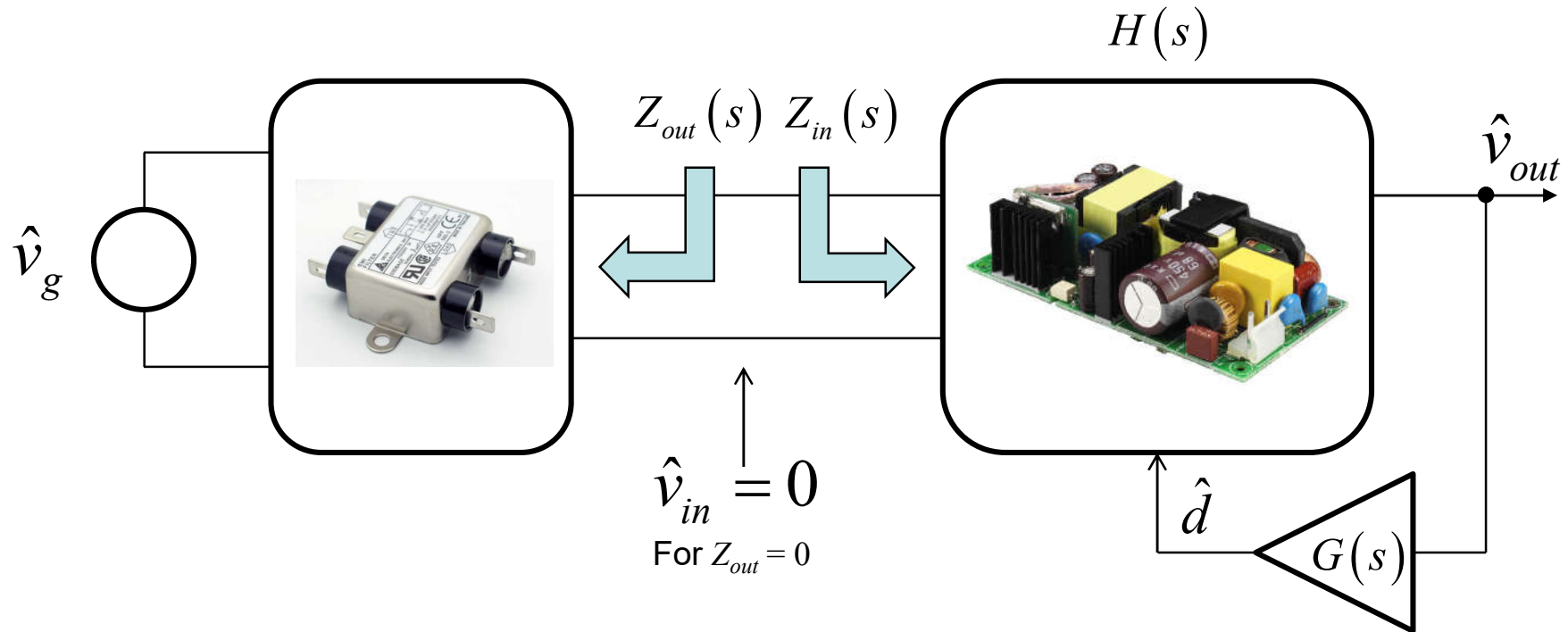
- The converter transfer function is evaluated at $Z_{out} = 0$



➔
$$T(s) = H(s)G(s) = \left. \frac{V_{out}(s)}{D(s)} \right|_{V_{in}(s)=0}$$


Considering the Filter Output Impedance

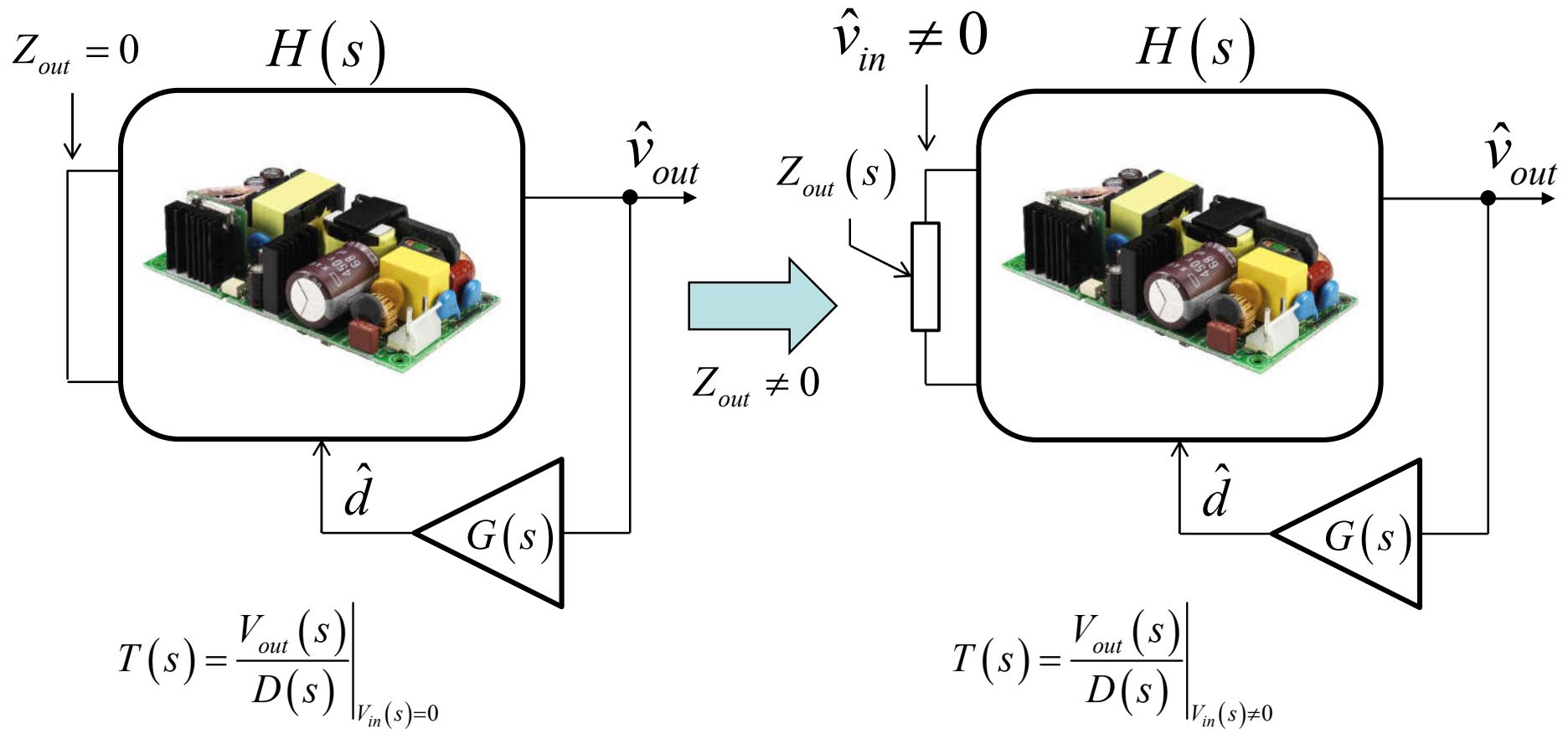- ❑ In reality, the EMI output impedance makes $Z_{out}(s) \neq 0$
- ❑ The converter ac input voltage is no longer zero



Extra Element Theorem to Help

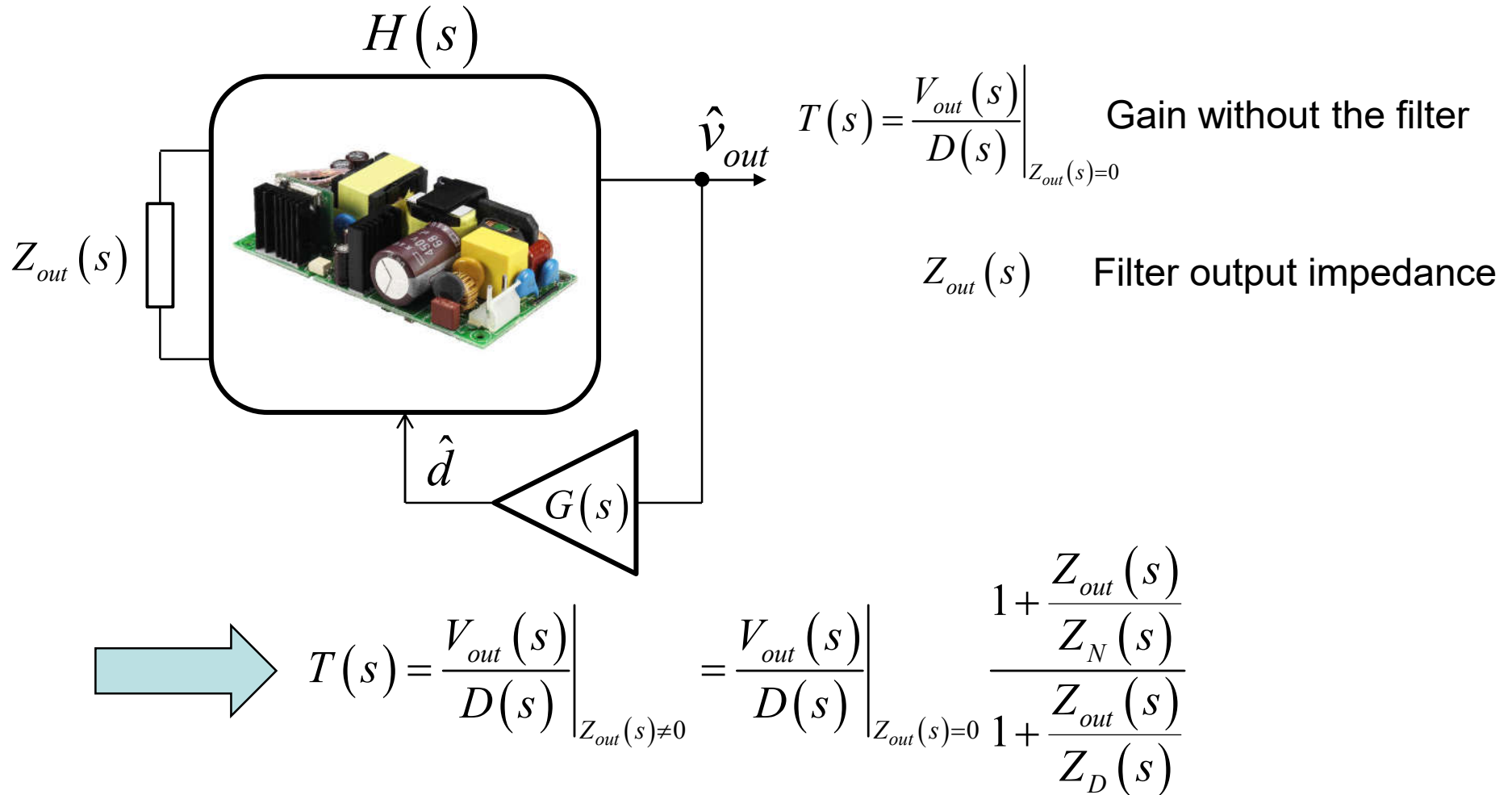- It can be shown how an EMI affects the open-loop gain:




What are Z_D and Z_N ?


□ Z_D and Z_N come from the Extra Element Theorem, EET

$Z_D(s) = Z_i(s) \Big|_{D(s)=0}$ \longrightarrow Open-loop input impedance

$Z_N(s) = Z_i(s) \Big|_{\hat{v}_{out}=0}$ \longrightarrow Input impedance for a nulled output

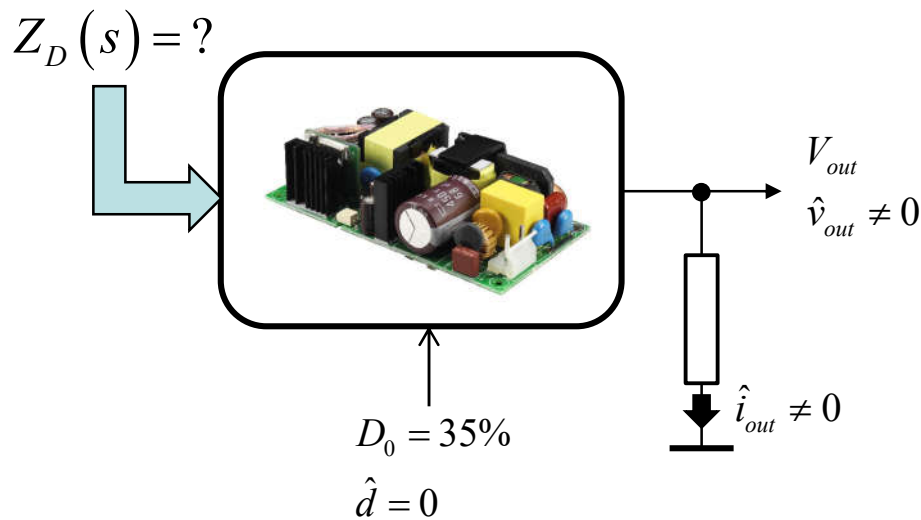

Open-loop input impedance

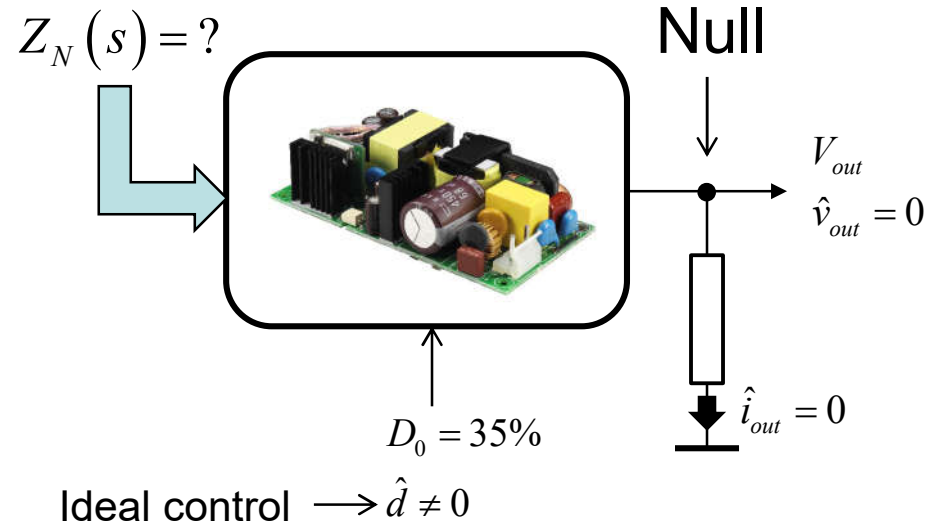

Input impedance for $V_{out}(s) = 0$

What are Z_D and Z_N for a Boost Converter?

- These values have already been derived

$$Z_N(s) = -D'^2 R \left(1 - \frac{sL}{D'^2 R} \right)$$

$$Z_D(s) = D'^2 R \left(\frac{1 + s \frac{L}{D'^2 R} + s^2 \frac{LC}{D'^2}}{1 + sRC} \right)$$


- The original loop gain (without filter) is untouched if

$$\frac{1 + \frac{Z_{out}(s)}{Z_N(s)}}{1 + \frac{Z_{out}(s)}{Z_D(s)}} \approx 1 \quad \Rightarrow \quad \begin{aligned} |Z_{out}(s)| &\ll |Z_N(s)| \\ |Z_{out}(s)| &\ll |Z_D(s)| \end{aligned}$$





Checking for Stability (1)

- ❑ You design the filter together with the converter
- ❑ Plot $|Z_{out}|$, $|Z_N|$ and $|Z_D|$ in the same graph
- ❑ Check that no overlap exists. If so, damp filter

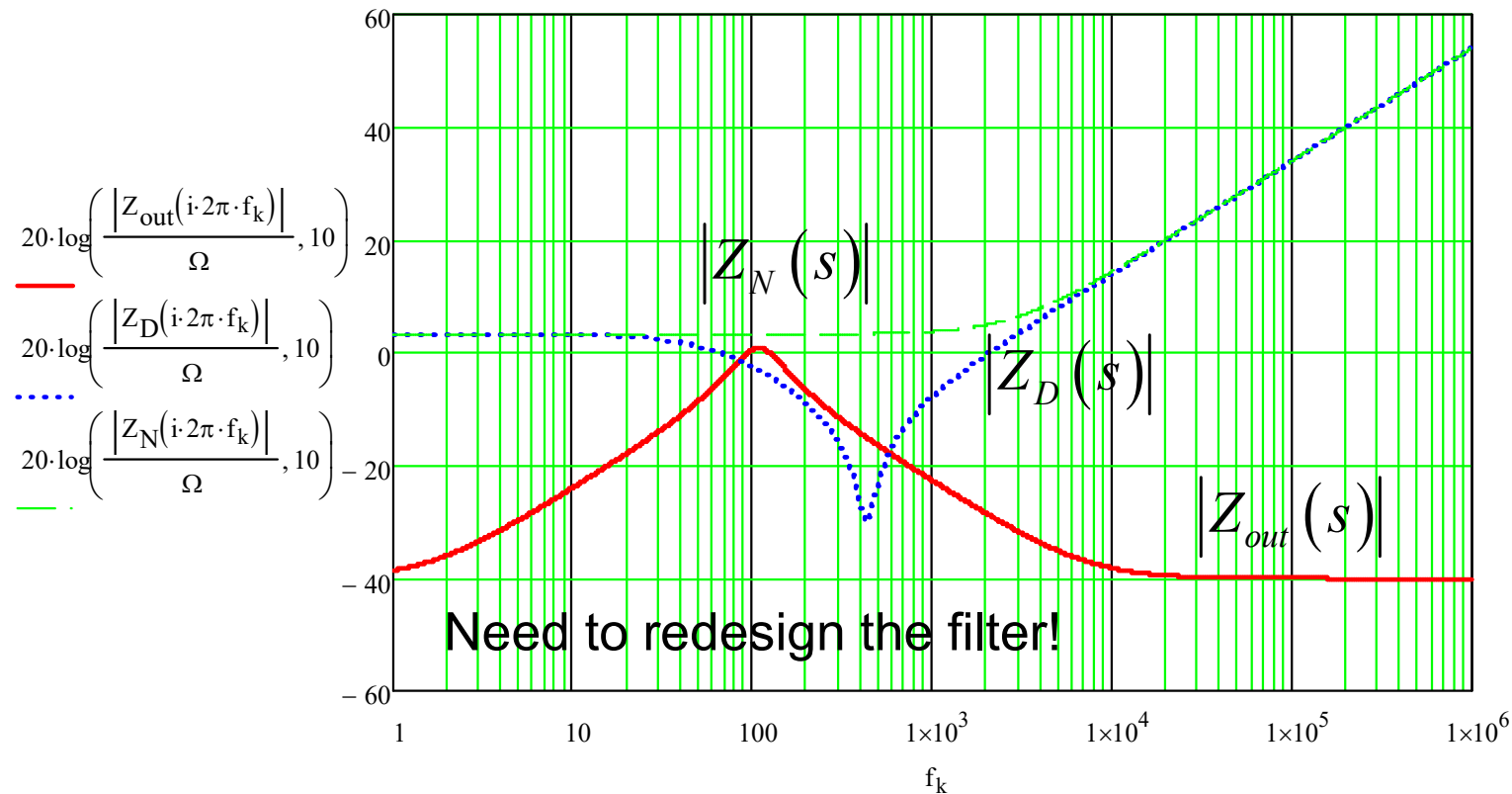

Checking for Stability (2)

- ❑ You design the filter after the converter
- ❑ Plot $|Z_{out}|$, $|Z_{in}|$ in the same graph
- ❑ Check that no overlap exists. If so, damp filter

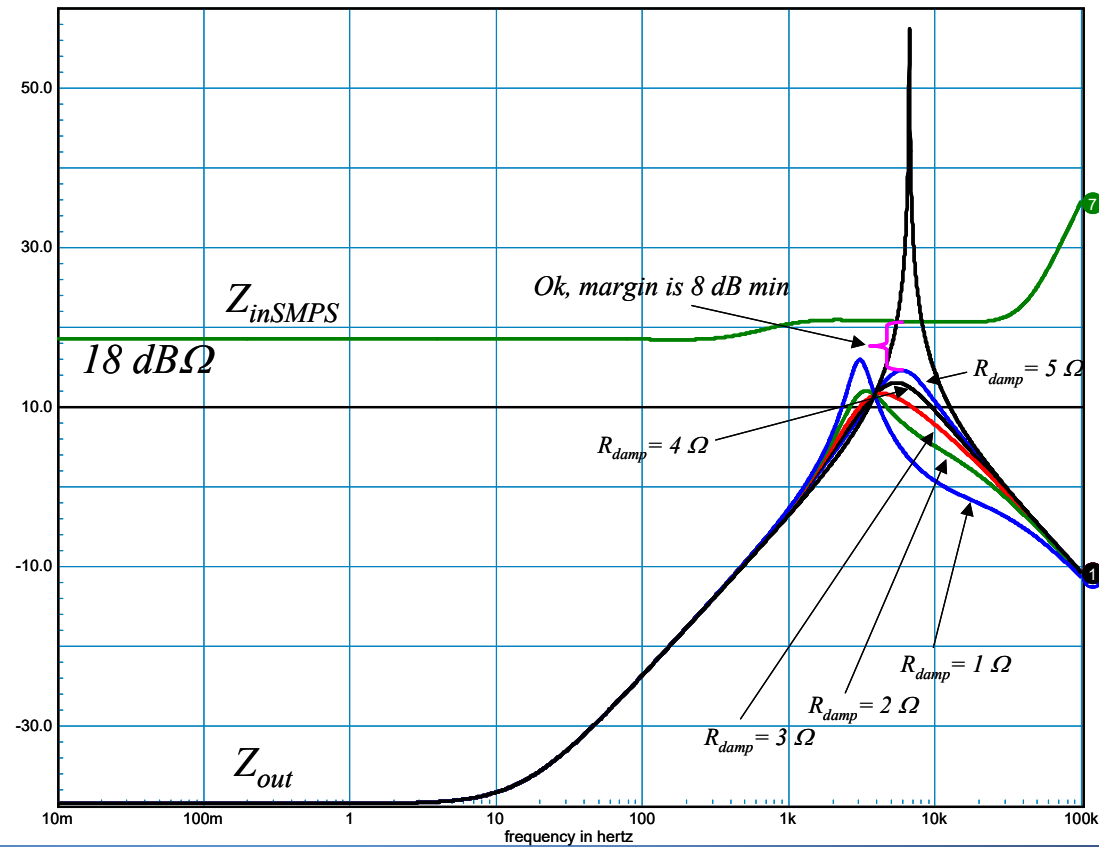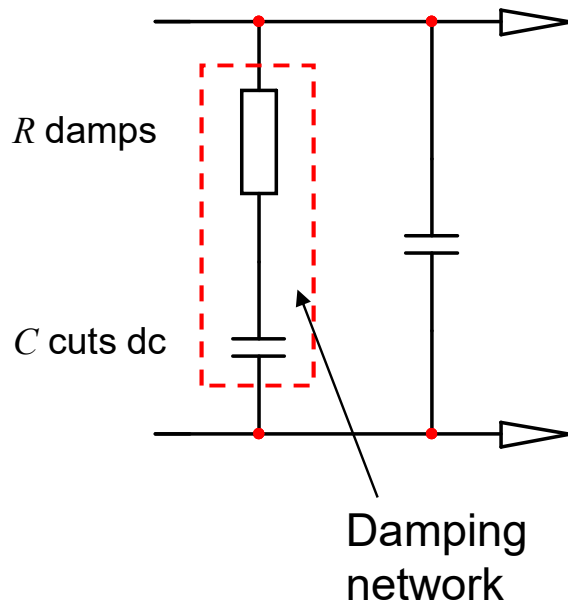


Course Agenda

- ❑ The PWW Switch Concept
- ❑ Small-Analysis in Continuous Conduction Mode
- ❑ Small-Signal Response in Discontinuous Mode
- ❑ EMI Filter Output Impedance
- ❑ **Cascaded Converters Operation**




Cascading Converters

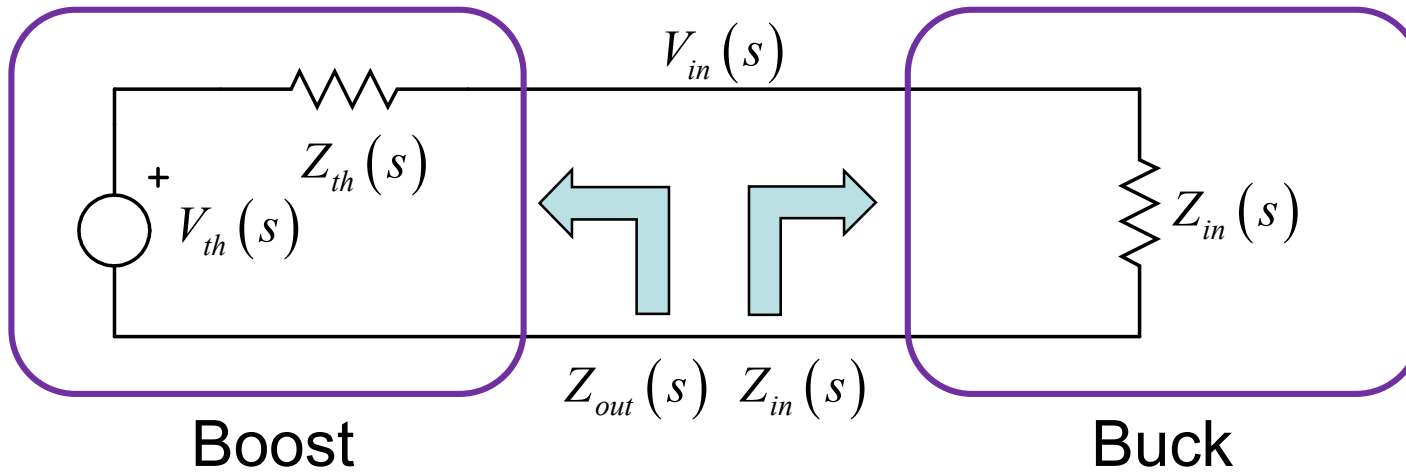- When cascading converters, impedances also matter



- The system can be modeled by a gain T_M
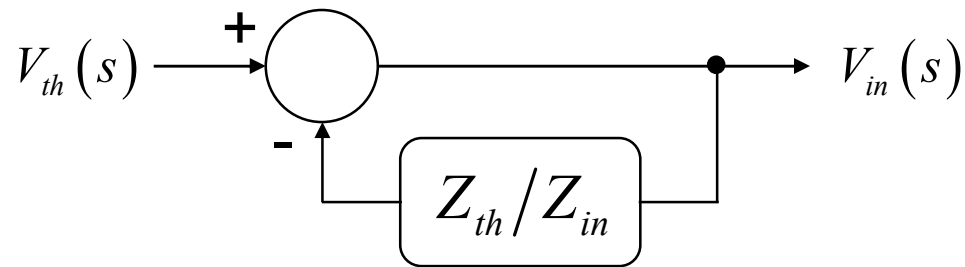
$$V_{in}(s) = V_{th}(s) \frac{1}{1 + \frac{Z_{th}(s)}{Z_{in}(s)}} \rightarrow T_M(s)$$



Check the Stability of the Minor Loop (1)

- The stability test requires the comparison of Z_{out} and Z_{in}
- The buck converter closed-loop input impedance is

$$\frac{1}{Z_{in}(s)} = \frac{1}{Z_N(s)} \frac{T(s)}{1+T(s)} + \frac{1}{Z_D(s)} \frac{1}{1+T(s)}$$

Low frequency $\xrightarrow{\quad}$ $Z_{in}(s) \approx Z_N(s)$
 $|T(s)| \gg 1$

- Z_N and Z_D are defined as

$$T(s) = H(s)G(s)$$

$$Z_D(s) = Z_i(s) \Big|_{D(s)=0} \quad \xrightarrow{\quad} \quad \text{Open-loop input impedance}$$


$$Z_N(s) = Z_i(s) \Big|_{V_{out}(s)=0} \quad \xrightarrow{\quad} \quad \text{Input impedance for } V_{out}(s) = 0$$

$$Z_D(s) = \frac{R}{D^2} \frac{1 + s \frac{L}{R} + s^2 LC}{1 + sRC} \quad Z_N(s) = -\frac{R}{D^2}$$




Use SPICE Models First

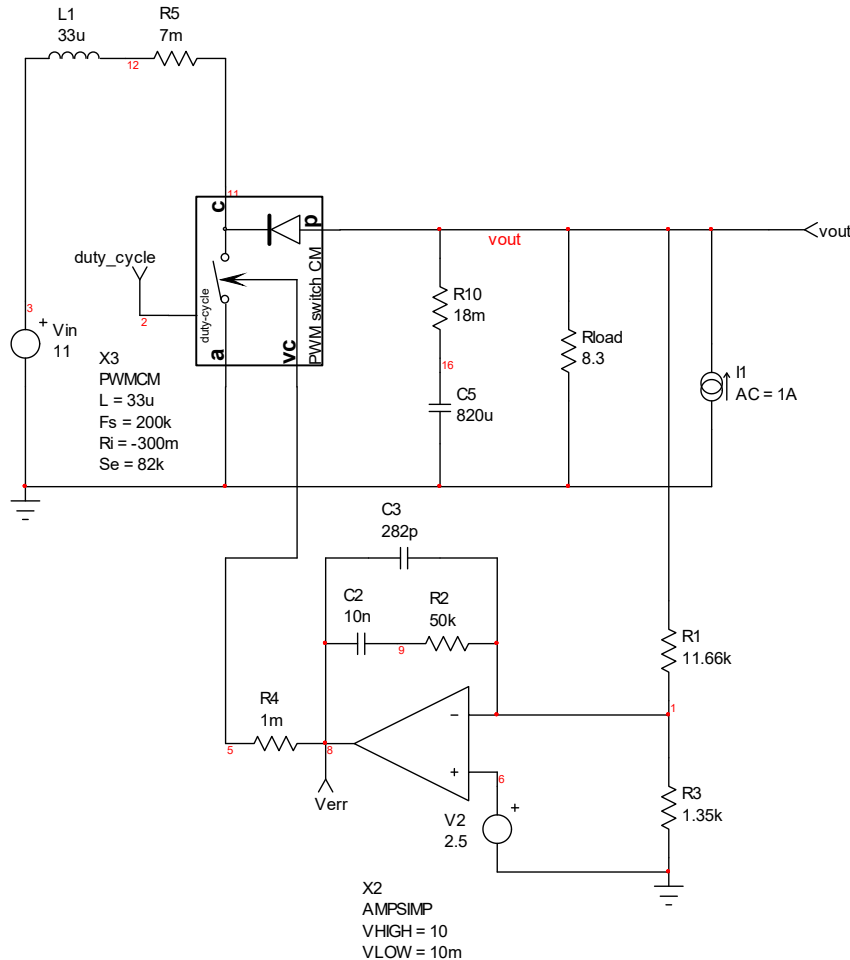□ Simulate the boost converter output impedance



Closed-loop Z_{out}

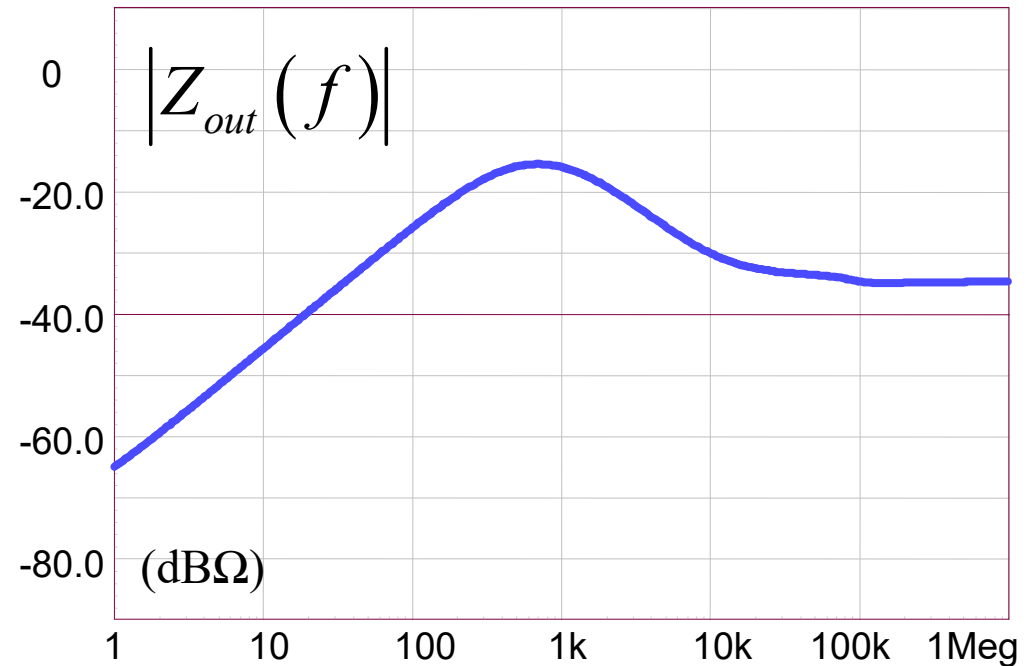


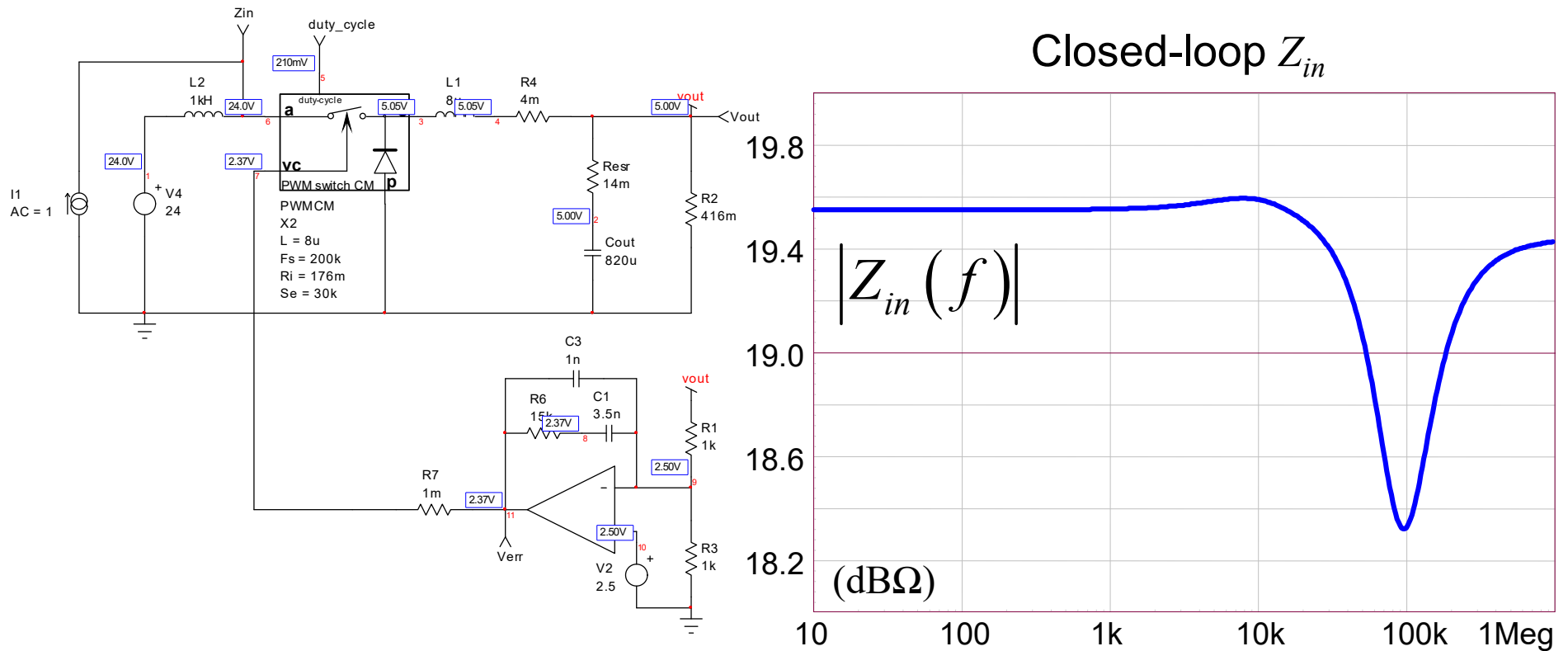11-15 V/24 V – 3 A



Use SPICE Models First


- Simulate the buck converter input impedance




24 V / 5 V – 12 A



Compare Magnitude Curves

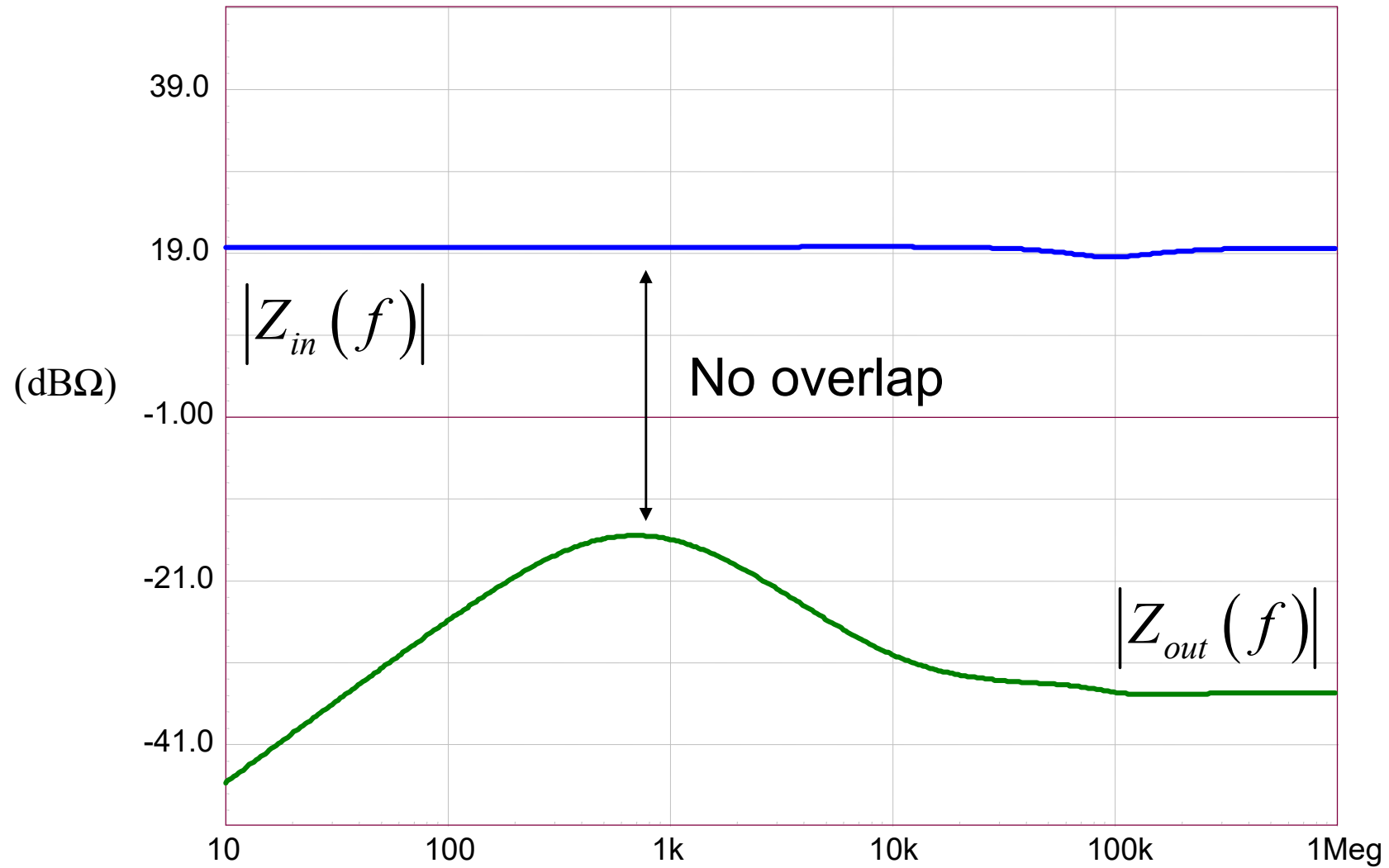


Compare Phase Curves

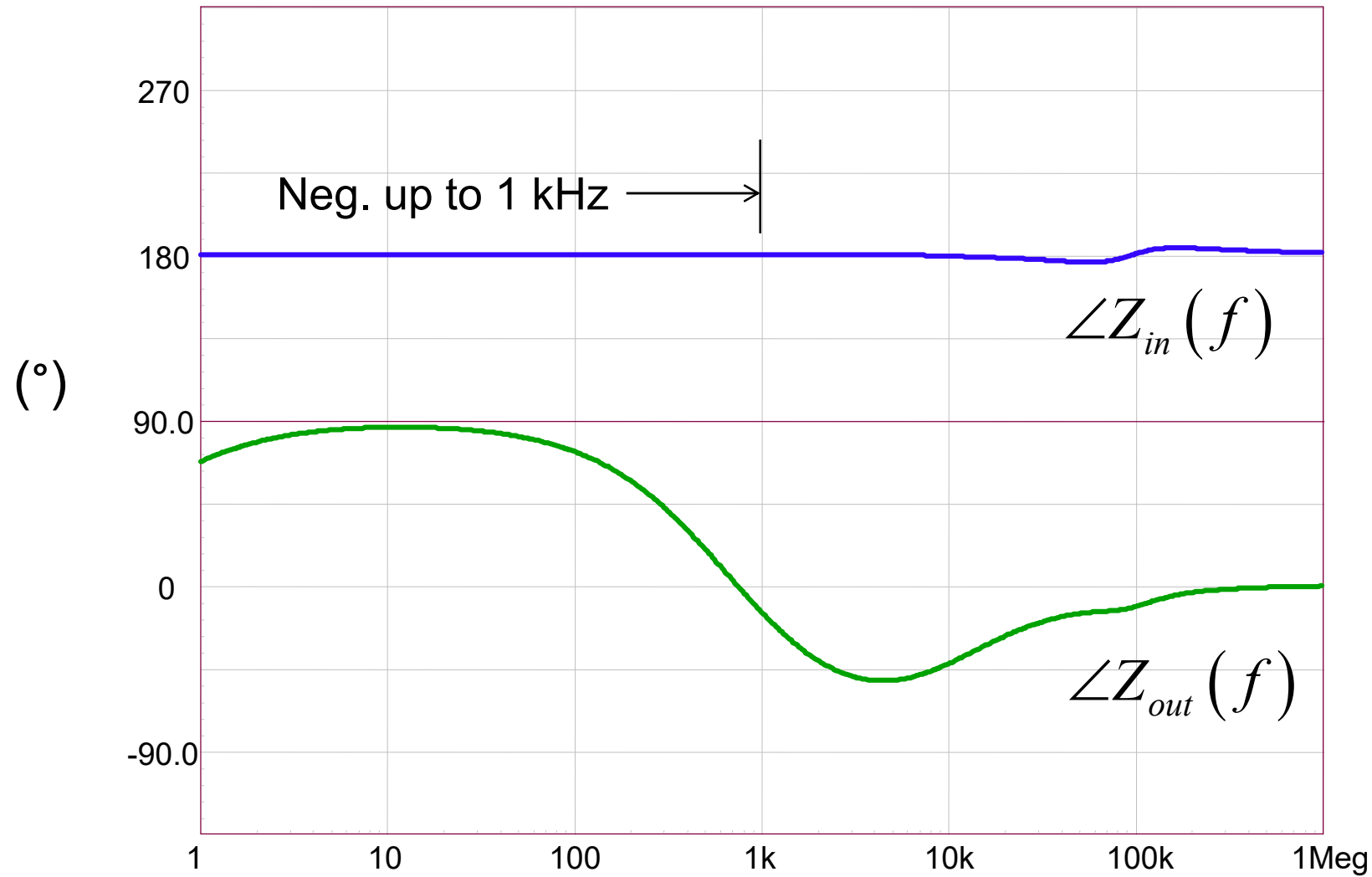


Check Minor Loop Gain

- There is no gain, $|Z_{out}| \ll |Z_{in}|$. The system is stable

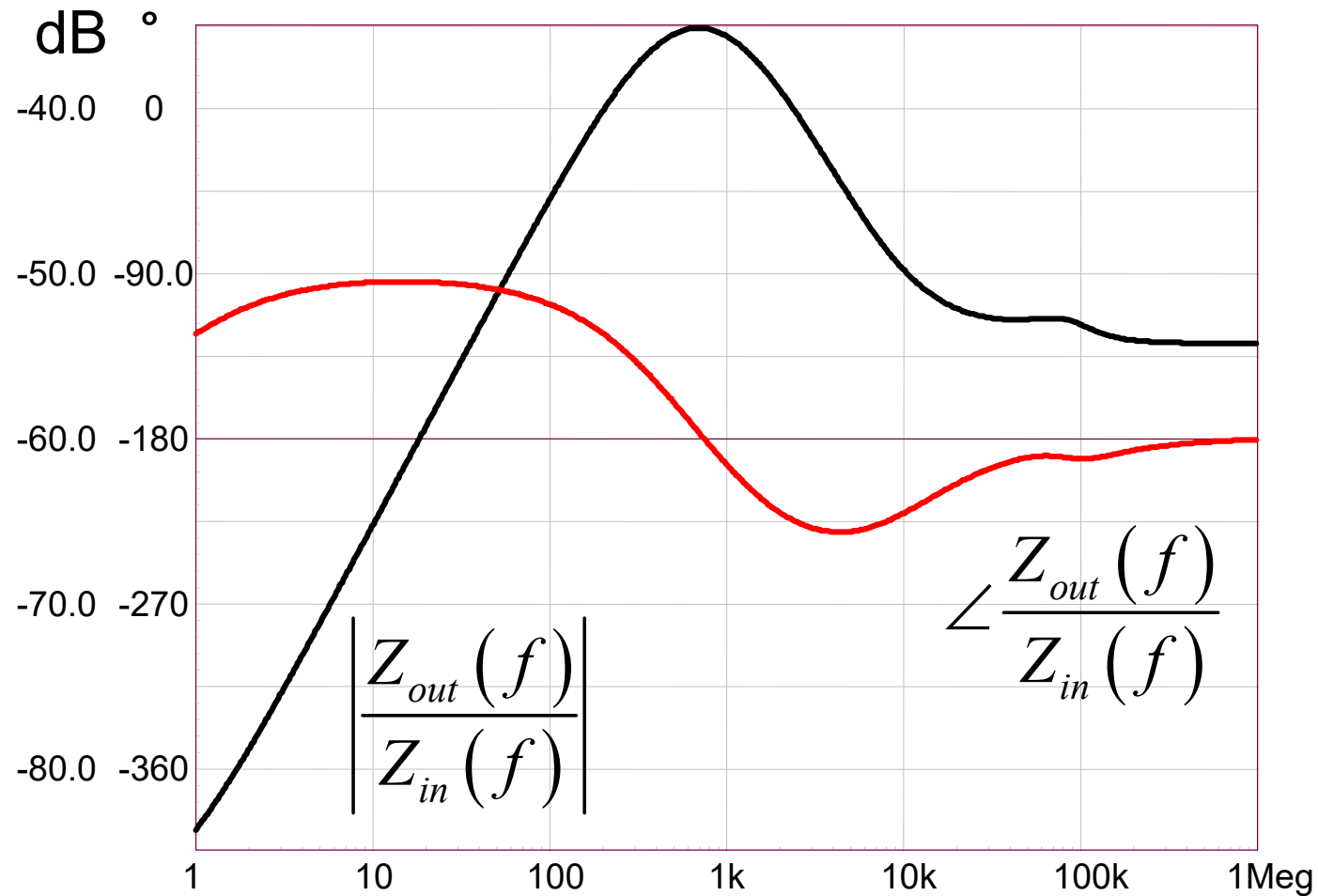


With Cascaded Converters

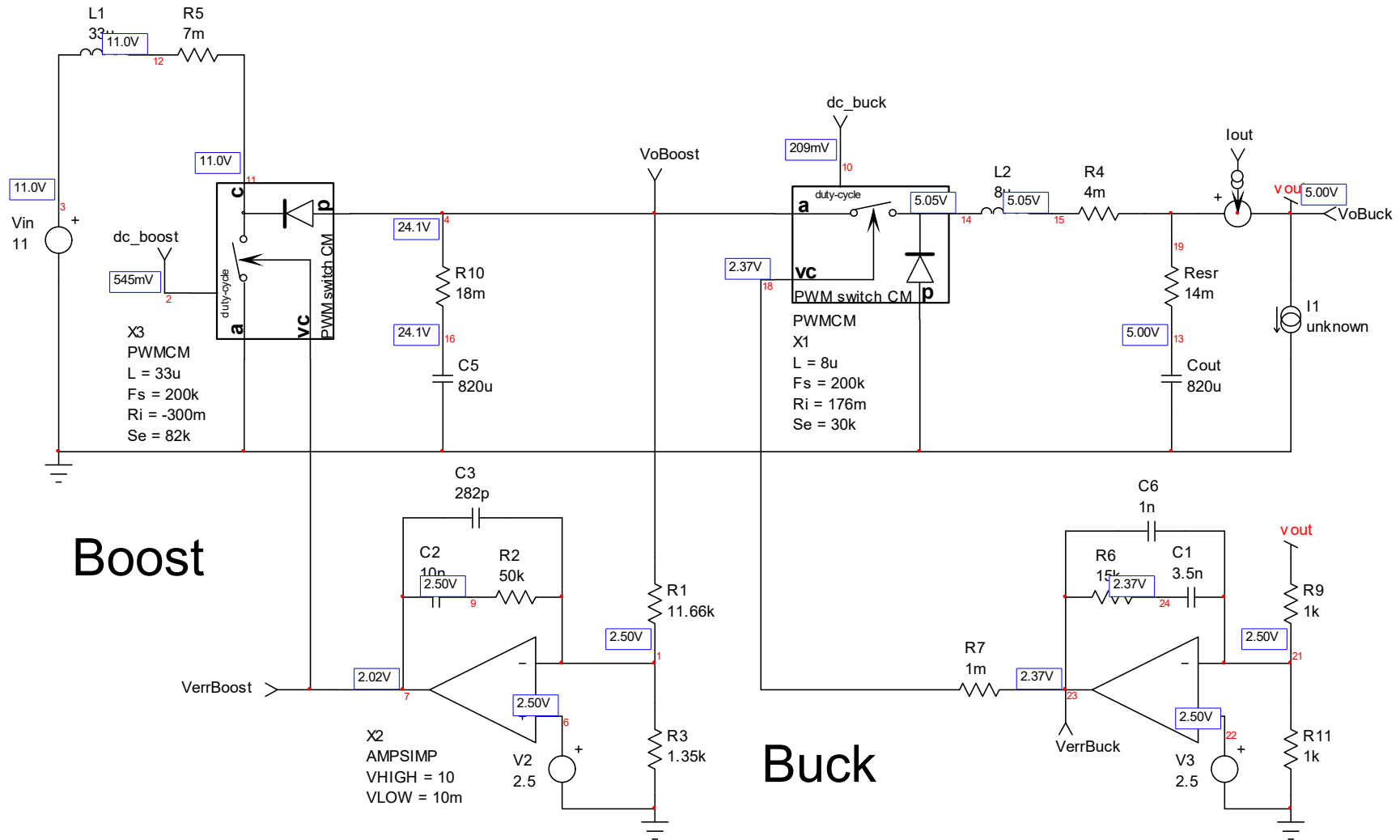

Check Transient Response

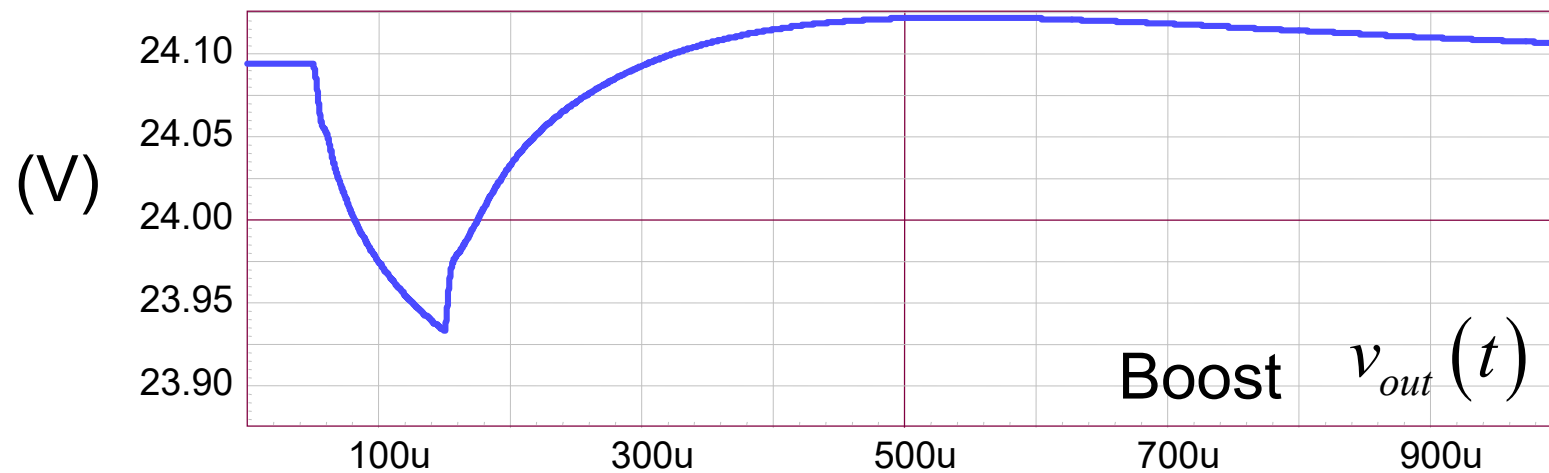- Transient response is good for the buck



Literature

“Fundamentals of Power Electronics”, R. Erickson, D. Maksimovic

“Designing Control Loops for Linear and Switching Power Supplies”, C. Basso

“Practical Issues of Input/Output Impedance Measurements”, Y. Panov,

M. Jovanović, IEEE Transactions on Power Electronics, 2005

“Physical Origins of Input Filter Oscillations in Current Programmed Converters”



, Y. Jang, R. Erickson, IEEE Transactions on Power Electronics, 1992

“Design Consideration for a Distributed Power System”, S. Schultz, B. Cho,

F. Lee, Power Electronics Specialists Conference, June 1990, pp. 611-617

“Input Filter Considerations in Design and Applications of Switching Regulators”,

R. D. Middlebrook, IAS 1976

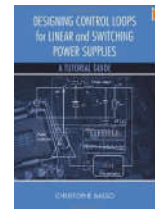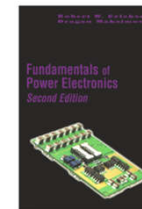

Conclusion

- ❑ The PWM switch model is an essential tool for modeling
- ❑ It can be used to derive small-signal response of a boost in CM
- ❑ Its SPICE implementation helps test various transfer functions
- ❑ It can be used to assess open- and closed-loop parameters
- ❑ Interactions with the EMI input filter can be analyzed
- ❑ Cascaded converters stability can be checked with the model
- ❑ Practical measurements on the bench must always be performed



Merci !
Thank you!
Xiè-xie!

