



ON Semiconductor®

Small-Signal Modeling and Analytical Analysis of Power Converters

Christophe Basso

IEEE Senior Member

Course Agenda

- ❑ Linear and Non-Linear Functions
- ❑ What is a Small-Signal Model?
- ❑ Fast Analytical Techniques at Work
- ❑ From a Switched to Linearized Model
- ❑ The CCM VM Small-Signal PWM Switch Model
- ❑ The DCM VM Small-Signal PWM Switch Model
- ❑ Peak Current Mode Control in Large Signal
- ❑ The CCM CM Small-Signal PWM Switch Model
- ❑ The DCM CM Small-Signal PWM Switch Model
- ❑ The PWM Switch in Boundary Mode





Course Agenda

- Linear and Non-Linear Functions**
- What is a Small-Signal Model?
- Fast Analytical Techniques at Work
- From a Switched to Linearized Model
- The CCM VM Small-Signal PWM Switch Model
- The DCM VM Small-Signal PWM Switch Model
- Peak Current Mode Control in Large Signal
- The CCM CM Small-Signal PWM Switch Model
- The DCM CM Small-Signal PWM Switch Model
- The PWM Switch in Boundary Mode



Linear and Nonlinear Functions

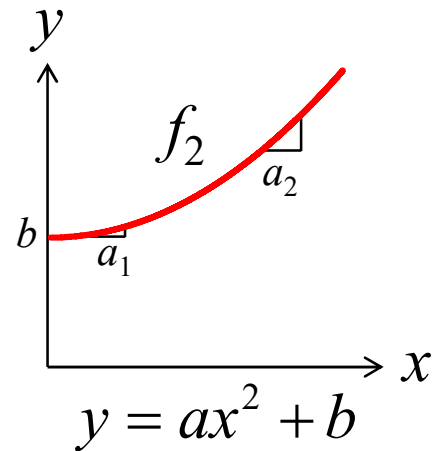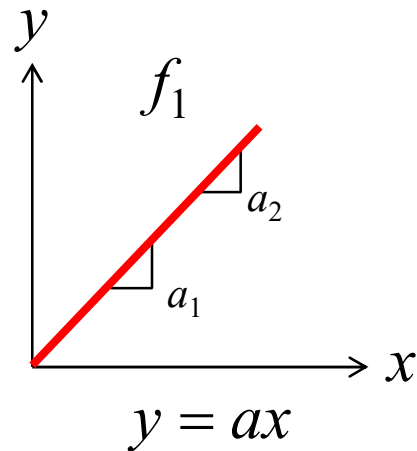- Functions or systems can be linear or non-linear



- The slope is constant along the considered section:

$$a_1 = a_2 \implies \text{the function } f_1 \text{ is linear}$$


- The slope is not constant along the considered section:

$$a_1 \neq a_2 \implies \text{the function } f_2 \text{ is non linear}$$


The Definition of Linear

- A linear system must fulfill the superposition principle
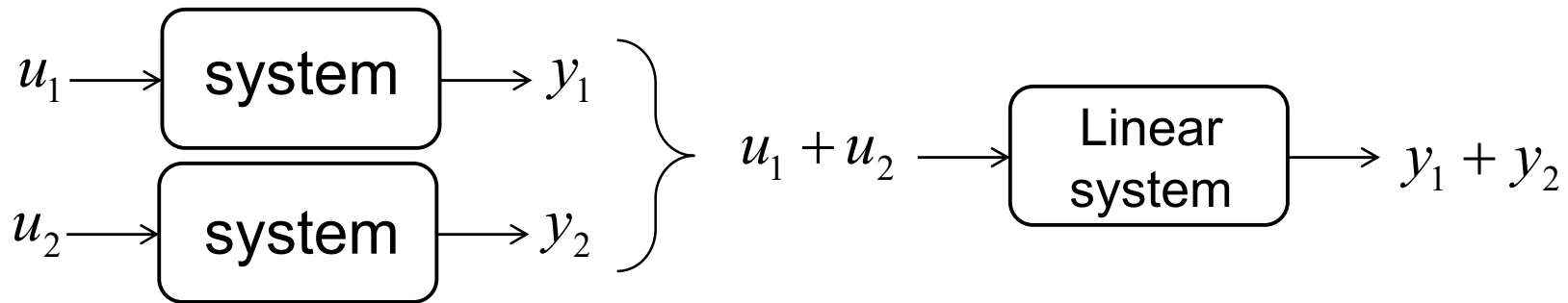
$$f(x + y) = f(x) + f(y) \quad \text{Additivity}$$




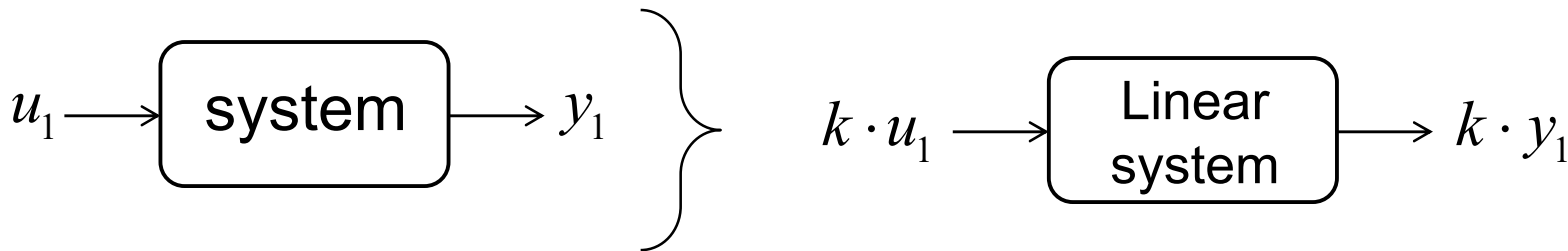
$$f(k \cdot x) = k \cdot f(x) \quad \text{Proportionality of homogeneity}$$



Time Invariance

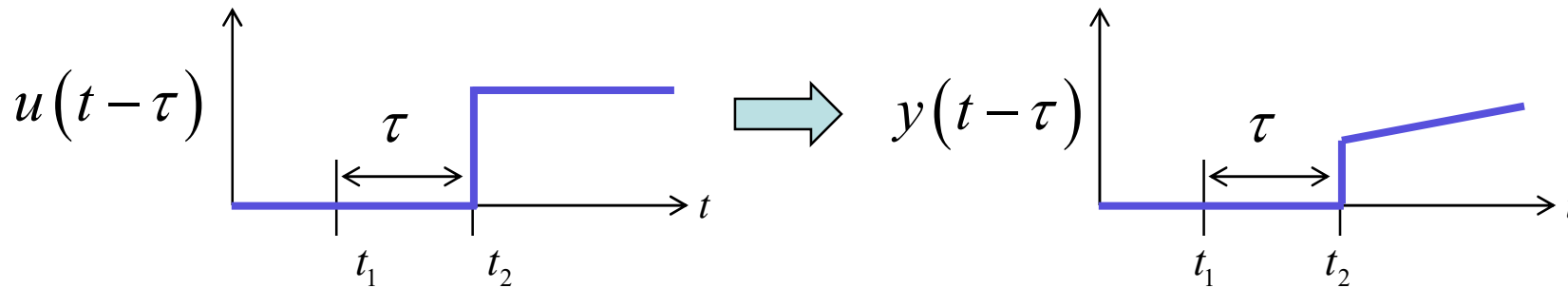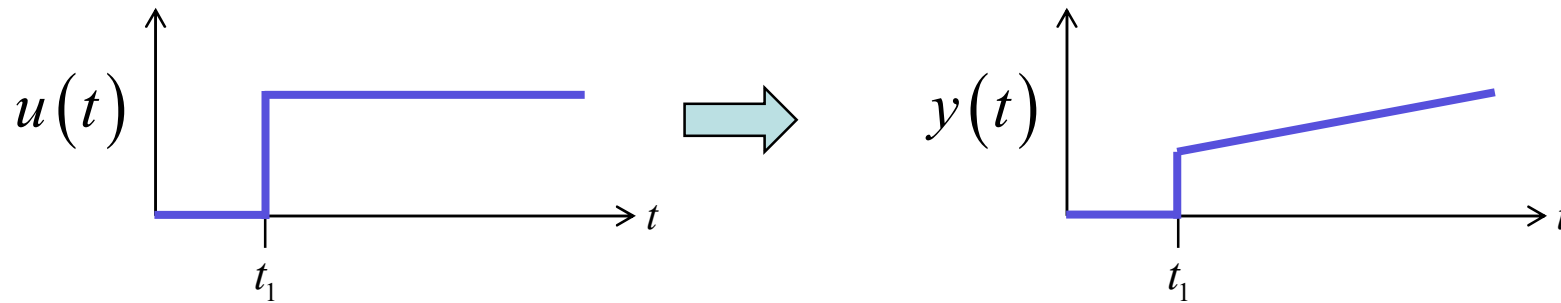- System properties do not change as time elapses



Superposition
Time invariance




Linear Time Invariant (LTI)






Who is Linear?

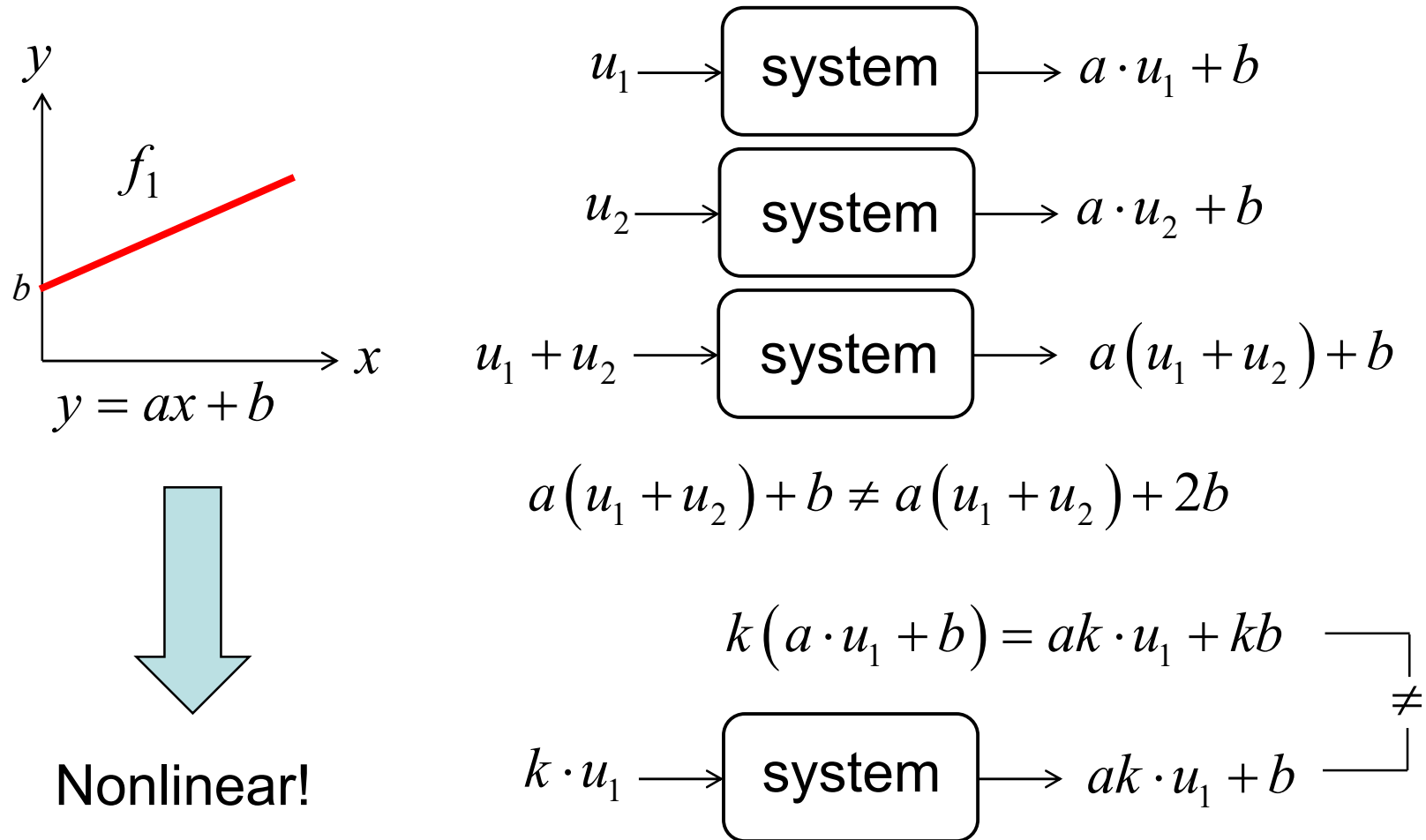- Check properties of the linear function with an offset




How to Linearize?

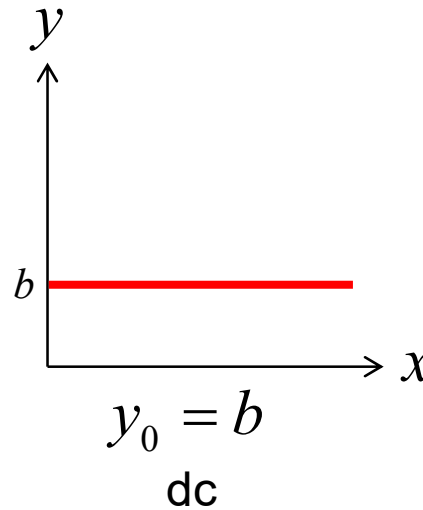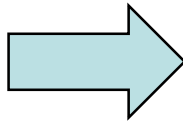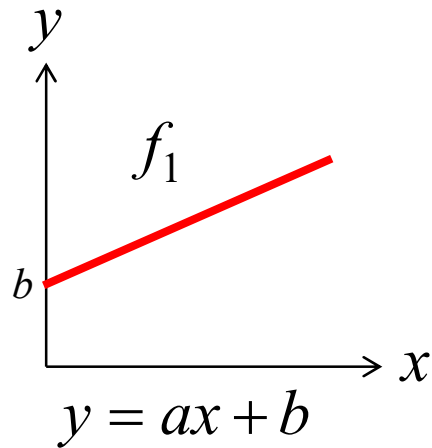
- Split the function in two parts, offset (dc) and curve (ac)



+

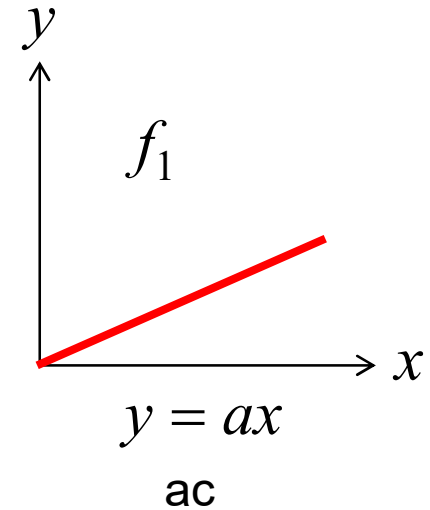
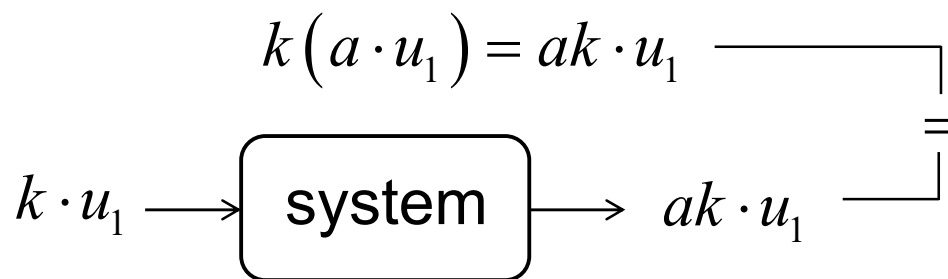
$$a(u_1 + u_2) = a \cdot u_1 + a \cdot u_2$$




} $y = ax$ is linear!



How Do You Calculate The Slope?

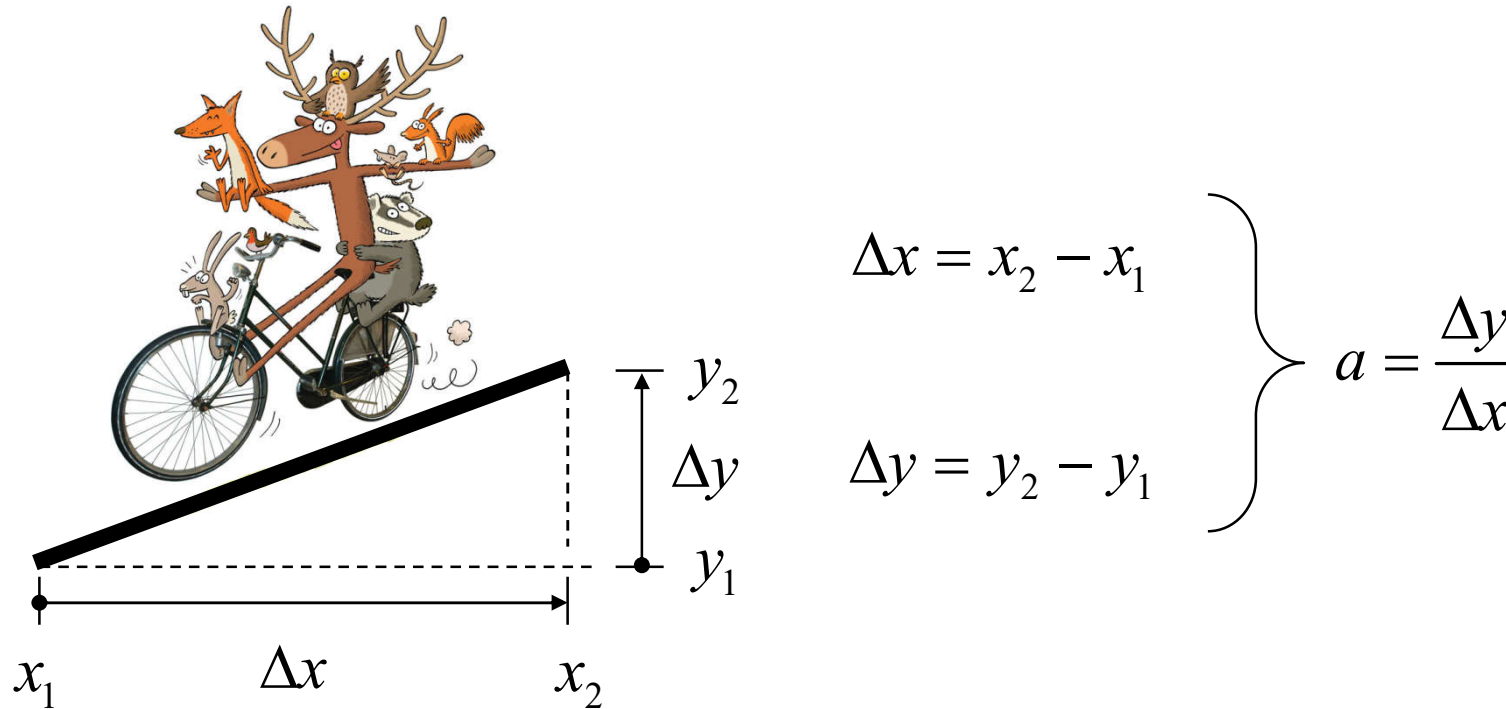
- Look at the vertical variation brought by a horizontal step



- As y_2 is larger than y_1 , the slope in this case is positive

Linearity in a Non-Linear Function

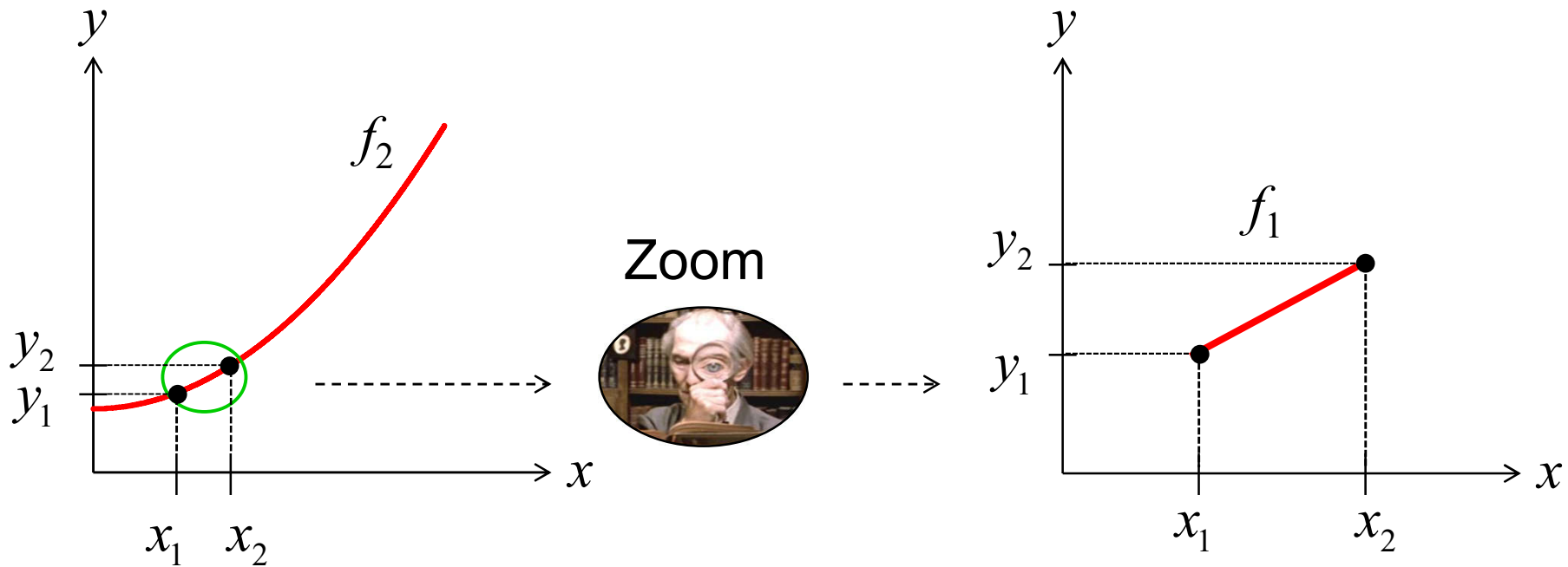- A non-linear function can be linear at an observation point




- $x_2 - x_1$ must be small enough to isolate a linear section
- Zooming further means having $x_2 - x_1$ close to each other



From Slope to Differentiation

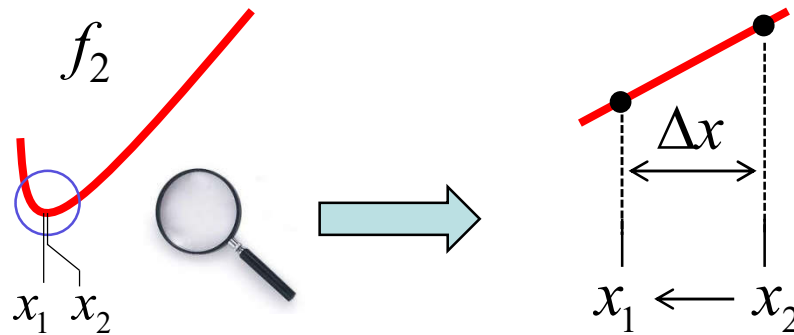- To see a linear zone Δy and Δx must be very small quantities




- When x_2 is close to x_1 , we have calculated the slope at x_1
- The slope at this point is called the derivative of f at x_1

$$f'(x_1) = \lim_{\Delta x \rightarrow 0} \frac{f(x_1 + \Delta x) - f(x_1)}{(x_1 + \Delta x) - x_1} \quad \begin{array}{c} \text{Also} \\ \text{noted} \end{array} \longrightarrow \frac{df(x)}{dx}$$

- Infinitesimal variations are noted dy and dx (Leibniz)

Tangent and Differentiation

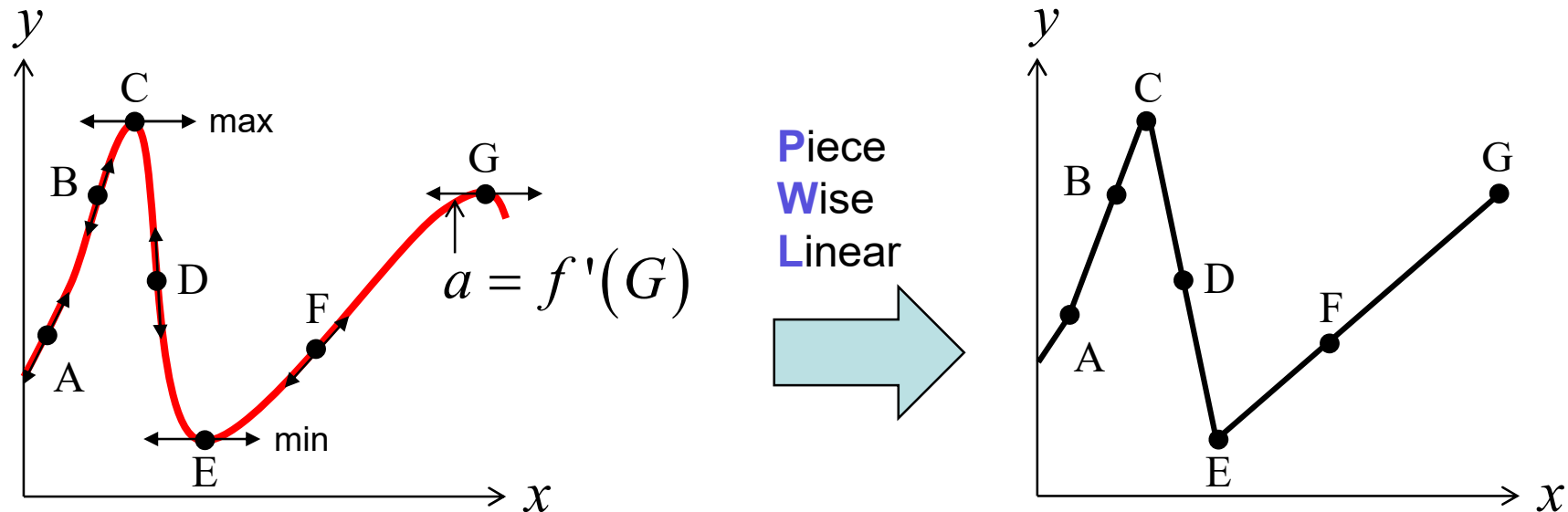
- A tangent is a graphical representation of a differentiation




- When the slope is zero, the function is minimum or maximum
- A PWL is a linear approximation of a non-linear function

Differentiation and Continuity

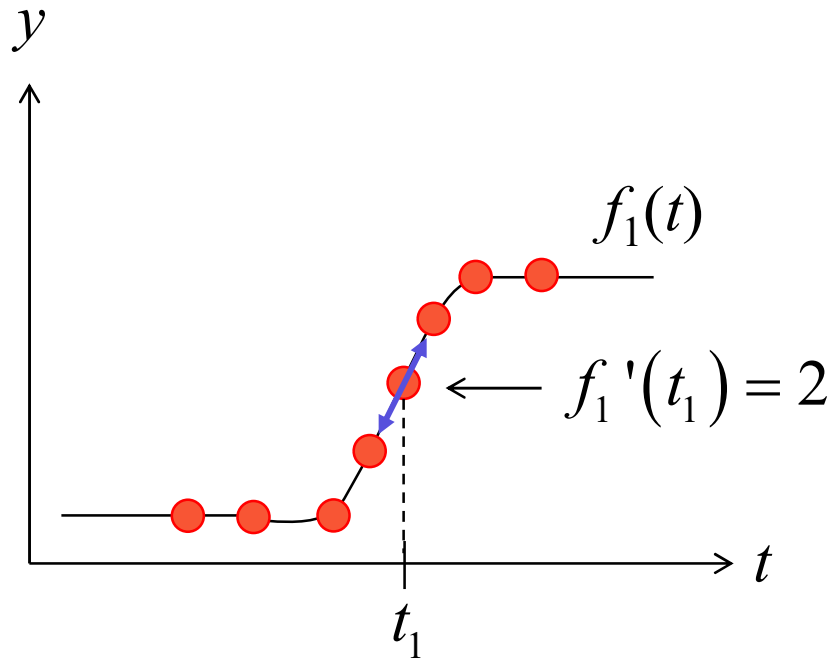- "A small input change gives a small output change"


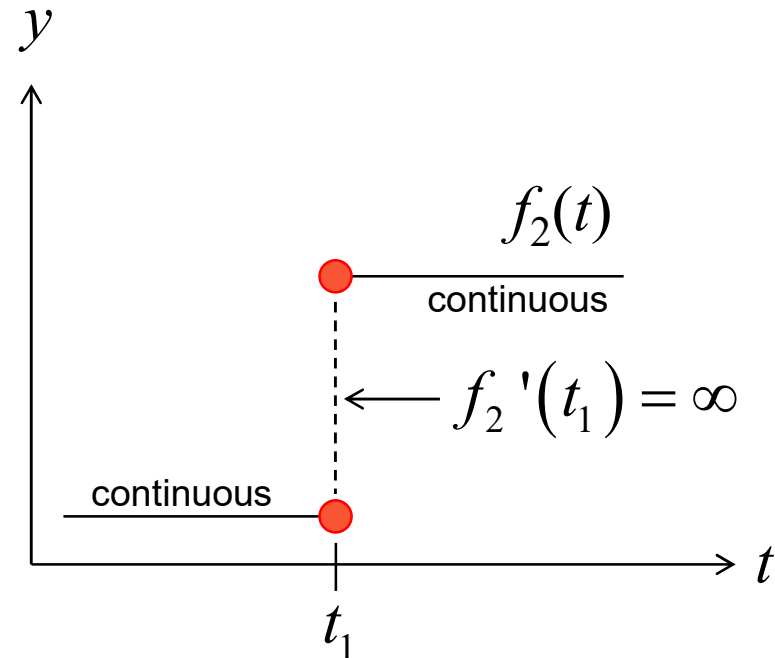
$$\lim_{t \rightarrow t_1} f_1(t) = f_1(t_1)$$




$$\lim_{t \rightarrow t_1} f_2(t) = ?$$


- Function f_2 is discontinuous at point t_1 : no finite differentiation

Why Do We Need Linear Equations?

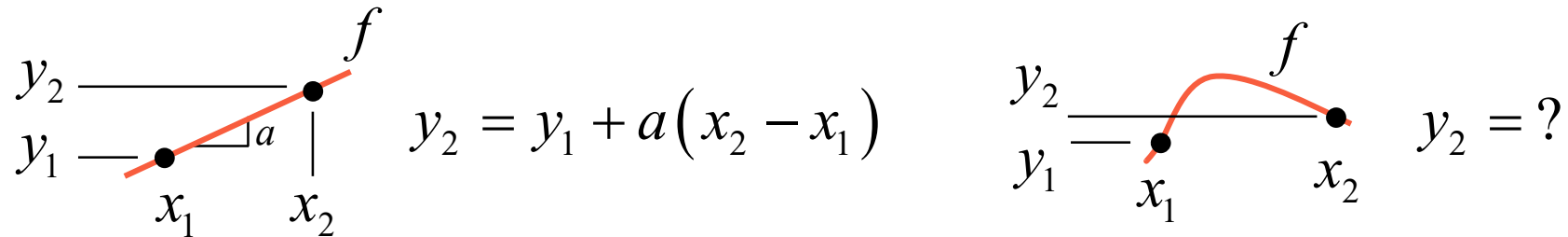- If the function is linear, we can extrapolate points positions



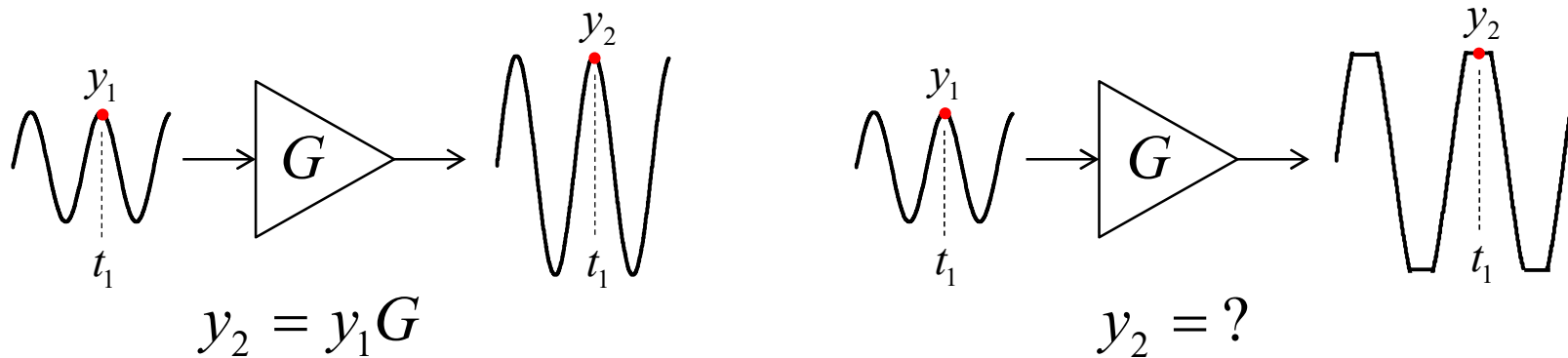
- Linearity implies no gain change during modulation



- Frequency response exploration requires linear blocks

What Does Small-Signal Operation Mean?

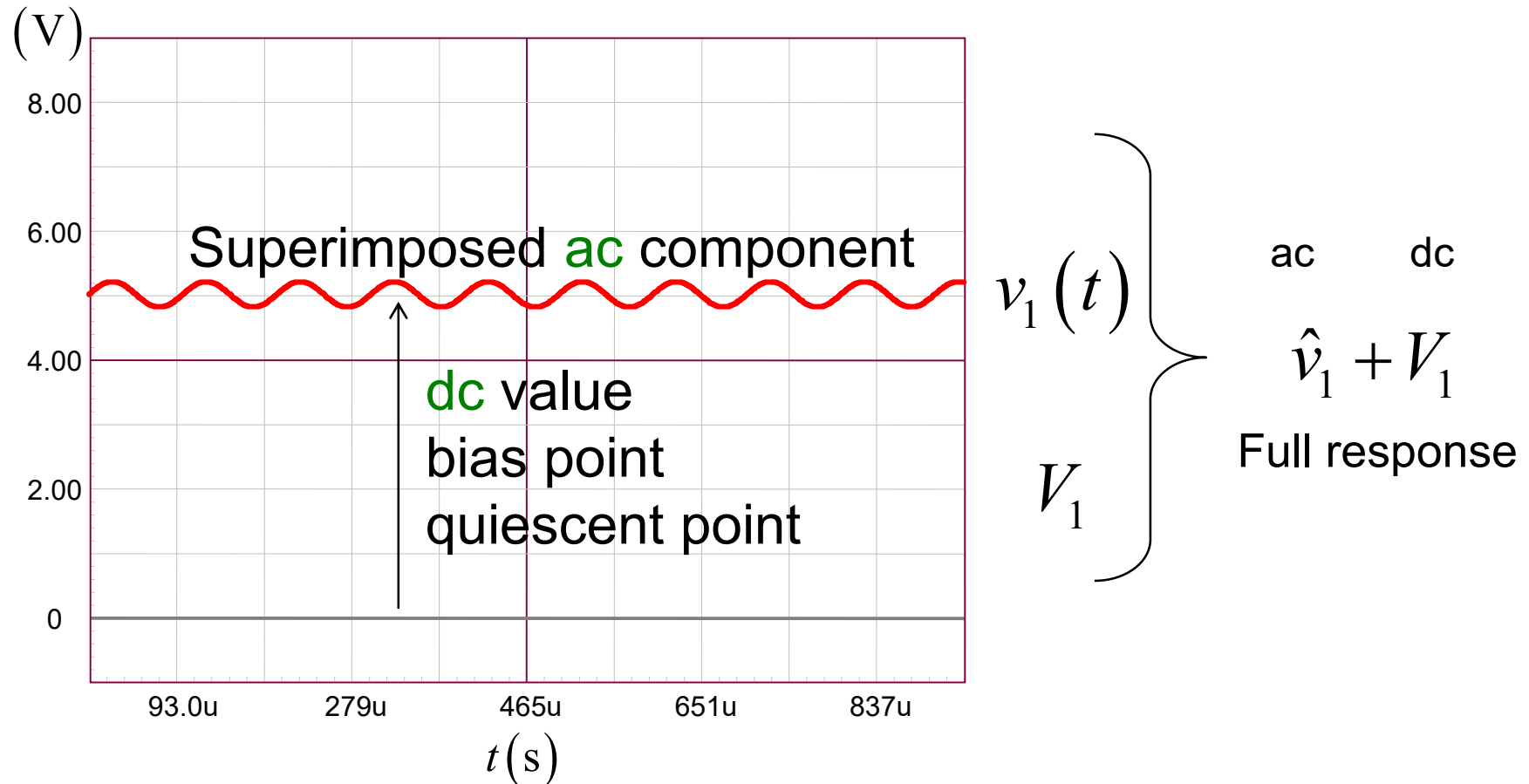
- A small amplitude ac component straddles a dc level




- The signal amplitude is small to maintain linearity

Bias Point and Linear Zone

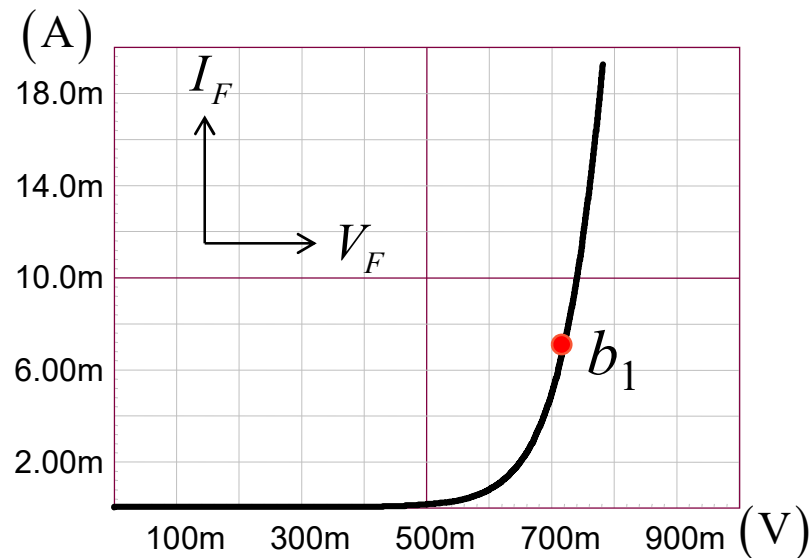□ Where does the device operate in its characteristics?


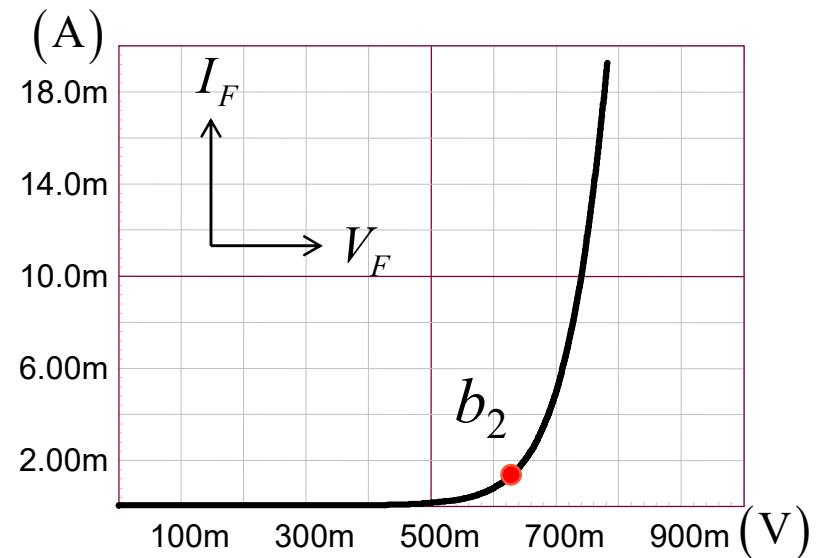
$$I_1 = 7 \text{ mA} \quad V_1 = 710 \text{ mV}$$




$$I_1 = 1.8 \text{ mA} \quad V_1 = 620 \text{ mV}$$

□ Bias point tells where the device stands in its dc response

□ Please note capital letters for dc values

Ac Modulation at Bias Point 1

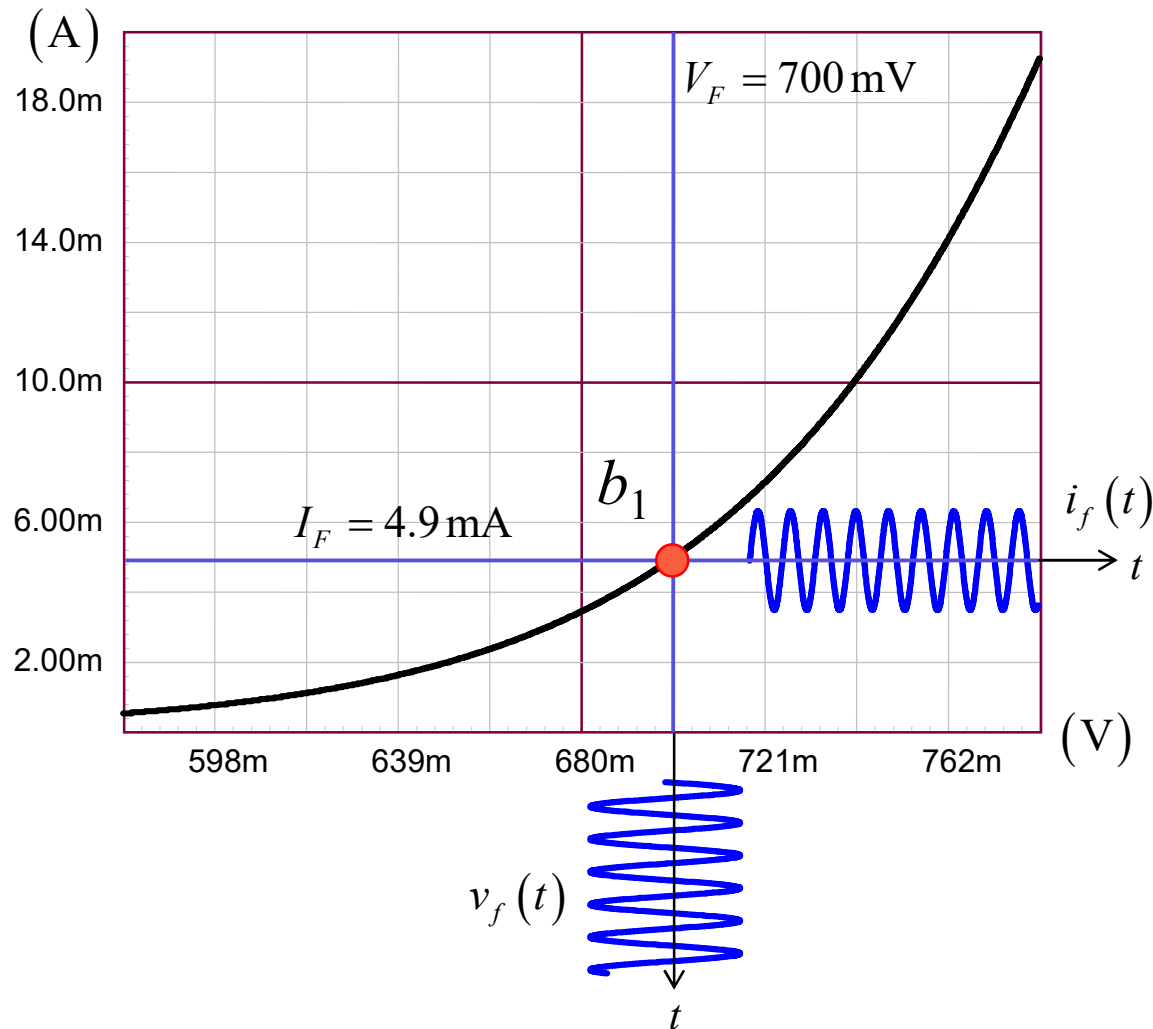- The ac modulation linearly moves the bias point



The modulation amplitude is small enough: system is in linear mode




Small-signal excitation



Ac Modulation at Bias Point 2

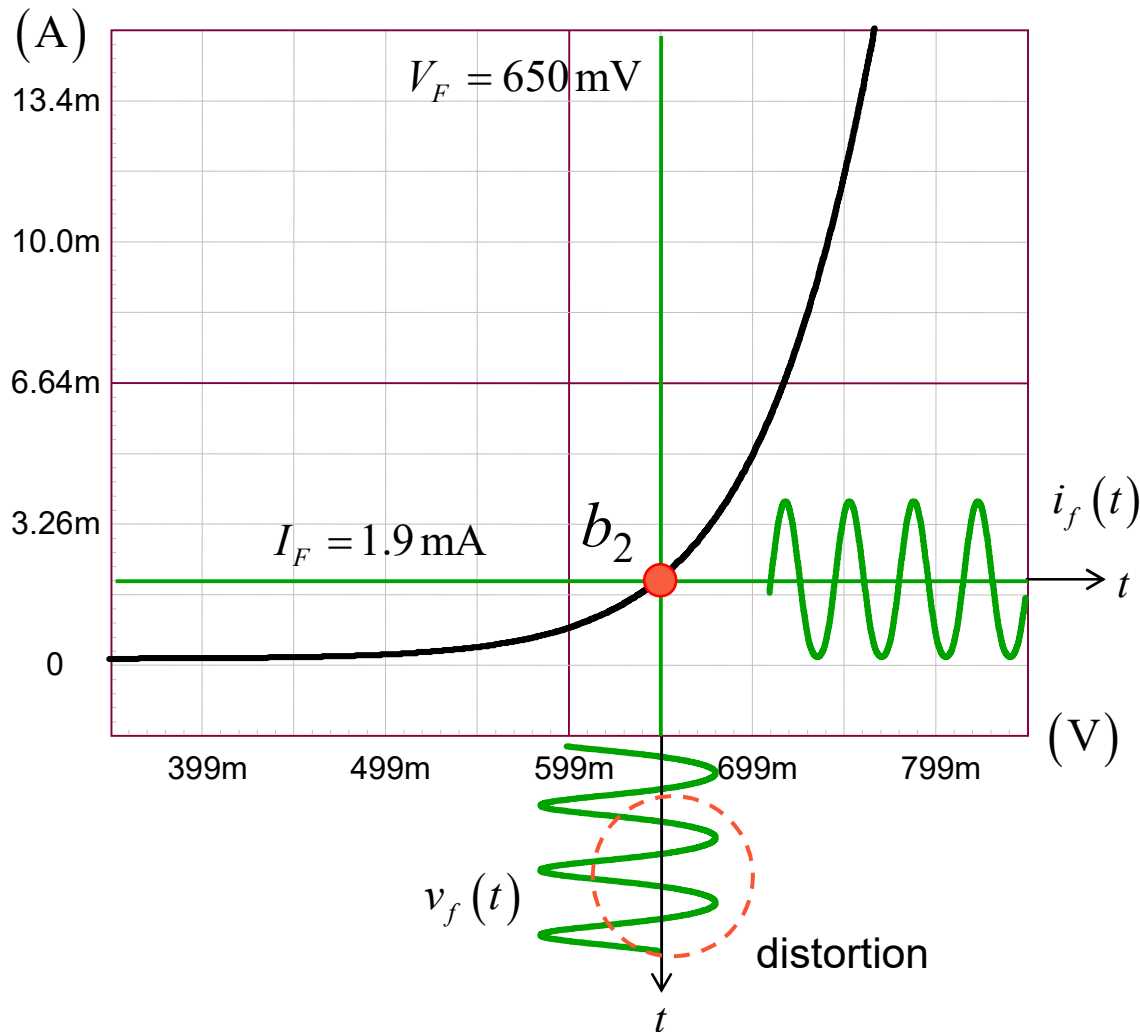- Bias point change brings distortion to the modulated signals



The modulation amplitude is too big: system is in nonlinear mode



Large-signal excitation

Course Agenda


- Linear and Non-Linear Functions
- What is a Small-Signal Model?**
- Fast Analytical Techniques at Work
- From a Switched to Linearized Model
- The CCM VM Small-Signal PWM Switch Model
- The DCM VM Small-Signal PWM Switch Model
- Peak Current Mode Control in Large Signal
- The CCM CM Small-Signal PWM Switch Model
- The DCM CM Small-Signal PWM Switch Model
- The PWM Switch in Boundary Mode



A Small-Signal Model

- How can we predict the ac response from the diode?
 1. We need a model accounting for the operating point
 2. It must reflect the relationship between I and V at this point.

We need a small-signal model

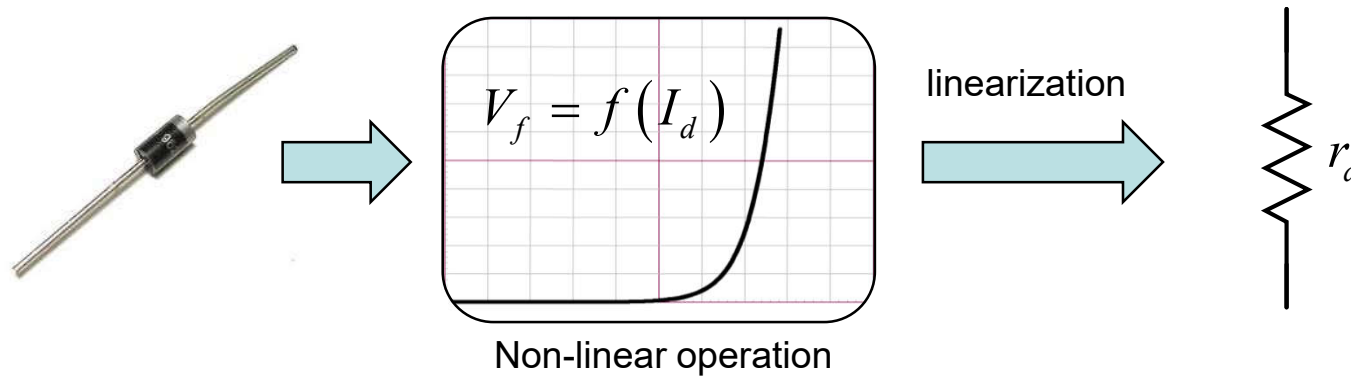

Methods to Derive a Small-Signal Model

□ Start from the non-linear equation

1. Perturb the equation: add a small ac variation to all variables
2. Re-arrange, sort dc and ac terms

□ The current in the diode obeys Shockley equation:

$$I_F = I_S \left(e^{\frac{V_F}{nV_T}} - 1 \right)$$

I_F the diode forward current

V_F the diode forward drop

V_T thermal voltage, ≈ 26 mV at 25 °C

n emission coefficient, varies between 1 and 2

I_S the reverse bias saturation current, few nA for a 1N4148



Method 1, Equation is Perturbed

- Considering the exponential much larger than 1, we have:

$$I_F = I_S \left(e^{\frac{V_F}{nV_T}} - 1 \right) \approx I_S e^{\frac{V_F}{nV_T}}$$

- Now, each variable is perturbed by a small ac variation
- The variation is considered small, the system remains linear

$$I = f(V_{in}, V_{out}) \xrightarrow{\text{perturb}} I + \hat{i} = f(V_{in} + \hat{v}_{in}, V_{out} + \hat{v}_{out})$$

- I_S , n and V_T are constant, perturb only I_F and V_F :

$$I_F + \hat{i}_F = I_S e^{\frac{V_F + \hat{v}_F}{nV_T}} = \underbrace{I_S e^{\frac{V_F}{nV_T}}}_{I_F} e^{\frac{\hat{v}_F}{nV_T}} = I_F e^{\frac{\hat{v}_F}{nV_T}}$$

Method 1, Equation is Perturbed

- Use the Padé approximant of order 1: $e^x \approx 1 + x$

$$\underbrace{I_F + \hat{i}_F}_{\text{Full response}} = I_F \left(1 + \frac{\hat{v}_F}{nV_T} \right) = \underbrace{I_F}_{\text{dc}} + \underbrace{I_F \frac{\hat{v}_F}{nV_T}}_{\text{ac}}$$


- Isolate the ac term

$$\hat{i}_F = I_F \frac{\hat{v}_F}{nV_T} \longrightarrow r_d = \frac{\hat{v}_F}{\hat{i}_F} = \frac{nV_T}{I_F} [\Omega]$$

- r_d is the small-signal model of the diode at a current I_F

Method 1, Equation is Perturbed

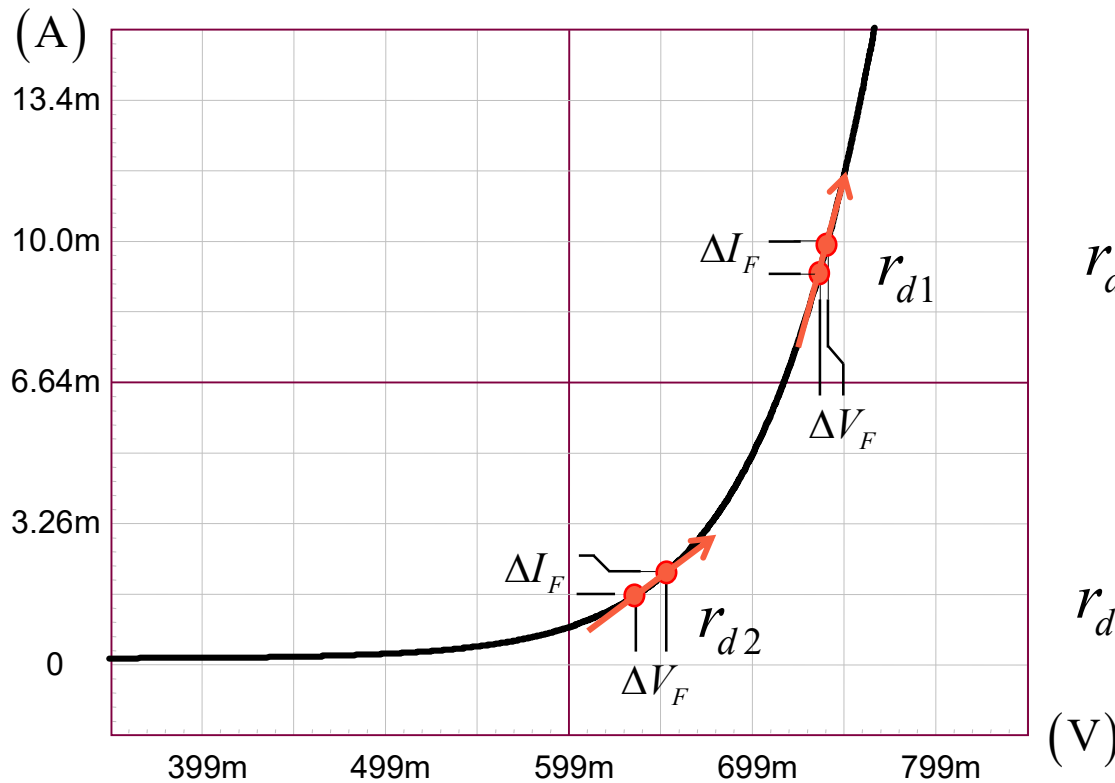- The dynamic resistance r_d is the tangent slope




$$r_{d1} = \left. \frac{\Delta V_F}{\Delta I_F} \right|_{I_{F1}}$$

$$r_{d2} = \left. \frac{\Delta V_F}{\Delta I_F} \right|_{I_{F2}}$$


- It is evaluated at a given operating point

Replace the Nonlinear Model

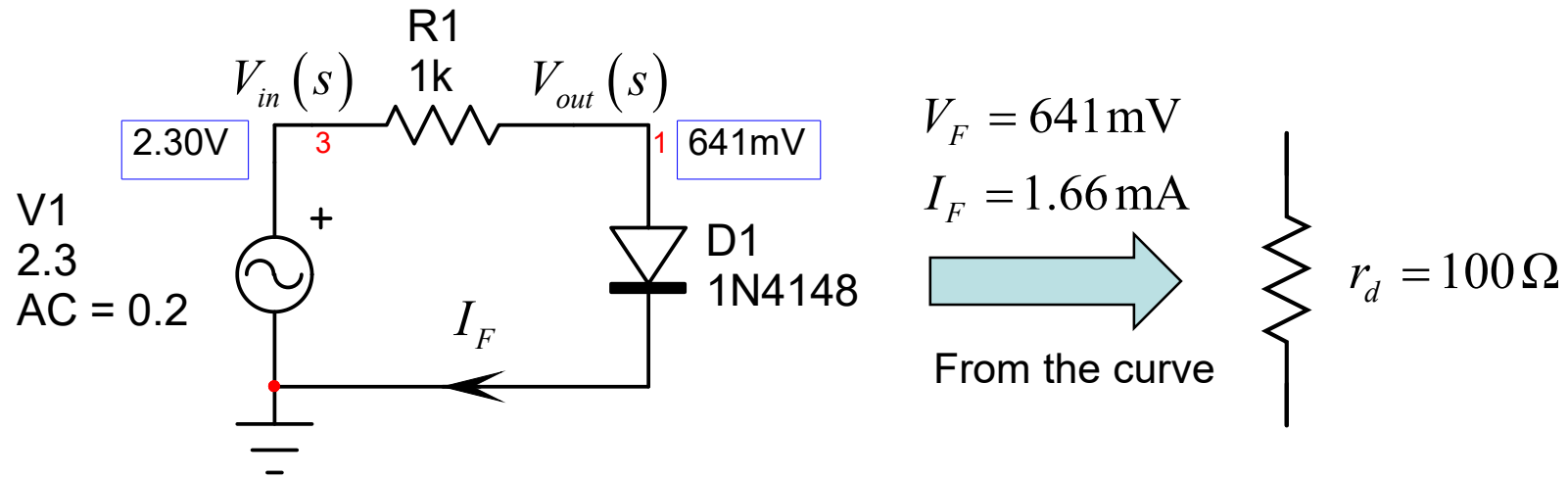- For the transfer function, compute the small-signal model




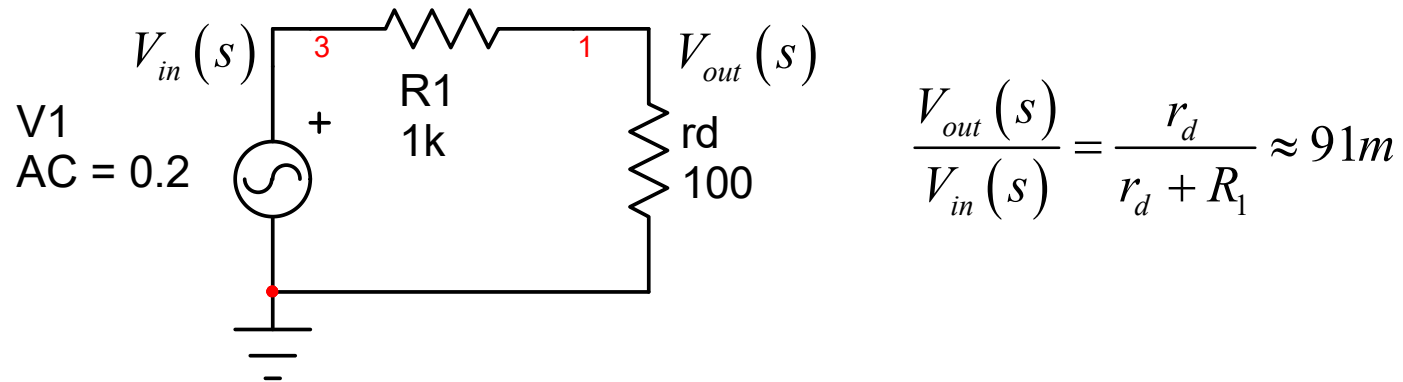- Plug it into the circuit and solve the equations



Method 2, Use Partial Differentiation

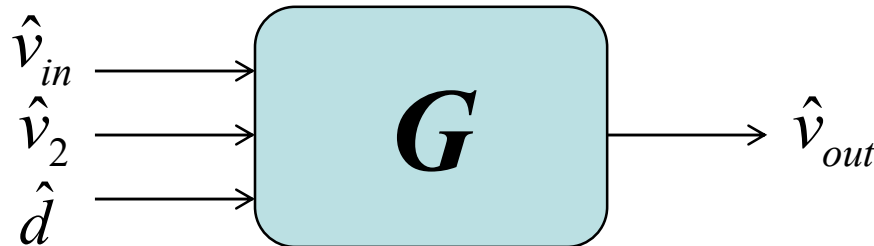- ❑ Sometimes, sorting out ac and dc equations is tricky
- ❑ Partial derivative is an easy way to get ac-only terms
- ❑ There is an analogy with the superposition theorem



- ❑ You compute the output value while 2 inputs are zero

$$\hat{v}_{out} = G_{V_{out}, V_{in}} \Big|_{V_2, d} \hat{v}_{in} + G_{V_{out}, V_2} \Big|_{V_{in}, d} \hat{v}_2 + G_{V_{out}, d} \Big|_{V_{in}, V_2} \hat{d}$$

- ❑ The total response is the sum of the individual responses

Partial Differentiation

□ A function depends on multiple variables $f(x, y, z)$

□ We can calculate the rate of change of this function when:

- x varies while y and z are constant $\frac{df(x)}{dx}$
- y varies while x and z are constant $\frac{df(y)}{dy}$
- z varies while x and y are constant $\frac{df(z)}{dz}$

□ Mathematically, we perform a partial differentiation, noted:

$$\begin{array}{l} \text{Total rate} \nearrow \\ \text{of change} \end{array} df = \frac{\partial f}{\partial x} dx + \frac{\partial f}{\partial y} dy + \frac{\partial f}{\partial z} dz$$

Partial rates
of change



Partial Differentiation

- With one variable, partial and total derivatives are similar

$$f'(x) = \frac{df(x)}{dx} = \frac{\partial f(x)}{\partial x}$$

- Partial derivative is faster with complex equations

$$I_{out} = \frac{L_p \left(\frac{V_c}{R_i} \right)^2 F_{sw}}{2V_{out}}$$

- You have three variables, you can perturb and collect...

$$I_{out} + \hat{i}_{out} = \frac{L_p \left(\frac{V_c + \hat{v}_c}{R_i} \right)^2 (F_{sw} + \hat{f}_{sw})}{2(V_{out} + \hat{v}_{out})} \quad \longrightarrow \quad \begin{array}{l} I_{out} = \dots \text{ dc equation} \\ \hat{i}_{out} = \dots \text{ ac equation} \end{array}$$

Partial Differentiation

- ... or you can use Mathcad® and automate the process

$$\hat{i}_{out} = \frac{\partial I_{out}(F_{sw}, V_c, V_{out})}{\partial F_{sw}} \hat{f}_{sw} + \frac{\partial I_{out}(F_{sw}, V_c, V_{out})}{\partial V_c} \hat{v}_c + \frac{\partial I_{out}(F_{sw}, V_c, V_{out})}{\partial V_{out}} \hat{v}_{out}$$

- You have the result in a twinkling of an eye



$$\hat{i}_{out} = \frac{L_p V_c^2}{2R_i^2 V_{out}} \hat{f}_{sw} + \frac{F_{sw} L_p V_c}{R_i^2 V_{out}} \hat{v}_c - \frac{F_{sw} L_p V_c^2}{2R_i^2 V_{out}^2} \hat{v}_{out}$$

- We can apply this technique to our diode equation

$$\hat{i}_F = \frac{\partial \left(I_S e^{\frac{V_F}{nV_T}} \right)}{\partial V_F} \hat{v}_F = I_S e^{\frac{V_F}{nV_T}} \frac{\hat{v}_F}{nV_T} = \frac{I_F}{nV_T} \hat{v}_F \quad \Rightarrow \quad r_d = \frac{nV_T}{I_F} [\Omega]$$




Course Agenda

- Linear and Non-Linear Functions
- What is a Small-Signal Model?
- Fast Analytical Techniques at Work**
- From a Switched to Linearized Model
- The CCM VM Small-Signal PWM Switch Model
- The DCM VM Small-Signal PWM Switch Model
- Peak Current Mode Control in Large Signal
- The CCM CM Small-Signal PWM Switch Model
- The DCM CM Small-Signal PWM Switch Model
- The PWM Switch in Boundary Mode




The Bipolar Small-Signal Model

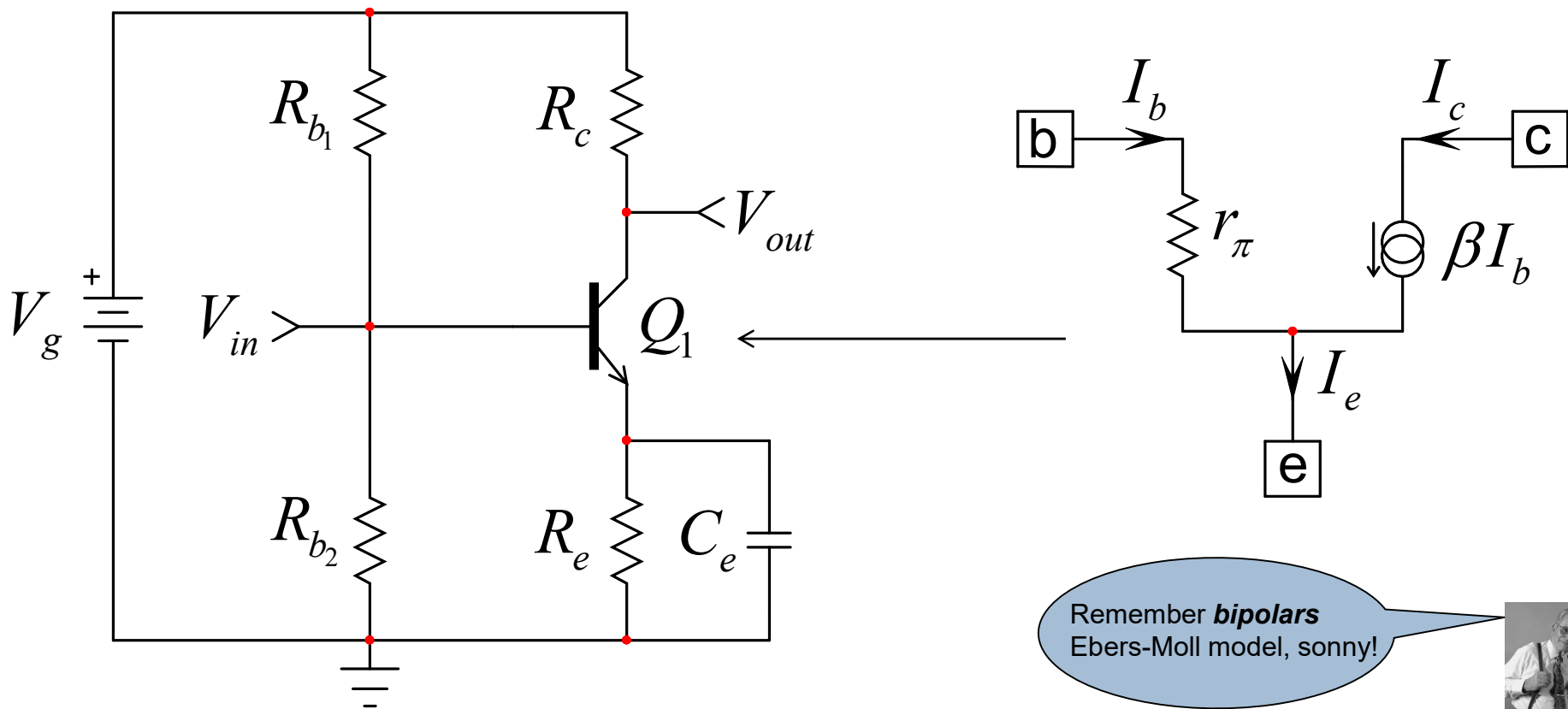- ❑ A bipolar transistor is a highly non-linear system
- ❑ Replace it by its small-signal model to get the response



A Linear System

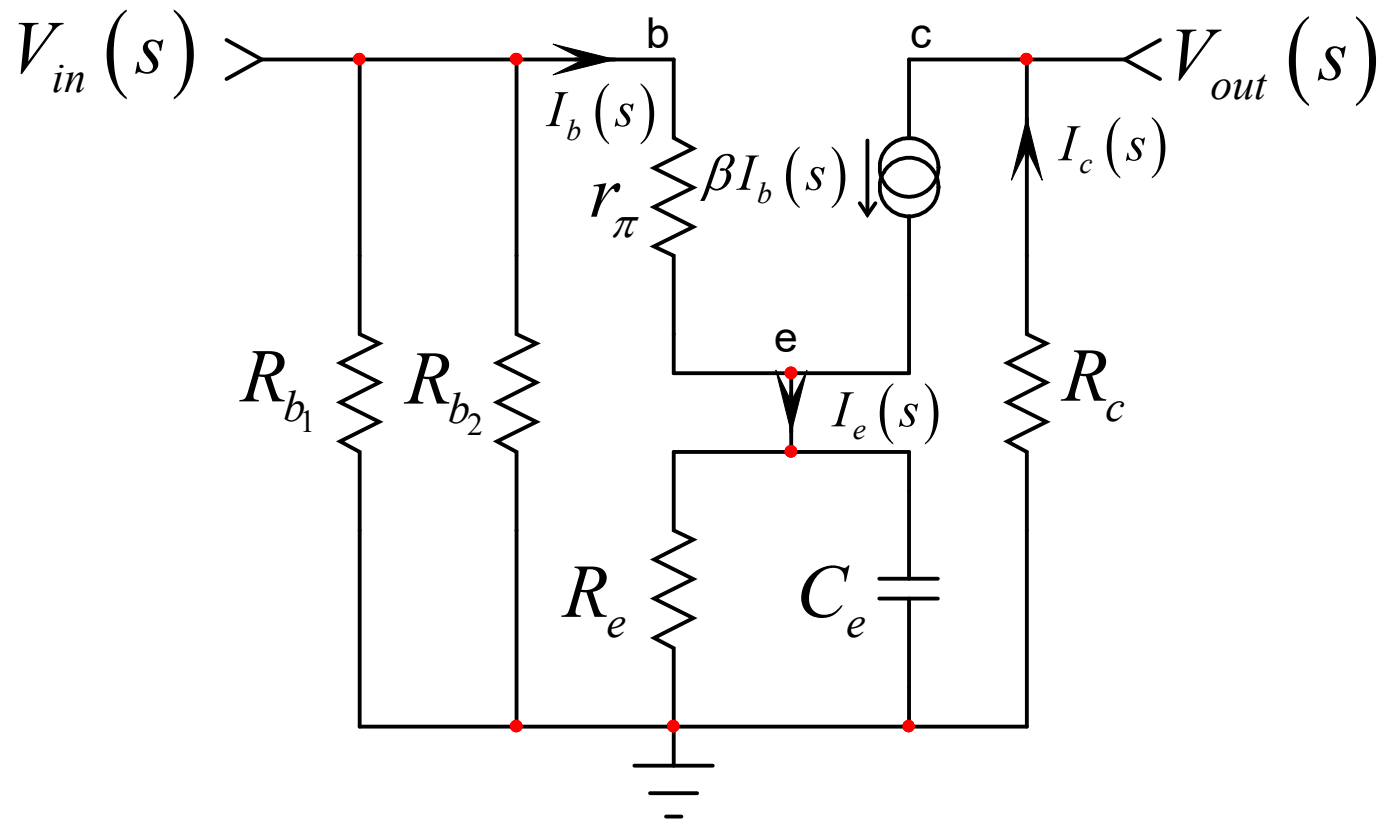- The new circuit is a small-signal linear architecture



- Laplace notation applies to get the transfer function

The Transfer Function

- A transfer function links a response to an excitation

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} \quad \begin{array}{l} \longleftarrow \text{response} \\ \longleftarrow \text{excitation} \end{array} \quad H(s) = \frac{N(s)}{D(s)} \quad \begin{array}{l} \longleftarrow \text{zeros} \\ \longleftarrow \text{poles} \end{array}$$

- It must be written in a so-called low entropy form

$$H(s) = \frac{b_0 + b_1s}{a_0 + a_1s} \xrightarrow[\text{factor } a_0]{\text{factor } b_0} \frac{b_0}{a_0} \frac{1 + s \frac{b_1}{b_0}}{1 + s \frac{a_1}{a_0}} \longrightarrow G_0 \frac{1 + s/\omega_{z_1}}{1 + s/\omega_{p_1}}$$

- In this 1st-order expression you can identify the terms


$$G_0 = \frac{b_0}{a_0} \quad \omega_{z_1} = \frac{b_0}{b_1} \quad \omega_{p_1} = \frac{a_0}{a_1}$$

dc gain, $s = 0$ zero pole




Finding the Zeros

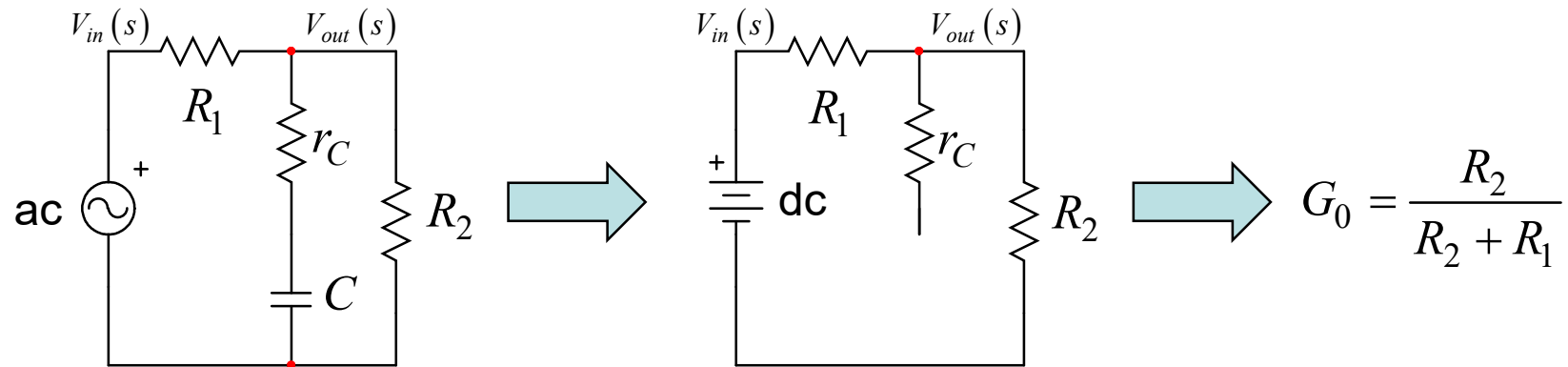- G_0 is found by shorting inductors and opening capacitors




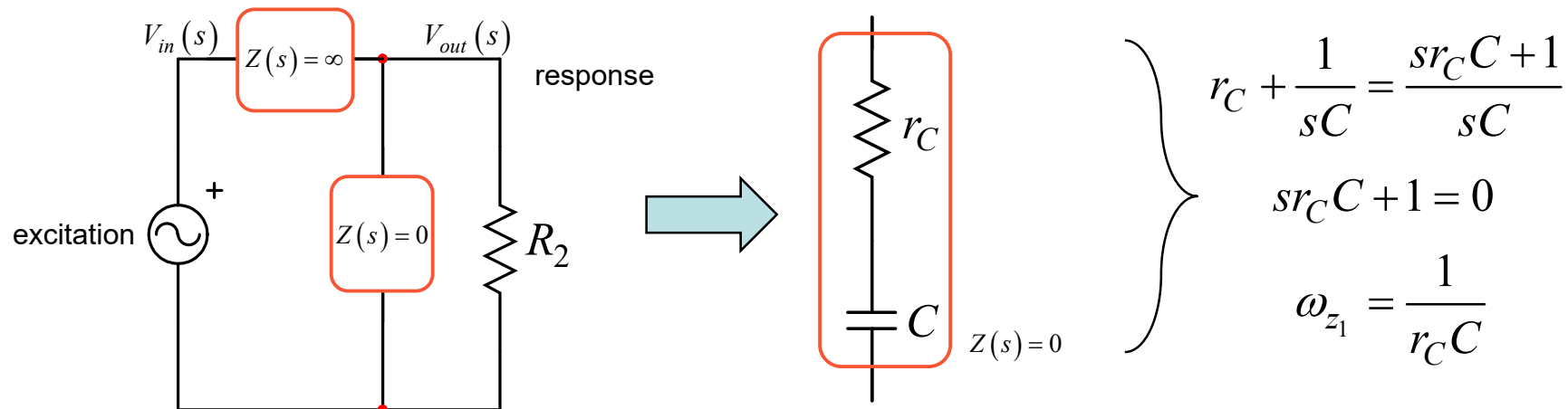- Zeros prevent the excitation from reaching the output




Finding the Poles

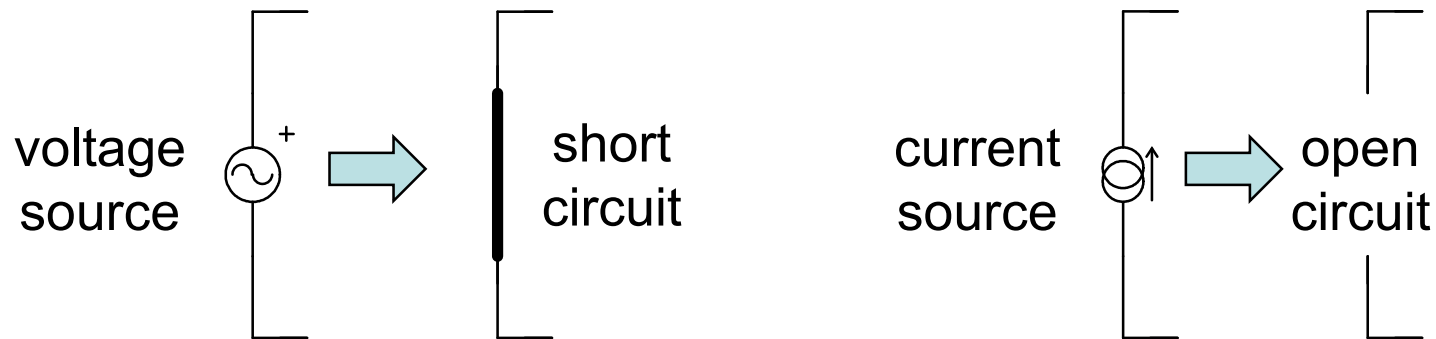- ❑ The poles are linked to the time constants of the system
- ❑ These time constants solely depend on the structure
- Remove the excitation signal to isolate the structure




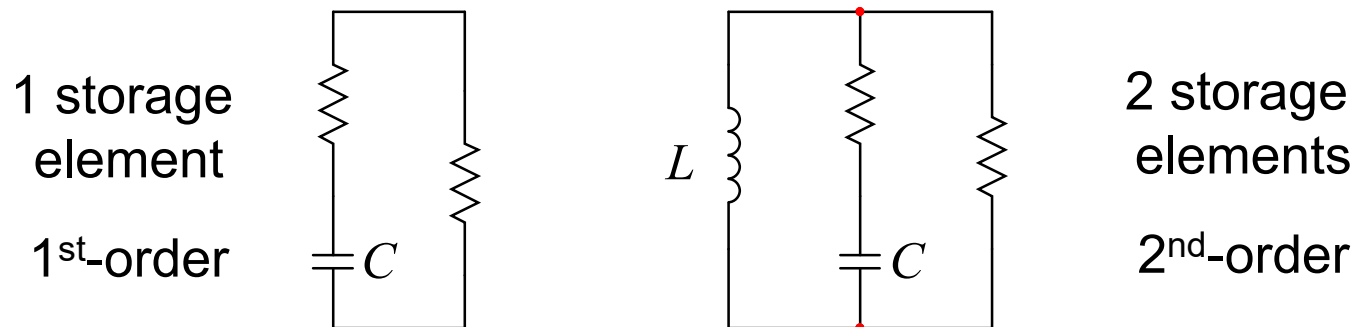- ❑ The denominator order depends on the storage elements



The Final Answer

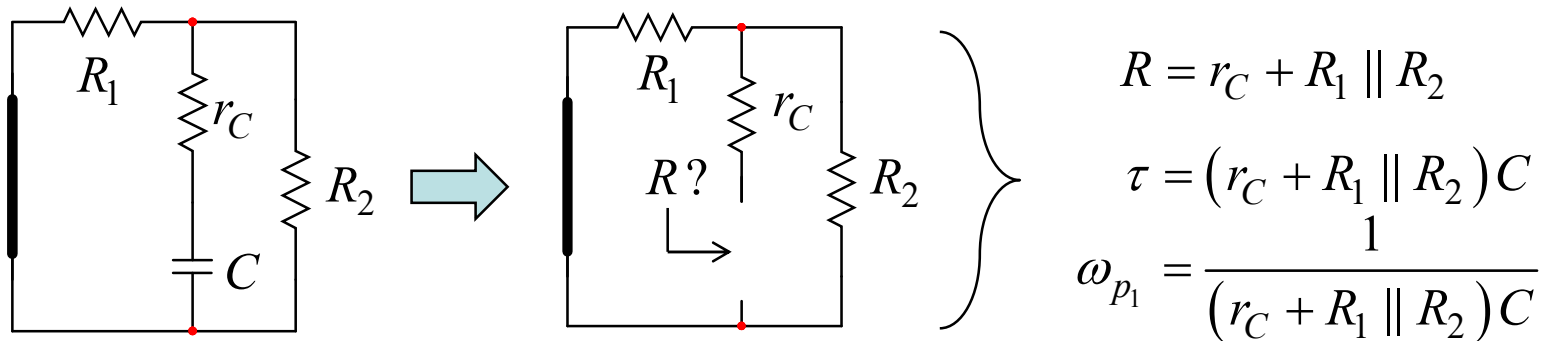- Short the voltage source and calculate the time constant



- The complete transfer function is obtained in 3 steps

$$H(s) = G_0 \frac{1 + s/\omega_{z_1}}{1 + s/\omega_{p_1}} = \frac{R_2}{R_2 + R_1} \frac{1 + sr_C C}{1 + s(r_C + R_1 \parallel R_2) C}$$

- We derived the transfer function by inspection!


“Fast Analytical Techniques for Electrical and Electronic Circuits”, V. Vorpérian, Cambridge Press, 2002

The Transistor Amplifier

- We have just one capacitor, this is a 1st-order system

$$\Rightarrow \frac{V_{out}(s)}{V_{in}(s)} = G_0 \frac{1 + s/\omega_{z1}}{1 + s/\omega_{p1}}$$

- G_0 is found by opening the capacitor

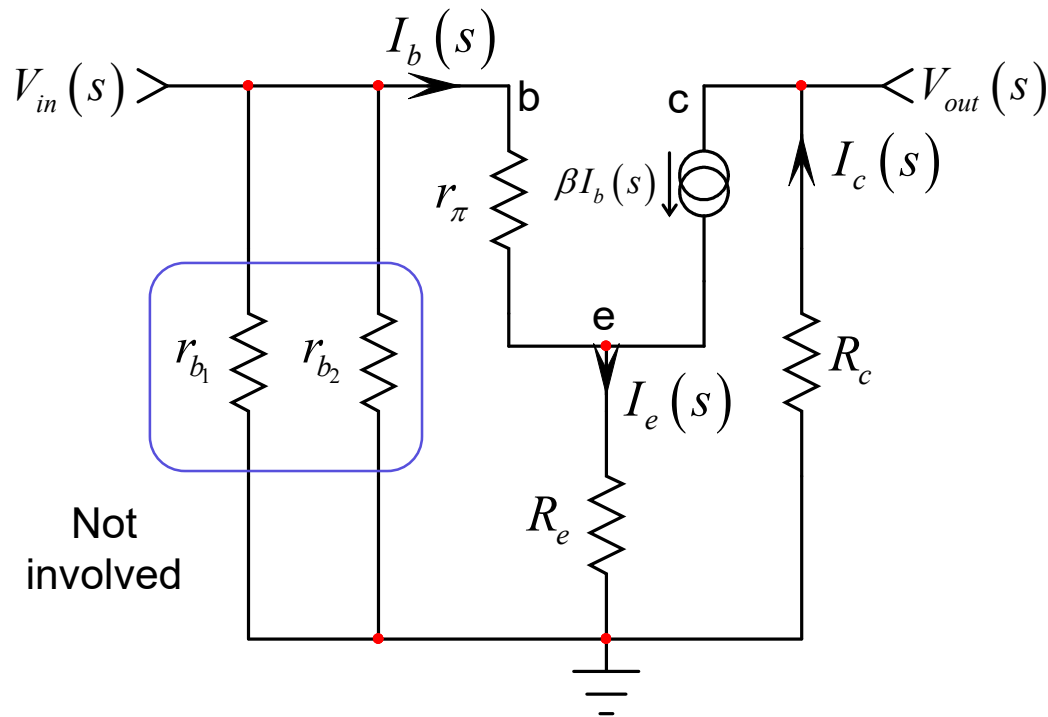

$$V_{out}(s) = -R_c I_c(s) = -R_c \beta I_b(s)$$

$$I_b(s) = \frac{V_{be}(s)}{r_\pi} = \frac{V_{in}(s) - I_e(s) R_e}{r_\pi}$$

$$I_e(s) = (\beta + 1) I_b(s)$$


$$I_b(s) = \frac{V_{in}(s) - (\beta + 1) I_b(s) R_e}{r_\pi}$$

$$I_b(s) = \frac{V_{in}(s) r_\pi}{r_\pi + (\beta + 1) R_e}$$

$$G_0 = -\frac{R_c \beta}{r_\pi + (\beta + 1) R_e} \approx -\frac{R_c}{R_e}$$

Looking for the Zeros

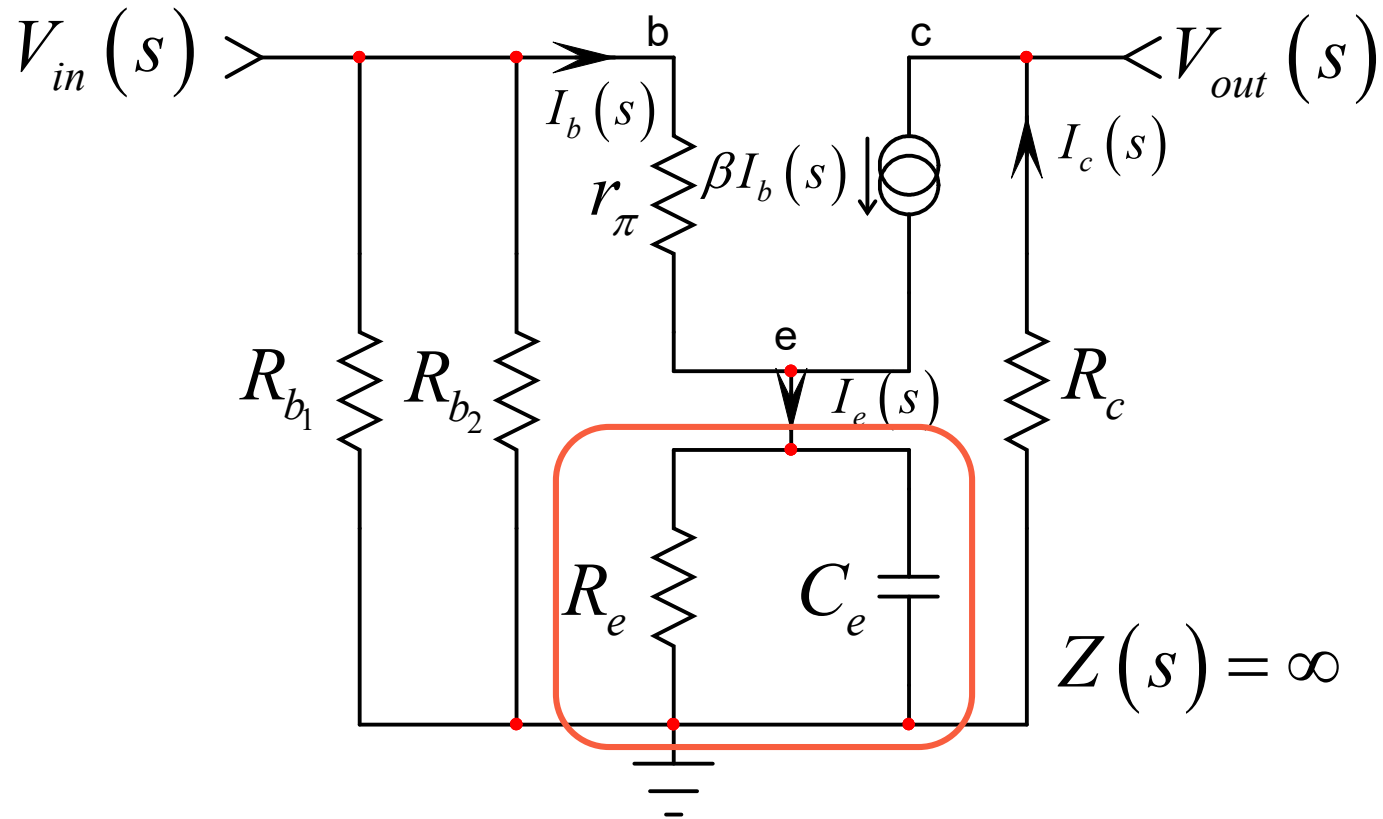
□ What could prevent the excitation from reaching the output?



□ When this impedance is infinite, there is no base current

Looking for the Zeros

- The frequency where the impedance is infinite is our zero

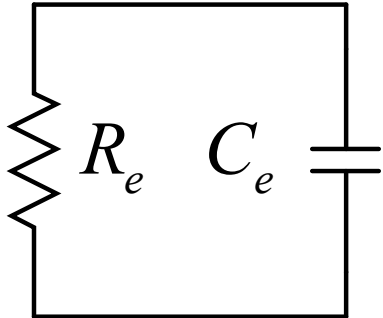
$$Z(s) = R_e \parallel \frac{1}{sC_e} = \frac{R_e}{1 + sR_e C_e}$$

- When the denominator is equal to zero, Z is infinite


$$1 + sR_e C_e = 0 \quad \longrightarrow \quad \omega_{z_1} = \frac{1}{R_e C_e}$$

- We are almost there

$$\frac{V_{out}(s)}{V_{in}(s)} = -\frac{R_c}{R_e} \frac{1 + sR_e C_e}{D(s)}$$

Looking for the Poles

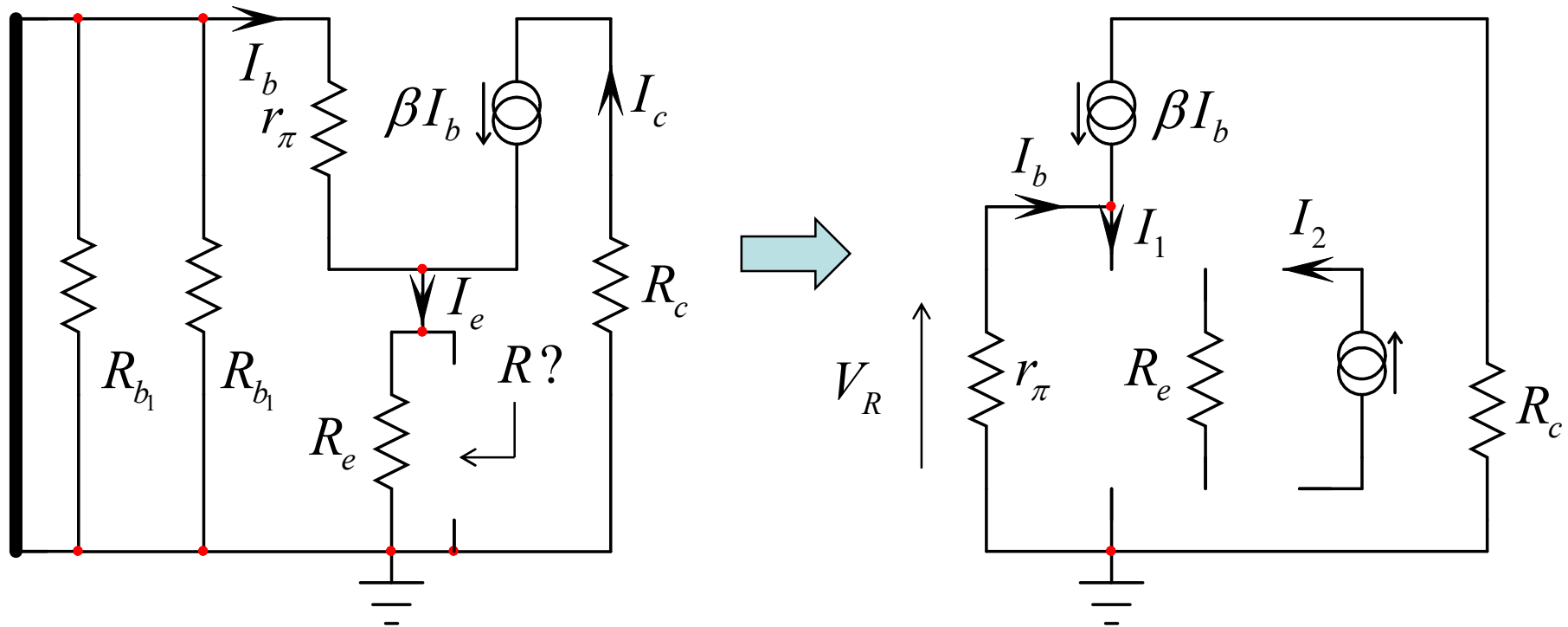- For the system time constant, short the excitation



- Write two simple equations


$$I_b = -\frac{V_R}{r_\pi} \quad I_1 = (\beta + 1)I_b = -I_2 \quad \Rightarrow \quad R = \frac{V_R}{I_2} = R_e \parallel \left(\frac{r_\pi}{\beta + 1} \right)$$

The Final Transfer Function

□ We have our transfer function in a few steps only

$$\frac{V_{out}(s)}{V_{in}(s)} \approx -\frac{R_c}{R_e} \frac{1 + sR_e C_e}{1 + sC_e R_e \parallel \left(\frac{r_{\pi}}{\beta + 1} \right)}$$

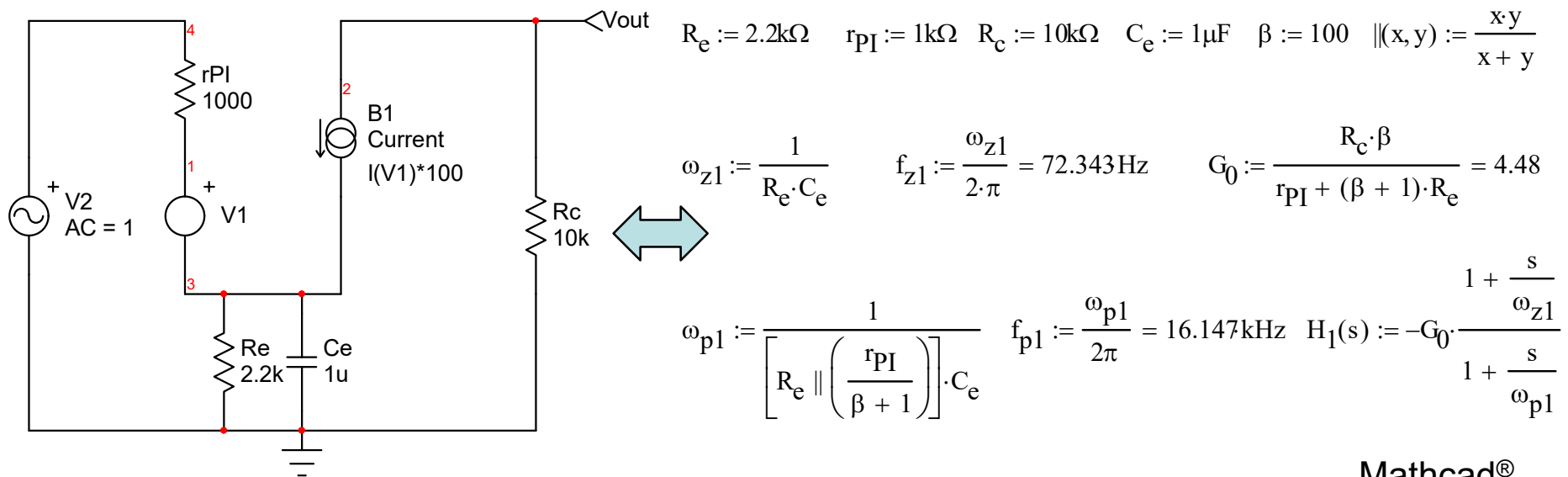□ The next step is to check maths versus simulation




Mathcad®



The Final Transfer Function

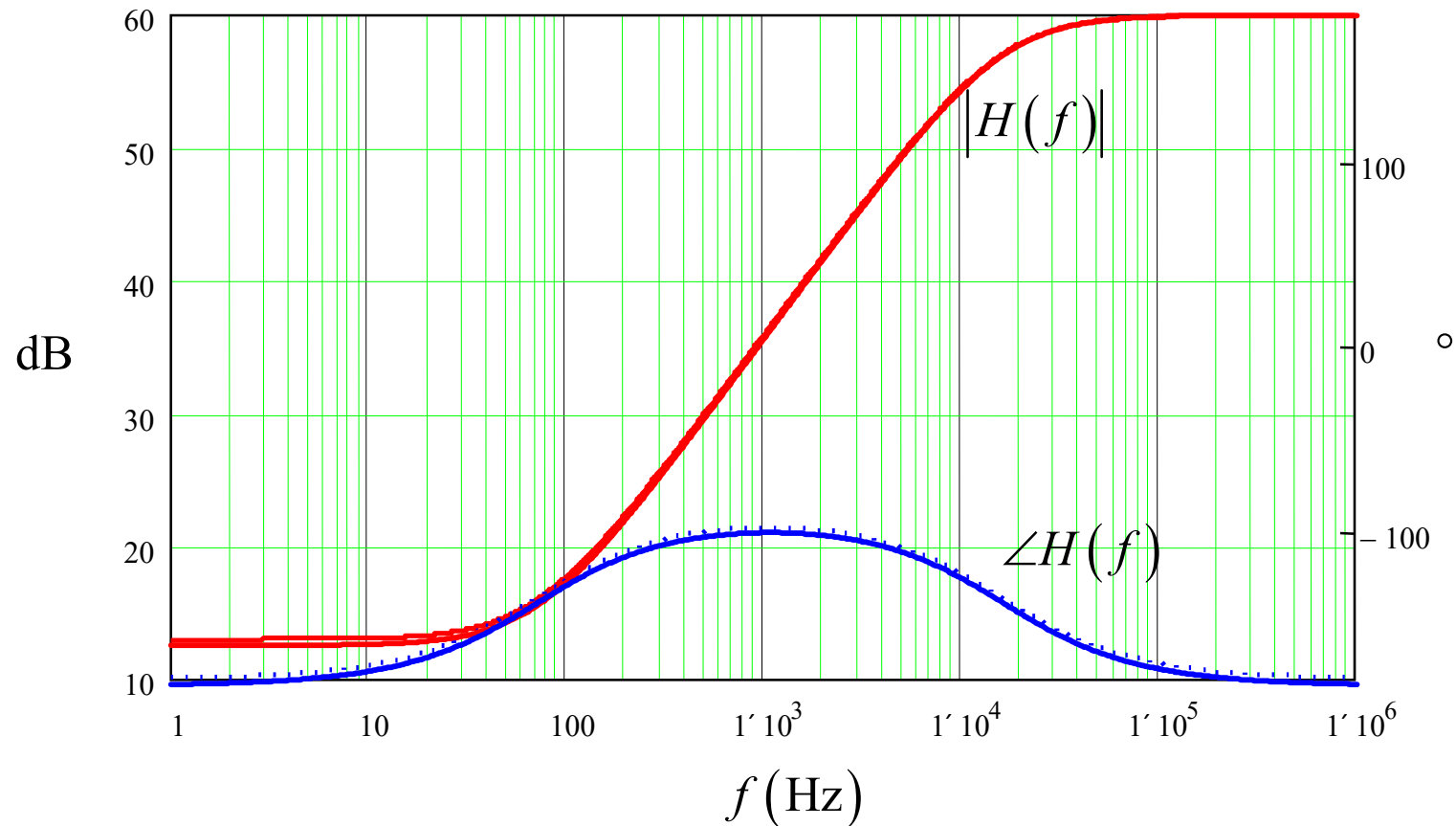- The curves superimpose, calculations are good!



- Always run this sanity check to verify your results



Agenda

- ❑ Linear and Non-Linear Functions
- ❑ What is a Small-Signal Model?
- ❑ Fast Analytical Techniques at Work
- ❑ **From a Switched to Linearized Model**
- ❑ The CCM VM Small-Signal PWM Switch Model
- ❑ The DCM VM Small-Signal PWM Switch Model
- ❑ Peak Current Mode Control in Large Signal
- ❑ The CCM CM Small-Signal PWM Switch Model
- ❑ The DCM CM Small-Signal PWM Switch Model
- ❑ The PWM Switch in Boundary Mode




Non-Linearity in a Switching Converter

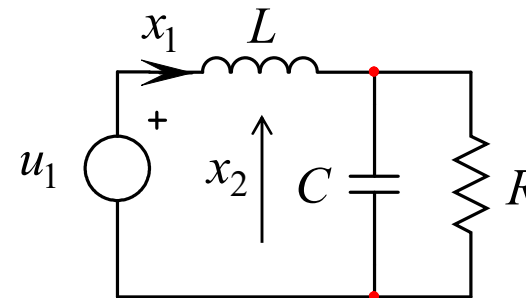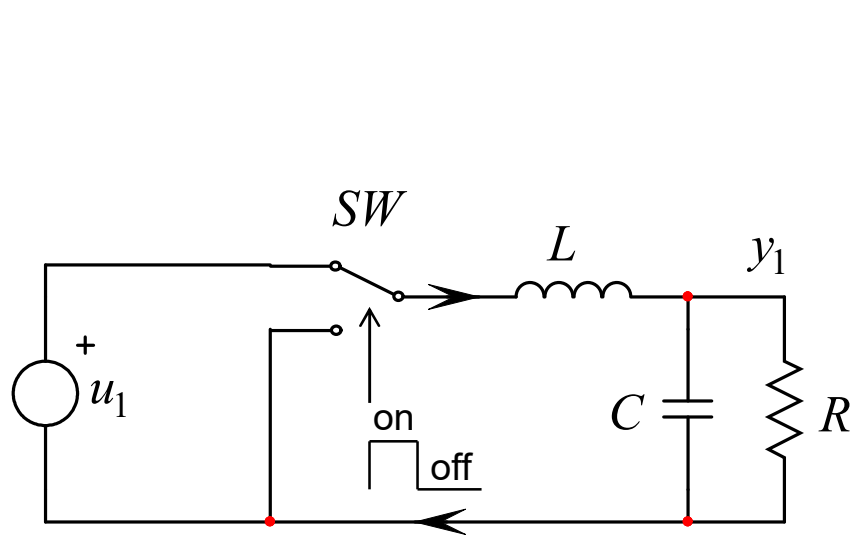□ A switching converter is ruled by linear equations...



during
 DT_{sw}

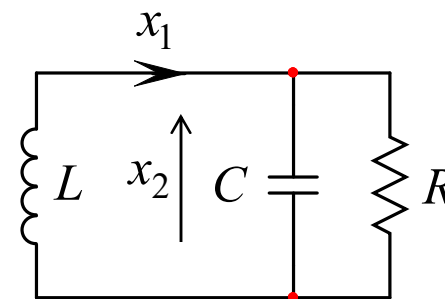


during
 $(1-D)T_{sw}$

□ ...combining so-called state variables

State Variables

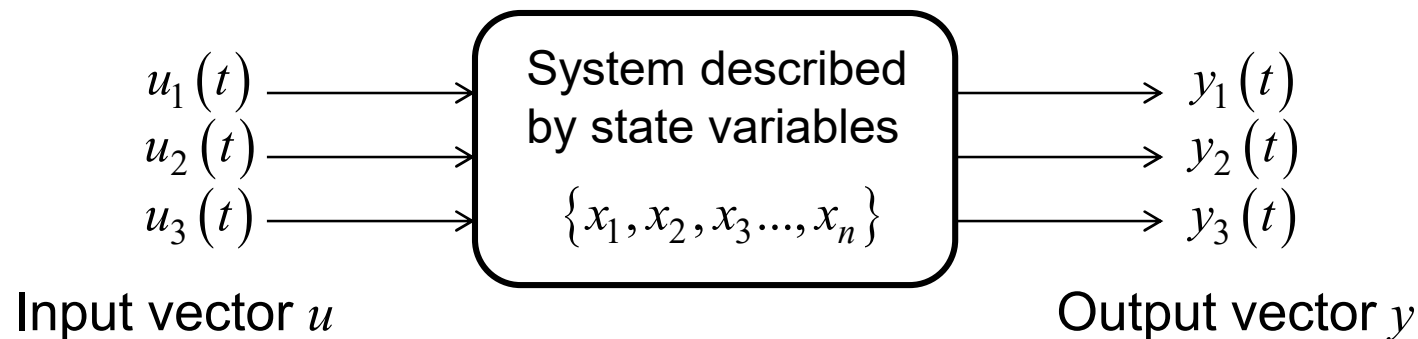- State variables describe the mathematical state of a system
- n state variables for n independent storage elements
- knowing variables state at t_0 helps compute outputs for $t > t_0$




- x_1 is the inductor current and x_2 is the capacitor voltage
- Differentiation gives the state variable rate of change

$$x_1 = i_L(t) \quad \dot{x}_1 = \frac{di_L(t)}{dt} \quad \text{Predict future system state} \quad x_2 = v_C(t) \quad \dot{x}_2 = \frac{dv_C(t)}{dt}$$



Describe the System During the On-Time

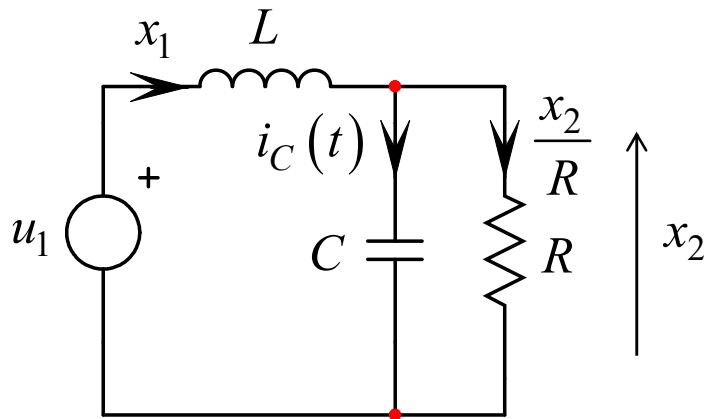- Observe the system during the on-time duration or dT_{SW} :



$$i_C(t) = C \frac{dv_C(t)}{dt} = C\dot{x}_2 = x_1 - \frac{1}{R}x_2$$

$$u_1 = L \frac{di_L(t)}{dt} + v_C(t) = L\dot{x}_1 + x_2$$


$$\left. \begin{aligned} \dot{x}_1 &= -\frac{1}{L}x_2 + \frac{1}{L}u_1 \\ \dot{x}_2 &= \frac{1}{C}x_1 - \frac{1}{RC}x_2 \end{aligned} \right\} \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 1/L & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix}$$

State coefficients Source coefficients



Describe the System During the Off-Time

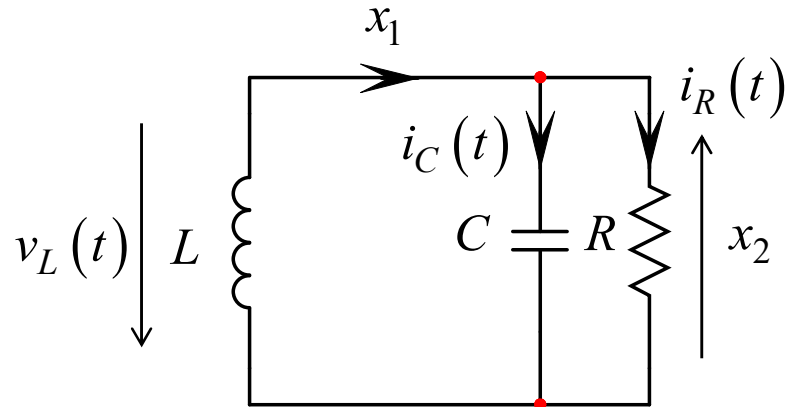- Repeat the exercise during the off-time duration or $1-dT_{SW}$



$$v_L(t) = -x_2 \quad v_L(t) = L\dot{x}_1$$

$$\Rightarrow x_2 = -L\dot{x}_1$$

$$i_R(t) = x_1 - i_C(t) = x_1 - C\dot{x}_2$$

$$x_2 = i_R(t)R$$

$$\Rightarrow x_2 = R(x_1 - C\dot{x}_2)$$

$$\Rightarrow \left. \begin{aligned} \dot{x}_1 &= 0 - \frac{1}{L}x_2 \\ \dot{x}_2 &= \frac{1}{C}x_1 - \frac{1}{RC}x_2 \end{aligned} \right\}$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix}$$

State coefficients

Source coefficients

Make it Fit the State Equation Format

- Arrange expressions to make them fit the format:

$$\dot{x} = \mathbf{A}x(t) + \mathbf{B}u(t) \quad \text{State equation}$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \overset{\text{on-time network}}{\begin{bmatrix} 1/L & 0 \\ 0 & 0 \end{bmatrix}} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} \Rightarrow \mathbf{A}_1 = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \mathbf{B}_1 = \begin{bmatrix} 1/L & 0 \\ 0 & 0 \end{bmatrix}$$

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \overset{\text{off-time network}}{\begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}} \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} \Rightarrow \mathbf{A}_2 = \begin{bmatrix} 0 & -1/L \\ 1/C & -1/RC \end{bmatrix} \mathbf{B}_2 = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix}$$

- How do we link matrixes \mathbf{A}_1 and \mathbf{A}_2 , \mathbf{B}_1 and \mathbf{B}_2 ?
- We smooth the discontinuity by weighting them by D and $1-D$

$$\dot{x} = \left[\mathbf{A}_1 D + \mathbf{A}_2 (1-D) \right] x(t) + \left[\mathbf{B}_1 D + \mathbf{B}_2 (1-D) \right] u(t)$$

The State-Space Averaging Method (SSA)


- We now have a continuous large-signal equation
- We need to linearize it via perturbations

$$D = D_0 + \hat{d} \quad x = x_0 + \hat{x} \quad u = u_0 + \hat{u}$$

$$\dot{x} = \left[\mathbf{A}_1 D + \mathbf{A}_2 (1 - D) \right] x(t) + \left[\mathbf{B}_1 d + \mathbf{B}_2 (1 - D) \right] u(t)$$


$$\hat{\dot{x}}_1 = \frac{1}{L} \hat{x}_2 + \frac{D_0}{L} \hat{u}_1 + \frac{\hat{d}}{L} u_{10}$$
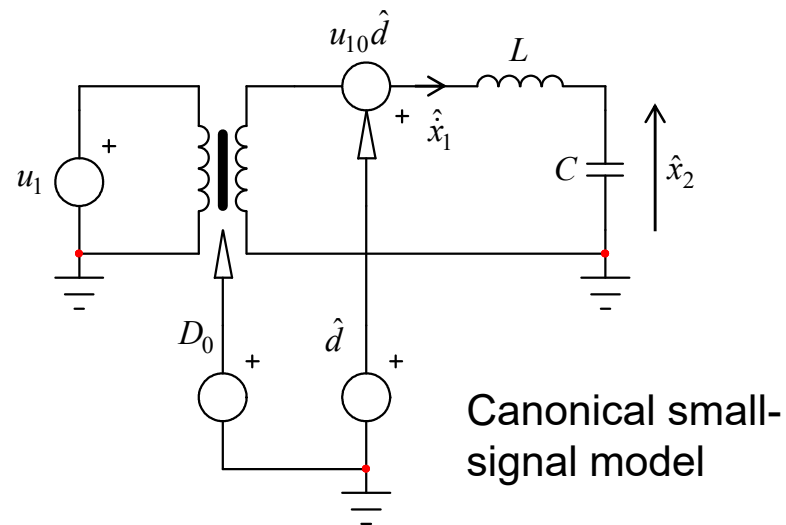
$$\hat{\dot{x}}_2 = \frac{1}{C} \hat{x}_1 - \frac{1}{RC} \hat{x}_2$$



The State-Space Averaging Method (SSA)

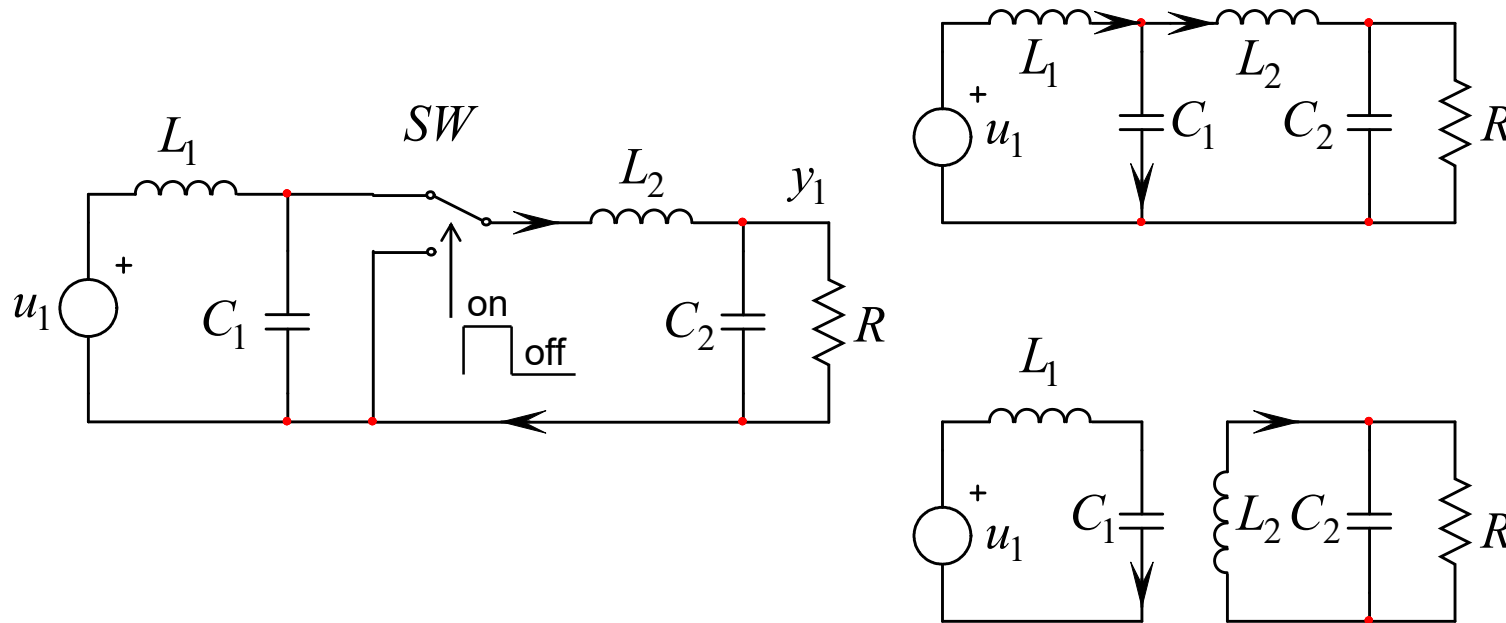
- ❑ SSA was applied to switching converters by Dr Ćuk in 1976
- ❑ It is a long, painful process, manipulating numerous terms
- ❑ What if you add an EMI filter for instance?




- ❑ 4 state variables and you have to re-derive all equations!

The PWM Switch Model in Voltage Mode

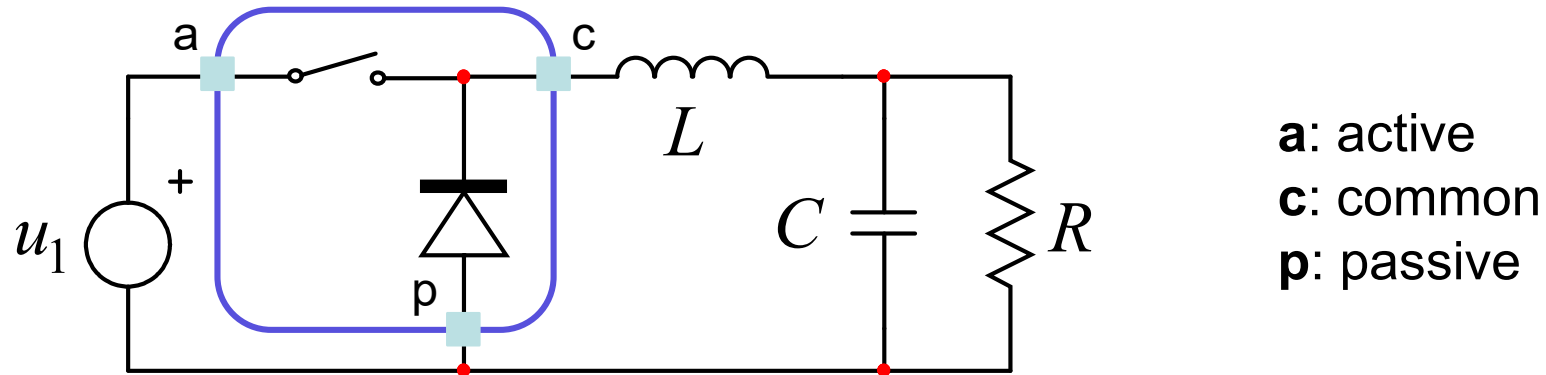- We know that non-linearity is brought by the switching cell




- Why don't we linearize the cell alone?

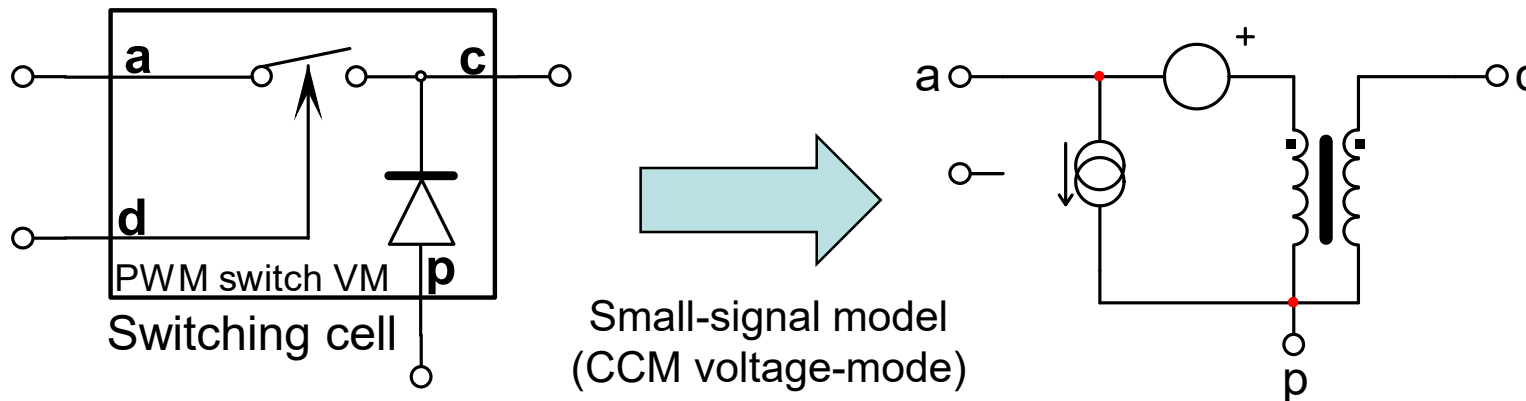

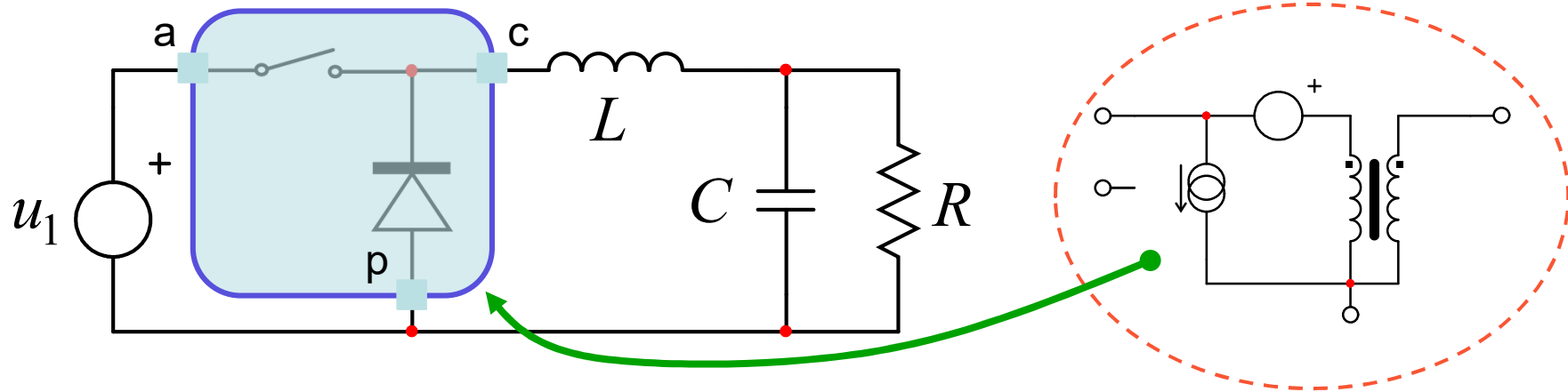
V. Vorperian, "Simplified Analysis of PWM Converters using Model of PWM Switch, parts I and II"
IEEE Transactions on Aerospace and Electronic Systems, Vol. 26, NO. 3, 1990

Replace the Switches by the Model

- Like in the bipolar circuit, replace the switching cell...








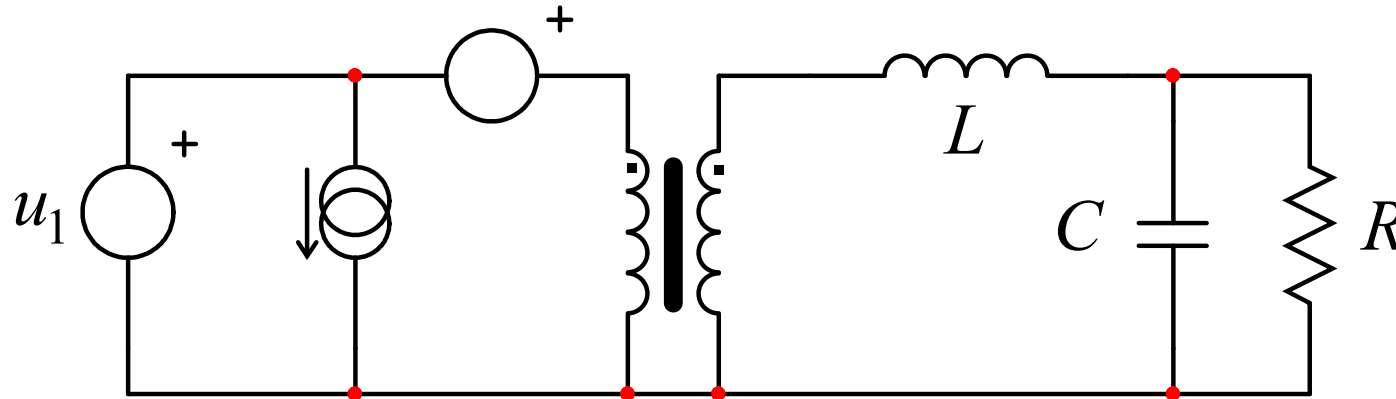- ...and solve a set of linear equations!




An Invariant Model

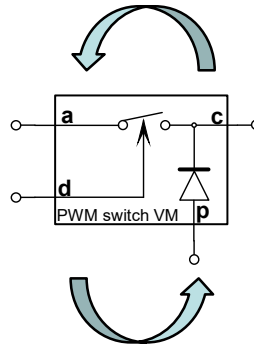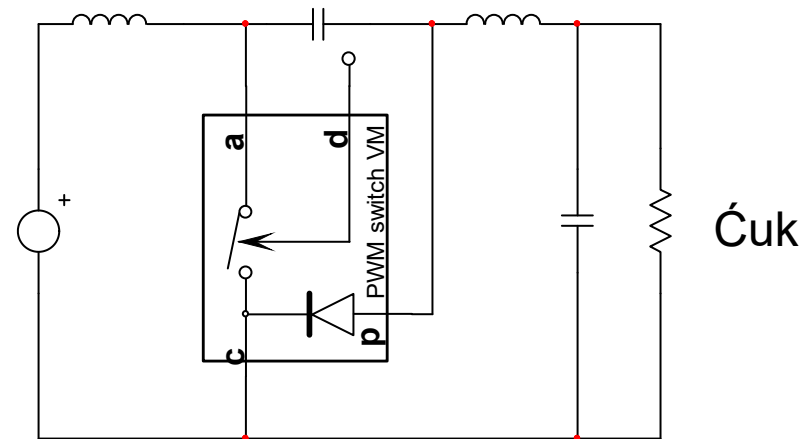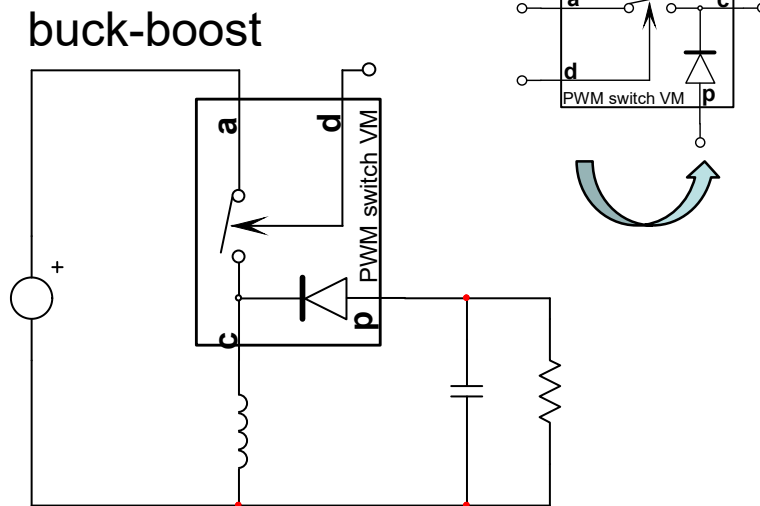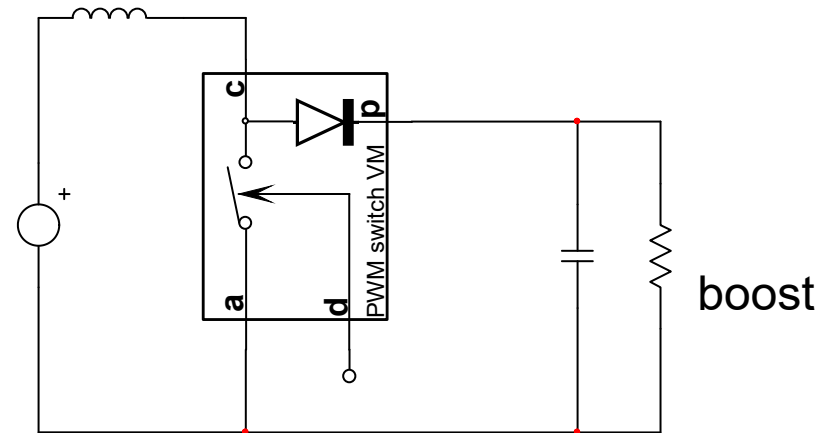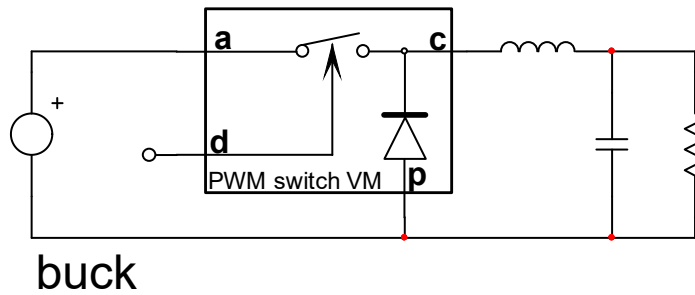- The switching cell made of two switches is everywhere!



Smoothing the Discontinuity

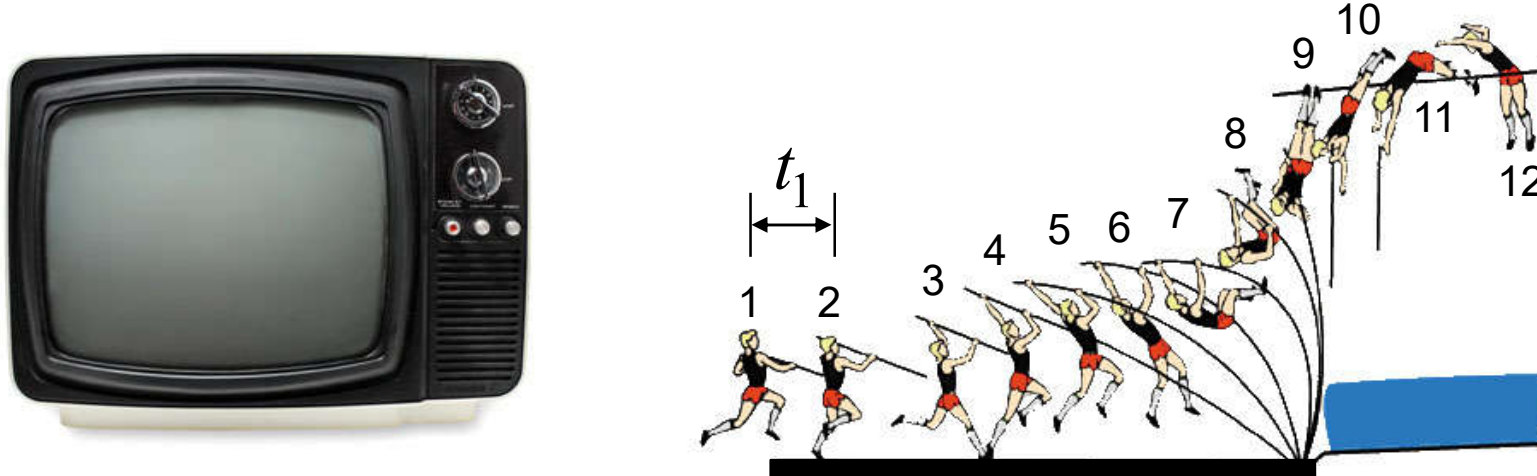- ❑ A CRT TV displays frames at a certain rate, 50 per second



- ❑ The optic nerve time constant is larger than an interval
- ❑ A succession of discrete events is seen as continuous


Low-frequency filtering
Integration



See "phi phenomena", www.wikipedia.org

Averaging Waveforms

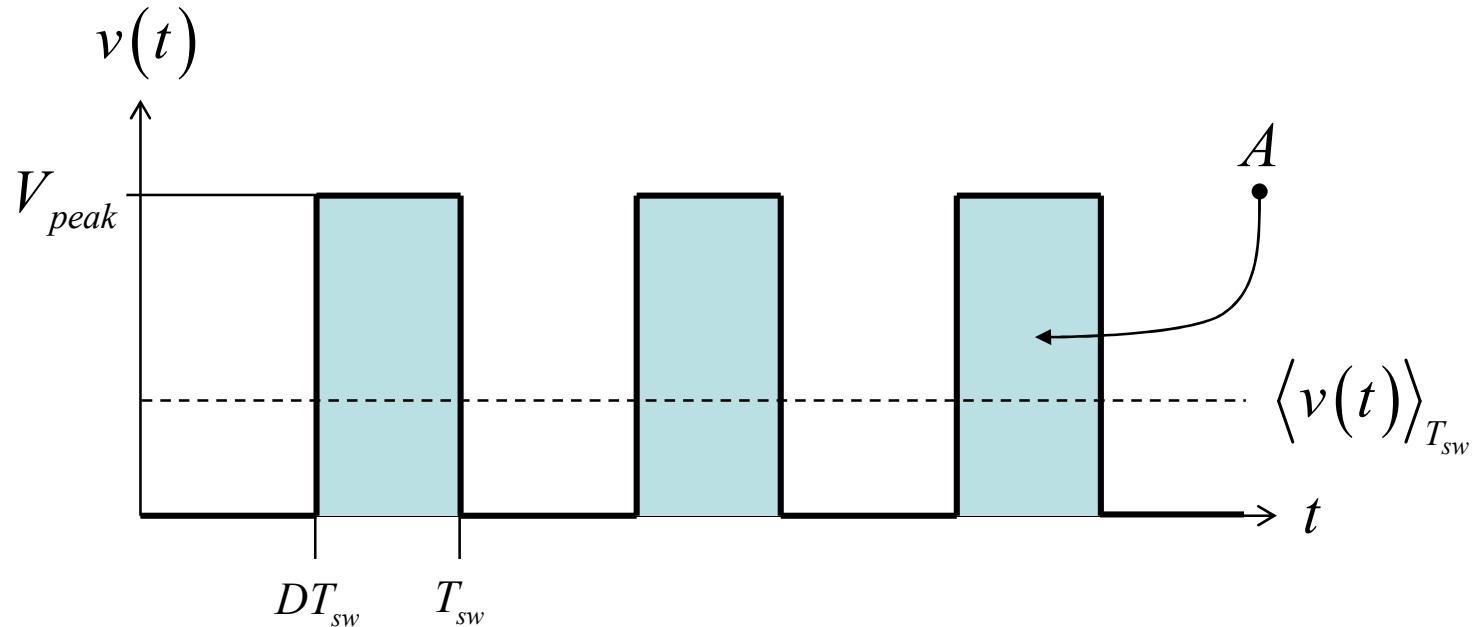- The keyword in the PWM switch is *averaging*




$$\langle v(t) \rangle_{T_{sw}} = \frac{1}{T_{sw}} \int_0^{T_{sw}} v(t) \cdot dt = \frac{1}{T_{sw}} \int_{DT_{sw}}^{T_{sw}} V_{peak} \cdot dt = V_{peak} (1 - D) = V_{peak} D'$$

- The resulting function is continuous in time

From Steps to a Continuous Function

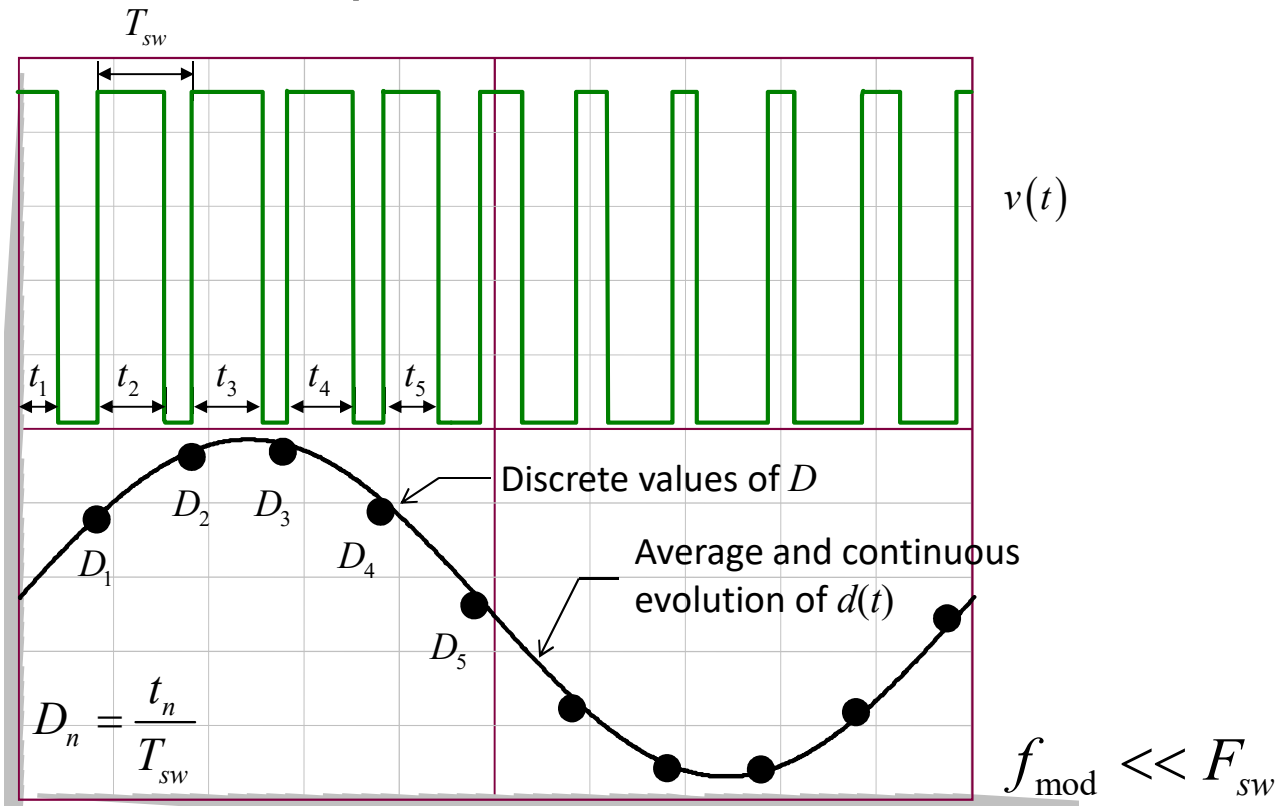
- ❑ Some functions require mathematical abstraction: duty ratio




- ❑ At the modulation frequency scale, points look contiguous
- ❑ Link them through a continuous-time ripple-free function $d(t)$

The Common Passive Configuration

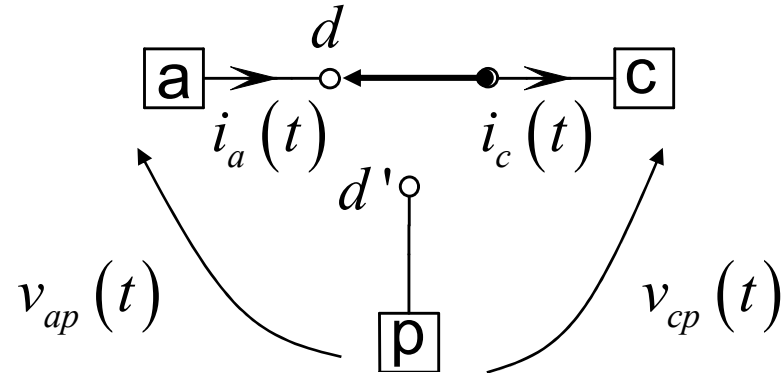- The PWM switch is a single-pole double-throw model




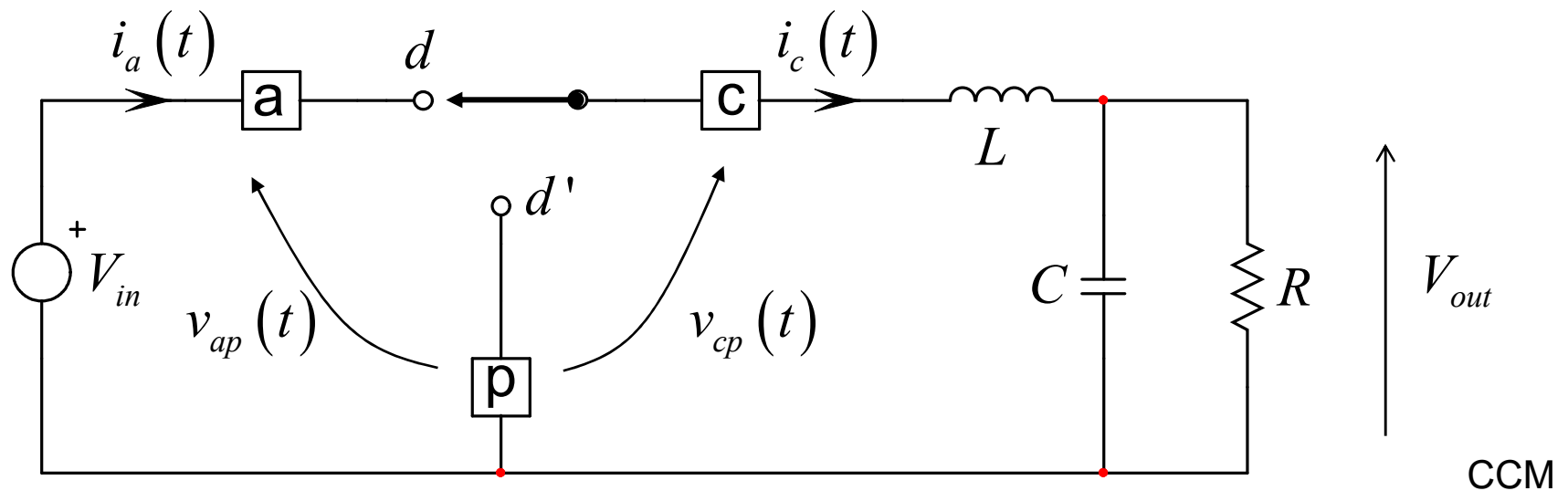- Install it in a buck converter and draw the waveforms



The Common Passive Configuration

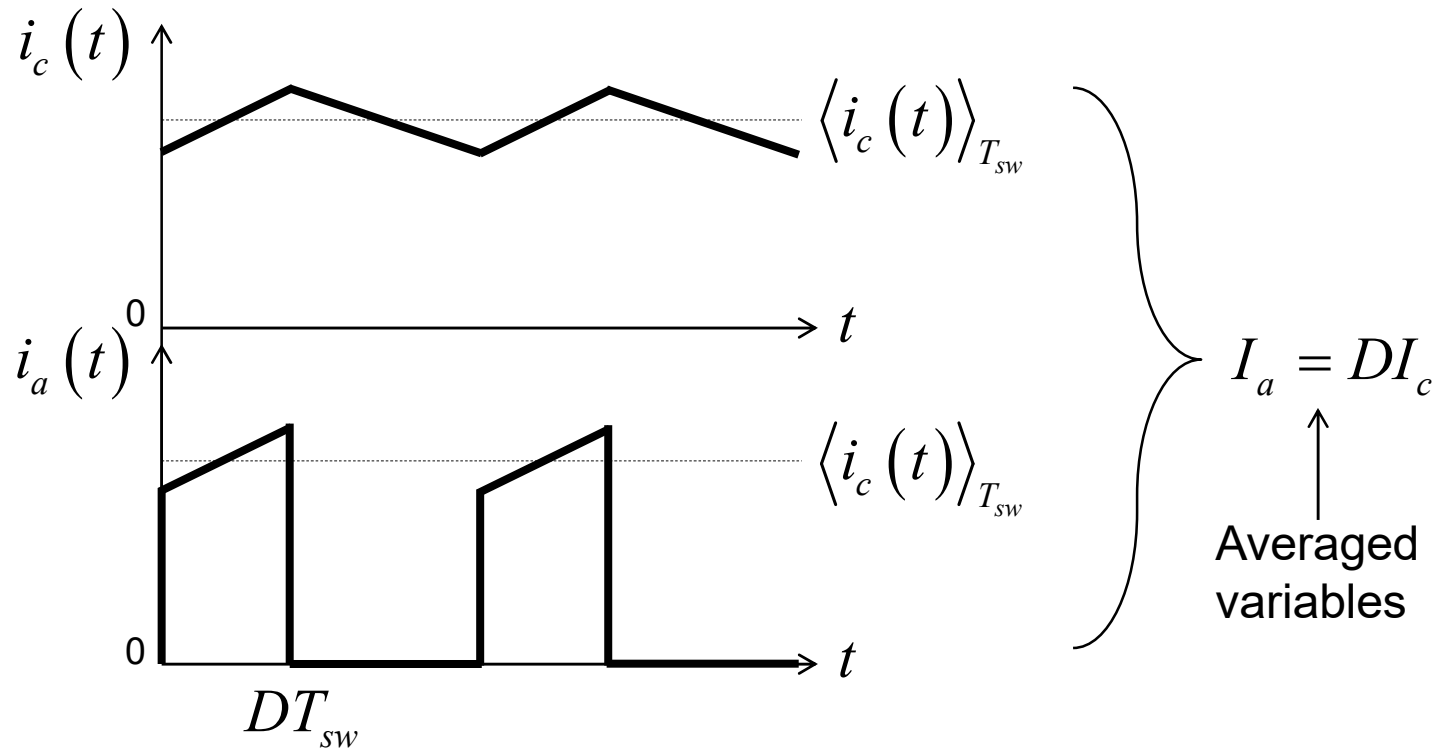- Average the current waveforms across the PWM switch




$$\langle i_a(t) \rangle_{T_{sw}} = I_a = \frac{1}{T_{sw}} \int_0^{dT_{sw}} i_a(t) dt = D \langle i_c(t) \rangle_{T_{sw}} = DI_c$$

CCM



The Common Passive Configuration

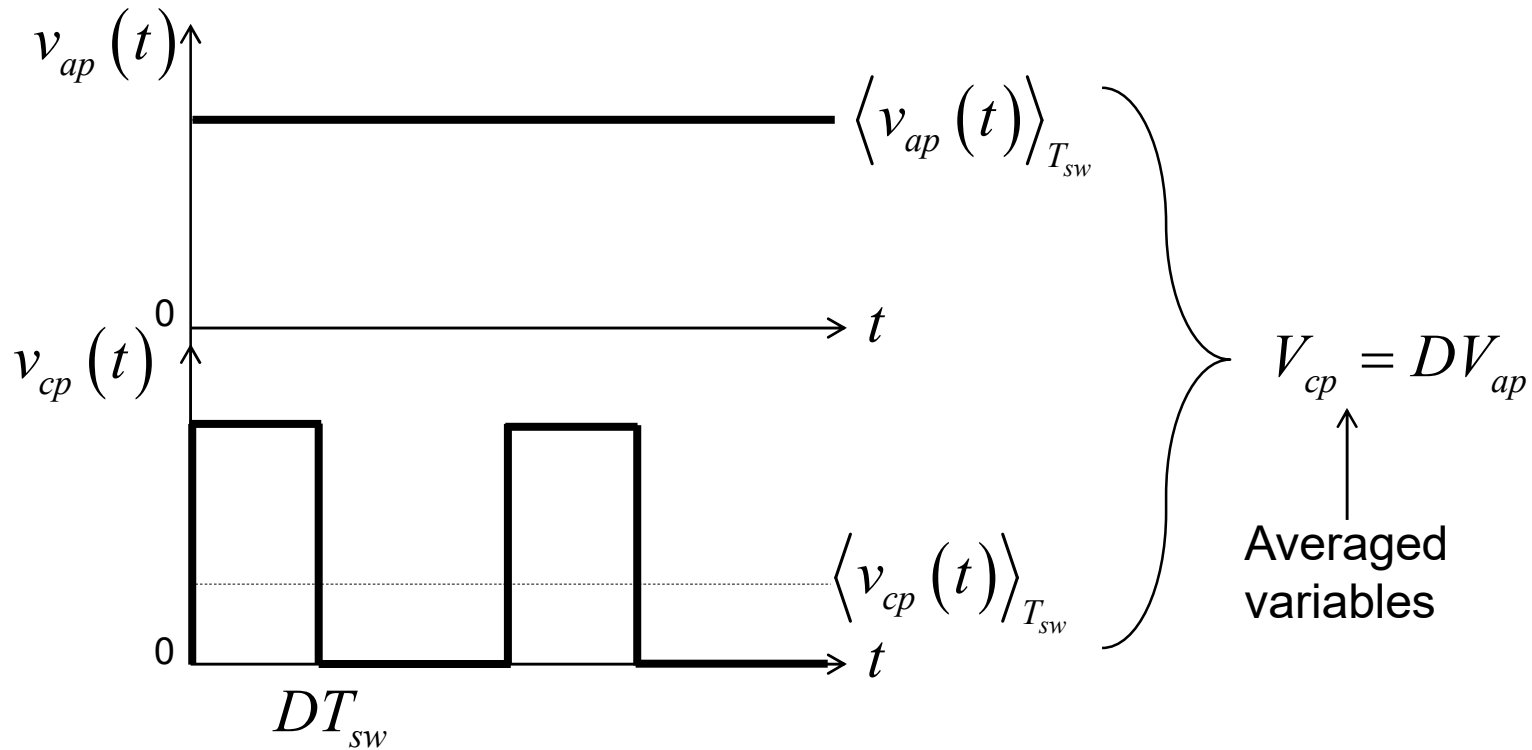- Average the voltage waveforms across the PWM switch




$$\langle v_{cp}(t) \rangle_{T_{sw}} = V_{cp} = \frac{1}{T_{sw}} \int_0^{dT_{sw}} v_{cp}(t) dt = D \langle v_{ap}(t) \rangle_{T_{sw}} = DV_{ap}$$

CCM




A Two-Port Representation

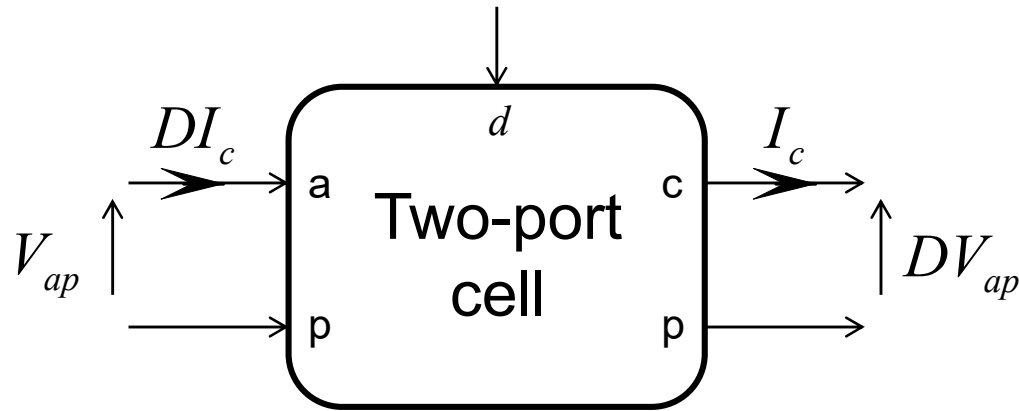- We have a link between input and output variables



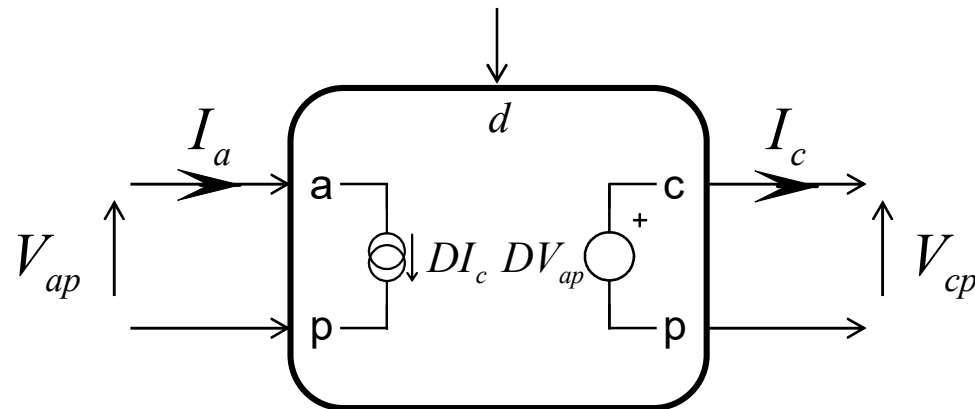
- It can further be illustrated with current and voltage sources




CCM

A Transformer Representation

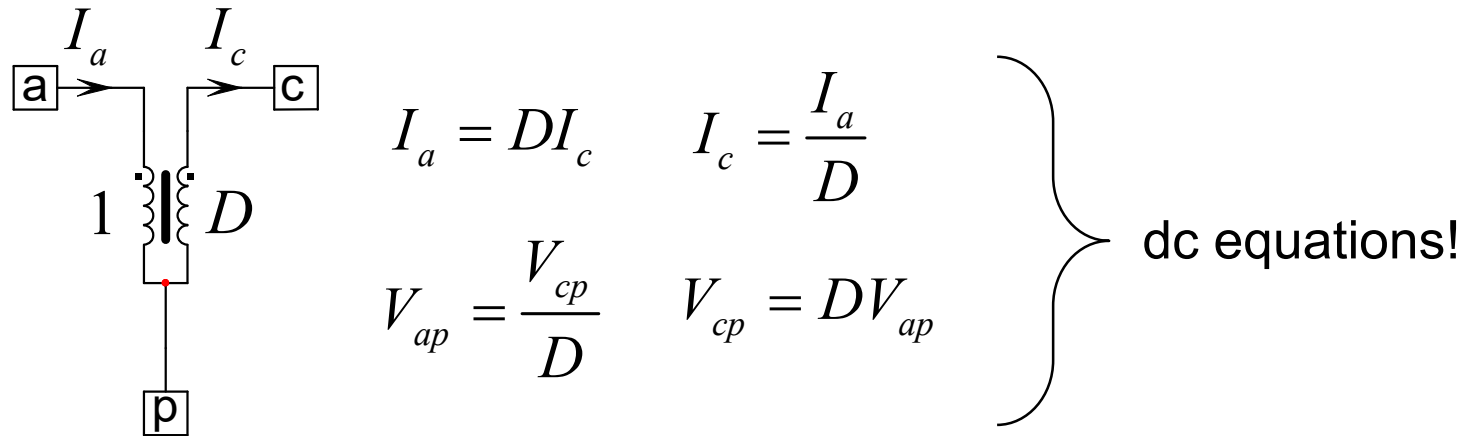- The PWM switch large-signal model is a dc "transformer"!



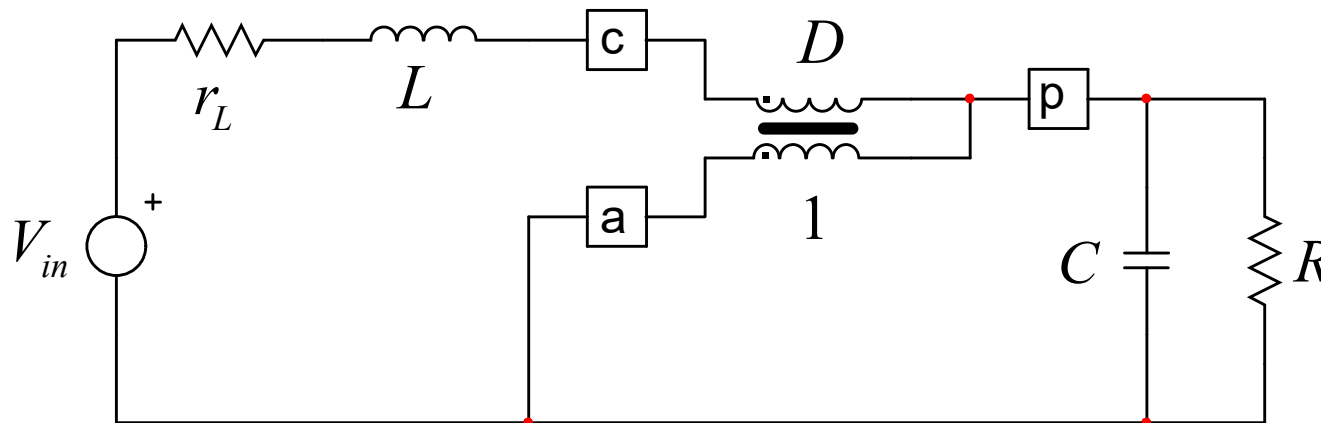- It can be immediately plugged into any 2-switch converter




CCM




Simulate Immediately with this Model

- SPICE can get you the dc bias point

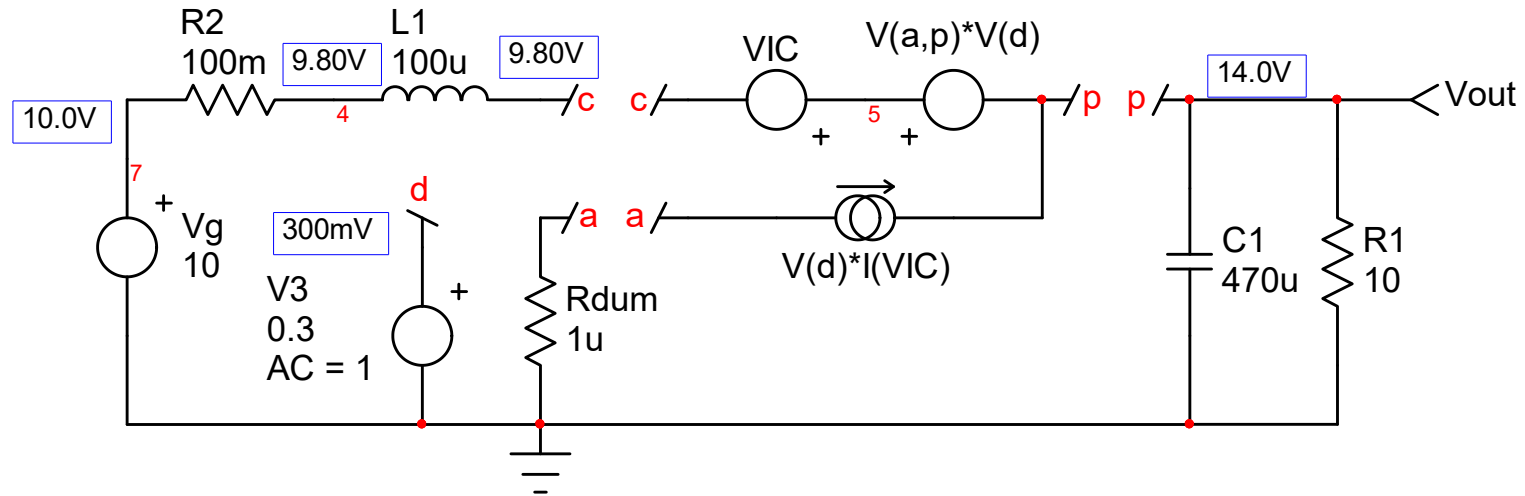

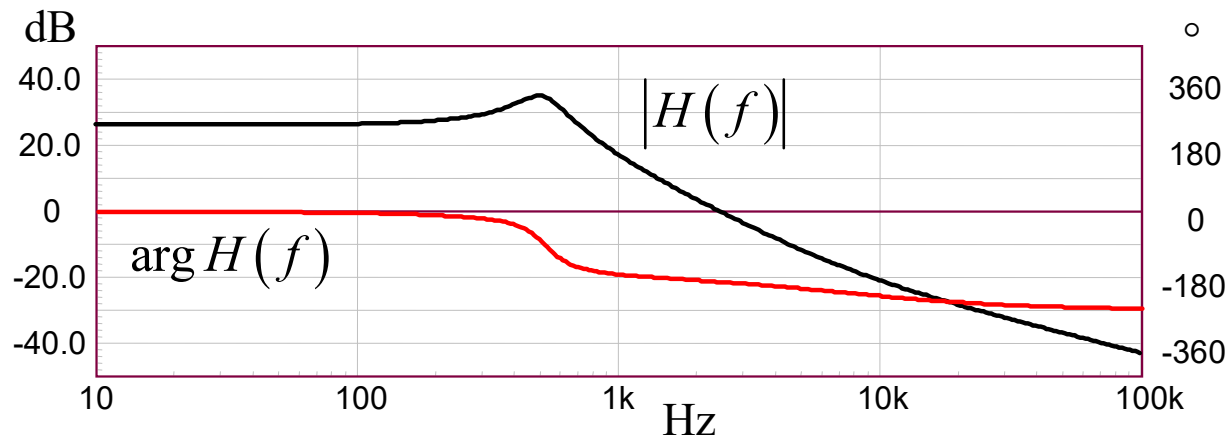- ...but also the ac response as it linearizes the circuit




CCM



We Want Transfer Functions

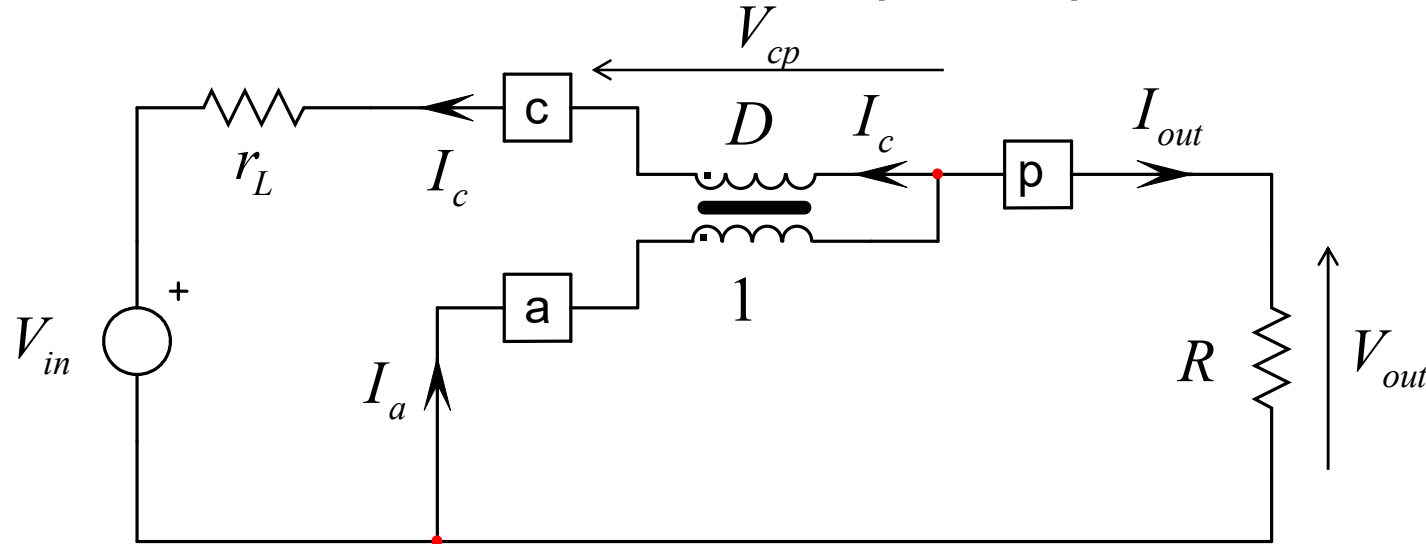- Derive the dc transfer function: open caps., short inductors



$$V_{out} = I_{out} R$$

$$V_{out} = (I_a - I_c) R$$

$$I_a = DI_c$$

$$V_{out} = I_c (D-1) R$$

$$V_{in} + r_L I_c - V_{cp} = V_{out}$$

$$V_{in} + r_L I_c + DV_{out} = V_{out}$$

$$I_c = \frac{V_{out} (1-D) - V_{in}}{r_L}$$


$$\frac{V_{out}}{V_{in}} = \frac{1}{(1-D) - \frac{r_L}{(D-1)R}}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{D'} \frac{1}{1 + \frac{r_L}{RD'^2}}$$

CCM

Plotting Transfer Functions

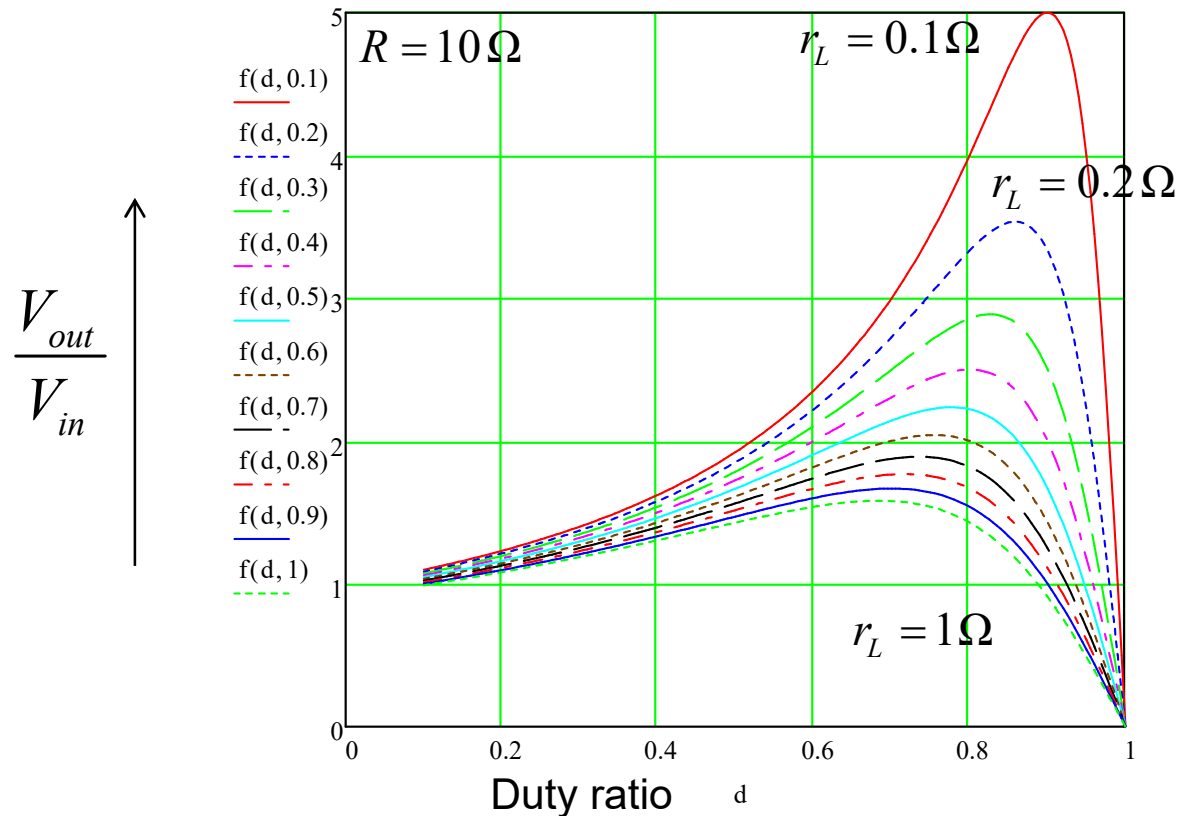- Plot the lossy boost transfer function in a snapshot



- Above a certain conversion ratio, latch-up occurs

CCM


Course Agenda

- Linear and Non-Linear Functions
- What is a Small-Signal Model?
- Fast Analytical Techniques at Work
- From a Switched to Linearized Model
- The CCM VM Small-Signal PWM Switch Model**
- The DCM VM Small-Signal PWM Switch Model
- Peak Current Mode Control in Large Signal
- The CCM CM Small-Signal PWM Switch Model
- The DCM CM Small-Signal PWM Switch Model
- The PWM Switch in Boundary Mode




A Small-Signal Model

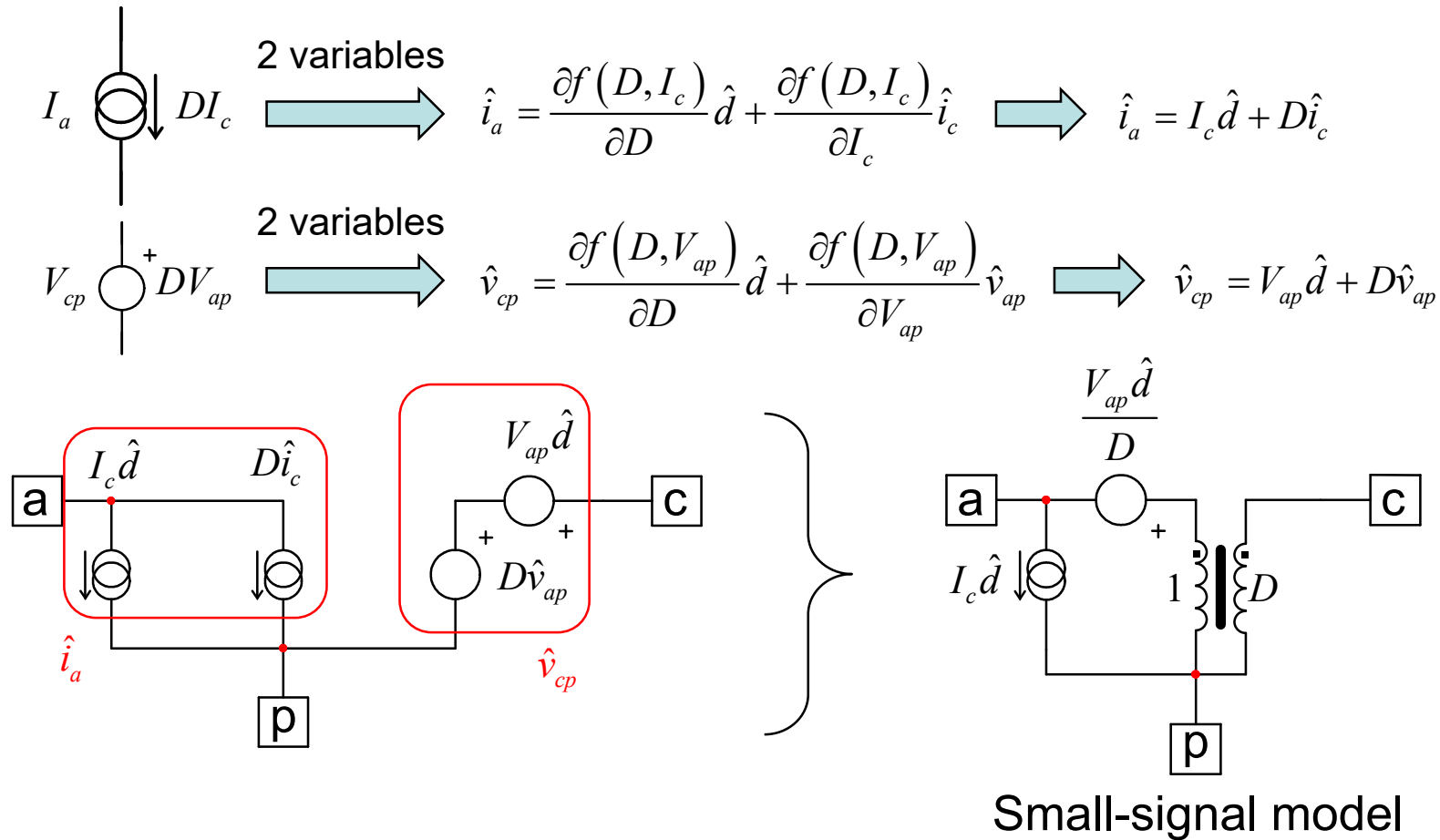- We need a small-signal version to get the ac response
- We can apply the linearization technique we learned




Plug this Small-Signal Model in the Boost

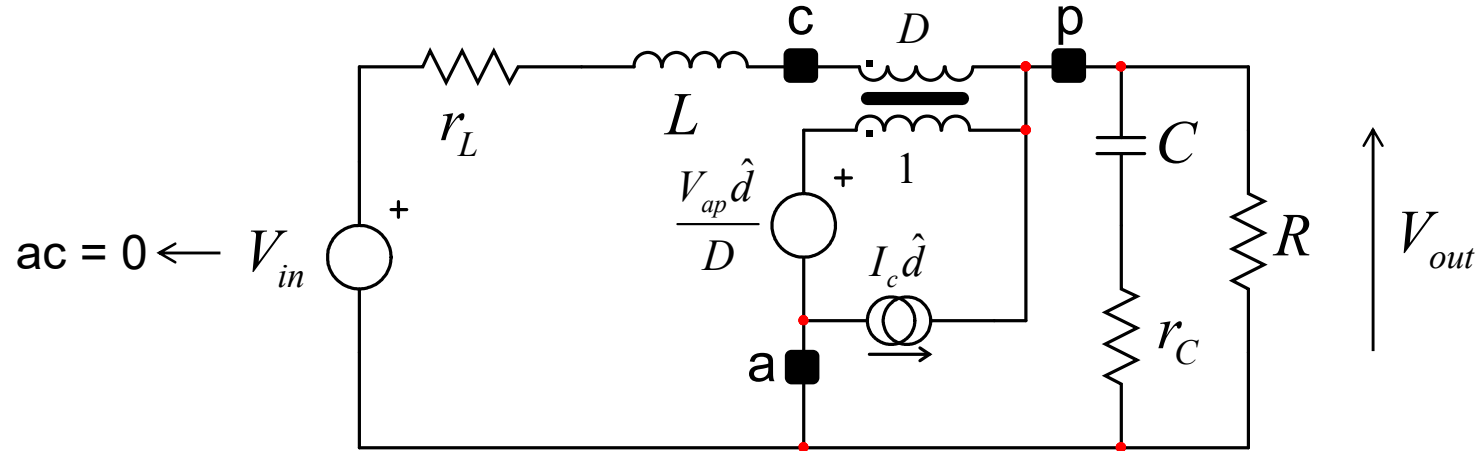- You now have a completely linear and continuous model




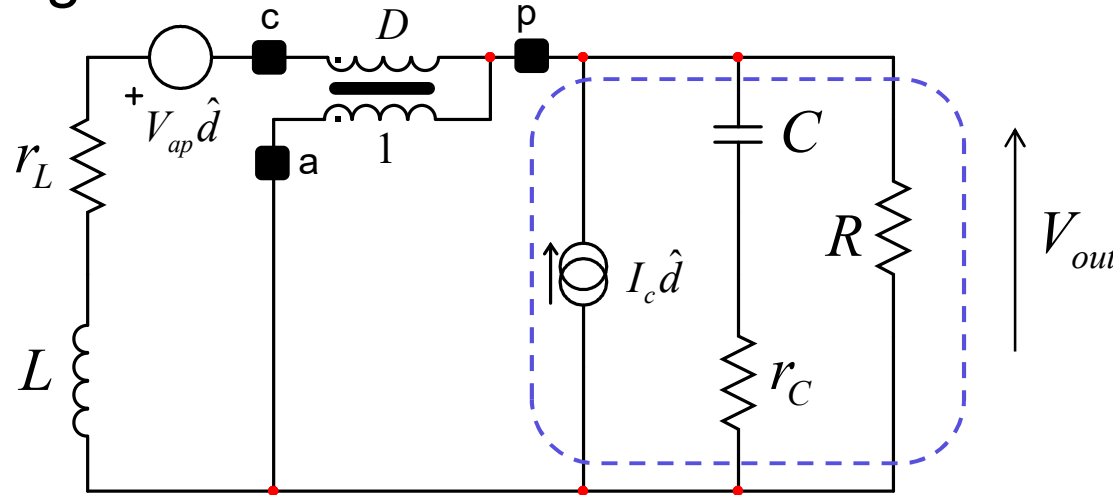- Re-arrange the circuit with the PWM switch



Reflect on the Other Side if Needed

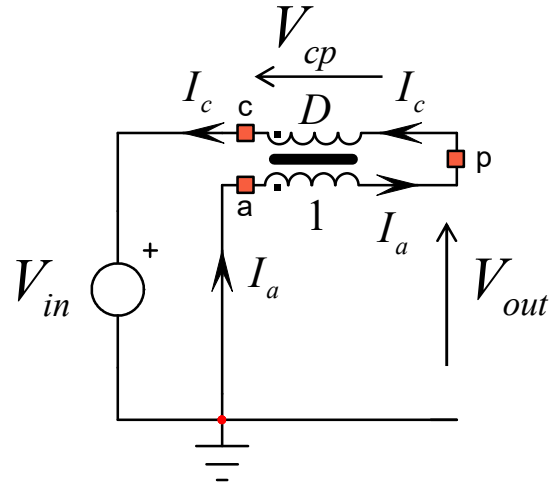
- Write dc equations to define the dc transfer function



$$V_{in} - V_{cp} = V_{out} \quad V_{cp} = -DV_{out}$$

$$V_{in} + DV_{out} = V_{out} \quad \frac{V_{out}}{V_{in}} = \frac{1}{1-D} = \frac{1}{D'}$$

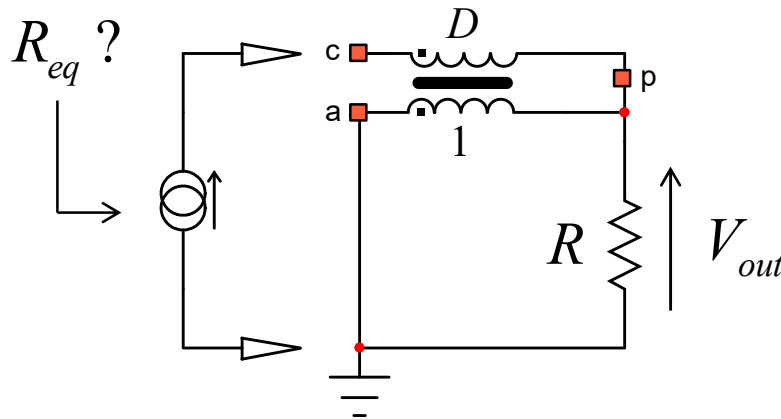- Apply a similar technique to reflect impedances




$$P_{out} = P_{in} = \frac{V_{out}^2}{R} = \frac{V_{in}^2}{R_{eq}} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} R_{eq} = RD'^2$$

$$\frac{V_{out}^2}{R} = \frac{V_{out}^2 D'^2}{R_{eq}}$$

Simplify the Circuit and Solve it!

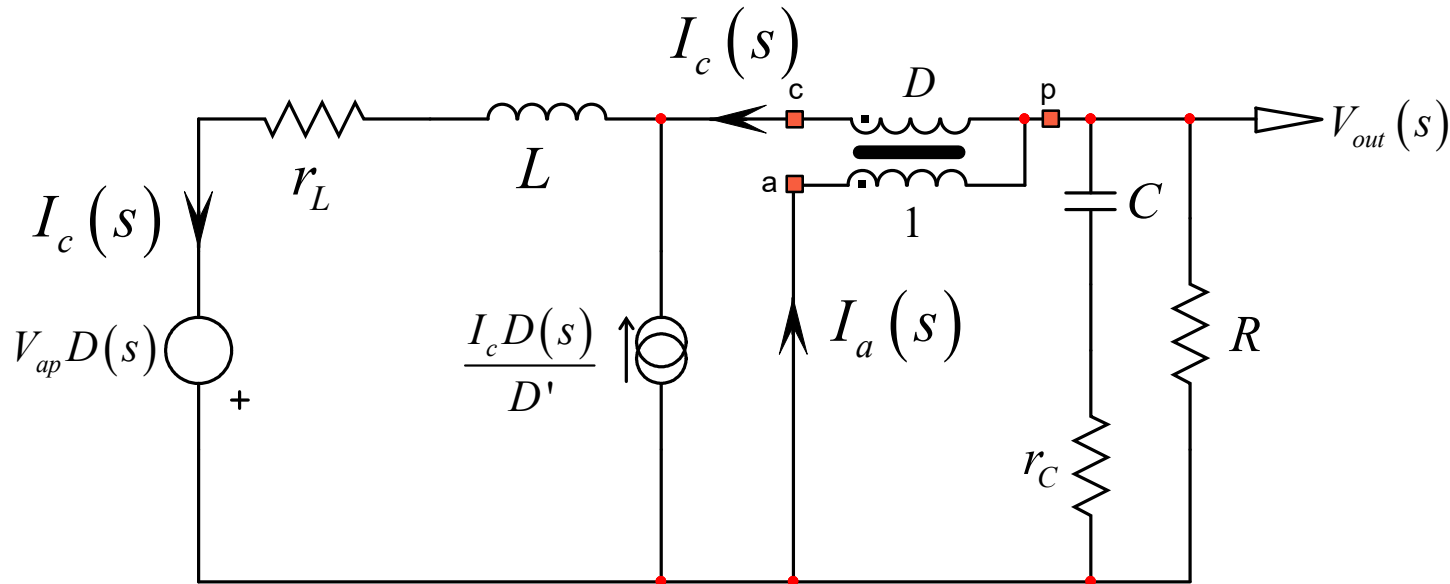- The circuit can now be updated with Laplace notations




- We have two storage elements, it is a second-order system

$$H(s) = \frac{V_{out}(s)}{D(s)} = H_0 \frac{N(s)}{D(s)} = H_0 \frac{(1 + s_{z_1})(1 + s_{z_2})(1 + \dots)}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

Identify the Zeros

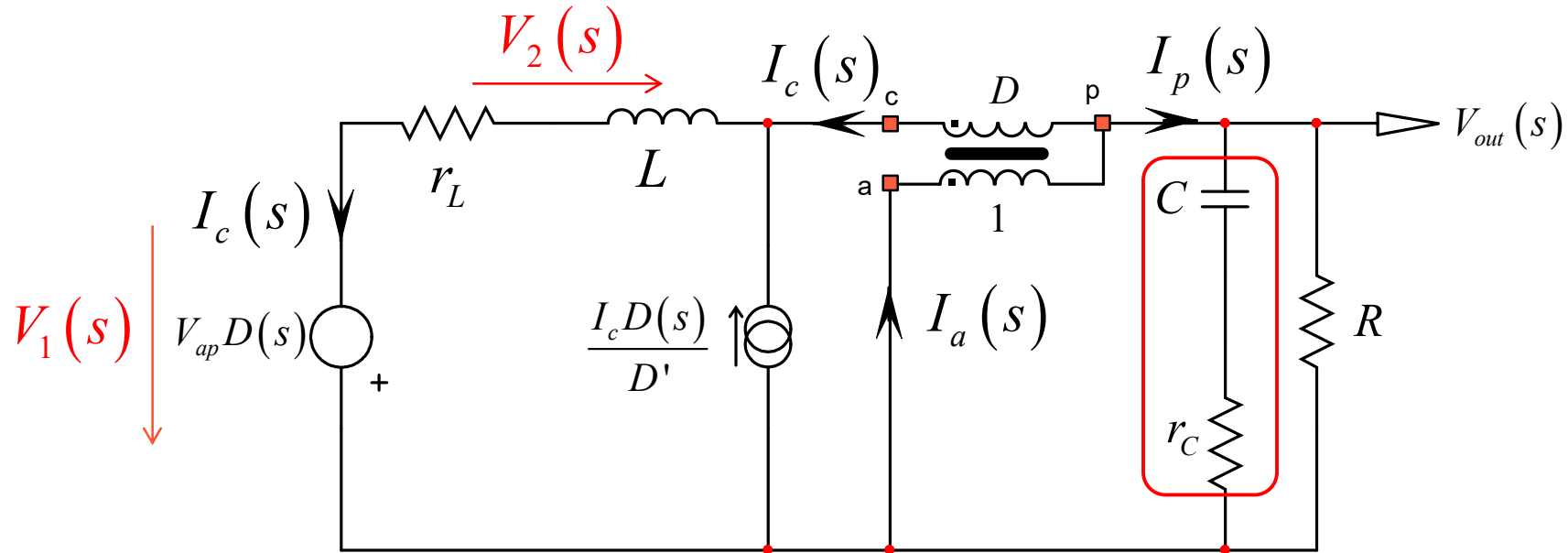- A zero prevents the excitation from reaching the output



- No response means: $r_c C$ is a short or $\hat{i}_p = 0$

$$\left. \begin{aligned} V_1(s) - V_2(s) &= 0 \\ r_c + \frac{1}{sC} &= 0 \end{aligned} \right\} \begin{aligned} V_{ap} D(s) - I_c(s)(sL + r_L) &= 0 \\ \frac{s r_c C + 1}{sC} &= 0 \end{aligned} \quad \Rightarrow \quad \text{Two zeros}$$

Identify the Zeros

- The first zero is straightforward

$$sr_c C + 1 = 0 \quad \longrightarrow \quad s_{z_1} = -\frac{1}{r_c C} \quad \text{This is a LHP zero}$$

- We know $I_a(s)$ from the small-signal model

$$I_a(s) = DI_c(s) + I_c D(s)$$

- Since $I_p(s) = 0$, we have $I_a(s) = I_c(s) \longrightarrow I_c(s) = DI_c(s) + I_c D(s)$

- We can rearrange the equations

$$V_{ap} D(s) - I_c(s)(sL + r_L) = 0 \quad \longrightarrow \quad I_c(s) = \frac{V_{ap} D(s)}{sL + r_L}$$

$$I_c(s) = DI_c(s) + I_c D(s) \longrightarrow I_c(s)(1 - D) = I_c D(s) \longrightarrow I_c(s) = \frac{I_c D(s)}{D'}$$




Identify the Zeros

□ Equate and solve for s

$$\frac{I_c \cancel{D(s)}}{D'} = \frac{V_{ap} \cancel{D(s)}}{sL + r_L} \longrightarrow s_{z_1} = \frac{D'V_{ap} - I_c r_L}{I_c L} = \frac{1}{L} \left(D' \frac{V_{ap}}{I_c} - r_L \right)$$

□ What is the value of I_c ?

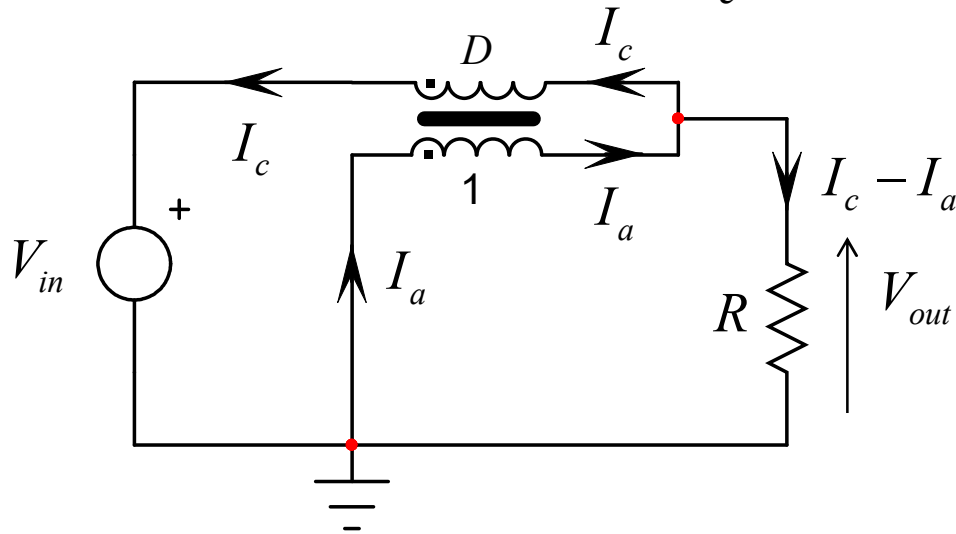

$$P_{in} = P_{out}$$

$$-I_c V_{in} = (I_c - I_a) V_{out} = I_{out} V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{D'}$$

$$\rightarrow I_c = -\frac{I_{out}}{D'}$$

$$\rightarrow V_{ap} = -V_{out}$$


$$\frac{V_{ap}}{I_c} = D'R$$

→ $s_{z_1} = \frac{1}{L} (D'^2 R - r_L)$ This is a RHP zero



Identify the Poles

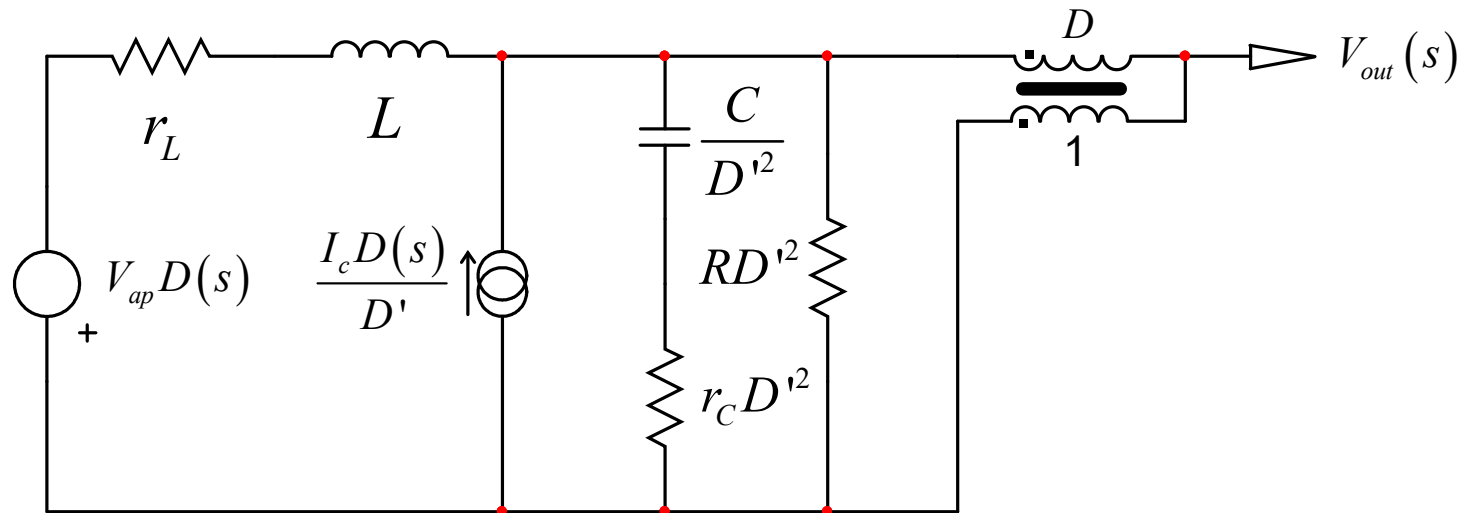
- Let's reflect the load and capacitor on the other side



- The denominator is solely dependent on the structure
 - It is independent from the excitation: set it to zero!
 - Identify the time constants

Identify the Poles

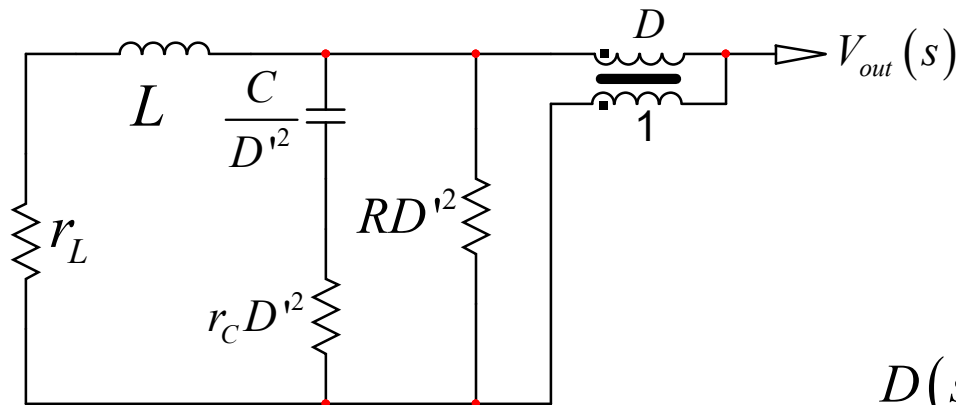- We reduce the excitation to zero: $D(s) = 0$



This is a two-storage elements network



$$D(s) = 1 + a_1 s + a_2 s^2 = 1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0} \right)^2$$

- D must be dimensionless thus: $a_1 \equiv (\text{Hz})^{-1}$ $a_2 \equiv (\text{Hz})^{-2}$


- The two possible terms for a_1 are $\left. \begin{matrix} \tau_1 + \tau_2 \\ \tau_1 \tau'_2 \\ \tau'_1 \tau_2 \end{matrix} \right\} \tau = \frac{L}{R} \text{ or } \tau = RC$
- The two possible terms for a_2 are

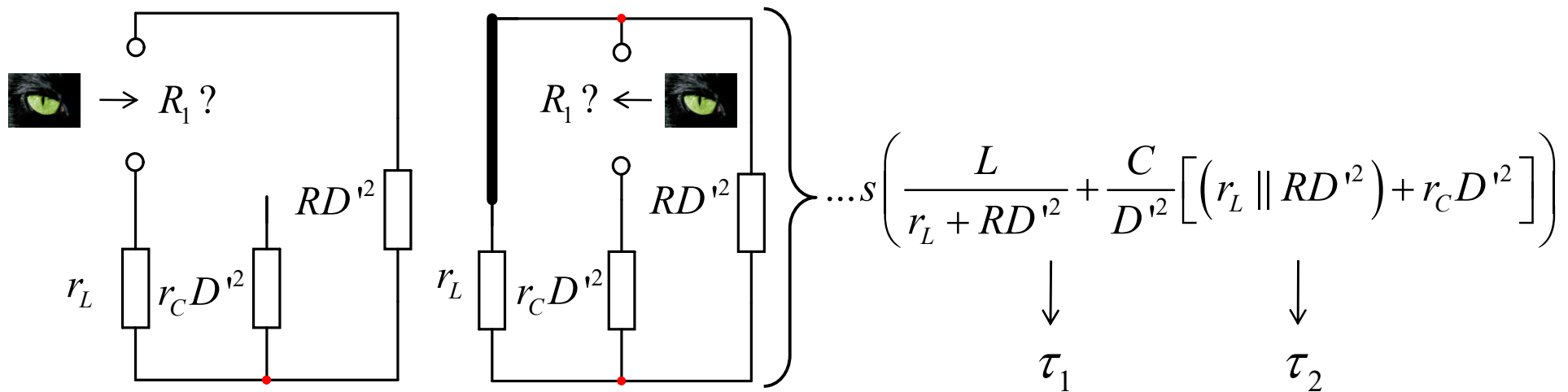B. Erickson, "The n Extra Element Theorem", <http://ecee.colorado.edu/copec/publications.php>



Identify the Poles

- For a_1 look at the resistance R driving L and C
- Look at the driving impedance at L while C is in its dc state
- Look at the driving impedance at C while L is in its dc state



$$R_1 = r_L + RD^2$$


$$R_1 = (r_L \parallel RD^2) + r_C D^2$$



Identify the Poles

- how τ_1 (involving L) combines with τ'_2 (involving C)?
- how τ_2 (involving C) combines with τ'_1 (involving L)? } a_2

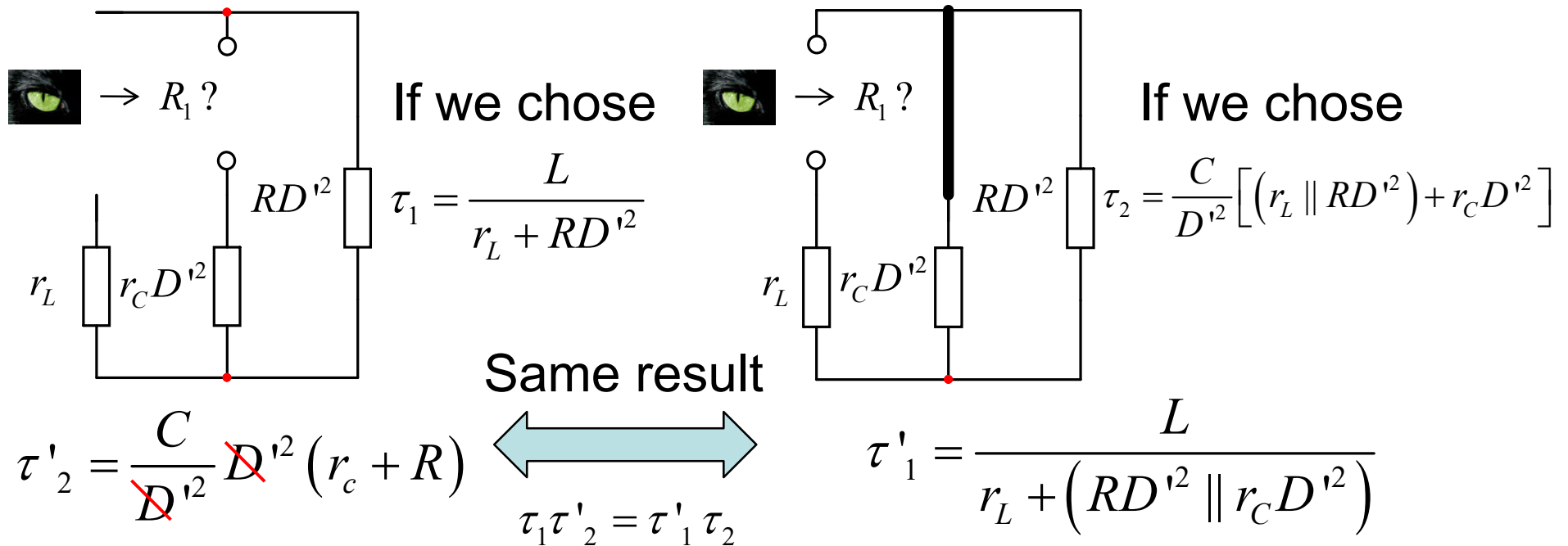- Look at the driving impedance at C while L is in its HF state
- Look at the driving impedance at L while C is in its HF state



Identify the Poles

- We have our denominator!

$$D(s) = 1 + s \left(\frac{L}{r_L + RD'^2} + C \left[\left(\frac{r_L R}{r_L + RD'^2} \right) + r_C \right] \right) + s^2 \left(LC \frac{(r_C + R)}{r_L + RD'^2} \right)$$

- We can identify the terms

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{r_L + RD'^2}{r_C + R}} \quad Q \approx \frac{\omega_0}{\frac{r_L}{L} + \frac{1}{C(r_C + R)}}$$

- The dc term H_0 in the transfer function is:

$$H_0 = \frac{dV_{out}(D)}{dD} \quad V_{out}(D) \approx \frac{V_{in}}{1-D} \quad \longrightarrow \quad H_0 = \frac{V_{in}}{(D-1)^2} = \frac{V_{in}}{D'^2}$$



The CCM Boost Transfer Function

□ The final transfer function can be written as:

$$\frac{V_{out}(s)}{D(s)} = H_0 \frac{\left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 - \frac{s}{\omega_{z_2}}\right)}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2} \quad \omega_{z_1} = \frac{1}{r_C C} \quad \omega_{z_2} = \frac{1}{L} (D'^2 R - r_L)$$


$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{r_L + RD'^2}{r_C + R}} \quad Q \approx \frac{\omega_0}{\frac{r_L}{L} + \frac{1}{C(r_C + R)}} \quad H_0 \approx \frac{V_{in}}{D'^2}$$

□ Time to check the ac response versus simulation!



Checking Ac Responses

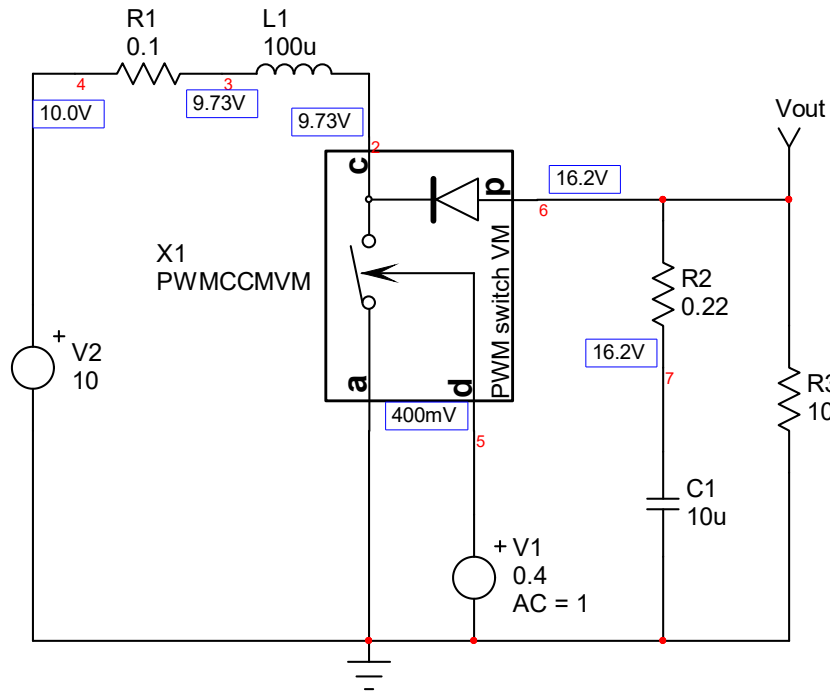- Capture a simple boost converter schematic



$$V_{in} := 10V \quad D := 0.4$$

$$V_{out} := \frac{V_{in}}{1-D} = 16.667V \quad D_a := 1 - D = 0.6$$

$$L_1 := 100\mu H \quad C_1 := 10\mu F \quad r_L := 0.1\Omega \quad r_C := 0.22\Omega \quad R_1 := 10\Omega$$

$$\omega_{z1} := \frac{1}{r_C \cdot C_1} \quad \omega_{z2} := \frac{1}{L_1} \cdot (D_a^2 \cdot R_1 - r_L) \quad f_1 := \frac{\omega_{z1}}{2\pi} = 72.343\text{kHz} \quad \text{ESR zero}$$

$$\omega_0 := \frac{1}{\sqrt{L_1 \cdot C_1}} \sqrt{\frac{r_L + D_a^2 \cdot R_1}{r_C + R_1}} \quad f_2 := \frac{\omega_{z2}}{2\pi} = 5.57 \times 10^3 \text{ Hz} \quad \text{RHP zero}$$

$$f_0 := \frac{\omega_0}{2\pi} = 3.028 \times 10^3 \text{ Hz}$$

$$Q := \frac{1}{\omega_0 \left[C_1 \cdot \left(r_C + \frac{R_1 \cdot r_L}{R_1 \cdot D_a^2 + r_L} \right) + \frac{L_1}{R_1 \cdot D_a^2 + r_L} \right]} = 1.646$$

$$H_0 := \frac{V_{in}}{D_a^2}$$


$$H_1(s) := H_0 \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \cdot \left(1 - \frac{s}{\omega_{z2}}\right)}{1 + \frac{s}{\omega_0 \cdot Q} + \left(\frac{s}{\omega_0}\right)^2}$$

- Check the result versus a Mathcad[®] spreadsheet



Checking the Ac Responses

- The curves must perfectly superimpose

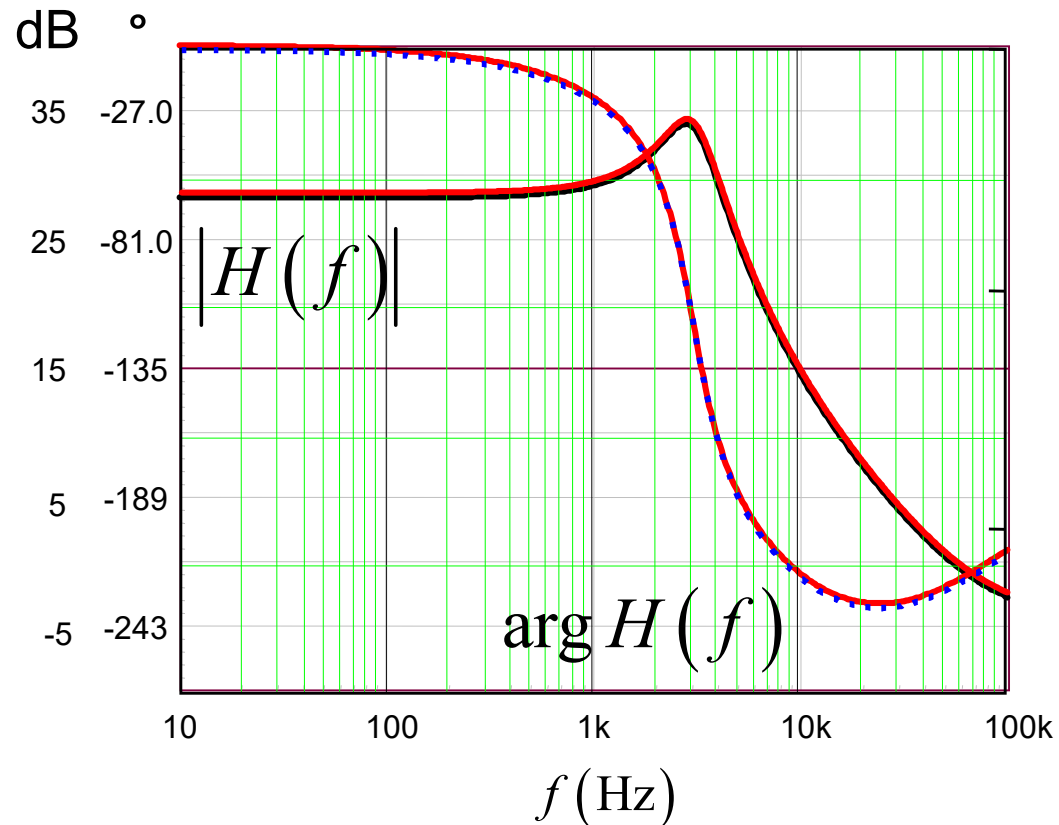

- If not, go back to the sheet and fix the equations!



Agenda

- Linear and Non-Linear Functions
- What is a Small-Signal Model?
- Fast Analytical Techniques at Work
- From a Switched to Linearized Model
- The CCM VM Small-Signal PWM Switch Model
- The DCM VM Small-Signal PWM Switch Model**
- Peak Current Mode Control in Large Signal
- The CCM CM Small-Signal PWM Switch Model
- The DCM CM Small-Signal PWM Switch Model
- The PWM Switch in Boundary Mode




The Discontinuous Case

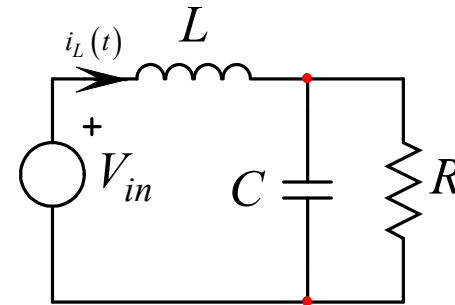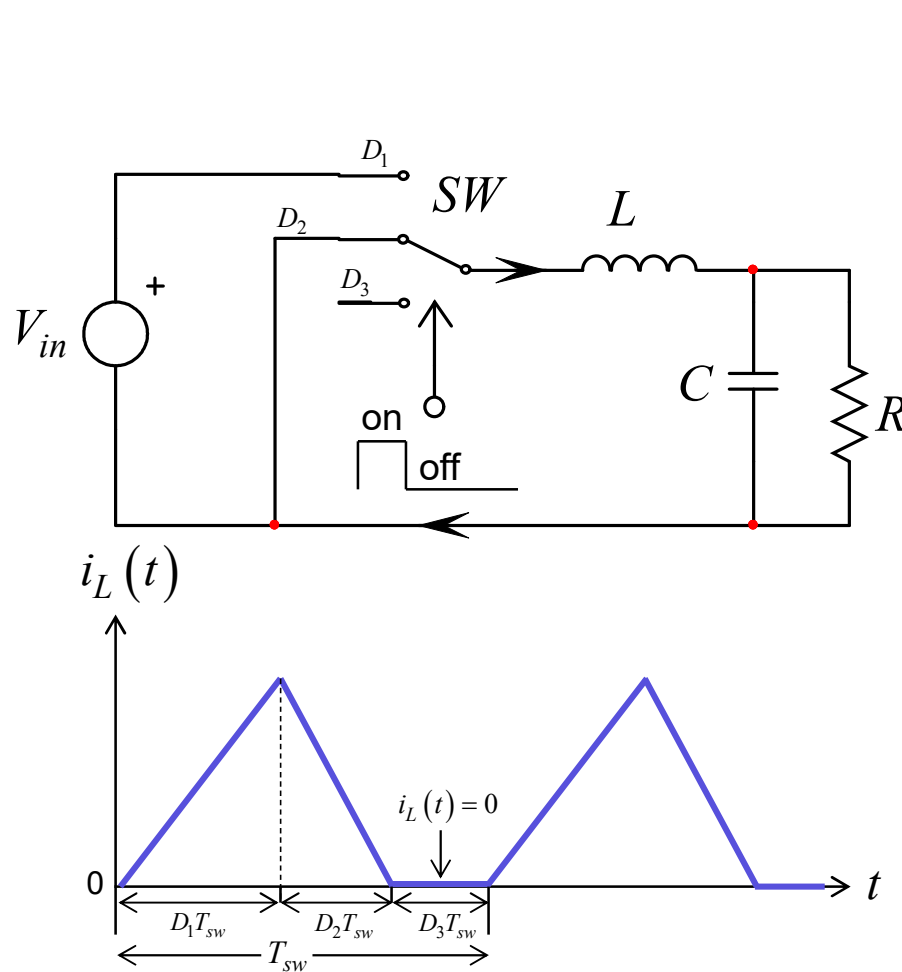
□ In DCM, a third timing event exists when $i_L(t) = 0$



during $D_1 T_{sw}$

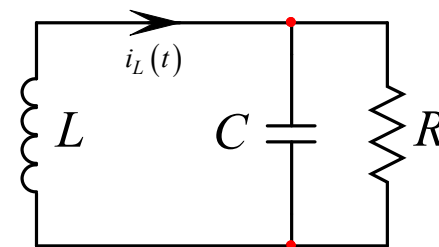

during $D_2 T_{sw}$


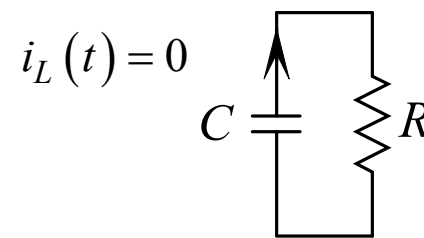


during $D_3 T_{sw}$



The Same Configuration as in CCM

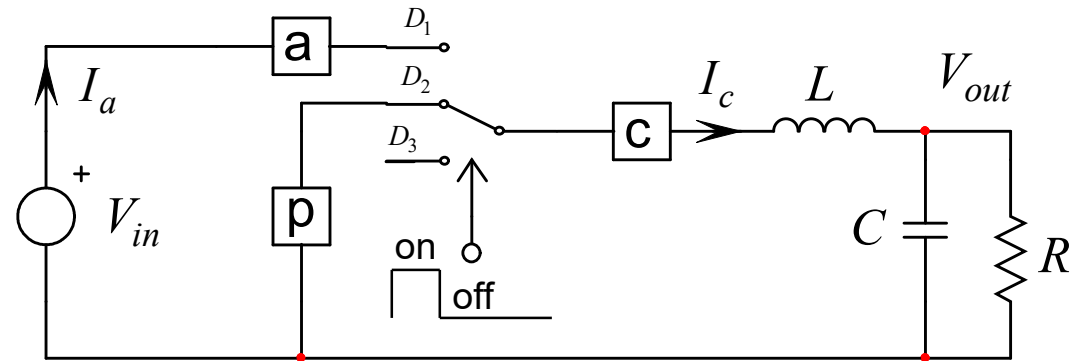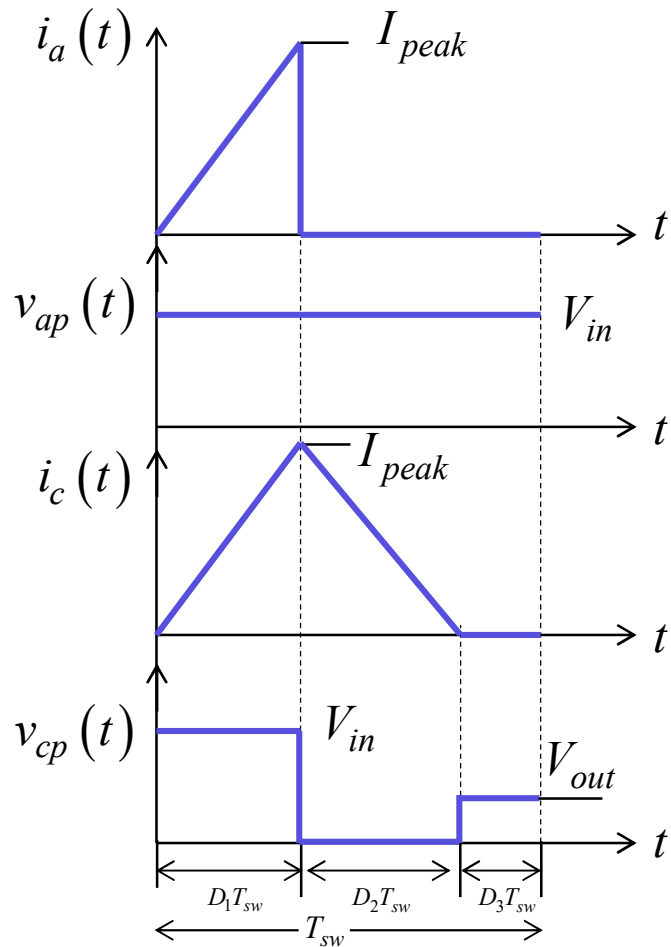□ Draw the waveforms in the "common passive" configuration



□ Average the waveforms:


$$I_a = \frac{I_{peak}}{2} D_1$$

$$I_c = \frac{I_{peak}}{2} D_1 + \frac{I_{peak}}{2} D_2 = \frac{I_{peak}}{2} (D_1 + D_2)$$

$$I_c = \frac{2I_a}{D_1} \frac{D_1 + D_2}{2} = I_a \frac{D_1 + D_2}{D_1}$$

Derive V_{cp} to Unveil the New Model

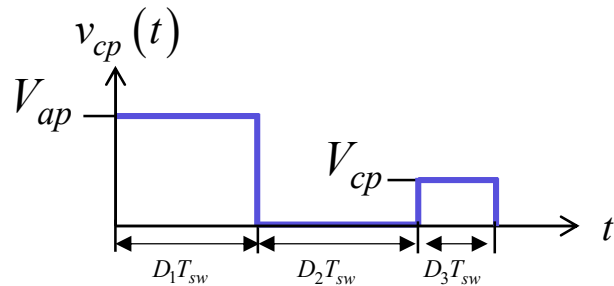
□ The addition of the third event complicates the equations



$$V_{cp} = V_{ap} D_1 + V_{cp} D_3 \quad D_1 + D_2 + D_3 = 1$$

$$V_{cp} = V_{ap} D_1 + V_{cp} (1 - D_1 - D_2)$$
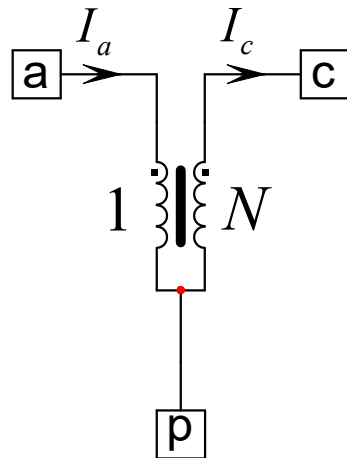
$$V_{cp} = V_{ap} \frac{D_1}{D_1 + D_2}$$




$$I_a = N I_c$$

$$I_c = \frac{I_a}{N}$$

$$V_{ap} = \frac{V_{cp}}{N}$$

$$V_{cp} = N V_{ap}$$

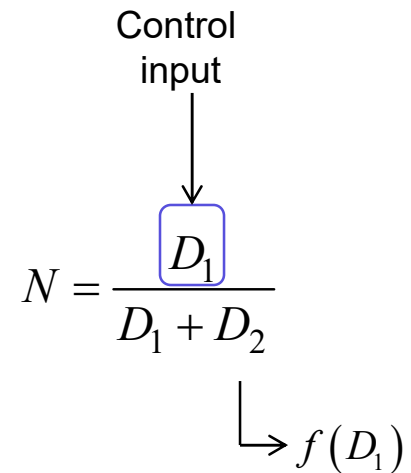

Finally, Get the D_2 Value

- In DCM the inductor average voltage per cycle is always 0

$$\longrightarrow V_{cp} = V_{out}$$

- What is the averaged inductor peak current?

$$\left. \begin{aligned} I_{peak} &= \frac{\langle v_L(t) \rangle_{D_1 T_{sw}}}{L} D_1 T_{sw} \\ \langle v_L(t) \rangle_{D_1 T_{sw}} &= V_{ac} \end{aligned} \right\} V_{ac} = L \frac{I_{peak}}{D_1 T_{sw}}$$

- The peak current uses a previous expression

$$I_c = \frac{I_{peak}}{2} (D_1 + D_2) \longrightarrow I_{peak} = \frac{2I_c}{D_1 + D_2}$$

$$\longrightarrow D_2 = \frac{2LF_{sw}}{D_1} \frac{I_c}{V_{ac}} - D_1$$

CCM to DCM Auto-Toggling is Possible

- We have two equations for the DCM model

$$I_c = I_a \frac{D_1 + D_2}{D_1} \quad V_{cp} = V_{ap} \frac{D_1}{D_1 + D_2}$$

- When D_3 shrinks and finally disappears

$$D_1 + D_2 + D_3 = 1 \longrightarrow D_2 = 1 - D_1$$

- If you substitute D_2 in the two above equations

$$\left. \begin{aligned} I_c &= I_a \frac{D_1 + (1 - D_1)}{D_1} \longrightarrow I_a = D_1 I_c \\ V_{cp} &= V_{ap} \frac{D_1}{D_1 + (1 - D_1)} \longrightarrow V_{cp} = D_1 V_{ap} \end{aligned} \right\} \text{CCM equations}$$



Clamp the Equation to Auto Toggle

- D_2 in DCM is smaller than D_2 in CCM

$$D_{2,DCM} = 1 - D_1 - D_3 \quad D_{2,CCM} = 1 - D_1$$

- Clamping D_2 equation to $1 - D_1$ offers auto-toggling

$$\text{IF } \frac{2LF_{sw}}{D_1} \frac{I_c}{V_{ac}} - D_1 > 1 - D_1 \text{ THEN } D_2 = 1 - D_1 \text{ (CCM)}$$

$$\text{ELSE } D_2 = \frac{2LF_{sw}}{D_1} \frac{I_c}{V_{ac}} - D_1 \text{ (DCM)}$$

- SPICE offers several means to clamp

Ed2 d2 0 value = { IF (((2*{L}*{Fs}*I(VM))/(V(dc)*V(a,c)+1u)) - V(dc)) > (1-V(D)), 1-V(D),
+ 2*{L}*{Fs}*I(VM)/(V(dc)*V(a,c)+1u)) - V(dc)) } PSpice


Bd2 d2 0 V = ((2*{L}*{Fs}*I(VM))/(V(dc)*V(a,c)+1u)) - V(dc) > (1-V(D)) ? 1-V(D) :
+ (2*{L}*{Fs}*I(VM))/(V(dc)*V(a,c)+1u)) - V(dc) IsSpice

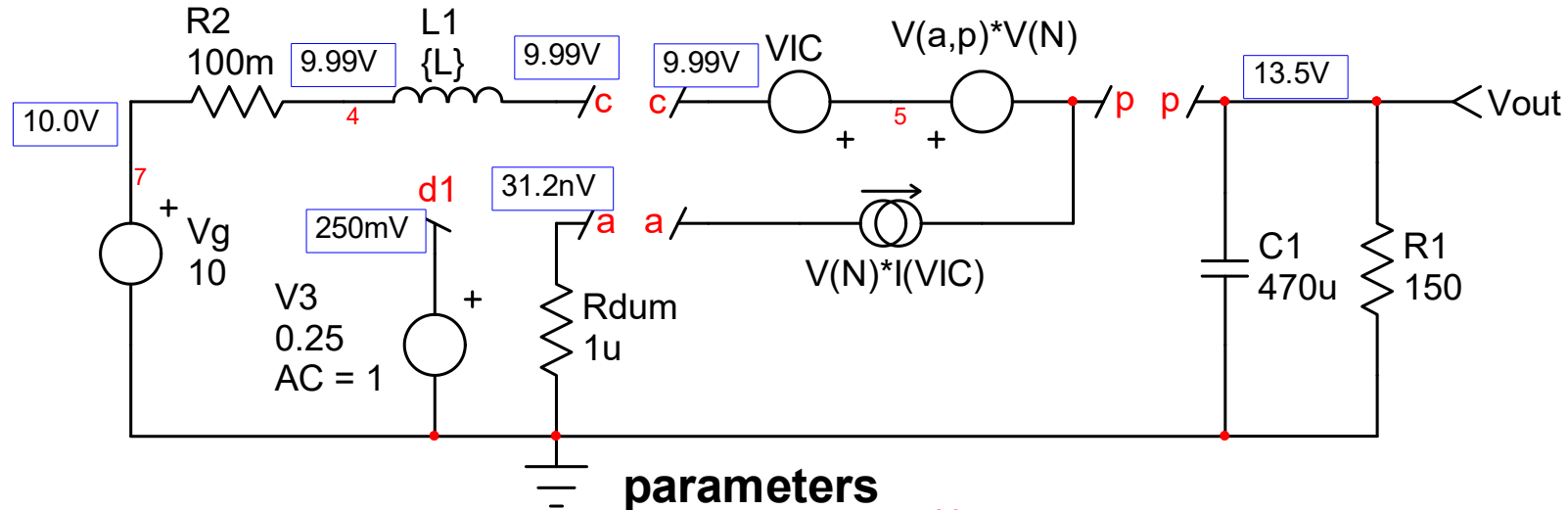C. Basso, "SMPS: SPICE Simulations and Practical Designs", McGraw-Hill 2008






Run a Simulation Immediately!

- Re-use the CCM boost example and plug the DCM model



parameters

Fsw=100k
L=100u

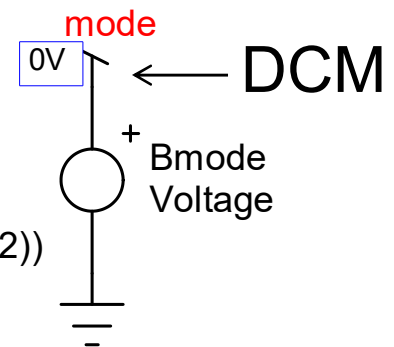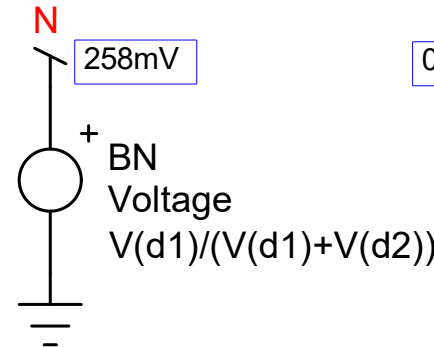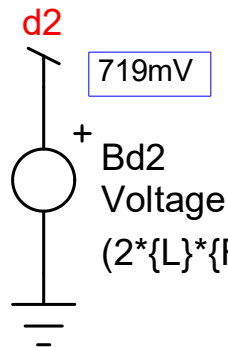


$$(2 * \{L\} * \{Fsw\} * I(VIC) / (V(d1) * V(a,c))) - V(d1) > (1 - V(d1)) ?$$

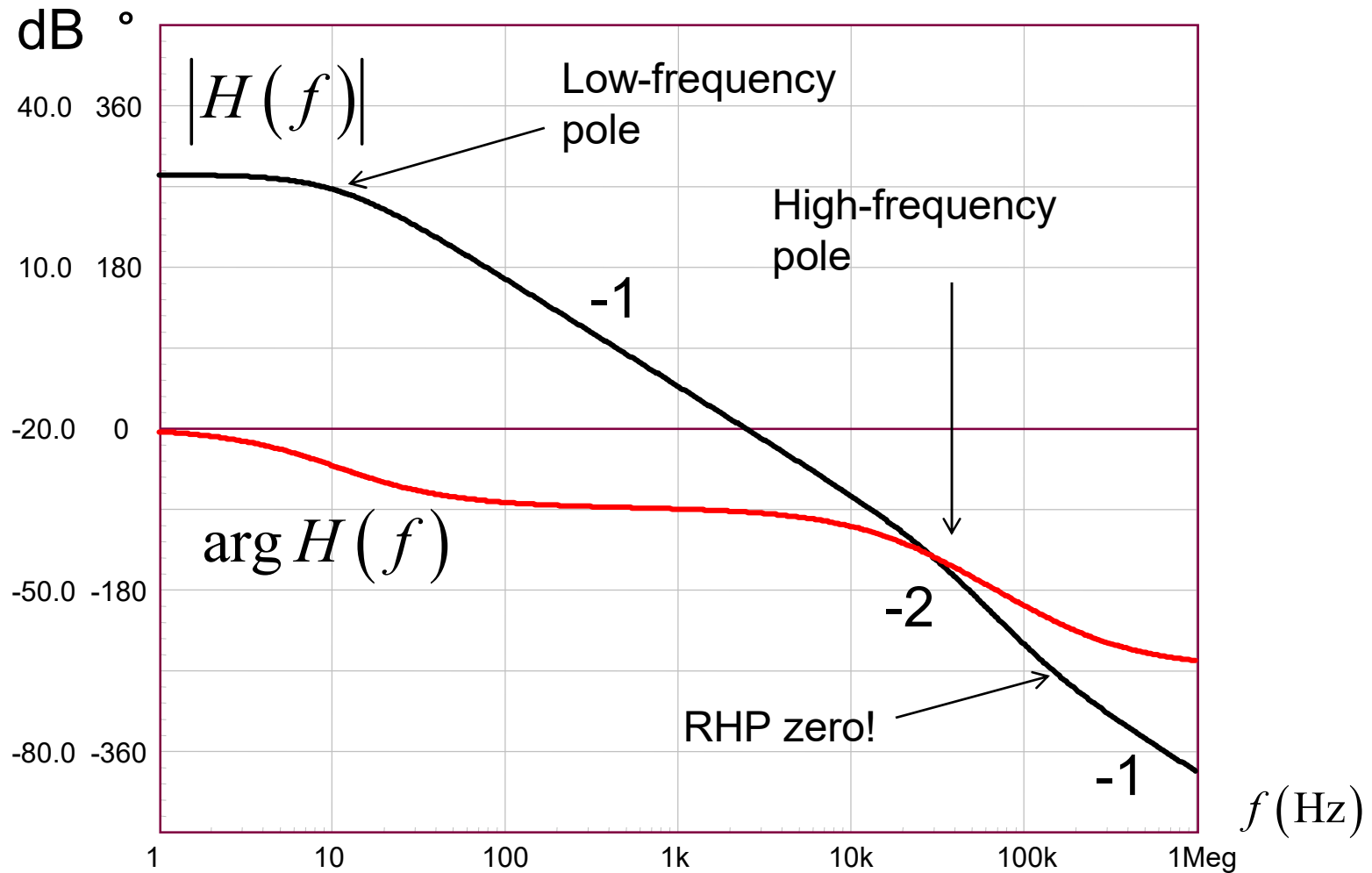1 : 0



Ac Response in a Snapshot

- The ac response is that of a second-order system!



Calculate the Dc Operating Point


□ Let's rework the DCM model to fit that of the CCM

$$N = \frac{D_1}{D_1 + D_2}$$

$$D_2 = \frac{2LF_{sw}}{D_1} \frac{I_c}{V_{ac}} - D_1$$

$$N = \frac{V_{ac} D_1^2}{2F_{sw} I_c L}$$

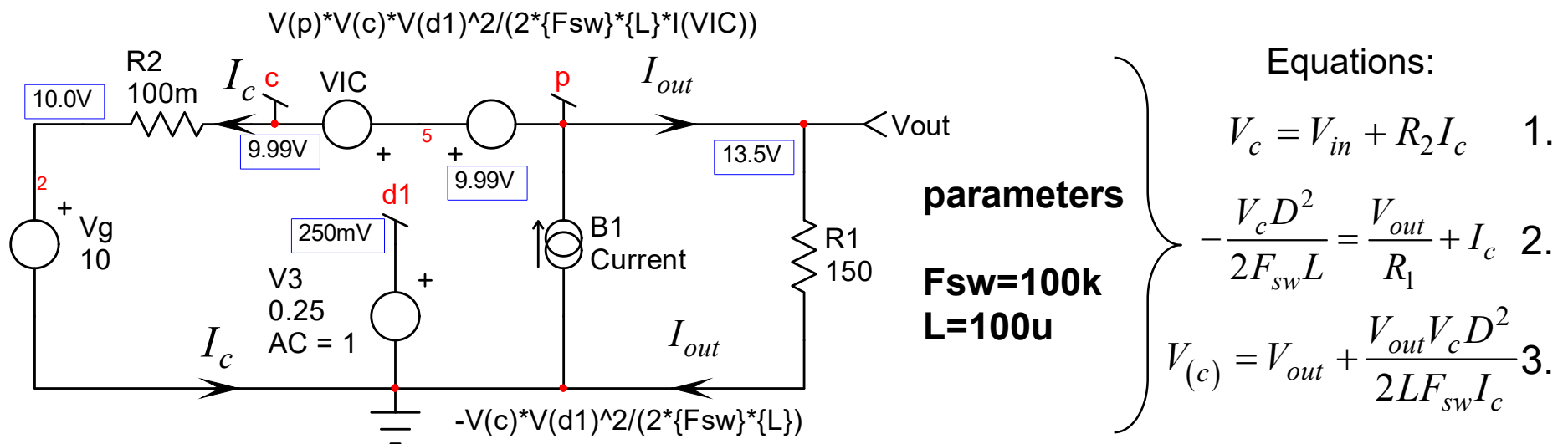□ Short inductors, open caps. and verify bias point



Identify the Duty Ratio and M Expressions

□ Solve I_c and V_c from the first equations:

$$\longrightarrow V_{(c)} = \frac{V_{in} - \frac{V_{out}R_2}{R_1}}{\frac{D^2R_2}{2LF_{sw}} + 1} \approx V_{in} \quad \text{Voltage at node c}$$

$R_2 = 0$

$$\longrightarrow I_c = -\frac{R_1V_{in}D^2 + 2LF_{sw}V_{out}}{R_1(R_2D^2 + 2F_{sw}L)} \approx \frac{V_{out}}{R_1} \left(-1 - \frac{V_{in}D^2R_1}{2LV_{out}F_{sw}} \right)$$

□ Substitute these variables in the third equation

$$V_{in} = \frac{2LF_{sw}V_{out}^2}{R_1V_{in}D^2 + 2LF_{sw}V_{out}}$$

$$D = \sqrt{\frac{2LF_{sw}V_{out} \left(\frac{V_{out}}{V_{in}} - 1 \right)}{V_{in}R_1}} = 0.251 \quad \text{ok}$$

$$\left(\frac{V_{in}}{V_{out}} \right)^2 R_1 D^2 + 2LF_{sw} \frac{V_{in}}{V_{out}} = 2LF_{sw}$$


$(1/M)^2 \qquad M$

$$M = \frac{1}{2} \left(1 + \sqrt{1 + \frac{2R_1D^2}{LF_{sw}}} \right) = 1.348 \quad \text{ok}$$



Deriving the Small-Signal Model

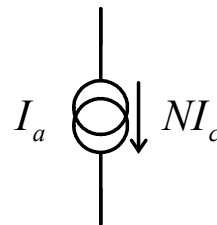- Large-signal expressions require linearization
- Apply partial derivatives to the equations



3 variables

$$\hat{i}_a = \frac{\partial f(D_1, I_c, V_{ac})}{\partial D_1} \hat{d}_1 + \frac{\partial f(D_1, I_c, V_{ac})}{\partial I_c} \hat{i}_c + \frac{\partial f(D_1, I_c, V_{ac})}{\partial V_{ac}} \hat{v}_{ac}$$

- Mathcad[®] automates the process easily


$$\hat{i}_a = \frac{V_{ac} D_1}{F_{sw} L} \hat{d}_1 + \frac{D_1^2}{2F_{sw} L} \hat{v}_{ac} \quad k_1 = \frac{V_{ac} D_1}{F_{sw} L} \quad k_2 = \frac{D_1^2}{2F_{sw} L}$$

$$\hat{i}_a = k_1 \hat{d}_1 + k_2 \hat{v}_{ac}$$

Small-Signal Sources in DCM

- Small-signal perturbations would be more difficult!

4 variables

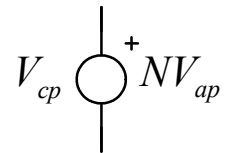

$$\hat{v}_{cp} = \frac{\partial f(D_1, I_c, V_{ac}, V_{ap})}{\partial D_1} \hat{d}_1 + \frac{\partial f(D_1, I_c, V_{ac}, V_{ap})}{\partial V_{ap}} \hat{v}_{ap} + \frac{\partial f(D_1, I_c, V_{ac}, V_{ap})}{\partial I_c} \hat{i}_c + \frac{\partial f(D_1, I_c, V_{ac}, V_{ap})}{\partial V_{ac}} \hat{v}_{ac}$$

$$\hat{v}_{cp} = \frac{V_{ap} V_{ac} D_1}{F_{sw} I_c L} \hat{d}_1 + \frac{V_{ac} D_1^2}{2 F_{sw} I_c L} \hat{v}_{ap} - \frac{V_{ap} V_{ac} D_1^2}{2 F_{sw} I_c^2 L} \hat{i}_c + \frac{V_{ap} D_1^2}{2 F_{sw} I_c L} \hat{v}_{ac}$$

$$k_3 = \frac{V_{ap} V_{ac} D_1}{F_{sw} I_c L} \quad k_4 = \frac{V_{ac} D_1^2}{2 F_{sw} I_c L} \quad k_5 = -\frac{V_{ap} V_{ac} D_1^2}{2 F_{sw} I_c^2 L} \quad k_6 = \frac{V_{ap} D_1^2}{2 F_{sw} I_c L}$$

$$\hat{v}_{cp} = k_3 \hat{d}_1 + k_4 \hat{v}_{ap} + k_5 \hat{i}_c + k_6 \hat{v}_{ac}$$

- A sanity check is recommended before proceeding




Verifying the Intermediate Step

□ A SPICE simulation will let us know if the derivation is ok


parameters

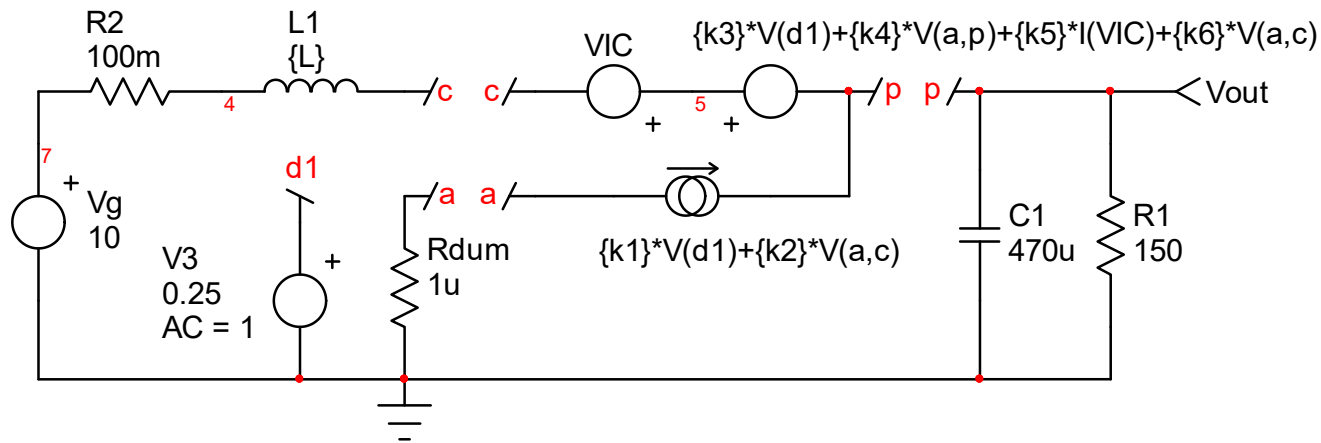Fsw=100k
L=100u
d1=250m
Vac=-9.99
Vap=-13.5
Ia=-31.21m
Ic=-120.956m




$k1 = Vac \cdot d1 / (Fsw \cdot L)$
 $k2 = d1^2 / (2 \cdot Fsw \cdot L)$
 $k3 = Vac \cdot Vap \cdot d1 / (Fsw \cdot L \cdot Ic)$
 $k4 = Vac \cdot d1^2 / (2 \cdot Fsw \cdot L \cdot Ic)$
 $k5 = -Vac \cdot Vap \cdot d1^2 / (2 \cdot Fsw \cdot Ic^2 \cdot L)$
 $k6 = Vap \cdot d1^2 / (2 \cdot Fsw \cdot Ic \cdot L)$

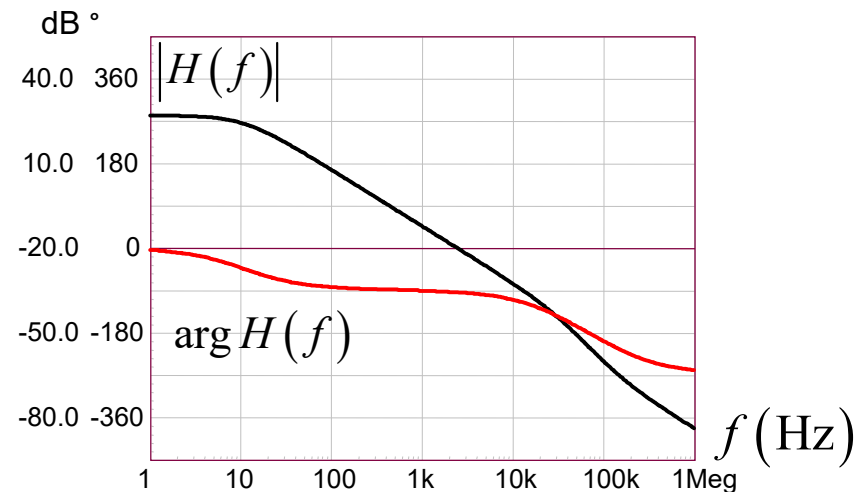Same results as with
 large-signal model!



Carefully Deriving the Expressions

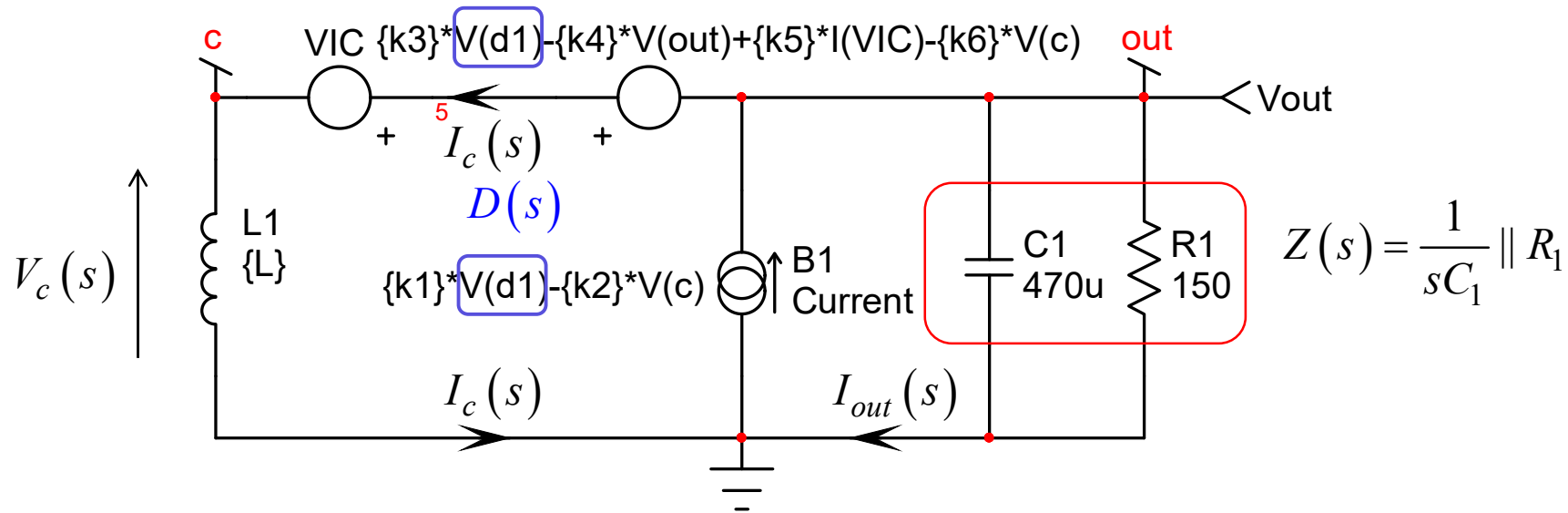- The circuit can be further simplified as $\hat{v}_{in} = 0$ is zero



- There are three equations

$$V_c(s) = I_c(s)sL$$

$$V_c(s) = V_{out}(s) + k_3 D(s) - k_4 V_{out}(s) + k_5 I_c(s) - k_6 V_c(s)$$

$$I_c(s) = k_1 D(s) - k_2 V_c(s) - \frac{V_{out}(s)}{Z(s)} - I_{out}(s)$$

Rearranging the Expression

□ Further to a few manipulations, you should find

$$H(s) = \frac{V_{out}(s)}{D(s)} = \frac{R_1 k_3 + R_1 k_1 k_5}{k_5 - R_1 + R_1 k_4} \frac{\left(1 - sL \frac{k_1 - k_2 k_3 + k_1 k_6}{k_3 + k_1 k_5}\right)}{1 + s \left(\frac{R_1 k_5 C_1 + L(R_1 k_2 k_4 - 1 - k_6 - R_1 k_2)}{k_5 - R_1 + R_1 k_4}\right) + s^2 C_1 L \frac{R_1 + R_1 k_6}{R_1 - k_5 - R_1 k_4}}$$

□ This is a second-order system affected by a RHP zero

$$H(s) = G_0 \frac{1 - \frac{s}{s_{z_1}}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2} \quad G_0 = \frac{R_1 k_3 + R_1 k_1 k_5}{k_5 - R_1 + R_1 k_4}$$

$$\omega_{z_1} = \frac{1}{L \left(\frac{k_1 - k_2 k_3 + k_1 k_6}{k_3 + k_1 k_5}\right)} \quad Q = \frac{k_5 / R_1 - 1 + k_4}{\omega_0 \left(L \left(\frac{k_6}{R_1} + k_2 - k_2 k_4 + \frac{1}{R_1}\right) - C_1 k_5\right)} \quad \omega_0 = \frac{1}{\sqrt{LC_1}} \sqrt{\frac{1 - \frac{k_5}{R_1} - k_4}{1 + k_6}}$$



A Low-Q System

- A second-order system features two poles
- These poles are the characteristic equation roots

$$D(s) = 1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2 \xrightarrow{D(s)=0} s_{p_1}, s_{p_2} = \frac{\omega_0}{2} \frac{1 \pm \sqrt{1-4Q^2}}{Q}$$

- When Q is low, use MacLaurin series to simplify

$$x \ll 1 \longrightarrow (1+x)^n \approx 1+nx \longrightarrow \sqrt{1+x} \approx 1+\frac{1}{2}x$$

$$\left. \begin{aligned} s_{p_1} &= \frac{\omega_0}{Q} \frac{1 + \sqrt{1-4Q^2}}{2} \approx -\frac{\omega_0}{Q} (Q^2 - 1) \approx \frac{\omega_0}{Q} \\ s_{p_2} &= \frac{\omega_0}{Q} \frac{1 - \sqrt{1-4Q^2}}{2} \approx \frac{\omega_0}{Q} \frac{1 - (1-2Q^2)}{2} \approx Q\omega_0 \end{aligned} \right\} D(s) \approx \left(1 + \frac{s}{s_{p_1}}\right) \left(1 + \frac{s}{s_{p_2}}\right)$$

- A 2nd-order low- Q system is equivalent to 2 cascaded poles




A Simpler Expression

- We can thus rewrite a simpler transfer function

$$H(s) \approx G_0 \frac{\left(1 - \frac{s}{s_{z_1}}\right) \left(1 + \frac{s}{s_{z_2}}\right)}{\left(1 + \frac{s}{s_{p_1}}\right) \left(1 + \frac{s}{s_{p_2}}\right)}$$

← Adding the ESR

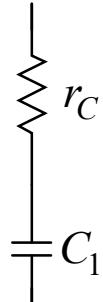
 $\frac{sr_C C_1 + 1}{sC_1} = 0$

- Further to rearranging, simplifying and having fun...

$$G_0 \approx \frac{2}{2M-1} \sqrt{\frac{M(M-1)R_1}{2F_{sw}L}} \quad \omega_{p_1} \approx \frac{2M-1}{M} \frac{1}{R_1 C_1} \quad \omega_{p_2} \approx 2F_{sw} \left(\frac{1-1/M}{D}\right)^2 \geq 2F_{sw}$$

$$\omega_{z_1} \approx \frac{R_2}{M^2 L} \geq 2F_{sw} \quad \omega_{z_2} \approx \frac{1}{r_C C_1}$$


- The DCM model is of the same order as the CCM model
- The difference is in the damping

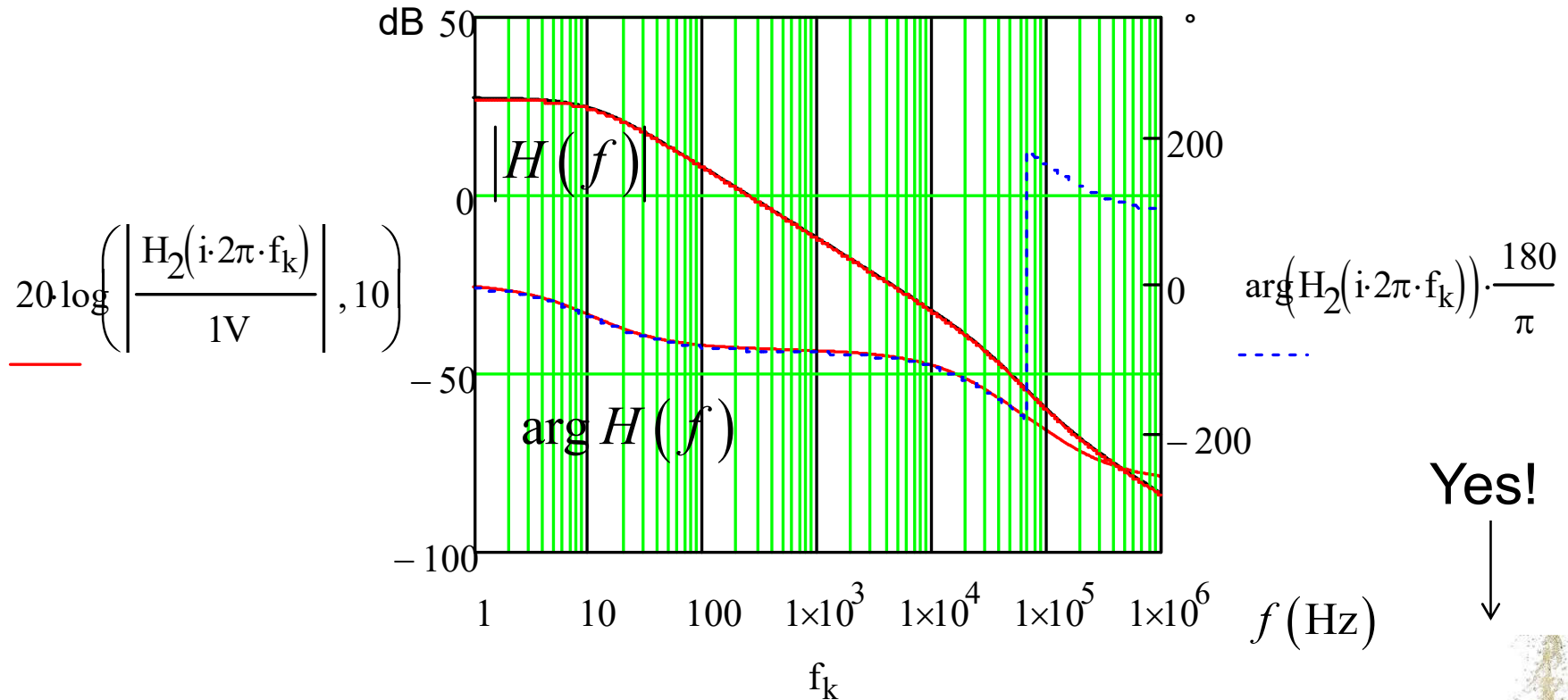V. Vorpérian, "Analytical Methods in Power Electronics", In-house class, Toulouse, 2004



Full Mathcad® Expression versus SPICE

□ The curves perfectly superimpose, calculations are correct!



Yes!




$$H_2(s) := \frac{(R_1 \cdot k_3 + R_1 \cdot k_1 \cdot k_5)}{(k_5 - R_1 + R_1 \cdot k_4)} \cdot \frac{\left[1 - s \cdot L_1 \cdot \left(\frac{k_1 - k_2 \cdot k_3 + k_1 \cdot k_6}{k_3 + k_1 \cdot k_5} \right) \right]}{1 + s \cdot \left[\frac{R_1 \cdot k_5 \cdot C_1 + L_1 \cdot (R_1 \cdot k_2 \cdot k_4 - 1 - k_6 - R_1 \cdot k_2)}{k_5 - R_1 + R_1 \cdot k_4} \right] + s^2 \cdot C_1 \cdot L_1 \cdot \frac{(R_1 + R_1 \cdot k_6)}{(-k_5 + R_1 - R_1 \cdot k_4)}}$$



Why a RHP Zero in DCM?

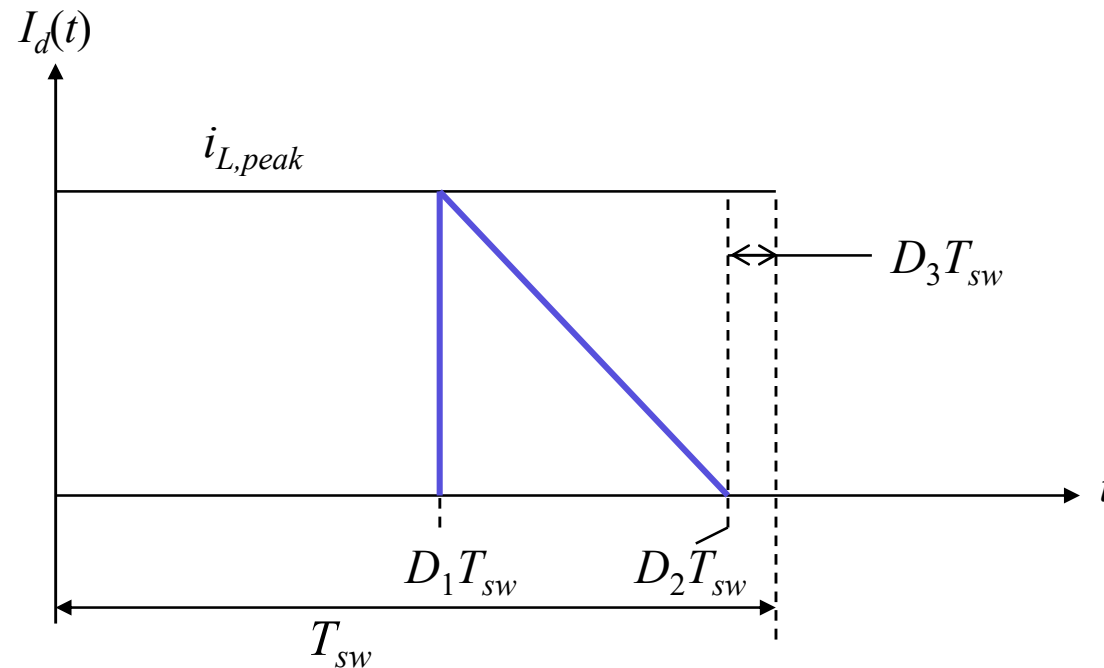
- The RHP Zero is present in CCM and is still there in DCM!



- When D_1 increases, $[D_1, D_2]$ stays constant but D_3 shrinks

Why a RHP Zero in DCM?



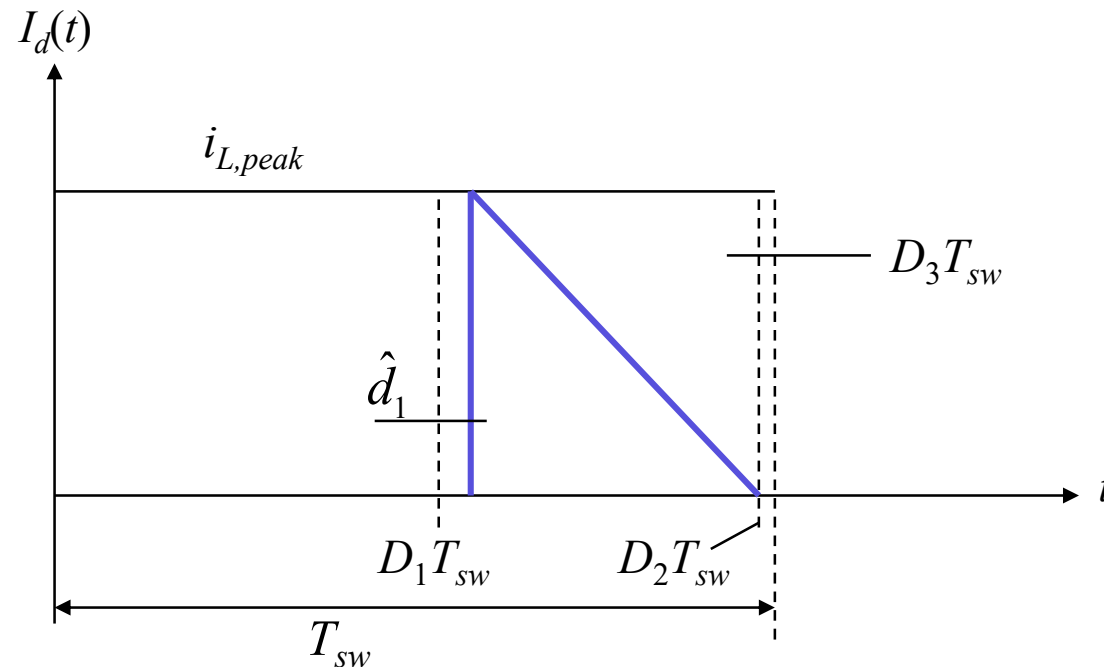
- The triangle is simply shifted to the right by \hat{d}_1



- The capacitor refueling time is delayed and a drop occurs

The Refueling Time is Shifted

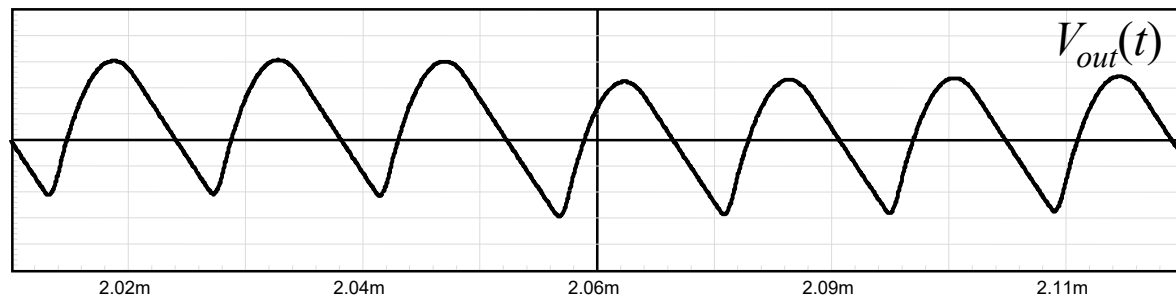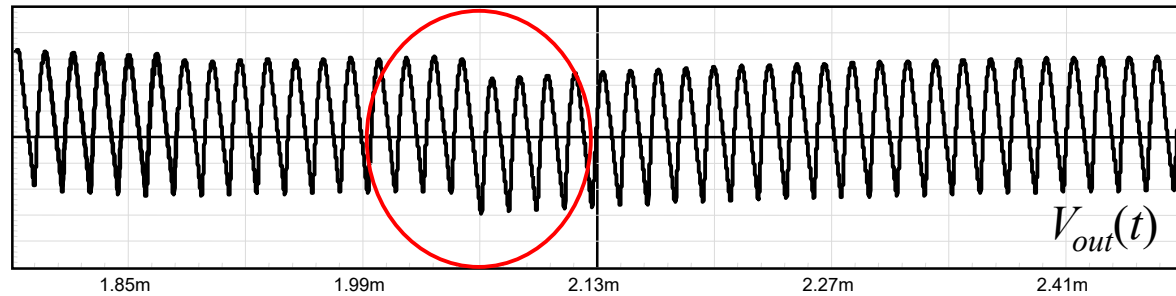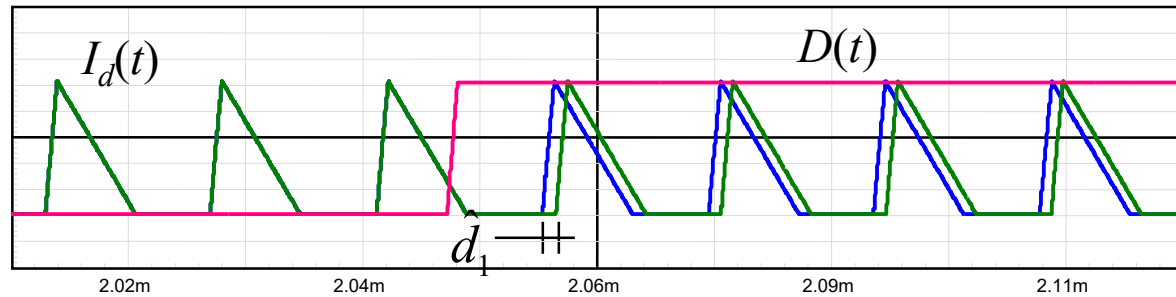- If D increases, the diode current is delayed by \hat{d}_1



Simulation, no peak increase




Course Agenda

- Linear and Non-Linear Functions
- What is a Small-Signal Model?
- Fast Analytical Techniques at Work
- From a Switched to Linearized Model
- The CCM VM Small-Signal PWM Switch Model
- The DCM VM Small-Signal PWM Switch Model
- Peak Current Mode Control in Large Signal**
- The CCM CM Small-Signal PWM Switch Model
- The DCM CM Small-Signal PWM Switch Model
- The PWM Switch in Boundary Mode



Peak Current Mode Control

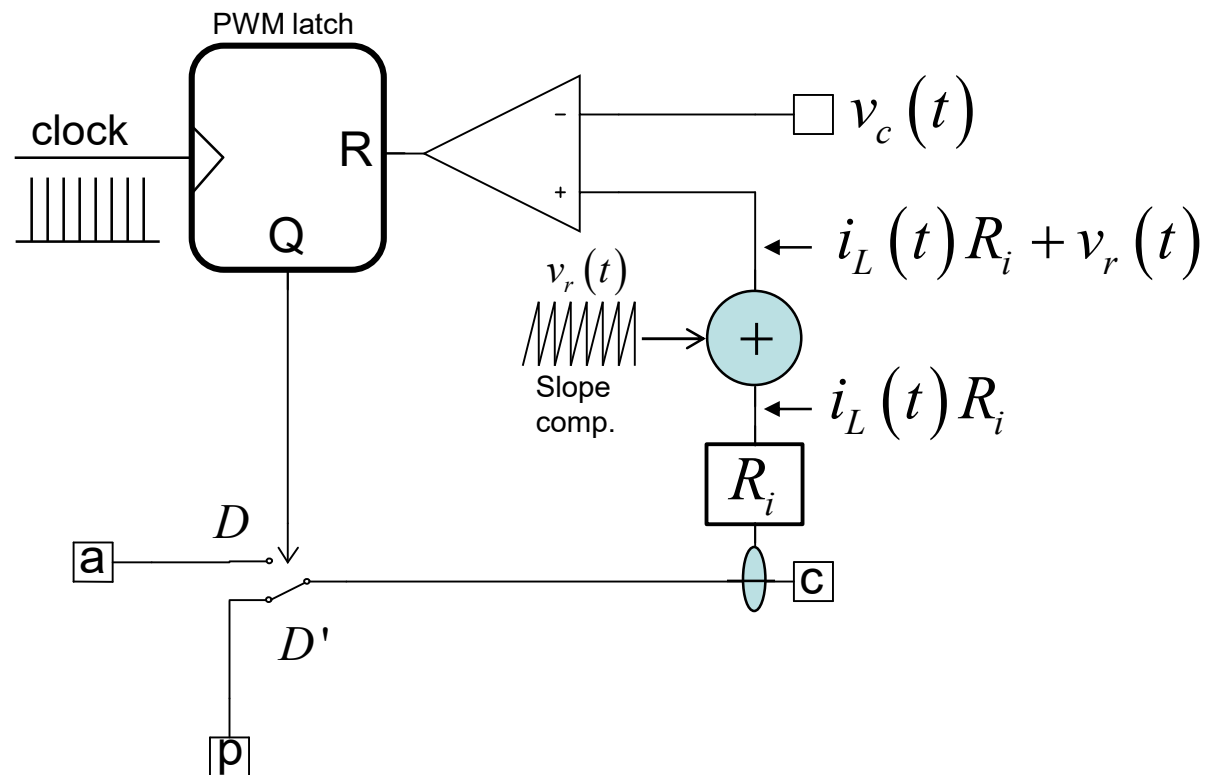
- ❑ In voltage-mode, the loop controls the duty ratio
- ❑ In current-mode, the inductor peak current is controlled



- ❑ An artificial ramp is added for stabilization purposes


How Does a Perturbation Propagate?

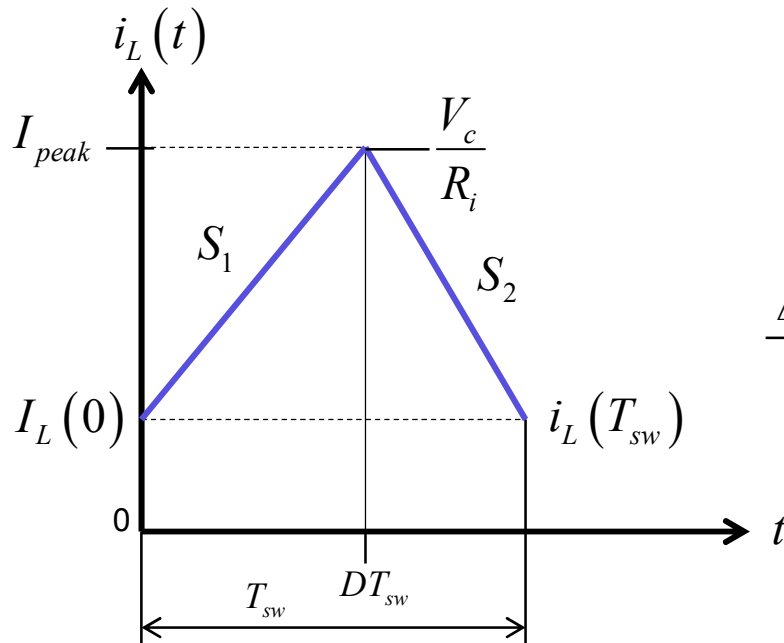- The perturbation is carried cycle by cycle in CCM



$$I_L(T_{sw}) = I_L(0) + \underbrace{S_1DT_{sw} - S_2D'T_{sw}}_{=0}$$
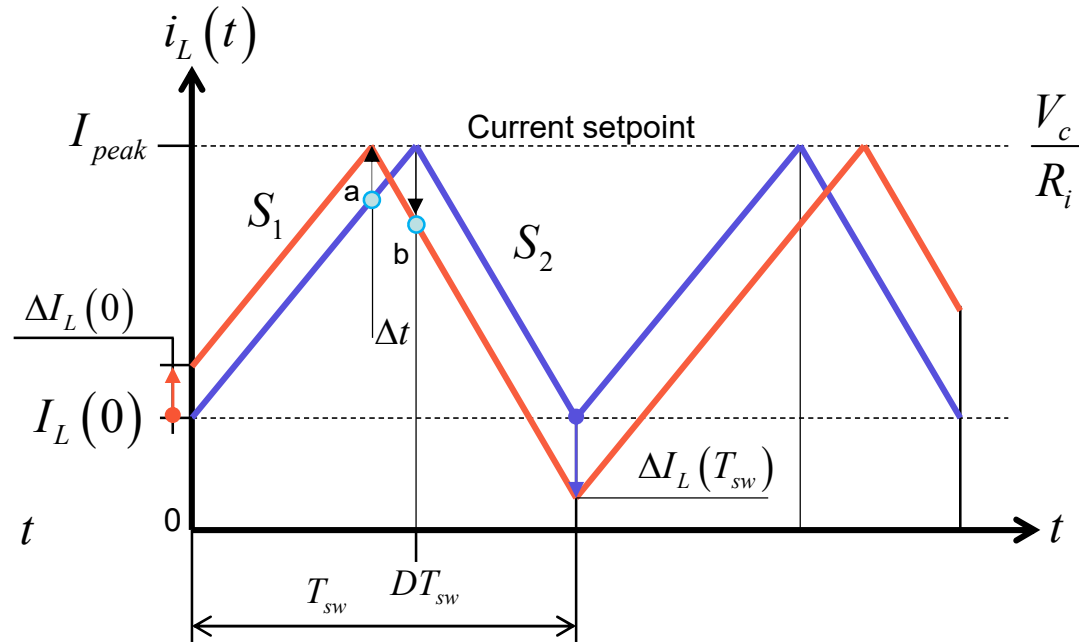
$$S_1DT_{sw} = S_2D'T_{sw} \longrightarrow \frac{S_2}{S_1} = \frac{D}{D'}$$




$$I_{peak} = a + S_1\Delta t \quad b = I_{peak} - S_2\Delta t$$

$$\frac{\Delta I_L(0)}{S_1} = \frac{\Delta I_L(T_{sw})}{S_2}$$

generalized \longrightarrow $\Delta I_L(nT_{sw}) = \Delta I_L(0) \left(-\frac{D}{D'}\right)^n$




Instability in CCM for $D > 50\%$

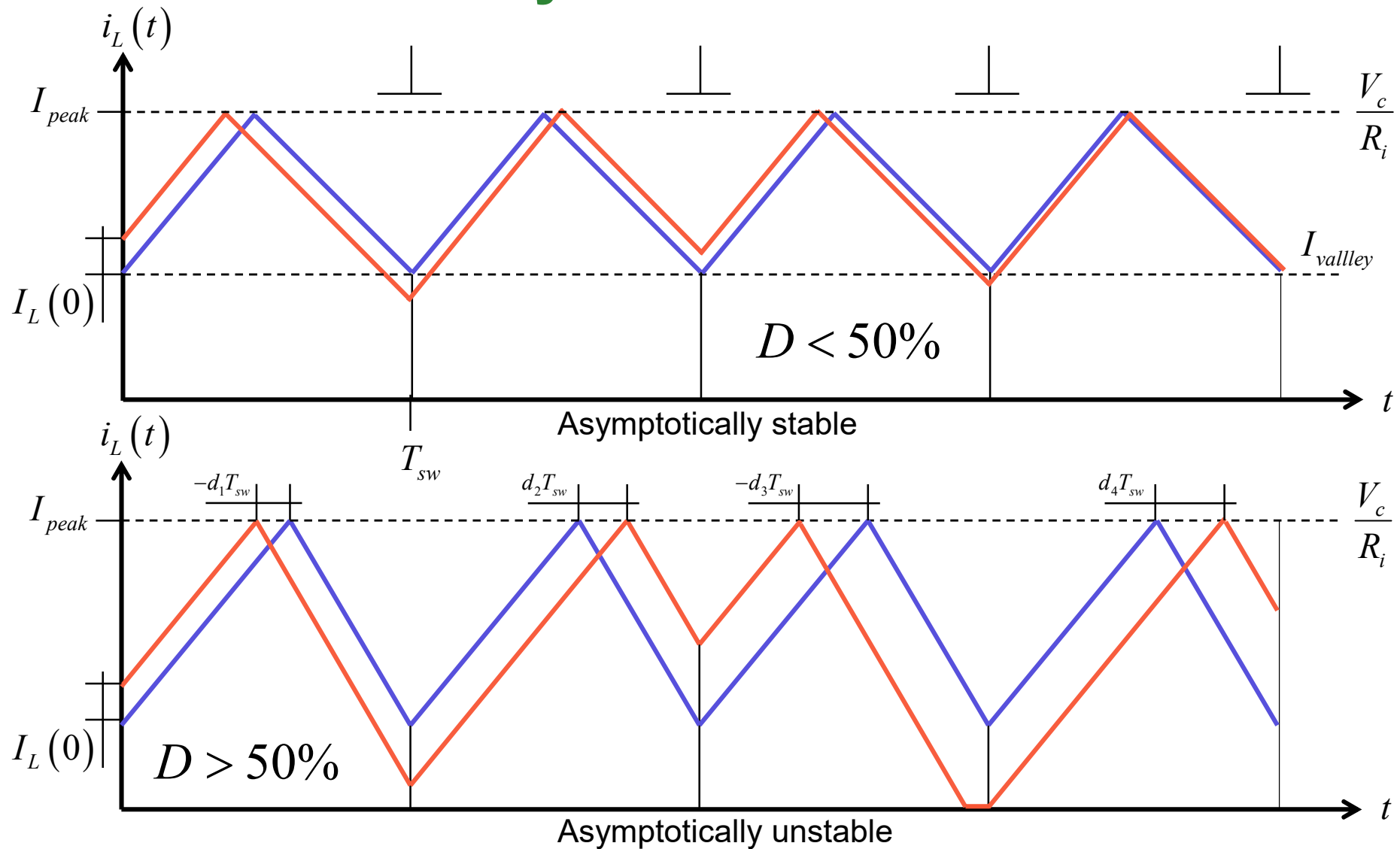

Add an Artificial Ramp

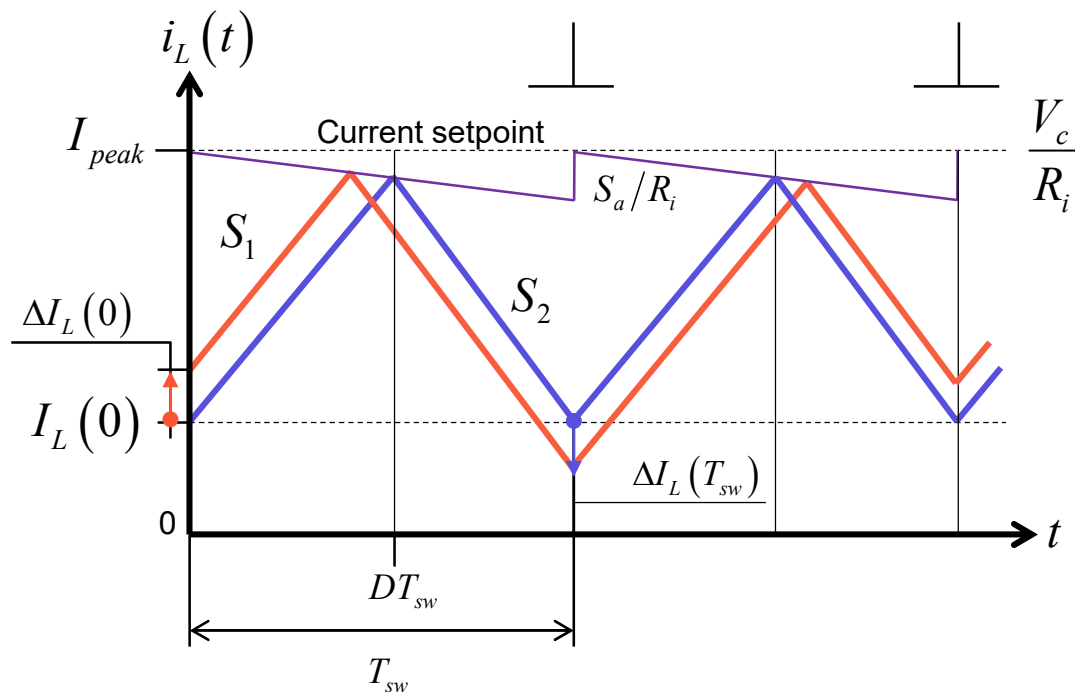- An external ramp helps to stabilize the current



$$\Delta I_L(nT_{sw}) = \Delta I_L(0) \left[\frac{1 - \frac{S_a}{S_2}}{\frac{D'}{D} + \frac{S_a}{S_2}} \right]^n$$

0 for 100%
duty ratio

$$\left| \frac{1 - \frac{S_a}{S_2}}{0 + \frac{S_a}{S_2}} \right| < 1$$


$$S_a > 50\% S_2$$

- Considering 100% duty ratio overcompensates the design



What is the Control Law in CCM?

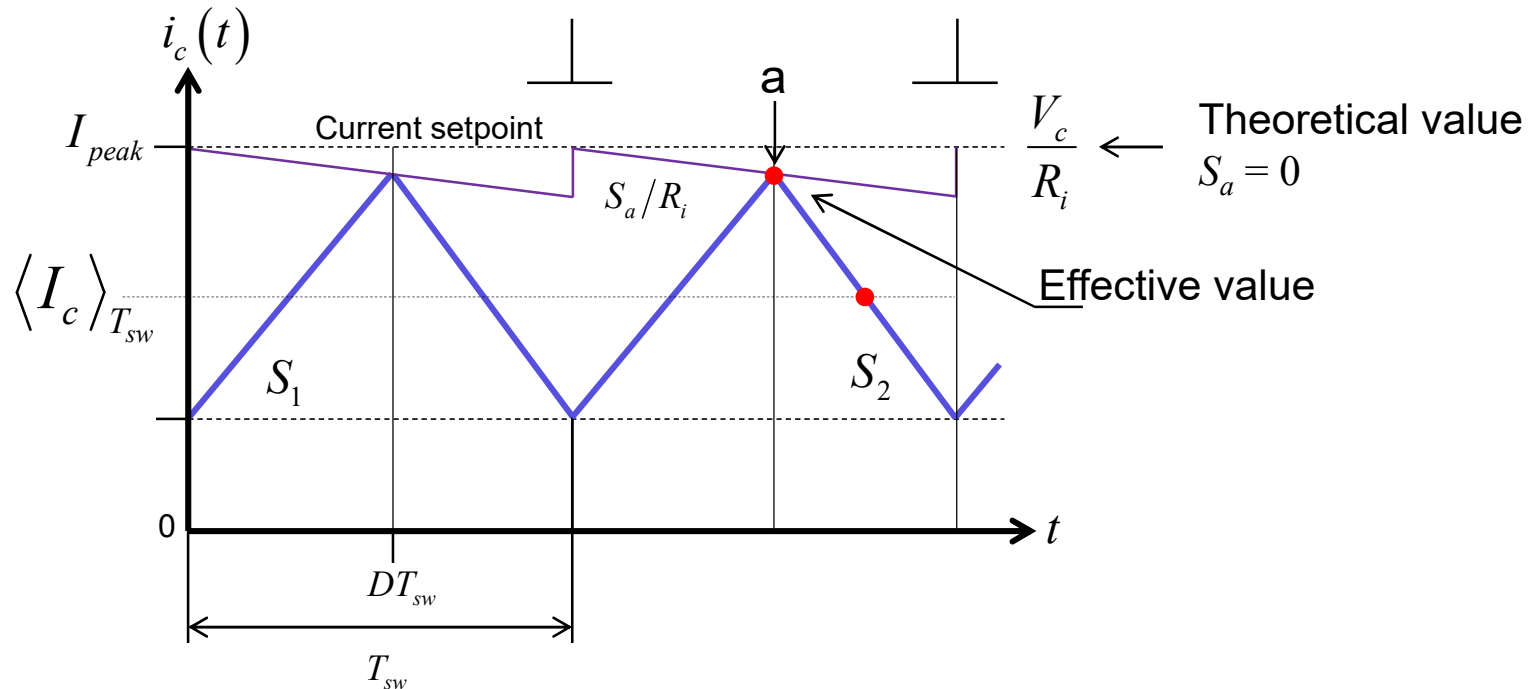- Draw the primary current with a stabilization ramp S_a




- The current at point **a** is defined by:

$$I_{c(a)} = \frac{V_c}{R_i} - \frac{S_a DT_{sw}}{R_i}$$

We Want the Average Current Definition

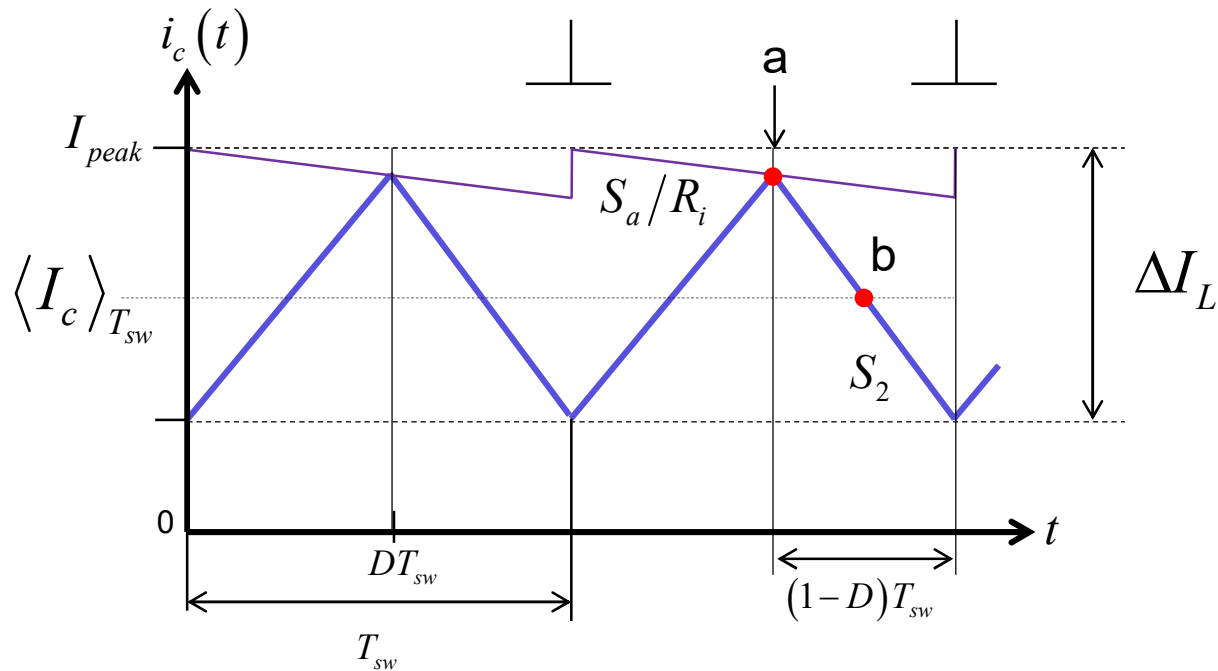- The value I_c is the inductor current at half the ripple




- Express current at point **b** and substitute the **a** definition

$$I_{c(b)} = \langle I_c \rangle_{T_{sw}} = I_{c(a)} - \frac{\Delta I_L}{2} = I_{c(a)} - \frac{S_2 D' T_{sw}}{2} \longrightarrow \langle I_c \rangle_{T_{sw}} = \frac{V_c}{R_i} - \frac{S_a}{R_i} D T_{sw} - \frac{S_2 D' T_{sw}}{2}$$

Define the Converter off-Slope

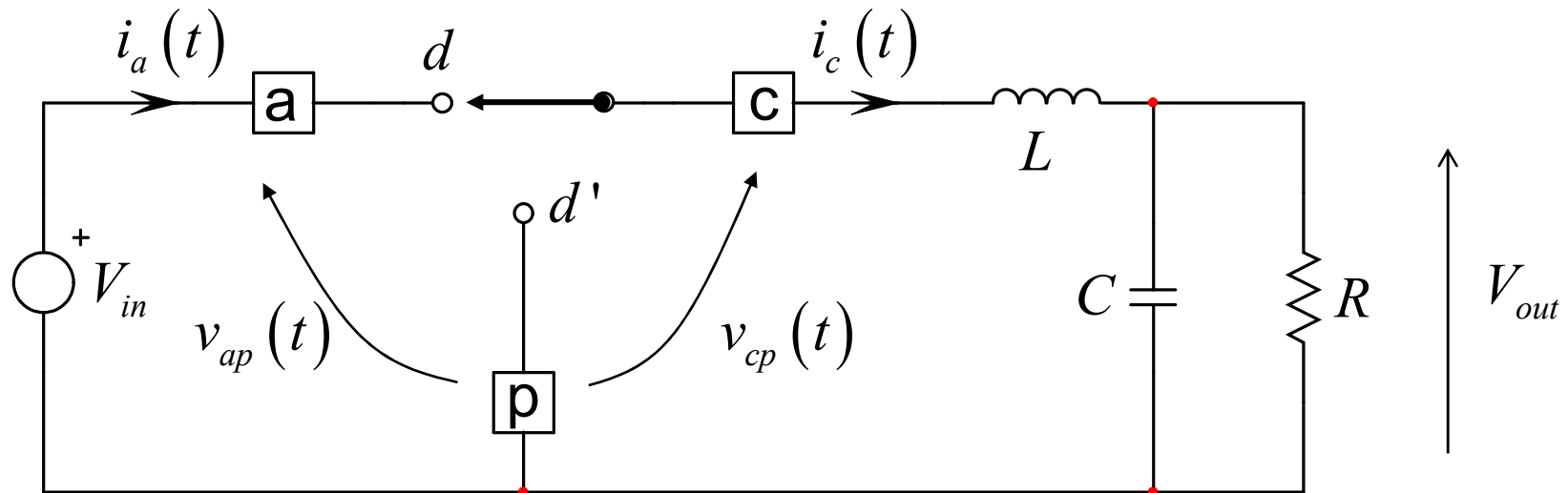- Use a buck configuration to see voltages at play



- The downslope depends on the output voltage V_{out} :

$$S_2 = -\frac{V_{out}}{L}$$

- The inductor average voltage is 0 at steady-state

$$V_{cp} = V_{out} \longrightarrow S_2 = -\frac{V_{cp}}{L}$$


A Current Mode Generator

- Update the previous equation to obtain final definition

$$I_c = \frac{V_c}{R_i} - V_{cp} (1-D) \frac{T_{sw}}{2L} - \frac{S_a}{R_i} DT_{sw} \quad \xrightarrow{\text{Group 2nd and 3rd terms}} \quad I_\mu = V_{cp} (1-D) \frac{T_{sw}}{2L} + \frac{S_a}{R_i} DT_{sw}$$


Peak current setpoint Half inductor ripple Compensation ramp

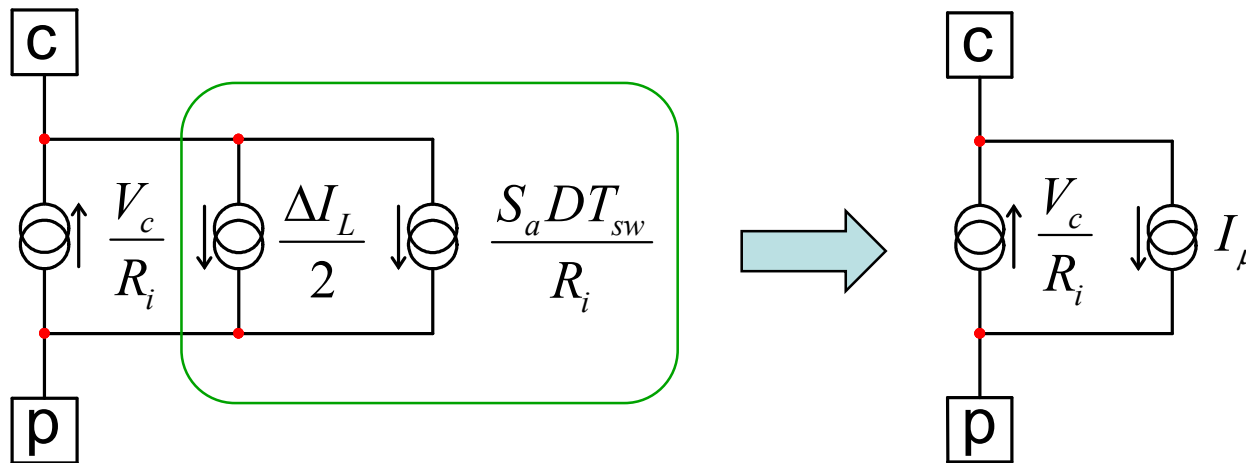- Inductor ripple and compensation ramp alter peak value



CM or VM Lead to Similar Input Currents

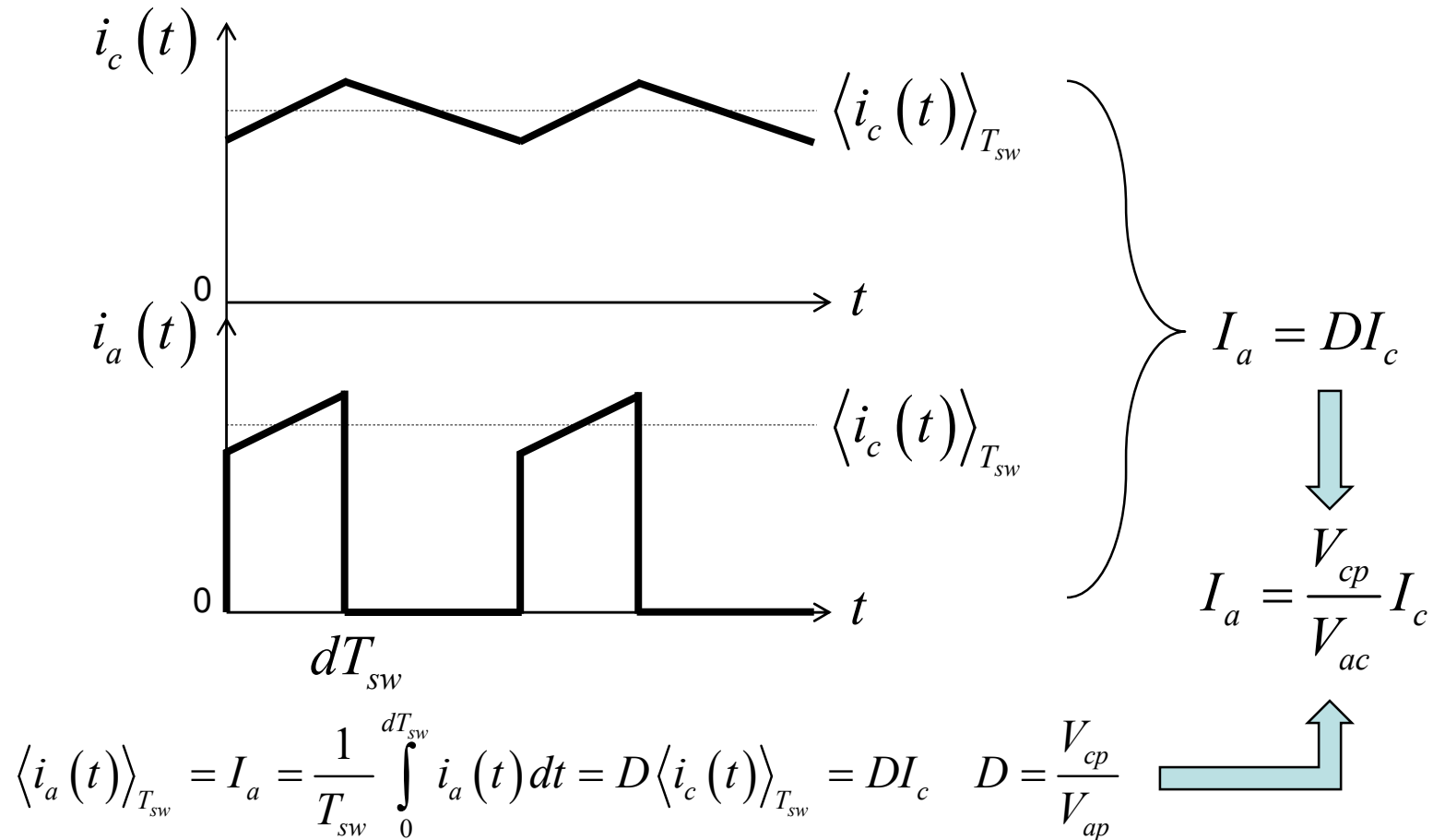- Average the current waveforms across the PWM switch




CCM




The PWM Switch Model in Current Mode

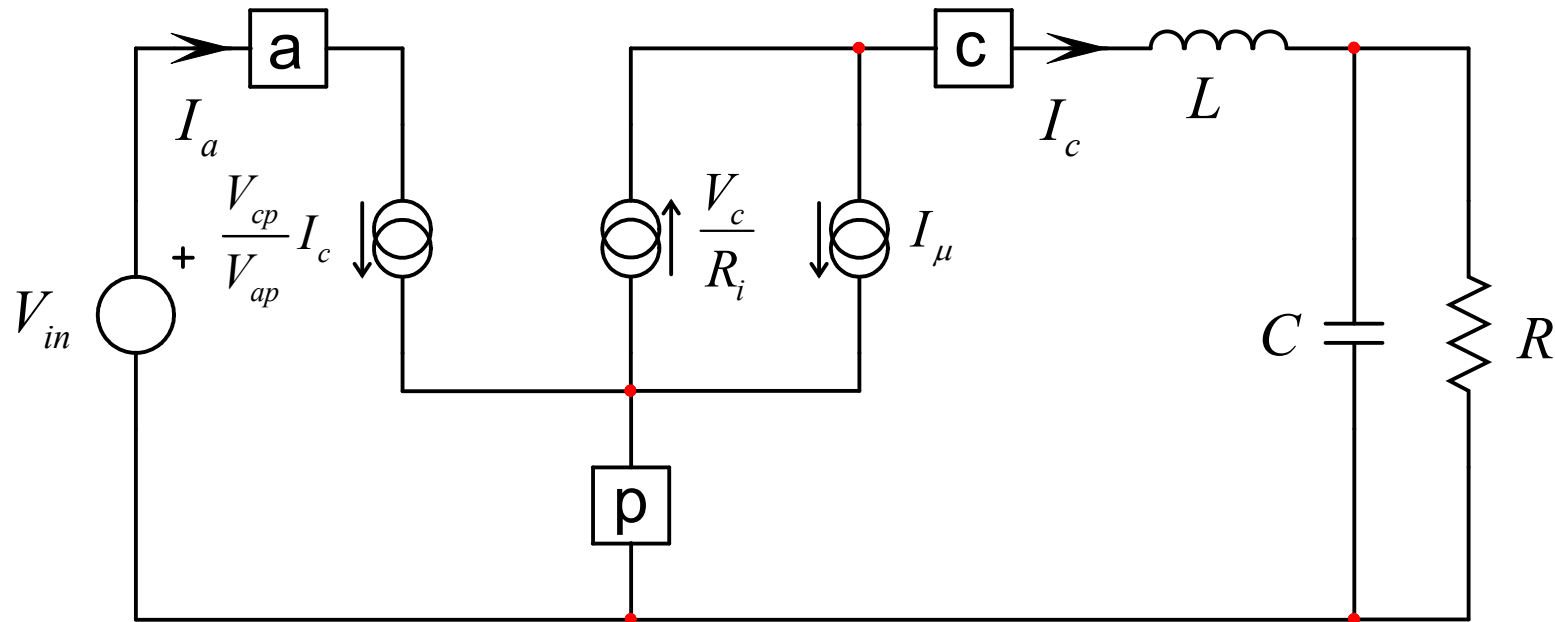- The final model associates three current sources



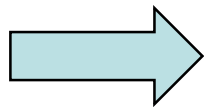- This is the large-signal current-mode PWM switch model



Can you think of something simpler?!




No!

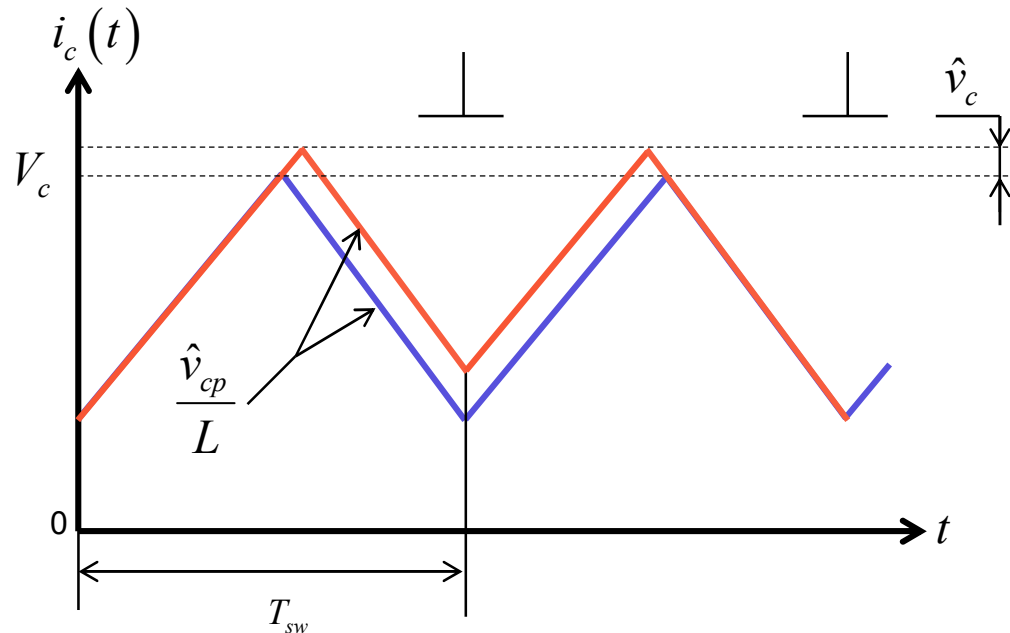V. Vorpérian, "Analysis of Current-Controlled PWM Converters using the Model of the PWM Switch", PCIM Conference, 1990



How to Model Subharmonic Instabilities?


- ❑ The model, as it is, cannot predict instabilities
- ❑ Let's observe a small-signal perturbation in v_c



- ❑ The off-slope does not change as \hat{v}_{cp} keeps constant
- ❑ This "memory" effect is modeled with a capacitor

Final Model Includes Subharmonic Effects

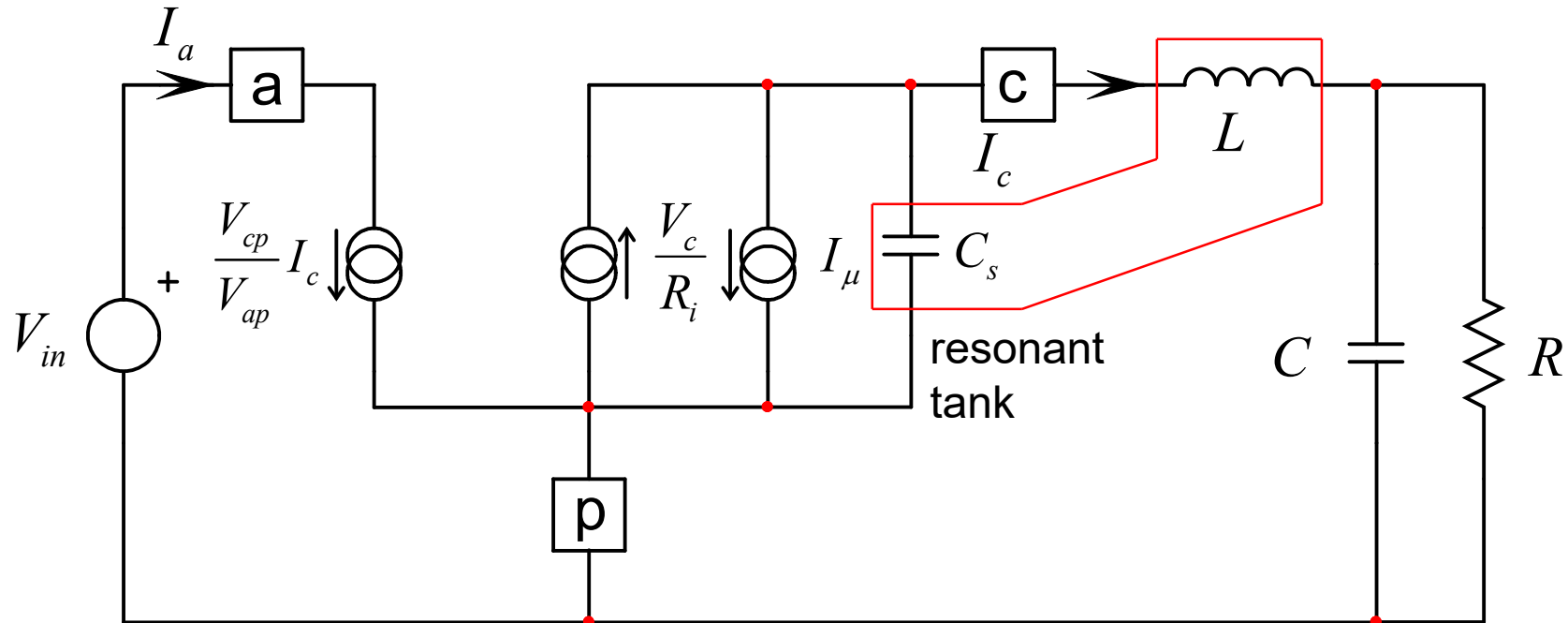- A simple capacitor is enough to mimic instability




- As the instability is placed at half the switching frequency:

$$\frac{F_{sw}}{2} = \frac{1}{2\pi\sqrt{LC_s}} \quad \Rightarrow \quad C_s = \frac{1}{L(F_{sw}\pi)^2}$$

The Large-Signal Model at Work

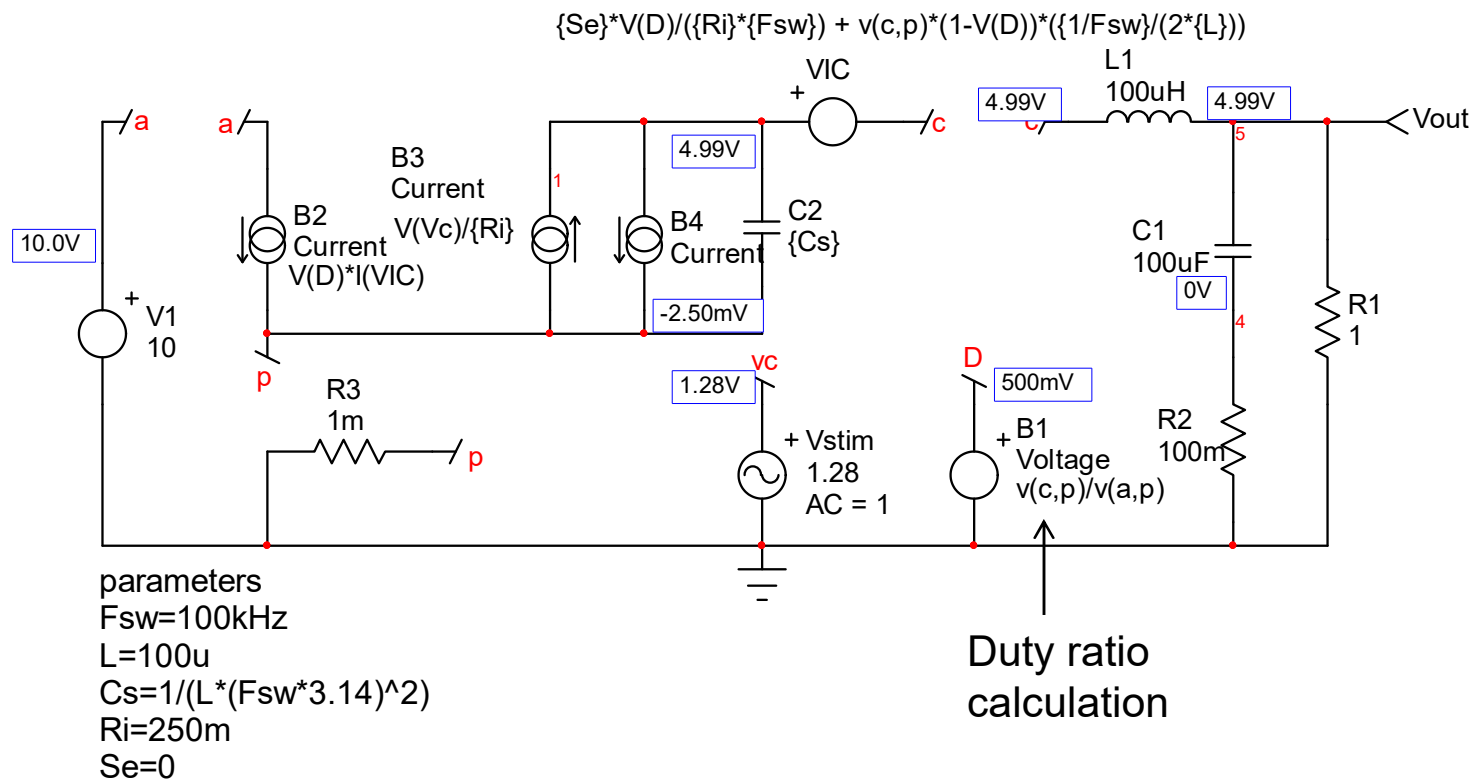
- A current-mode 5-V/5-A buck converter as an example



- Ramp compensation is adjusted to see its effects


Instabilities Show up as Expected

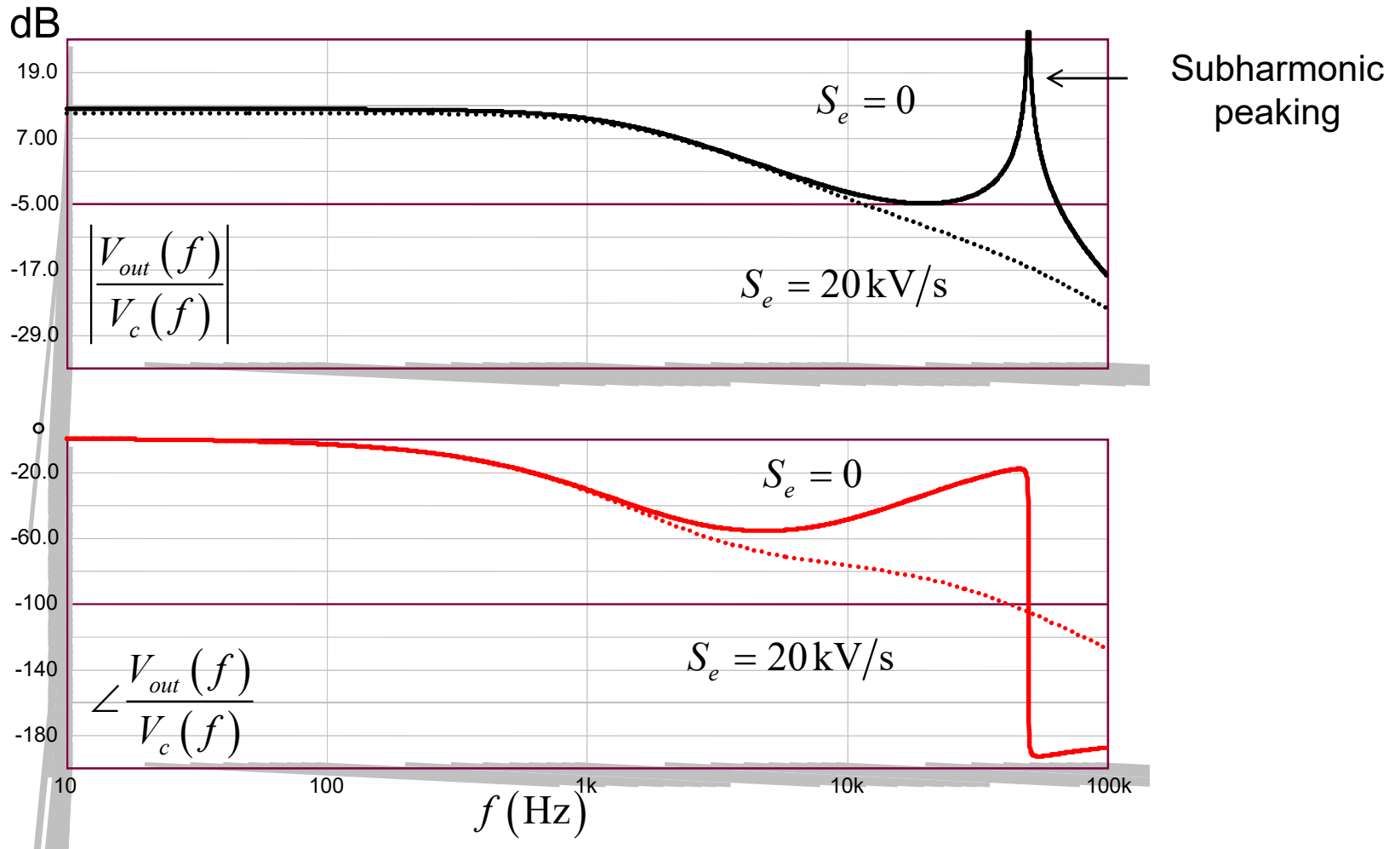- Peaking is tamed by increasing slope compensation



Another Way of Modeling

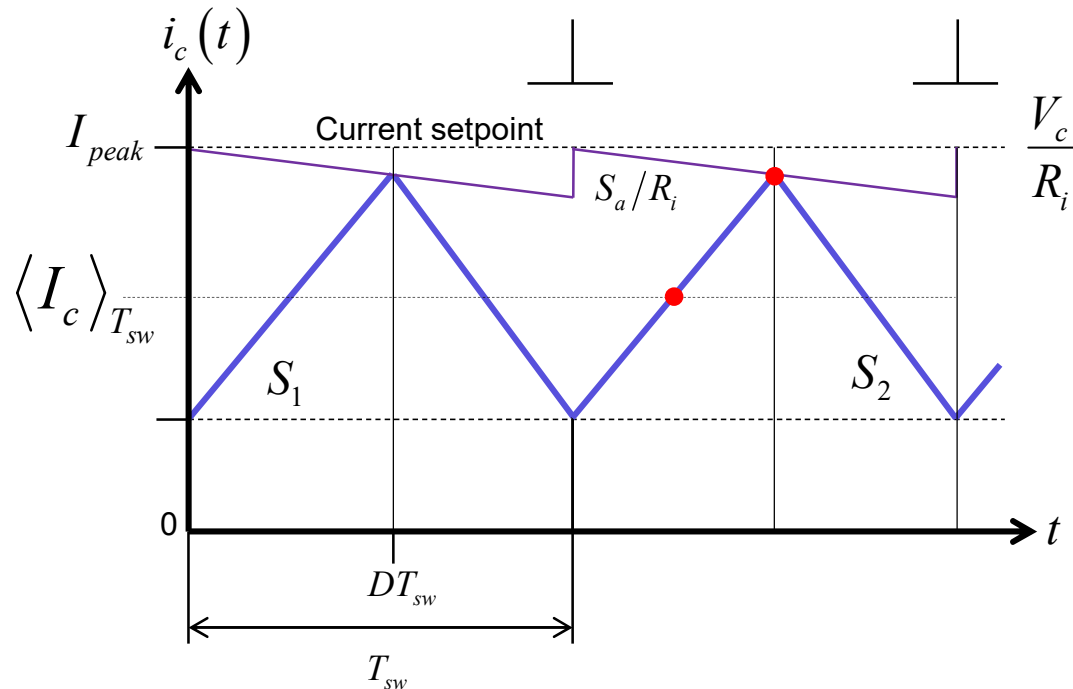
- We can build a duty ratio factory and use the VM model



$$I_c = \frac{V_c}{R_i} - \frac{S_a}{R_i} DT_{sw} - \frac{V_{ac}}{2L} DT_{sw} \quad \Rightarrow \quad D = \frac{F_{sw} (V_c - R_i I_c)}{S_a + \frac{R_i V_{ac}}{2L}}$$


Build a Duty Ratio Factory

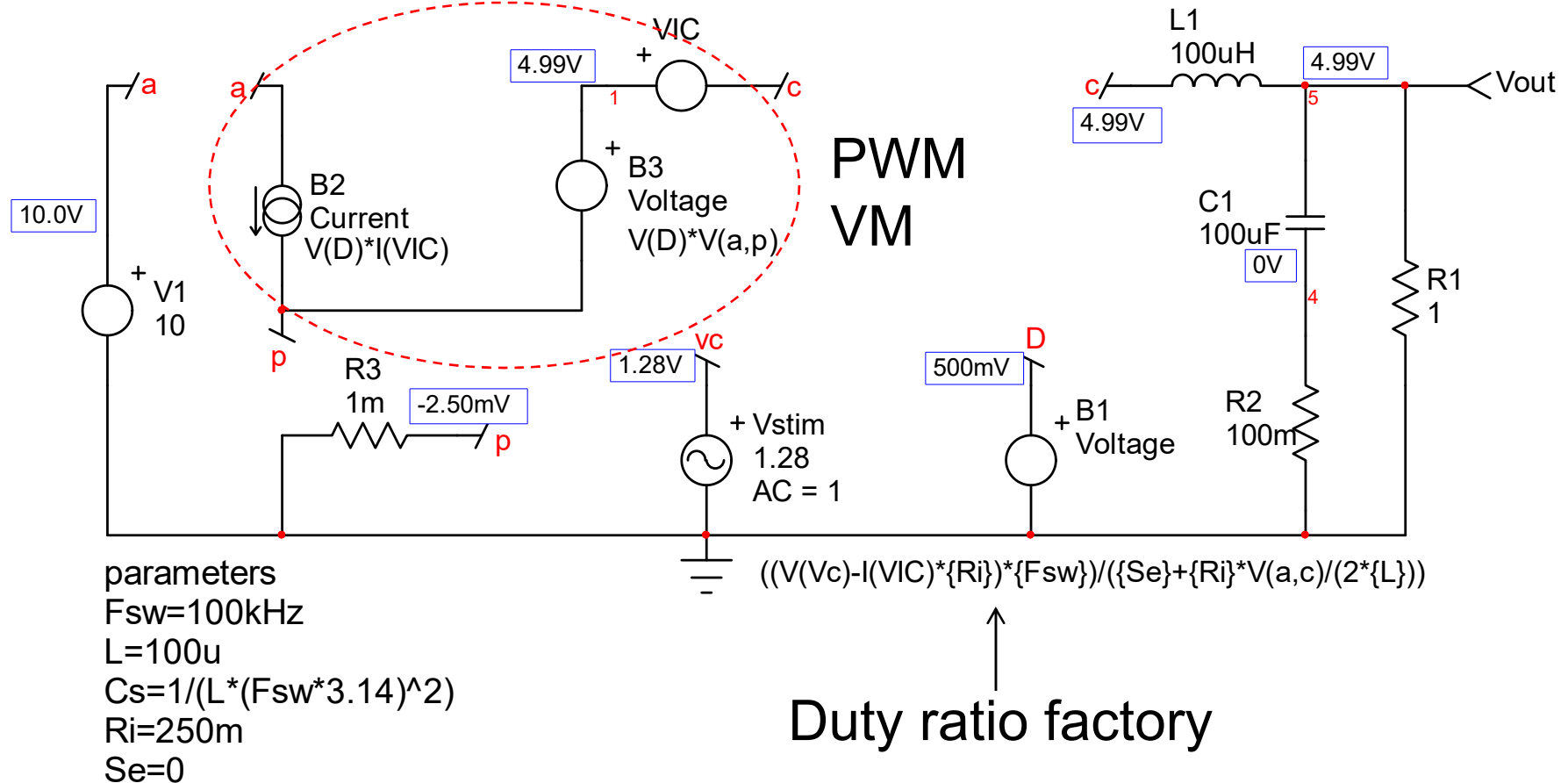- An in-line equation builds D from the control voltage V_c



No Sub-Harmonic Oscillations Prediction

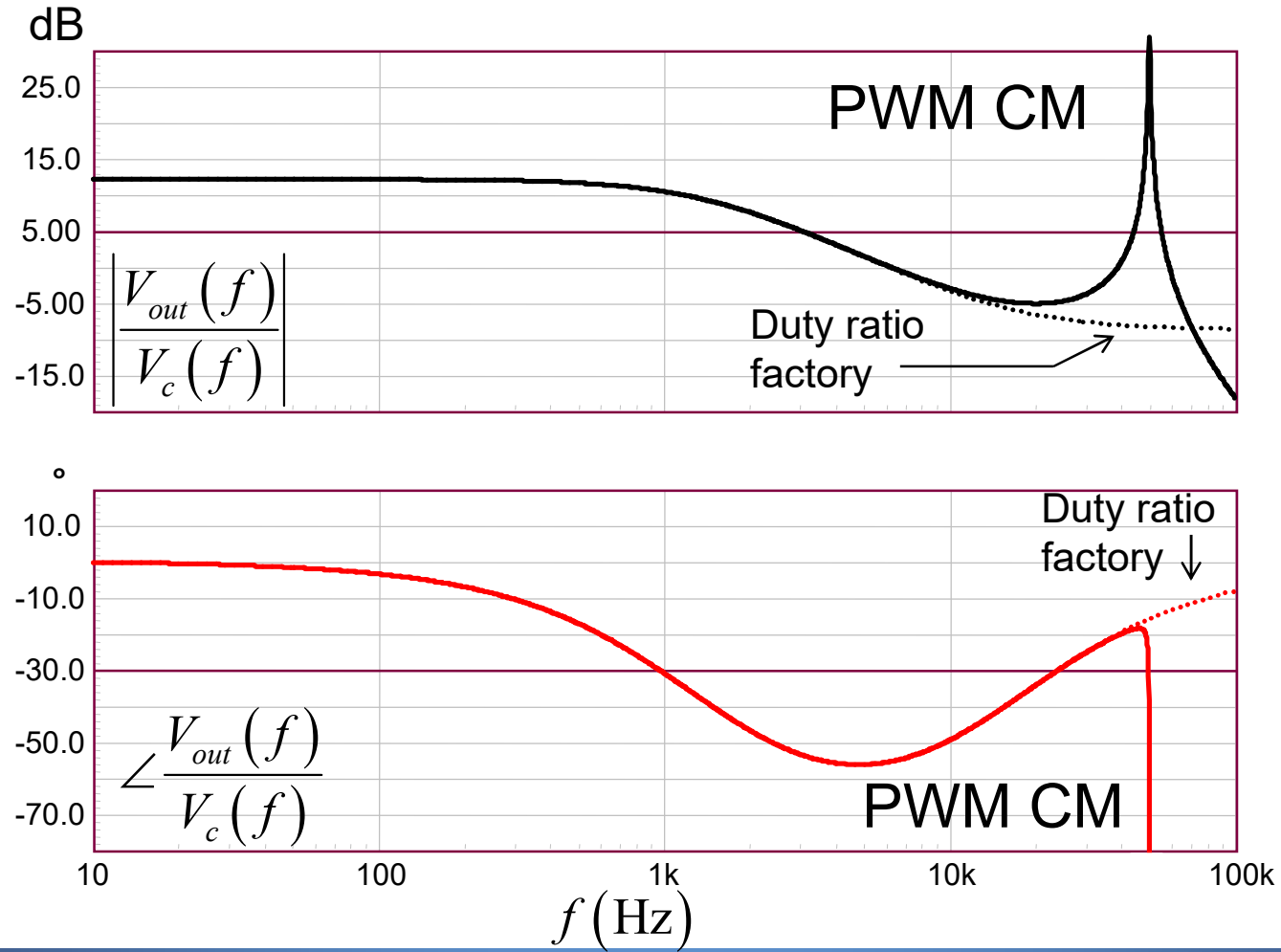- Low-frequency gains are identical but no peaking at $F_{sw}/2$



$$S_e = 0$$



Agenda

- Linear and Non-Linear Functions
- What is a Small-Signal Model?
- Fast Analytical Techniques at Work
- From a Switched to Linearized Model
- The CCM VM Small-Signal PWM Switch Model
- The DCM VM Small-Signal PWM Switch Model
- Peak Current Mode Control in Large Signal
- The CCM CM Small-Signal PWM Switch Model**
- The DCM CM Small-Signal PWM Switch Model
- The PWM Switch in Boundary Mode



Small-Signal Modeling of PWM CM

□ There are two equations to linearize:

$$I_c = \frac{V_c}{R_i} - V_{cp} \left(1 - \frac{V_{cp}}{V_{ap}} \right) \frac{T_{sw}}{2L} - \frac{S_a}{R_i} \frac{V_{cp}}{V_{ap}} T_{sw} \longrightarrow 3 \text{ variables}$$

$$I_a = \frac{V_{cp}}{V_{ap}} I_c = \frac{V_{cp}}{V_{ap}} \left(\frac{V_c}{R_i} - V_{cp} \left(1 - \frac{V_{cp}}{V_{ap}} \right) \frac{T_{sw}}{2L} - \frac{S_a}{R_i} \frac{V_{cp}}{V_{ap}} T_{sw} \right) \longrightarrow 3 \text{ variables}$$

□ Apply partial differentiation:

$$\hat{i}_c = \frac{\partial I_c(V_c, V_{ap}, V_{cp})}{\partial V_c} \hat{v}_c + \frac{\partial I_c(V_c, V_{ap}, V_{cp})}{\partial V_{ap}} \hat{v}_{ap} + \frac{\partial I_c(V_c, V_{ap}, V_{cp})}{\partial V_{cp}} \hat{v}_{cp}$$

$$\hat{i}_a = \frac{\partial I_a(V_c, V_{ap}, V_{cp})}{\partial V_c} \hat{v}_c + \frac{\partial I_a(V_c, V_{ap}, V_{cp})}{\partial V_{ap}} \hat{v}_{ap} + \frac{\partial I_a(V_c, V_{ap}, V_{cp})}{\partial V_{cp}} \hat{v}_{cp}$$



Small-Signal Modeling of PWM CM

□ Rearrange the coefficients and rewrite equations:

$$\hat{i}_c = k_o \hat{v}_c + g_f \hat{v}_{ap} + g_o \hat{v}_{cp} \quad \hat{i}_a = k_i \hat{v}_c + g_i \hat{v}_{ap} + g_r \hat{v}_{cp}$$

Where:

$$k_o = \frac{1}{R_i} \quad g_f = \frac{S_a T_{sw} D}{R_i V_{ap}} - \frac{T_{sw} D^2}{2L} \quad g_o = \frac{T_{sw} (D-1)}{2L} + \frac{T_{sw} D}{2L} - \frac{S_a T_{sw} D}{R_i V_{cp}}$$

$$k_i = \frac{D}{R_i} \quad g_i = D \left(g_f - \frac{I_c}{V_{ap}} \right) \quad g_r = \frac{I_c}{V_{ap}} + D \left[\frac{T_{sw} (2D-1)}{2L} - \frac{S_a T_{sw}}{R_i V_{ap}} \right]$$

↓

Using Vorperian notation and $\hat{i}_c = \dots - g_o \hat{v}_{cp}$

$$k_o = \frac{1}{R_i} \quad g_f = D g_o - \frac{D D' T_{sw}}{2L} \quad g_o = \frac{T_{sw}}{L} \left(D' \frac{S_a}{S_n} + \frac{1}{2} - D \right)$$


$$k_i = \frac{D}{R_i} \quad g_i = D \left(g_f - \frac{I_c}{V_{ap}} \right) \quad g_r = \frac{I_c}{V_{ap}} - g_o D$$

S_n , on-slope
 S_f , off-slope
 S_a , external ramp



A Small Signal Model

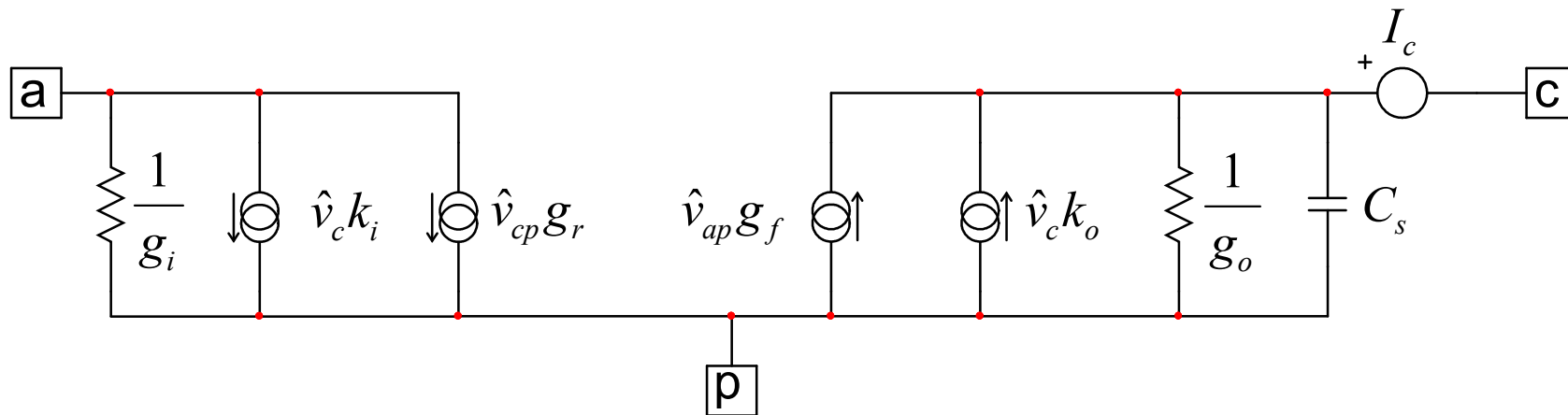
- The model includes current sources and conductances




$$\begin{aligned}
 k_o &= \frac{1}{R_i} & g_f &= Dg_o - \frac{DD'T_{sw}}{2L} & g_o &= \frac{T_{sw}}{L} \left(D' \frac{S_a}{S_n} + \frac{1}{2} - D \right) \\
 k_i &= \frac{D}{R_i} & g_i &= D \left(g_f - \frac{I_c}{V_{ap}} \right) & g_r &= \frac{I_c}{V_{ap}} - g_o D
 \end{aligned}$$

The Model at Work

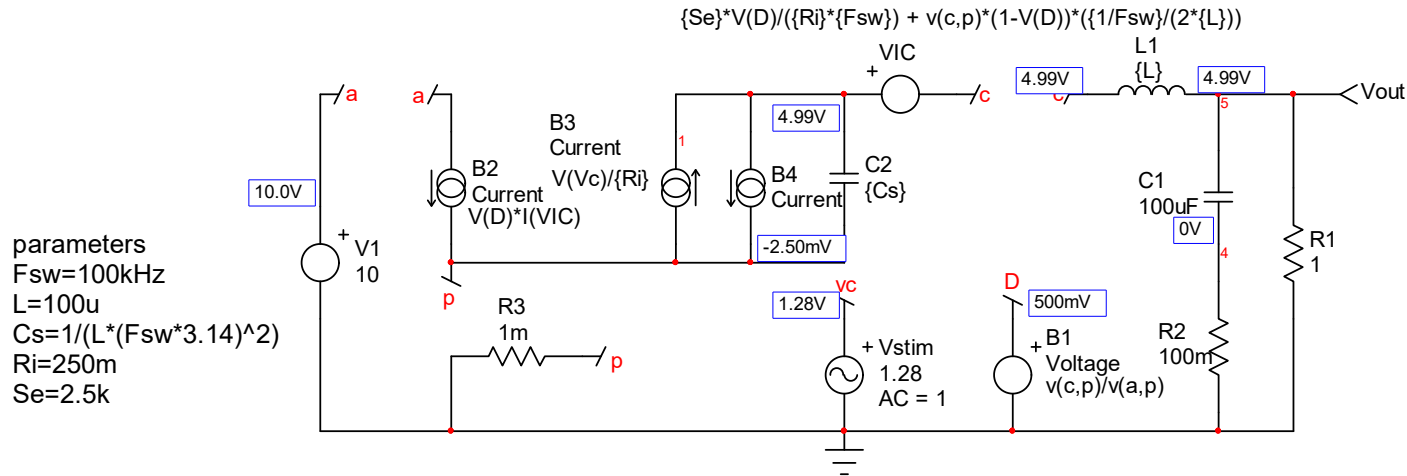- Compare ac responses of the linearized large-signal model



- ...with that of the small-signal model

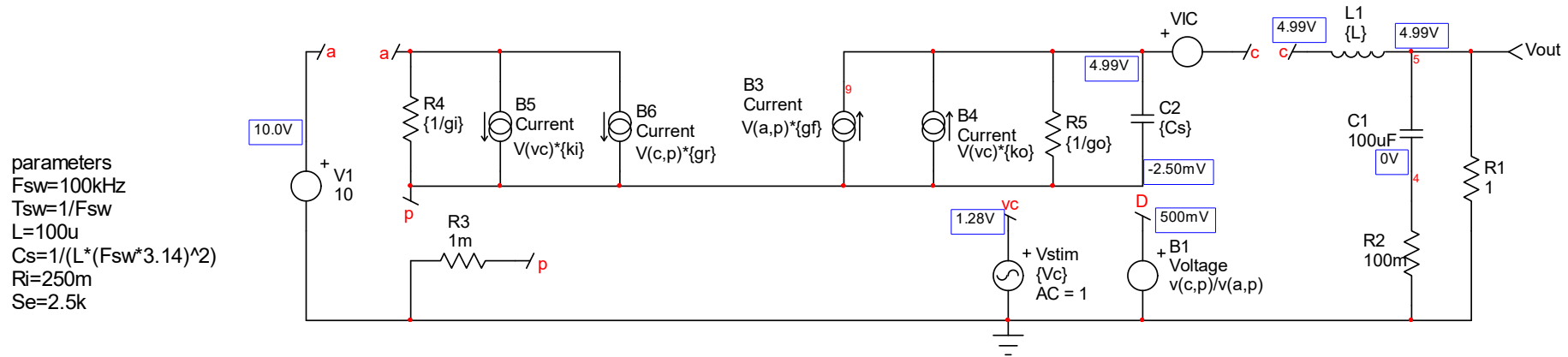

Results are Identical

- Identical results prove that our small-signal modeling is ok!




Current Loop Instabilities

- Let's assume input and output voltages are constant

$$V_c = \text{constant} \rightarrow \hat{v}_c = 0$$

$$V_{in}, V_{out} = \text{constant} \rightarrow V_{ap} = \text{constant} \rightarrow \hat{v}_{ap} = 0$$


- The buck implementation simplifies to:

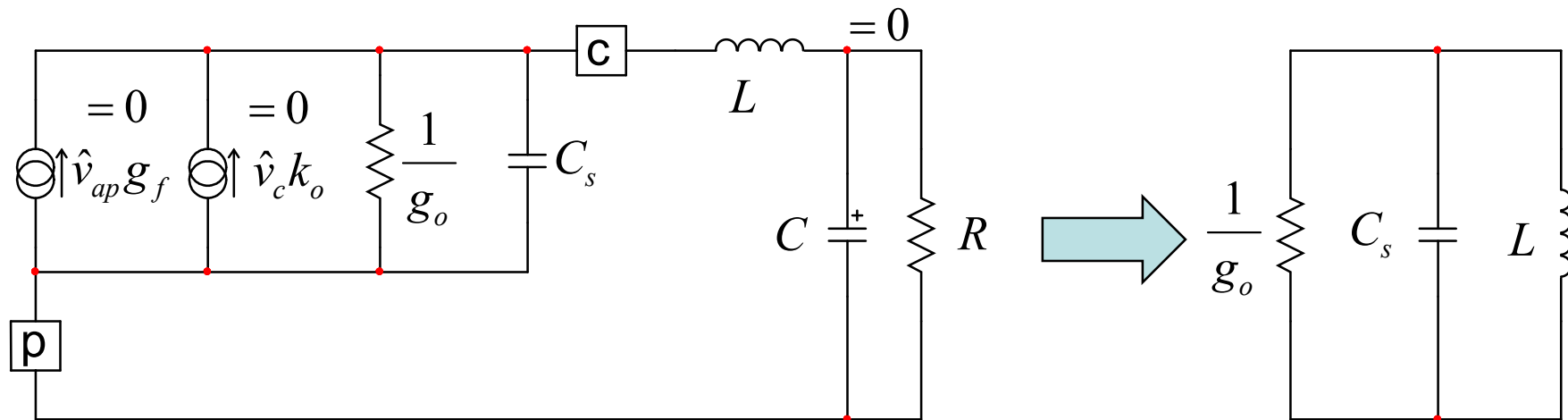

- Circuit approximates current loop dynamics near $\frac{F_{sw}}{2}$

This is a Resonating Tank

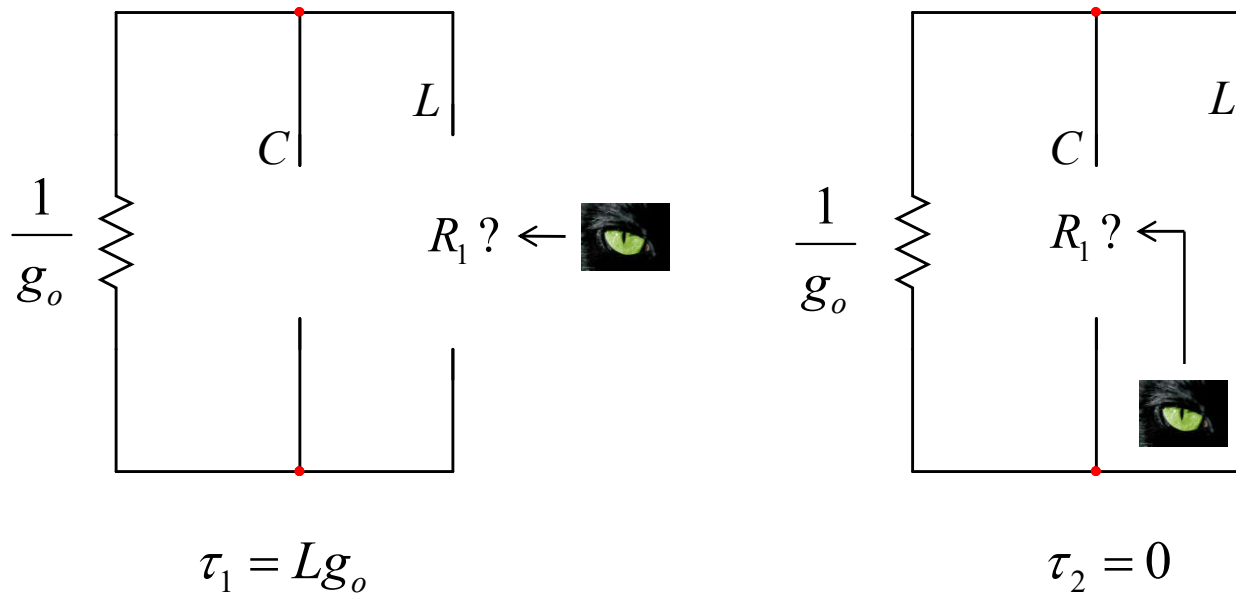
- For a_1 look at the resistance R driving L and C
- Look at the driving impedance at L while C is in its dc state
- Look at the driving impedance at C while L is in its dc state



$$D(s) = 1 + sLg_o + a_2^2 s^2$$

Find the Second-Order Coefficient a_2

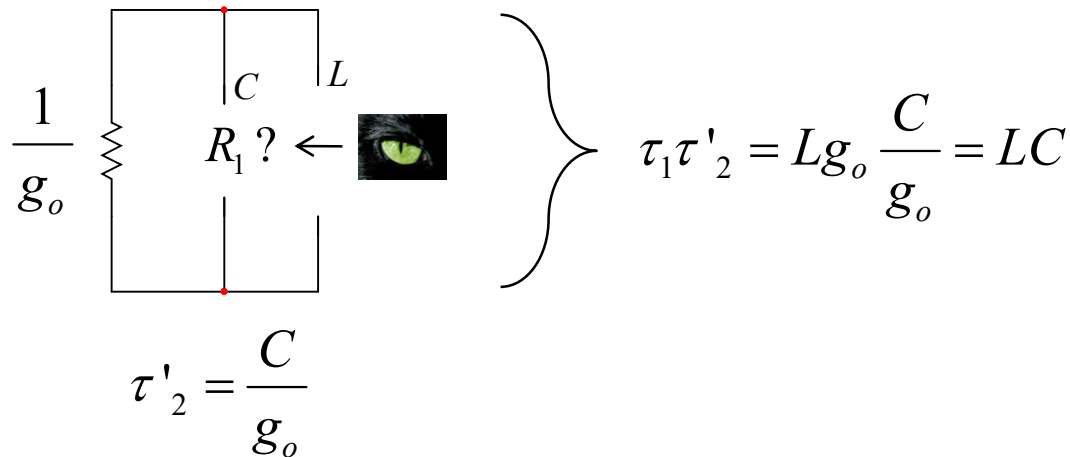- how τ_1 (involving L) combines with τ'_2 (involving C)?
- Look at the driving impedance at C while L is in its HF state



- The denominator can thus be expressed as:

$$D(s) = 1 + sLg_o + s^2LC \longrightarrow D(s) = 1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2$$

$$\omega_0 = \frac{\omega_{sw}}{2} \longrightarrow Lg_o = \frac{1}{\omega_0 Q} = \frac{2}{\omega_{sw} Q}$$

$$Q = \frac{2}{\omega_{sw} Lg_o}$$

What Brings Q to Infinity?

- We now substitute the definition of g_o

$$Q = \frac{2}{\omega_{sw} L g_o} = \frac{2}{\frac{2\pi}{T_{sw}} L \frac{T_{sw}}{L} \left(D' \frac{S_a}{S_n} + \frac{1}{2} - D \right)} = \frac{1}{\pi \left(D' \frac{S_a}{S_n} + \frac{1}{2} - D \right)}$$

- This definition matches the one derived by Ray Ridley

$$Q = \frac{1}{\pi (m_c D' - 0.5)} \quad m_c = 1 + \frac{S_a}{S_n}$$

- What happens if $S_a = 0$ with a 50% duty ratio?

$$Q = \frac{1}{\pi \left(\frac{1}{2} - D \right)} \xrightarrow[D = 50\%]{\text{blue arrow}} Q = \infty$$

R. B. Ridley, "A New Continuous-Time Model for Current-Mode Control", IEEE Transactions of Power Electronics, April 1991



How to Keep the Loop Stable?

- Keeps the denominator away from 0 up to $D = 100\%$

$$D' \frac{S_a}{S_n} + \frac{1}{2} - D \neq 0 \rightarrow D' \frac{S_a}{S_n} = D - 0.5 \xrightarrow[\frac{S_f = D}{S_n = D'}]{D \rightarrow 1} \frac{S_n}{S_f} \frac{S_a}{S_n} = D - 0.5 \rightarrow S_a \geq \frac{1}{2} S_f$$

- To prevent overcompensation, damp Q below 1

$$\frac{1}{\pi \left(D' \frac{S_a}{S_n} + \frac{1}{2} - D \right)} < 1 \quad \Rightarrow \quad S_a \geq \frac{S_n \left(D - 0.5 + \frac{1}{\pi} \right)}{D'}$$


- Using Ray Ridley's notations, we have:

$$m_c = \frac{\frac{1}{\pi} + 0.5}{D'} \rightarrow 1 + \frac{S_a}{S_n} = \frac{\frac{1}{\pi} + 0.5}{D'} \rightarrow S_a \geq \frac{S_n \left(D - 0.5 + \frac{1}{\pi} \right)}{D'}$$



Do Not Over Compensate the Loop

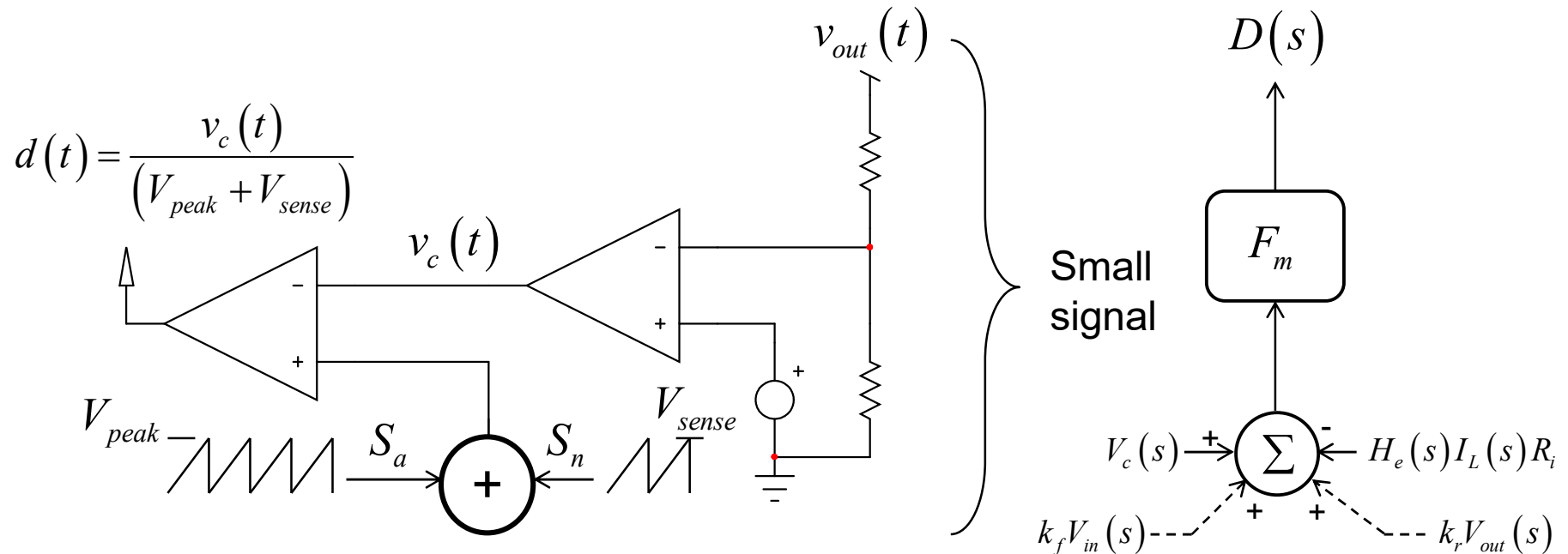- Adding more ramp shifts the control towards voltage mode




- The modulator transfer function changes to

$$F_m = \frac{1}{(S_a + S_n)T_{sw}} \xrightarrow{S_a \gg S_n} F_m \approx \frac{1}{S_a T_{sw}} \xrightarrow{S_a = \frac{V_{peak}}{T_{sw}}} G_{PWM} = \frac{1}{V_{peak}}$$

External Ramp Effects on Power Stage

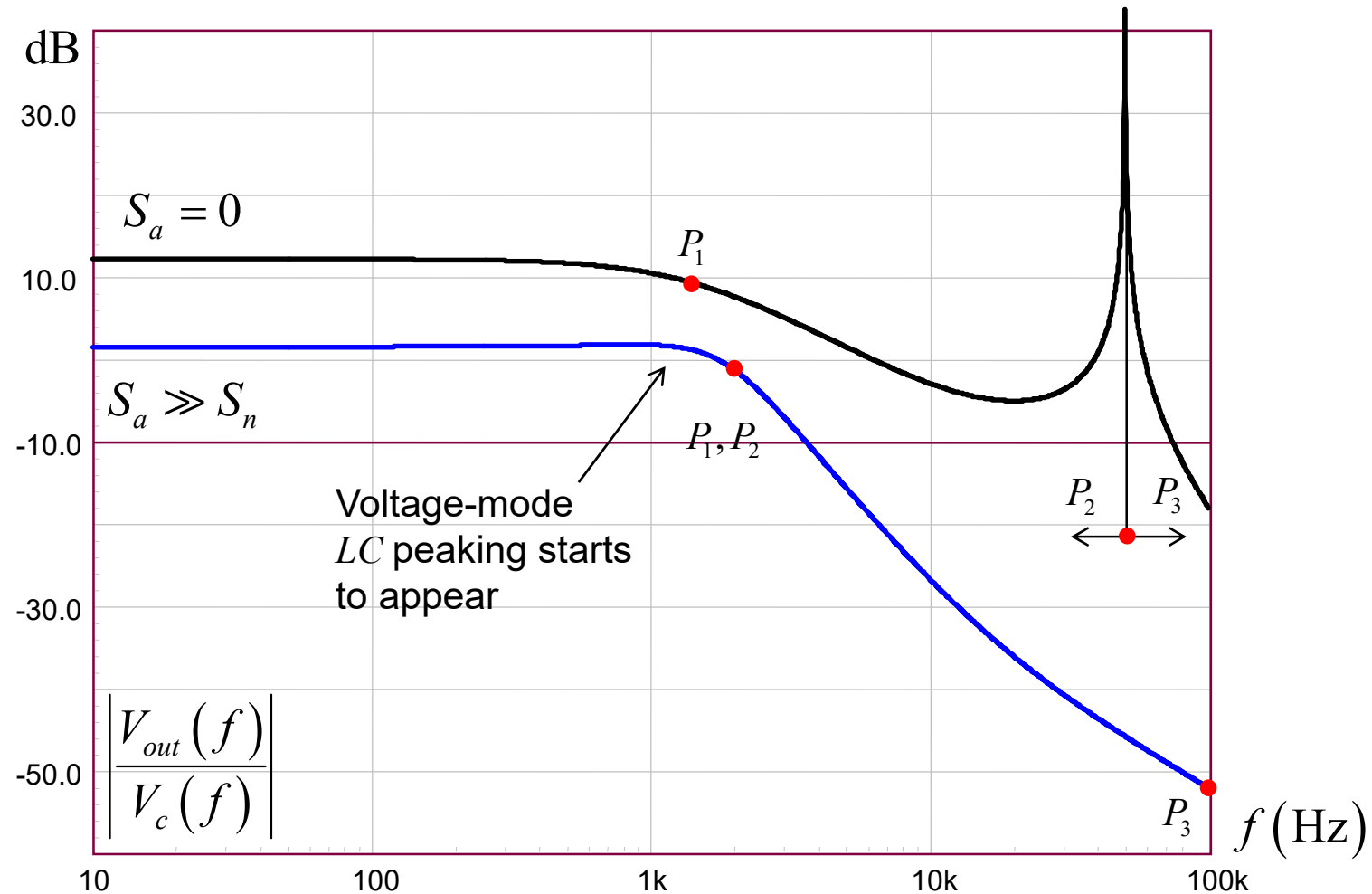- The double pole splits and joins the low-frequency one




Agenda

- Linear and Non-Linear Functions
- What is a Small-Signal Model?
- Fast Analytical Techniques at Work
- From a Switched to Linearized Model
- The CCM VM Small-Signal PWM Switch Model
- The DCM VM Small-Signal PWM Switch Model
- Peak Current Mode Control in Large Signal
- The CCM CM Small-Signal PWM Switch Model
- The DCM CM Small-Signal PWM Switch Model**
- The PWM Switch in Boundary Mode



The PWM Switch in DCM

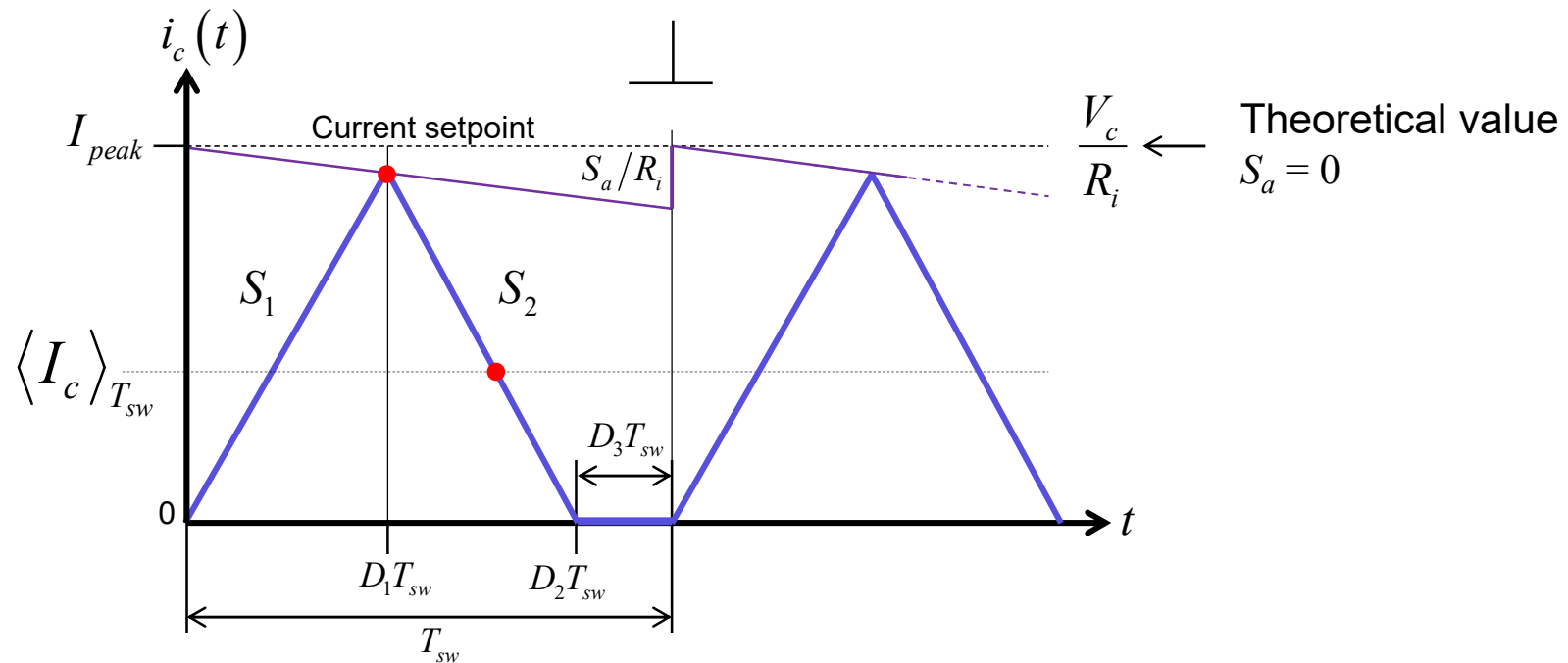- The PWM CM can work in discontinuous mode




- The average current I_c is somewhere in the downslope S_2

$$I_{peak} = \frac{V_c - D_1 T_{sw} S_a}{R_i} \longrightarrow I_c = \frac{V_c - D_1 T_{sw} S_a}{R_i} - \alpha D_2 T_{sw} S_2$$

Derive the Inductor Average Current

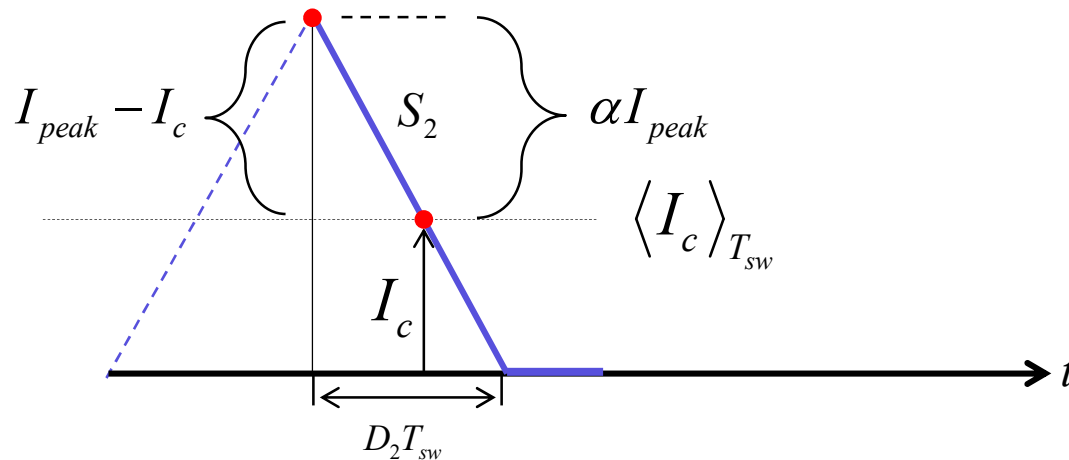- We must now obtain the value of α to get I_c



- I_c is the area under the triangle divided by the switching period

$$I_c = \frac{I_{peak} D_1}{2} + \frac{I_{peak} D_2}{2} = I_{peak} \frac{D_1 + D_2}{2}$$

$$\alpha I_{peak} = I_{peak} - I_{peak} \frac{D_1 + D_2}{2}$$

$$\alpha = 1 - \frac{D_1 + D_2}{2}$$


Adopt the CCM Structure for DCM

- Substitute and rearrange to get the inductor current

$$I_c = \frac{V_c}{R_i} - \frac{D_1 T_{sw} S_a}{R_i} - D_2 T_{sw} \frac{V_{cp}}{L} \left(1 - \frac{D_1 + D_2}{2} \right)$$


- If we stick to the original CCM architecture
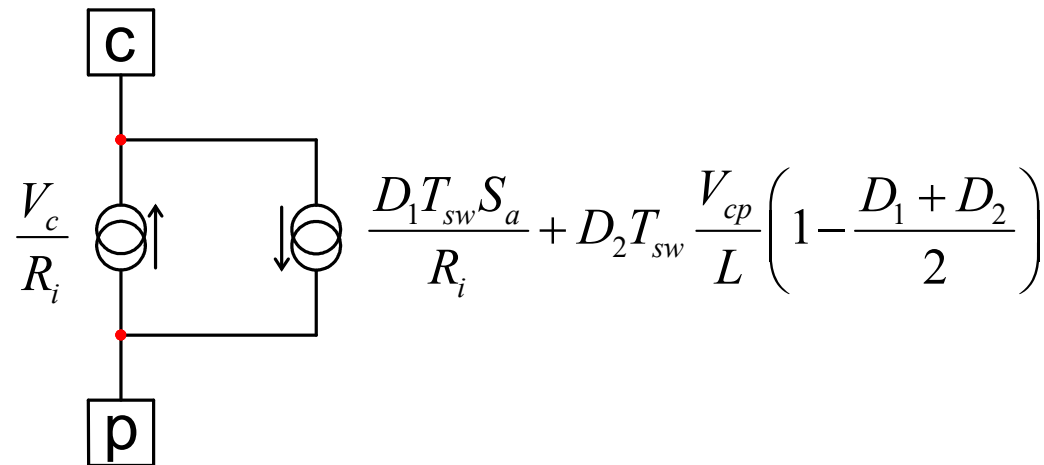
$$I_c = \frac{V_c}{R_i} - I_\mu \quad \text{with} \quad I_\mu = \frac{D_1 T_{sw} S_a}{R_i} + D_2 T_{sw} \frac{V_{cp}}{L} \left(1 - \frac{D_1 + D_2}{2} \right)$$



Discontinuous Waveforms

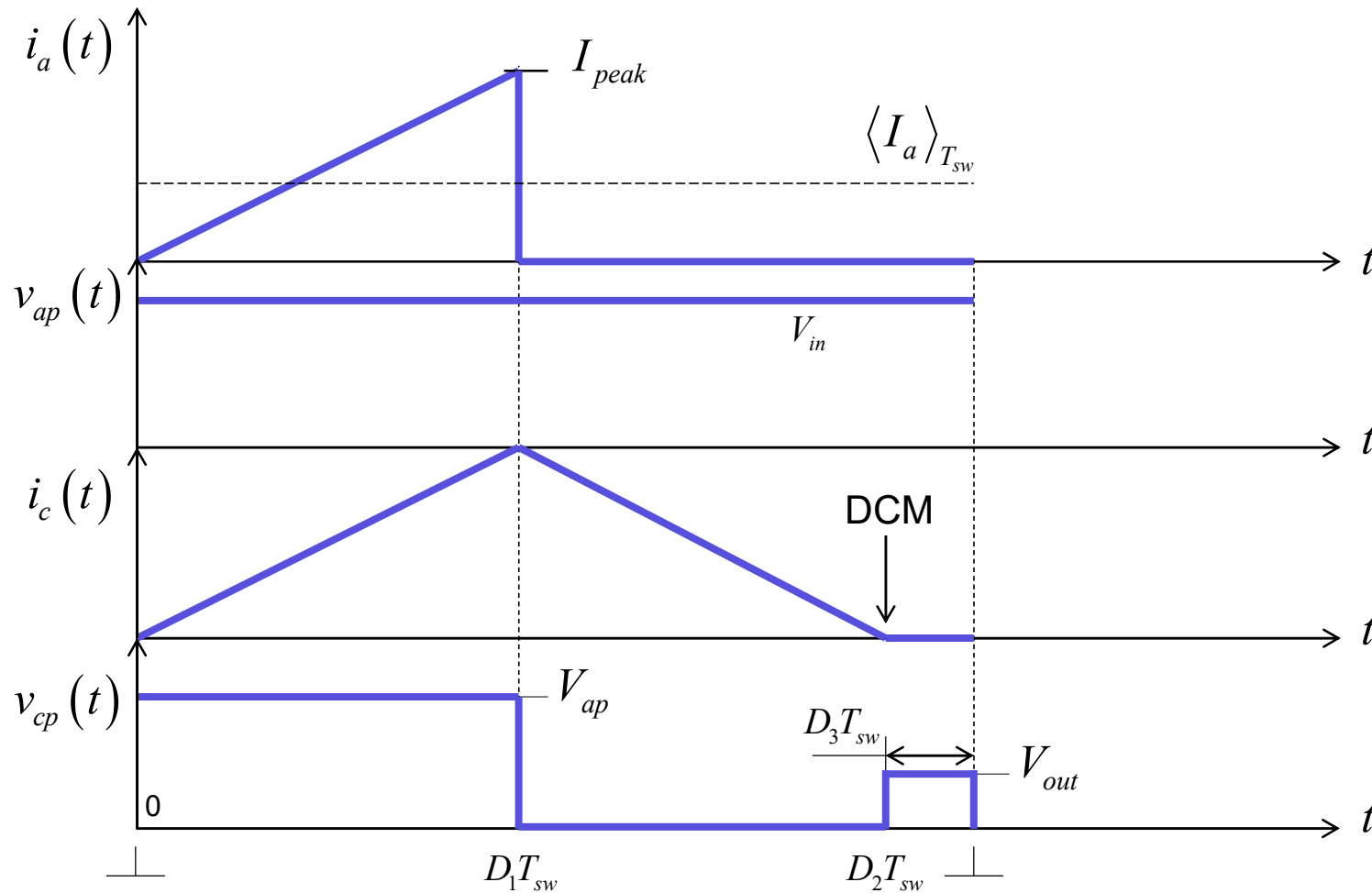□ Let's have a look at the PWM switch voltages in DCM



Derive the Duty Ratios

- From the DCM voltage-mode PWM switch we have:

$$V_{cp} = V_{ap} \frac{D_1}{D_1 + D_2} \longrightarrow D_1 = \frac{D_2 V_{cp}}{V_{ap} - V_{cp}}$$

- From the operating DCM waveforms

$$I_a = \frac{I_{peak} D_1}{2} \longrightarrow I_{peak} = \frac{2I_a}{D_1} \longrightarrow I_c = I_{peak} \frac{D_1 + D_2}{2} \longrightarrow I_a = I_c \frac{D_1}{D_1 + D_2}$$


- Almost there, just need to express D_2

$$\left. \begin{aligned} I_{peak} &= \frac{V_{ac}}{L} D_1 T_{sw} & \text{and} & & I_{peak} &= \frac{2I_c}{D_1 + D_2} \\ \frac{V_{ac}}{L} D_1 T_{sw} &= \frac{2I_c}{D_1 + D_2} \end{aligned} \right\} D_2 = \frac{2LF_{sw}}{D_1} \frac{I_c}{V_{ac}} - D_1$$



The DCM Model is Complete!

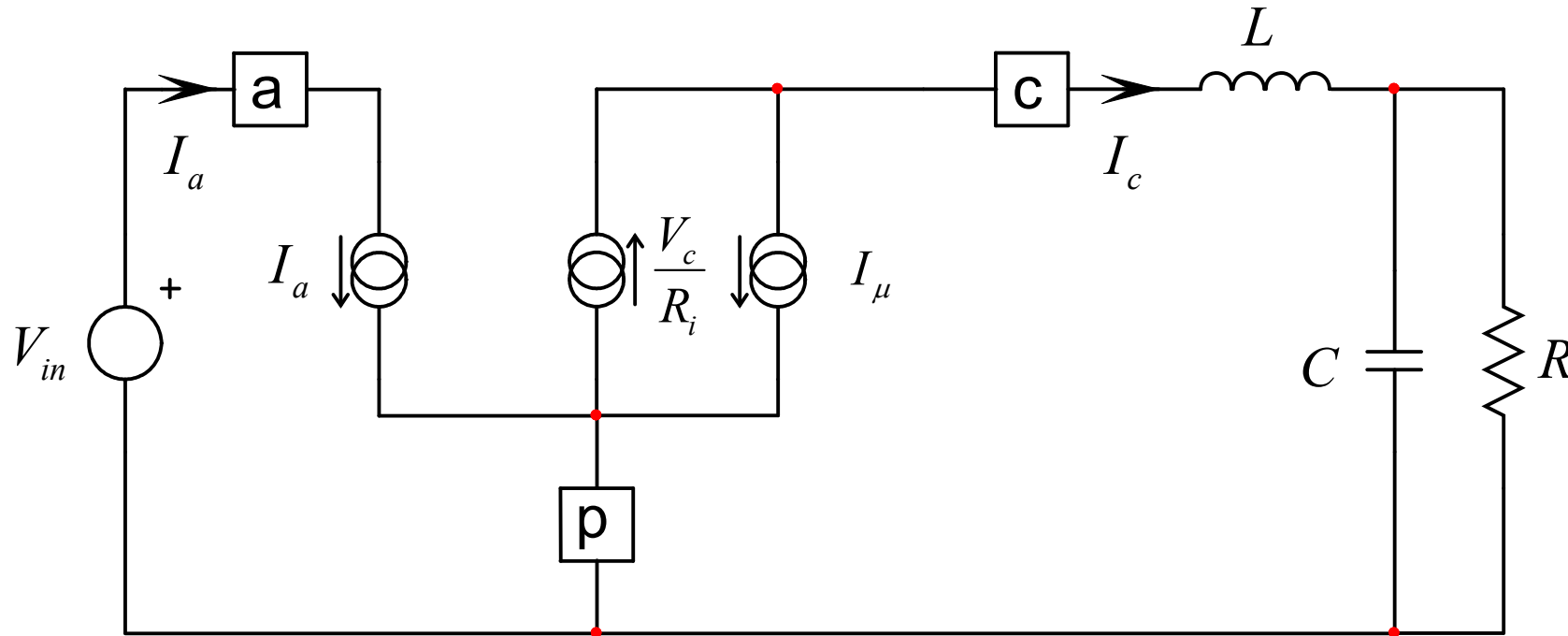- We can use this model for DCM simulations




$$I_a = I_c \frac{D_1}{D_1 + D_2}$$

$$I_\mu = \frac{D_1 T_{sw} S_a}{R_i} + D_2 T_{sw} \frac{V_{cp}}{L} \left(1 - \frac{D_1 + D_2}{2} \right)$$

Another Way of Modeling

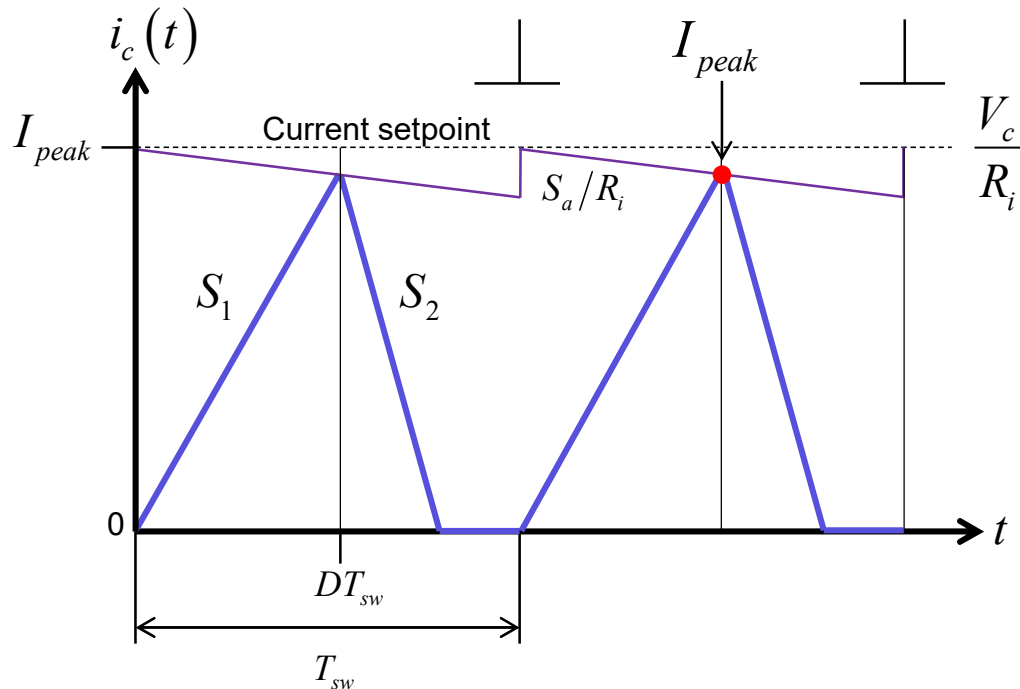- We can build a duty ratio factory and use the VM model



$$I_{peak} = \frac{V_c}{R_i} - \frac{S_a}{R_i} DT_{sw}$$


$$I_{peak} = \frac{V_{ac}}{L} DT_{sw}$$

➔

$$D = \frac{F_{sw} V_c}{R_i} \frac{1}{\left(\frac{V_{ac}}{L} + \frac{S_a}{R_i} \right)}$$

Build a Duty Ratio Factory

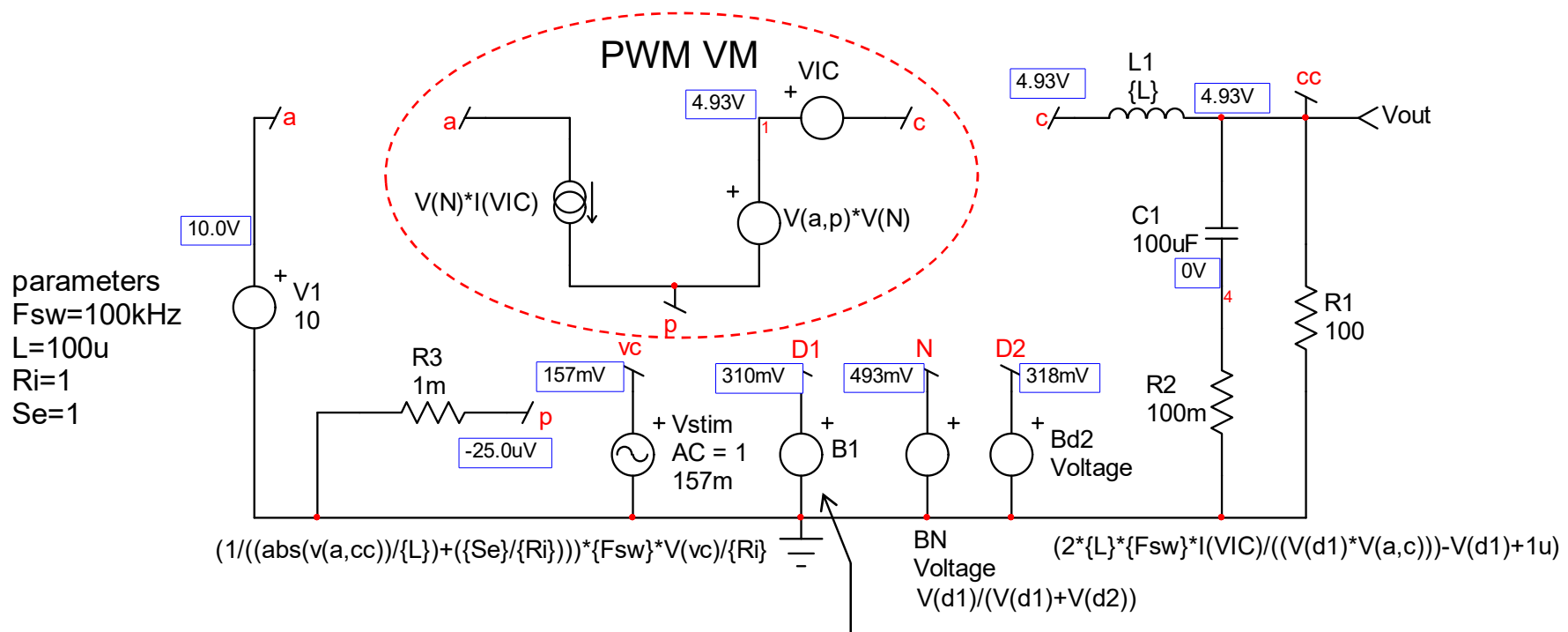
- An in-line equation builds D from the control voltage V_c



Duty ratio factory

Build a Duty Ratio Factory

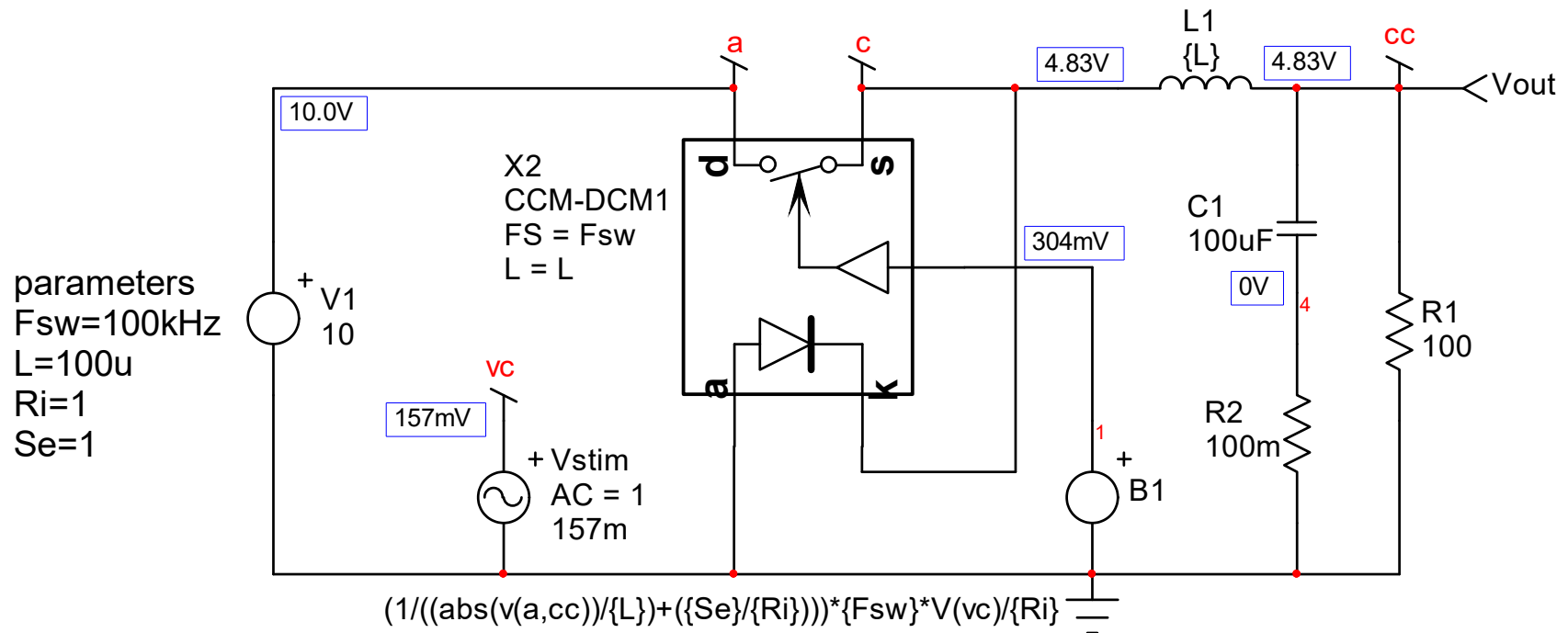
- ❑ You can apply the technique to another VM model



- ❖ This is the auto-toggling CoPEC model


Check the DCM Model Results

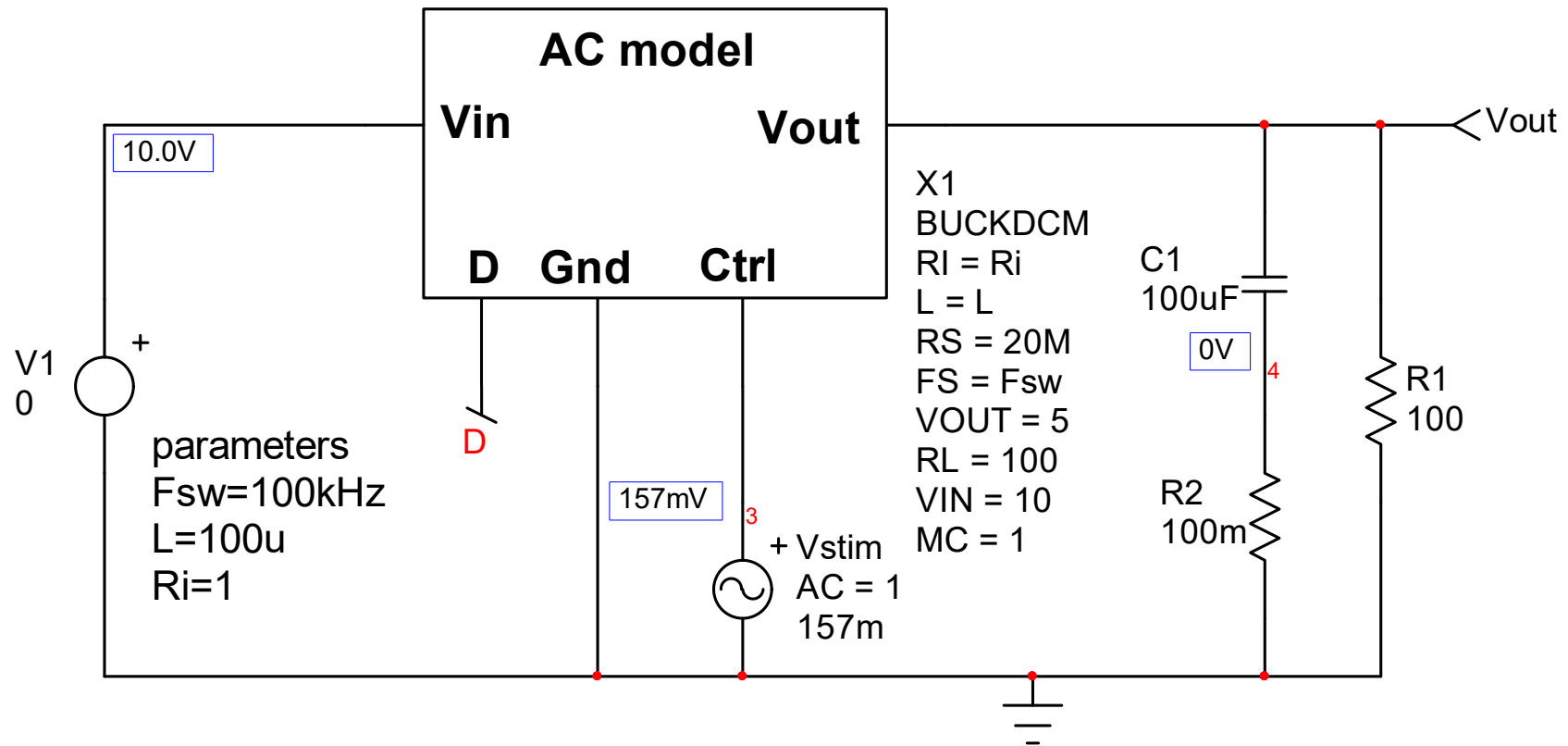- ❑ Check simulation results with Ridley's models



Check the DCM Model Results

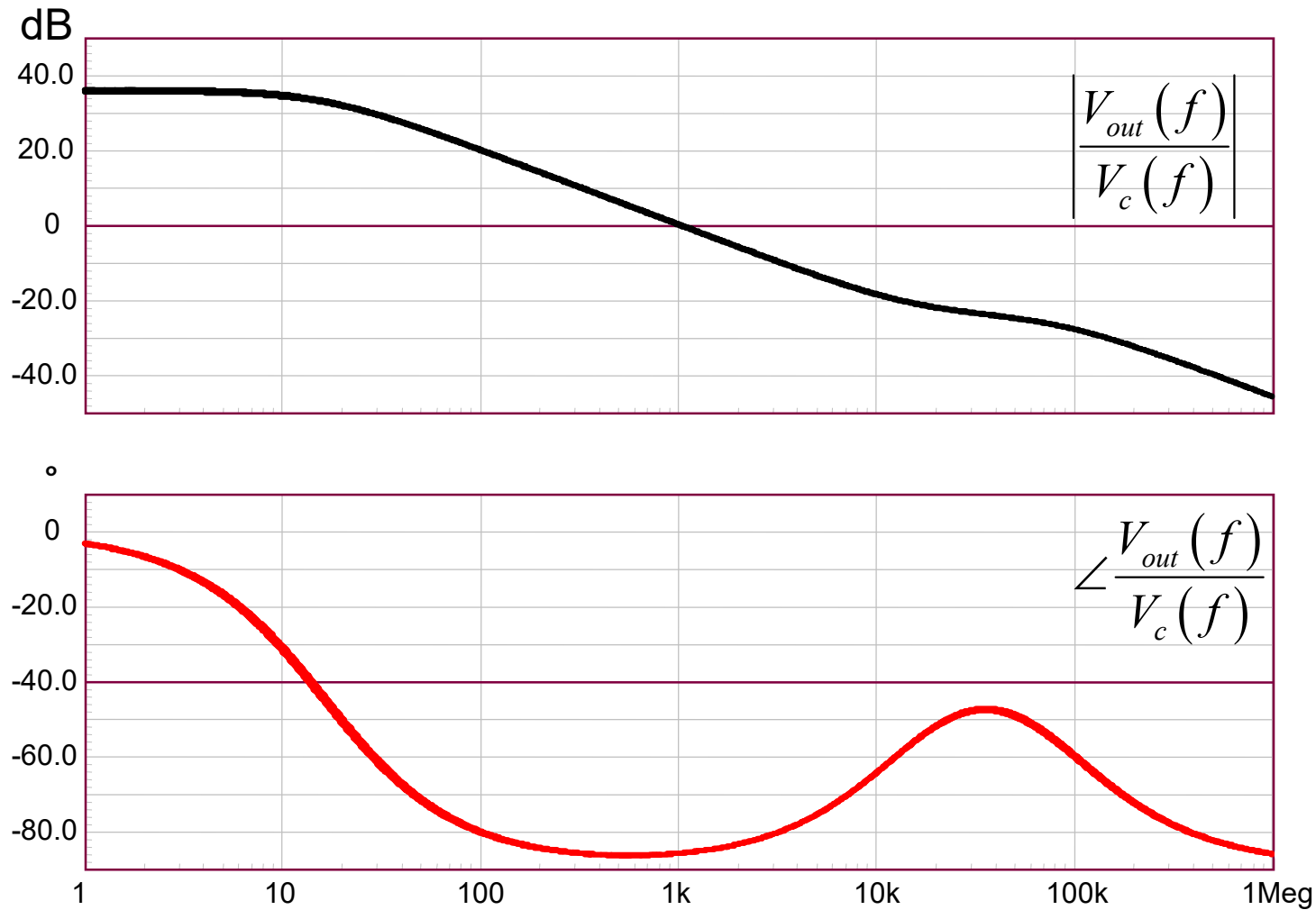- Bode plots are similar along the frequency axis





Agenda

- Linear and Non-Linear Functions
- What is a Small-Signal Model?
- Fast Analytical Techniques at Work
- From a Switched to Linearized Model
- The CCM VM Small-Signal PWM Switch Model
- The DCM VM Small-Signal PWM Switch Model
- Peak Current Mode Control in Large Signal
- The CCM CM Small-Signal PWM Switch Model
- The DCM CM Small-Signal PWM Switch Model
- The PWM Switch in Boundary Mode**




Why QR Operation?

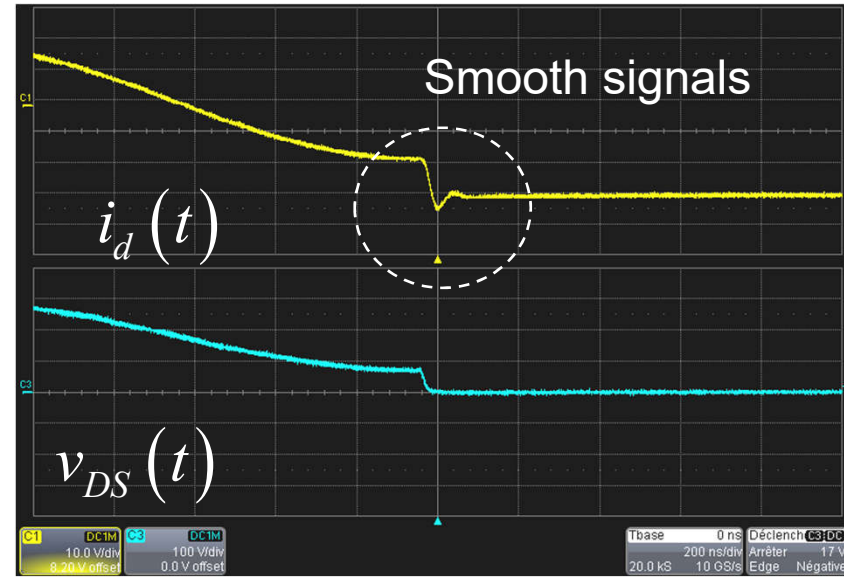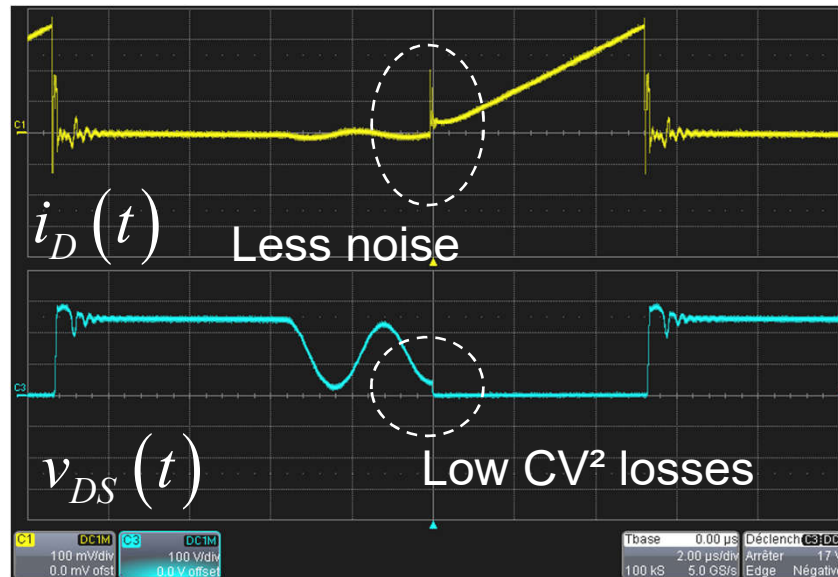- ❑ More converters are using variable-frequency operation
- ❑ This is known as Quasi-Square Wave Resonant mode: QR
 - Valley switching ensures extremely low capacitive losses
 - DCM operation saves losses in the secondary-side diode
 - Easier synchronous rectification
 - The Right Half-Plane Zero is pushed to high frequencies



What is the Principle of Operation?

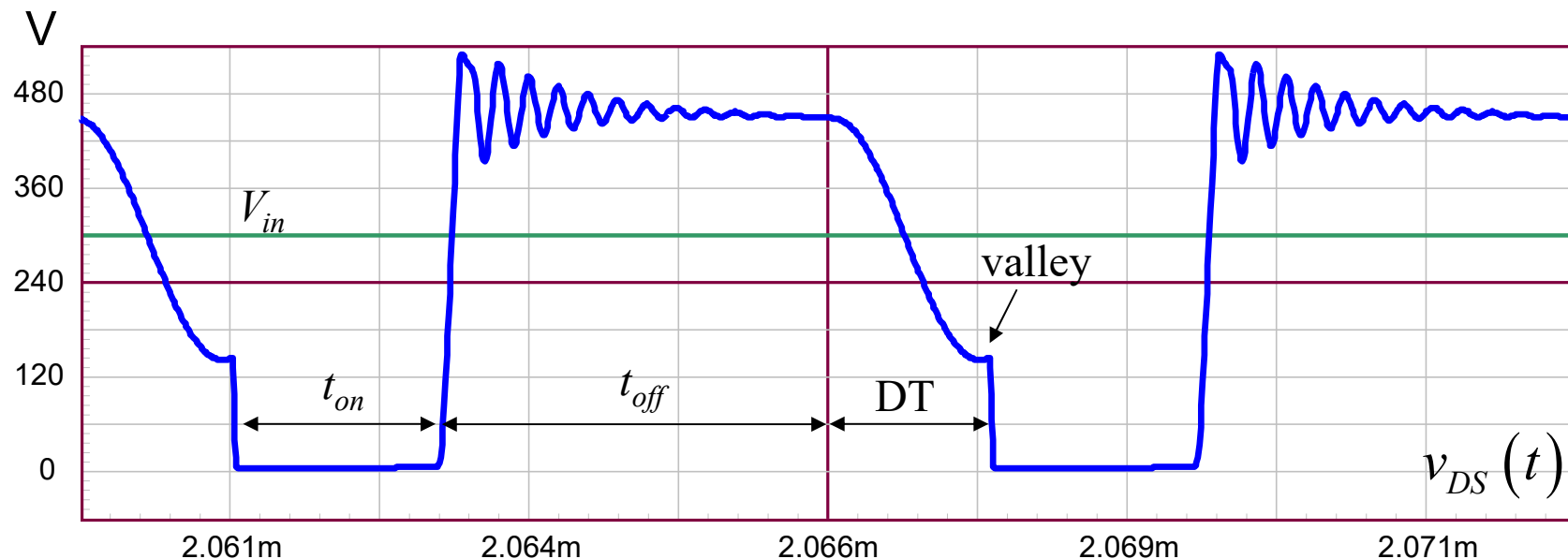- ❑ The drain-source signal is made of peaks and valleys
- ❑ A valley presence means:
 - The drain is at a minimum level, capacitors are naturally discharged
 - The converter is operating in the discontinuous conduction mode




BCM = Borderline or Boundary Conduction Mode

Flyback structure




A QR Circuit Does not Need a Clock

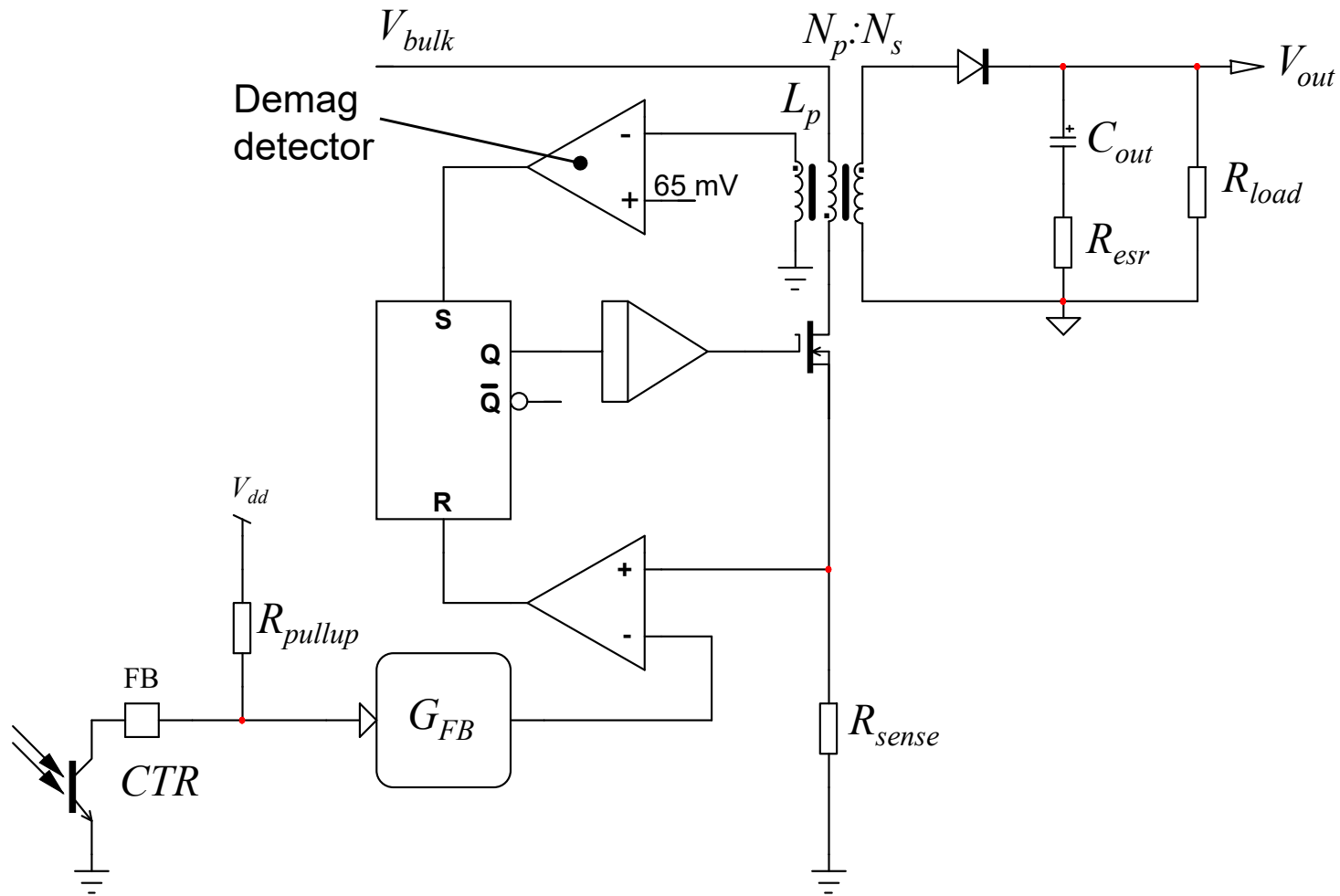- The system is a self-oscillating current-mode converter




A Winding is Used to Detect Core Reset

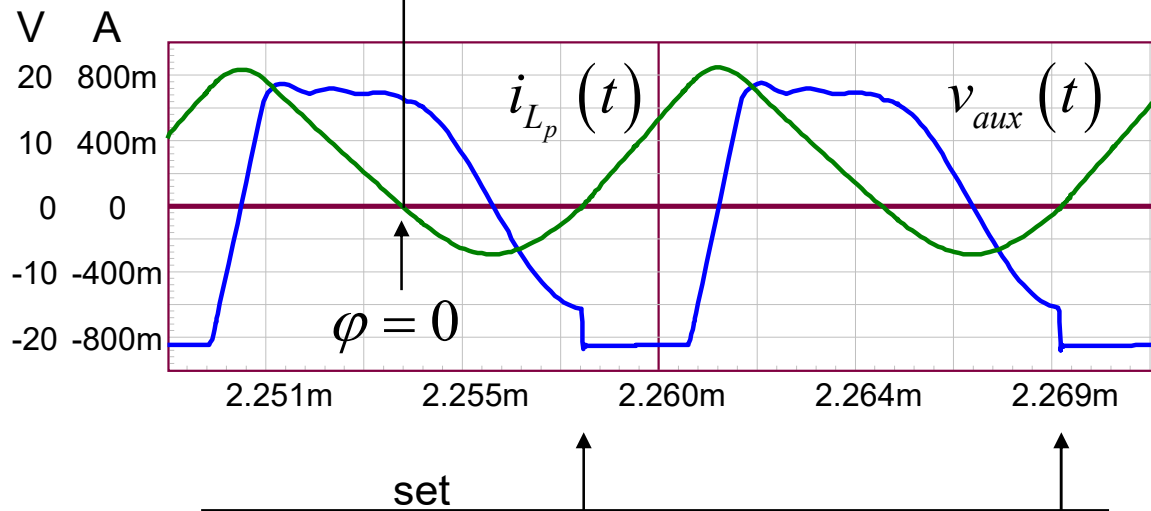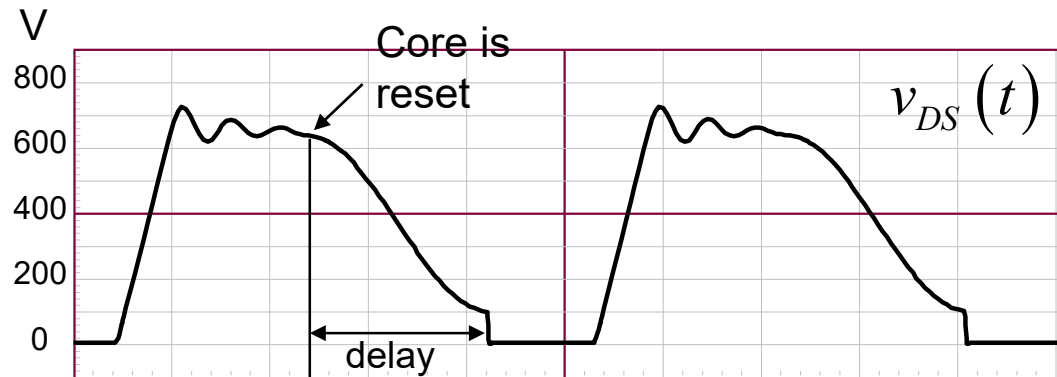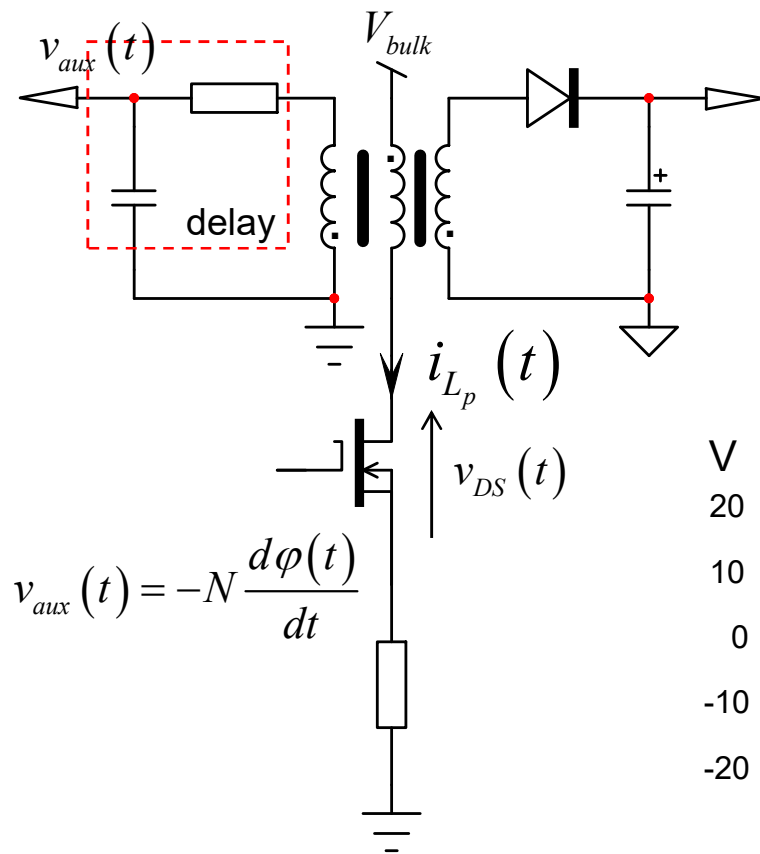- ❑ When the flux returns to zero, the aux. voltage drops
- ❑ Discontinuous mode is always maintained




Variable-Frequency Current-Mode

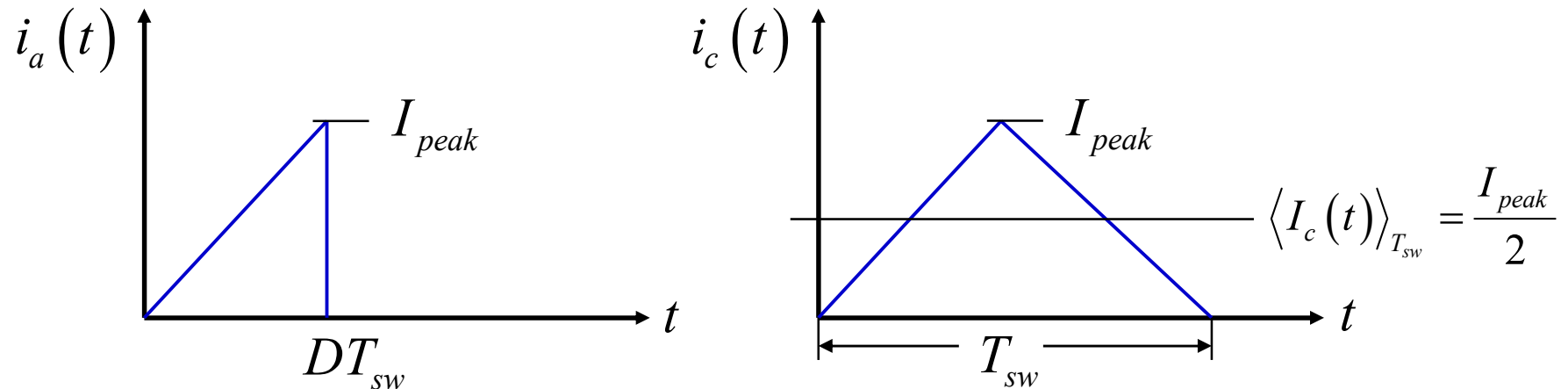- Observing the waveforms helps us deriving an average model




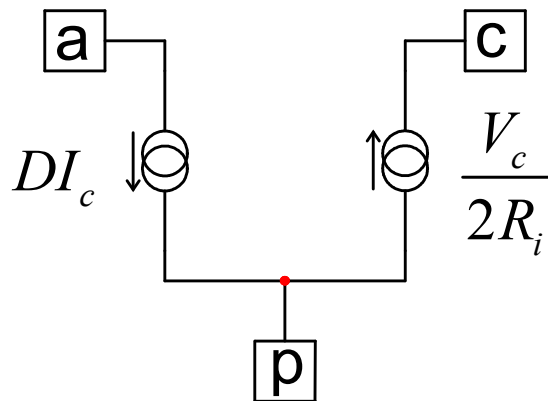- The structure is similar to that of the current-mode model



Derive the Operating Point

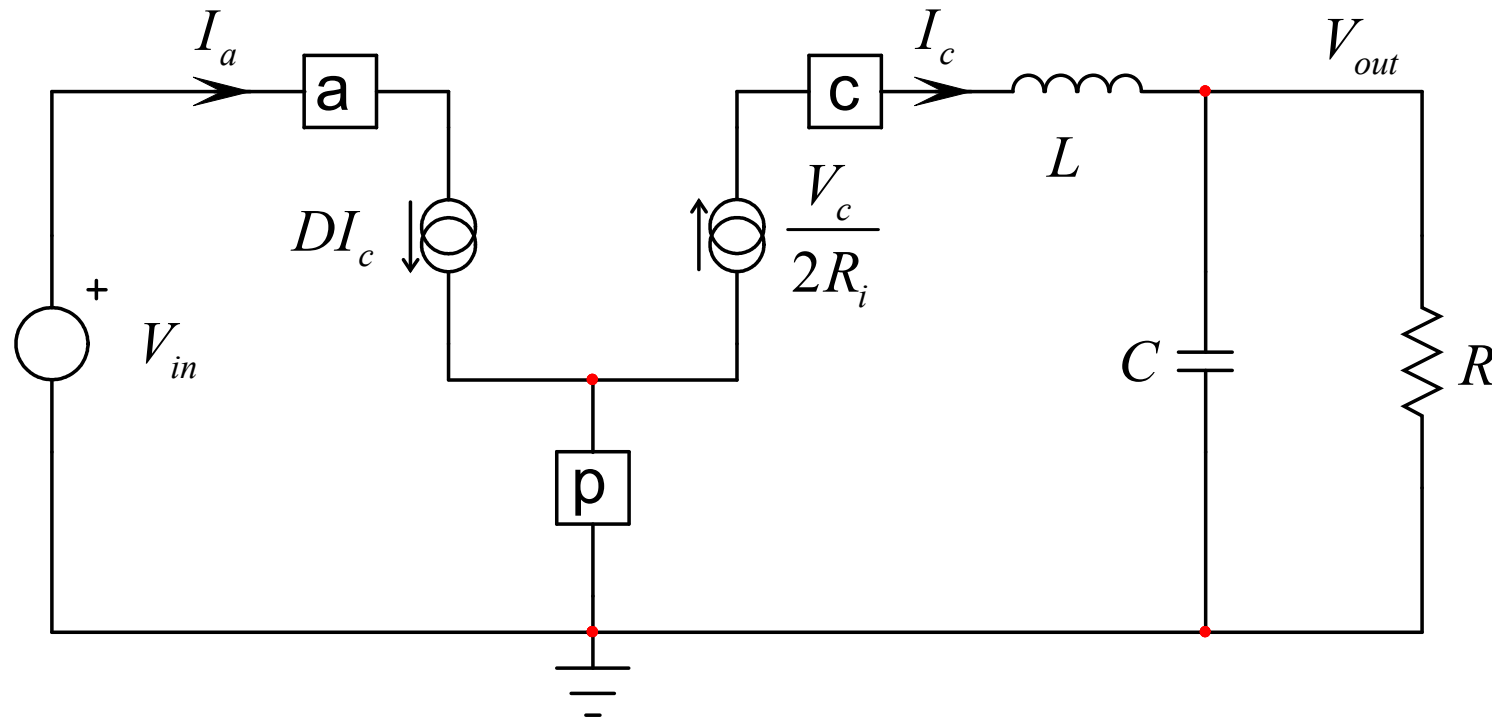
- Insert the model in a simple buck converter application



- Derive the dc operating point: short inductors, open caps

Write dc Equations

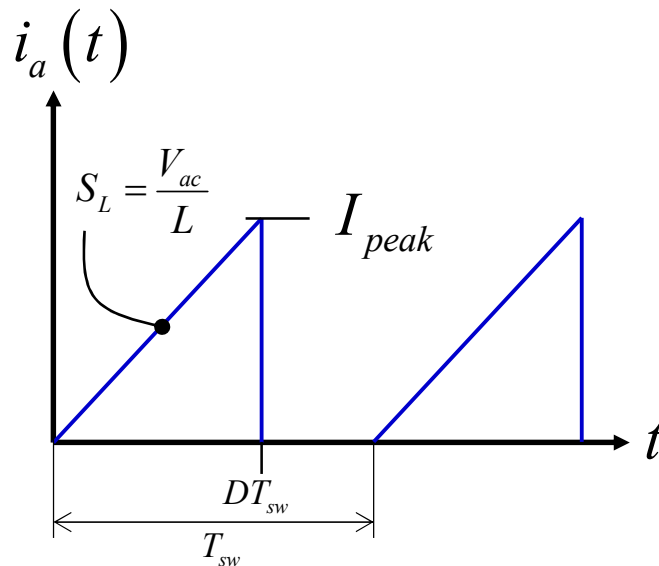- The inductor peak current is discontinuous



$$I_{peak} = \frac{V_c}{R_i} \quad I_{peak} = S_L t_{on} = \frac{V_{ac}}{L} DT_{sw}$$

$$\Rightarrow D = \frac{V_c}{R_i} \frac{L}{V_{ac} T_{sw}}$$

- Derive the switching frequency expression


$$t_{on} = \frac{V_c}{R_i} \frac{L}{V_{ac}} \quad t_{on} = \frac{V_c}{R_i} \frac{L}{V_{cp}}$$

\uparrow $1/S_{on}$ \uparrow $1/S_{off}$

$$\Rightarrow T_{sw} = t_{on} + t_{off} = \frac{V_c L}{R_i} \left(\frac{1}{V_{ac}} + \frac{1}{V_{cp}} \right)$$

A Large Signal Model

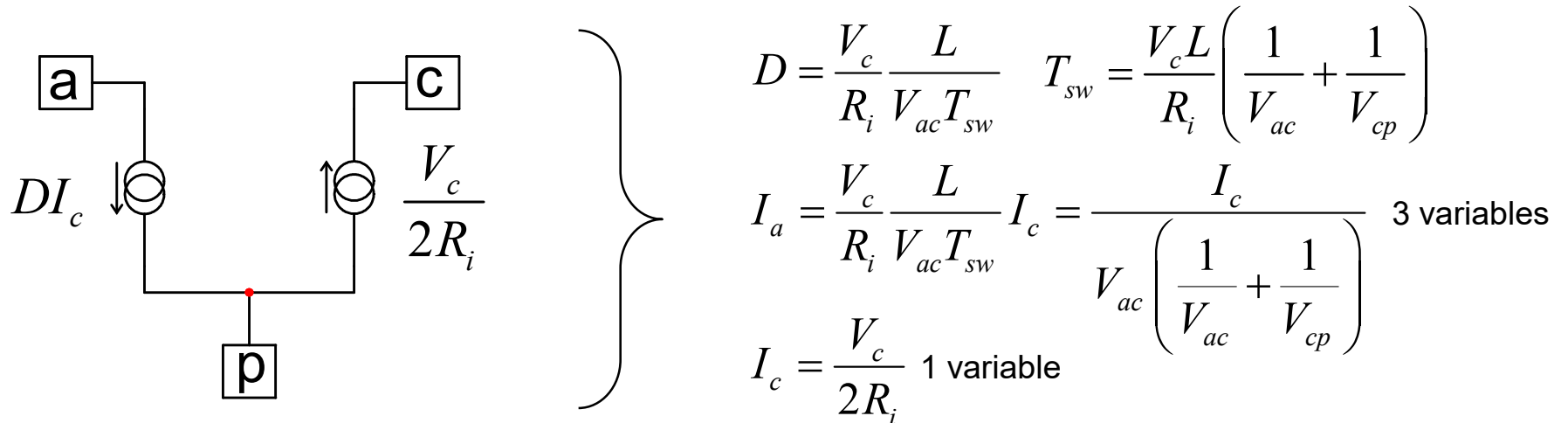- A Quasi Resonant model is built with the PWM switch model



- These are large-signal equations that need linearization

$$I_c = f(V_c) \longrightarrow \hat{i}_c = \frac{\partial I_c(V_c)}{\partial V_c} \hat{v}_c \quad \hat{i}_c = \hat{v}_c \left(\frac{1}{2R_i} \right) = \hat{v}_c k_c \quad k_c = \frac{1}{2R_i}$$

$$\hat{i}_a = \left. \frac{\partial I_a(V_{cp}, V_{ac}, I_c)}{\partial V_{cp}} \right|_{I_c, V_{ac}} \hat{v}_{cp} + \left. \frac{\partial I_a(V_{cp}, V_{ac}, I_c)}{\partial I_c} \right|_{V_{cp}, V_{ac}} \hat{i}_c + \left. \frac{\partial I_a(V_{cp}, V_{ac}, I_c)}{\partial V_{ac}} \right|_{I_c, V_{cp}} \hat{v}_{ac}$$




Large to Small-Signal

- Final steps before the small-signal model

$$\hat{i}_a = \hat{v}_{cp} \frac{I_{c0} V_{ac0}}{(V_{ac0} + V_{cp0})^2} + \frac{V_{cp0}}{V_{cp0} + V_{ac0}} \hat{i}_c - \hat{v}_{ac} \frac{V_{cp0} I_{c0}}{(V_{ac0} + V_{cp0})^2}$$


$$k_{cp} = \frac{I_{c0} V_{cp0}}{(V_{ac0} + V_{cp0})^2} \quad k_{ic} = \frac{V_{cp0}}{V_{cp0} + V_{ac0}} \quad k_{ac} = \frac{V_{cp0} I_{c0}}{(V_{ac0} + V_{cp0})^2}$$

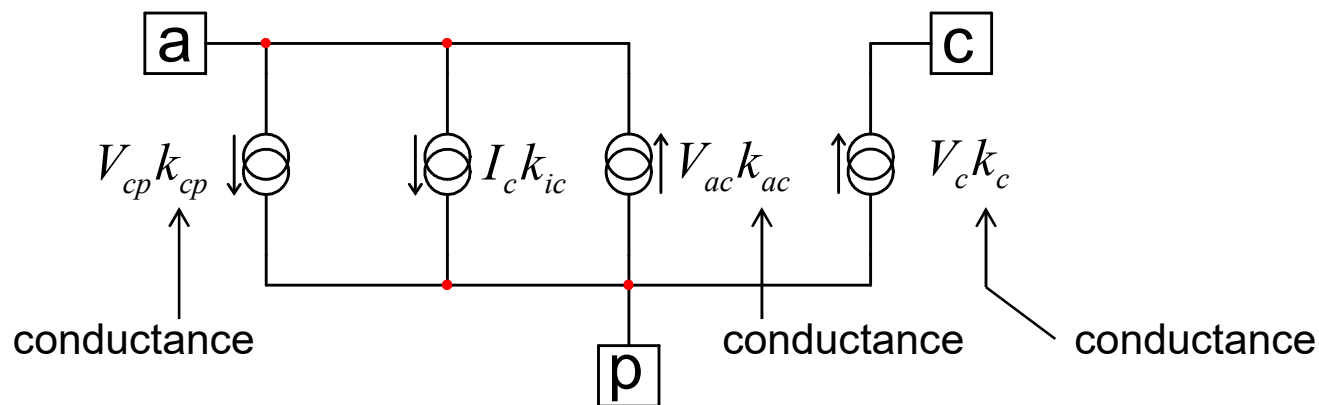- A small-signal model can now be assembled



The Model at Work in an Isolated Converter

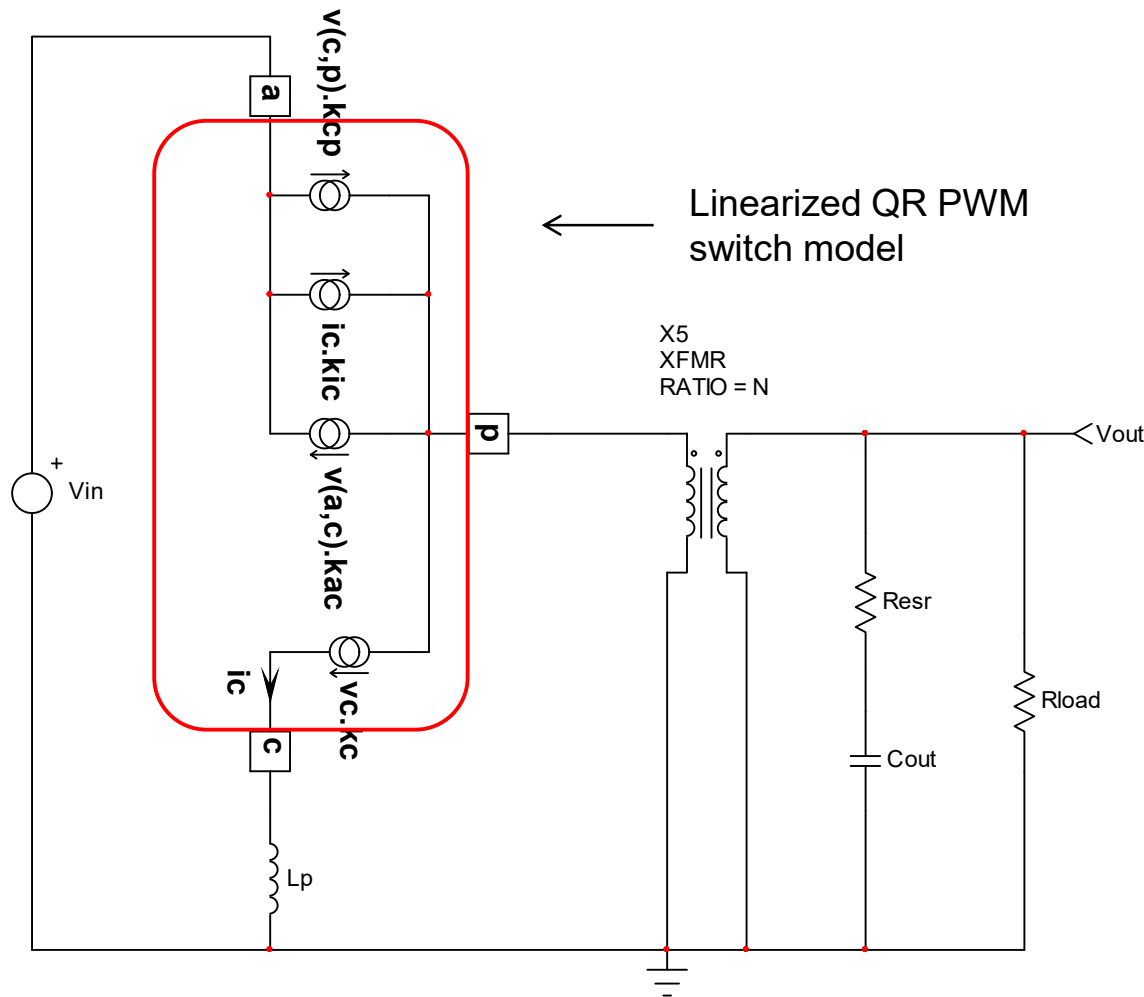- The model can be inserted into a flyback configuration



$$V_{cp0} = \frac{V_{out}}{N} \quad I_{c0} = \frac{V_{c0}}{2R_i}$$

$$V_{ac0} = V_{in}$$



$$k_{cp} = \frac{V_{in} V_{c0} N^2}{2R_i (V_{out} + NV_{in})^2}$$


$$k_{ic} = \frac{V_{out}}{V_{out} + NV_{in}}$$


$$k_{ac} = \frac{V_{out} V_{c0} N}{2R_i (V_{out} + NV_{in})^2}$$



Start the Study with the dc Gain

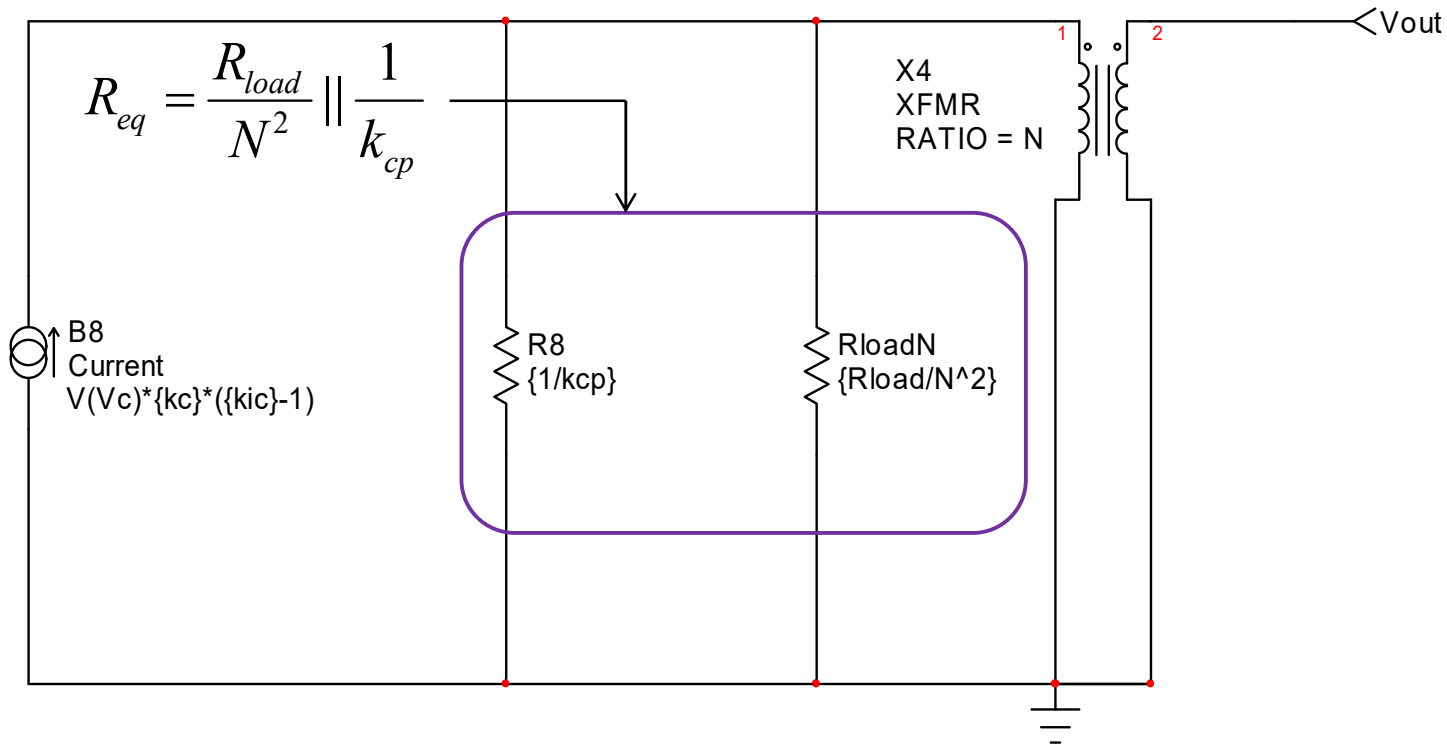
- V_{in} is constant in small-signal, hence $\hat{v}_{in} = 0$



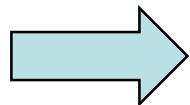
 $G_0 = k_c (1 - k_{ic}) R_{eq} N$

Put all Elements Back in Place

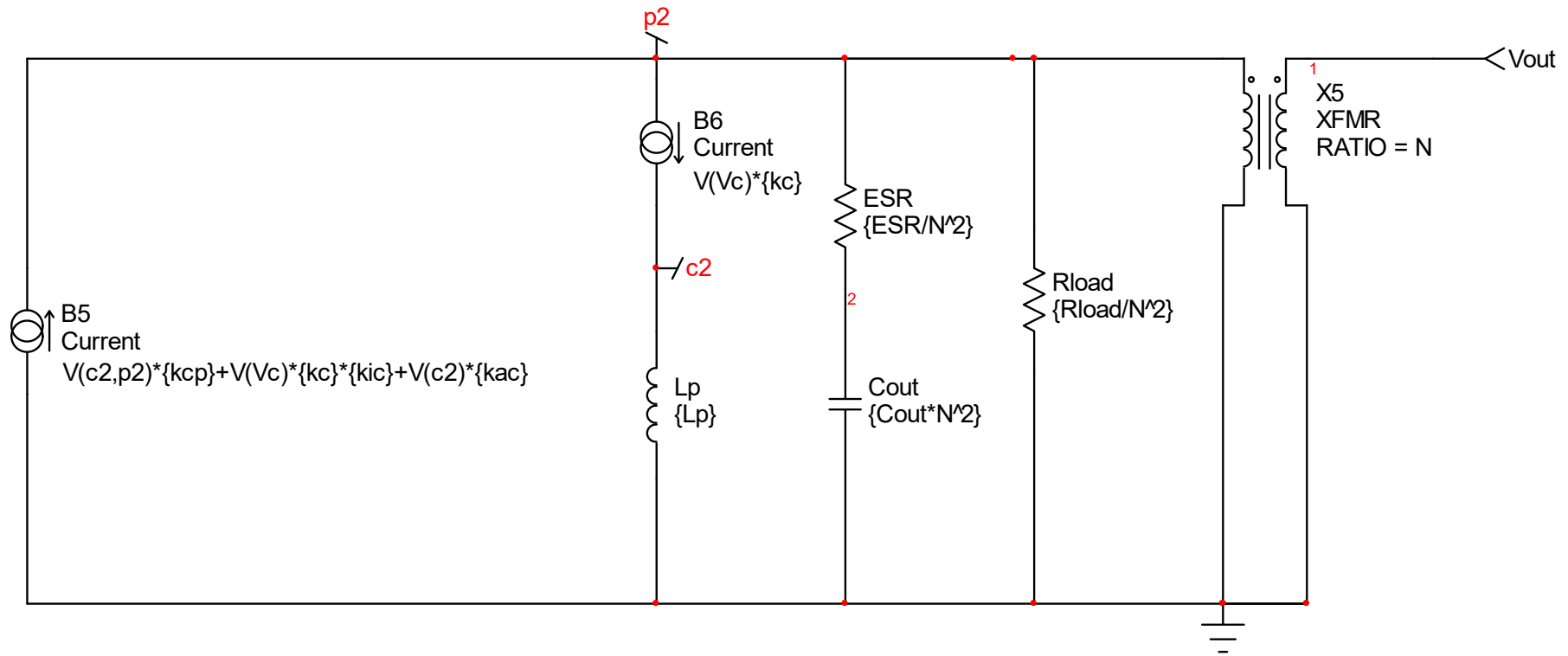- The ac analysis requires the complete model



- Kirchhoff's Current and Voltage Laws now apply

Final Transfer Function Equations

- The plant features one Right Half-Plane Zero

$$\frac{\hat{v}_{out}(s)}{\hat{v}_c(s)} = \frac{Nk_c(1-k_{ic})}{k_{cp} + \frac{N^2}{R_{load}}} \frac{(1+sR_{ESR}C_{out}) \left(1 - sL_p \frac{k_{cp} + k_{ac}}{1-k_{ic}}\right)}{1+sC_{out} \left(\frac{N^2 + \frac{N^2 R_{ESR}}{R_{load}} + k_{cp} R_{ESR}}{k_{cp} + \frac{N^2}{R_{load}}} \right)} = G_0 \frac{\left(1 + \frac{s}{s_{z_1}}\right) \left(1 - \frac{s}{s_{z_2}}\right)}{\left(1 + \frac{s}{s_{p_1}}\right)}$$

$$G_0 = \frac{Nk_c(1-k_{ic})}{k_{cp} + \frac{N^2}{R_{load}}} \quad s_{z_1} = \frac{1}{R_{ESR}C_{out}} \quad s_{z_2} = \frac{1-k_{ic}}{(k_{cp} + k_{ac})L_p} = \frac{1}{L_p \frac{V_c}{2R_i V_{in}}}$$

$$s_{p_1} = \frac{1}{C_{out} \left(\frac{N^2 + \frac{N^2 R_{ESR}}{R_{load}} + k_{cp} R_{ESR}}{k_{cp} + \frac{N^2}{R_{load}}} \right)}$$



Check Analytical Results Versus Simulation


□ A sanity check is important to verify the derivation

parameters

$V_{in}=100$
 $R_{load}=10$
 $N=-0.25$
 $ESR=1$
 $C_{out}=100\mu$
 $L_p=1m$
 $V_c=1.7$
 $R_i=1$
 $F_{sw}=25.6k$


$I_c=V_c/(2 \cdot R_i)$
 $V_{ac}=100$
 $V_{cp}=76.9$

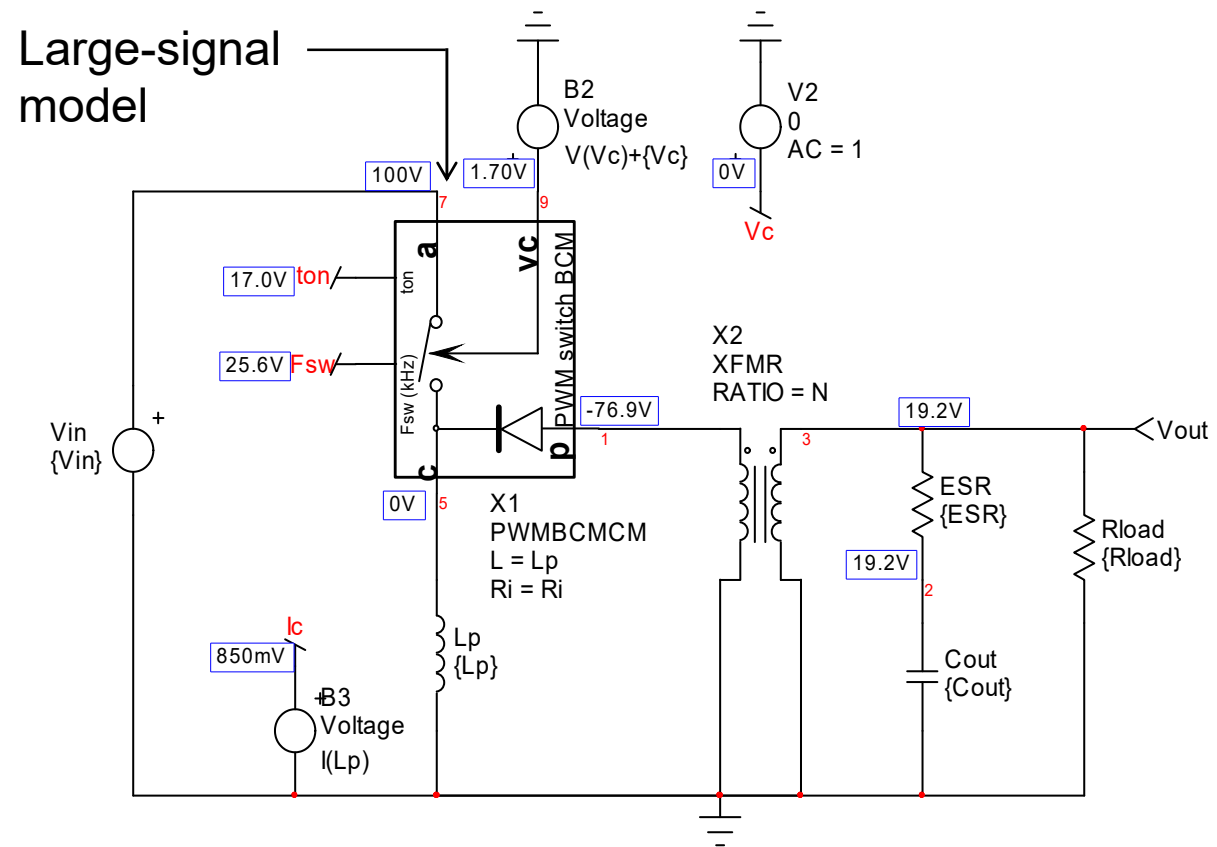$k_c=1/(2 \cdot R_i)$
 $k_{cp}=V_{ac} \cdot I_c / (V_{cp} + V_{ac})^2$
 $k_{ic}=V_{cp} / (V_{cp} + V_{ac})$
 $k_{ac}=V_{cp} \cdot I_c / (V_{cp} + V_{ac})^2$



Final Lap!

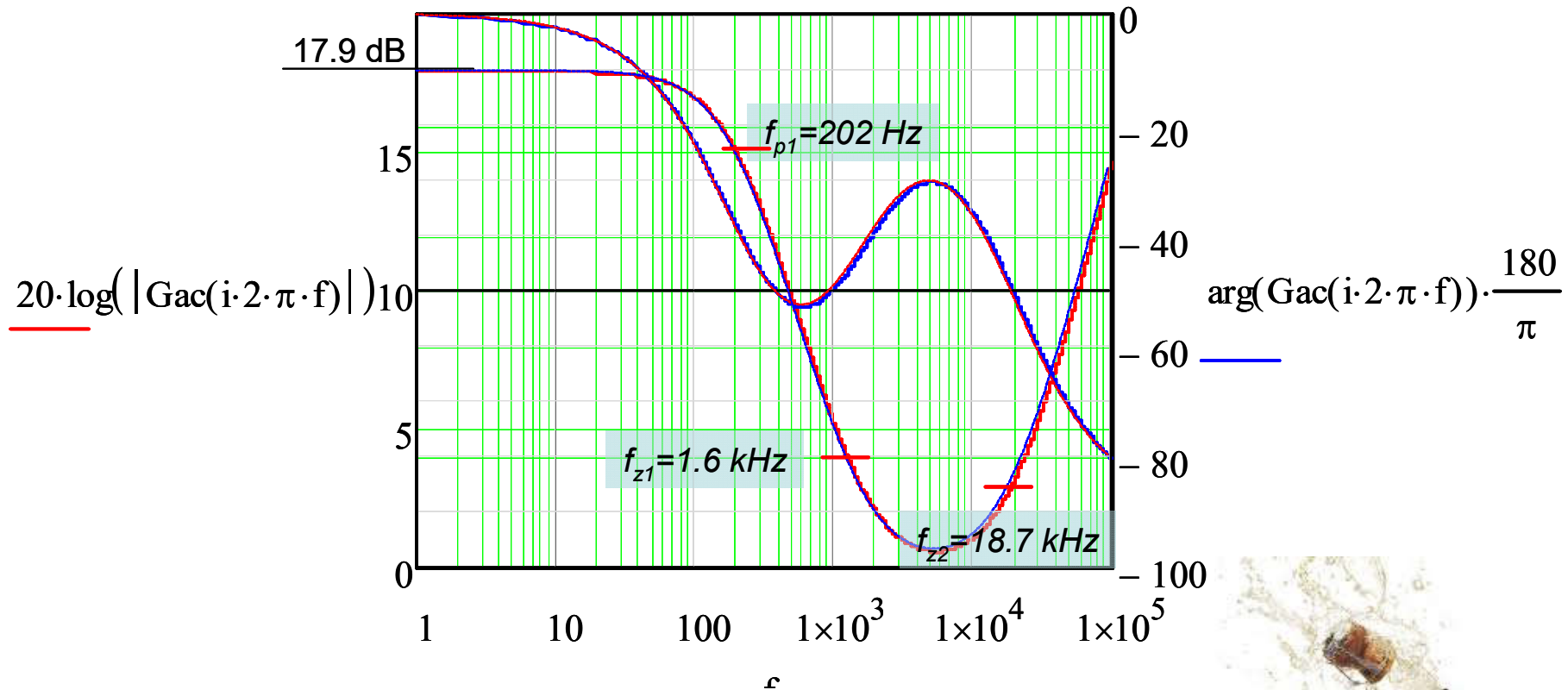- Compare simulated results with Mathcad® plots



- They perfectly superimpose...



Conclusion

- ❑ Small-signal modeling is an important part of design
- ❑ Understanding the technique is key to quickly deriving equations
- ❑ State-space averaging is an option but it is tedious and long
- ❑ Small-signal modeling using the PWM switch is simple and fast
- ❑ Available tools help to perform intermediate sanity checks
- ❑ Analytical analysis does not shield you against lab. experiments
- ❑ Analytical analysis, simulation and bench: the best combination!



Merci !
Thank you!
Xiè-xie!

