



ON Semiconductor®

Small-Signal Modeling at Work with Power Converters

Christophe Basso

IEEE Senior Member

Course Agenda

- ❑ Introducing the PWM Switch Model
- ❑ CCM, DCM and BCM in Voltage Mode
- ❑ Pulse Width Modulator Gain
- ❑ The PWM Switch Model in Current Mode
- ❑ PWM Switch at Work in a Buck Converter
- ❑ A Simplified Approach to Modeling a DCM Boost
- ❑ Transfer Function of a BCM Boost in Current Mode
- ❑ Small-Signal Model of The Active Clamp Forward




Course Agenda

- Introducing the PWM Switch Model**
- CCM, DCM and BCM in Voltage Mode
- Pulse Width Modulator Gain
- The PWM Switch Model in Current Mode
- PWM Switch at Work in a Buck Converter
- A Simplified Approach to Modeling a DCM Boost
- Transfer Function of a BCM Boost in Current Mode
- Small-Signal Model of The Active Clamp Forward




Manipulating Linear Networks

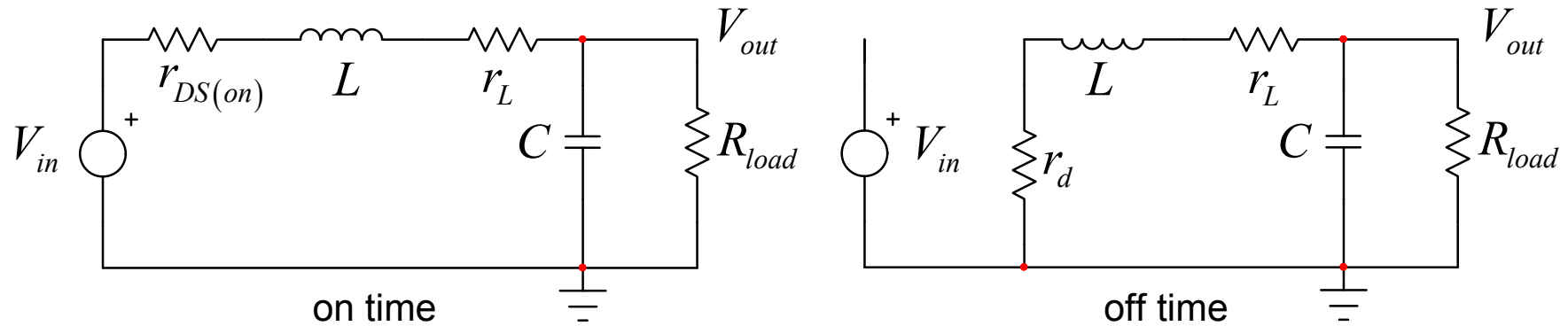- A switching converter is made of linear elements!




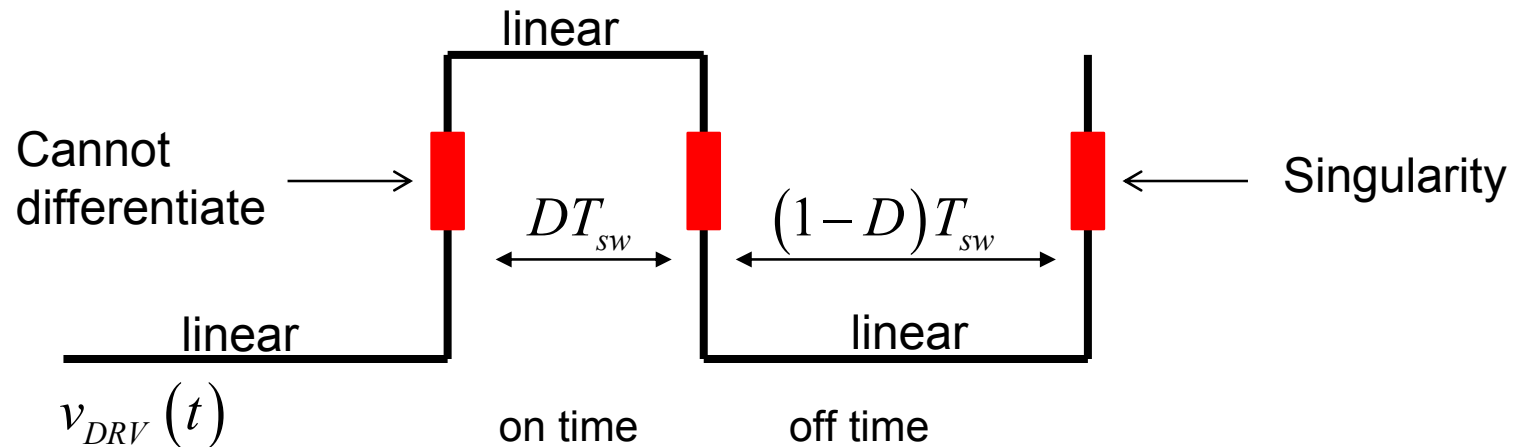- The non-linearity or discontinuity is coming from transitions




The PWM Switch Model in Voltage Mode

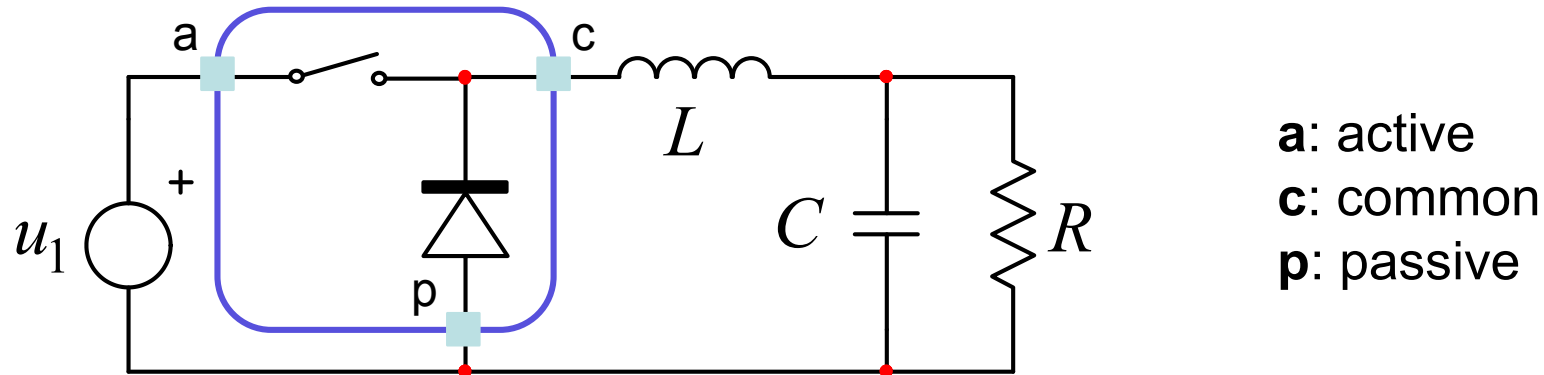- We know that non-linearity is brought by the switching cell




- Why don't we linearize the cell alone?

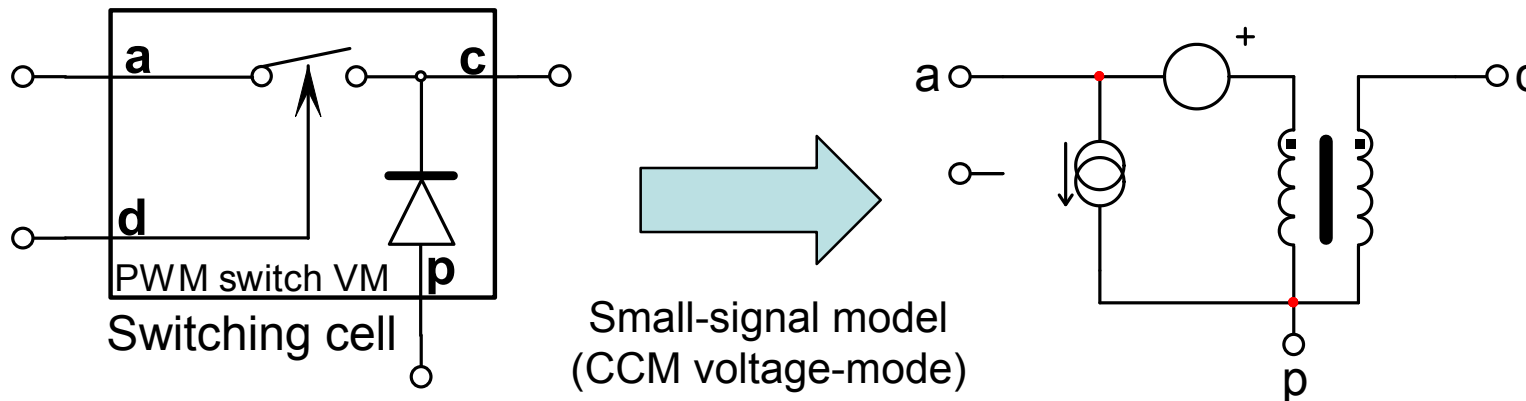

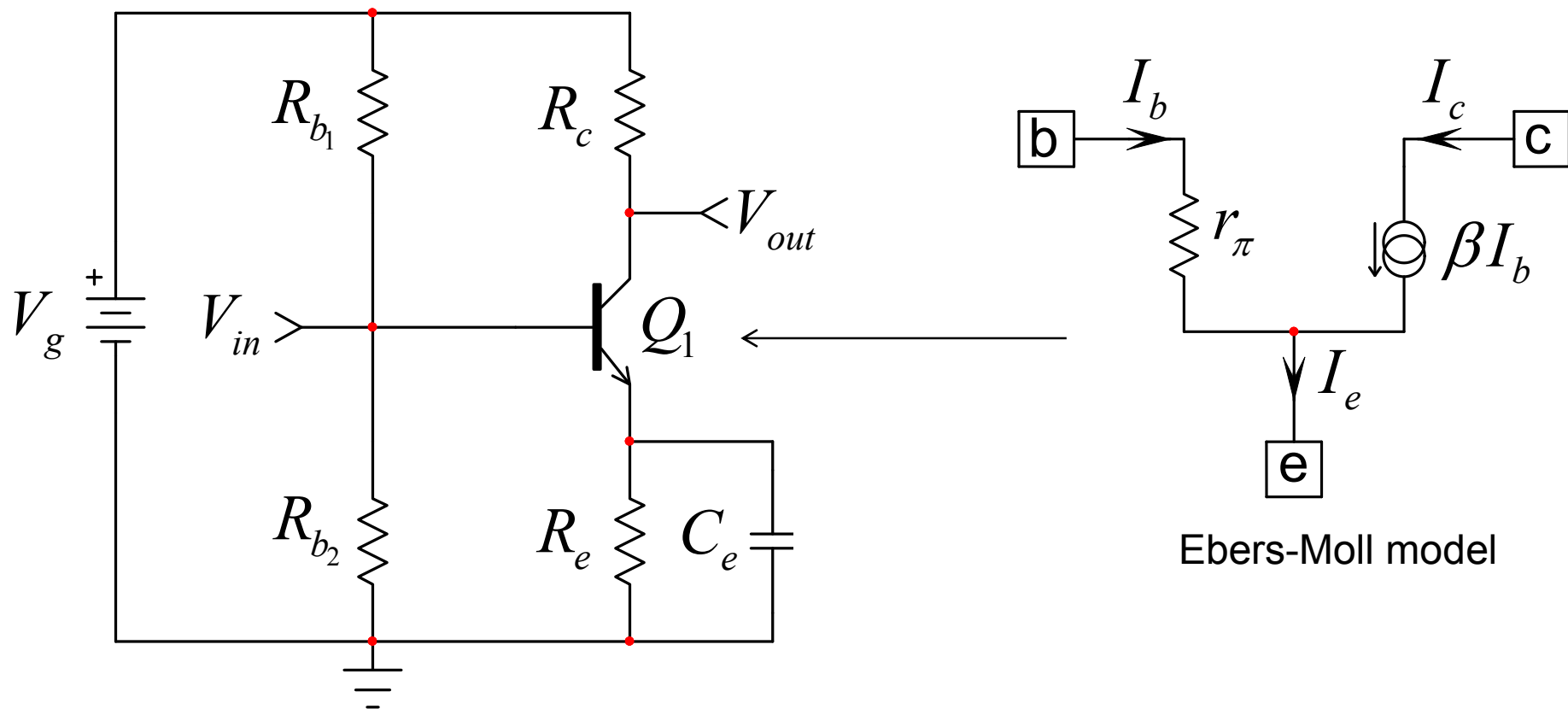V. Vorperian, "Simplified Analysis of PWM Converters using Model of PWM Switch, parts I and II" IEEE Transactions on Aerospace and Electronic Systems, Vol. 26, NO. 3, 1990


The Bipolar Small-Signal Model

- ❑ A bipolar transistor is a highly non-linear system
- ❑ Replace it by its small-signal model to get the response




Replace the Switches by the Model

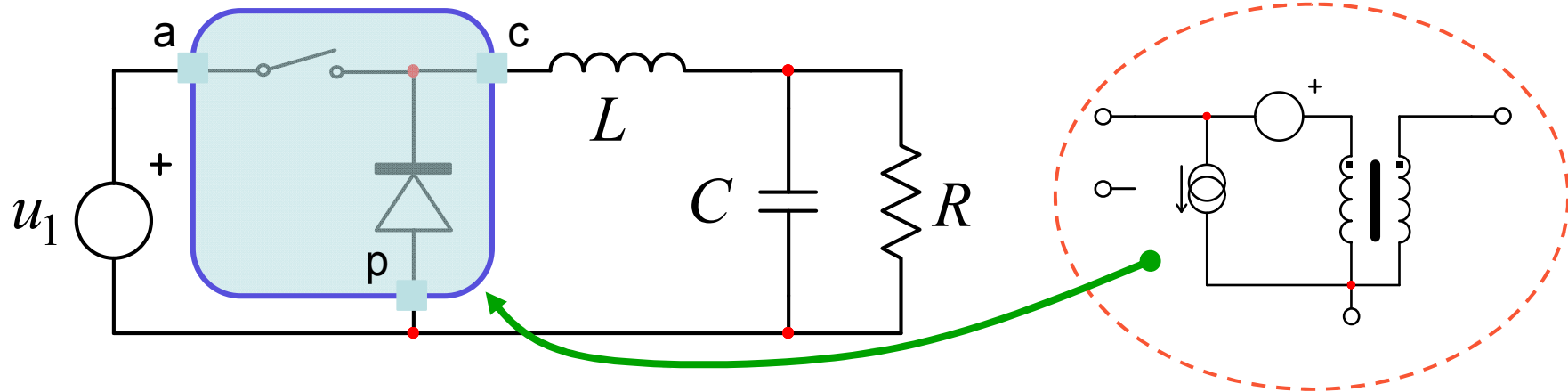- Like in the bipolar circuit, replace the switching cell...




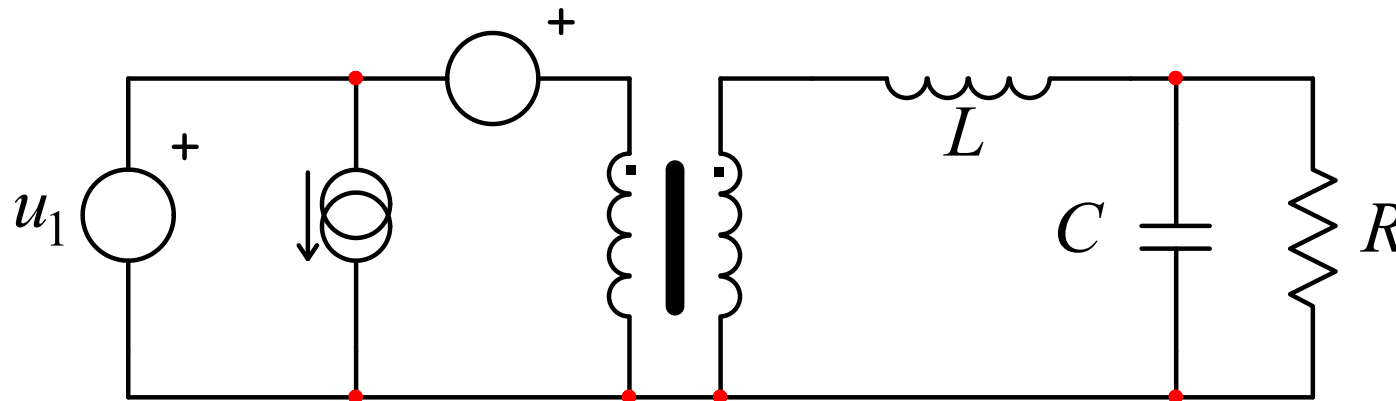- ...and solve a set of linear equations!




An Invariant Model

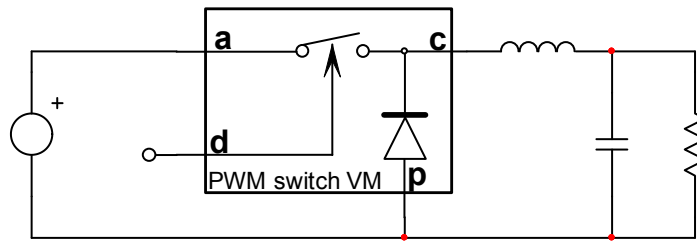
- The switching cell made of two switches is everywhere!





buck

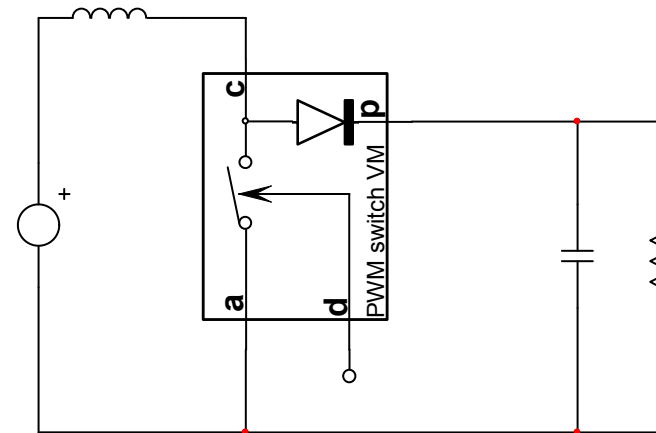

boost

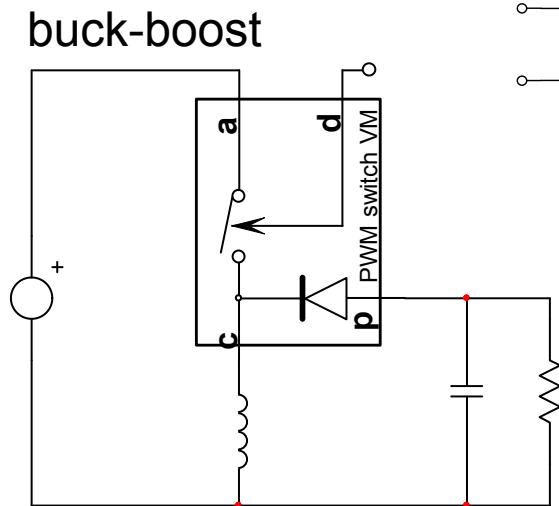

buck-boost

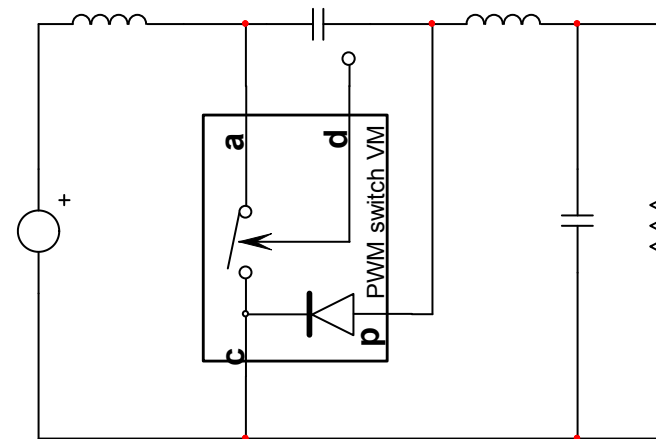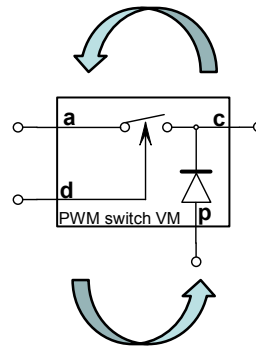

Ćuk




Course Agenda

- Introducing the PWM Switch Model
- **CCM, DCM and BCM in Voltage Mode**
- Pulse Width Modulator Gain
- The PWM Switch Model in Current Mode
- PWM Switch at Work in a Buck Converter
- A Simplified Approach to Modeling a DCM Boost
- Transfer Function of a BCM Boost in Current Mode
- Small-Signal Model of The Active Clamp Forward




CCM, DCM and BCM Operations


□ Three types of conduction modes exist

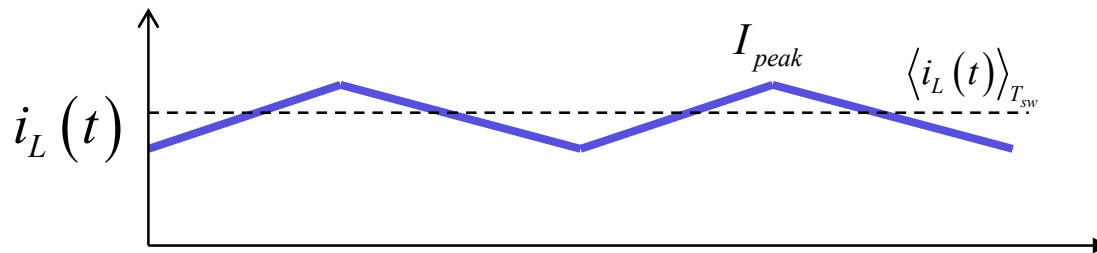

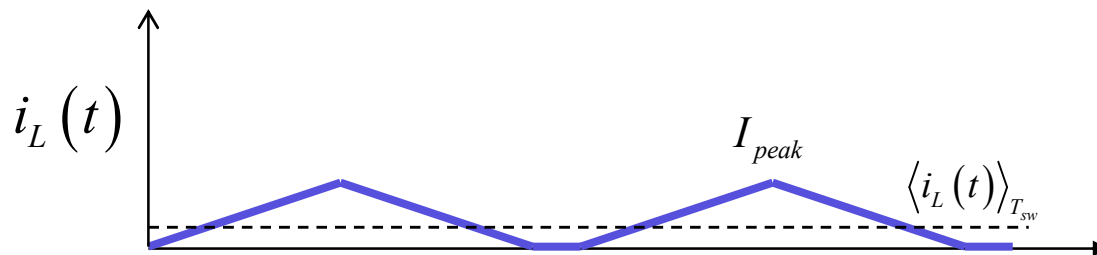Continuous
Conduction
Mode $\langle i_L(t) \rangle_{T_{sw}} > \frac{I_{peak}}{2}$



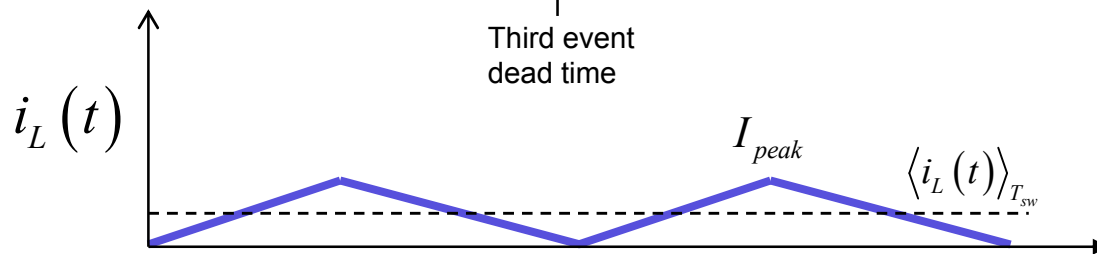Discontinuous
Conduction
Mode $\langle i_L(t) \rangle_{T_{sw}} < \frac{I_{peak}}{2}$



Boundary
Conduction
Mode $\langle i_L(t) \rangle_{T_{sw}} = \frac{I_{peak}}{2}$


□ Each mode has its own small-signal characteristics

➤ A model is needed for these three modes!




CCM Common Passive Configuration

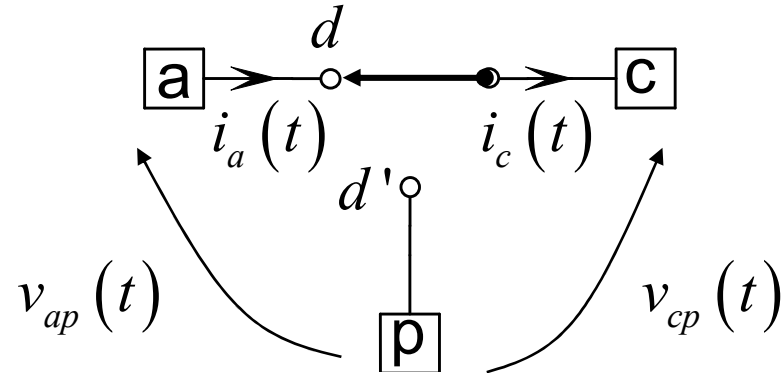- The PWM switch is a single-pole double-throw model




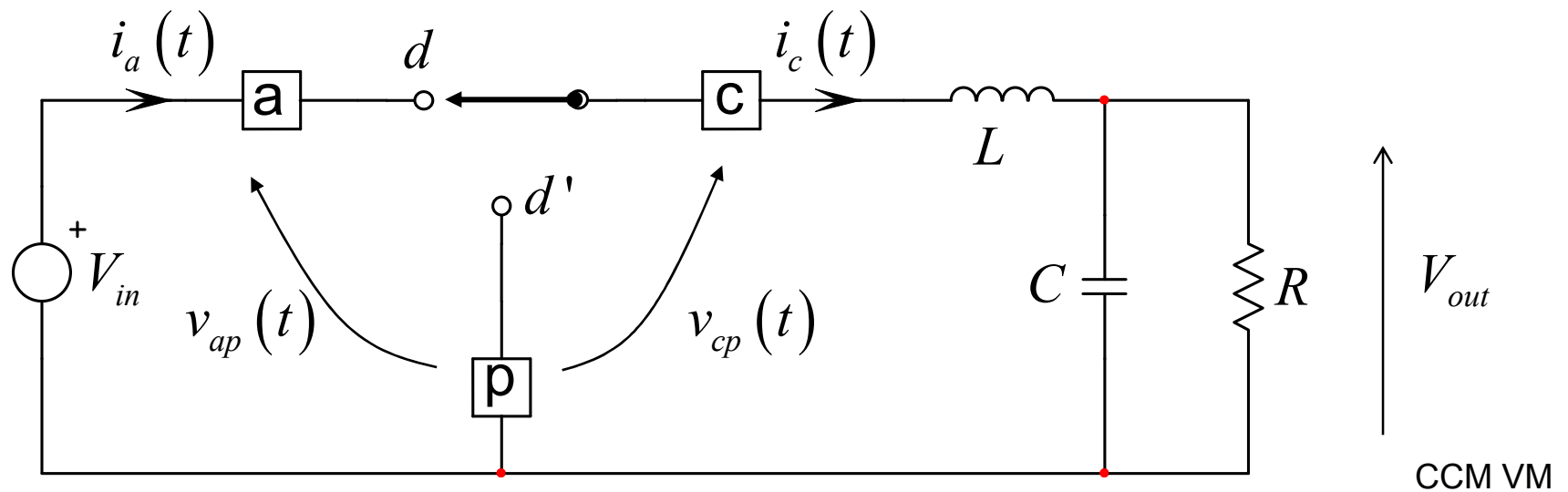- Install it in a buck and draw its terminals waveforms



The Common Passive Configuration

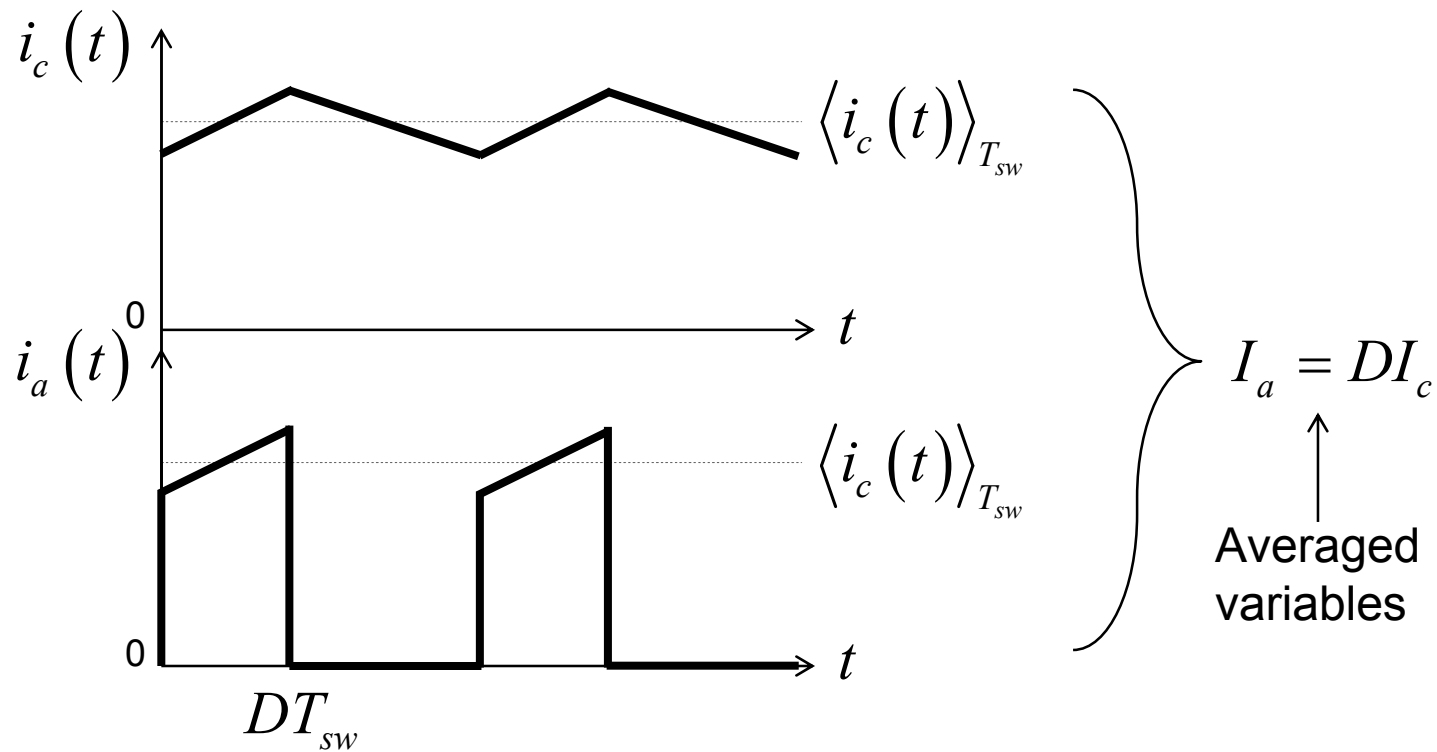- Average the current waveforms across the PWM switch




$$\langle i_a(t) \rangle_{T_{sw}} = I_a = \frac{1}{T_{sw}} \int_0^{DT_{sw}} i_a(t) dt = D \langle i_c(t) \rangle_{T_{sw}} = DI_c$$

CCM VM



The Common Passive Configuration

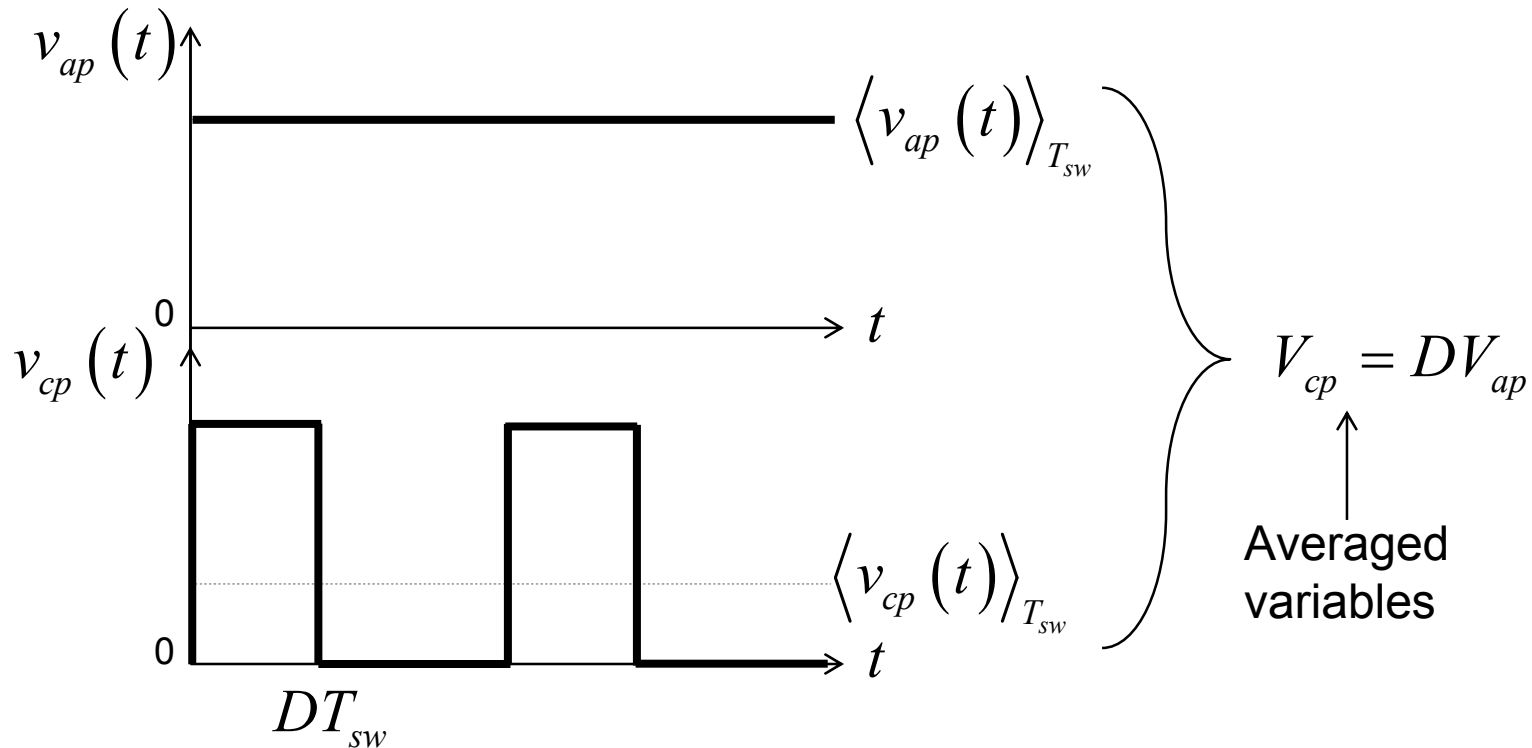- Average the voltage waveforms across the PWM switch




$$\langle v_{cp}(t) \rangle_{T_{sw}} = V_{cp} = \frac{1}{T_{sw}} \int_0^{DT_{sw}} v_{cp}(t) dt = D \langle v_{ap}(t) \rangle_{T_{sw}} = DV_{ap}$$

CCM VM




A Two-Port Representation

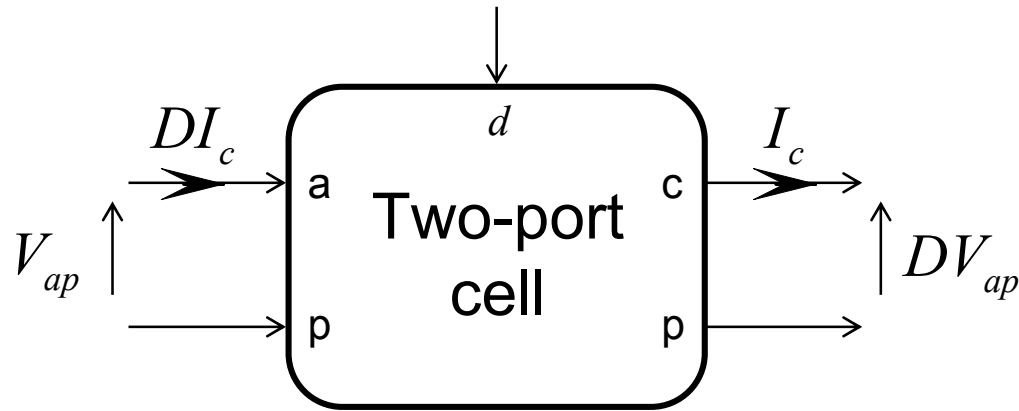- We have a link between input and output variables



- It can further be illustrated with current and voltage sources

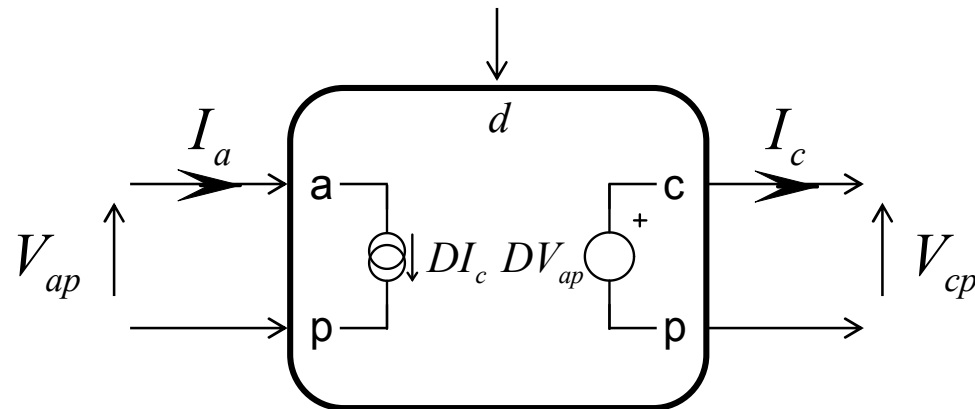


CCM VM




A Transformer Representation

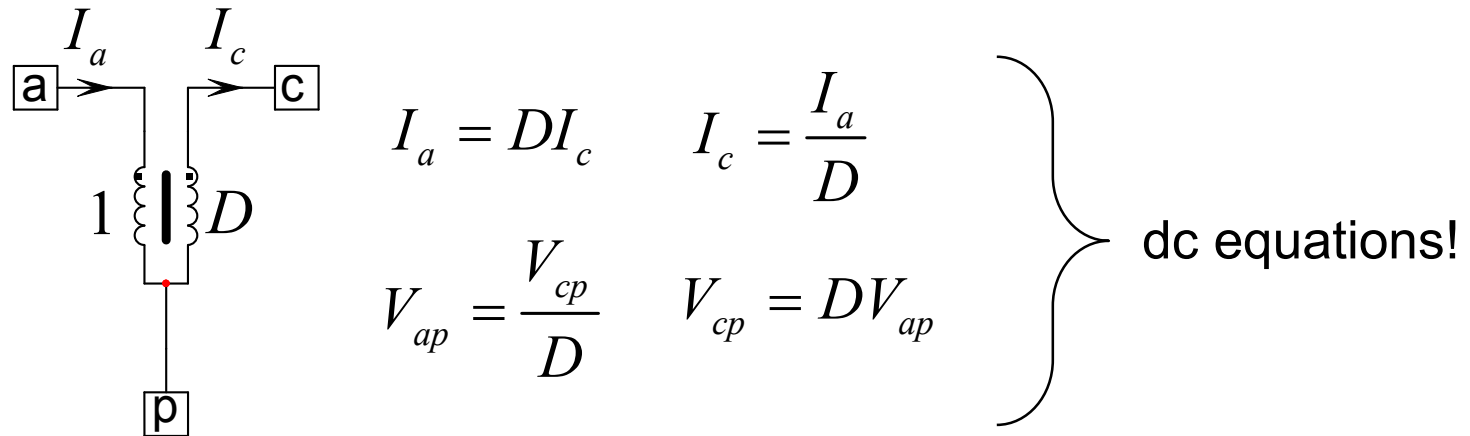- The PWM switch large-signal model is a dc "transformer"!







- It can be plugged into any 2-switch CCM converter

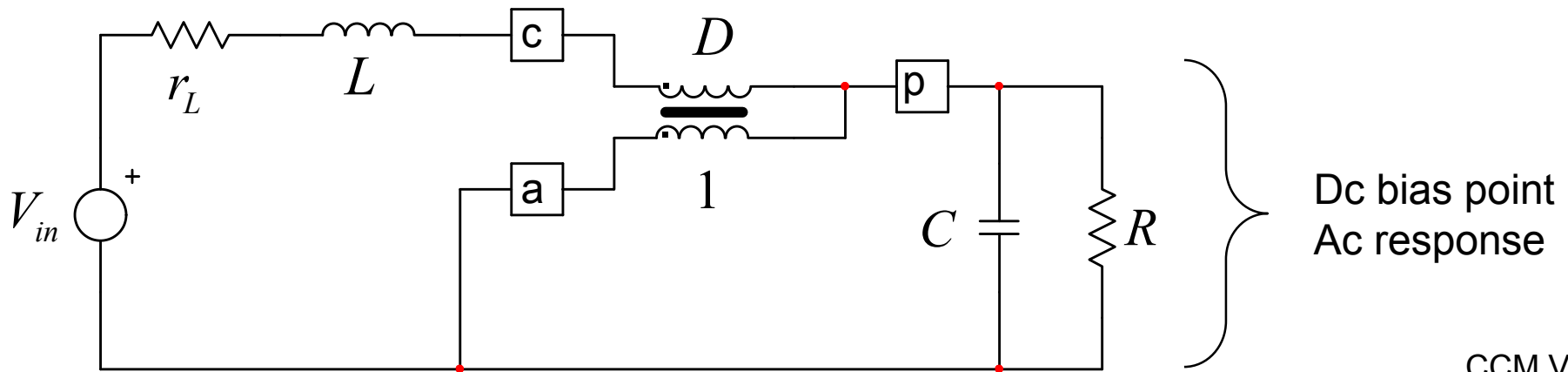

CCM VM

The Discontinuous Case

□ In DCM, a third timing event exists when $i_L(t) = 0$

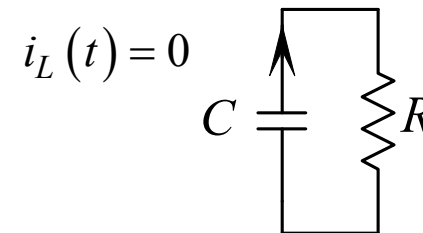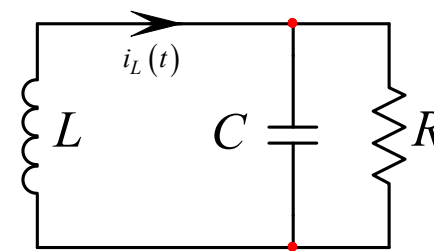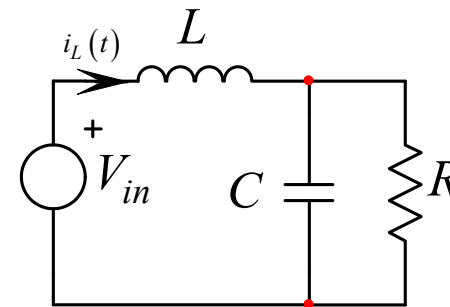
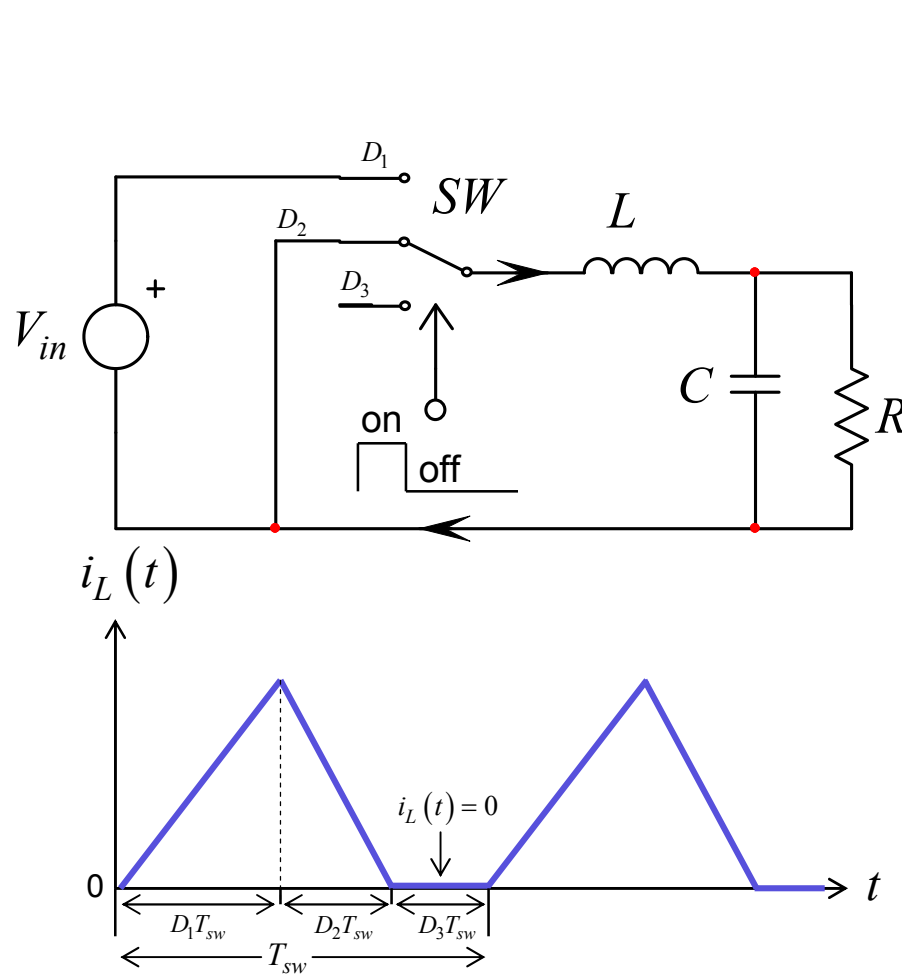


DCM VM



The Same Configuration as in CCM

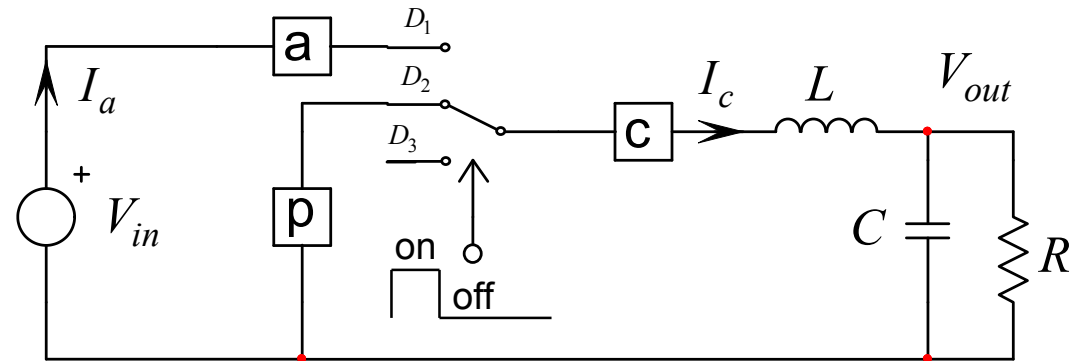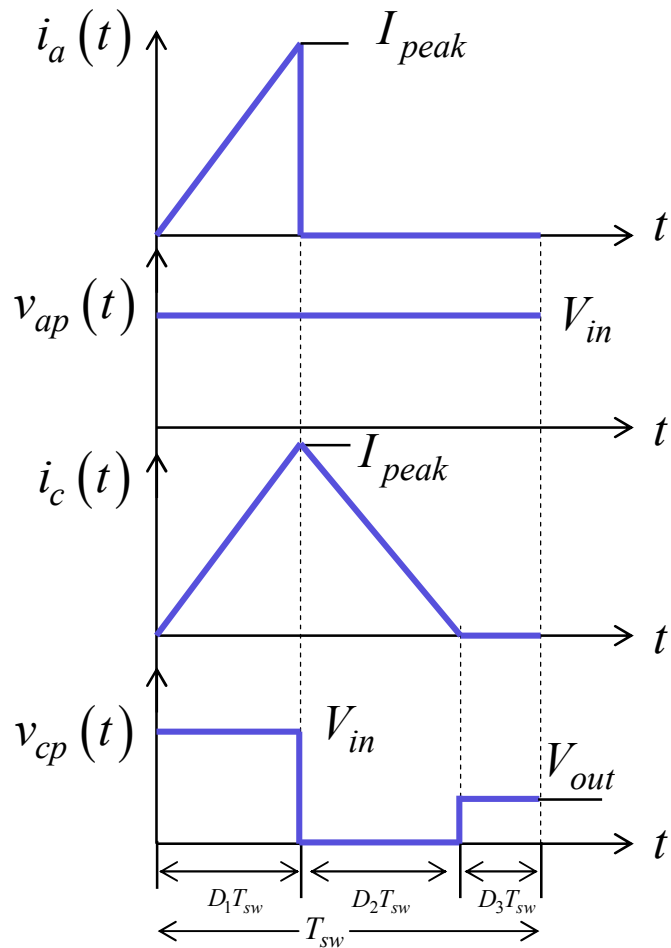□ Draw the waveforms in the "common passive" configuration



□ Average the waveforms:

$$I_a = \frac{I_{peak}}{2} D_1$$

$$I_c = \frac{I_{peak}}{2} D_1 + \frac{I_{peak}}{2} D_2 = \frac{I_{peak}}{2} (D_1 + D_2)$$


$$I_c = \frac{2I_a}{D_1} \frac{D_1 + D_2}{2} = I_a \frac{D_1 + D_2}{D_1}$$

DCM VM



Derive V_{cp} to Unveil the New Model

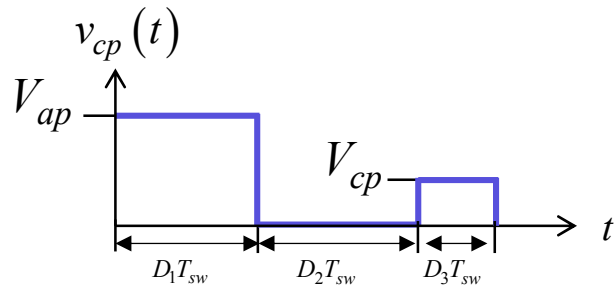
□ The addition of the third event complicates the equations



$$V_{cp} = V_{ap} D_1 + V_{cp} D_3 \quad D_1 + D_2 + D_3 = 1$$


$$V_{cp} = V_{ap} D_1 + V_{cp} (1 - D_1 - D_2)$$
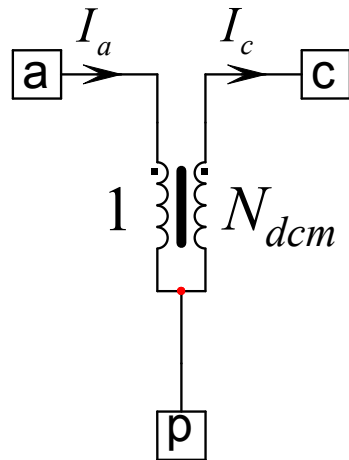
$$V_{cp} = V_{ap} \frac{D_1}{D_1 + D_2}$$



$$I_a = N_{dcm} I_c \quad I_c = \frac{I_a}{N_{dcm}}$$

$$V_{ap} = \frac{V_{cp}}{N_{dcm}} \quad V_{cp} = N_{dcm} V_{ap}$$

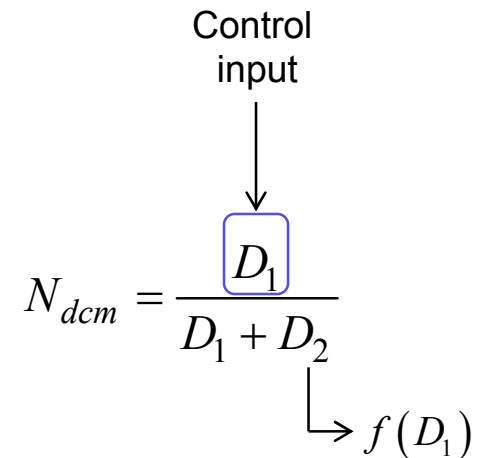

DCM VM



Finally, Get the D_2 Value

- In DCM the inductor average voltage per cycle is always 0

$$\longrightarrow V_{cp} = V_{out}$$

- What is the averaged inductor peak current?

$$\left. \begin{aligned} I_{peak} &= \frac{\langle v_L(t) \rangle_{D_1 T_{sw}}}{L} D_1 T_{sw} \\ \langle v_L(t) \rangle_{D_1 T_{sw}} &= V_{ac} \end{aligned} \right\} V_{ac} = L \frac{I_{peak}}{D_1 T_{sw}}$$

- The peak current uses a previous expression

$$I_c = \frac{I_{peak}}{2} (D_1 + D_2) \longrightarrow I_{peak} = \frac{2I_c}{D_1 + D_2}$$


$$\longrightarrow D_2 = \frac{2LF_{sw}}{D_1} \frac{I_c}{V_{ac}} - D_1$$

DCM VM



Benefits of Quasi-Resonance

- Wait for core demagnetization and valley voltage

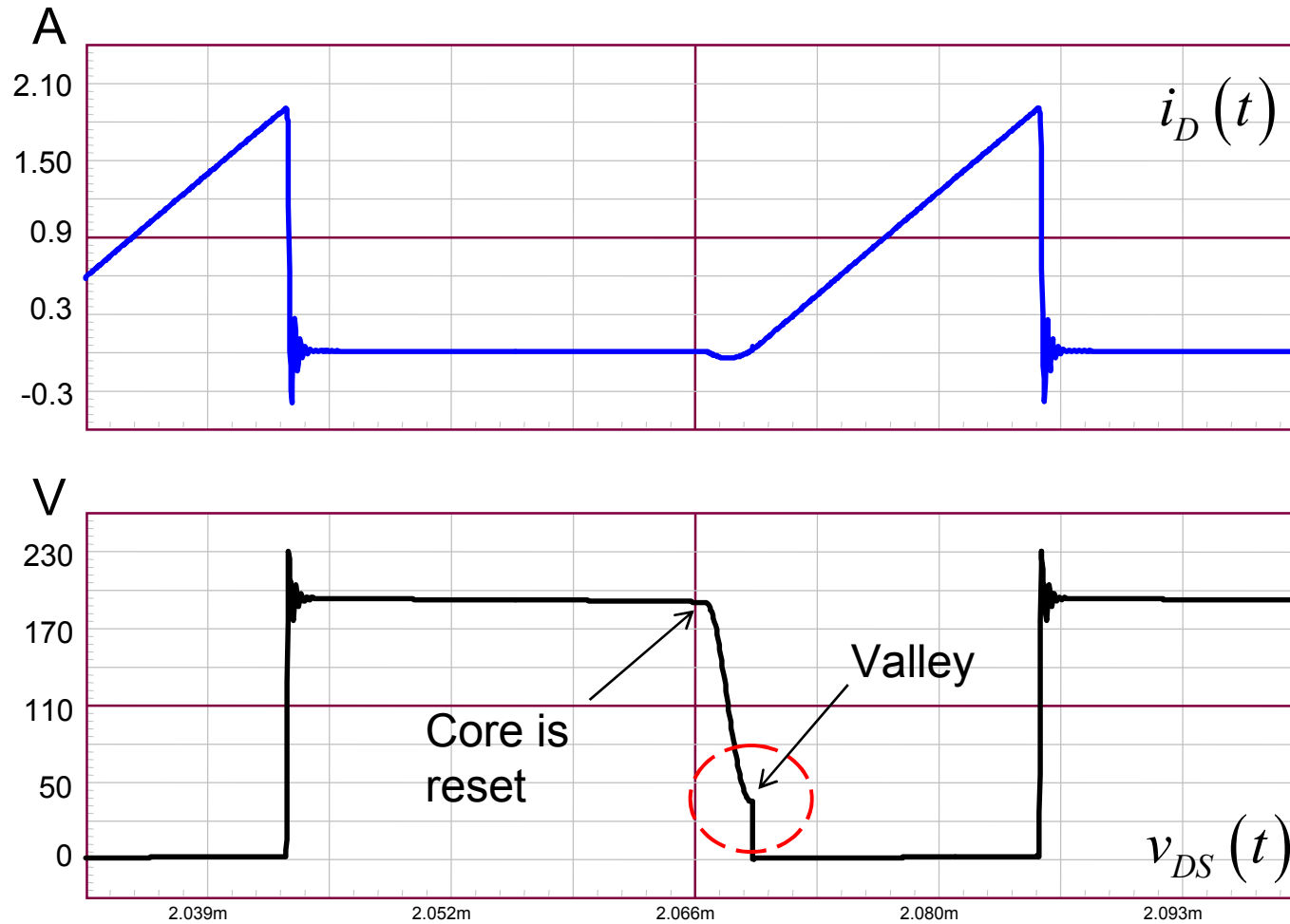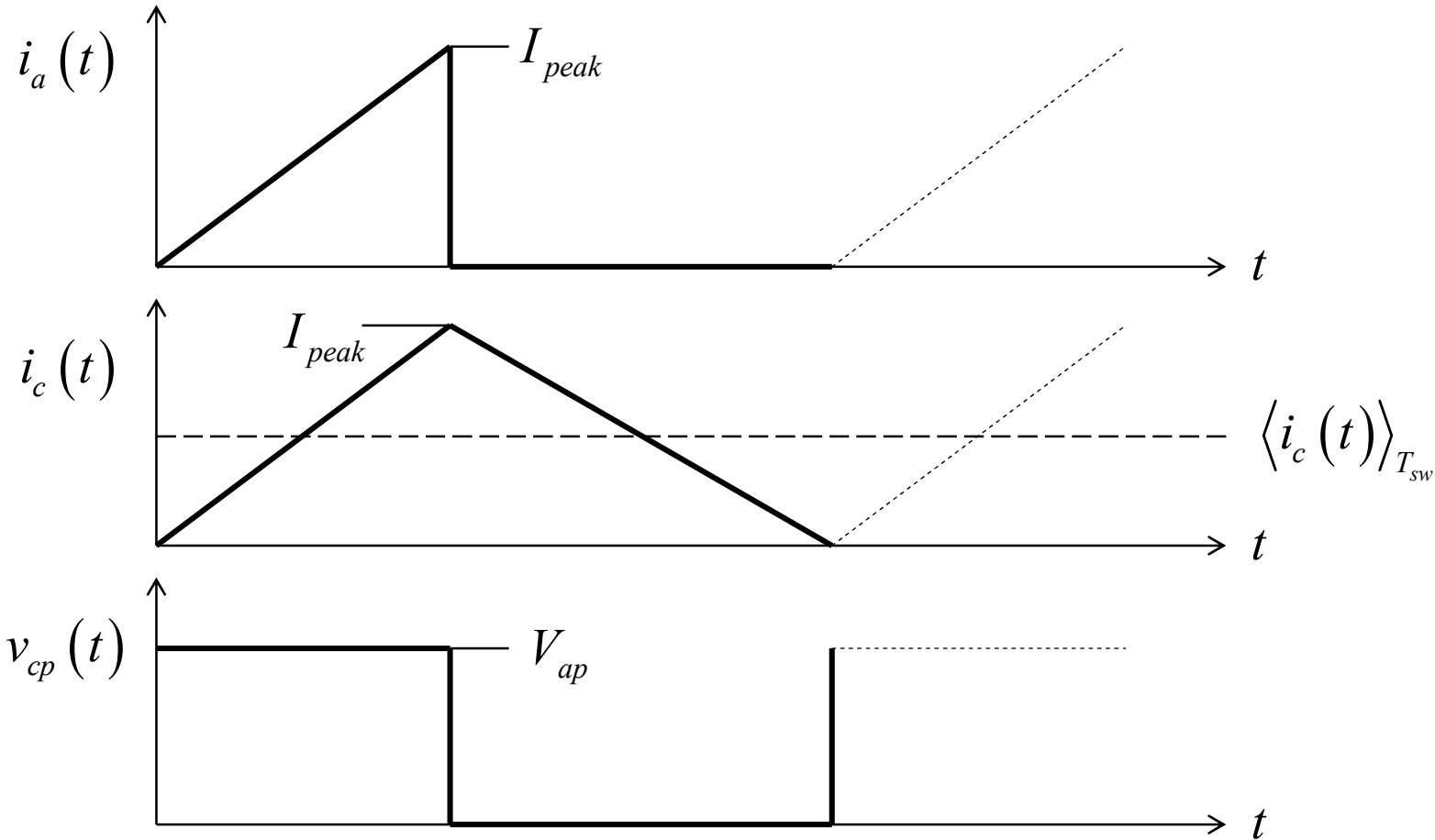


BCM VM



Idealized Waveforms

□ Draw the PWM switch waveforms in a buck configuration

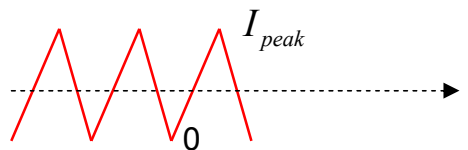


BCM VM



Derive Founding Equations

- Average current in terminal C is straightforward


$$\langle i_c(t) \rangle_{T_{sw}} = \frac{I_{peak}}{2}$$

- The off time depends on the voltage across the inductor

$$t_{off} = \frac{L}{V_{cp}} I_{peak} \quad I_{peak} = 2I_c \quad \longrightarrow \quad t_{off} = \frac{2LI_c}{V_{cp}}$$

- Period and duty ratio come easily as t_{on} is imposed

$$t_{on} + t_{off} = T_{sw} \quad D = \frac{t_{on}}{T_{sw}}$$




Need to transform the error voltage into time

BCM VM



Generating the On Time

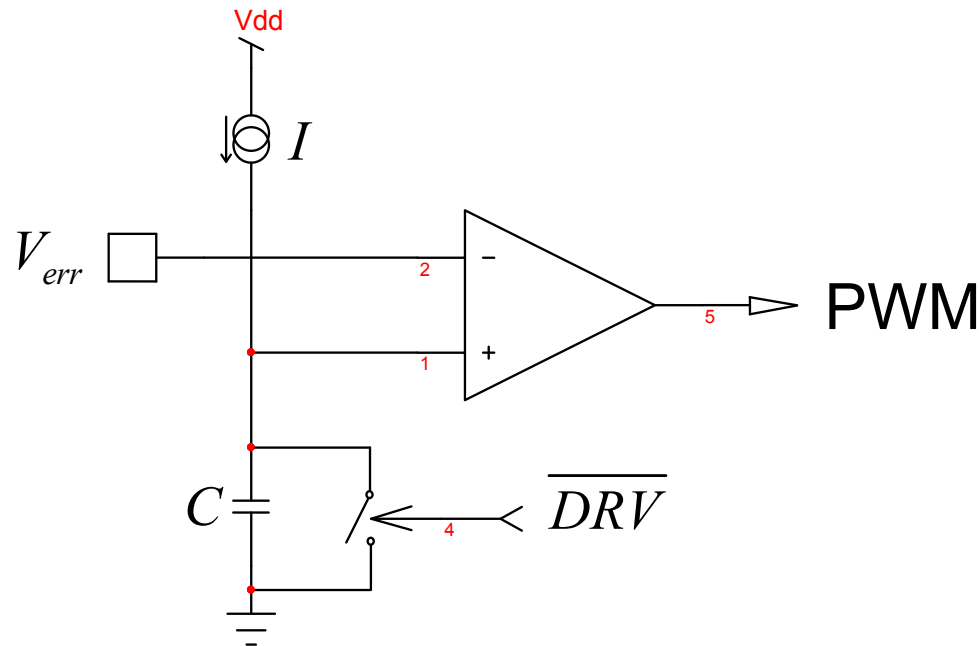- The on time modulator works as a PWM block



$$t_{on}(V_{err}) = \frac{V_{err} C}{I}$$


$$\downarrow$$

$$\frac{d}{dV_{err}} t_{on}(V_{err}) = \frac{C}{I}$$

- The modulator small-signal gain is a simple coefficient

$$\left. \begin{array}{l} C = 100 \text{ pF} \\ I = 20 \mu\text{A} \end{array} \right\} \frac{C}{I} = 5 \mu$$

Assuming 1 V = 1 μs

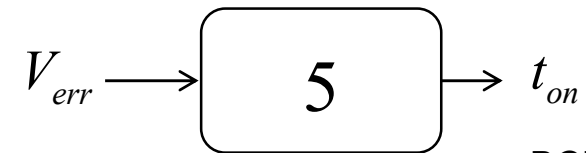


BCM VM



Final PWM Switch Model in BCM

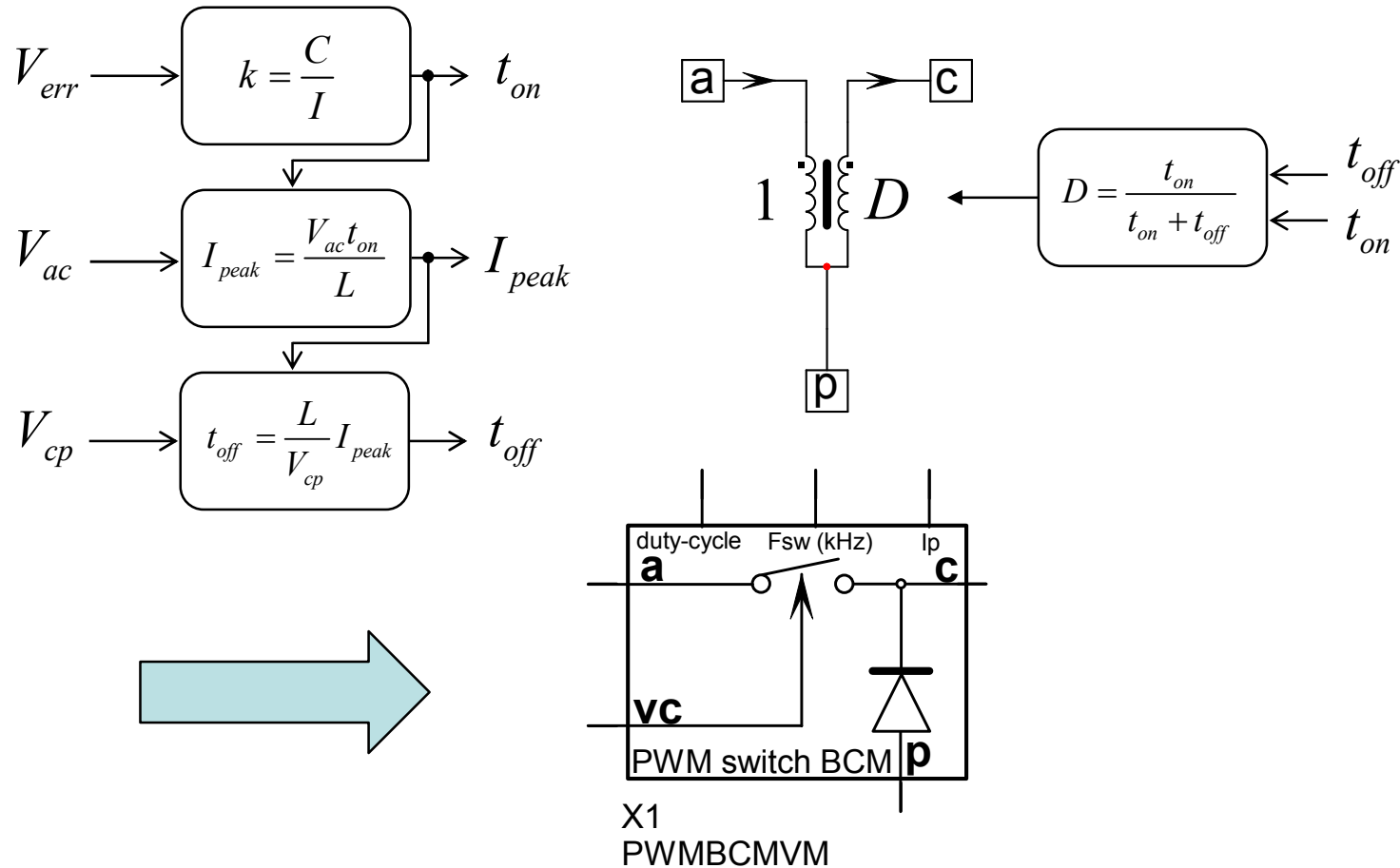□ Just add the on-time modulator to the VM PWM switch



C. Basso, "Switch Mode Power Supplies: SPICE Simulations and Practical Design", McGraw-Hill 2008

BCM VM




Course Agenda

- ❑ Introducing the PWM Switch Model
- ❑ CCM, DCM and BCM in Voltage Mode
- ❑ **Pulse Width Modulator Gain**
- ❑ The PWM Switch Model in Current Mode
- ❑ PWM Switch at Work in a Buck Converter
- ❑ A Simplified Approach to Modeling a DCM Boost
- ❑ Transfer Function of a BCM Boost in Current Mode
- ❑ Small-Signal Model of The Active Clamp Forward




What About the PWM Block?

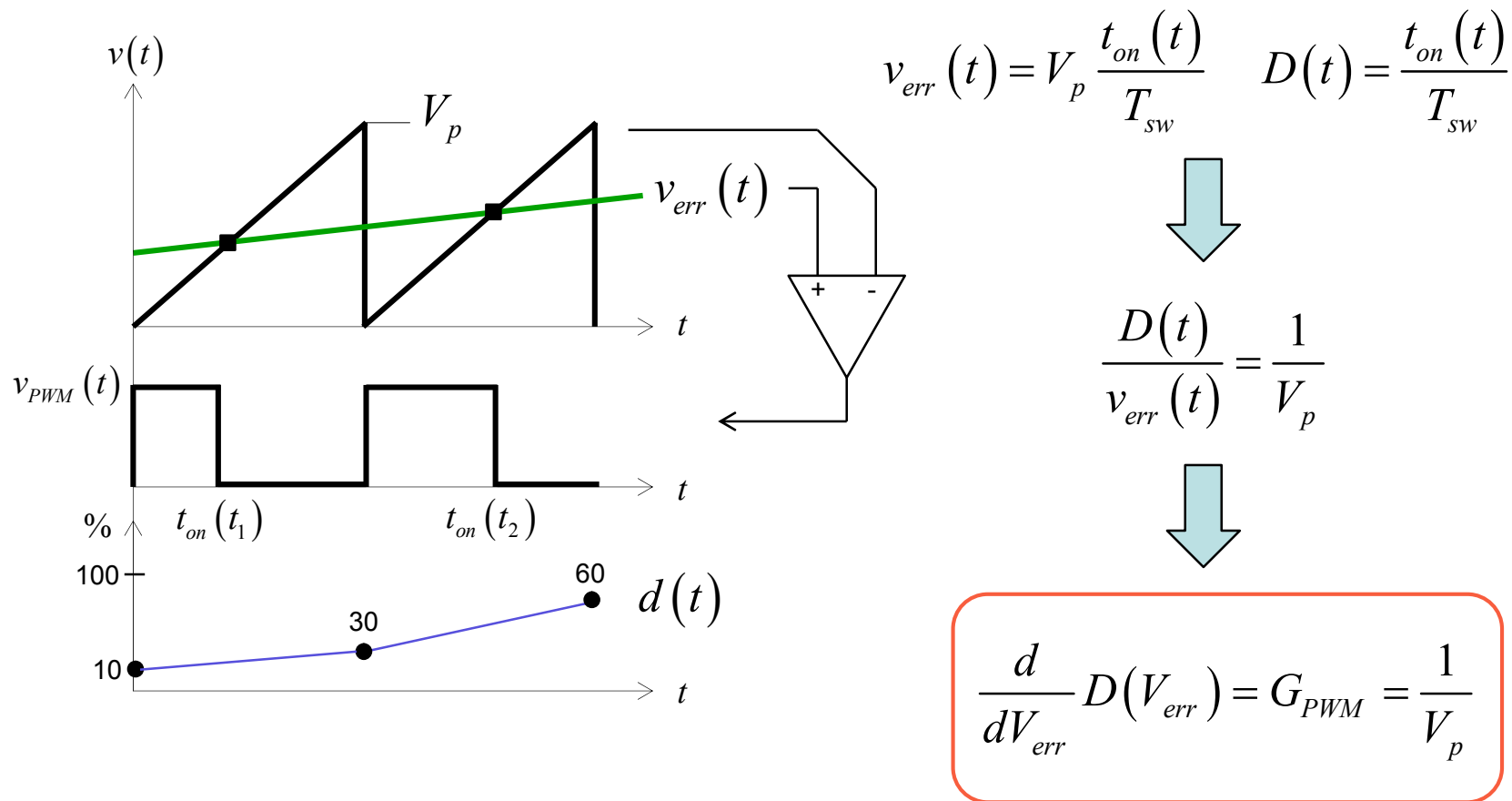□ In voltage mode, the duty ratio depends on V_{err}




Including the PWM Contribution

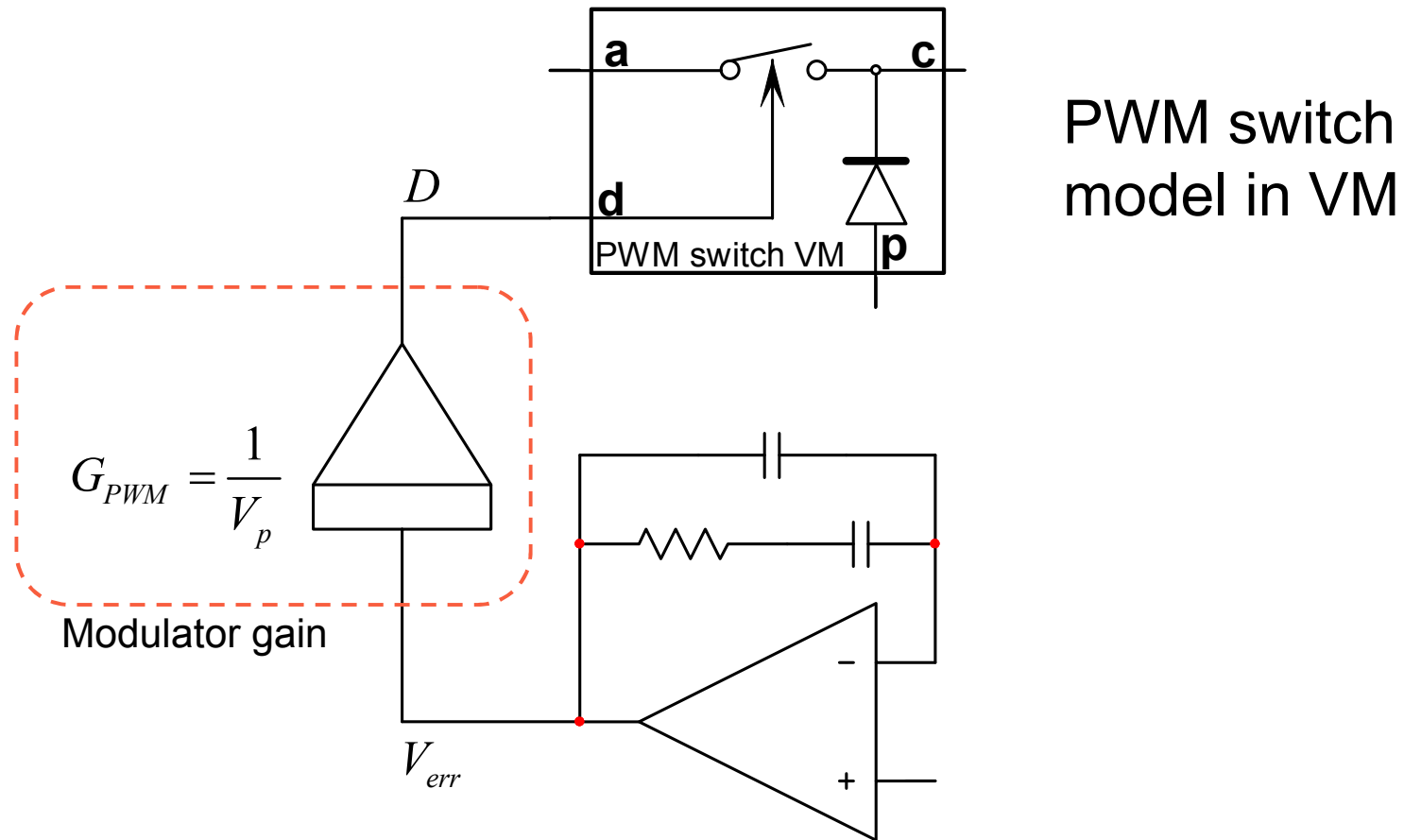- In a simulation fixture, insert a gain block after V_{err}



Considering Feedforward

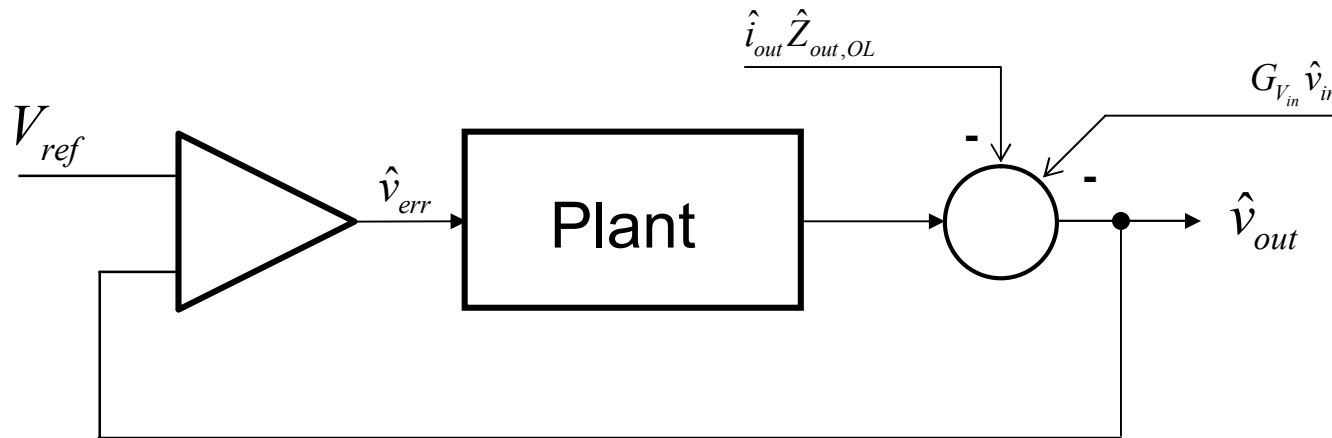- ❑ A perturbation disturbs operations and must be fought
- ❑ In a power supply, the input voltage is a perturbation



- ❑ The perturbation must affect the output to trigger action
 - Why not reacting before perturbation reaches the output?
 - ✓ This is the principle of feedforward

Input Contribution in a Buck Converter

- The transfer function of a CCM buck converter includes V_{in}

$$H(s) = \frac{V_{in}}{V_p} \frac{1 + \frac{s}{s_{z_1}}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

- Let's make V_p a function of V_{in} : $V_p(V_{in}) = k_{FF} V_{in}$


→
$$H(s) = \frac{V_{in}}{k_{FF} V_{in}} \frac{1 + \frac{s}{s_{z_1}}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2} = \frac{1}{k_{FF}} \frac{1 + \frac{s}{s_{z_1}}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

- The transfer function no longer depends on V_{in}



How to Make V_p a Function of V_{in} ?

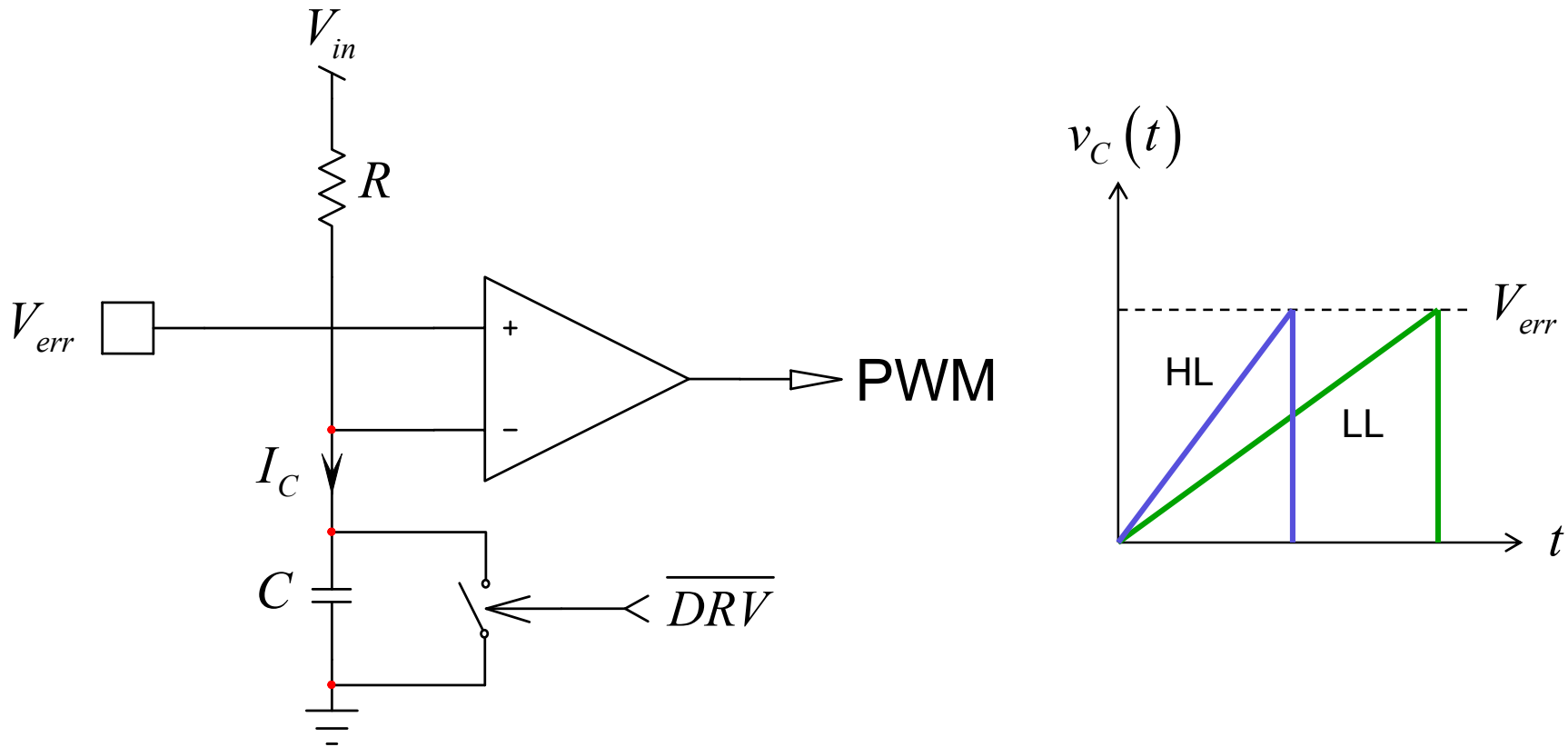- Make the sawtooth capacitor current depend on V_{in}



HL = hi line
LL = lo line



Ramp Amplitude and Input Voltage

- We can neglect the sawtooth ramp amplitude

$$I_C \approx \frac{V_{in}}{R}$$

- The peak value, V_p , is linked to the time constant τ

$$V_p = \frac{I_C}{C_{ramp}} T_{sw} = \frac{V_{in}}{C_{ramp} R_{ramp}} T_{sw} = \frac{V_{in}}{\tau F_{sw}}$$

- In the time domain, the peak value will change

$$v_{ramp}(t) = V_p \frac{t}{T_{sw}} = \frac{V_{in}}{\tau F_{sw}} \frac{t}{T_{sw}}$$

- At $t = t_{on}$, the error voltage equals V_{ramp}

$$V_{err} = \frac{V_{in}}{\tau F_{sw}} \frac{t_{on}}{T_{sw}} = \frac{V_{in}}{\tau F_{sw}} D \quad \longrightarrow \quad D(V_{err}) = V_{err} \frac{\tau F_{sw}}{V_{in}}$$




An In-Line Equation to Include Feedforward

- Differentiate the expression to get the small-signal gain

$$G_{PWM} = \frac{\partial D(V_{err})}{\partial V_{err}} = \frac{\tau F_{sw}}{V_{in}} = \frac{1}{k_{FF} V_{in}} \quad \Rightarrow \quad k_{FF} = \frac{1}{F_{sw} \tau}$$

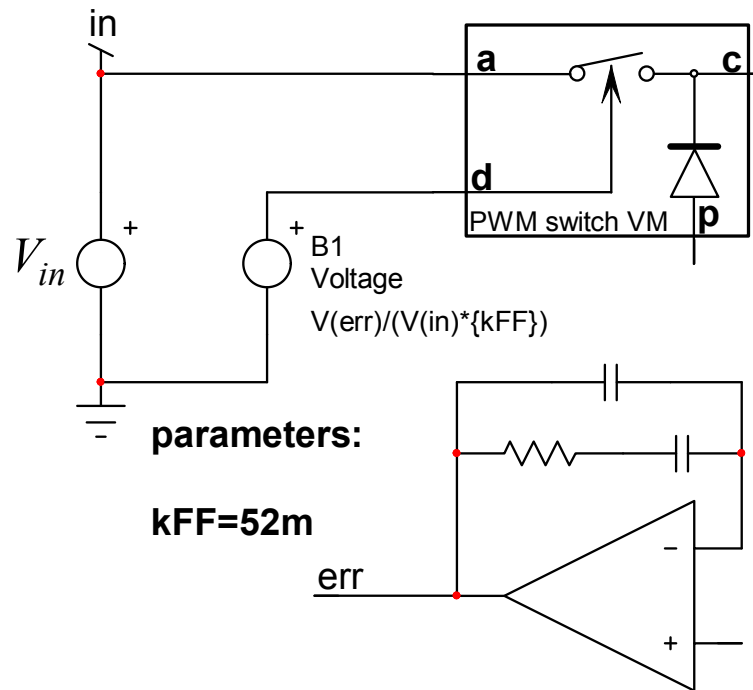- The feedforward block requires an ABM source



$$R = 82 \text{ k}\Omega$$

$$C = 470 \text{ pF}$$

$$F_{sw} = 500 \text{ kHz}$$

$$k_{FF} = \frac{1}{500k \times 470p \times 82k} = 52m$$

ABM: Analog Behavioral Model


Course Agenda

- Introducing the PWM Switch Model
- CCM, DCM and BCM in Voltage Mode
- Pulse Width Modulator Gain
- **The PWM Switch Model in Current Mode**
- PWM Switch at Work in a Buck Converter
- A Simplified Approach to Modeling a DCM Boost
- Transfer Function of a BCM Boost in Current Mode
- Small-Signal Model of The Active Clamp Forward



Peak Current Mode Control

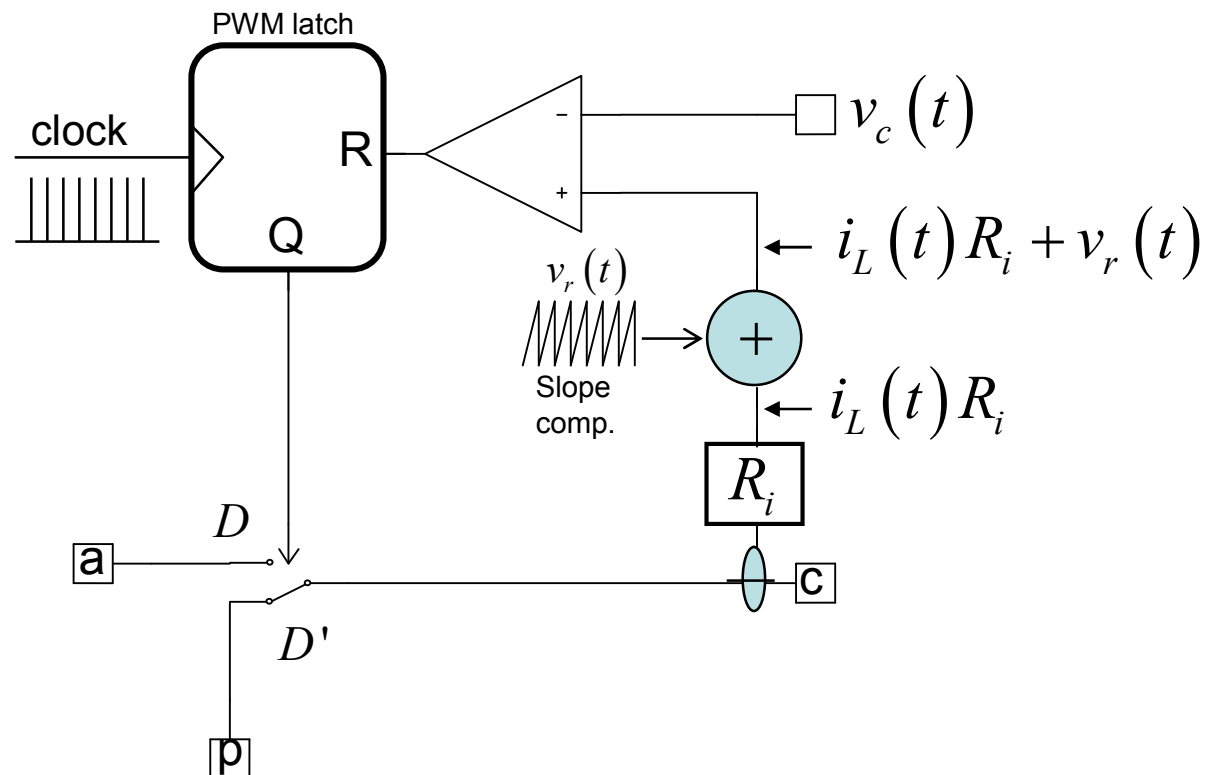
- ❑ In voltage-mode, the loop controls the duty ratio
- ❑ In current-mode, the inductor peak current is controlled



- ❑ An artificial ramp is added for stabilization purposes

We Want the Average Current Definition

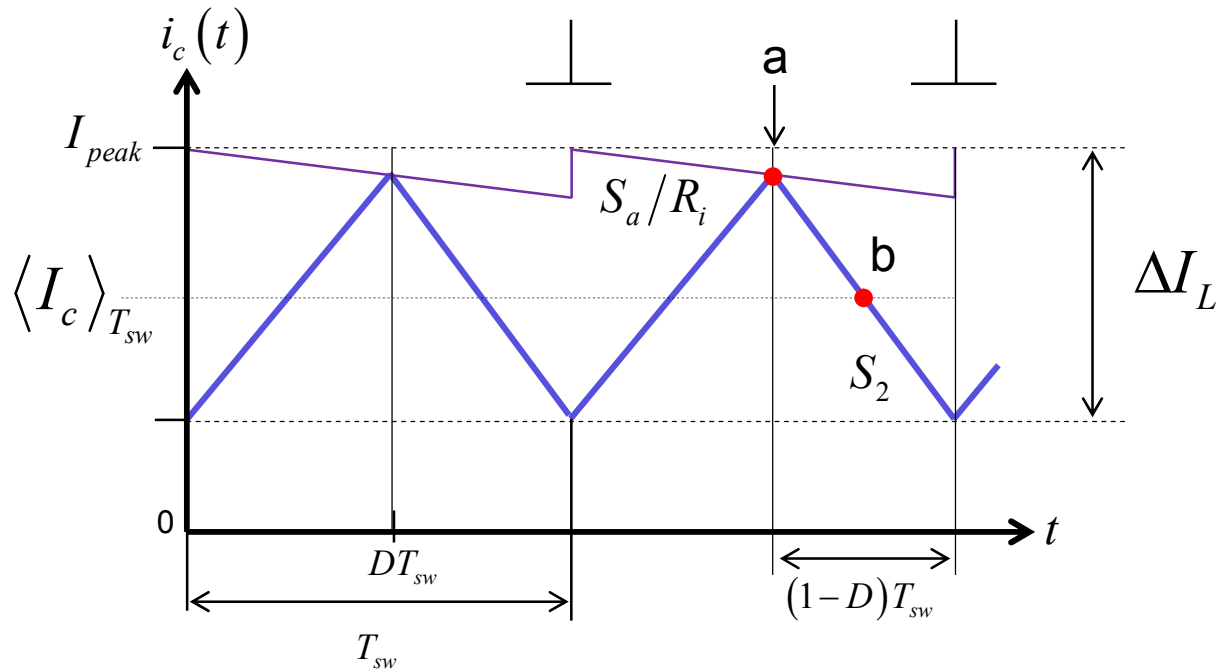- The value I_c is the inductor current at half the ripple



- Current at point **b** is that of **a** minus half the inductor ripple


$$\langle I_c \rangle_{T_{sw}} = \frac{V_c}{R_i} - \frac{S_a}{R_i} DT_{sw} - \frac{S_2 D' T_{sw}}{2}$$

CCM CM



Define the Converter off-Slope

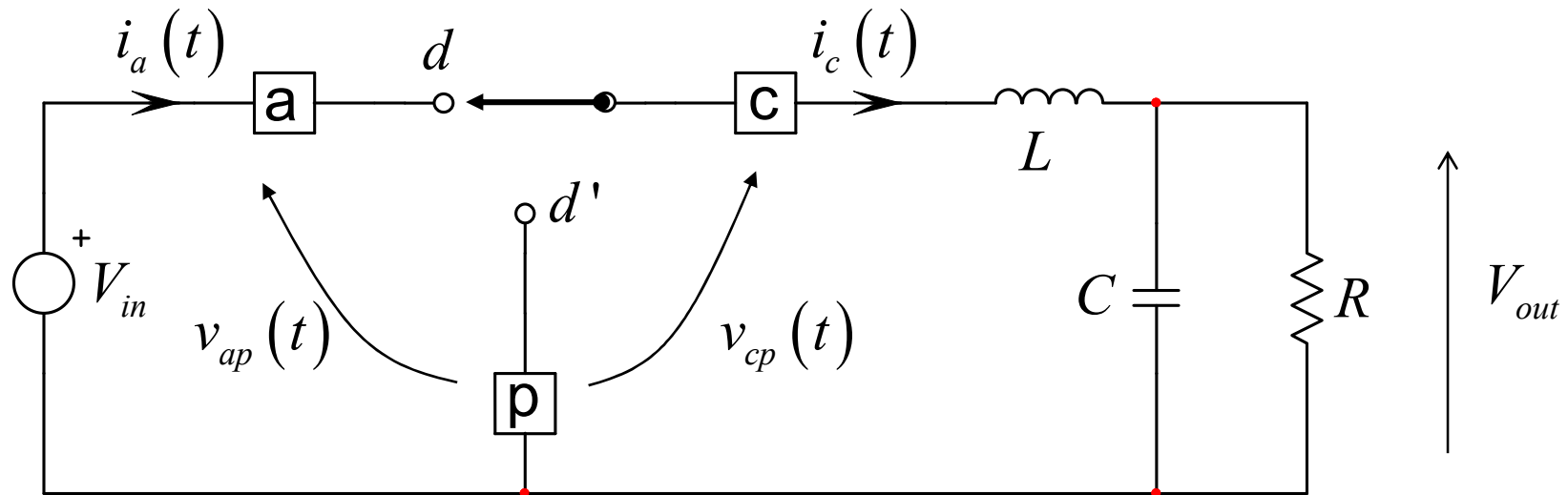- Use a buck configuration to see voltages at play



- The downslope depends on the output voltage V_{out} :

$$S_2 = -\frac{V_{out}}{L}$$

- The inductor average voltage is 0 at steady-state

$$V_{cp} = V_{out} \longrightarrow S_2 = -\frac{V_{cp}}{L}$$

CCM CM




A Current Mode Generator

- Update the previous equation to obtain final definition

$$I_c = \frac{V_c}{R_i} - V_{cp} (1-D) \frac{T_{sw}}{2L} - \frac{S_a}{R_i} DT_{sw} \quad \xrightarrow{\text{Group 2nd and 3rd terms}} \quad I_\mu = V_{cp} (1-D) \frac{T_{sw}}{2L} + \frac{S_a}{R_i} DT_{sw}$$

Peak current setpoint
Half inductor ripple
Compensation ramp

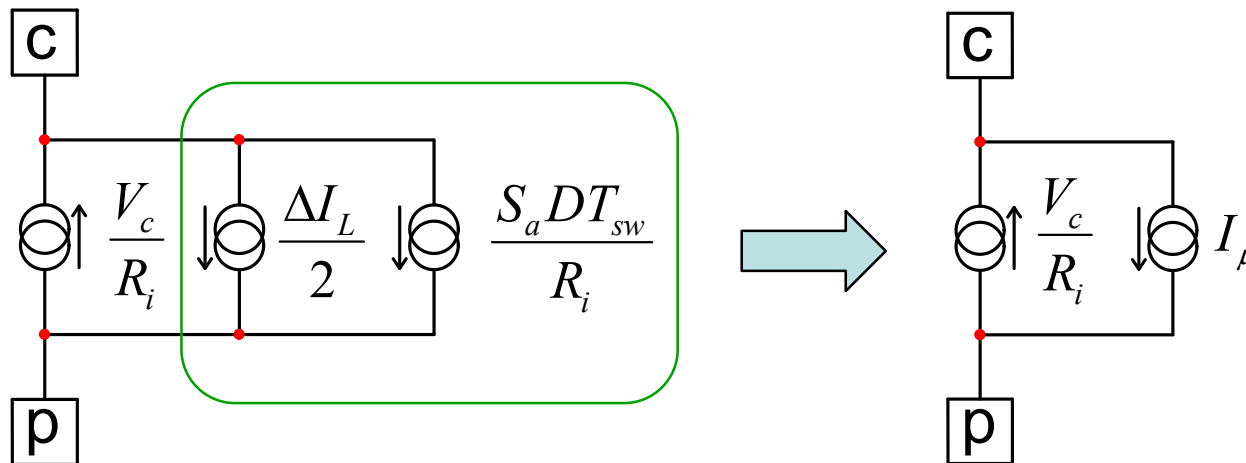- Inductor ripple and compensation ramp alter peak value




CCM CM



CM or VM Lead to Similar Input Currents

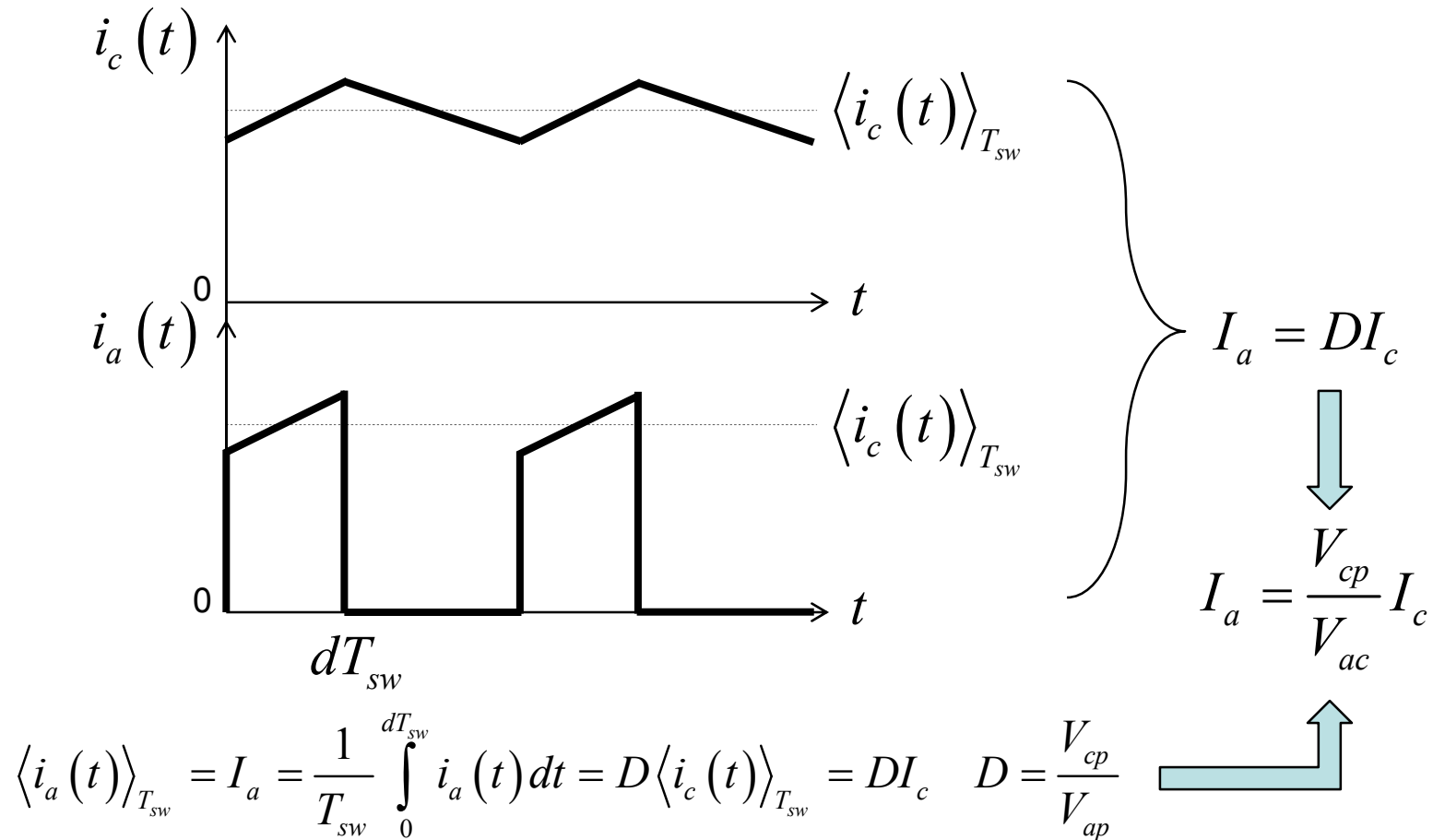- Average the current waveforms across the PWM switch




CCM CM



The PWM Switch Model in Current Mode

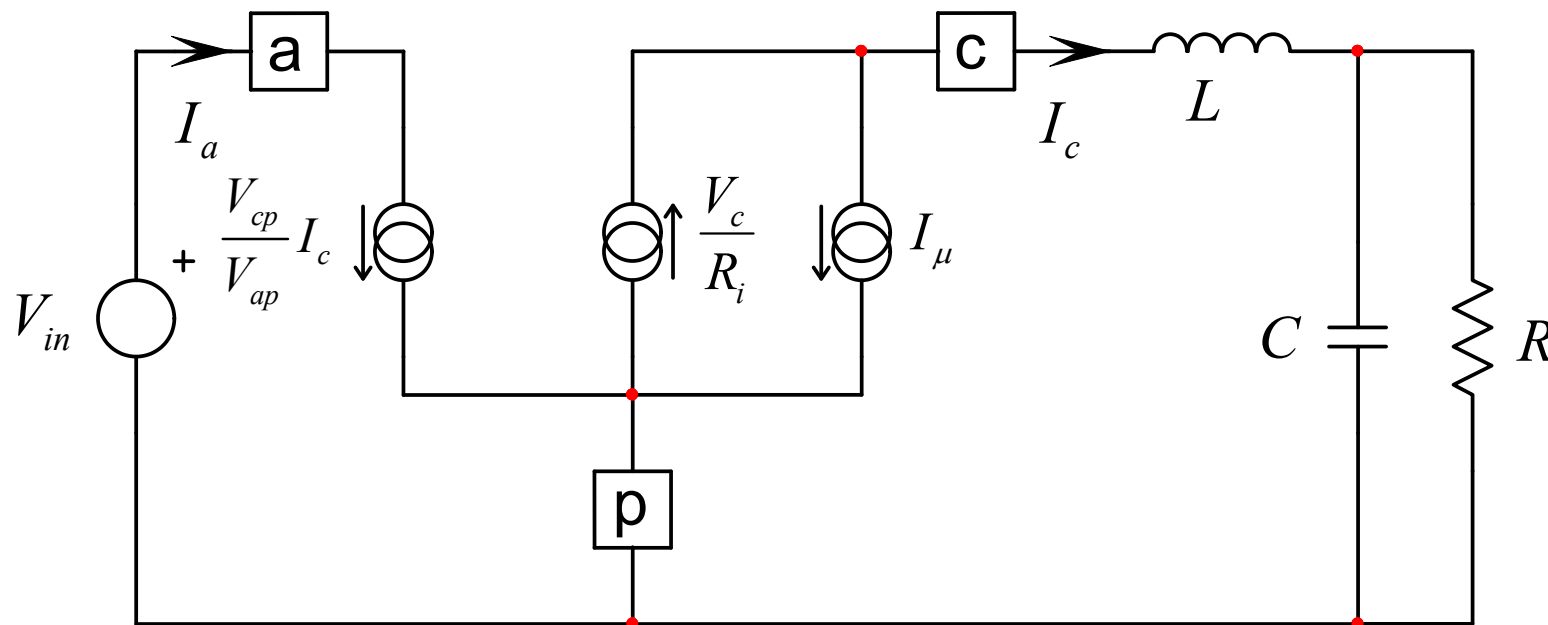- The final model associates three current sources




- This is the large-signal current-mode PWM switch model

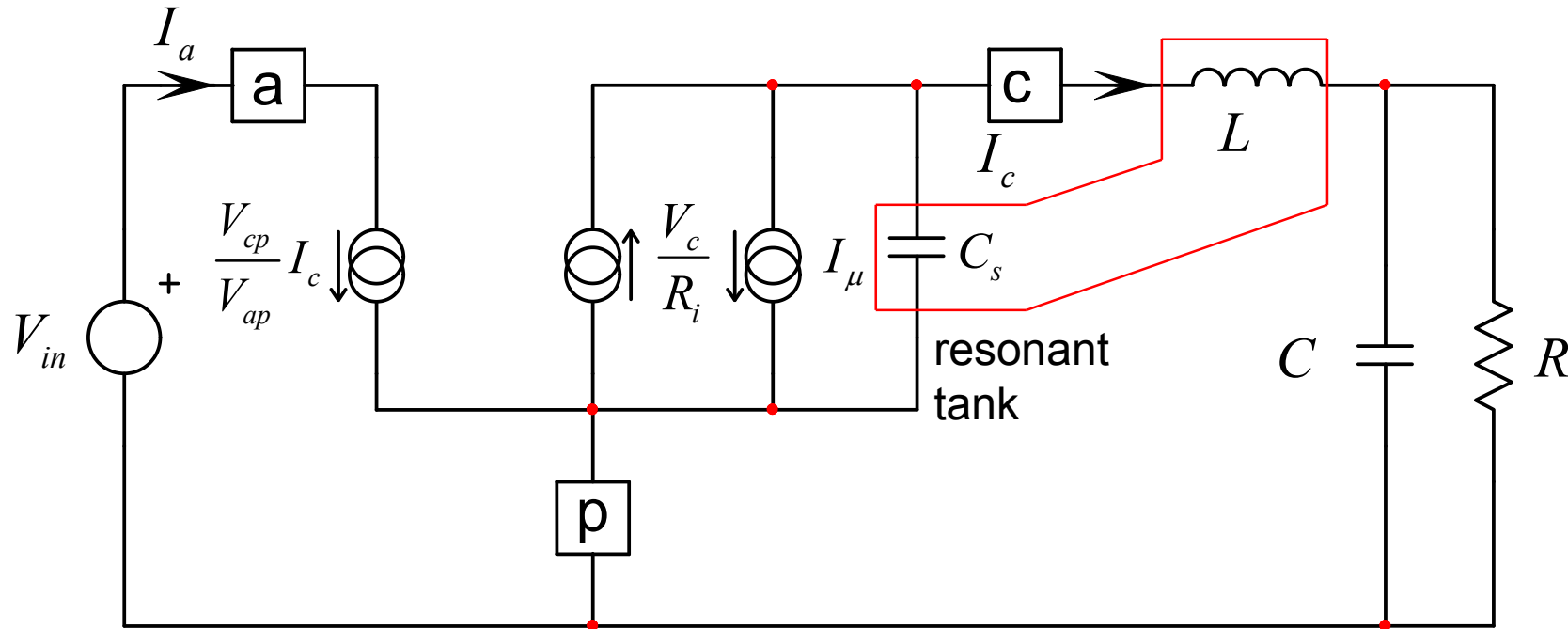V. Vorpérian, "Analysis of Current-Controlled PWM Converters using the Model of the PWM Switch", PCIM Conference, 1990

Final Model Includes Subharmonic Effects

- A simple capacitor is enough to mimic instability




- As the instability is placed at half the switching frequency:

$$\frac{F_{sw}}{2} = \frac{1}{2\pi\sqrt{LC_s}} \quad \Rightarrow \quad C_s = \frac{1}{L(F_{sw}\pi)^2}$$

CCM CM

The PWM Switch in DCM

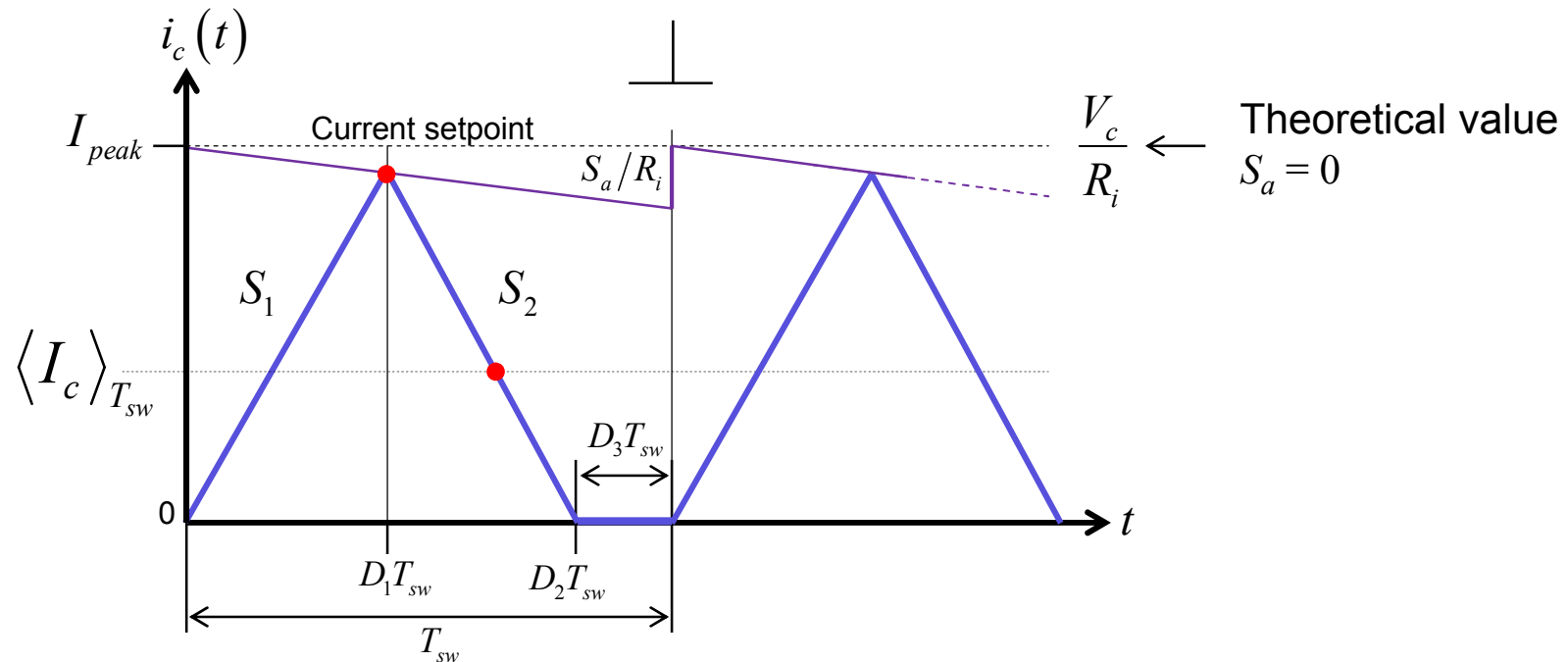- The PWM CM can work in discontinuous mode



- The average current I_c is somewhere in the downslope S_2


$$I_{peak} = \frac{V_c - D_1 T_{sw} S_a}{R_i} \longrightarrow I_c = \frac{V_c - D_1 T_{sw} S_a}{R_i} - \alpha D_2 T_{sw} S_2$$

DCM CM



Derive the Inductor Average Current

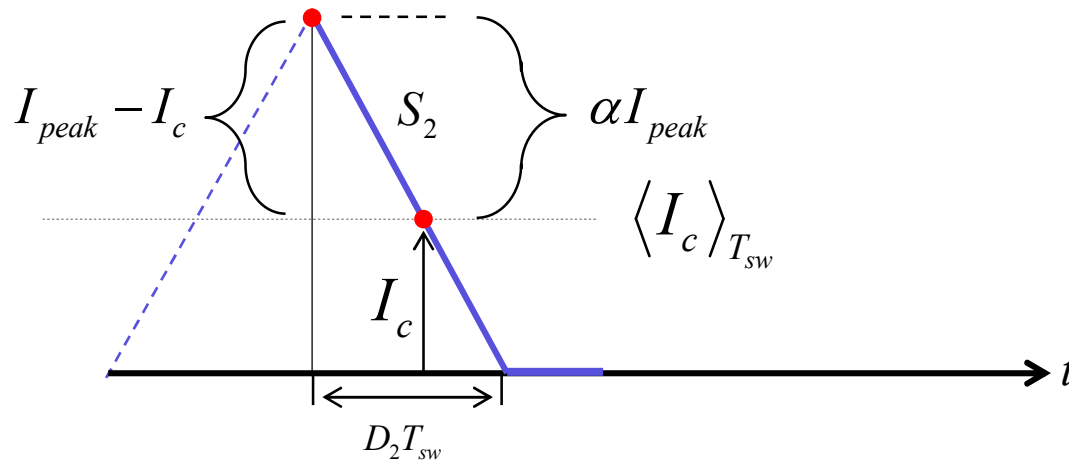- We must now obtain the value of α to get I_c



- I_c is the area under the triangle divided by the switching period

$$I_c = \frac{I_{peak} D_1}{2} + \frac{I_{peak} D_2}{2} = I_{peak} \frac{D_1 + D_2}{2}$$

$$\alpha I_{peak} = I_{peak} - I_{peak} \frac{D_1 + D_2}{2}$$

$$\alpha = 1 - \frac{D_1 + D_2}{2}$$

DCM CM




Adopt the CCM Structure for DCM

- Substitute and rearrange to get the inductor current

$$I_c = \frac{V_c}{R_i} - \frac{D_1 T_{sw} S_a}{R_i} - D_2 T_{sw} \frac{V_{cp}}{L} \left(1 - \frac{D_1 + D_2}{2} \right)$$

- If we stick to the original CCM architecture
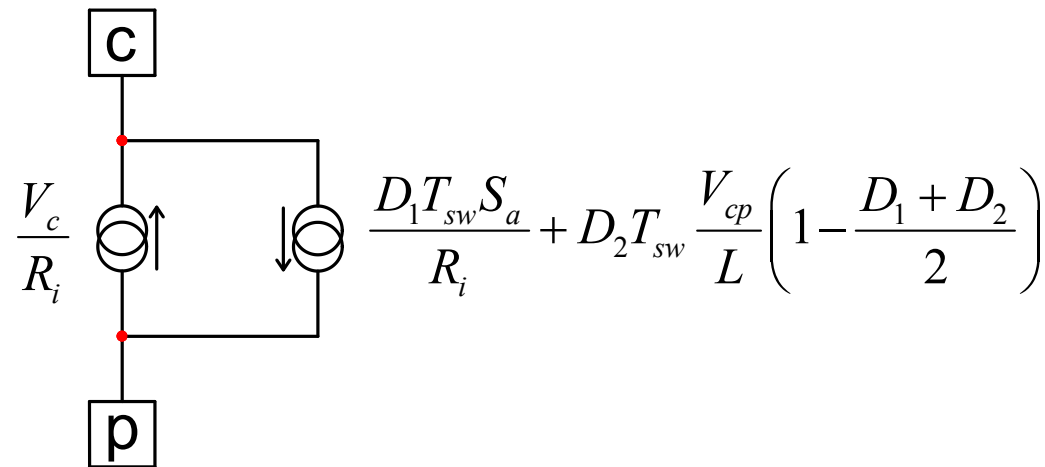
$$I_c = \frac{V_c}{R_i} - I_\mu \quad \text{with} \quad I_\mu = \frac{D_1 T_{sw} S_a}{R_i} + D_2 T_{sw} \frac{V_{cp}}{L} \left(1 - \frac{D_1 + D_2}{2} \right)$$




DCM CM



Discontinuous Waveforms

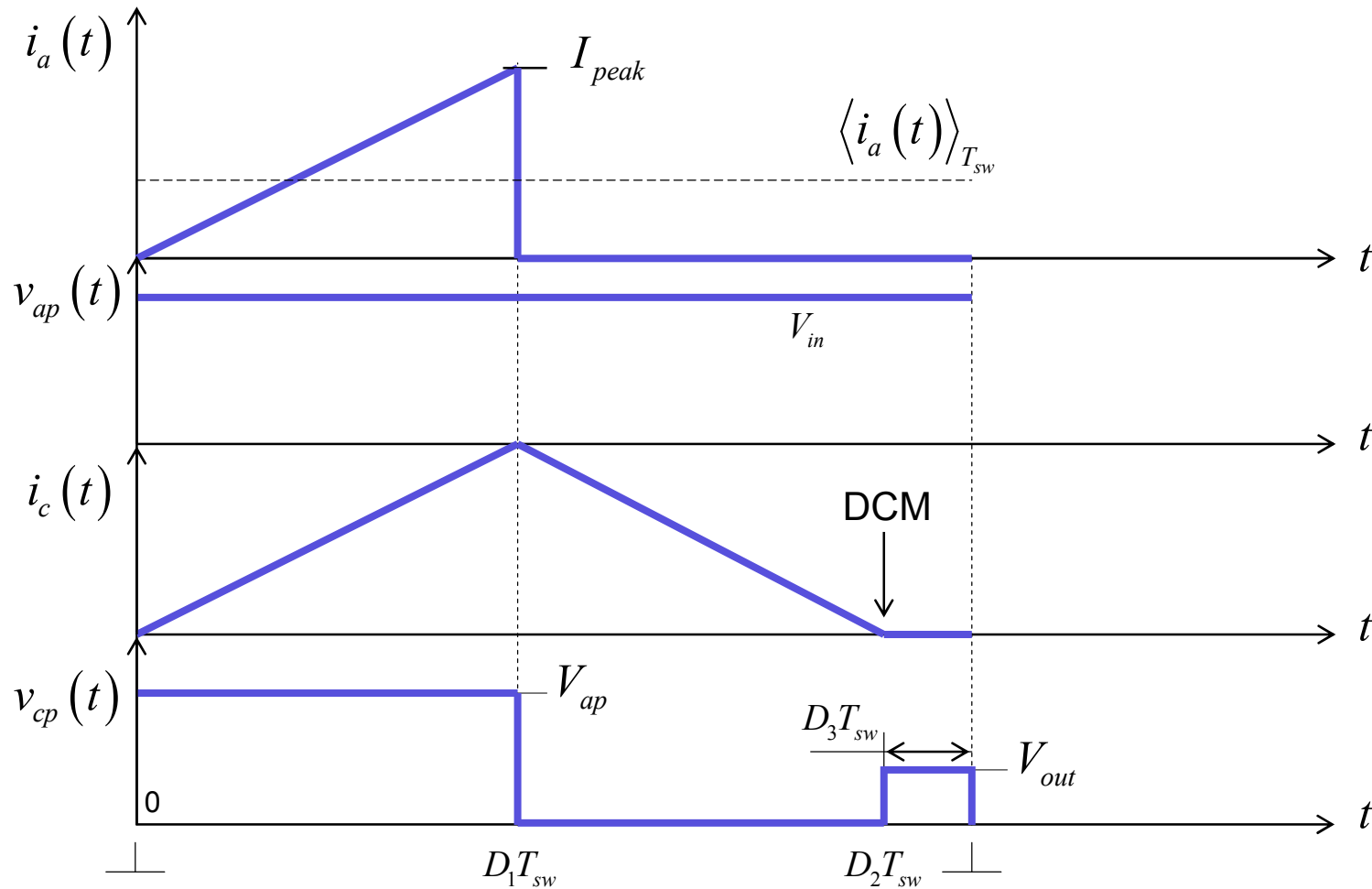□ Let's have a look at the PWM switch voltages in DCM



DCM CM



Derive the Duty Ratios

- From the DCM voltage-mode PWM switch we have:

$$V_{cp} = V_{ap} \frac{D_1}{D_1 + D_2} \longrightarrow D_1 = \frac{D_2 V_{cp}}{V_{ap} - V_{cp}}$$

- From the operating DCM waveforms

$$I_a = \frac{I_{peak} D_1}{2} \longrightarrow I_{peak} = \frac{2I_a}{D_1} \longrightarrow I_c = I_{peak} \frac{D_1 + D_2}{2} \longrightarrow I_a = I_c \frac{D_1}{D_1 + D_2}$$

- Almost there, just need to express D_2

$$I_{peak} = \frac{V_{ac}}{L} D_1 T_{sw} \quad \text{and} \quad I_{peak} = \frac{2I_c}{D_1 + D_2}$$


$$\left. \begin{array}{l} \frac{V_{ac}}{L} D_1 T_{sw} = \frac{2I_c}{D_1 + D_2} \\ I_{peak} = \frac{2I_c}{D_1 + D_2} \end{array} \right\} D_2 = \frac{2LF_{sw}}{D_1} \frac{I_c}{V_{ac}} - D_1$$

DCM CM



The DCM Model is Complete!

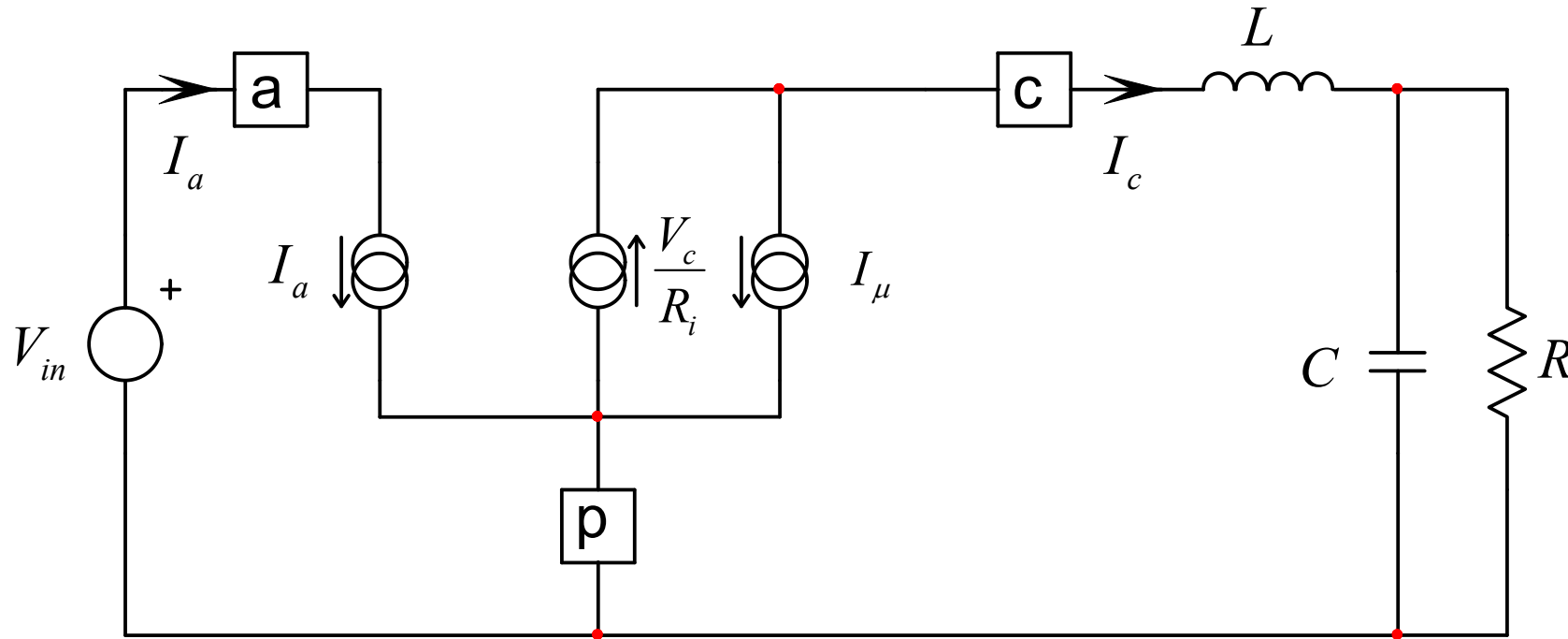- We can use this model for DCM simulations



$$I_a = I_c \frac{D_1}{D_1 + D_2}$$

$$I_\mu = \frac{D_1 T_{sw} S_a}{R_i} + D_2 T_{sw} \frac{V_{cp}}{L} \left(1 - \frac{D_1 + D_2}{2} \right)$$

DCM CM




Current Mode Borderline

- In CM, the error voltage sets the peak current

$$I_{peak} = \frac{V_c}{R_i}$$

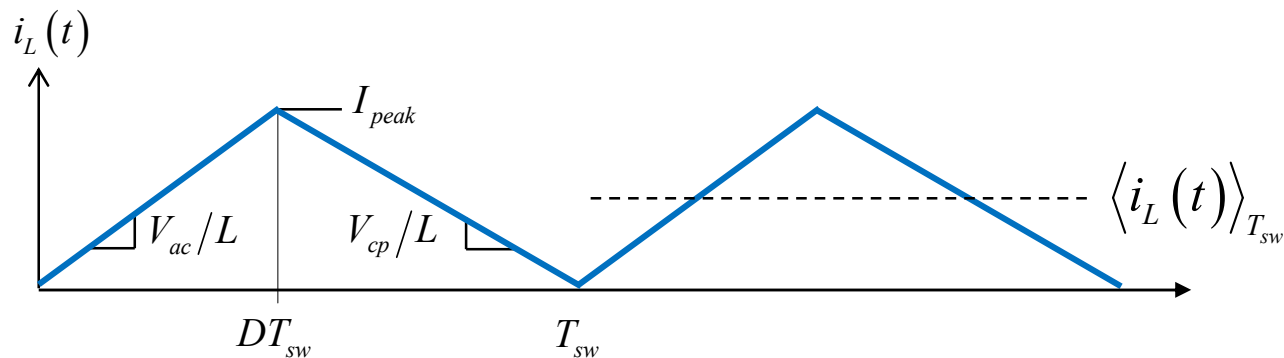- The peak current also depends on duty ratio D



$$I_{peak} = \frac{V_{ac}}{L} DT_{sw} \quad \Rightarrow \quad D = \frac{V_c}{R_i} \frac{L}{V_{ac} T_{sw}} \quad \Rightarrow \quad t_{on} = \frac{V_c}{R_i} \frac{L}{V_{ac}}$$

BCM CM



Operating Points of BCM Current Mode

- ❑ The off-time duration depends on I_{peak} too

$$I_{peak} = \frac{V_{cp}}{L}(1-D)T_{sw} \longrightarrow t_{off} = \frac{V_{err}}{R_i} \frac{L}{V_{cp}}$$

- ❑ Switching frequency comes easily

$$T_{sw} = t_{on} + t_{off} = \frac{V_c L}{R_i} \left(\frac{1}{V_{ap}} + \frac{1}{V_{cp}} \right)$$

- ❑ The average inductor current I_c is straightforward

$$I_c = \frac{I_{peak}}{2} = \frac{V_c}{2R_i}$$

- ❑ The relationship between I_a and I_c is always the same


$$I_a = DI_c$$

BCM CM



This Completes the BCM CM Model

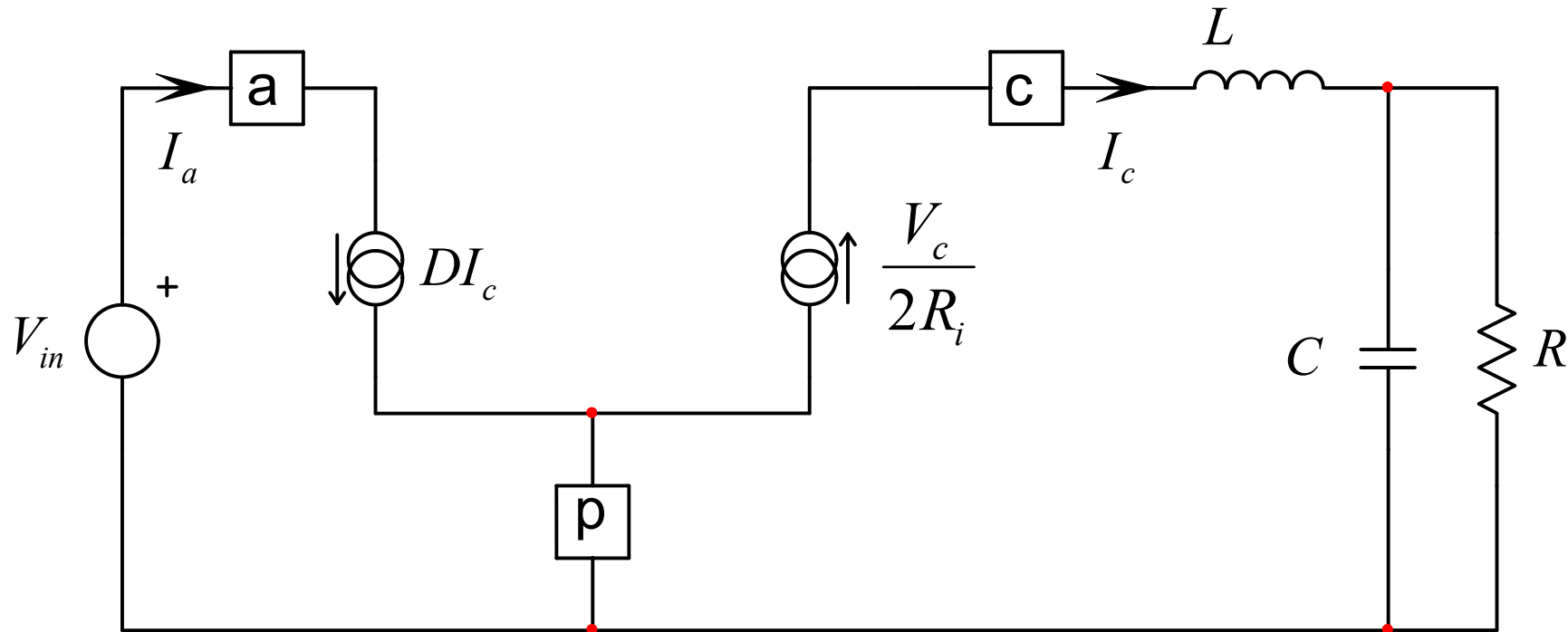- The model is really simple, two current sources



- Other ABM sources will compute D and T_{sw}

BCM CM




Course Agenda

- ❑ Introducing the PWM Switch Model
- ❑ CCM, DCM and BCM in Voltage Mode
- ❑ Pulse Width Modulator Gain
- ❑ The PWM Switch Model in Current Mode
- ❑ **PWM Switch at Work in a Buck Converter**
- ❑ A Simplified Approach to Modeling a DCM Boost
- ❑ Transfer Function of a BCM Boost in Current Mode
- ❑ Small-Signal Model of The Active Clamp Forward



A Buck Converter in Current Mode

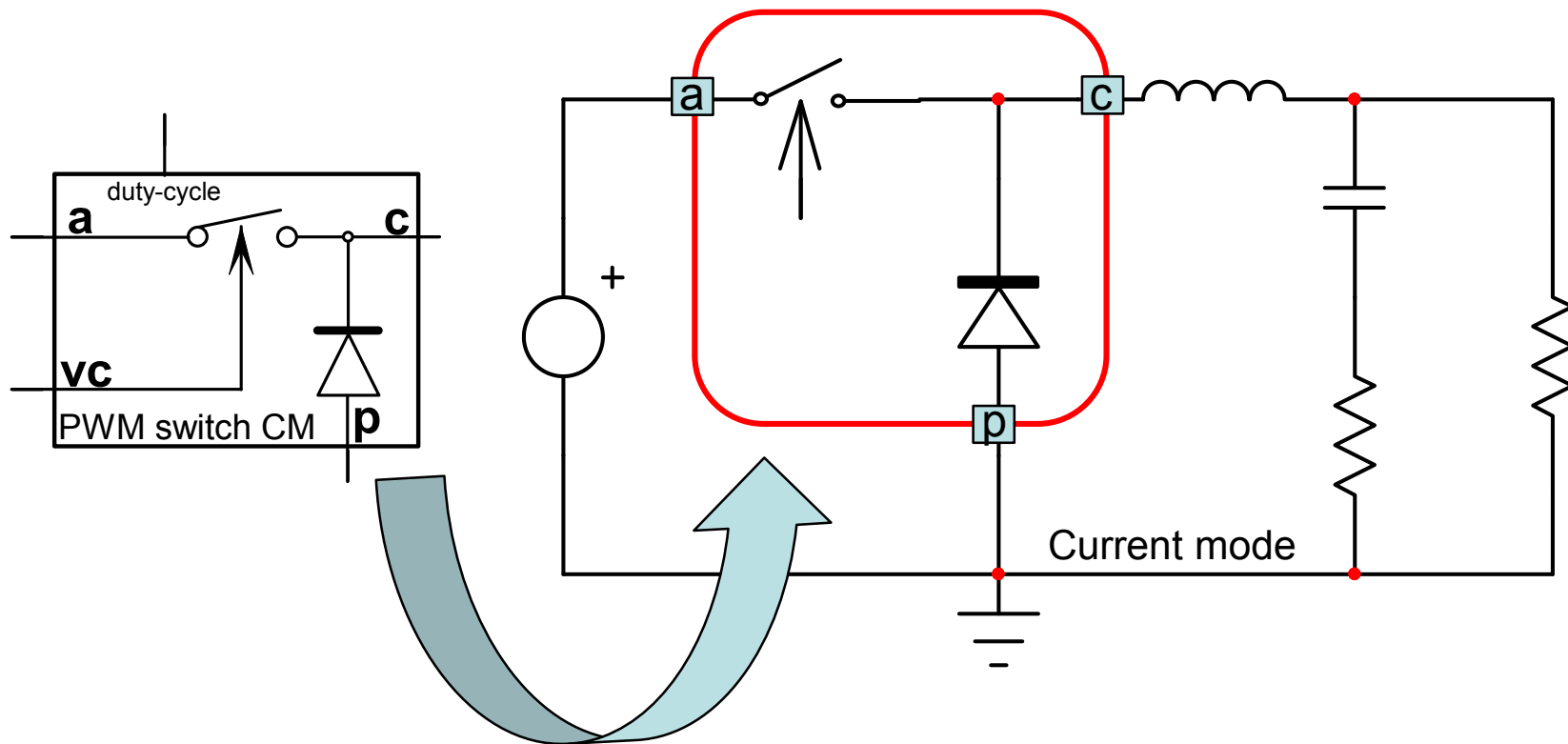
- Identify the diode and switch position in a buck CM



- Replace switches by the small-signal PWM switch model

A Small Signal Model

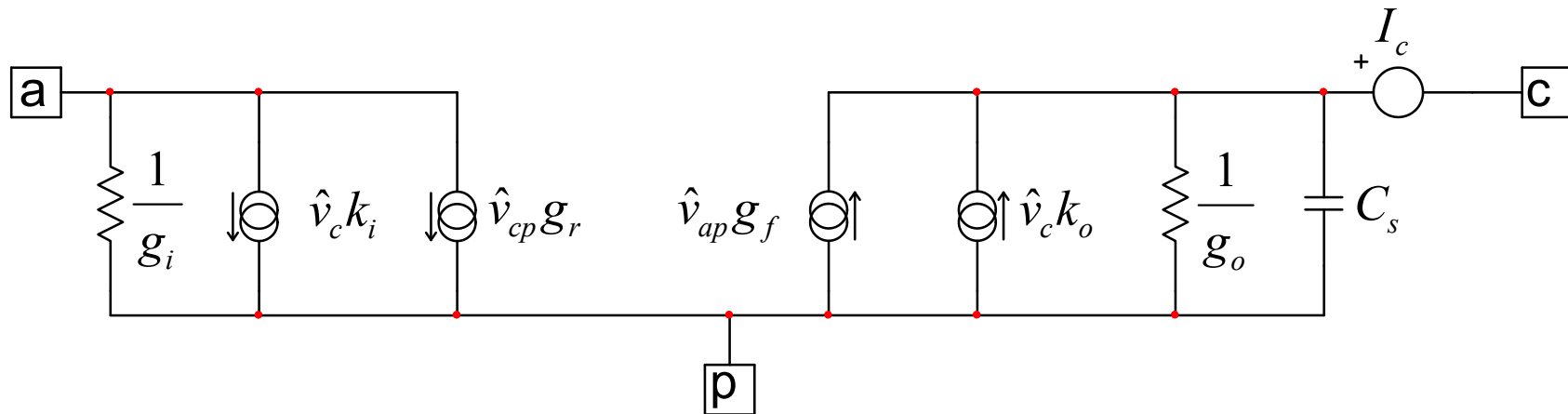- The model includes current sources and conductances



$$k_o = \frac{1}{R_i} \quad g_f = Dg_o - \frac{DD'T_{sw}}{2L} \quad g_o = \frac{T_{sw}}{L} \left(D' \frac{S_a}{S_n} + \frac{1}{2} - D \right)$$


$$k_i = \frac{D}{R_i} \quad g_i = D \left(g_f - \frac{I_c}{V_{ap}} \right) \quad g_r = \frac{I_c}{V_{ap}} - g_o D$$

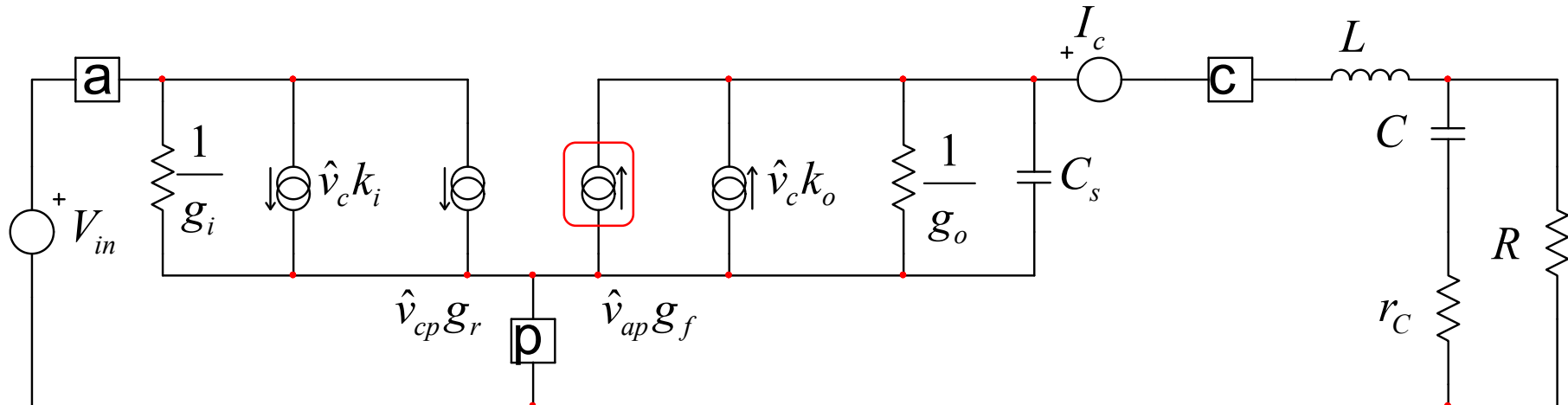V. Vorpérian, "Analysis of Current-Controlled PWM Converters using the Model of the PWM Switch", PCIM Conference, 1990



Plug the Model and Simplify

- Plug, simplify and rearrange: test in between!




- We want the control-to-output function, remove input stimulus

$$\hat{v}_{in} = 0 \longrightarrow \hat{v}_{ap} g_f = 0$$

- The input contribution can also disappear, no interest in Z_{in}

Time to Call FACTS!

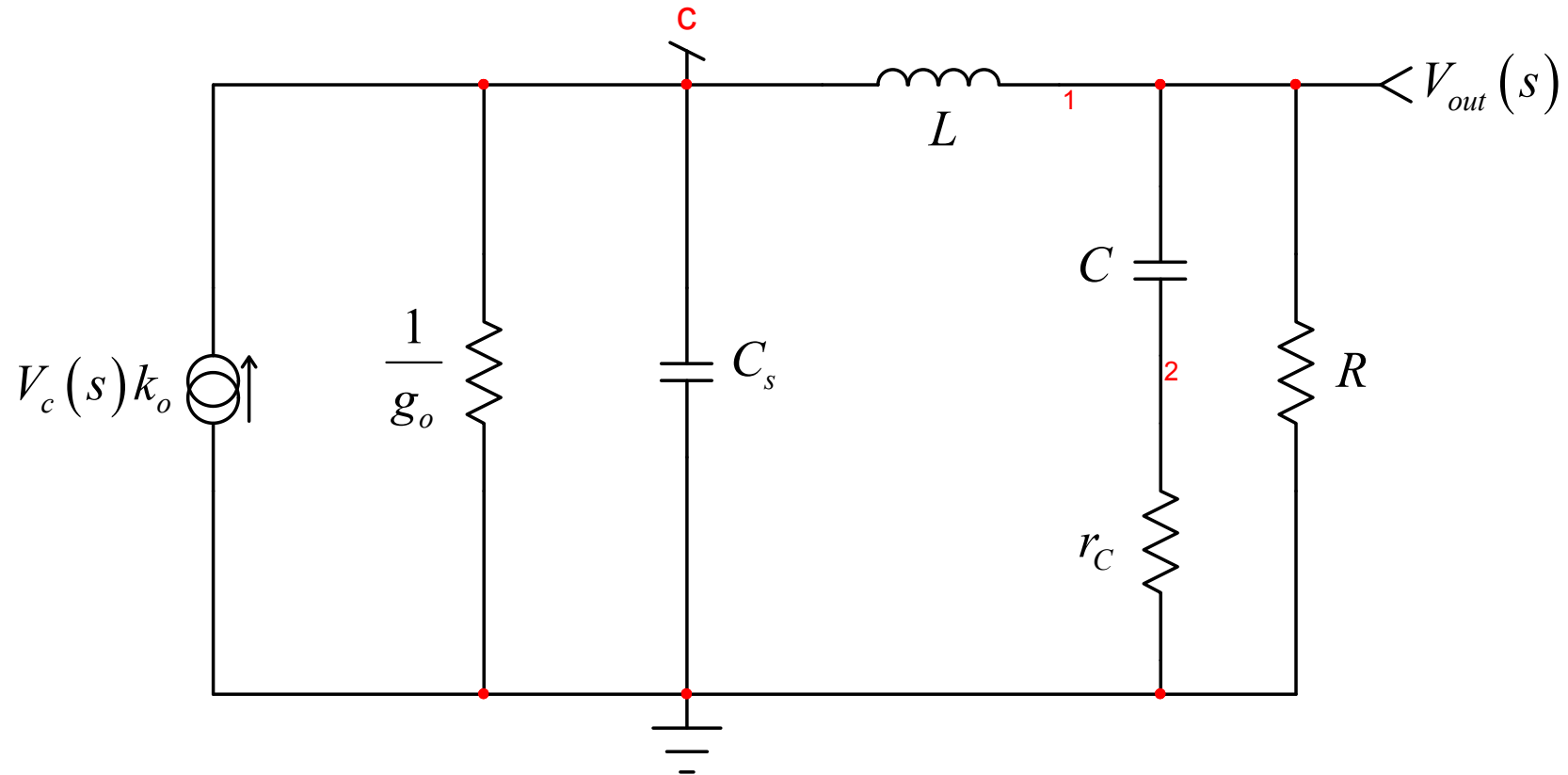- End-up with a simpler and less ugly sketch




- There are 3 storage elements: 3rd-order system

FACTS: Fast Analytical Circuit Techniques



Don't Use Brute-Force Algebra!

- ❑ You can use brute-force analysis...

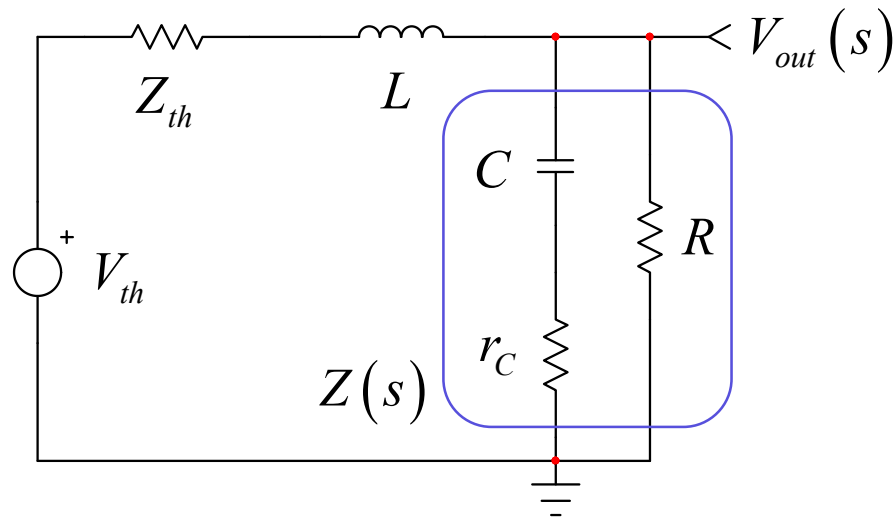

$$V_{th} = V_c(s) k_0 \left(\frac{1}{g_o} \parallel \frac{1}{sC_s} \right)$$



$$Z_{th} = \left(\frac{1}{g_o} \parallel \frac{1}{sC_s} \right)$$



- ❑ ...or consider FACTS to write a 3rd-order system TF

$$H(s) = H_0 \frac{N(s)}{D(s)} = H_0 \frac{N(s)}{1 + a_1s + a_2s^2 + a_3s^3}$$


Start with the Dc Gain

- Consider dc and high-frequency states for L and C

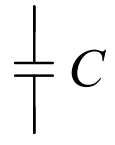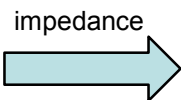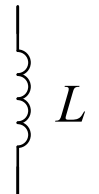 C		$Z_C = \frac{1}{sC}$	Dc state	$Z_C = \infty$	Cap. is an open circuit
			HF state	$Z_C = 0$	Cap. is a short circuit


 L		$Z_L = sL$	Dc state	$Z_L = 0$	Inductor is a short circuit
			HF state	$Z_L = \infty$	Inductor is an open circuit

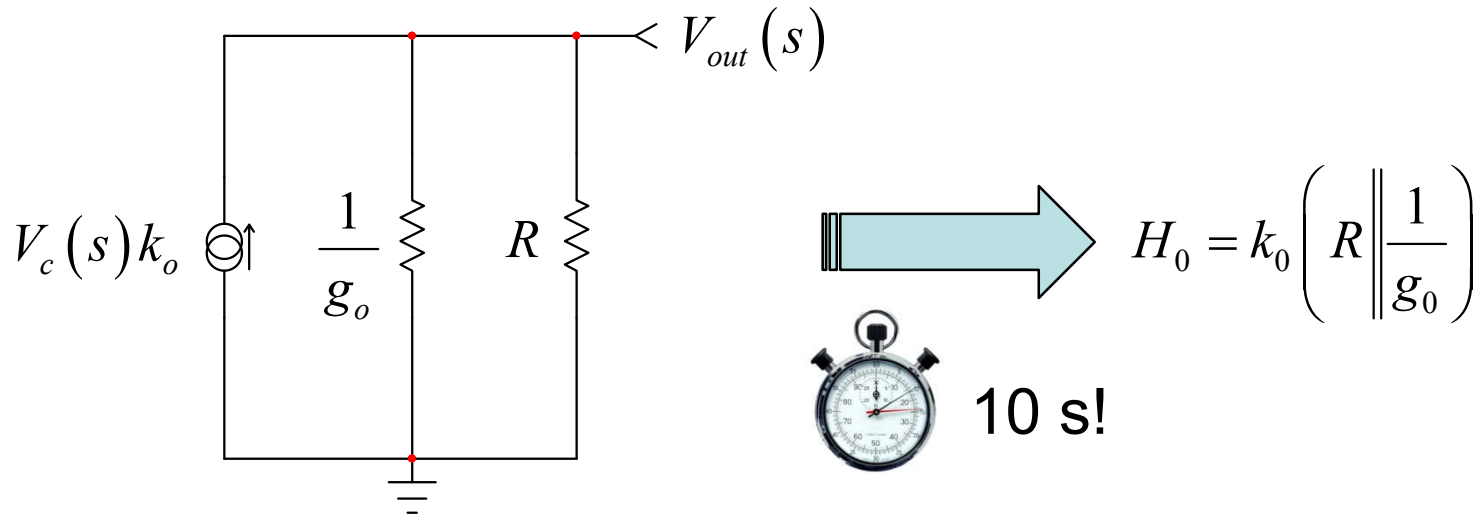- In the circuit, open capacitors and short inductors



Identify The Zeros

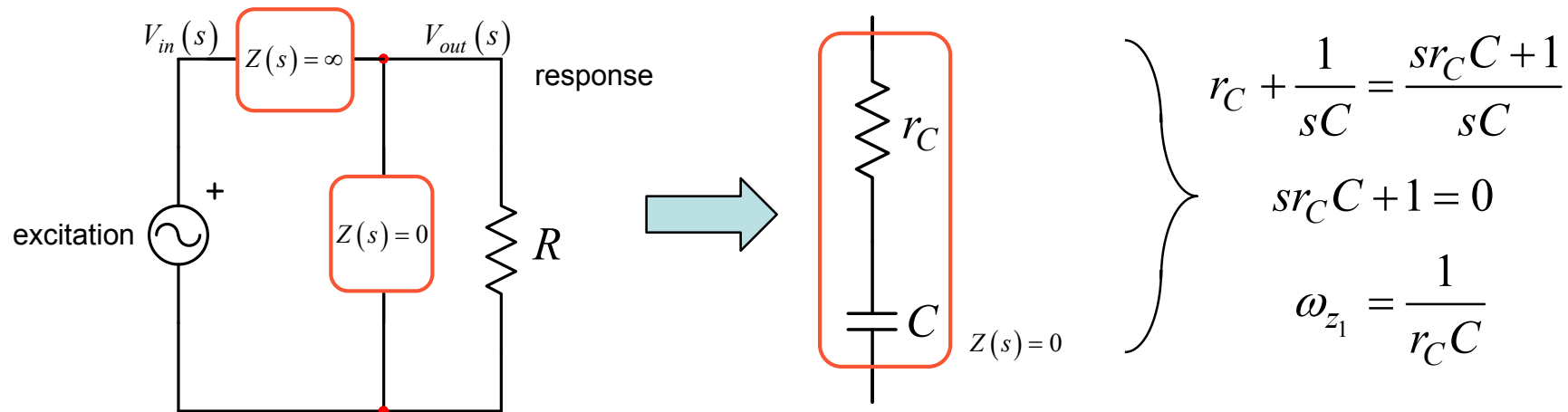- Zeros prevent the excitation from reaching the output




- We have the zero expression, half of the work is done


$$H(s) = H_0 \frac{1 + \frac{s}{s_{z_1}}}{1 + a_1 s + a_2 s^2 + a_3 s^3}$$

Finding the Poles

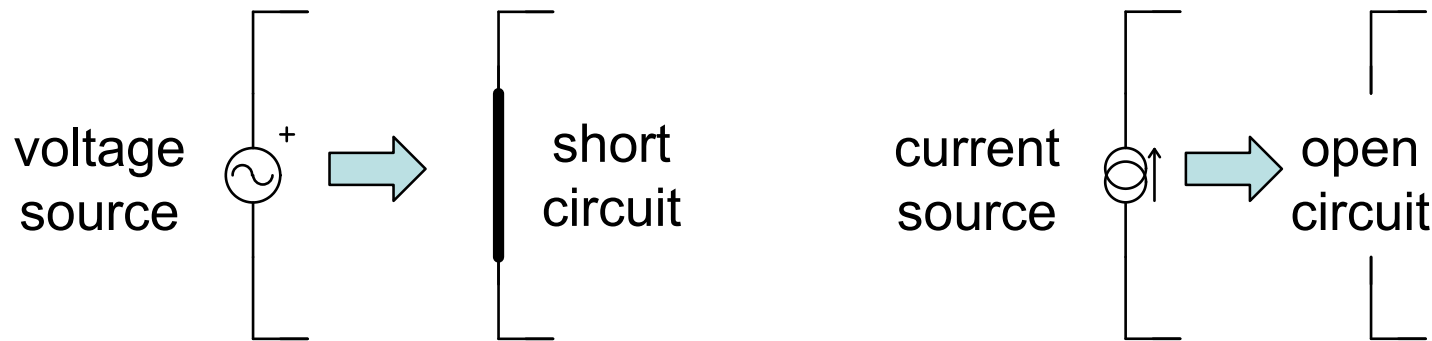- ❑ The poles are linked to the time constants of the system
- ❑ These time constants solely depend on the structure
- Remove the excitation signal to isolate the structure



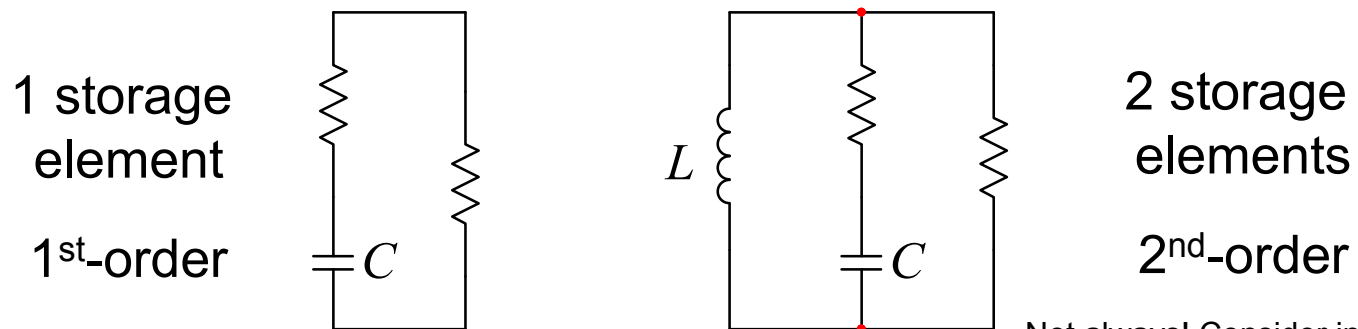
- ❑ The denominator order depends on the storage elements




Not always! Consider individual state variables.

Start by Identifying the Time Constants

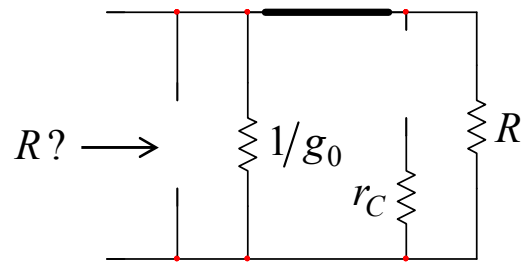
- The excitation is zero, elements are in their dc states
- 3 storage elements, 3 time constants, 3 drawings


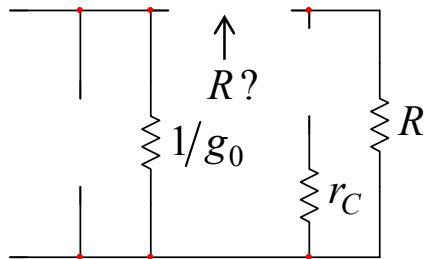
$$\tau_1 = f(C_s) \longrightarrow \tau_1 = C_s \left(\frac{1}{g_0} \parallel R \right)$$


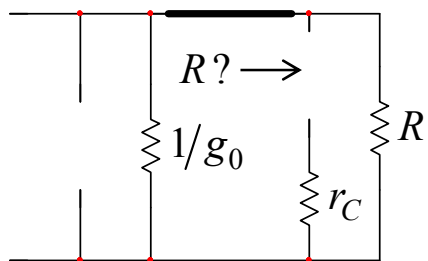
$$\tau_2 = f(L) \longrightarrow \tau_2 = \frac{L}{\frac{1}{g_0} + R}$$



$$\tau_3 = f(C) \longrightarrow \tau_3 = C \left(r_C + \left(\frac{1}{g_0} \parallel R \right) \right)$$

First Coefficients a_1 and a_2


- FACTs tell us that a_1 sums up all time constants

$$a_1 = \tau_1 + \tau_2 + \tau_3 \longrightarrow \text{Dimension is time}$$

- For a_2 , we multiply combined-time constants

$$a_2 = \tau_1\tau_2^1 + \tau_1\tau_3^1 + \tau_2\tau_3^2 \longrightarrow \text{Dimension is time}^2$$

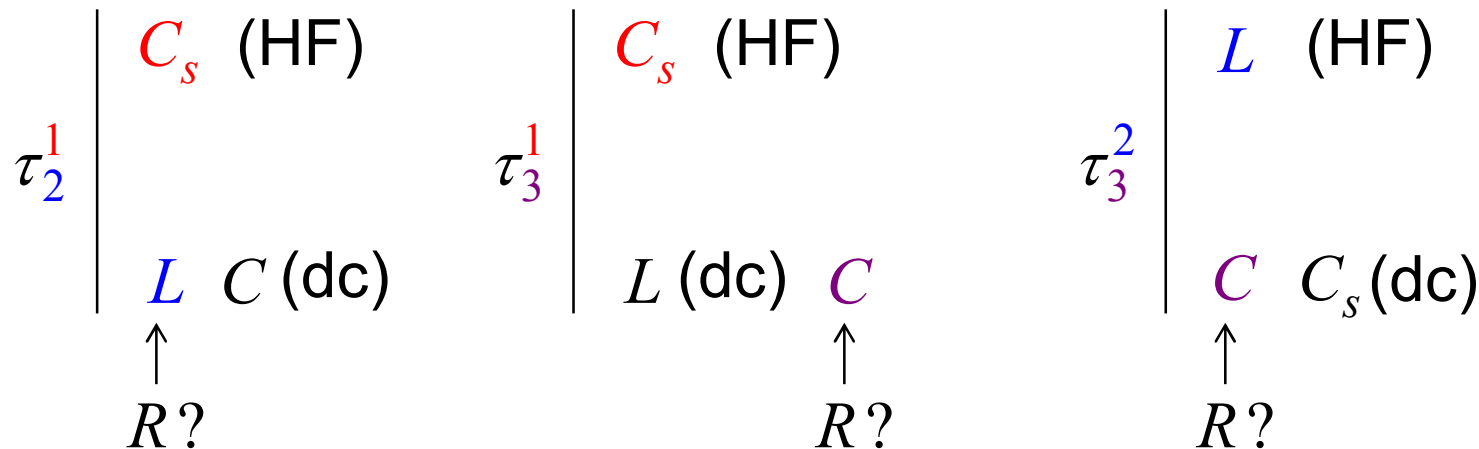- What is this new time constants definition, τ_2^1 ?





V. Vorpérian, "Fast Analytical Techniques for Electrical and Electronic Circuits", Cambridge Press, 2002




Coefficient a_2 Mixes Time Constants

□ Drawings are key to avoid mistakes

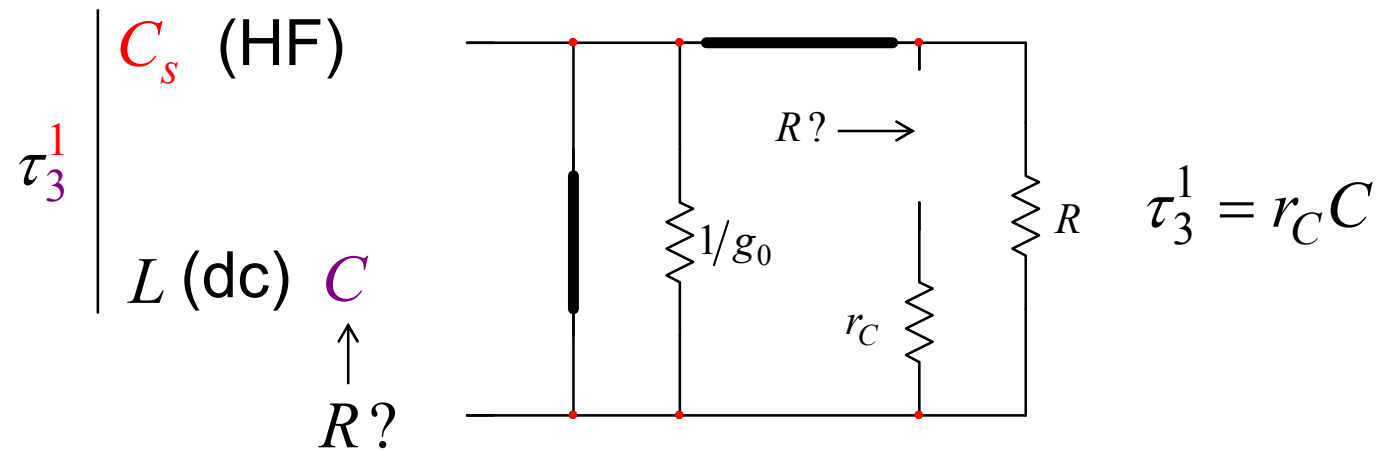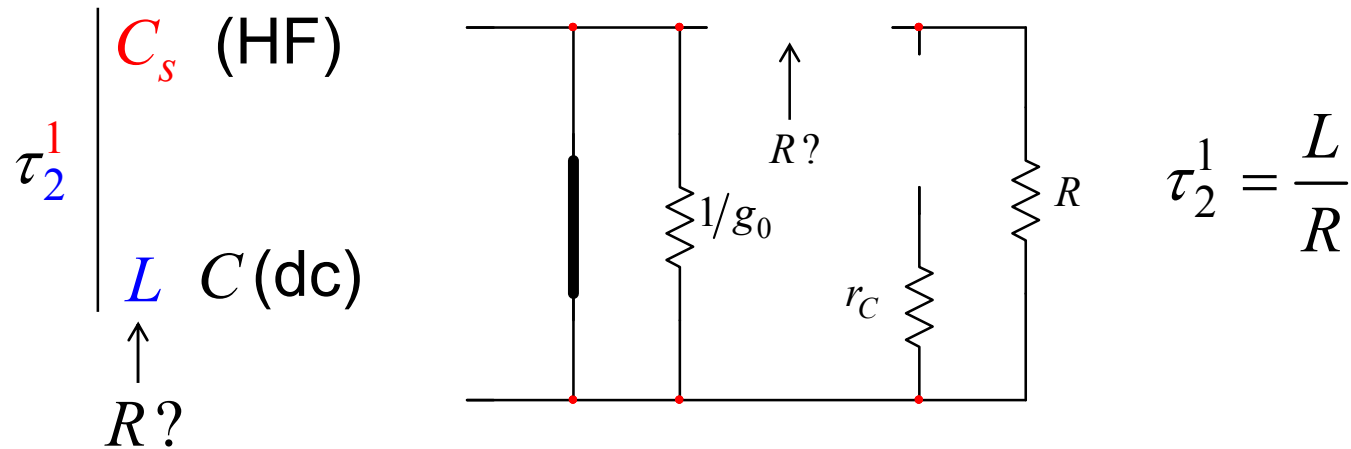

(Carefully) Mixing Time Constants

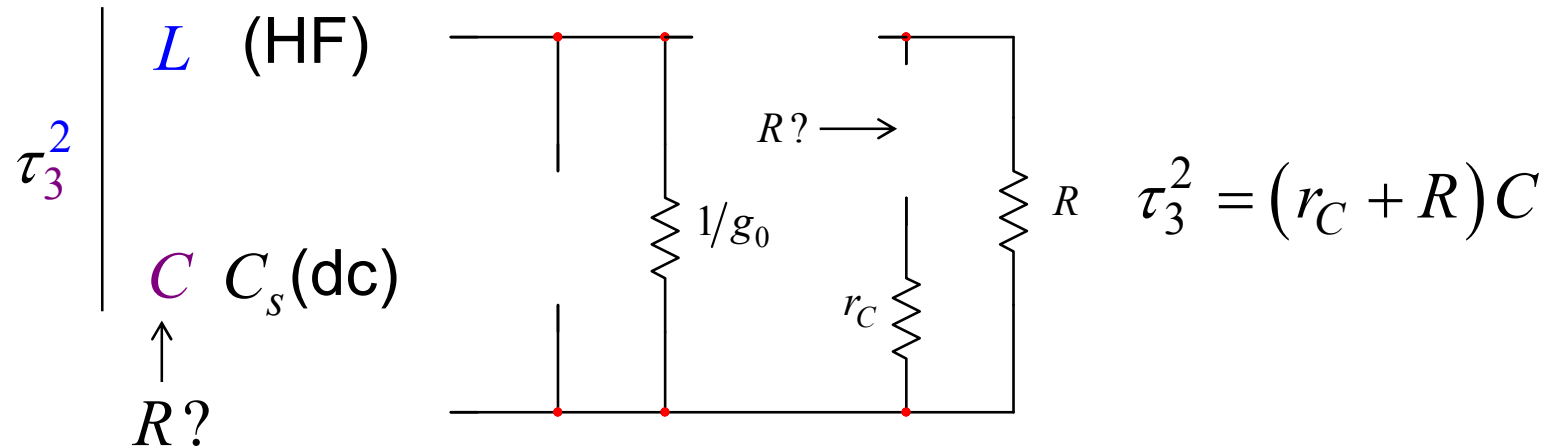- The last drawing completes the a_2 expression



- a_2 coefficient is there!


$$a_2 = C_s \left(\frac{1}{g_0} \parallel R \right) \frac{L}{R} + C_s \left(\frac{1}{g_0} \parallel R \right) r_c C + \frac{L}{\frac{1}{g_0} + R} (r_c + R) C$$

...And a_3 is ?

- For a_3 , we multiply by a third time-constant

$$a_3 = \tau_1 \tau_2 \tau_3^{1,2} \longrightarrow \text{Dimension is time}^3$$

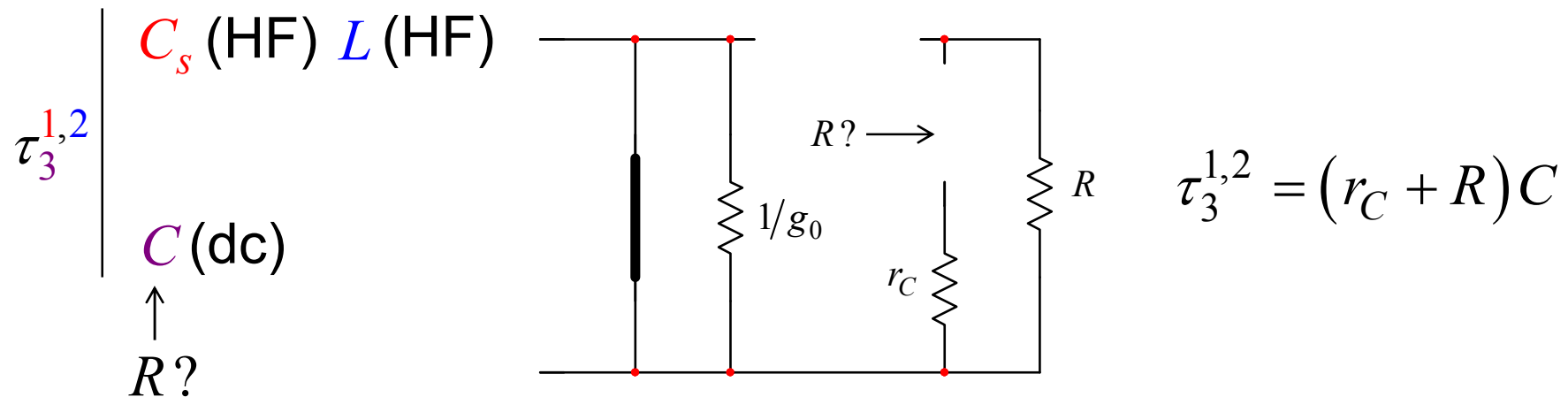- What is this new time constant definition?



- The final coefficient has been identified

$$a_3 = C_s \left(\frac{1}{g_o} \parallel R \right) \frac{L}{R} (r_c + R) C$$

Time to Check Results

□ A Mathcad® sheet can be built to verify these calculations

$$H(s) = G_0 \frac{1 + \frac{s}{s_{z_1}}}{1 + a_1 s + a_2 s^2 + a_3 s^3} \quad G_0 = k_0 \left(R \parallel \frac{1}{g_0} \right)$$

$$\omega_{z_1} = \frac{1}{r_C C}$$

$$a_1 = C_s \left(\frac{1}{g_o} \parallel R \right) + \frac{L}{\frac{1}{1} + R} + C \left(r_C + \left(\frac{1}{g_0} \parallel R \right) \right)$$

$$a_2 = C_s \left(\frac{1}{g_o} \parallel R \right) \frac{L}{R} + C_s \left(\frac{1}{g_o} \parallel R \right) r_C C + \frac{L}{\frac{1}{1} + R} (r_C + R) C$$

$$a_3 = C_s \left(\frac{1}{g_o} \parallel R \right) \frac{L}{R} (r_C + R) C$$

5 V/1 A buck

$V_{in} = 10 \text{ V}, F_{sw} = 100 \text{ kHz}, R_i = 0.25 \Omega, S_e = 2.5 \text{ kV/s}$
 $C = 100 \mu\text{F}, r_C = 0.1 \Omega, L = 100 \mu\text{H}, C_s = 101 \text{ nF}, V_c = 1.28 \text{ V}$

$$I_c = 4.94 \text{ A}$$

$$k_i = 2 \Omega^{-1} \quad k_0 = 4 \Omega^{-1}$$

$$g_0 = 0.01 \Omega^{-1}$$

$$g_f = -7.5 \text{ m}\Omega^{-1} \quad g_r = 0.49 \Omega^{-1}$$


$$g_i = -250 \text{ m}\Omega^{-1}$$

$$G_0 = 12 \text{ dB} \quad f_{z_1} = 15.9 \text{ kHz}$$



See What SPICE is Saying

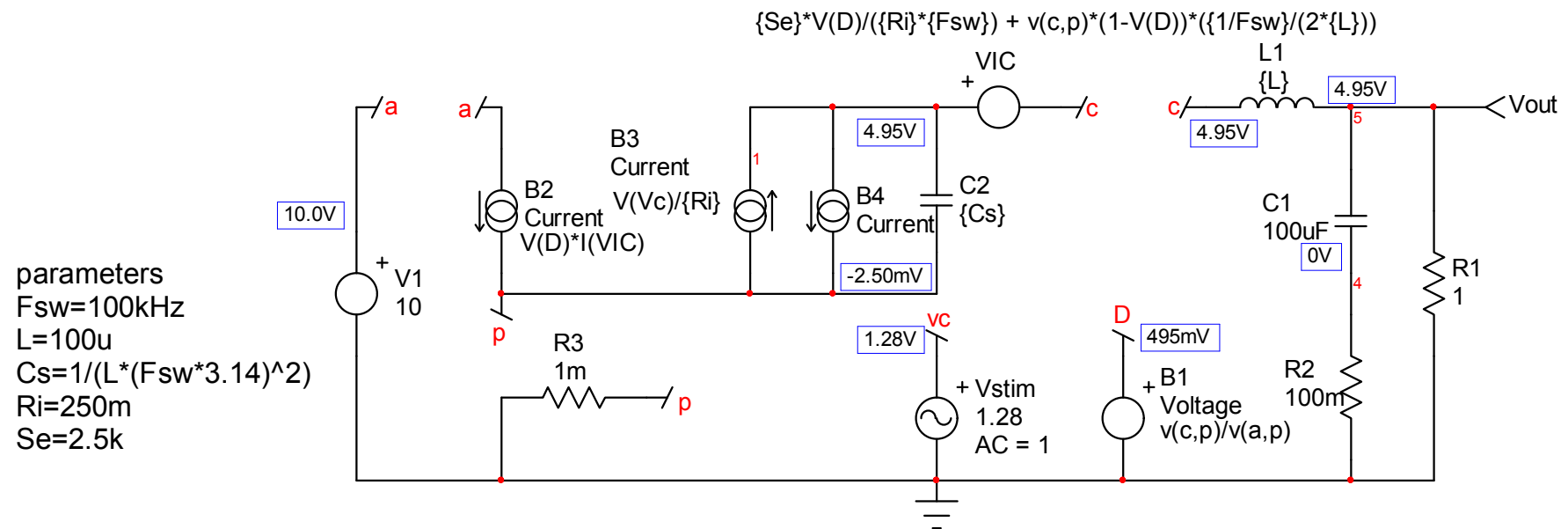
- Use the large-signal model, SPICE linearizes it for you



- Then compare results with those of Mathcad®

Excellent Agreement!

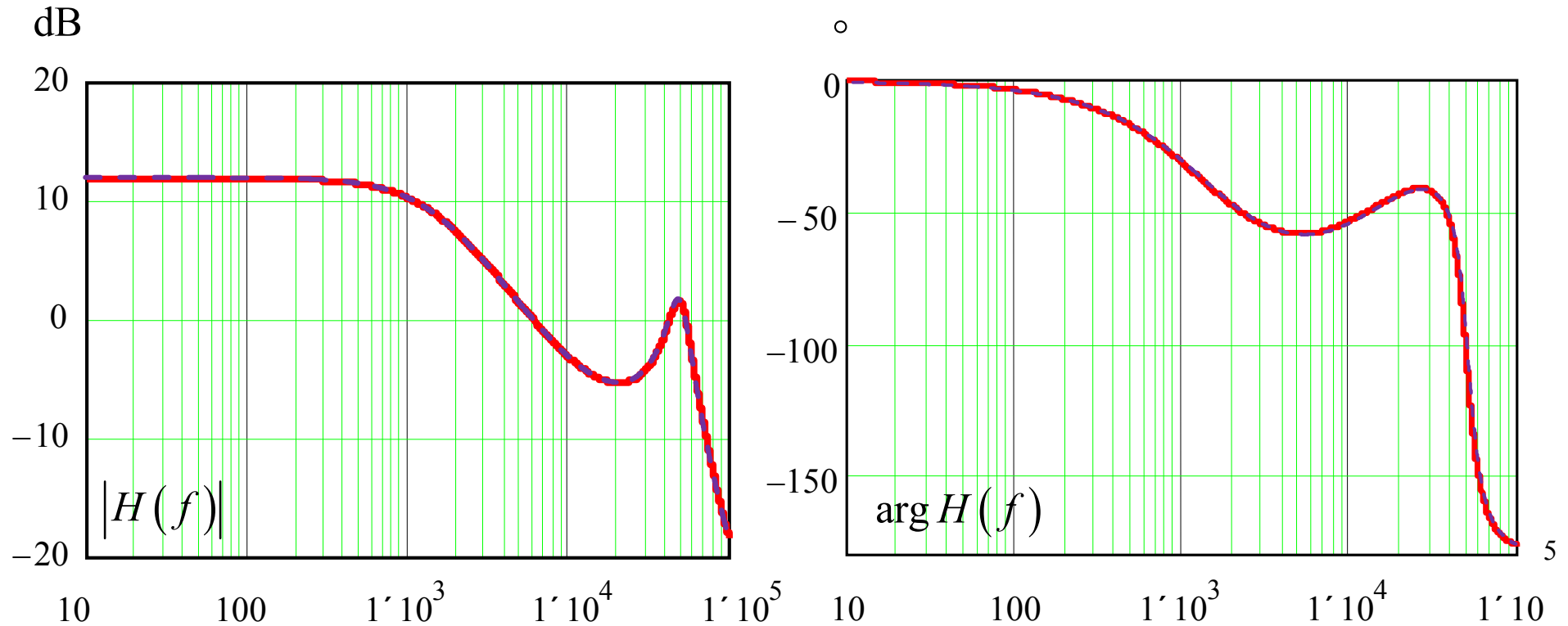- Superimposed curves mean transfer functions are identical




Rearranging Expressions

- ❑ The denominator is not really in a low-entropy form

$$D(s) = 1 + a_1s + a_2s^2 + a_3s^3$$

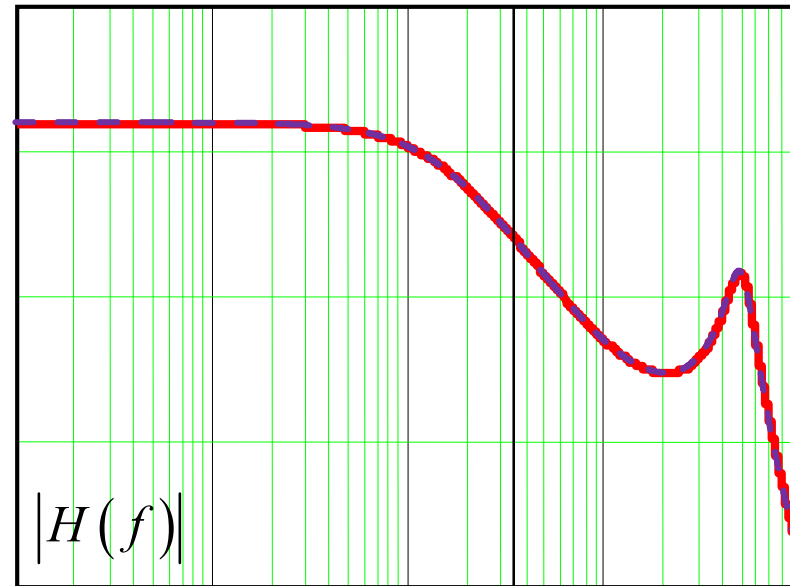- ❑ This is a third-order polynomial form that can be factored



$$D(s) \approx 1 + a_1s$$

Low frequency

High frequency

$$D(s) \approx 1 + \frac{a_2}{a_1}s + \frac{a_3}{a_1}s^2$$

Final Lap!


- The transfer function can now unveil peaking and damping

$$H(s) \approx H_0 \frac{1 + \frac{s}{\omega_{z_1}}}{1 + \frac{s}{\omega_{p_1}} + \frac{1}{\omega_n Q} + \left(\frac{s}{\omega_n}\right)^2} \quad H_0 = \frac{R}{R_i} \frac{1}{1 + \frac{RT_{sw}}{L} [m_c(1-D) - 0.5]}$$

$$\omega_{p_1} = \frac{1}{RC} + \frac{T_{sw}}{LC} [m_c(1-D) - 0.5] \quad \omega_{z_1} = \frac{1}{r_C C}$$

$$\omega_n = \frac{\pi}{T_{sw}} \quad Q = \frac{1}{\pi [m_c(1-D) - 0.5]}$$
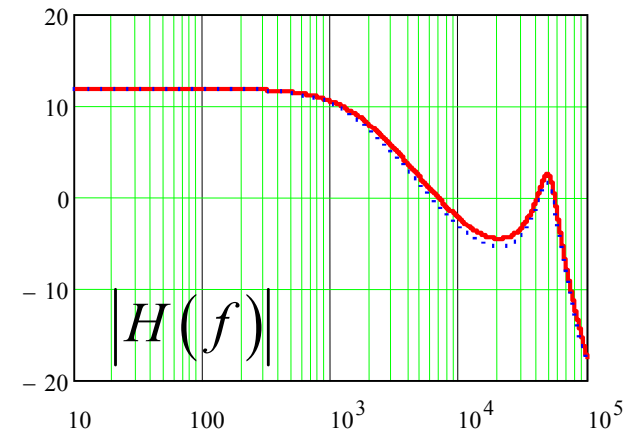
$$m_c = 1 + \frac{S_e}{S_n} \quad \begin{array}{l} \text{Artificial ramp} \\ \text{Inductor on slope} \end{array}$$



R. B. Ridley, "A new Continuous-Time Model for CM Control", IEEE Transactions of Power Electronics, Vol. 6, April 1991




Course Agenda

- ❑ Introducing the PWM Switch Model
- ❑ CCM, DCM and BCM in Voltage Mode
- ❑ Pulse Width Modulator Gain
- ❑ The PWM Switch Model in Current Mode
- ❑ PWM Switch at Work in a Buck Converter
- ❑ **A Simplified Approach to Modeling a DCM Boost**
- ❑ Transfer Function of a BCM Boost in Current Mode
- ❑ Small-Signal Model of The Active Clamp Forward



Characterize the LED String

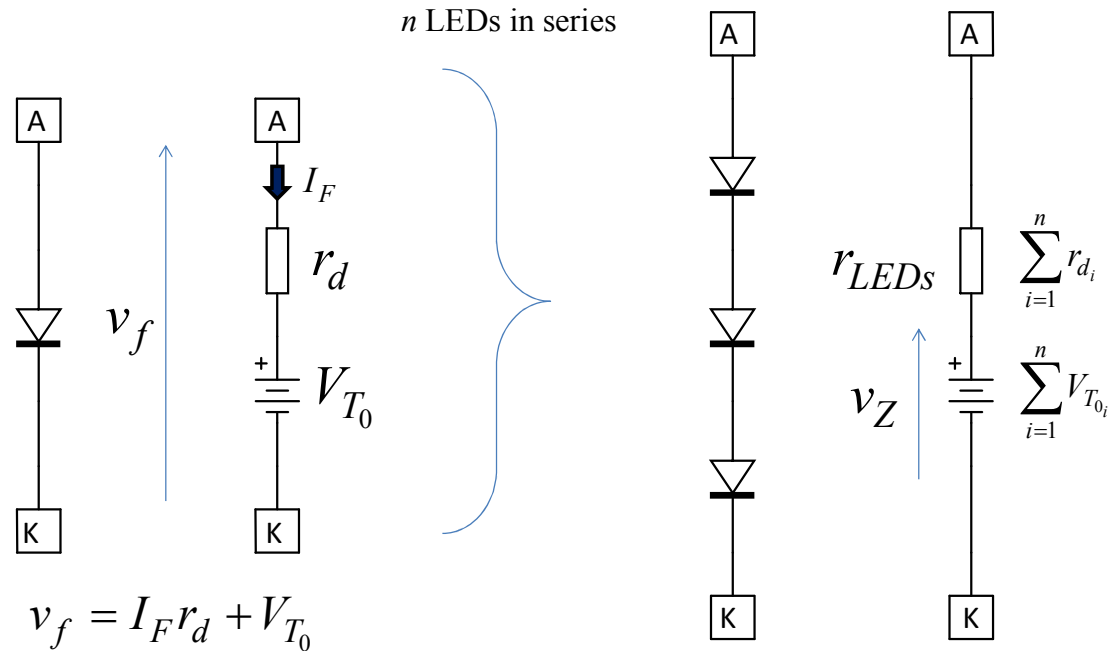- Evaluate forward drop and dynamic resistance




- Lab. measurements require simple V and A-meters

$$r_{LEDs} = \frac{V_{f_1} - V_{f_2}}{I_{F_1} - I_{F_2}} = \frac{27.5 - 26.4}{0.1 - 0.08} = 55 \Omega \quad V_Z \approx V_{f_1} - R_{LEDs} I_{F_1} = 27.5 - 0.1 \times 55 = 22 \text{ V}$$

A Simplified Approach

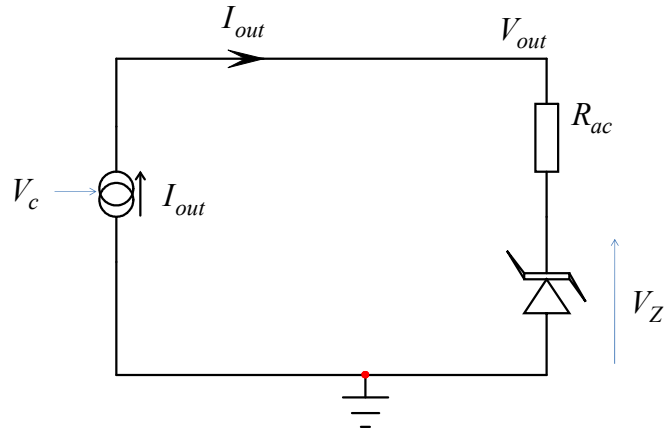- The LED string is driven by a current source




$$R_{ac} = r_{LEDs} + R_{sense}$$

$$V_{out} = R_{ac} I_{out} + V_Z$$



$$V_{out}(s) = R_{ac} I_{out}(s)$$

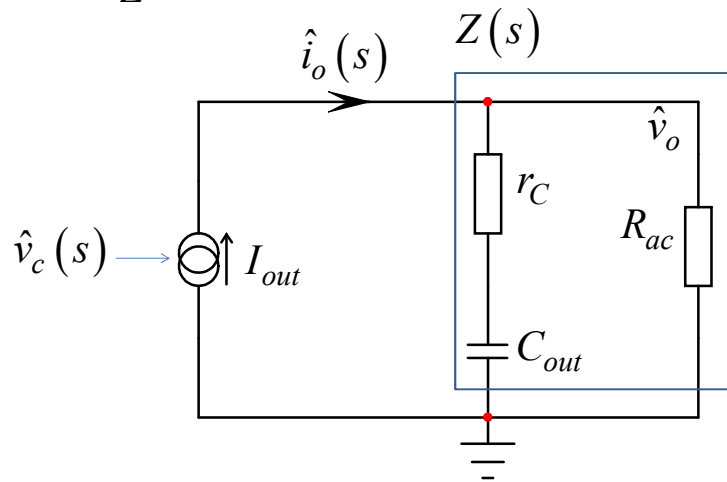- V_Z sets the operating point, R_{ac} sets the ac response




Current Source Model

- ❑ It is convenient and fast to consider 1st-order models
- ❑ Use the converter transfer function in DCM


$$\frac{V_{out}}{V_{in}} = \frac{1 + \sqrt{1 + \frac{2T_{sw}D^2R_{dc}}{L}}}{2}$$

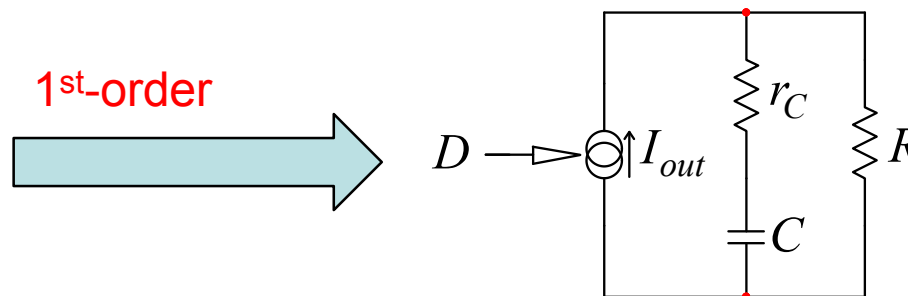- ❑ We purposely consider an instantaneous power response
 - if D changes, P_{out} immediately translates
 - this is not true for boost or buck-boost converters: RHPZ
 - high-frequency phenomena are also lost



Define the Duty Ratio

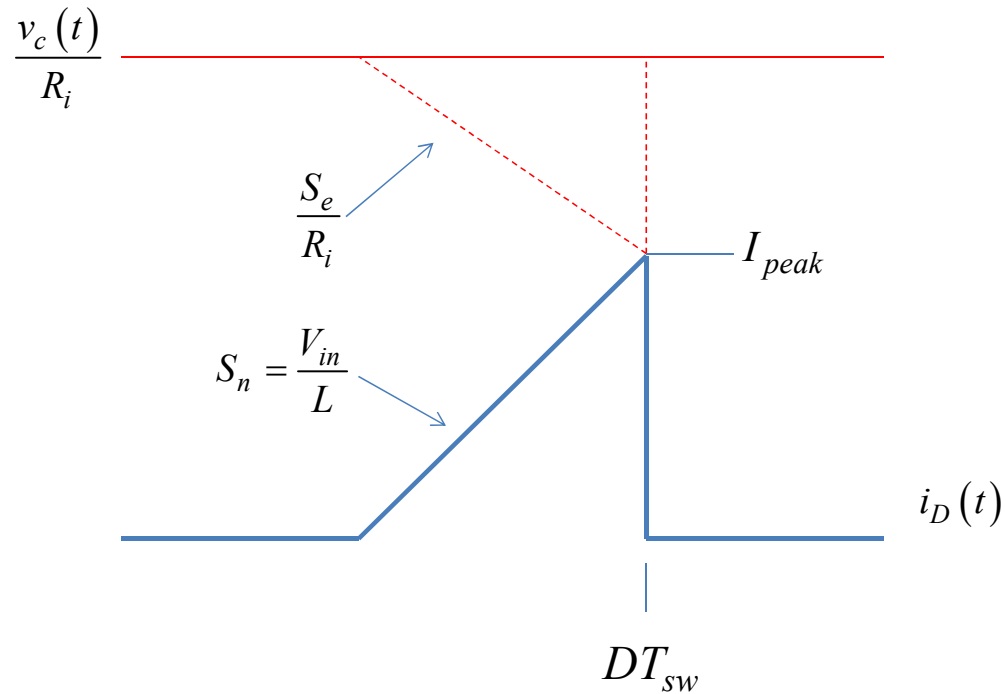□ In the previous expression, D is unknown



$$\left. \begin{aligned} I_{peak} &= \frac{V_c}{R_i} - \frac{S_e}{R_i} DT_{sw} \\ I_{peak} &= \frac{DT_{sw} V_{in}}{L} \end{aligned} \right\} D = \frac{V_c L}{S_e T_{sw} L + R_i T_{sw} V_{in}}$$



Update the Output Current Equation

- Massage the dc transfer equation to unveil I_{out}

$$\frac{V_{out}}{V_{in}} = \frac{1 + \sqrt{1 + \frac{2T_{sw}D^2 V_{out}}{L} I_{out}}}{2}$$

- Inject the duty ratio definition, solve for I_{out}

$$I_{out} = \frac{2V_{out}LV_c^2}{T_{sw}} \frac{1}{\left[\left(\frac{2V_{out}}{V_{in}} - 1 \right)^2 - 1 \right] (S_e L + R_i V_{in})^2}$$

- There are two modulated variables, V_c and V_{out}

$$\longrightarrow \hat{v}_{in} = 0$$

$$\left. \begin{array}{l} \frac{\partial I_{out}}{\partial V_c} \Big|_{\hat{v}_{out}} \hat{v}_c \\ \frac{\partial I_{out}}{\partial V_{out}} \Big|_{\hat{v}_c} \hat{v}_o \end{array} \right\}$$




A Simple Model

□ You obtain two small-signal sources: $\hat{i}_{out} = g_1 \hat{v}_c + g_2 \hat{v}_{out}$

$$g_1 = \frac{\partial I_{out}(V_c, V_{out})}{\partial V_c} = \frac{V_{in}^2 V_c L}{T_{sw} (V_{out} - V_{in}) (S_e L + R_i V_{in})^2}$$


$$g_2 = \frac{\partial I_{out}(V_c, V_{out})}{\partial V_{out}} = - \frac{V_{in}^2 V_c^2 L}{2 T_{sw} (V_{in} - V_{out})^2 (S_e L + R_i V_{in})^2}$$

□ The circuit is quite simple

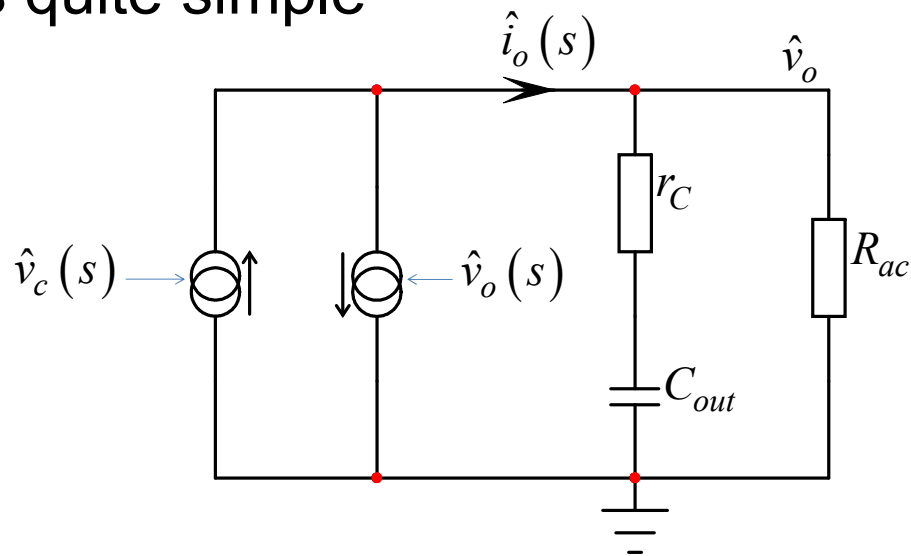


A Current Driving an Impedance

- The second term is a simple resistance

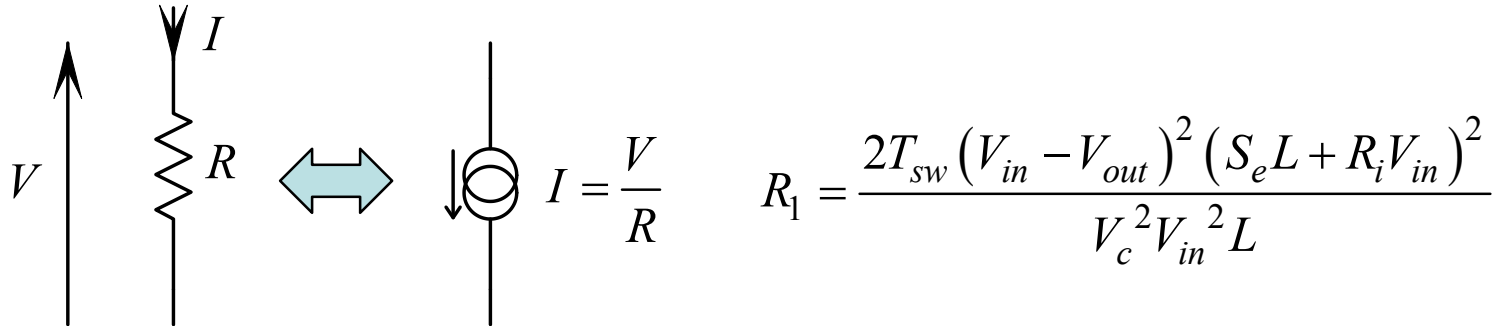


- Update the final model

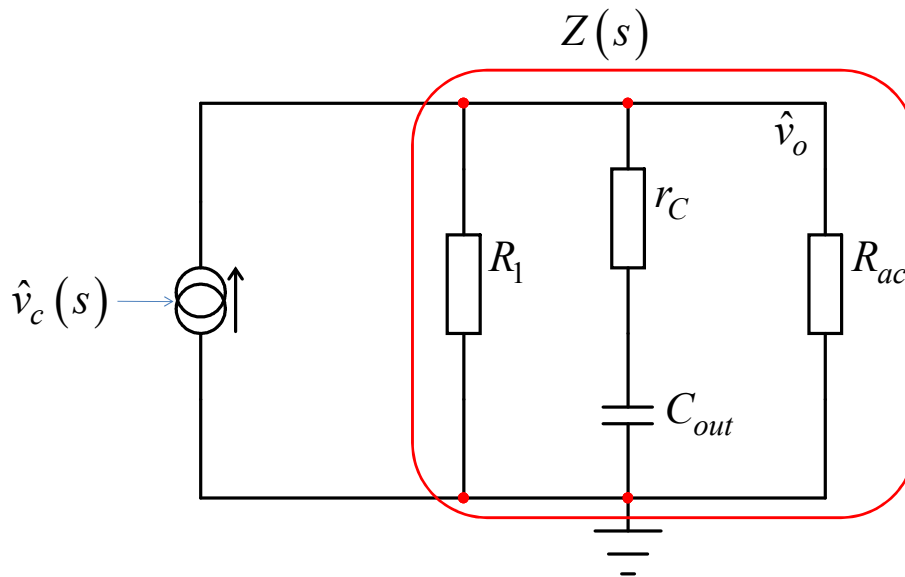


$$V_{out}(s) = V_c(s) g_1 Z(s)$$

Use FACTS to Get the Impedance

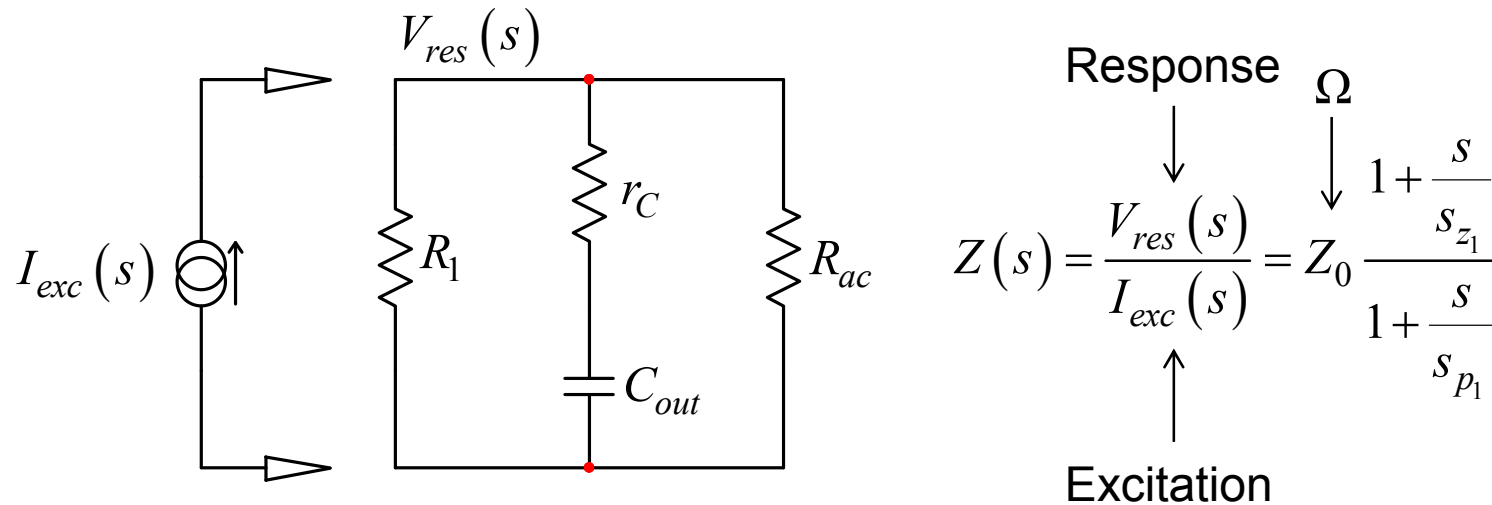- Obtain the impedance (transfer function) in a snapshot




- For dc, open the capacitor

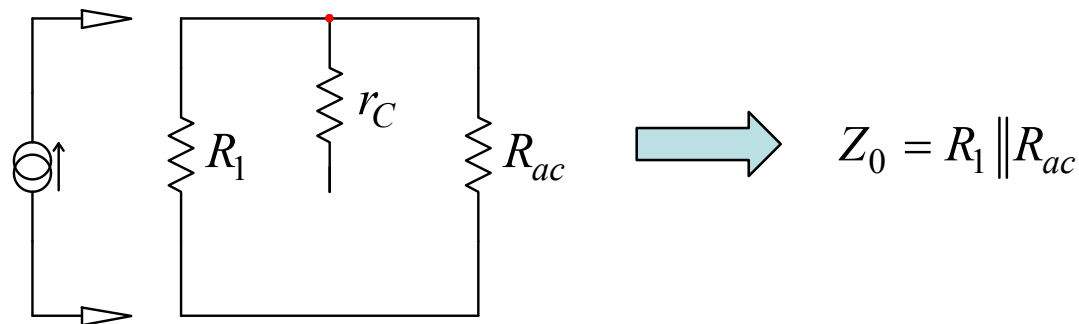

No Algebra to Get the Result!

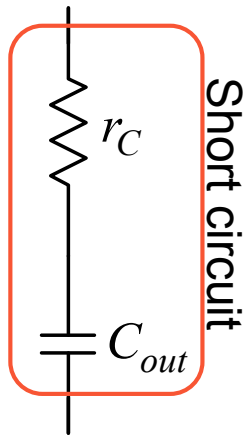- At the zero frequency, the response disappears




$$r_C + \frac{1}{sC_{out}} = \frac{sr_C C_{out} + 1}{sC_{out}}$$

$$sr_C C_{out} + 1 = 0$$

$$\omega_{z_1} = \frac{1}{r_C C_{out}}$$

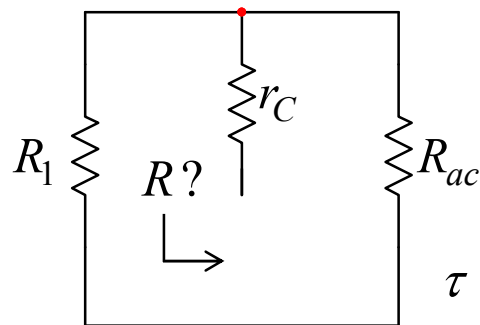- Remove the excitation and look at the resistance driving C_{out}



$$\Rightarrow Z(s) = R_1 \parallel R_{ac} \frac{1 + sr_C C_{out}}{1 + sC_{out} (r_C + R_1 \parallel R_{ac})}$$

$$\tau = \left[r_C + (R_1 \parallel R_{ac}) \right] C_{out}$$


Final Expression

- Associate the impedance expression with g_1

$$\frac{V_{out}(s)}{V_c(s)} = H_0 \frac{1 + \frac{s}{\omega_{z_1}}}{1 + \frac{s}{\omega_{p_1}}} \quad H_0 = \frac{V_{in}^2 V_c L}{T_{sw} (V_{out} - V_{in}) (S_e L + R_i V_{in})^2} (R_{ac} \parallel R_1)$$

$$\omega_{z_1} = \frac{1}{r_C C_{out}} \quad \omega_{p_1} = \frac{1}{C_{out} (r_C + R_1 \parallel R_{ac})}$$

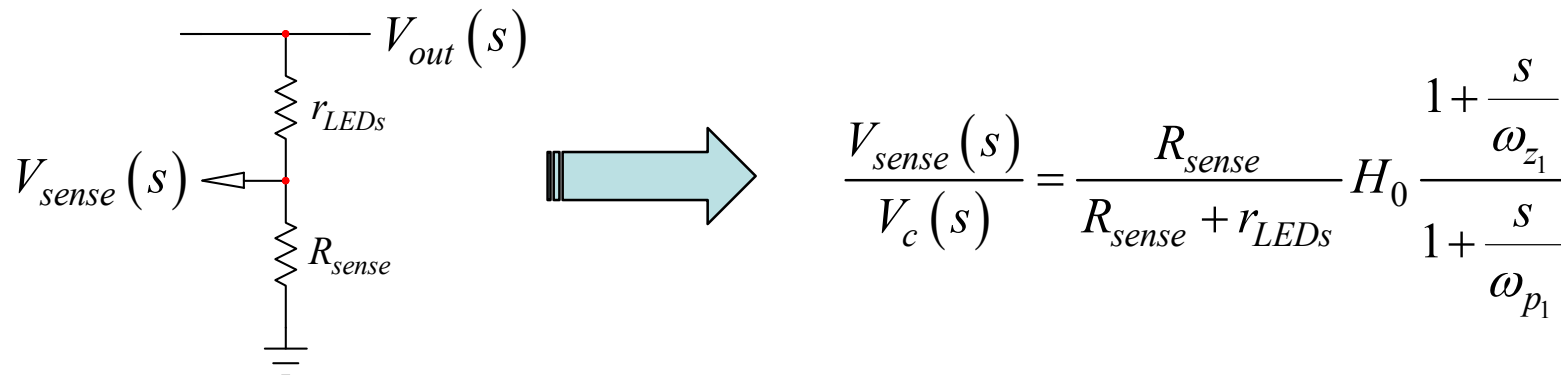- However, we want the control-to-output current expression



Checking our Model Response

- Ac simulation of the current source-based approach

parameters

$$R_i = 0.25$$

$$v_c = 0.4$$

$$S_e = 100k$$

$$F_{sw} = 1Meg$$

$$L = 3.3u$$

$$T_{sw} = 1/F_{sw}$$


$$V_{in} = 12$$

$$V_{out} = 32.85$$

$$k_1 = V_{in}^2 * v_c * L$$


$$k_2 = T_{sw} * (V_{out} - V_{in}) * (S_e * L + R_i * V_{in})^2$$
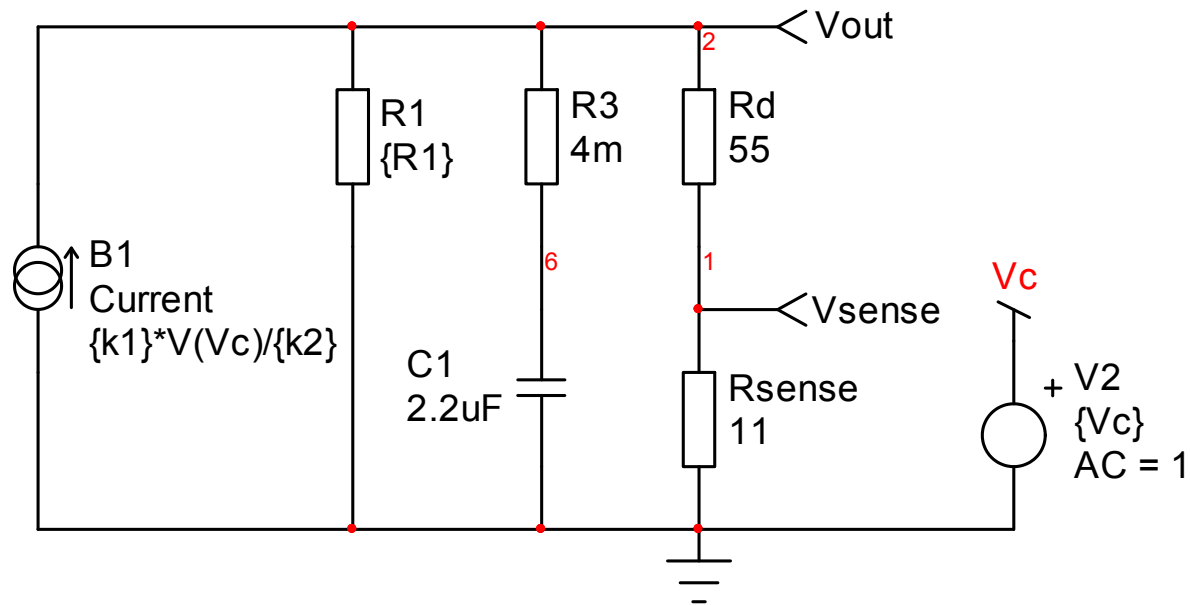
$$R_1 = 2 * T_{sw} * (V_{in} - V_{out})^2 * (S_e * L + R_i * V_{in})^2 / (V_c^2 * (V_{in}^2) * L)$$




Final Results

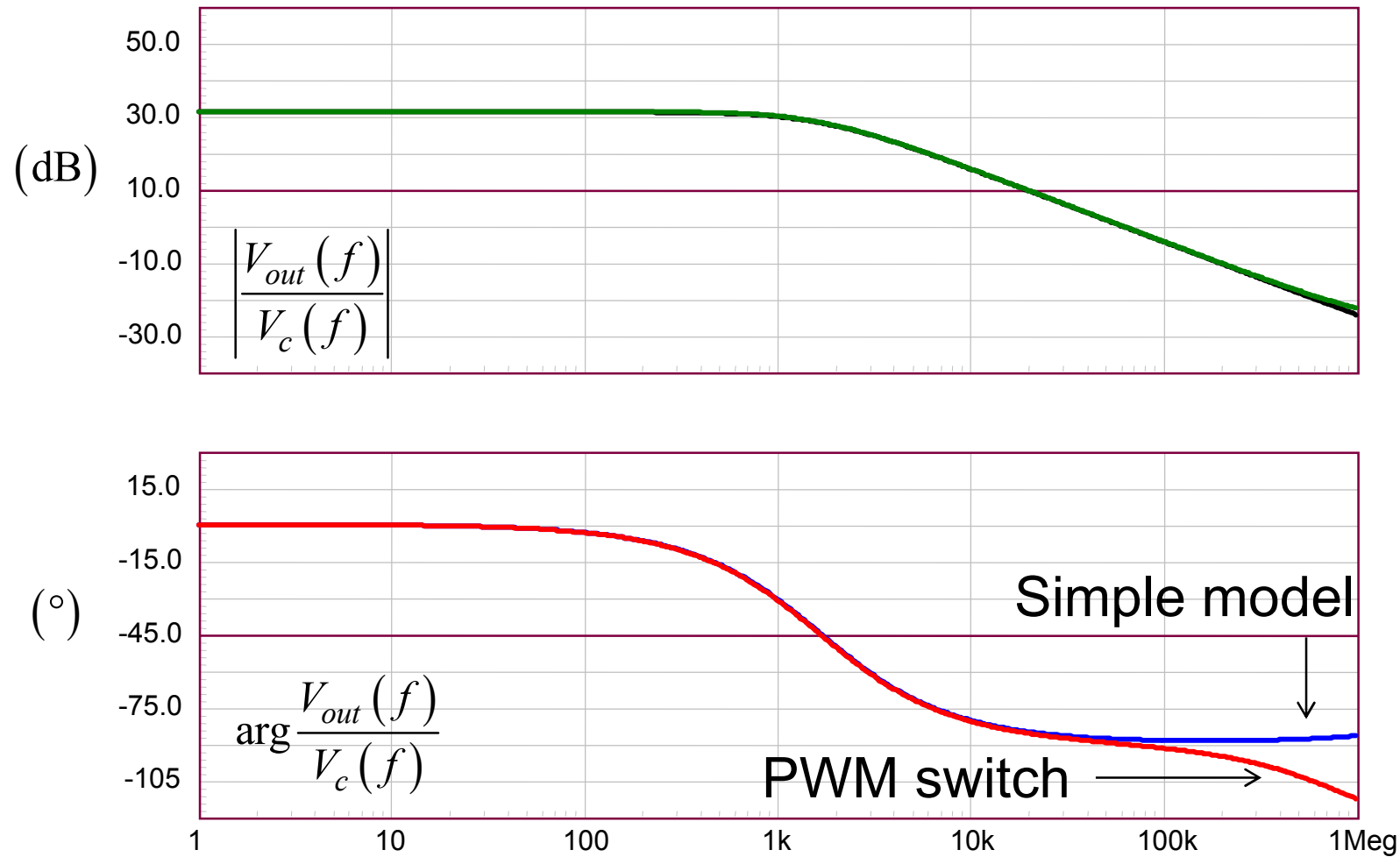- The RHPZ effect is not modeled in the simplified approach



Real Measurement vs Model

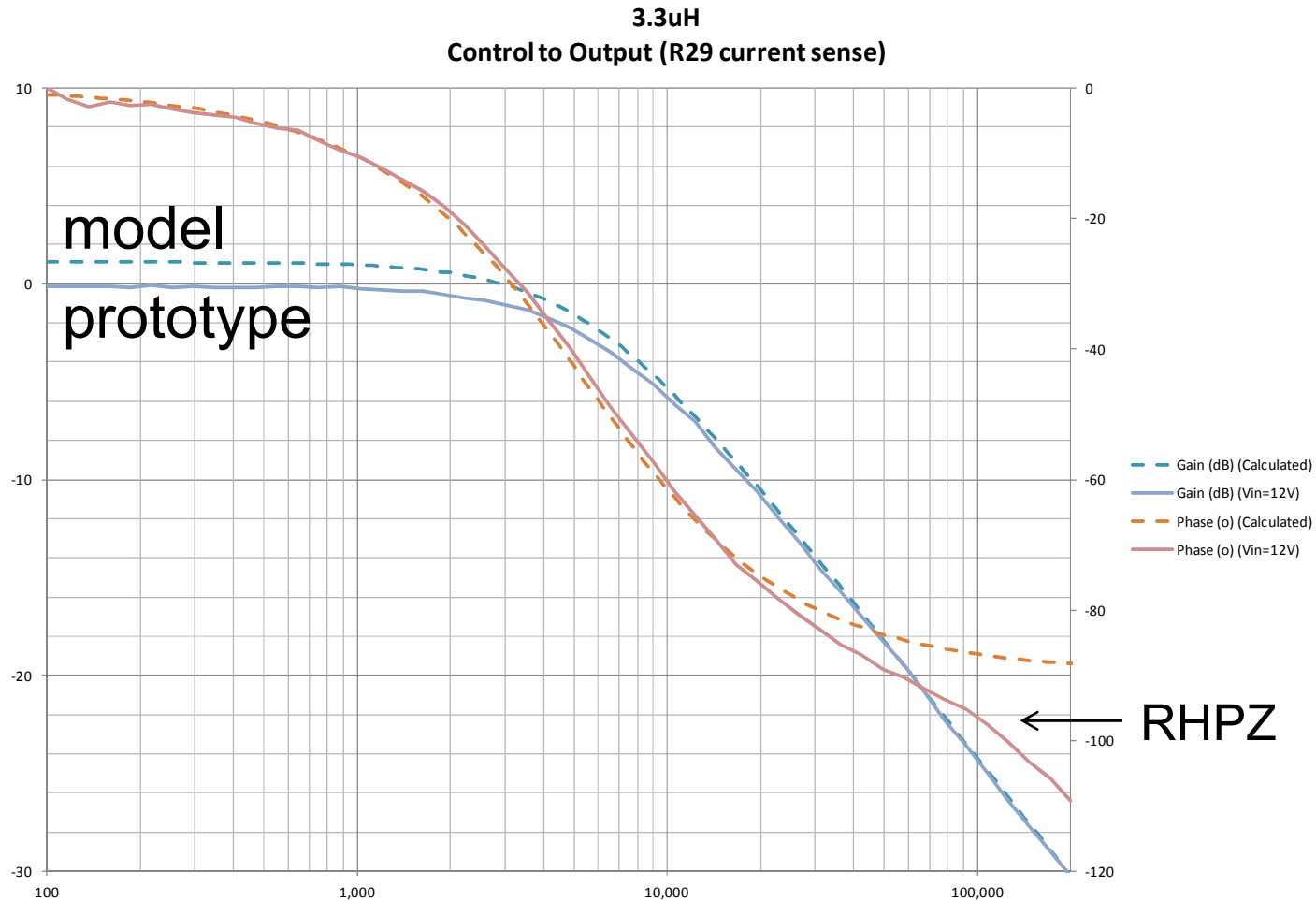□ Deviation occurs, as expected, because of the RHPZ



C. Basso, A. Laprade, "Simplified Analysis of a DCM Boost Converter Driving an LED String", www.how2power.com



Course Agenda

- ❑ Introducing the PWM Switch Model
- ❑ CCM, DCM and BCM in Voltage Mode
- ❑ Pulse Width Modulator Gain
- ❑ The PWM Switch Model in Current Mode
- ❑ PWM Switch at Work in a Buck Converter
- ❑ A Simplified Approach to Modeling a DCM Boost
- ❑ **Transfer Function of a BCM Boost in Current Mode**
- ❑ Small-Signal Model of The Active Clamp Forward




Why Bordeline Operation?

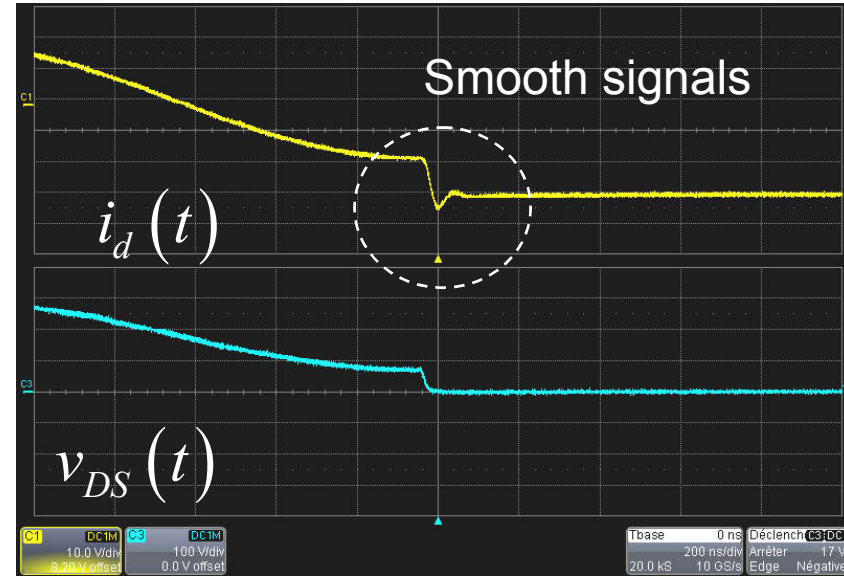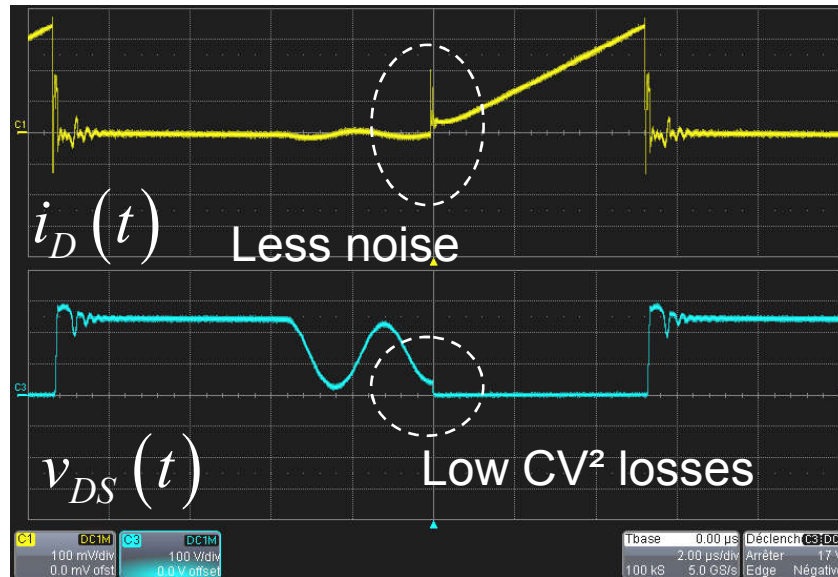- ❑ More converters are using variable-frequency operation
- ❑ This is known as Quasi-Square Wave Resonant mode: QR
 - Valley switching ensures extremely low capacitive losses
 - DCM operation saves losses in the secondary-side diode
 - Easier synchronous rectification
 - The Right Half-Plane Zero is pushed to high frequencies



What is the Principle of Operation?

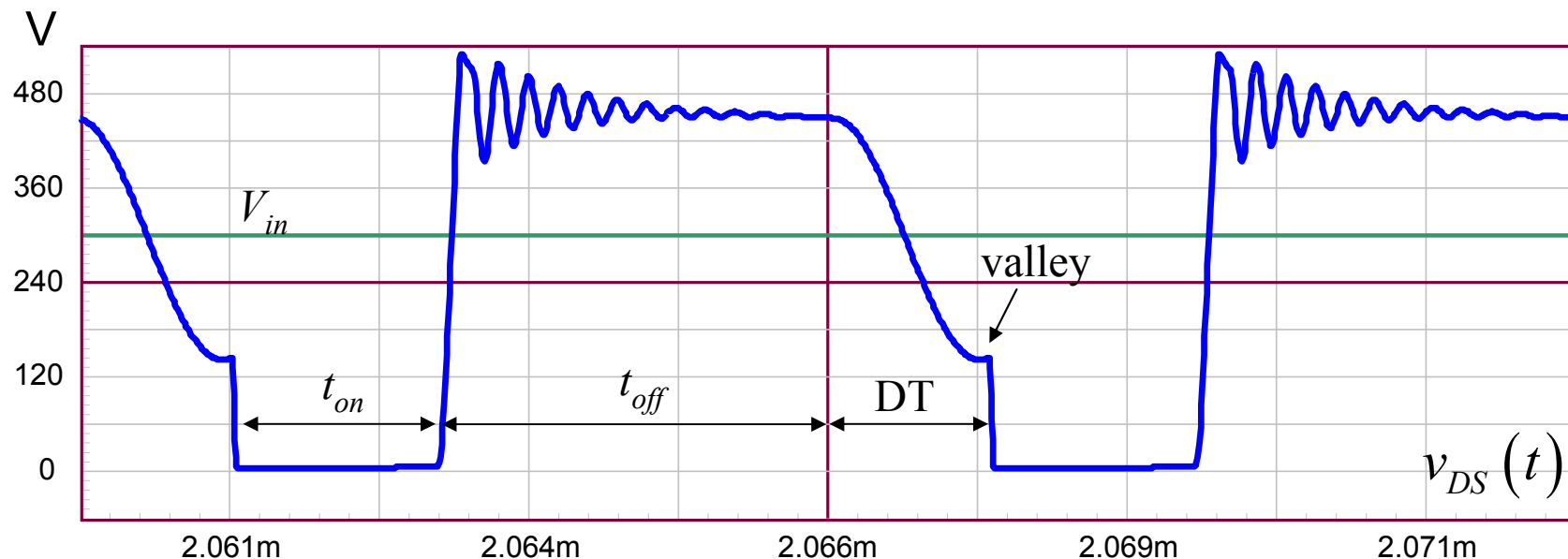- ❑ The drain-source signal is made of peaks and valleys
- ❑ A valley presence means:
 - The drain is at a minimum level, capacitors are naturally discharged
 - The converter is operating in the discontinuous conduction mode




BCM = Borderline or Boundary Conduction Mode

Flyback structure




A QR Circuit Does not Need a Clock

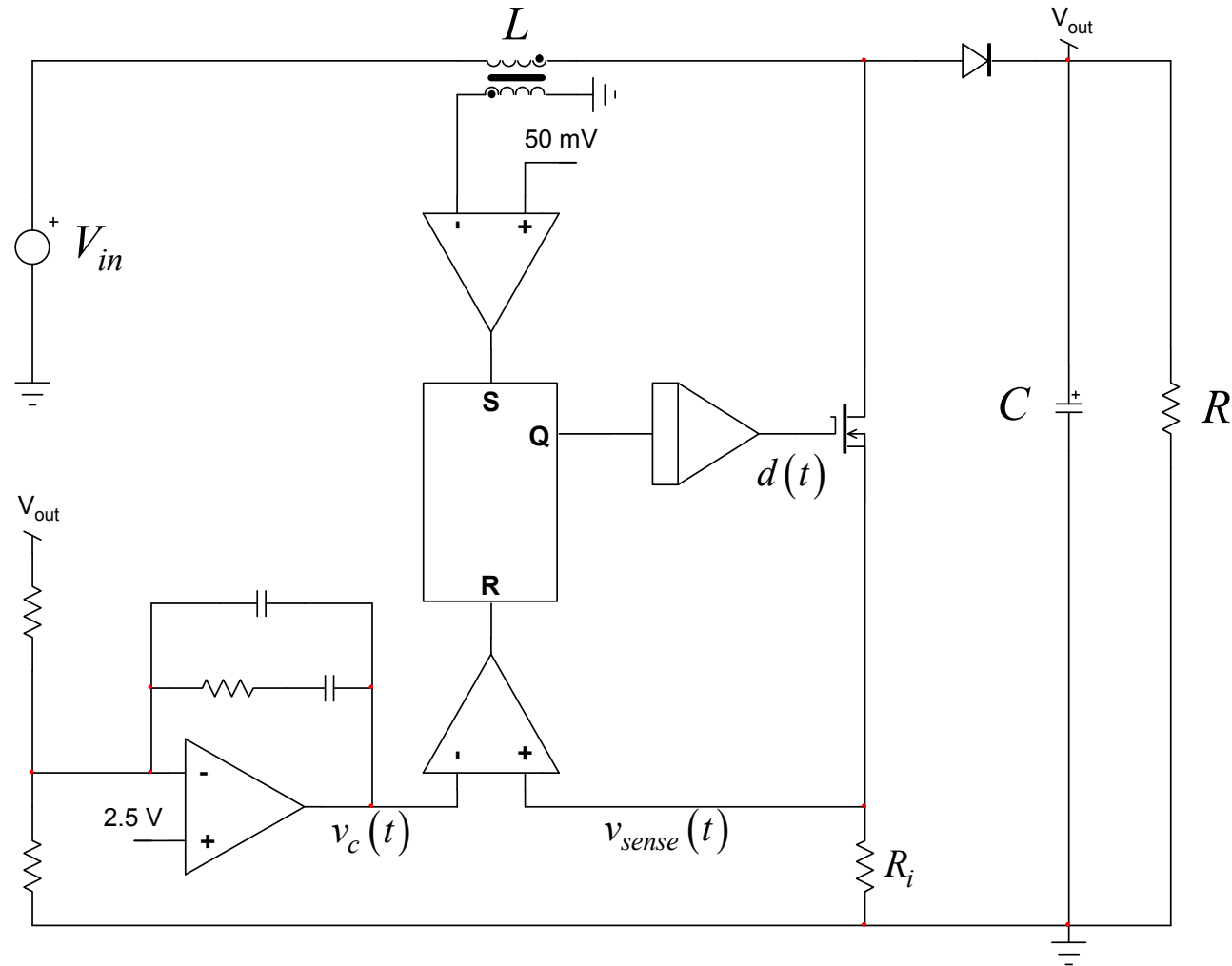- The system is a self-oscillating current-mode converter




A Winding is Used to Detect Core Reset

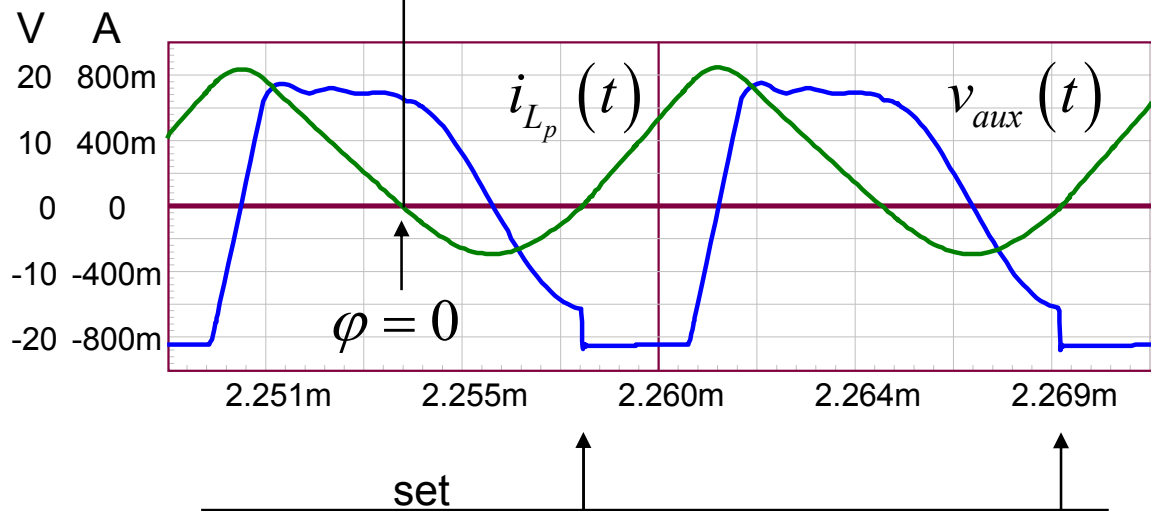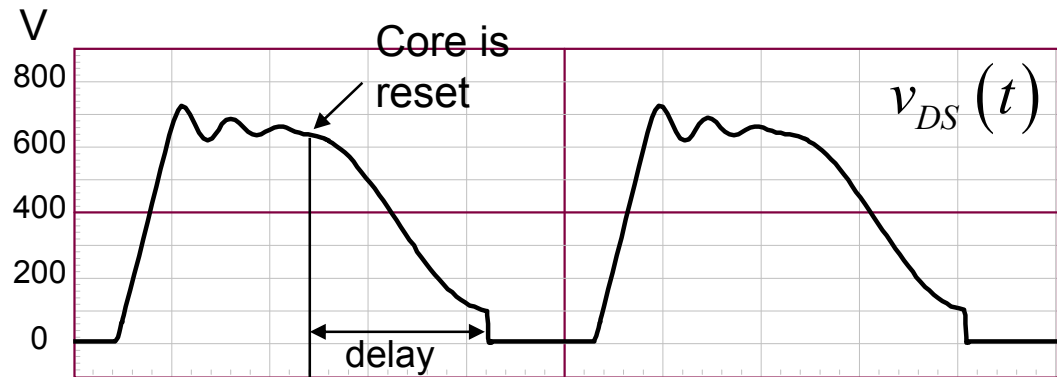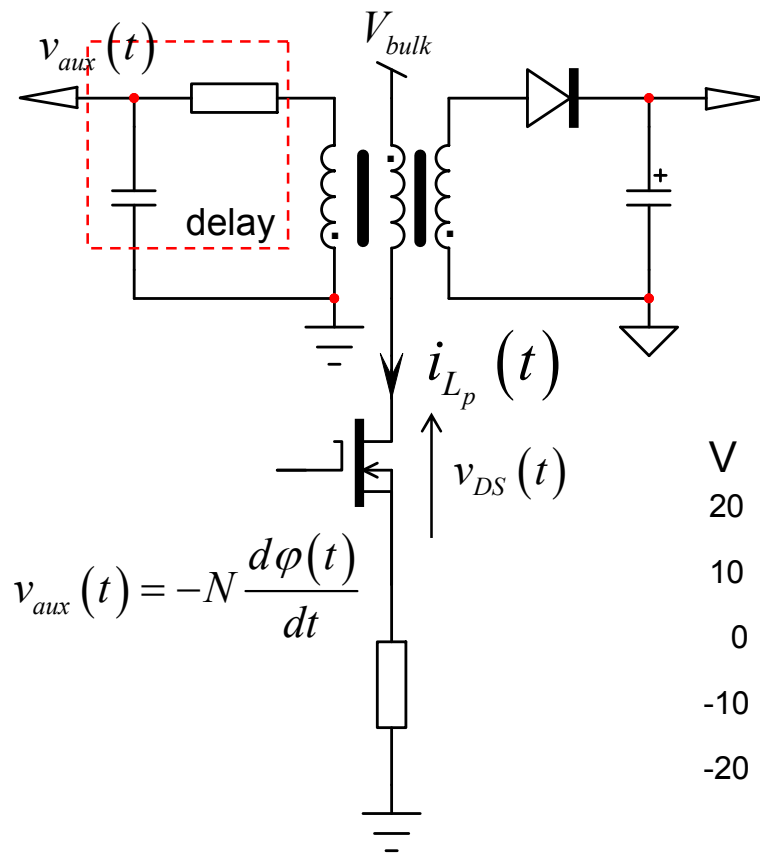- ❑ When the flux returns to zero, the aux. voltage drops
- ❑ Discontinuous mode is always maintained




Test the Large-Signal Model Response

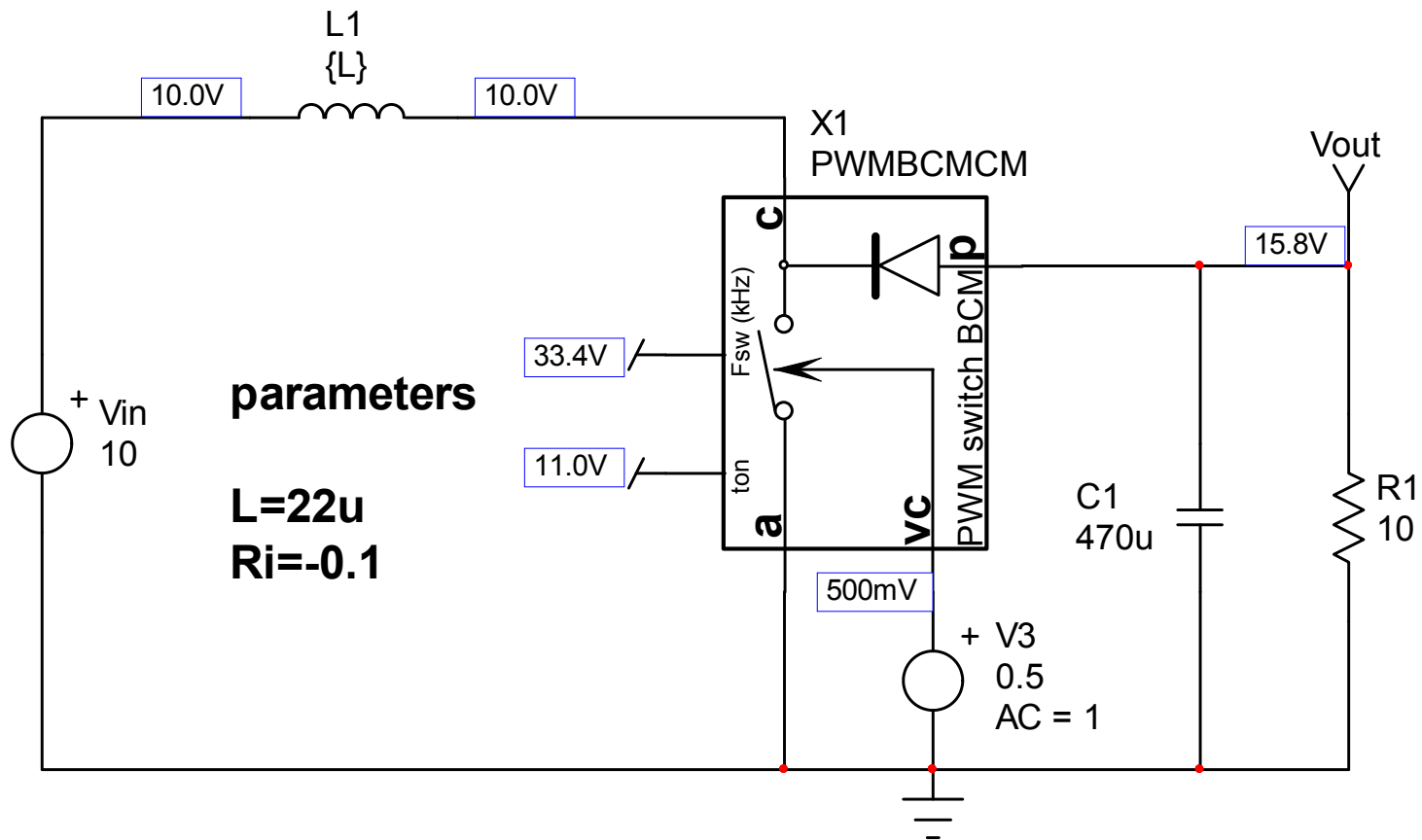- Insert the PWM BCM CM model in the boost converter




SPICE Gives Us the Response

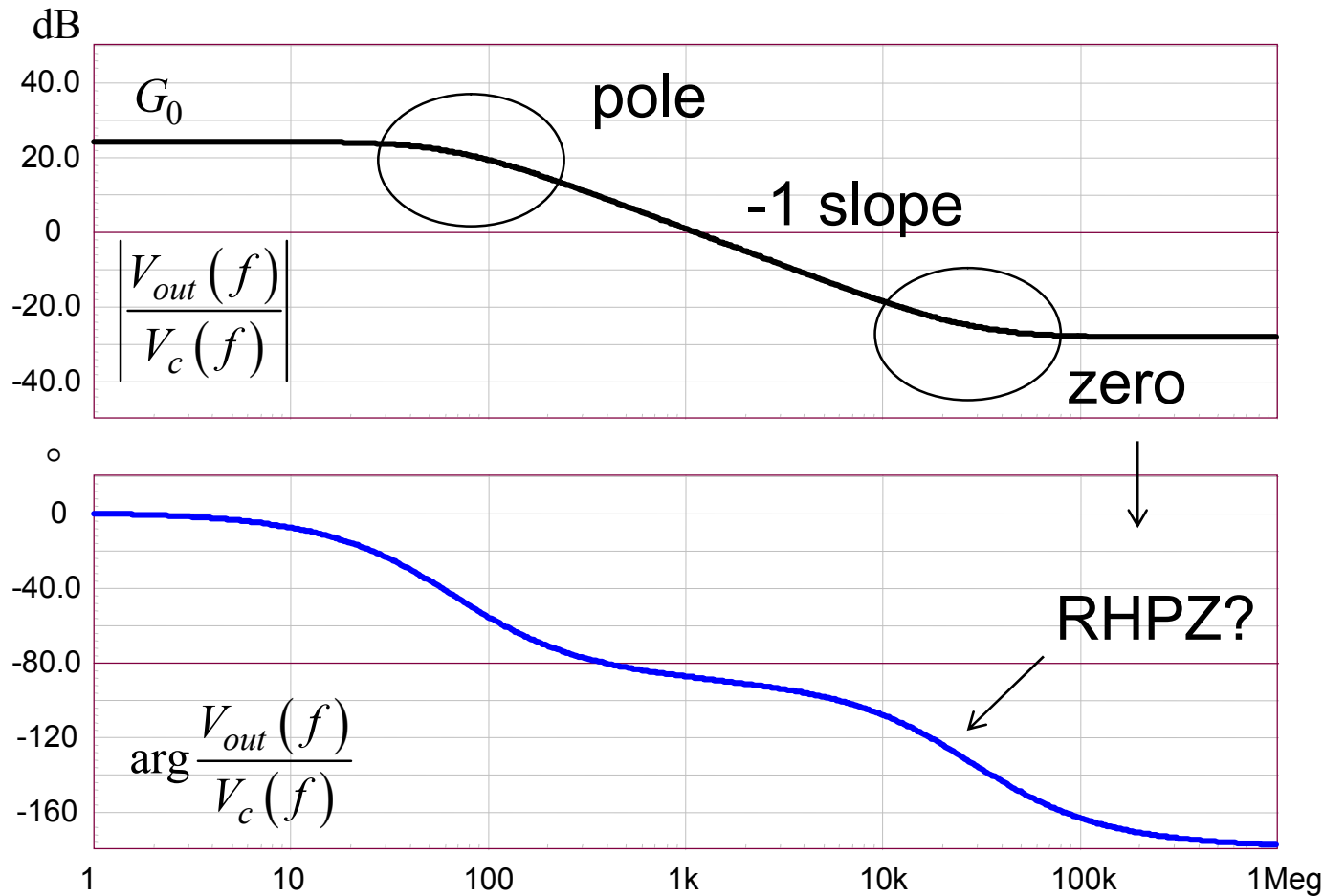- SPICE linearizes the model for us around the bias point



Derive a Small-Signal Model

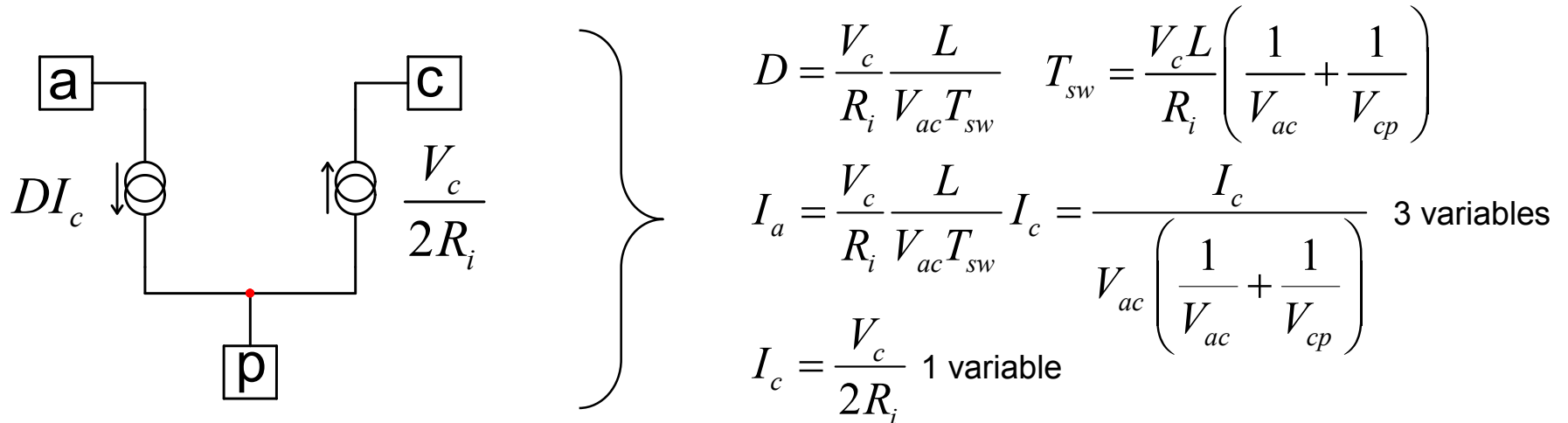- A Quasi Resonant model is built with the PWM switch model



- These are large-signal equations that need linearization

$$I_c = f(V_c) \longrightarrow \hat{i}_c = \frac{\partial I_c(V_c)}{\partial V_c} \hat{v}_c \quad \hat{i}_c = \hat{v}_c \left(\frac{1}{2R_i} \right) = \hat{v}_c k_c \quad k_c = \frac{1}{2R_i}$$

$$\hat{i}_a = \left. \frac{\partial I_a(V_{cp}, V_{ac}, I_c)}{\partial V_{cp}} \right|_{I_c, V_{ac}} \hat{v}_{cp} + \left. \frac{\partial I_a(V_{cp}, V_{ac}, I_c)}{\partial I_c} \right|_{V_{cp}, V_{ac}} \hat{i}_c + \left. \frac{\partial I_a(V_{cp}, V_{ac}, I_c)}{\partial V_{ac}} \right|_{I_c, V_{cp}} \hat{v}_{ac}$$


Large to Small-Signal

- Final steps before the small-signal model

$$\hat{i}_a = \hat{v}_{cp} \frac{I_{c0} V_{ac0}}{(V_{ac0} + V_{cp0})^2} + \frac{V_{cp0}}{V_{cp0} + V_{ac0}} \hat{i}_c - \hat{v}_{ac} \frac{V_{cp0} I_{c0}}{(V_{ac0} + V_{cp0})^2}$$

$$k_{cp} = \frac{I_{c0} V_{ac0}}{(V_{ac0} + V_{cp0})^2} \quad k_{ic} = \frac{V_{cp0}}{V_{cp0} + V_{ac0}} \quad k_{ac} = \frac{V_{cp0} I_{c0}}{(V_{ac0} + V_{cp0})^2}$$

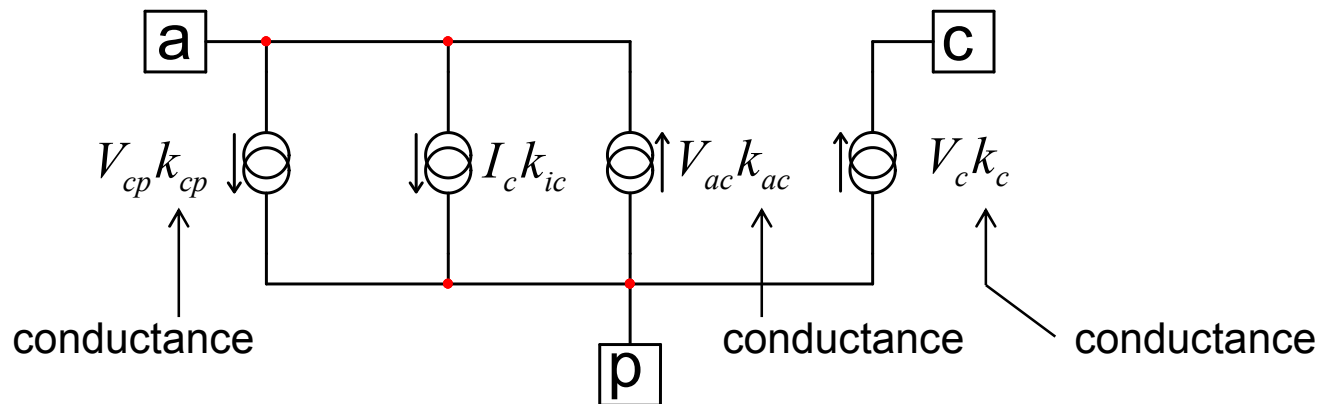- A small-signal model can now be assembled



Always Check the Small-Signal Response



□ Always verify if coefficients are well derived!

parameters

$L=22\mu$
 $R_i=-0.1$


$V_{in}=10$
 $V_{out}=15.6$
 $M=V_{out}/V_{in}$
 $I_c=-2.5$
 $V_{ac}=-10$

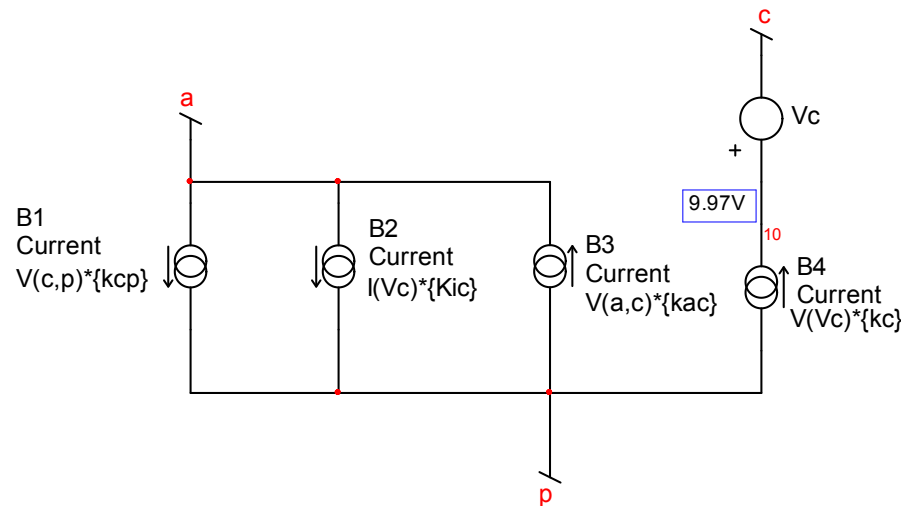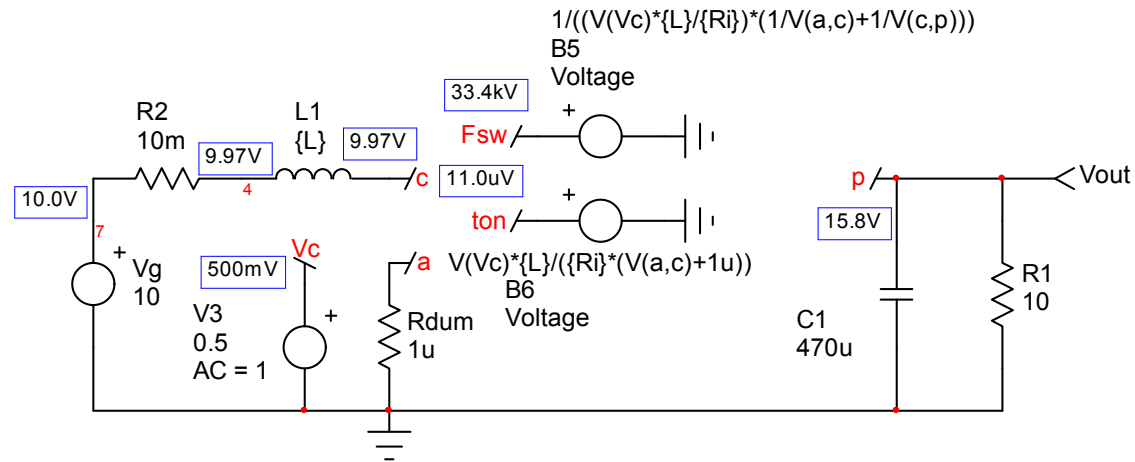$V_{ap}=-V_{out}$
 $V_{cp}=V_{in}-V_{out}$
 $k_{cp}=I_c \cdot V_{ac} / (V_{ac} + V_{cp})^2$
 $k_{ic}=V_{cp} / (V_{cp} + V_{ac})$
 $k_{ac}=V_{cp} \cdot I_c / (V_{ac} + V_{cp})^2$
 $k_c=1 / (2 \cdot R_i)$




A Simple Intermediate Sanity Check

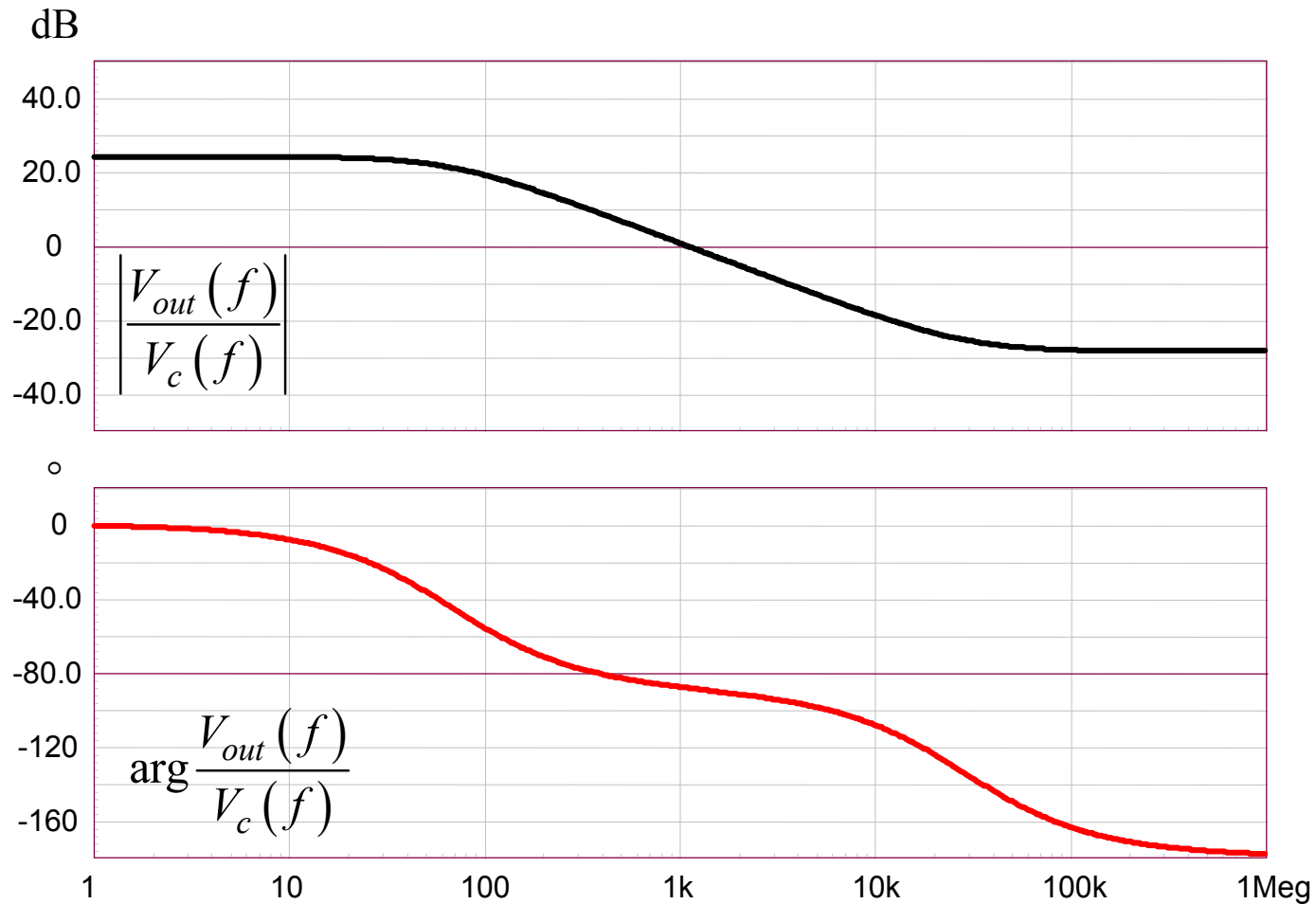- Same response as with the non-linear model: good to go



The Model at Work in the BCM Boost

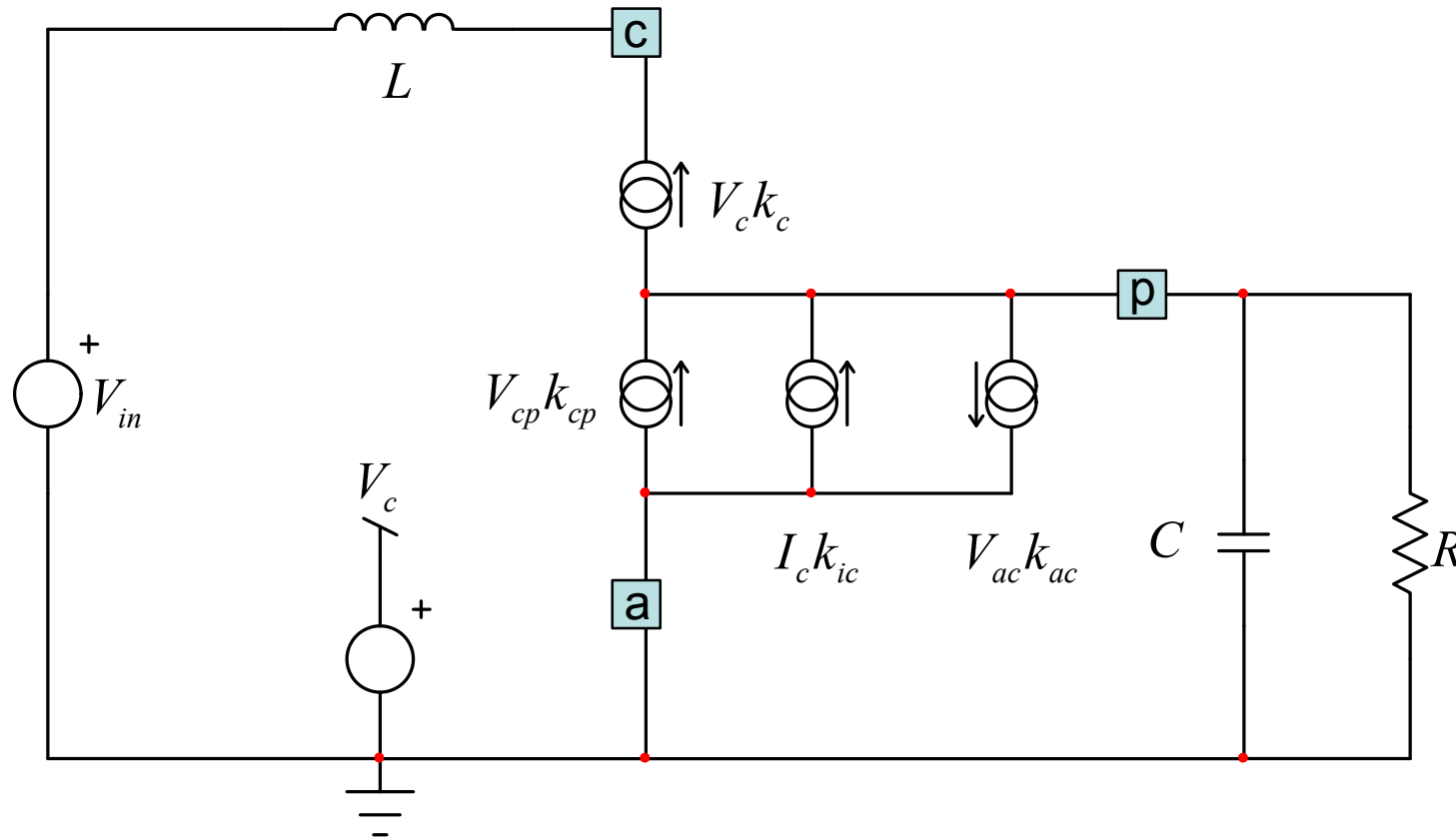- Replace the switch/diode in the boost configuration



- In the original model, I_c leaves node c. It enters it in a boost.

Identify Static Parameters in the Coefficients

- Depending on configurations, update variables in coefficients

$$V_{cp0} = V_{in} - V_{out}$$

$$k_{cp} = \frac{I_{out} V_{out}}{V_{in}} \frac{V_{in}}{(-V_{in} + V_{in} - V_{out})^2}$$


$$I_{c0} = -\frac{I_{out} V_{out}}{V_{in}}$$



$$k_{ac} = -\frac{I_{out} V_{out}}{V_{in}} \frac{(V_{in} - V_{out})}{(-V_{in} + V_{in} - V_{out})^2}$$

$$V_{ac0} = -V_{in}$$
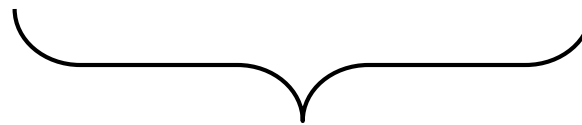
$$k_{ic} = \frac{V_{in} - V_{out}}{V_{in} - V_{out} - V_{in}}$$



$$k_{cp} = \frac{1}{R}$$


$$k_{ac} = \frac{M}{R} - \frac{1}{R}$$

$$k_{ic} = 1 - \frac{1}{M}$$

$$k_c = \frac{1}{2R_i}$$

First Step is Dc Gain

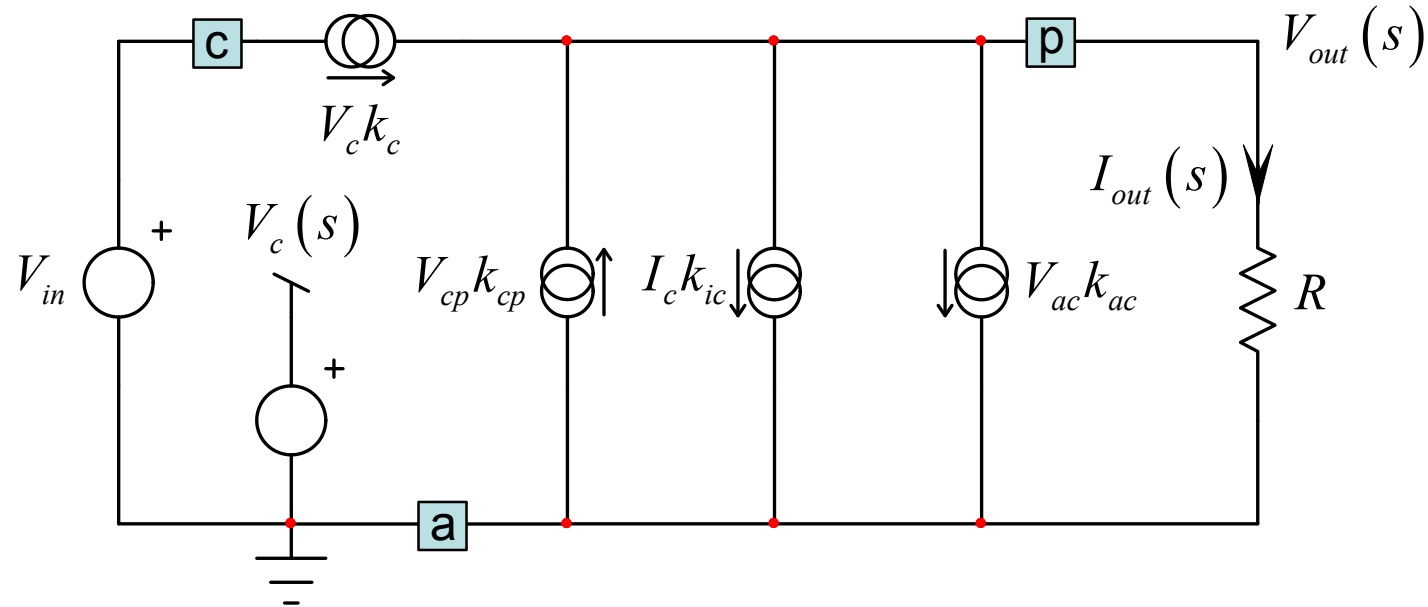- Open the output capacitor, short the inductor



- Write output voltage expression

$$I_{out}(s) = V_c(s)k_c + V_{cp}(s)k_{cp} - I_c(s)k_{ic} - V_{ac}(s)k_{ac}$$

$$\rightarrow I_{out}(s) = V_c(s)k_c + \left(\cancel{V_c(s)} - V_{(p)}(s) \right) k_{cp} - V_c(s)k_c k_{ic} - \left(\cancel{V_c(s)} - \cancel{V_{(c)}}(s) \right) k_{ac}$$

Dc Gain Derivation

□ There is no contribution from the source, $V_{in}(s) = 0$

$$I_{out}(s) = V_c(s)k_c - V_{out}(s)k_{cp} - V_c(s)k_c k_{ic} = V_c(s)k_c(1 - k_{ic}) - V_{out}(s)k_{cp}$$

$$I_{out}(s) = \frac{V_{out}(s)}{R} \longrightarrow V_c(s)k_c(1 - k_{ic}) = V_{out}(s)\left(k_{cp} + \frac{1}{R}\right)$$

$$\frac{V_{out}(s)}{V_c(s)} = \frac{k_c(1 - k_{ic})}{k_{cp} + \frac{1}{R}} \quad \Longrightarrow \quad H_0 = \frac{R}{4MR_i}$$


□ We have the first term of our transfer function

$$\frac{V_{out}(s)}{V_c(s)} = H_0 \frac{1 + \frac{s}{s_{z_1}}}{1 + \frac{s}{s_{p_1}}}$$



Deriving the Zero Position

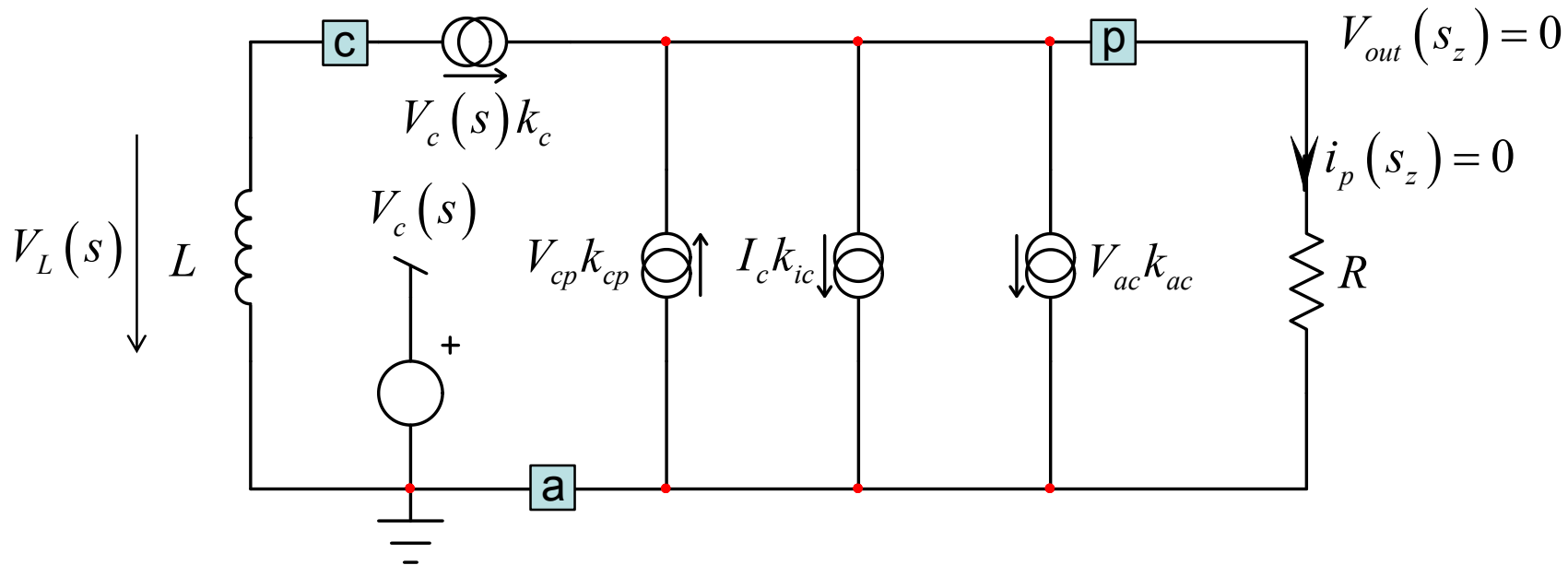- For the zero, the stimulus does not reach the output
 - current in the resistance is 0, node p voltage is also 0



- All the inductor ac current is absorbed before reaching R

$$V_c(s)k_c + [V_{(c)}(s) - V_{(p)}(s)]k_{cp} = V_c(s)k_c k_{ic} + [V_{(a)}(s) - V_{(c)}(s)]k_{ac}$$

What is the Root to $N(s) = 0$?

- The voltage at node c depends on the inductance

$$V_{(c)}(s) = -V_L(s) = -I_c(s)sL = -V_c(s)k_c sL$$

- Substitute in the previous equations and simplify

$$\cancel{V_c(s)k_c} - \cancel{V_c(s)k_c} sLk_{cp} = \cancel{V_c(s)k_c} k_{ic} + \cancel{V_c(s)k_c} sLk_{ac}$$

- Solve for s , this is the zero position

$$1 - k_{ic} = sL(k_{ac} + k_{cp}) \quad \longrightarrow \quad s_{z_1} = \frac{1 - k_{ic}}{L(k_{ac} + k_{cp})} \quad \begin{array}{l} \text{Substitute} \\ k_{ic}, k_{ac}, k_{cp} \end{array}$$


- The root is positive, this is a Right Half Plane Zero

$$s_{z_1} = \frac{R}{LM^2}$$



For the Pole, Reduce Excitation to 0

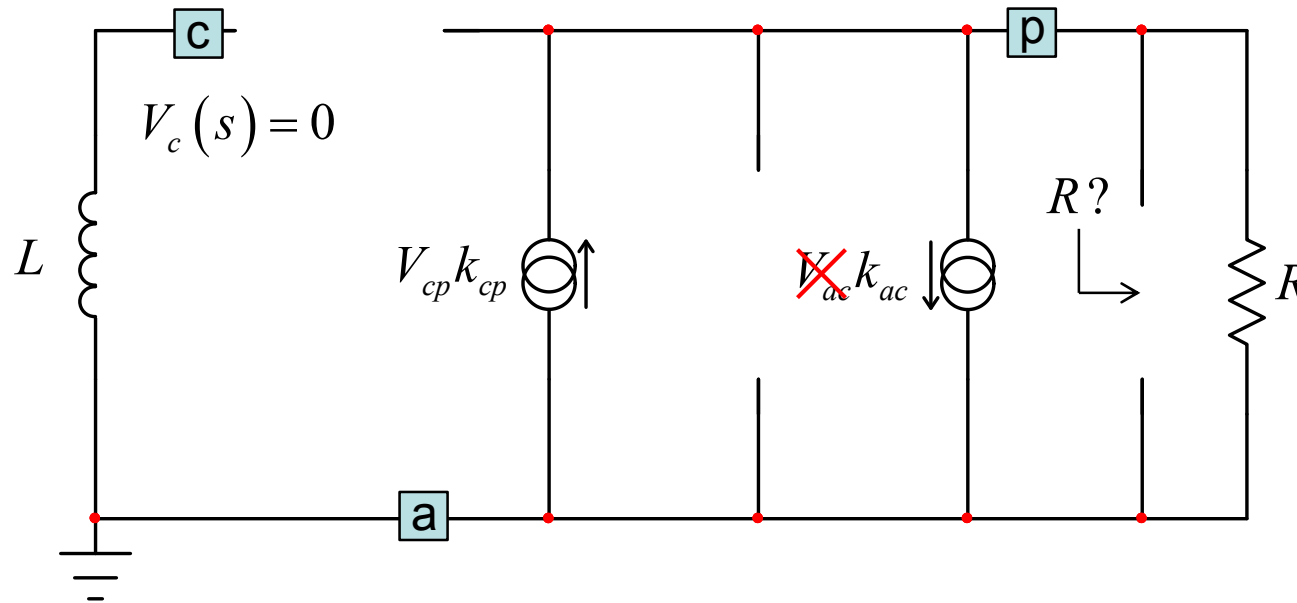- Excitation is V_c : all current sources $f(V_c)$ are open




- Look for the resistance “seen” by the capacitor C
- The source $V_{cp}k_{cp}$ can be reworked

$$\hat{v}_c = 0 \rightarrow V_{cp}(s)k_{cp} = -V_p(s)k_{cp} = -\frac{V_{out}(s)}{R} \rightarrow \text{Replace by a resistance } R$$

A Really Simple Circuit

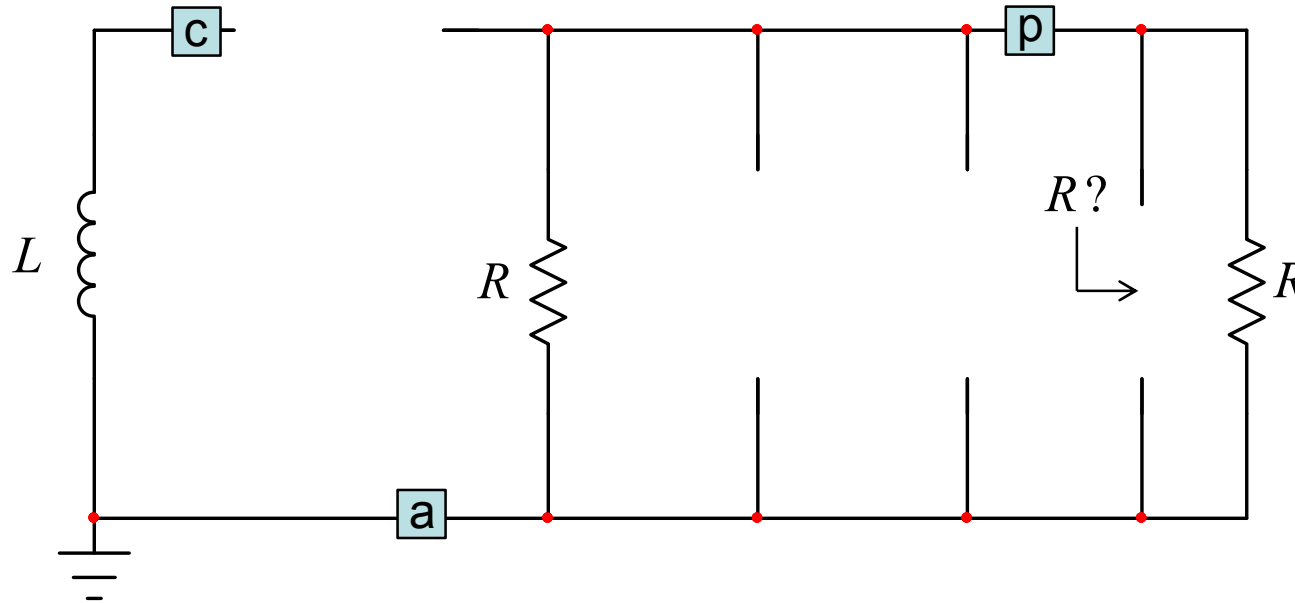- Difficult to beat in terms of problem solving



- The pole due to the capacitor comes immediately


$$R? = R \parallel R = \frac{R}{2} \longrightarrow \tau = \frac{R}{2}C \longrightarrow s_{p_1} = \frac{2}{RC}$$

The Complete Expression is Ready

□ With a few steps, we have our transfer function

$$\frac{V_{out}(s)}{V_c(s)} = H_0 \frac{1 - \frac{s}{\omega_{z_1}}}{1 + \frac{s}{\omega_{p_1}}} \quad H_0 = \frac{R}{4MR_i} \quad \omega_{p_1} = \frac{2}{RC} \quad \omega_{z_1} = \frac{R}{LM^2}$$

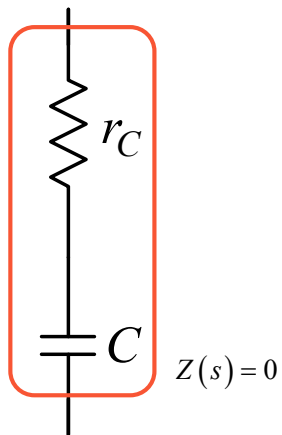
□ We can easily add the capacitor ESR contribution



$$\left. \begin{aligned} r_C + \frac{1}{sC} &= \frac{sr_C C + 1}{sC} \\ sr_C C + 1 &= 0 \\ \omega_{z_2} &= \frac{1}{r_C C} \end{aligned} \right\} \Rightarrow \frac{V_{out}(s)}{V_c(s)} = H_0 \frac{\left(1 - \frac{s}{\omega_{z_1}}\right) \left(1 + \frac{s}{\omega_{z_2}}\right)}{1 + \frac{s}{\omega_{p_1}}}$$

Time to Confront Mathcad® with SPICE!

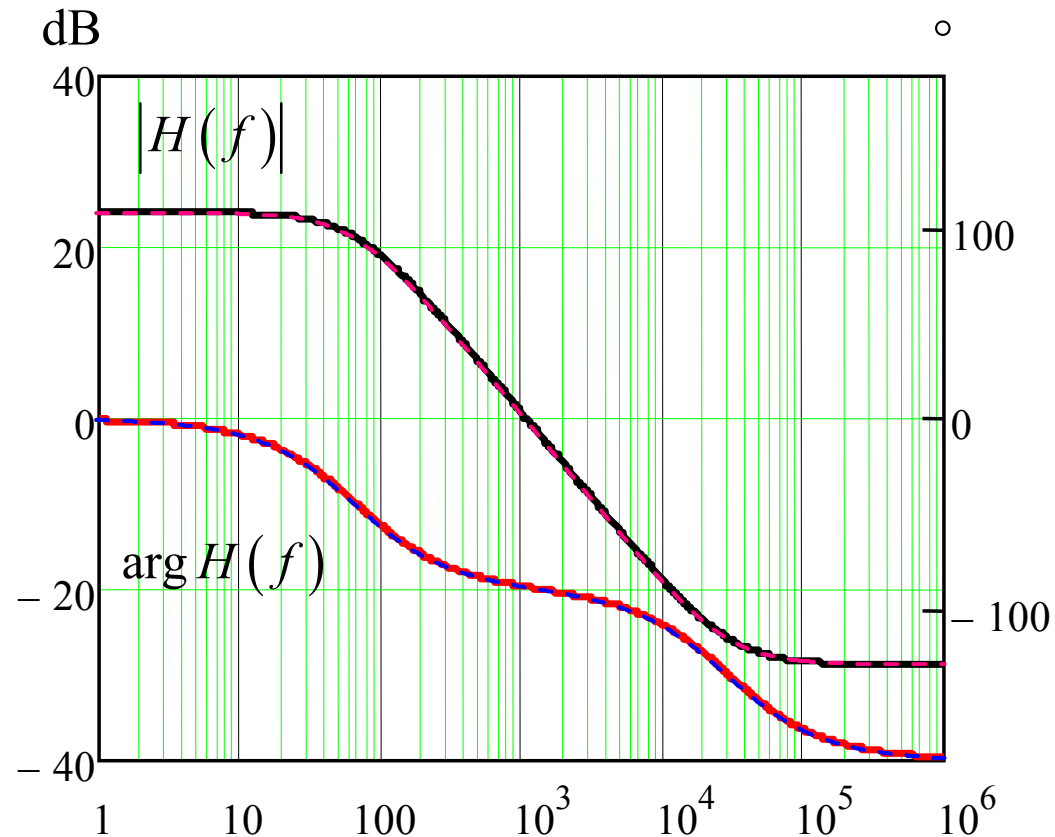- If equations are correct, curves must superimpose perfectly



- The BCM boost response in CM is first-order with RHPZ


Course Agenda

- ❑ Introducing the PWM Switch Model
- ❑ CCM, DCM and BCM in Voltage Mode
- ❑ Pulse Width Modulator Gain
- ❑ The PWM Switch Model in Current Mode
- ❑ PWM Switch at Work in a Buck Converter
- ❑ A Simplified Approach to Modeling a DCM Boost
- ❑ Transfer Function of a BCM Boost in Current Mode
- ❑ **Small-Signal Model of The Active Clamp Forward**



Active Clamp Forward in Voltage Mode

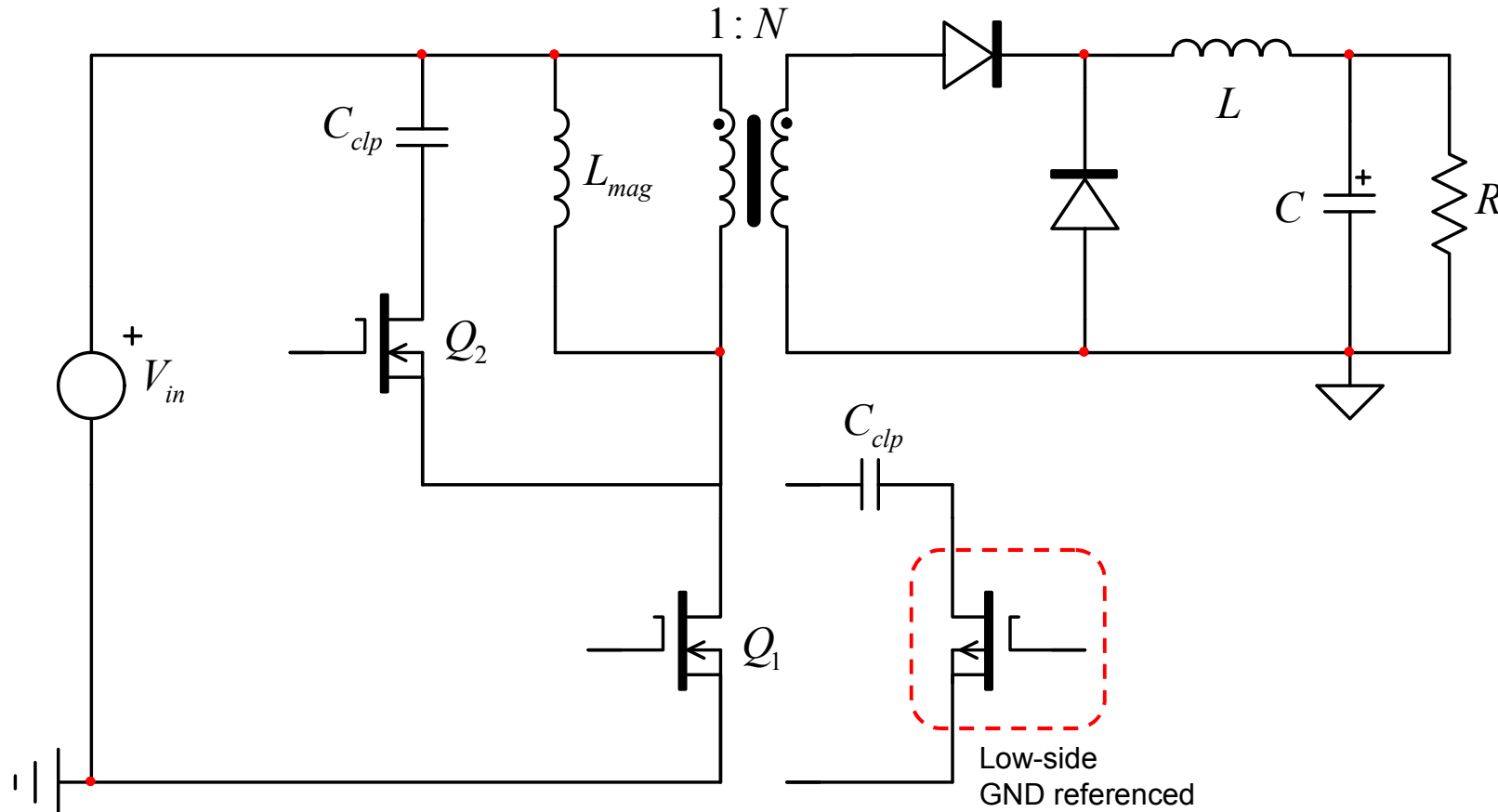
- An Active Clamp Forward (ACF) is a forward converter...



- ...featuring a controlled-upper-side switch for ZVS operations

Control Strategy

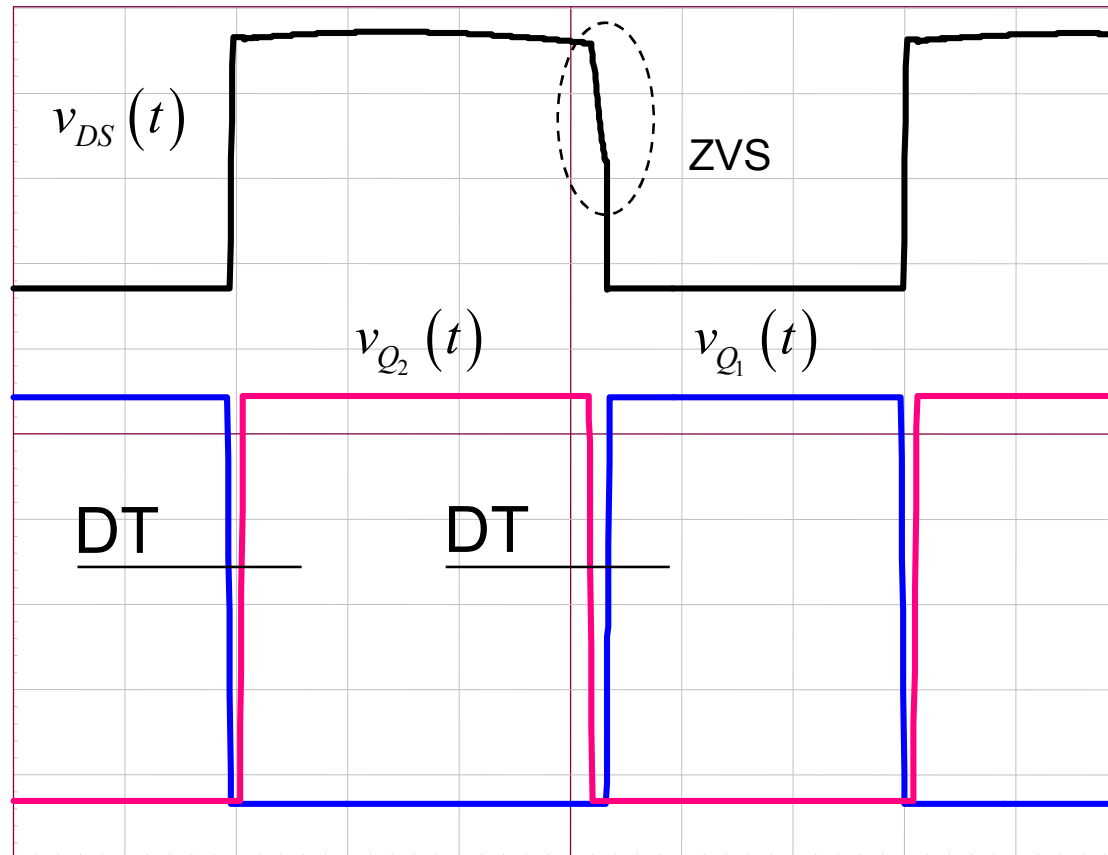
- A deadtime is inserted to let V_{DS} swing towards grounds



- Quasi-ZVS can be implemented on the drain voltage

Active Clamp Forward in Voltage Mode

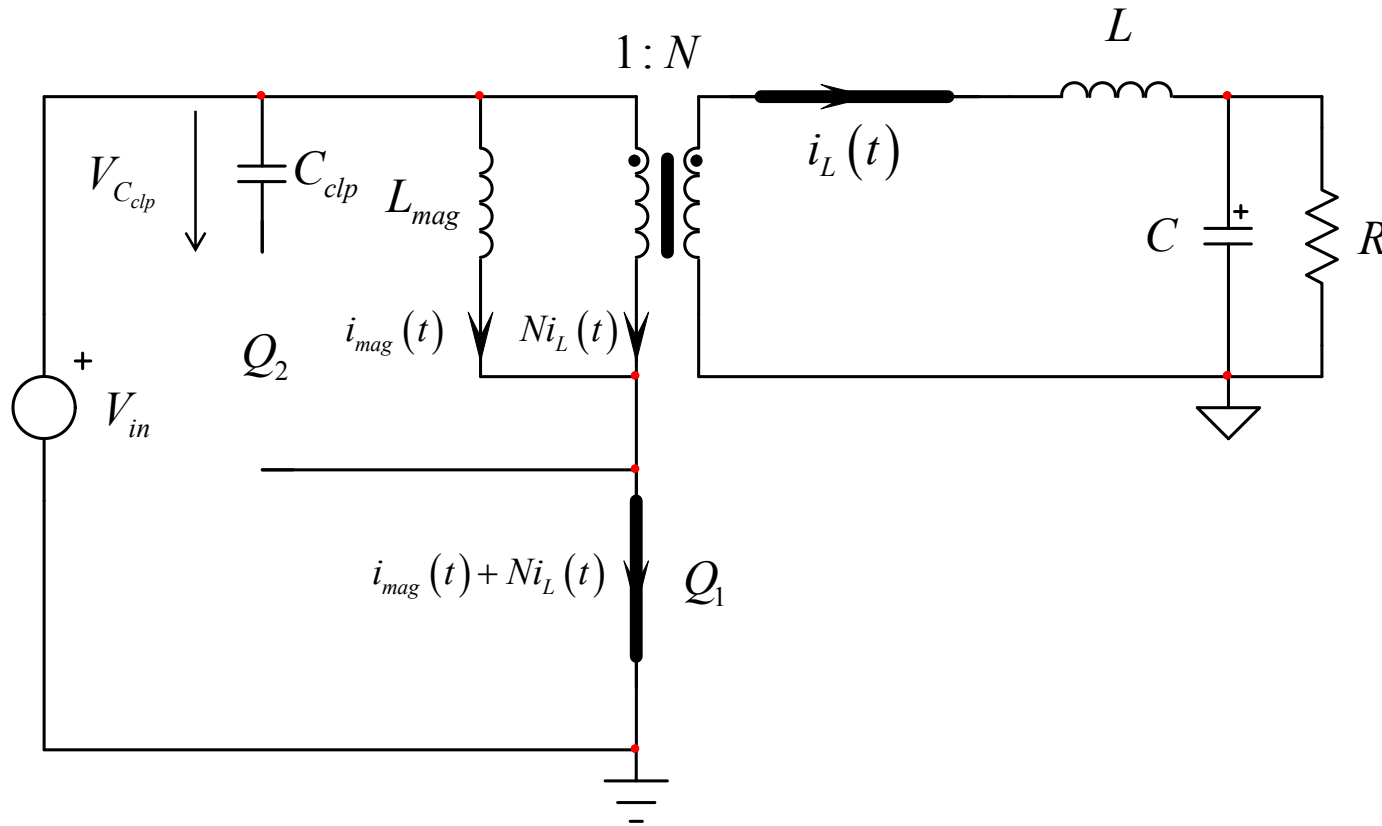
- Energy is stored in the magnetizing inductance at turn on



- We need to offer a path at turn off to demagnetize the core

Magnetizing Current Resonates

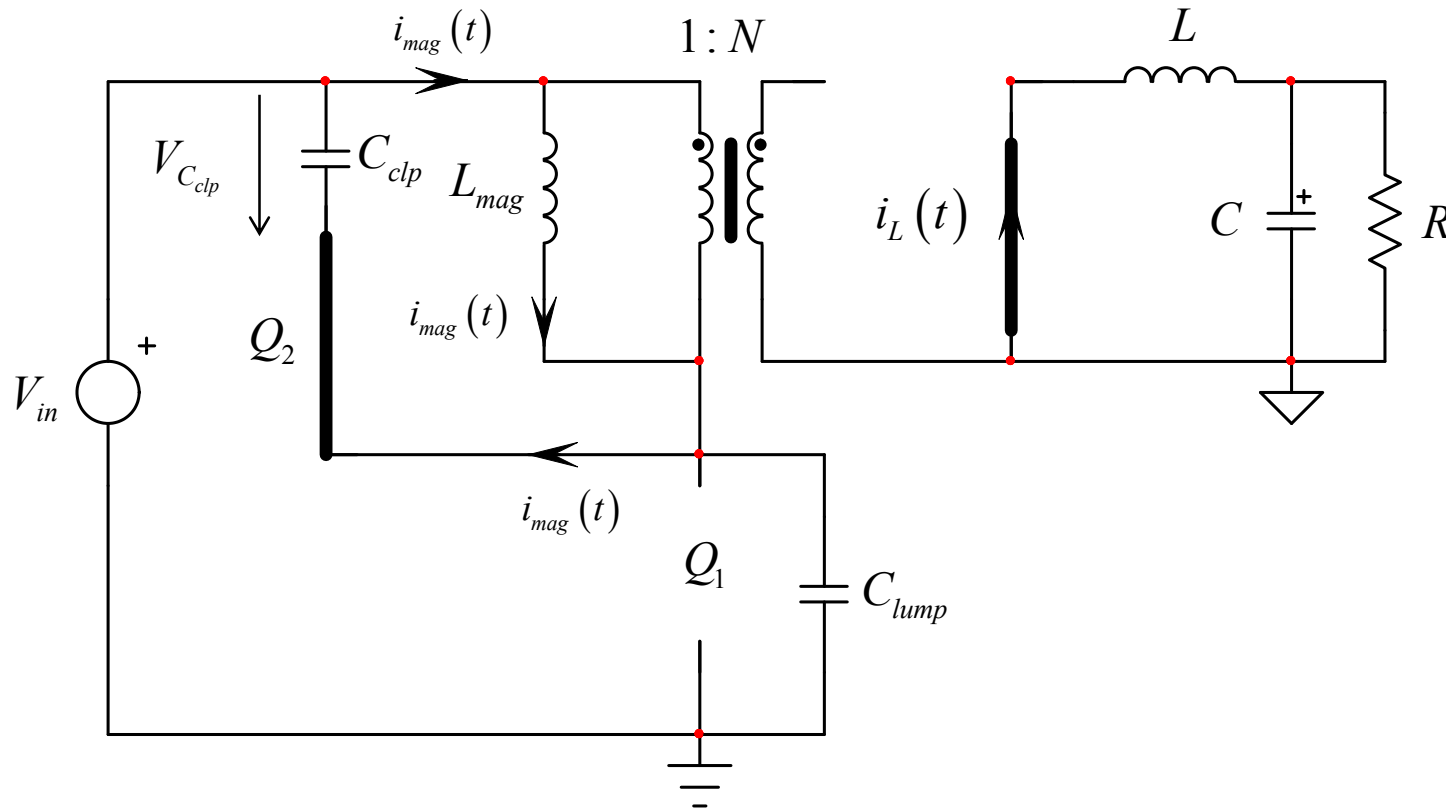
- The upper-side MOSFET switches on with delay: ZVS



- Magnetizing current decreases to 0 then reverses

Deadtime Gives Quasi-ZVS Operation

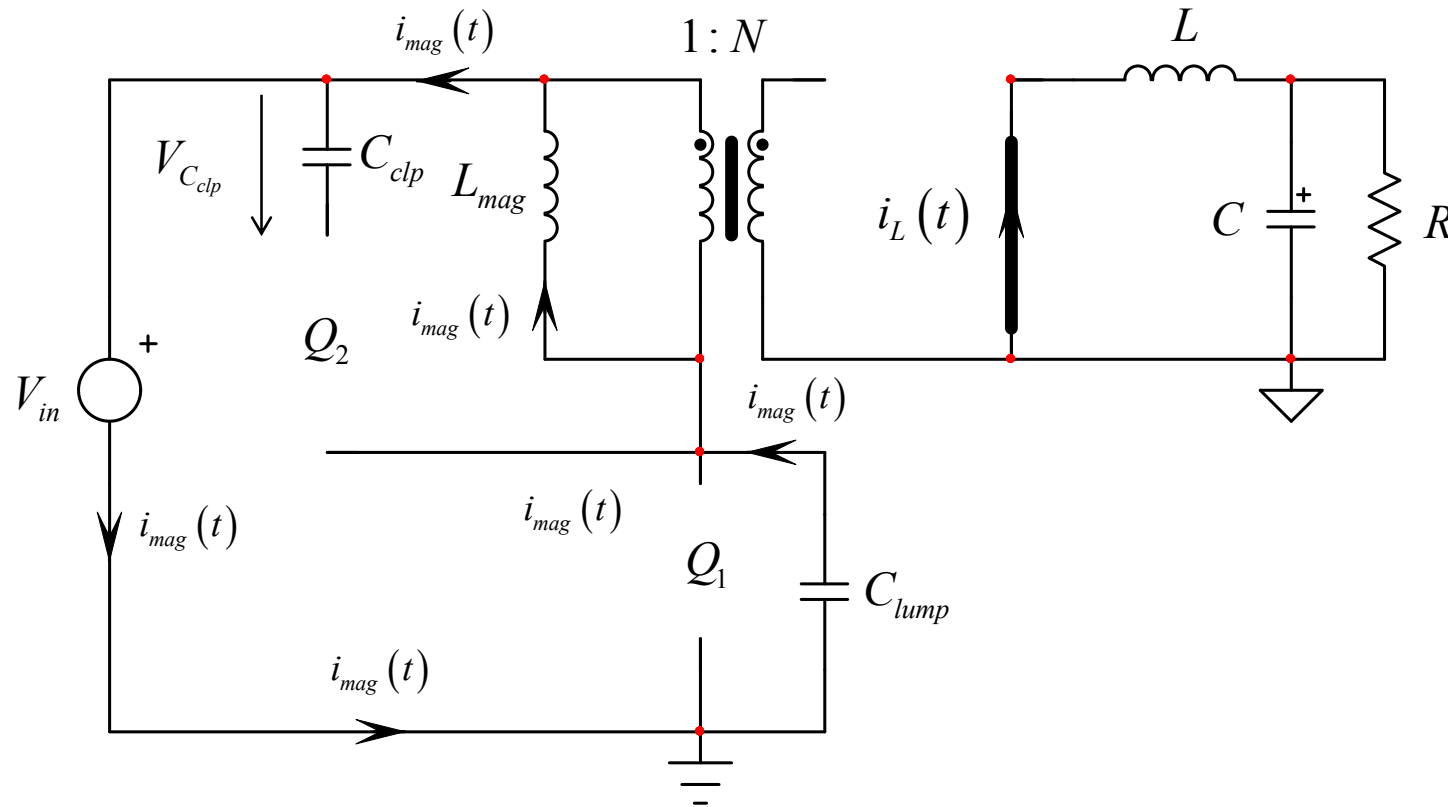
- The deadtime lets magnetizing current reach $-I_{mag,peak}$



- At this moment, Q_2 opens and current discharges C_{lump}

Full ZVS at Nominal Power is Difficult

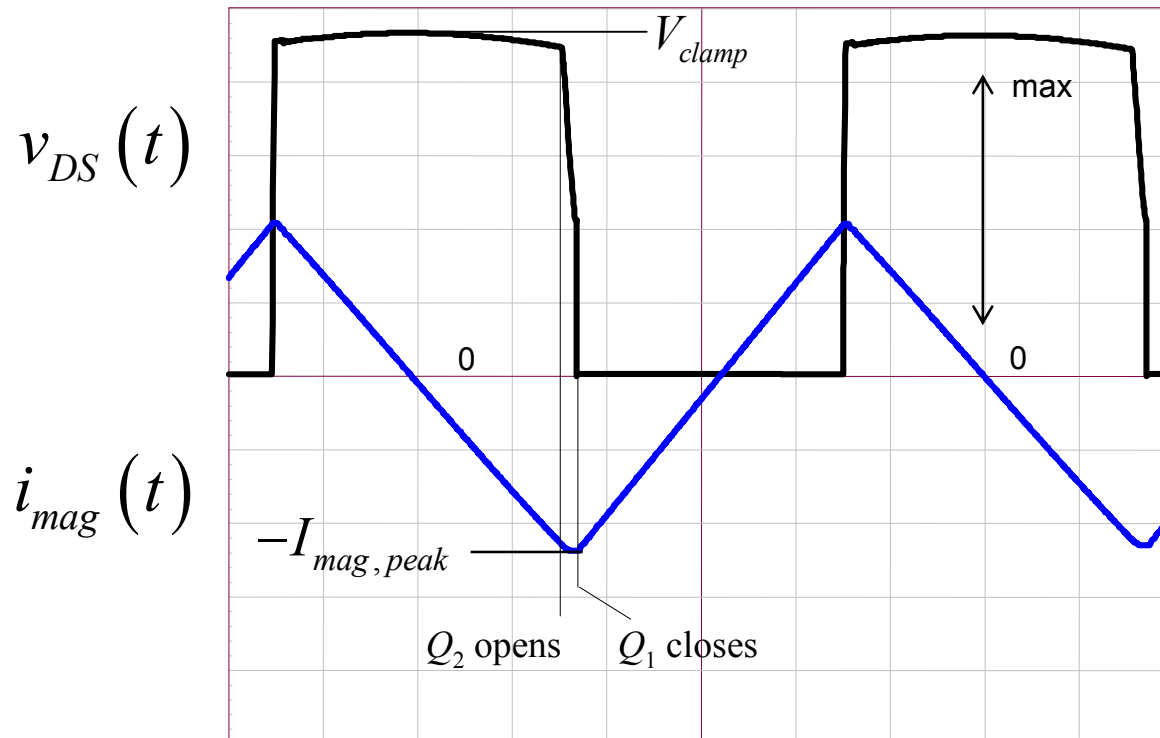- True ZVS is difficult to reach, quasi-ZVS is usually obtained



True ZVS



$$\frac{1}{2} L_{mag} (I_{mag,peak-} - NI_L)^2 > \frac{1}{2} C_{lump} V_{in}^2$$




Building an Ac Model

- ❑ A model can be built following different methods
 - ❖ Write large-signal equations of voltages and currents
 - ❖ Assemble sources to build a large-signal model
 - ❖ Linearize expressions and derive transfer functions
- Reveal the presence of the PWM Switch model
- Implant its already-available small-signal model
- Solve for the transfer function expression
- ❑ Both approaches have pros and cons
- ❑ Going along both paths helps to cross-check results




Identify PWM Switches Pair

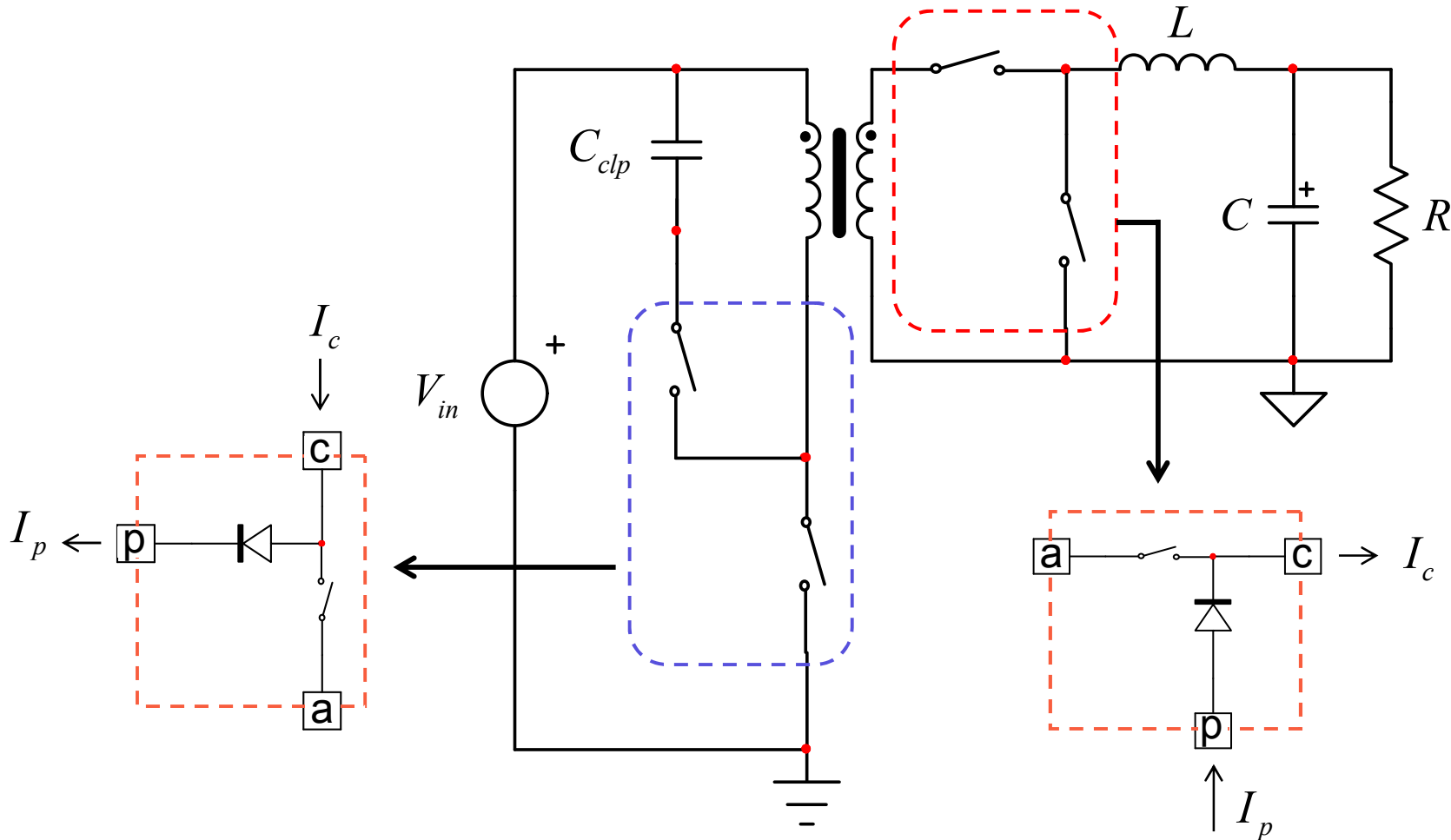- A pair of switches appear in primary and secondary sides




Primary-Side PWM Switch Model

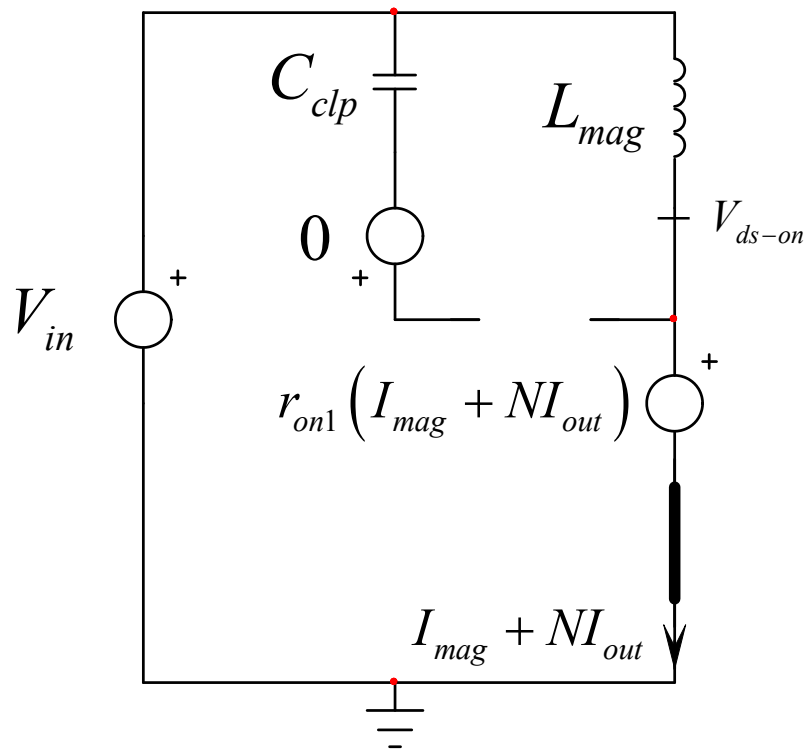- Identify currents and voltages during transitions



During the on-time DT_{sw}
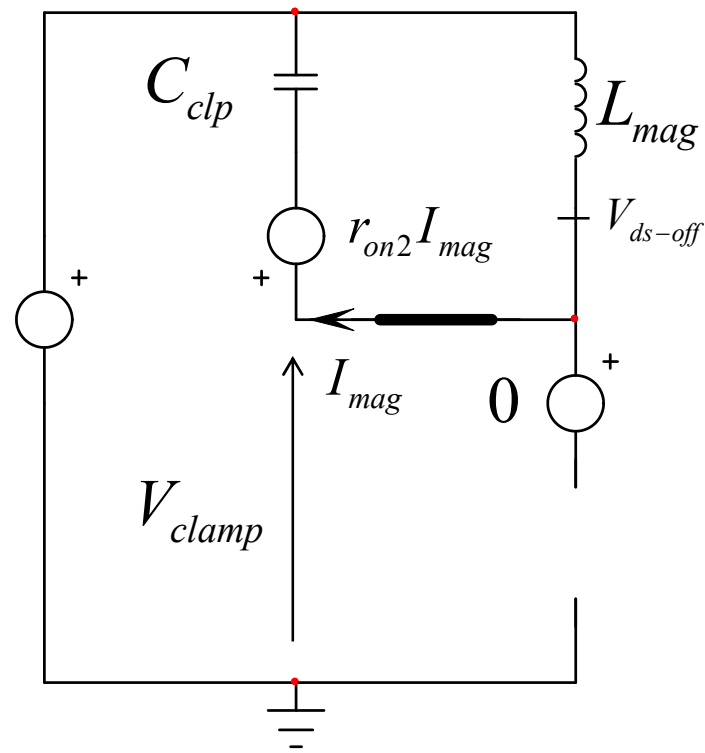
$$\langle v_{DS-on}(t) \rangle_{DT_{sw}} = (I_{mag} + NI_{out})r_{on1}$$




During the off-time $(1-D)T_{sw}$

$$\langle v_{DS-off}(t) \rangle_{(1-D)T_{sw}} = V_{in} + V_C + r_{on2}I_{mag}$$


The First PWM Switch Model is Here

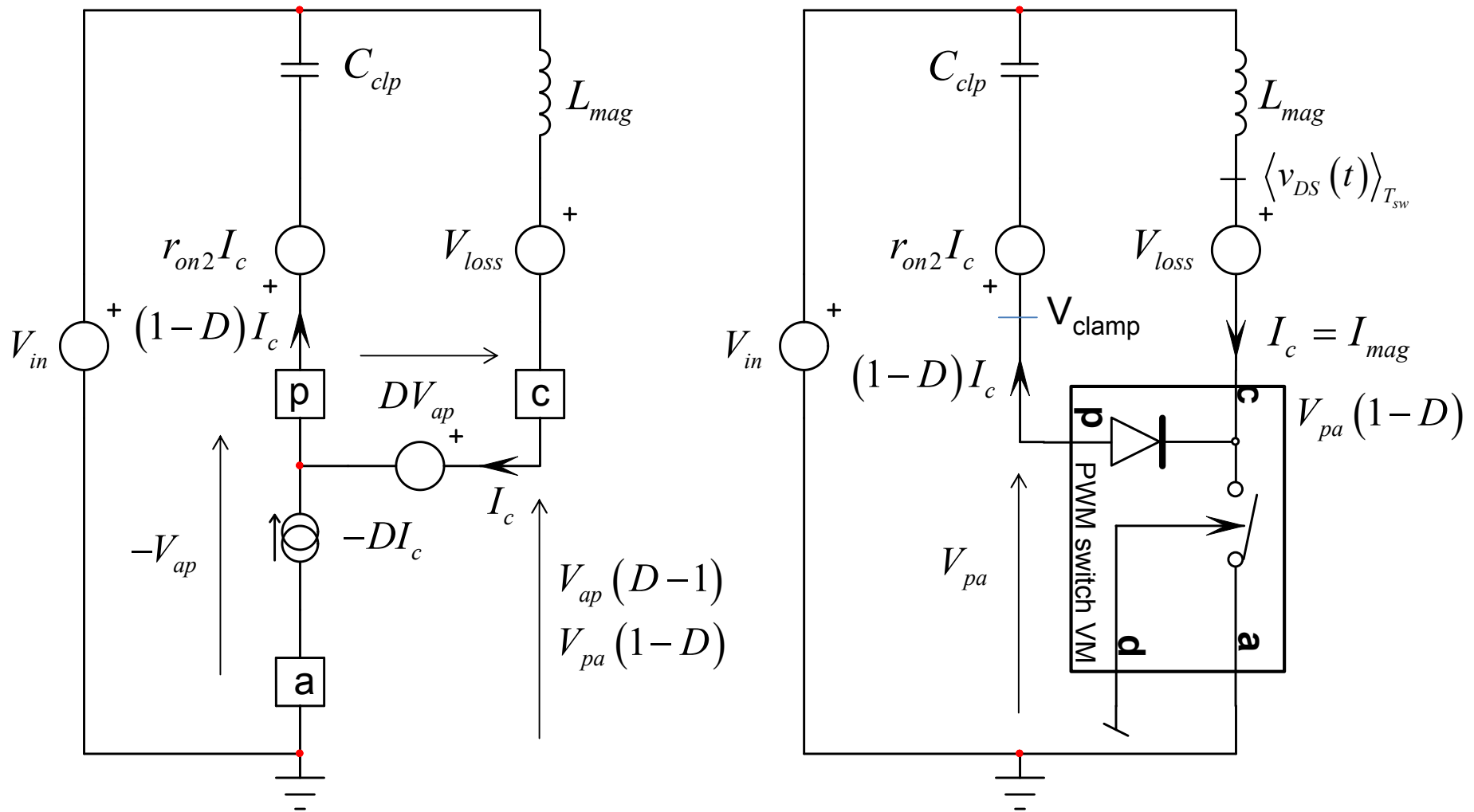- ❑ Connect the PWM Switch the right way, check polarities




Secondary-Side PWM Switch Model

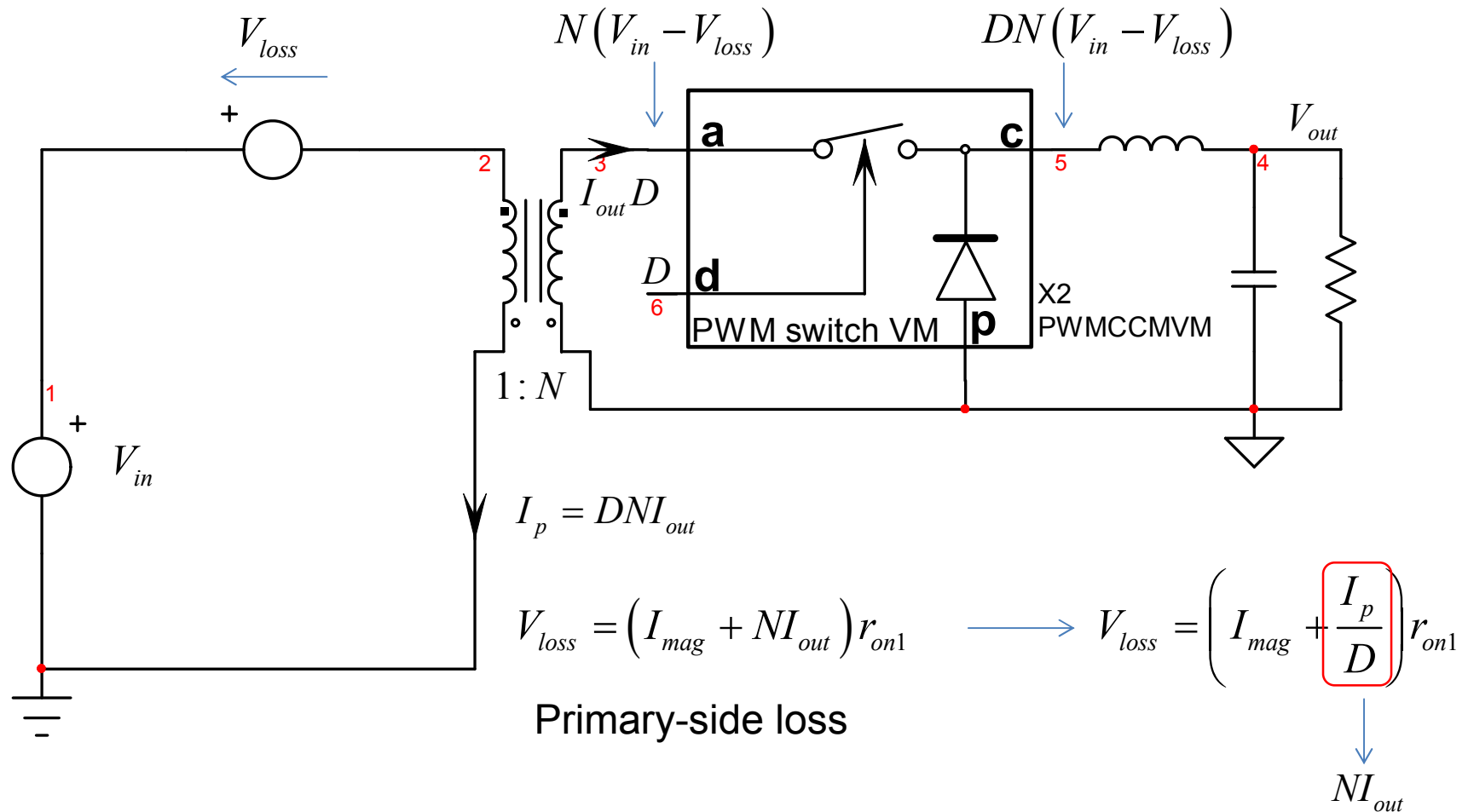- The forward converter is a buck-derived topology



Check the Dual-PWM Switch Response

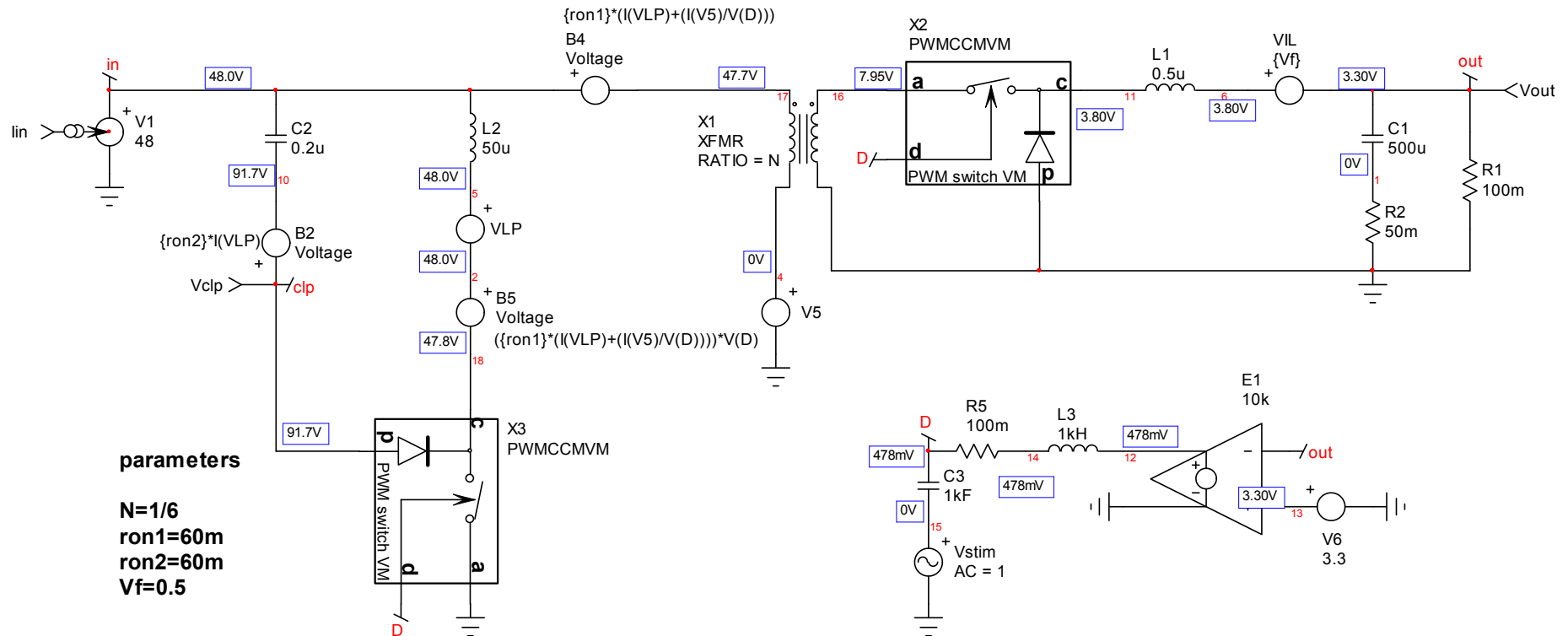
- ❑ Compare ac response with that of the large-signal version



- ❑ Check first if dc operating points are similar
- ❑ Use this fixture to also run transient simulations

Large-Signal Equations with SPICE

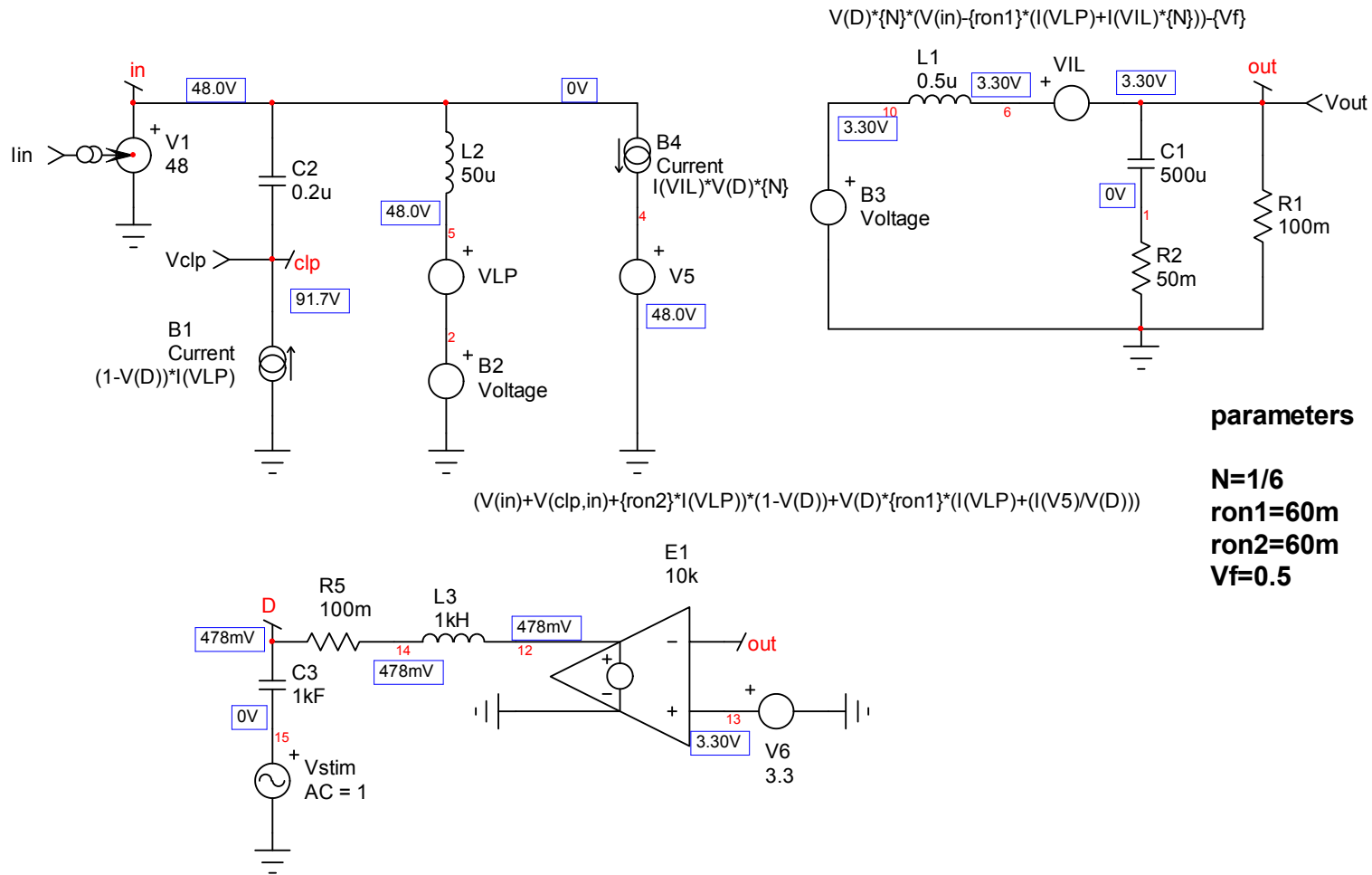□ Non-linear equations are linearized by SPICE




Proposed by Dr. José Capilla, ON Semi, November 2012




Curves Perfectly Superimpose


$$\left| \frac{V_{out}(f)}{D(f)} \right|$$

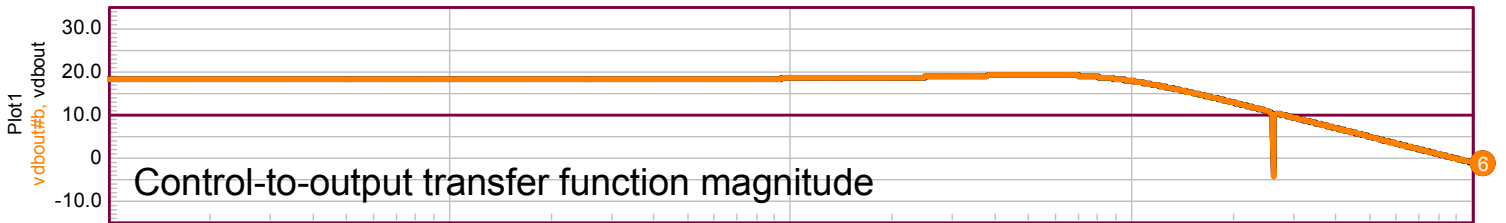


$$\left| \frac{V_{clamp}(f)}{D(f)} \right|$$

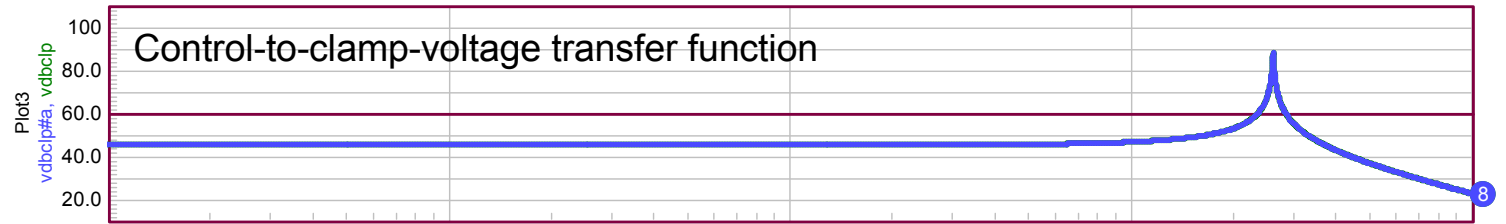

$$\left| \frac{I_{in}(f)}{D(f)} \right|$$

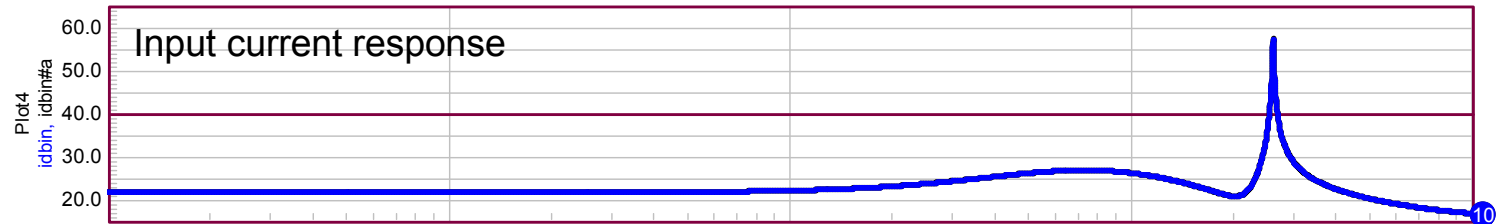


$$\angle \frac{V_{out}(f)}{D(f)}$$

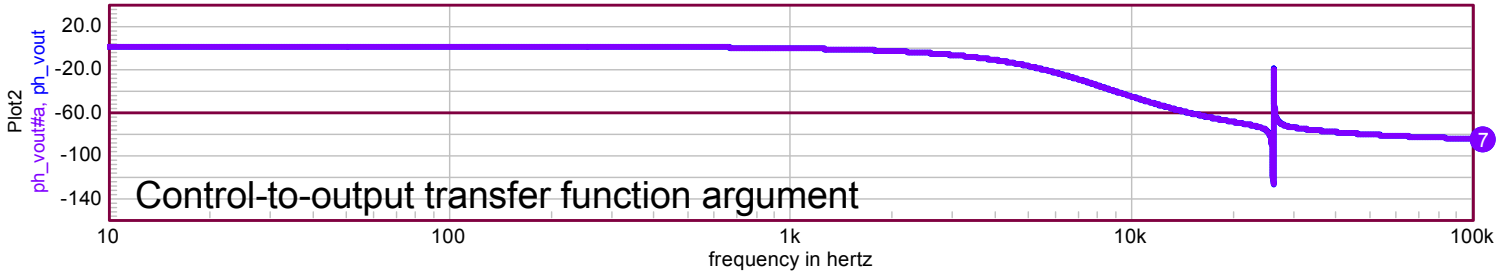


Compare Transient Responses

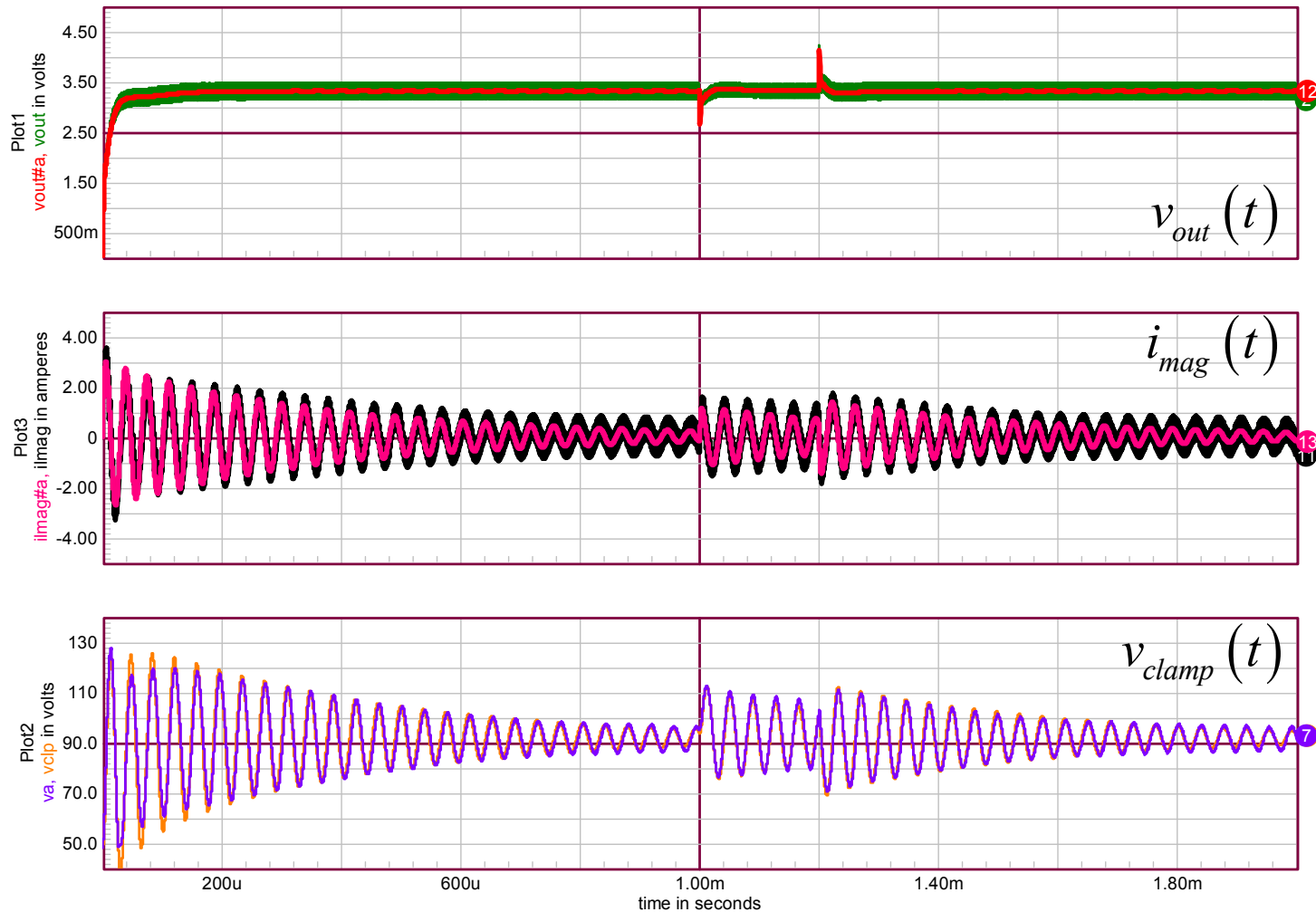- Cycle-by-cycle results are similar to that of average model



Simulate with Small-Signal Sources

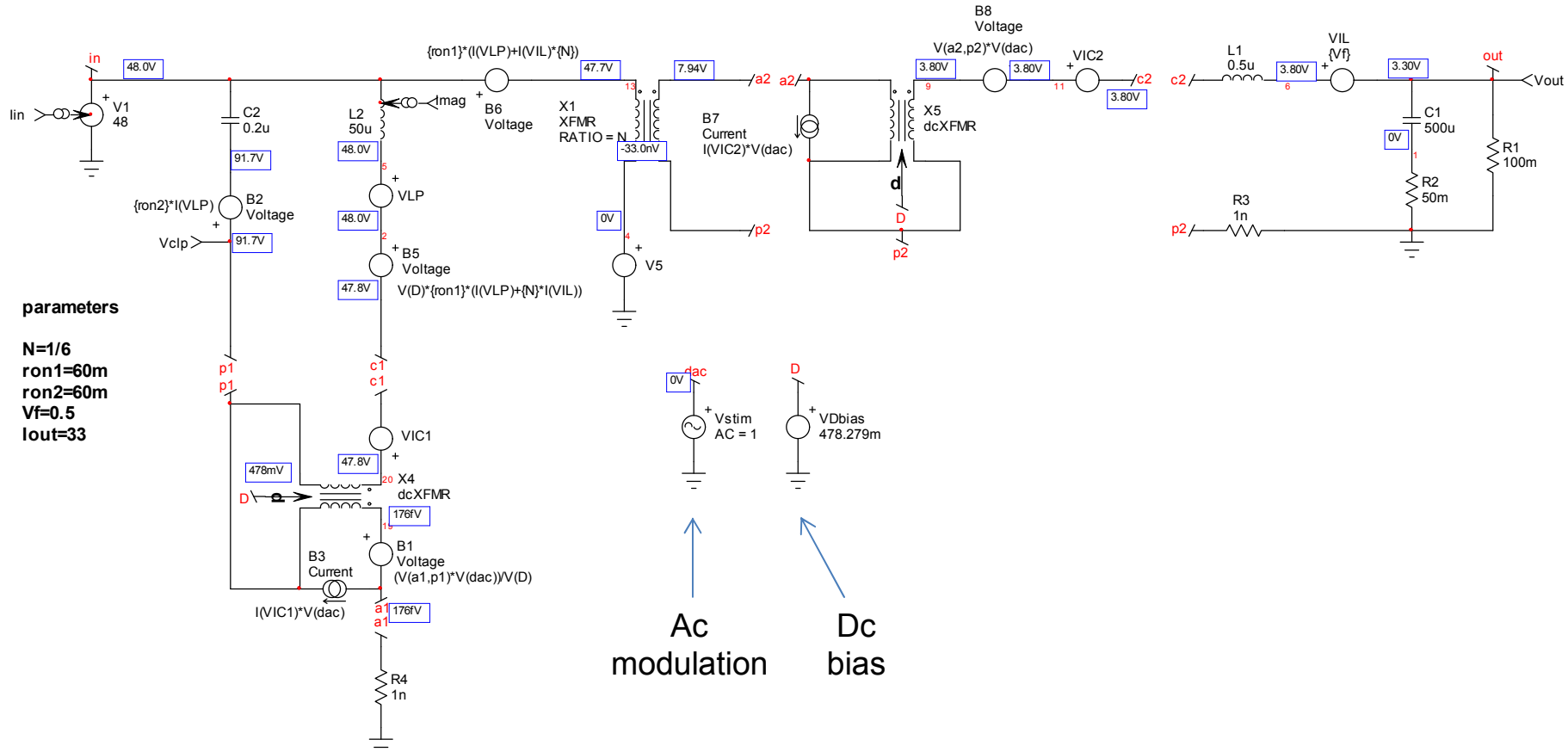
❑ Plug the small-signal models of the PWM Switch in



❑ Check if ac response is ok before proceeding!


❑ Simplify circuitry to concentrate on control-to-output only

Same Response Between Fixtures

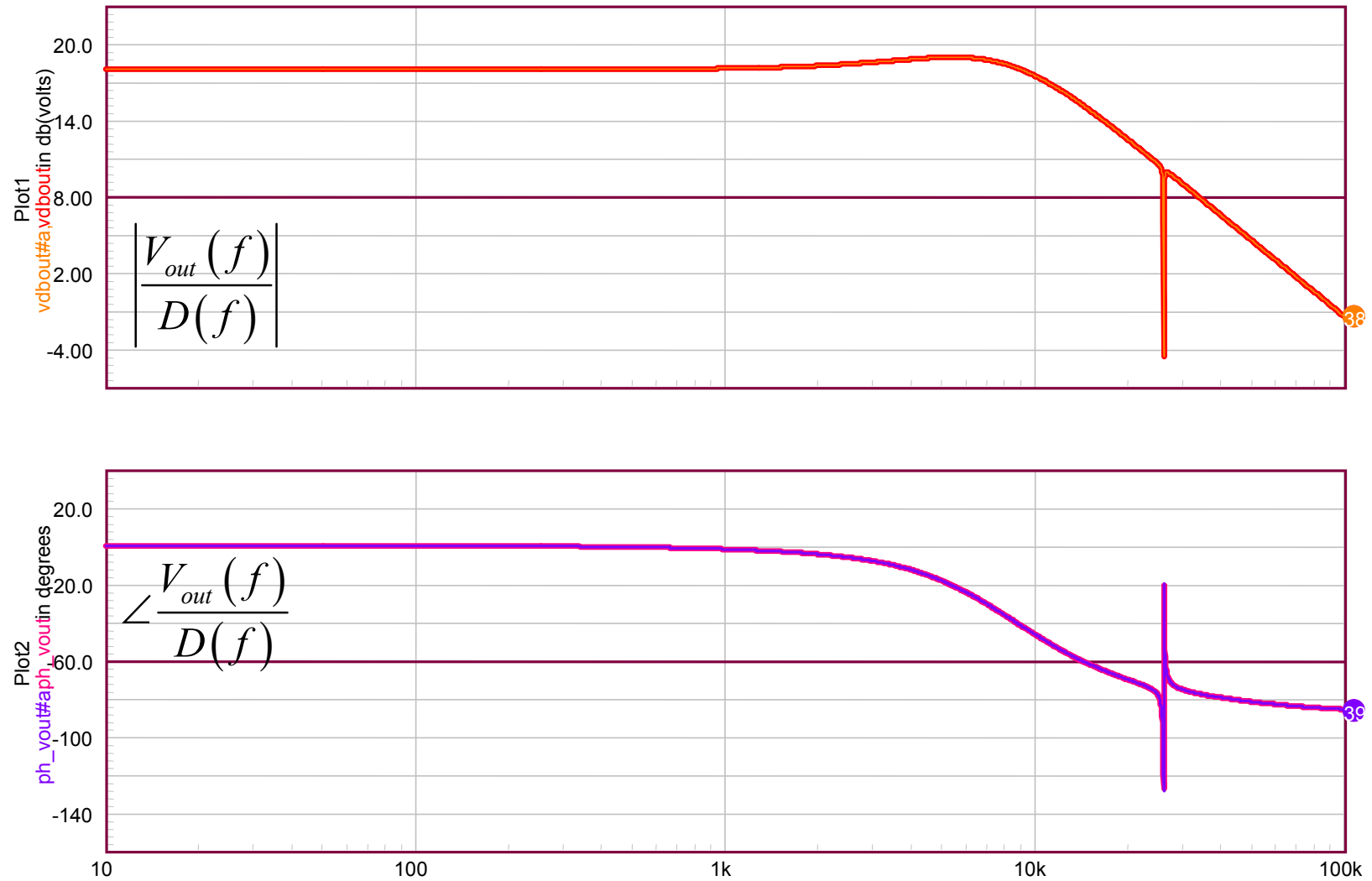

Make the Circuit Look Friendlier

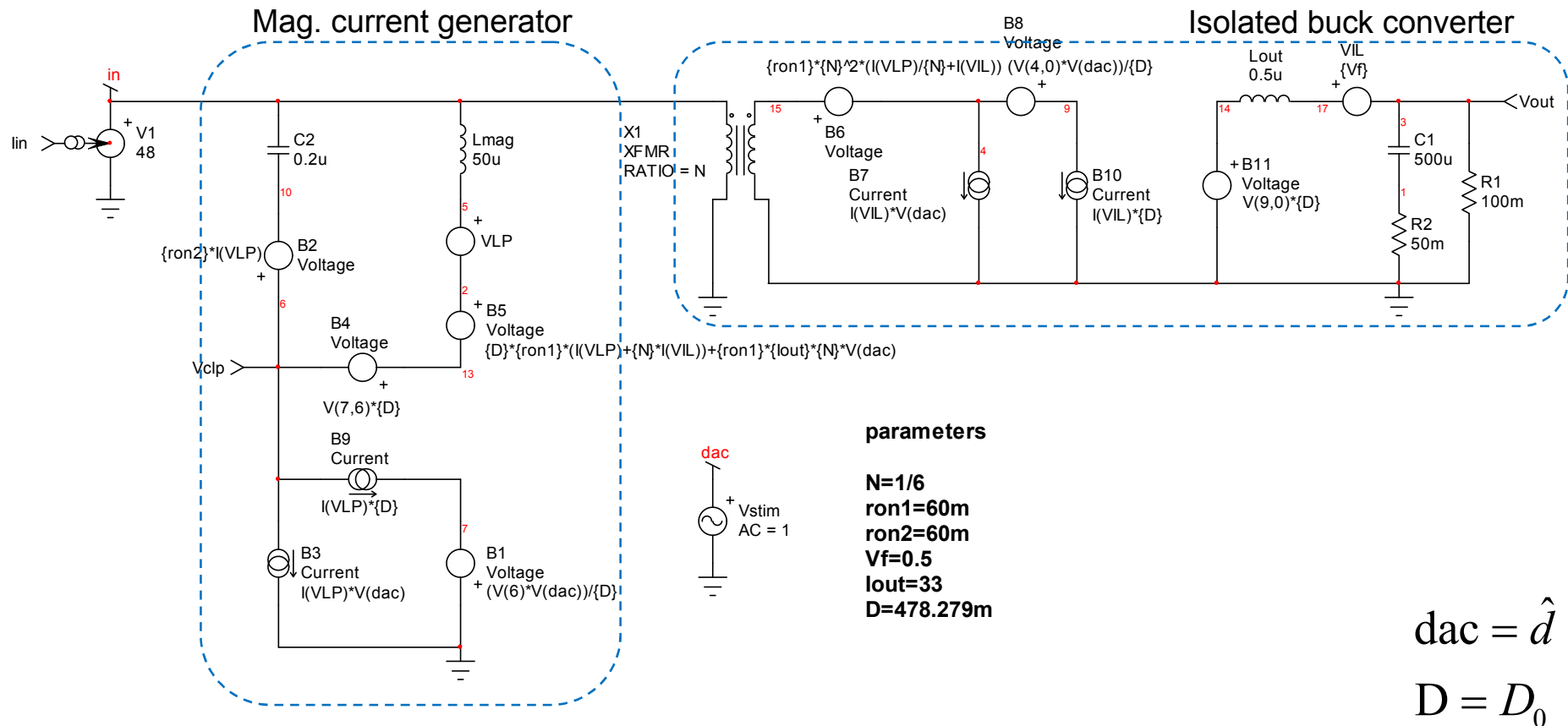- ❑ Re-arrange sources to simplify the electrical circuit




- ❑ Run a sanity check further to any simplification



Circuit is Looking Simpler Now

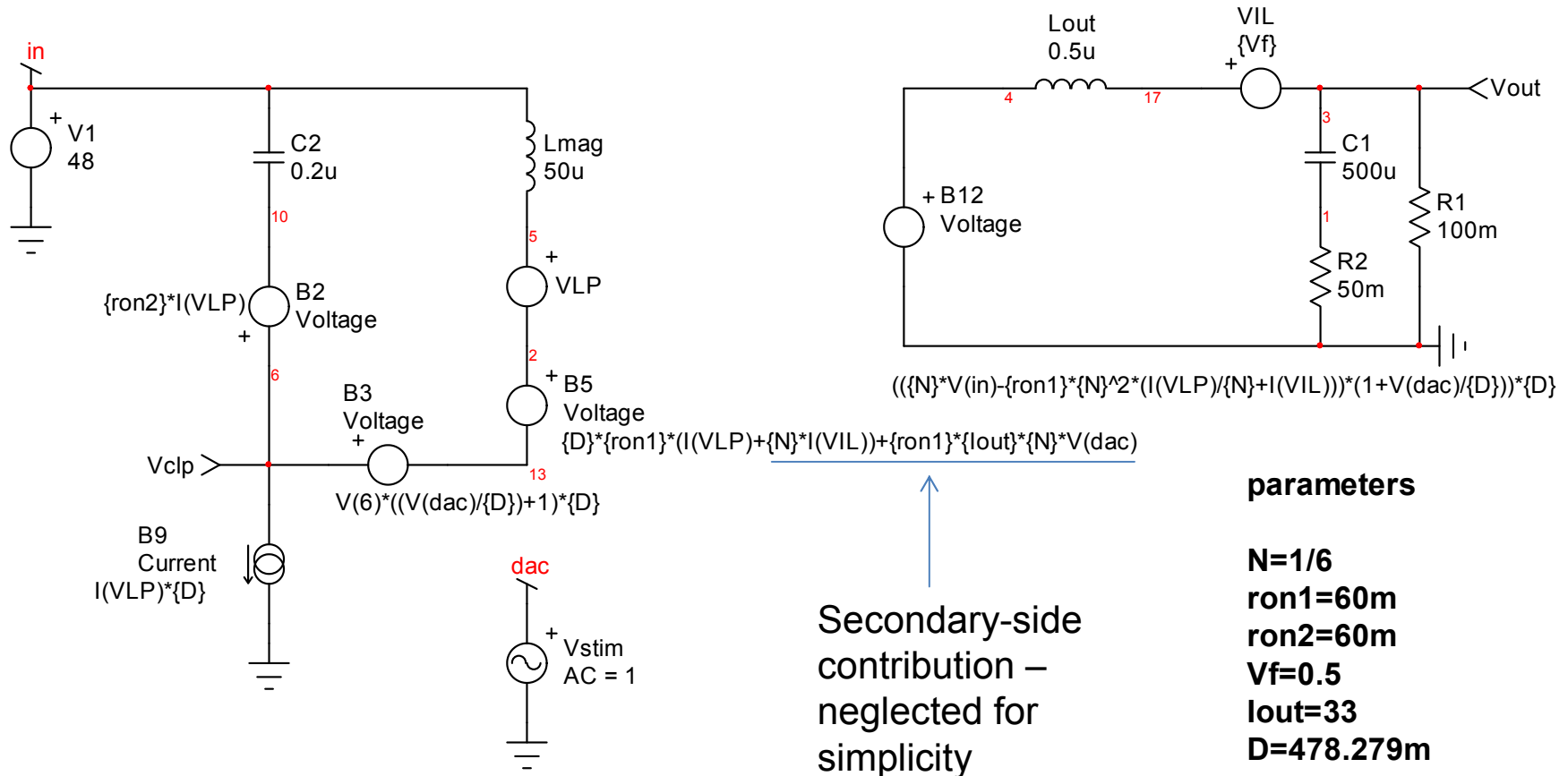- Look for ways to get simpler equations, final arrangement




- Final ac check is mandatory!




Simpler Circuit Does Not Distort Response

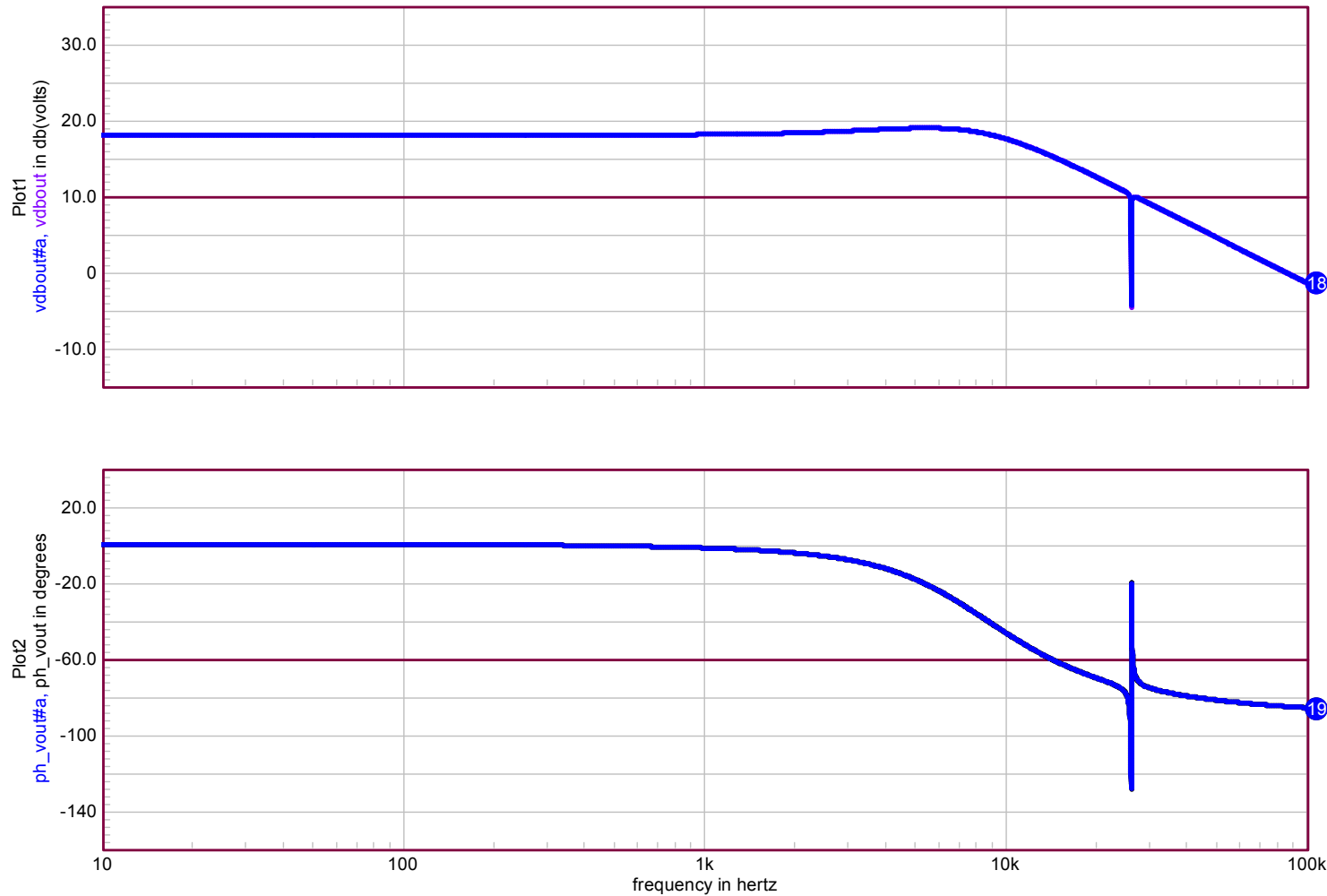- We are good to start analyzing the equivalent circuit



Start with the Clamp Circuitry

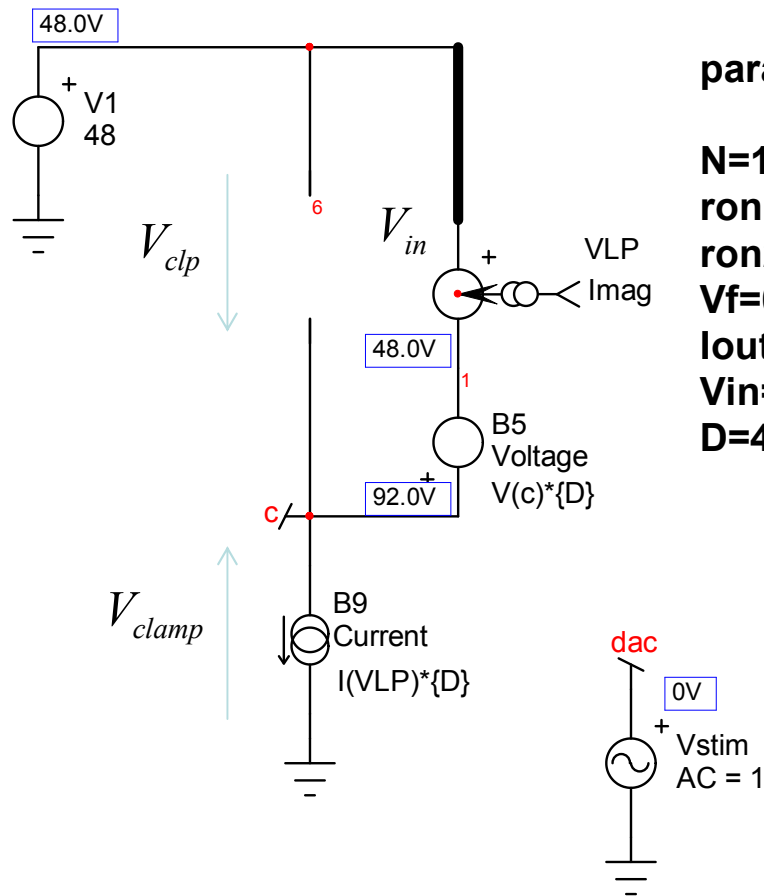- For the dc transfer function, open caps and short inductors



parameters

N=1/6
ron1=60m
ron2=60m
Vf=0.5
Iout=33
Vin=48
D=478.279m

$$V_{clp} = V_{(c)}D = V_{clamp}D$$

$$V_{clamp} = V_{in} + V_{clp}$$



$$V_{clp} = (V_{in} + V_{clp})D$$

$$V_{clp} = V_{in} \frac{D}{1-D} = 48 \frac{0.478}{1-0.478} \approx 44 \text{ V}$$


$$V_{clamp} = V_{in} + V_{clp} = 92 \text{ V}$$

This is a buck-boost dc transfer function



We Need the Magnetizing Current

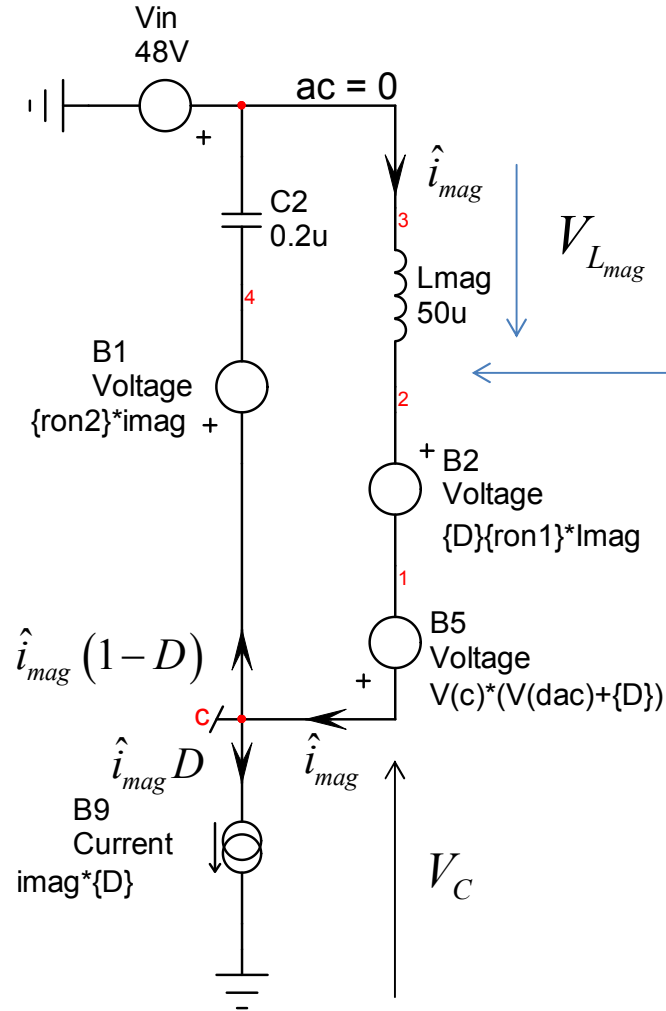- Use KVL and KCL to get the mag. current expression



$$V_{L_{mag}} = V_{(c)} - V_{(c)} (\hat{d} + D_0) + D_0 r_{on1} \hat{i}_{mag}$$



The secondary side contribution has been purposely neglected, I_{out} and \hat{i}_{out}



Express the Magnetizing Current i_{mag}

- The clamp capacitor ac voltage depends on i_{mag}

$$\hat{v}_{(C)} = \hat{i}_{mag} (1 - D_0) \left(\frac{1}{sC_{clp}} \right) + \hat{i}_{mag} r_{on2} = \hat{i}_{mag} \left[(1 - D_0) \left(\frac{1}{sC_{clp}} \right) + r_{on2} \right]$$

substitute

$$\hat{i}_{mag} = -\frac{\hat{v}_{L_{mag}}}{sL_{mag}} = -\frac{\hat{v}_{(C)} (1 - D_0) - V_{clamp} \hat{d} + D_0 r_{on1} \hat{i}_{mag}}{sL_{mag}}$$

Solve for i_{mag}

$$I_{mag}(s) = D(s) V_{clamp} \frac{sC_{clp}}{D_0^2 - 2D_0 + 1 + sC_{clp} (r_{on2} + D_0 r_{on1} - D_0 r_{on2}) + s^2 L_{mag} C_{clp}}$$

Identify Second-Order Coefficients

- Identify terms with a second-order polynomial form

$$\frac{I_{mag}(s)}{D(s)} = \frac{V_{clamp}}{(1-D_0)^2} \frac{sC_{clp}}{1 + sC_{clp} \left[\frac{r_{on2}(1-D_0) + D_0 r_{on1}}{(1-D_0)^2} \right] + s^2 \frac{L_{mag} C_{clp}}{(1-D_0)^2}}$$

Develop and rearrange:

$$\frac{I_{mag}(s)}{D(s)} = M_0 \frac{sC_{clp}}{1 + \frac{s}{\omega_{0M} Q_M} + \left(\frac{s}{\omega_{0M}} \right)^2}$$


$$M_0 = \frac{V_{clamp}}{(1-D_0)^2} = \frac{V_{in}}{(1-D_0)^3} \quad \omega_{0M} = \frac{1-D_0}{\sqrt{L_{mag} C_{clp}}}$$

$$Q_M = \sqrt{\frac{L_{mag}}{C_{clp}}} \frac{1-D_0}{r_{on2}(1-D_0) + D_0 r_{on1}}$$



Re-Write the Expression Nicely

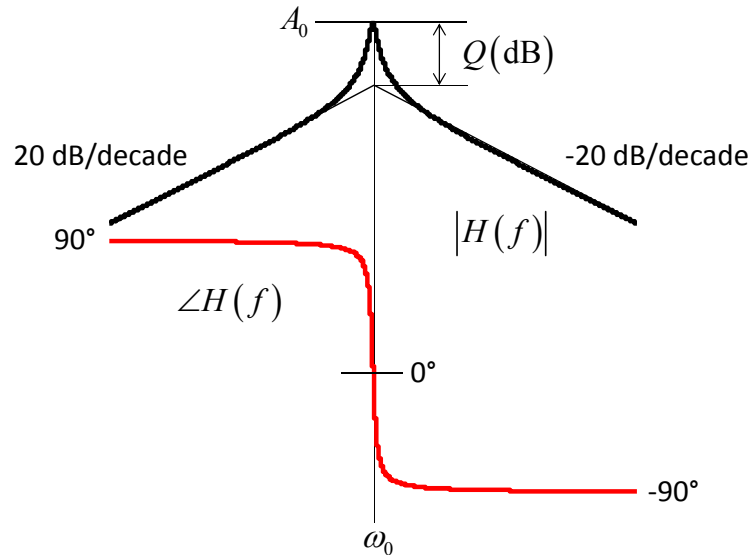- A tuned network offers the following transfer function




$$H(s) = A_0 \frac{1}{1 + \left(\frac{\omega_0}{s} + \frac{s}{\omega_0} \right) Q}$$

$$\frac{I_{mag}(s)}{D(s)} = M_0 \frac{sC_{clp}}{1 + \frac{s}{\omega_{0M}Q_M} + \left(\frac{s}{\omega_{0M}} \right)^2} \longrightarrow \frac{I_{mag}(s)}{D(s)} = A_0 \frac{1}{1 + \left(\frac{\omega_{0M}}{s} + \frac{s}{\omega_{0M}} \right) Q_M}$$

$$A_0 = \frac{V_{clamp}}{r_{on2}(1-D_0) + D_0 r_{on1}} \longrightarrow |A_0(\omega_{0M})| = 67.713 \text{ dB}$$


Time for an ac Check

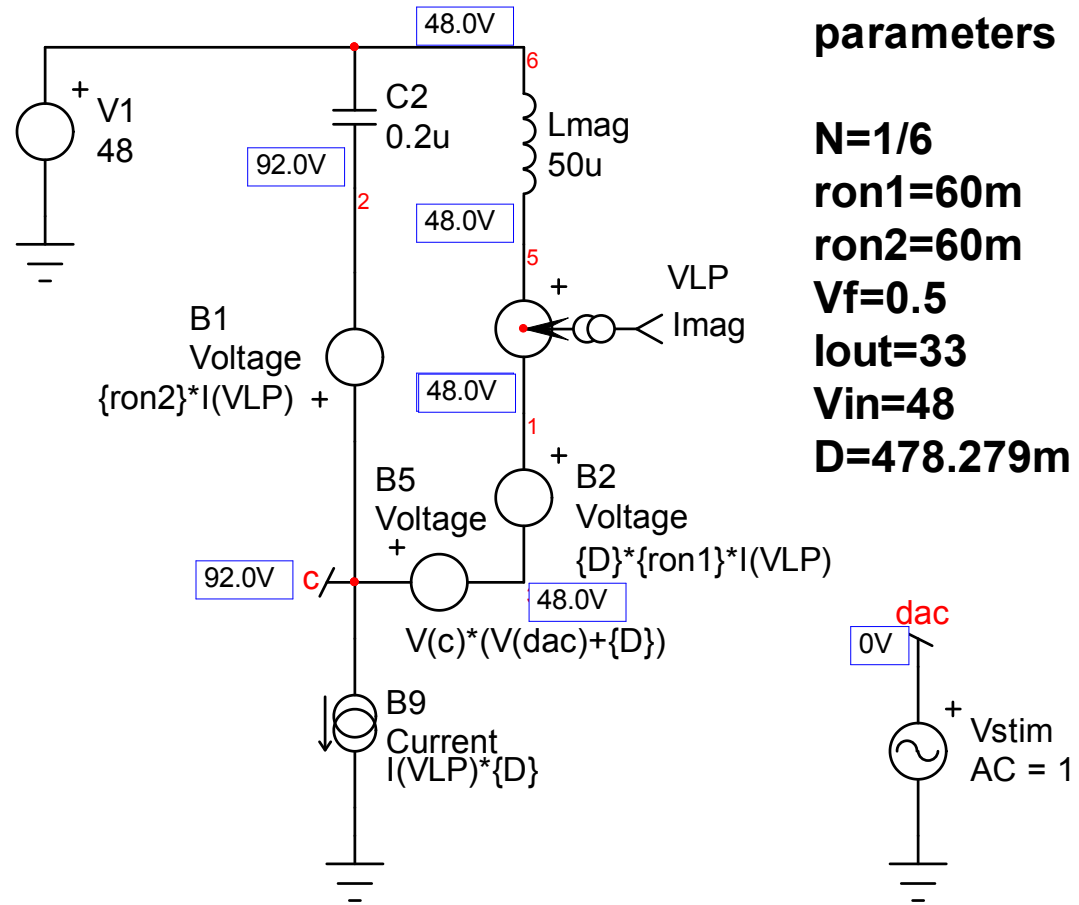□ SPICE can obtain the ac response in a snap-shot



Curves Perfectly Superimpose

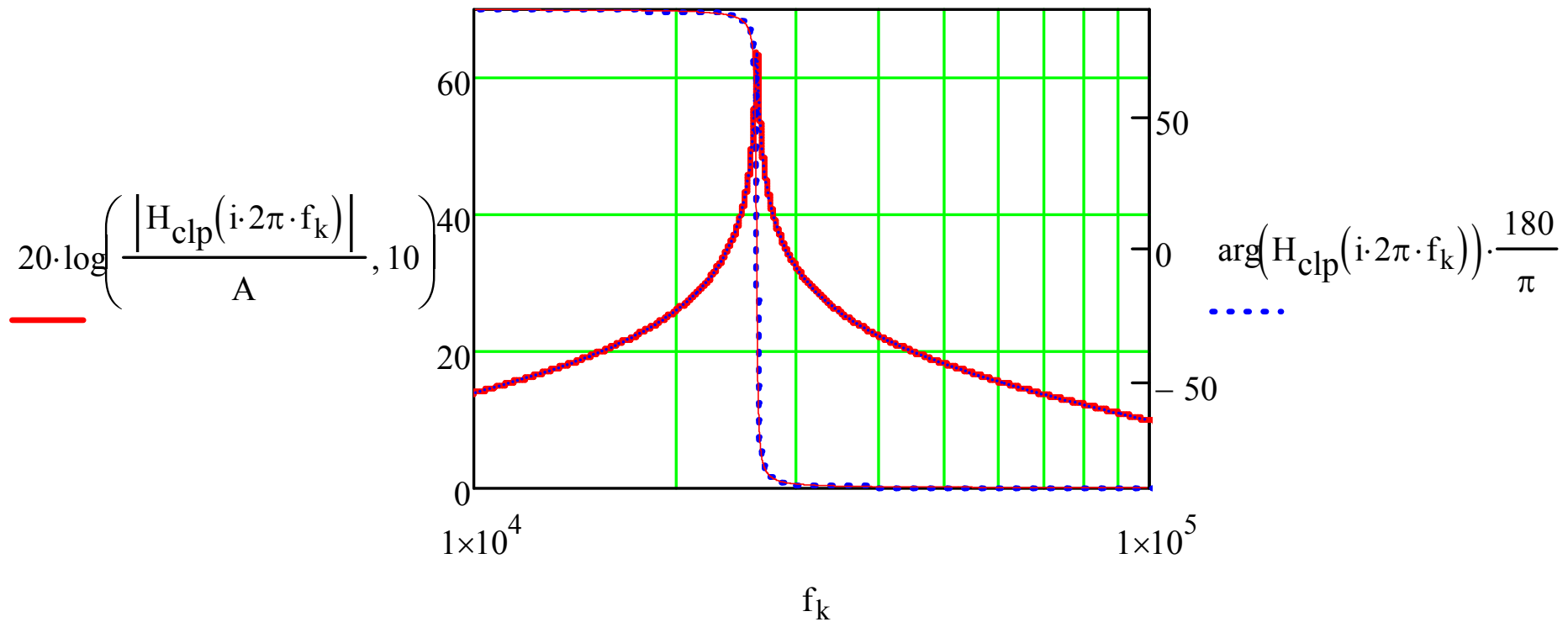- It is important to obtain similar plots, otherwise: error!




Max SPICE is 63.710 dB
Max Mathcad® is 63.713 dB

➔ "Can do!"




Run Another Round of Rearrangement

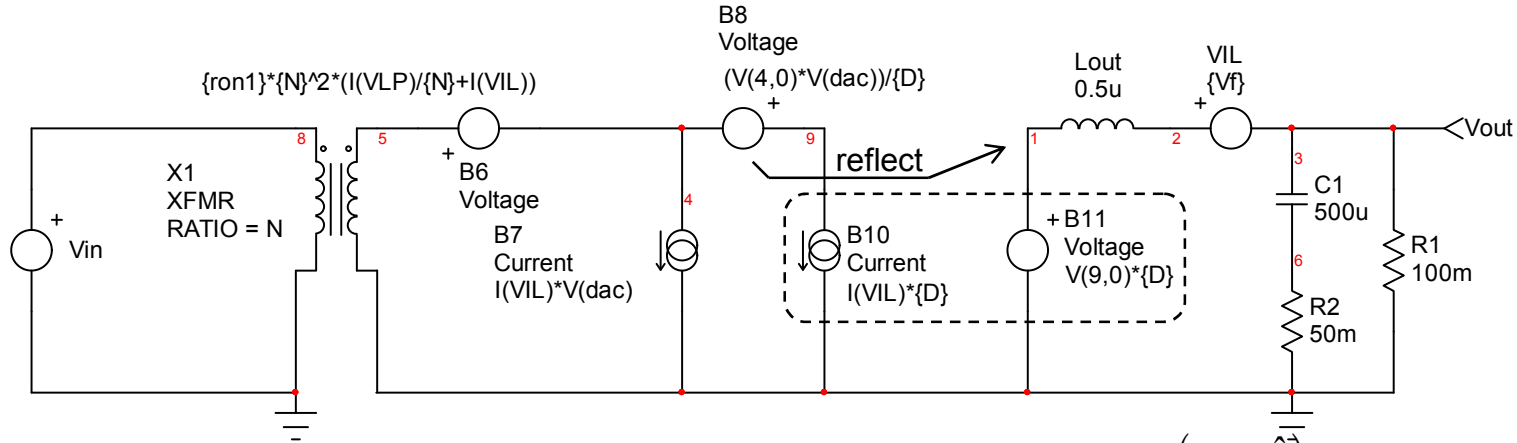□ Now concentrate on the buck output stage only


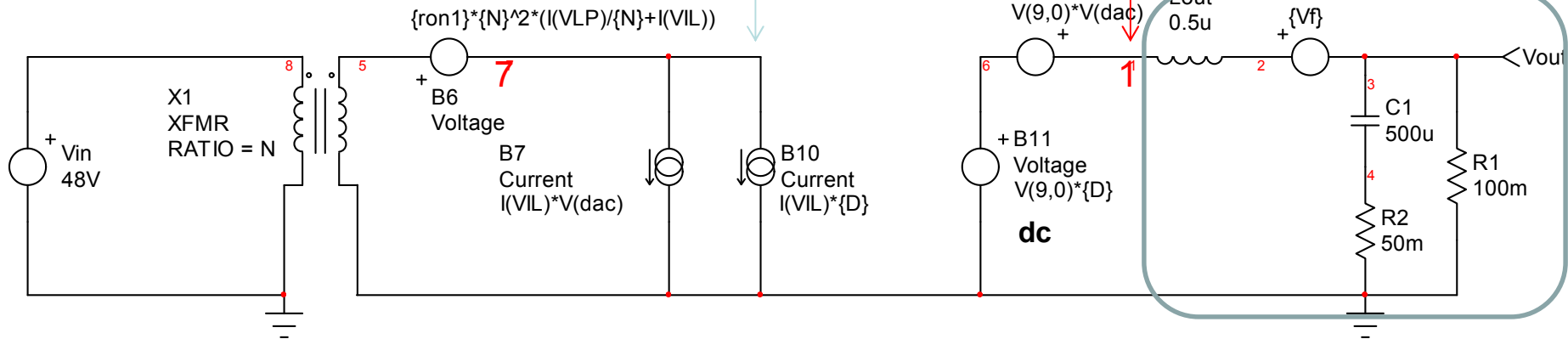
$$V(7) = NV_{in} - r_{on1} N^2 \left(\frac{I_{mag}}{N} + I_{out} \right)$$



Further Simplification is Necessary

□ Extract the ac current from the equation, $\langle i_{mag}(t) \rangle_{T_{sw}} = 0$

$$V_{(7)} = NV_{in} - r_{on1} N^2 \left(\frac{\hat{i}_{mag}}{N} + (I_{out} + \hat{i}_{out}) \right) \longrightarrow V_{(1)} = \left[NV_{in} - r_{on1} N^2 \left(\frac{\hat{i}_{mag}}{N} + (I_{out} + \hat{i}_{out}) \right) \right] (D + \hat{d})$$

Develop $V_{(1)}$ keep ac terms only

$$\begin{array}{ccccccc}
 DNV_{in} + NV_{in}\hat{d} - DN\hat{i}_{mag}r_{on1} - \color{red}N\hat{d}\hat{i}_{mag}r_{on1} - DI_{out}N^2r_{on1} - DN^2\hat{i}_{out}r_{on1} - I_{out}N^2\hat{d}r_{on1} - \color{red}N^2\hat{d}\hat{i}_{out}r_{on1} & & & & & & \\
 \text{dc} & & \approx 0 & \text{dc} & & & \approx 0
 \end{array}$$

Rearranging the result, we obtain:

$$\begin{array}{l}
 NV_{in}\hat{d} - DN\hat{i}_{mag}r_{on1} - DI_{out}N^2r_{on1} - DN^2\hat{i}_{out}r_{on1} - I_{out}N^2\hat{d}r_{on1} \qquad r_{on1} \ll 1 \\
 \hat{d}(NV_{in} - I_{out}N^2\hat{d}r_{on1}) - DN\hat{i}_{mag}r_{on1} - DN^2\hat{i}_{out}r_{on1} \qquad \hat{d} \ll 1 \\
 \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad \qquad N^2 \ll 1
 \end{array}$$

Neglecting small terms, we finally obtain:

$$\hat{v}_{(1)} = \hat{d}NV_{in} - DN\hat{i}_{mag}r_{on1}$$



Add the Second-Order Response of LC Filter

The magnetizing current definition is:


$$\frac{I_{mag}(s)}{D(s)} = M_0 \frac{sC_{clp}}{1 + \frac{s}{\omega_{0M}Q_M} + \left(\frac{s}{\omega_{0M}}\right)^2} = M(s)$$

Once re-injected in to the previous definition, we have:

$$V_1(s) = D(s)NV_{in} - D_0Nr_{onl}D(s)M(s)$$

$$V_1(s) = D(s)[NV_{in} - D_0Nr_{onl}M(s)]$$

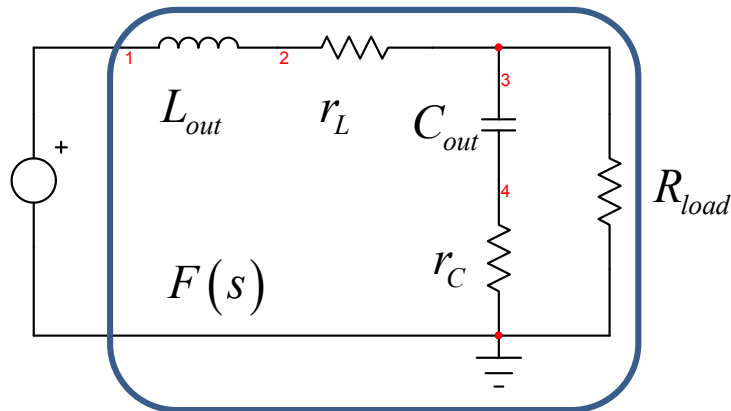The source is filtered by the 2nd-order LC filter:



$$F(s) = F_0 \frac{1 + \frac{s}{s_{zF}}}{1 + \frac{s}{\omega_{0F}Q_F} + \left(\frac{s}{\omega_{0F}}\right)^2}$$

$$F_0 = \frac{R_{Load}}{R_{load} + r_L} \quad \omega_{zF} = \frac{1}{r_C C_{out}}$$

$$\omega_{0F} = \frac{1}{\sqrt{L_{out}C_{out}}} \sqrt{\frac{r_L + R_{load}}{r_C + R_{load}}}$$

$$Q_F = \frac{L_{out}C_{out}\omega_{0F}(r_C + R_{Load})}{L_{out} + C_{out}(r_L r_C + R_{load}(r_L + r_C))}$$

We Have the Final Transfer Function

- The transfer function reveals the mag. current contribution

$$\frac{V_{out}(s)}{D(s)} = F(s) \left(N V_{in} - \boxed{D_0 N r_{on1} M(s)} \right) \quad \longrightarrow \quad \text{YES!}$$

- The mag. current subtracts and explains the notch


$$\frac{V_{out}(s)}{D(s)} = F_0 \frac{1 + \frac{s}{s_{zF}}}{1 + \frac{s}{\omega_{0F} Q_F} + \left(\frac{s}{\omega_{0F}} \right)^2} N \left(V_{in} - D_0 r_{on1} M_0 \frac{s C_{clp}}{1 + \frac{s}{\omega_{0M} Q_M} + \left(\frac{s}{\omega_{0M}} \right)^2} \right)$$

- This is the control-to-output transfer function of the ACF



Final Sanity Check - Magnitude

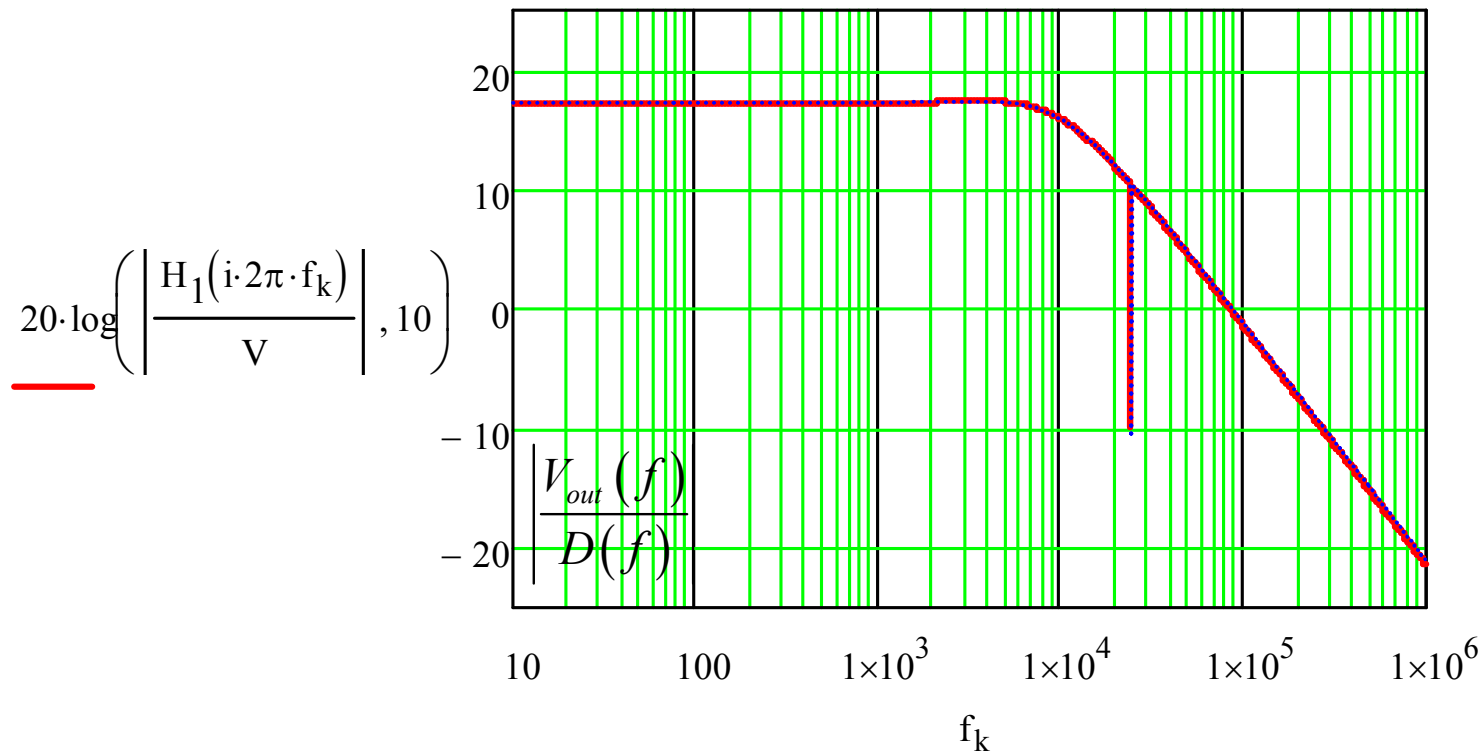
- Compare the analytical ac response with that of SPICE



- Magnitude curves superimpose perfectly

Final Sanity Check - Phase

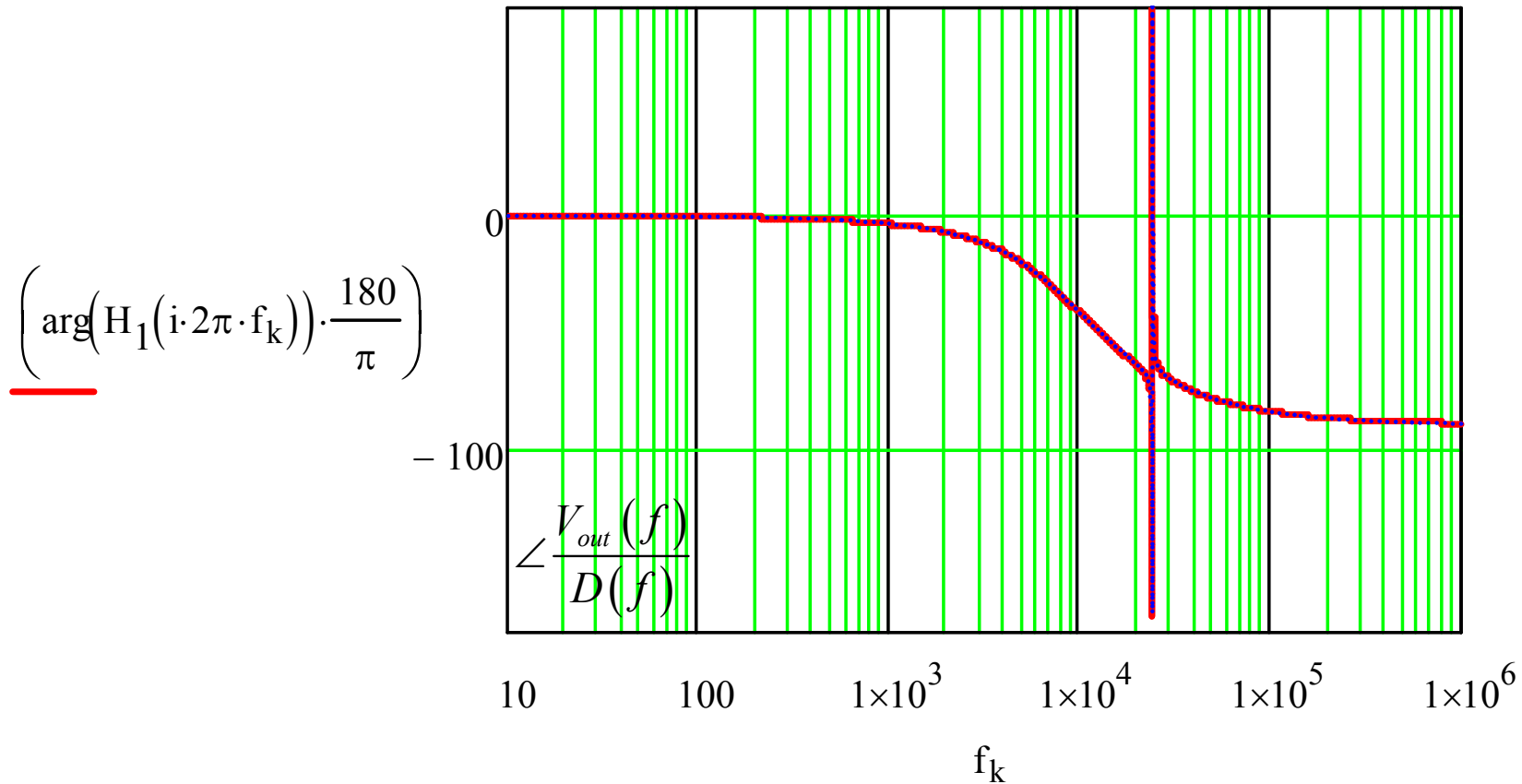
- Compare the analytical ac response with that of SPICE



- Argument curves are in excellent agreement too

The Prototype Hardware

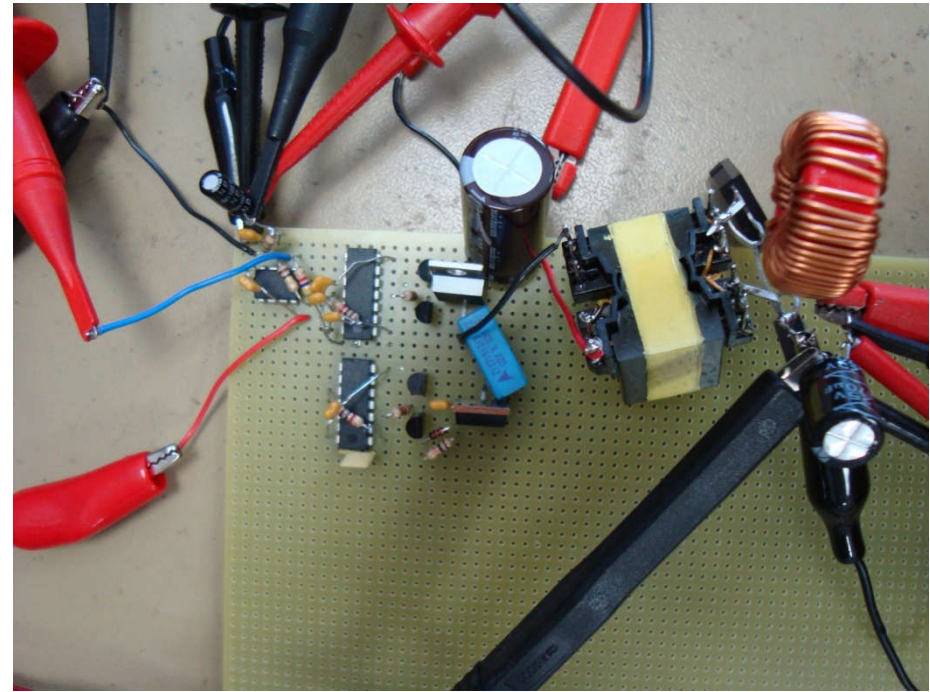- ❑ The circuit is assembled using available components




- ❑ Make sure caps. are well characterized before soldering


With the kind help of Yann Vaquette, Application engineer




Typical Prototype Waveforms

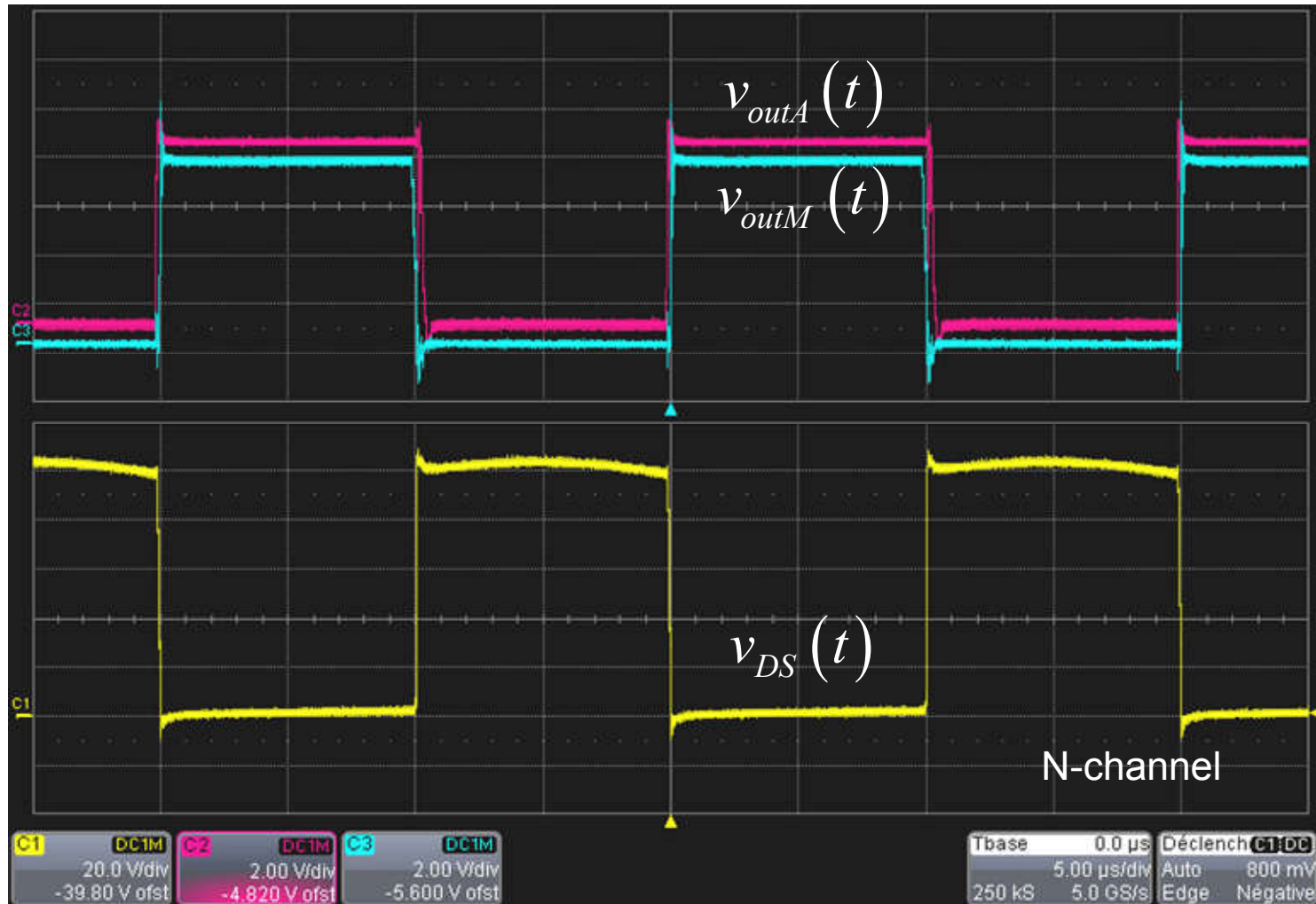


Quasi-ZVS is Ensured on the Drain

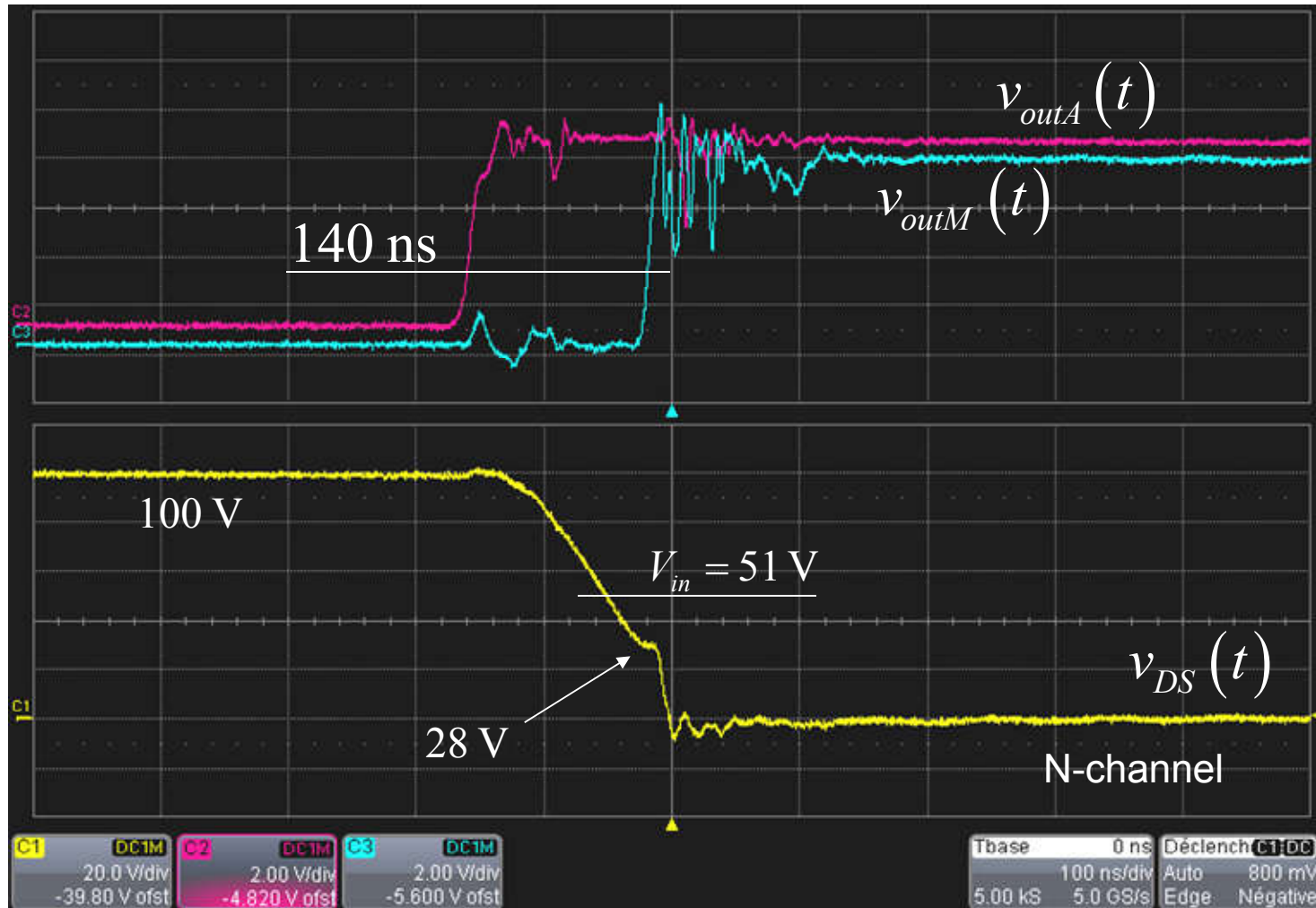

ZVS is Also Ensured on Clamp Switch

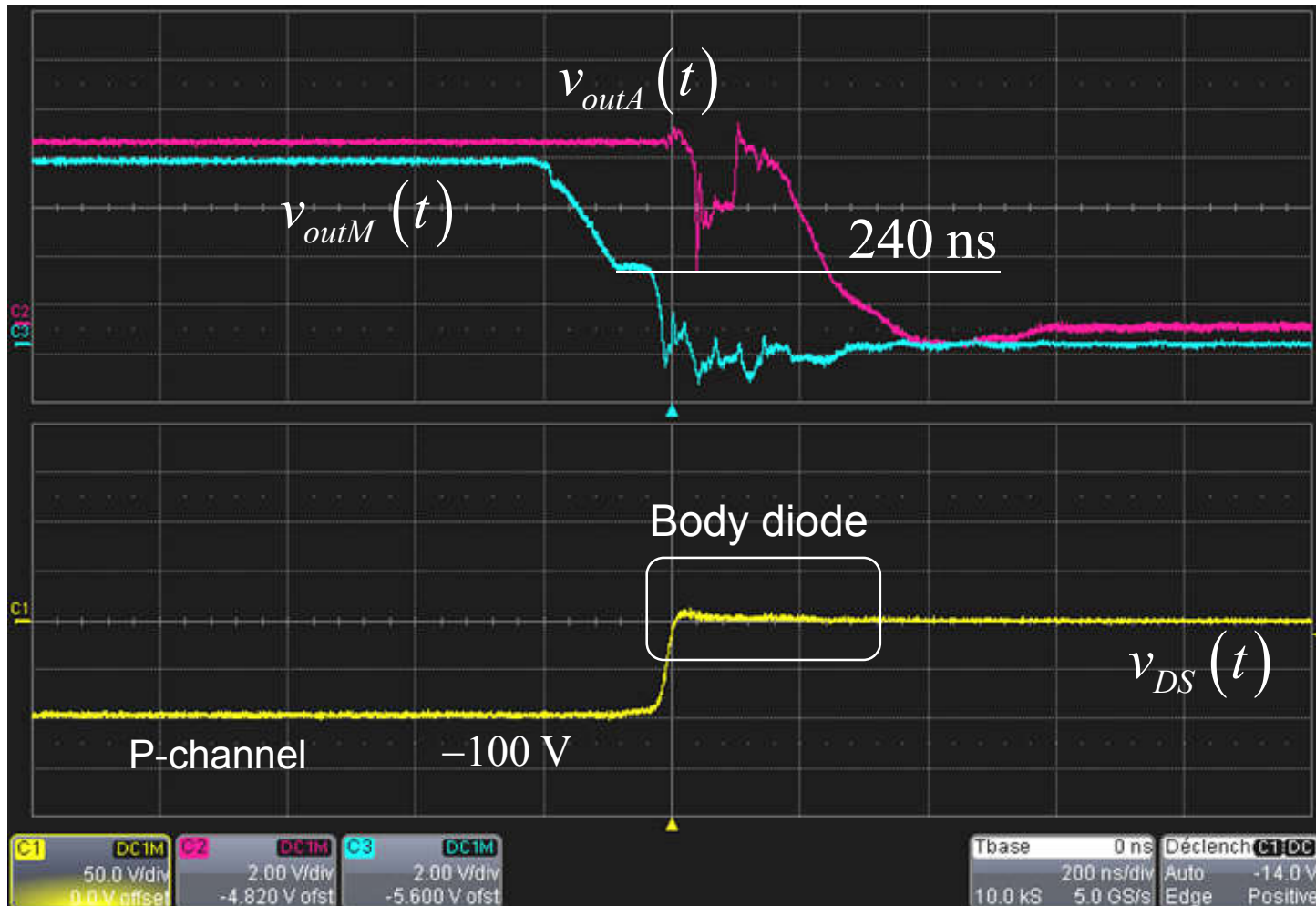


Current in the Clamping Network

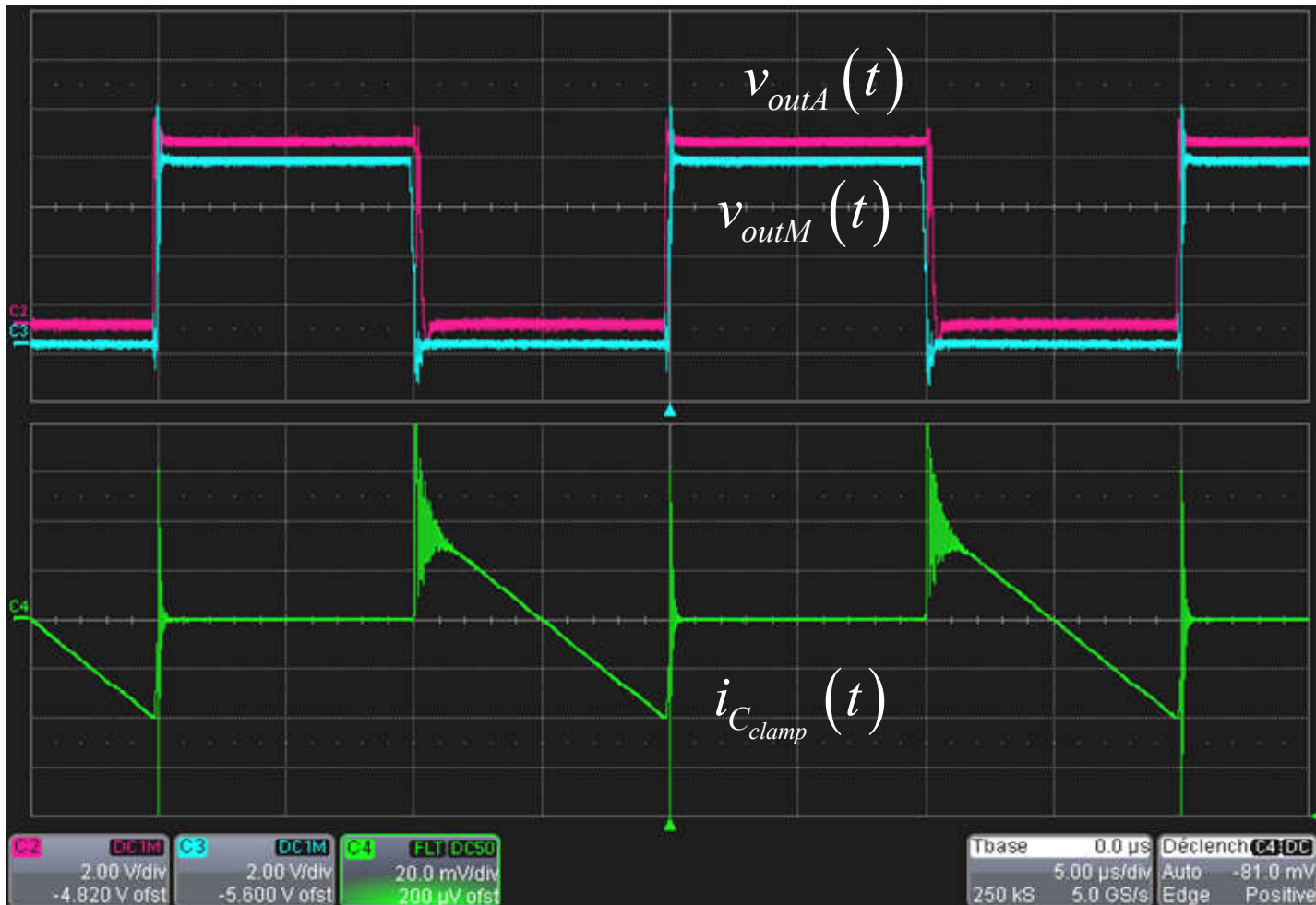

SPICE Test Fixture

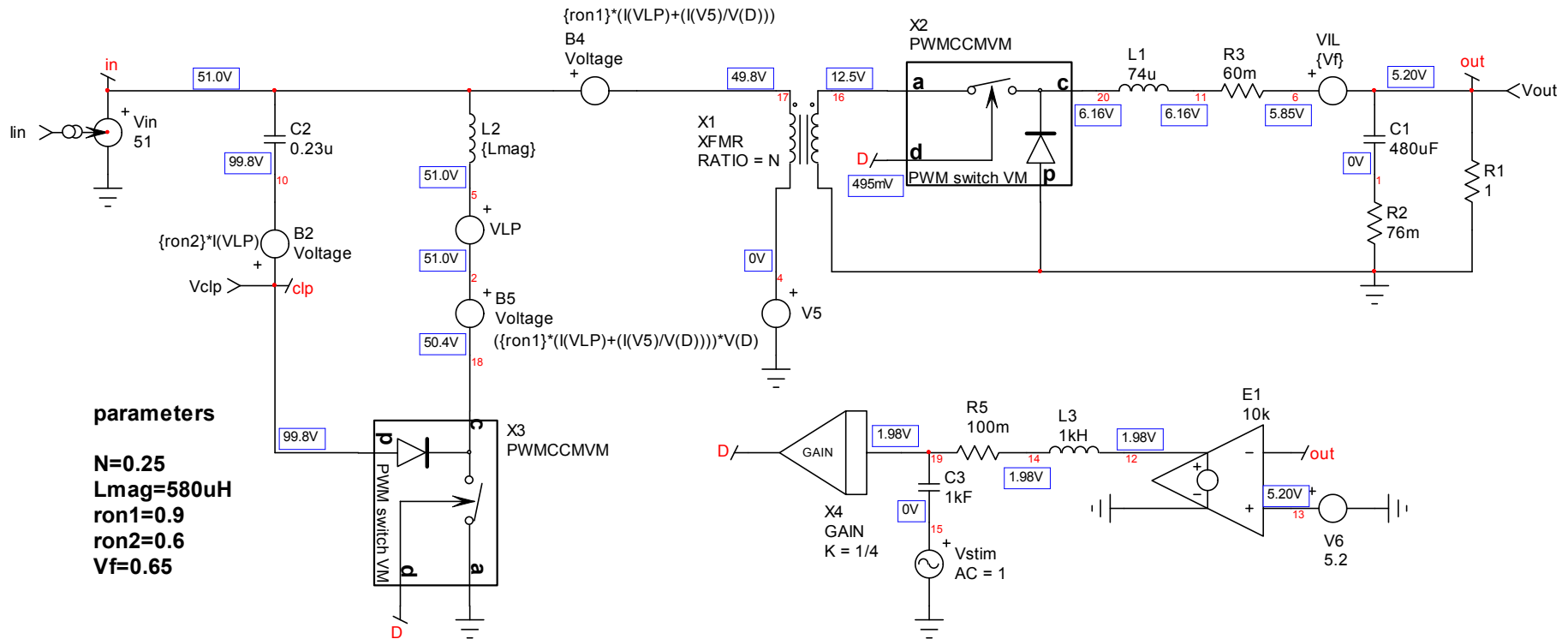□ We have used the following SPICE simulation fixture




□ Check dc points versus hardware values: ok



Magnitude Response

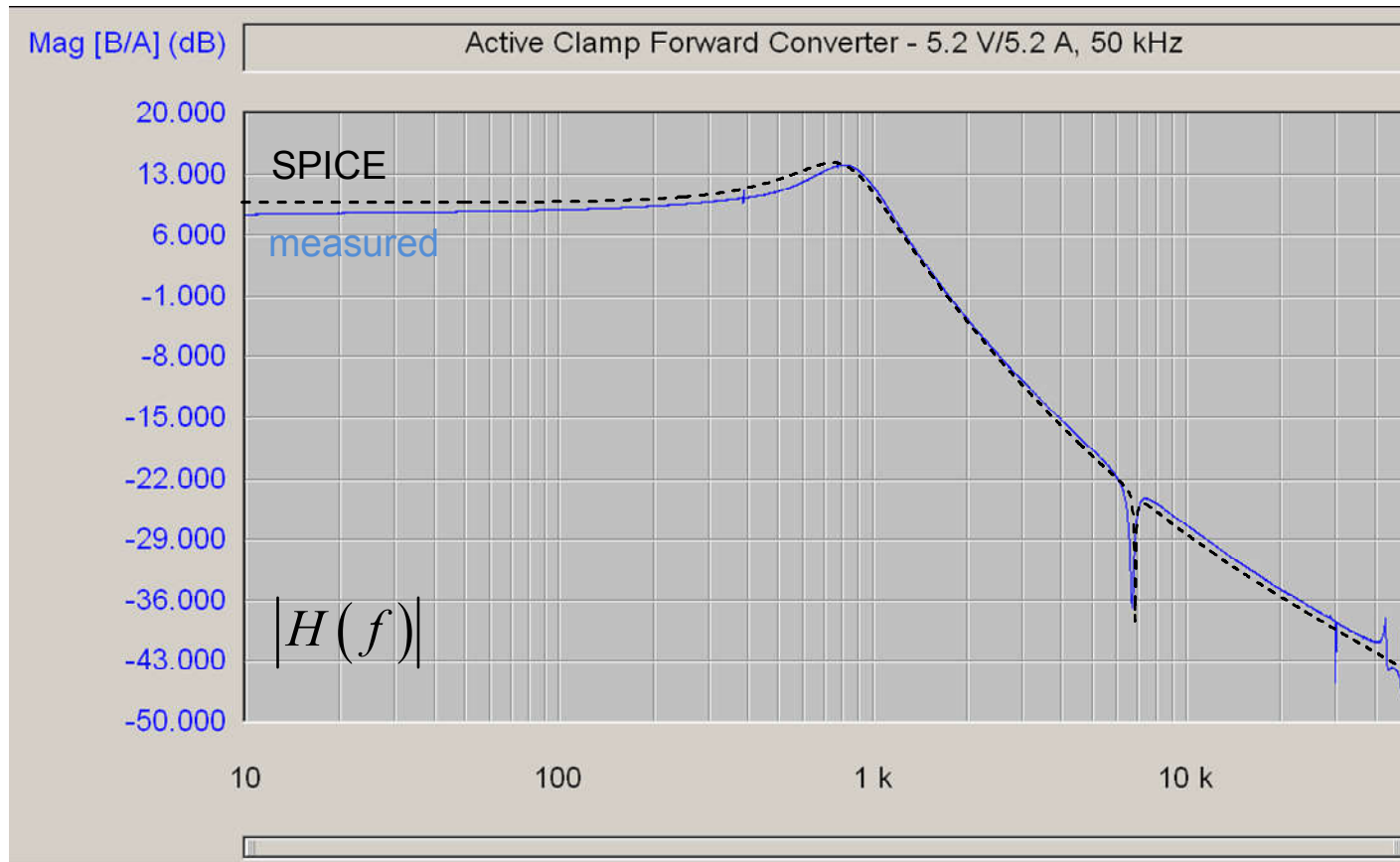
- There is a slight shift but overall agreement is good



- cap. ESR is often the offender in loop measurement

Phase Response

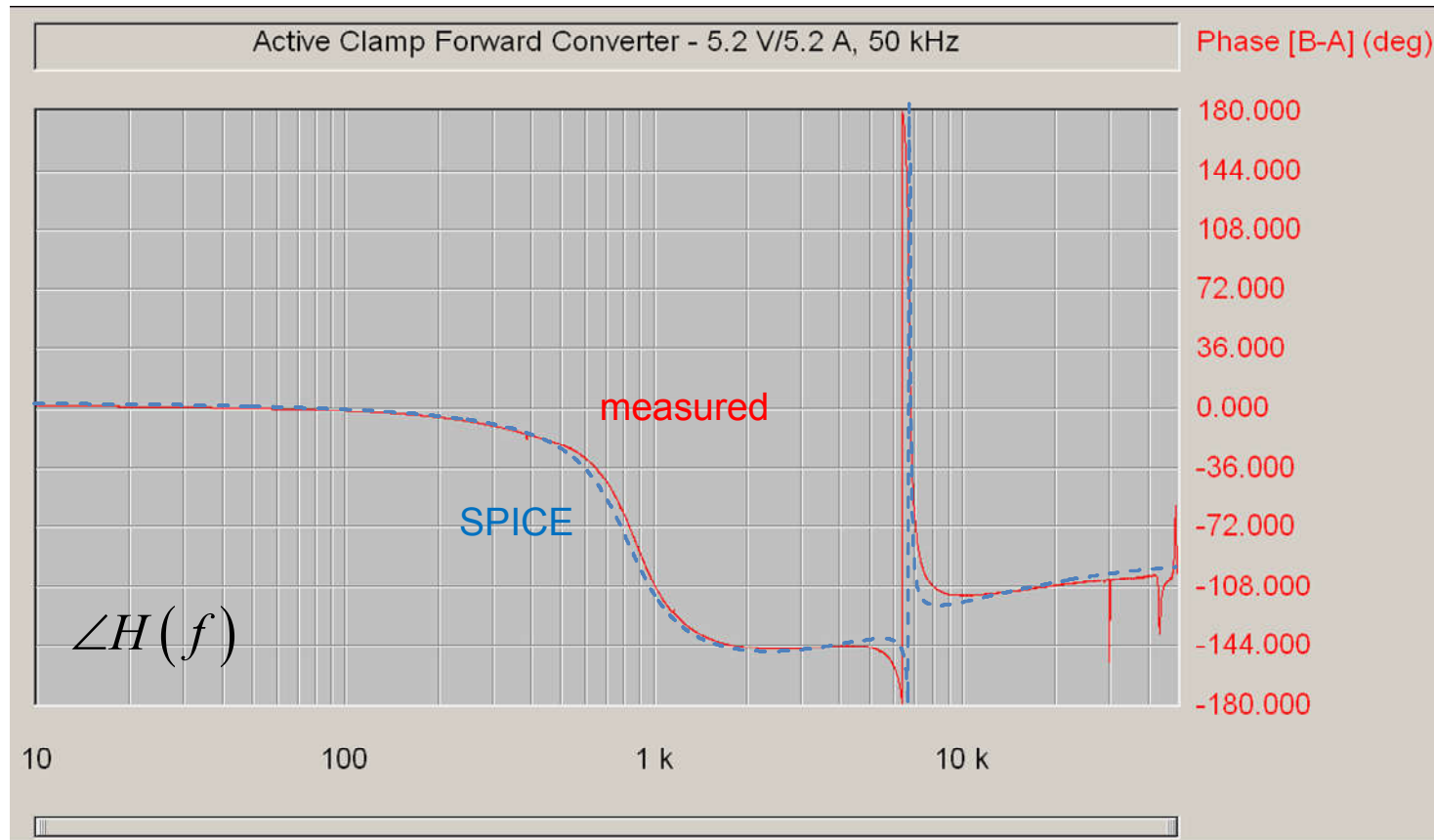
- Good agreement between curves, especially peaking



- The notch Q depends on resistive elements $r_{DS(on)}$ etc.


Comparison with Simplis Response

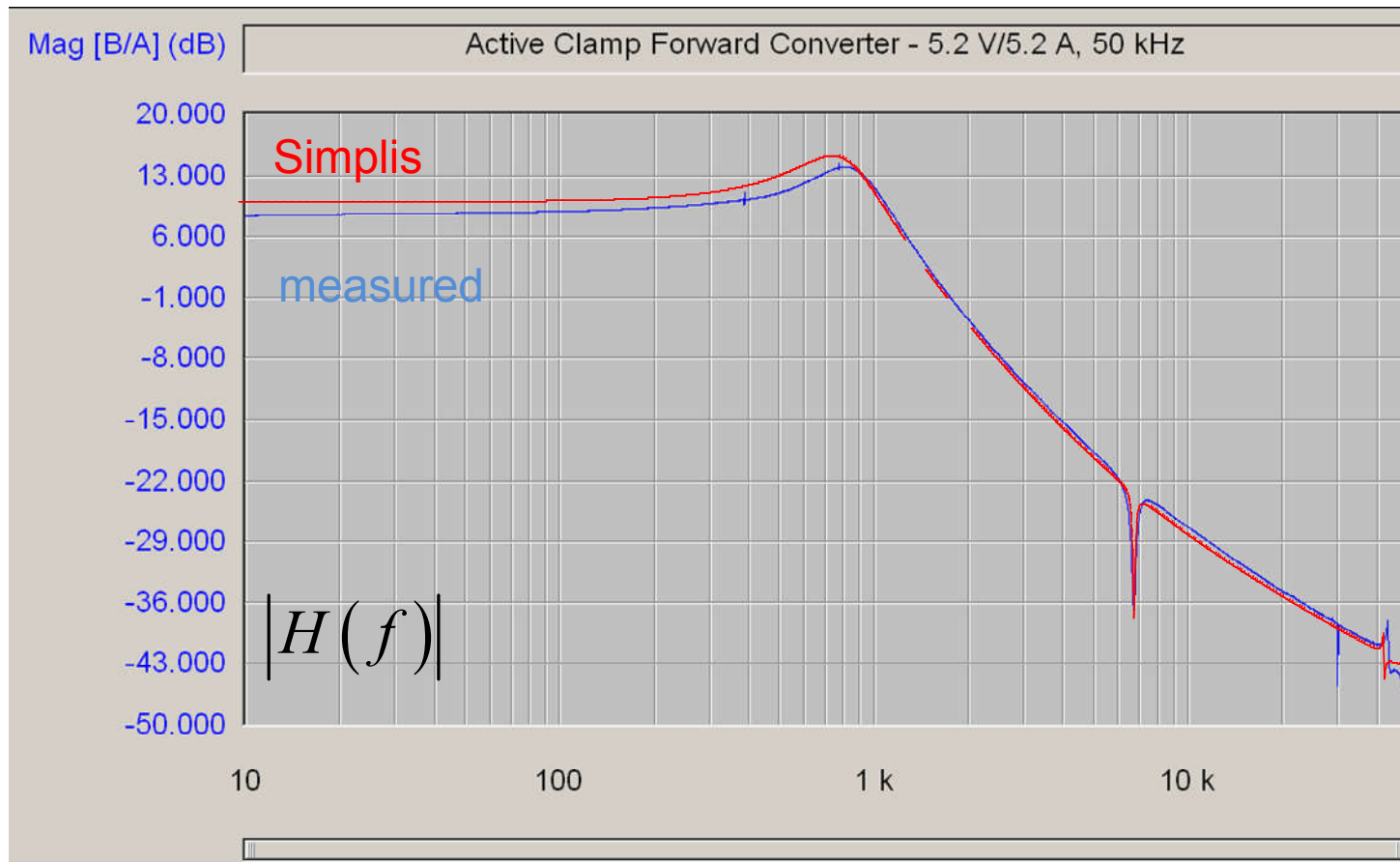- Excellent agreement between curves, almost no shift




Comparison with Simplis Response

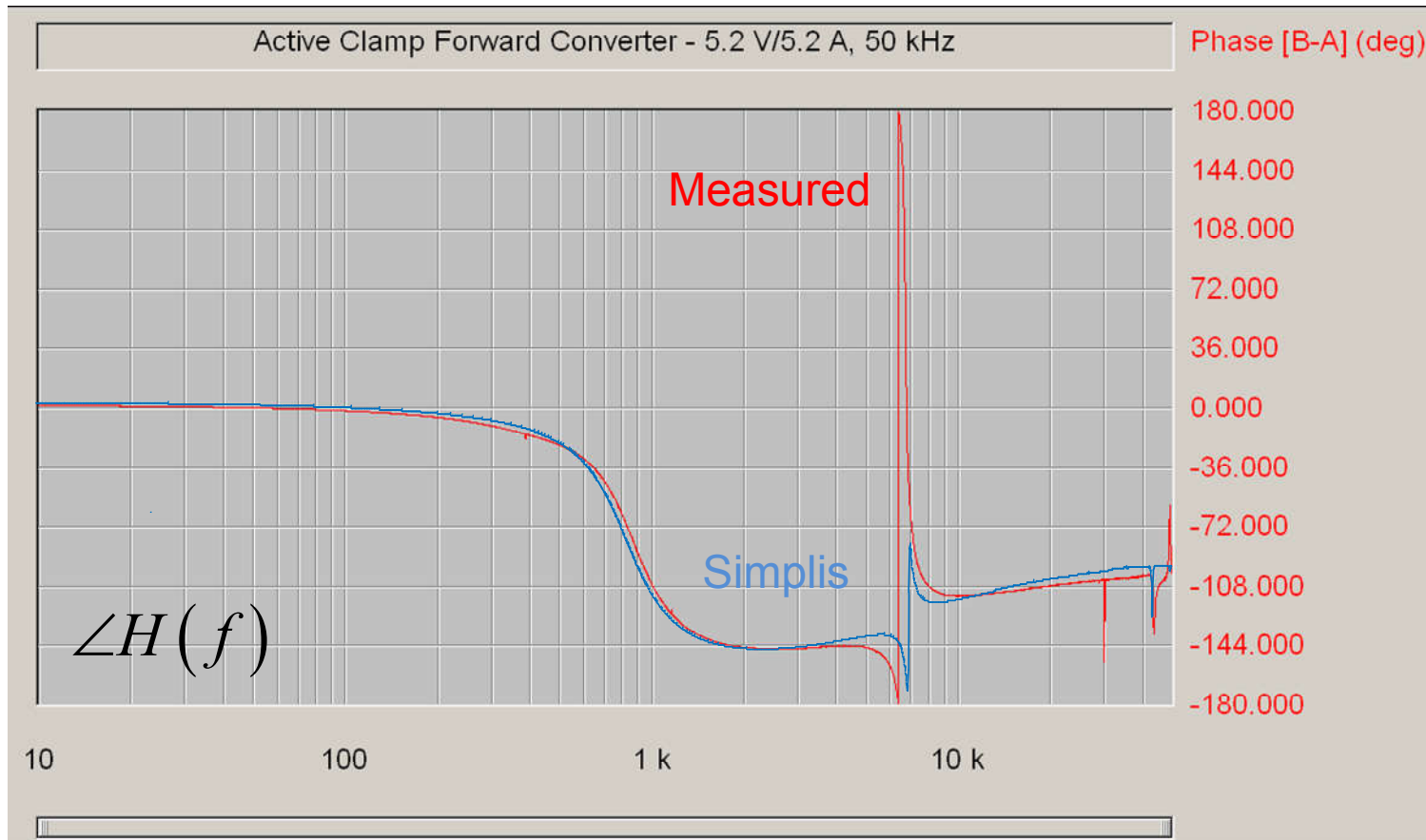- Despite a slightly lower peaking, phase agreement is ok




Simulation also Confirms Damping!

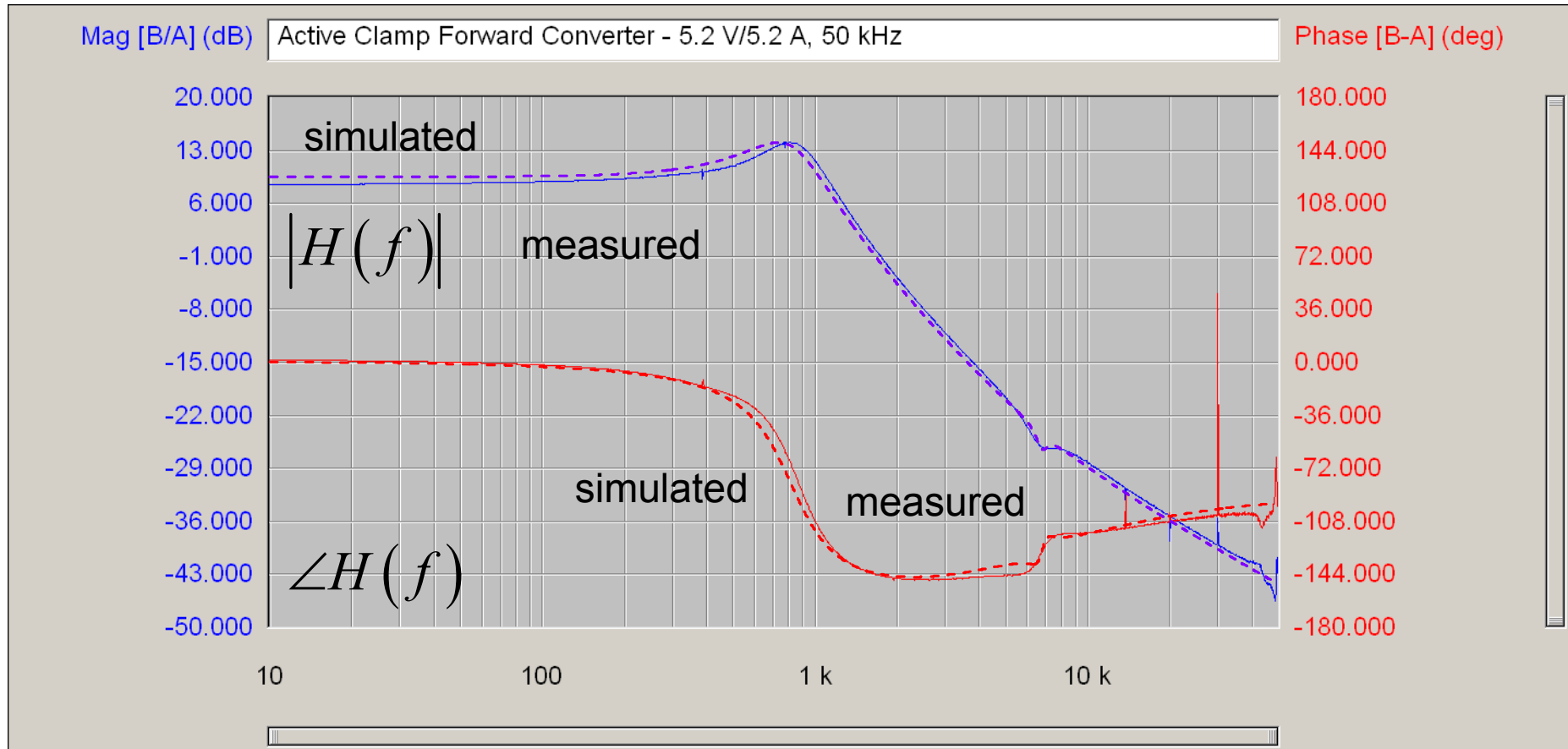- Inserting a 10-Ω resistance damps the notch nicely



A Practical Case

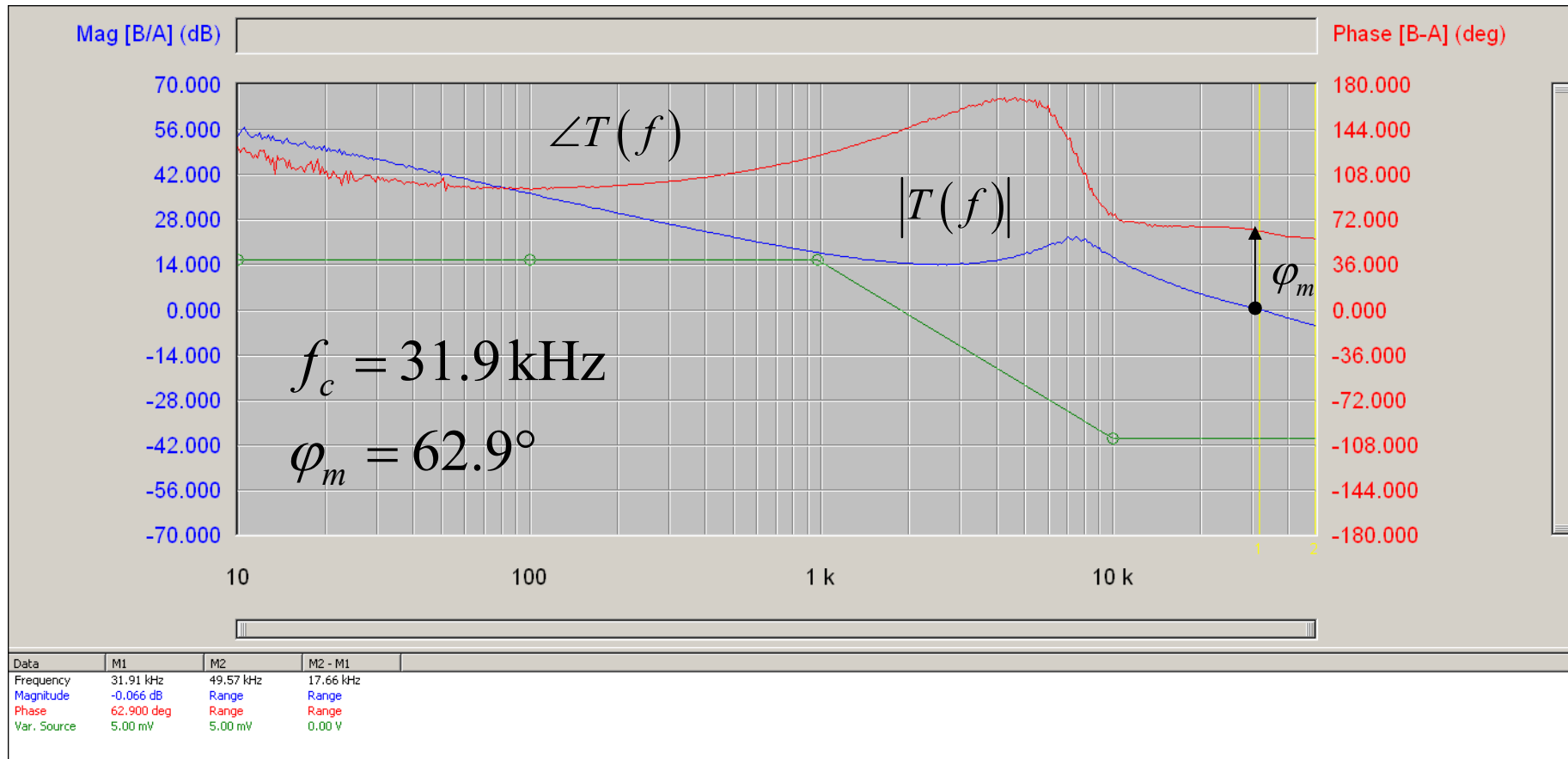- The model helped to stabilize this 3.3-V/30-A converter



Transient Response Test

- Step-load transient response confirms stability margins



$V_{IN} = 36 \text{ V}$, 15 A to 22.5 A - Slew rate 1 A / μ s

Conclusion

- ❑ The PWM switch model is an essential tool for modeling
- ❑ We have seen how to derive it in different operating modes
- ❑ Small-signal modeling using the PWM switch is simple and fast
- ❑ When modeling converters, always proceed step by step
- ❑ Always perform intermediate sanity checks (SPICE, Mathcad[®]...)
- ❑ Analytical analysis does not shield you against lab. experiments
- ❑ Analysis, simulation and bench: the path to success!



Merci !
Thank you!
Xiè-xie!

