



ON Semiconductor®

Practical Implementation of Loop Control in Power Converters

Christophe Basso

IEEE Senior Member

Course Agenda

- ❑ Control System Basics
- ❑ Operational Amplifier and Low-Frequency Pole
- ❑ Gain-Bandwidth Impact on Phase Boost
- ❑ Op Amp Slew Rate Effects in Loop Control
- ❑ Start-Up Sequence and Auxiliary Supply
- ❑ Characterizing the Optocoupler Pole
- ❑ Dealing with the Fast Lane
- ❑ Going Around the TL431 Fast Lane



Course Agenda


Control System Basics

- Operational Amplifier and Low-Frequency Pole
- Gain-Bandwidth Impact on Phase Boost
- Op Amp Slew Rate Effects in Loop Control
- Start-Up Sequence and Auxiliary Supply
- Characterizing the Optocoupler Pole
- Dealing with the Fast Lane
- Going Around the TL431 Fast Lane




What is a Control System?

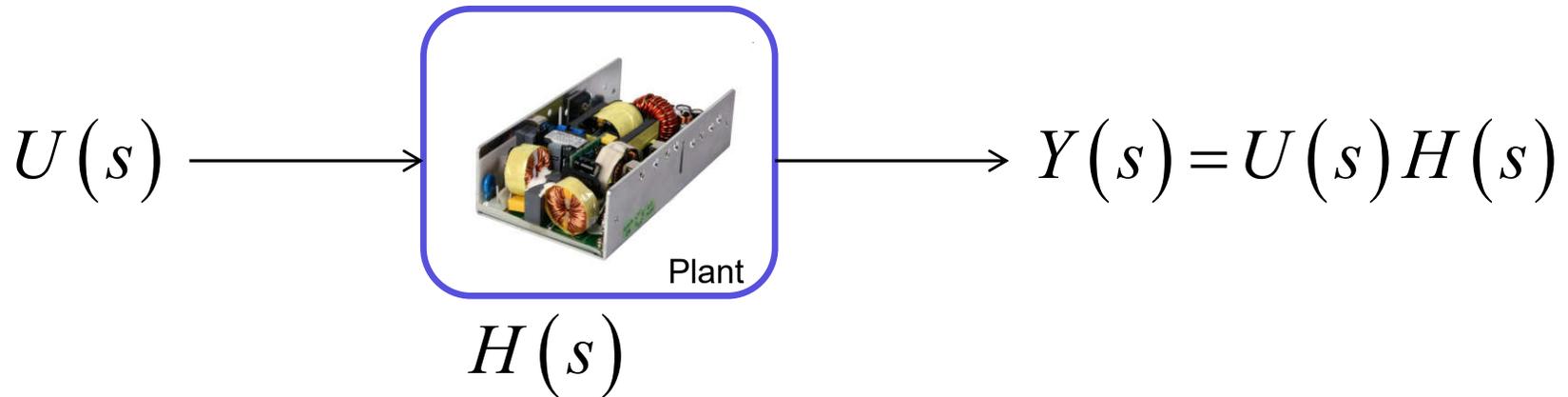- An *open-loop* system links the output to the control variable




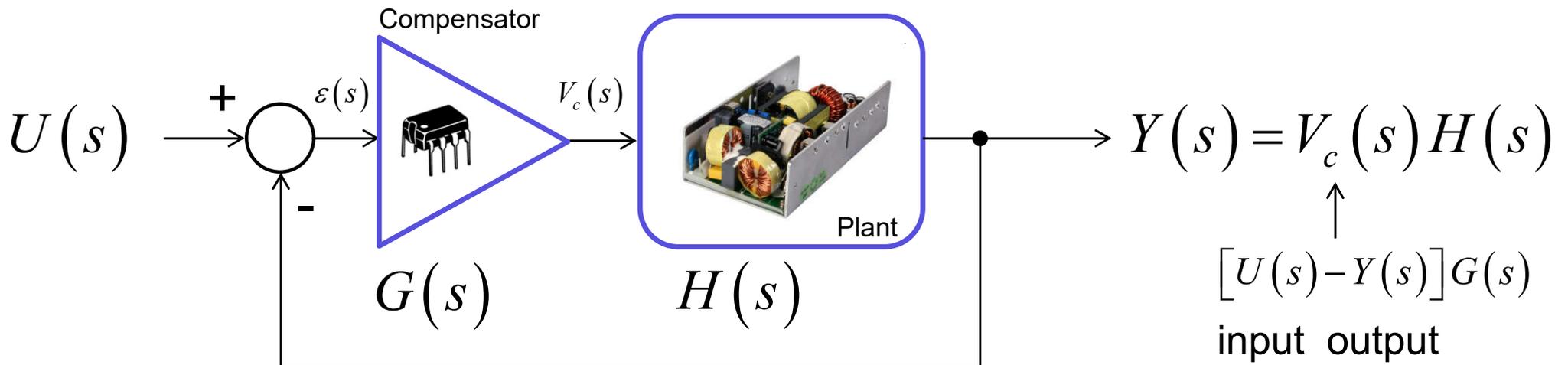
- A *control system* observes the output to induce correction



Performance of a Control System

□ We want the following operating characteristics:


- ✓ Speed
- ✓ Precision
- ✓ Robustness

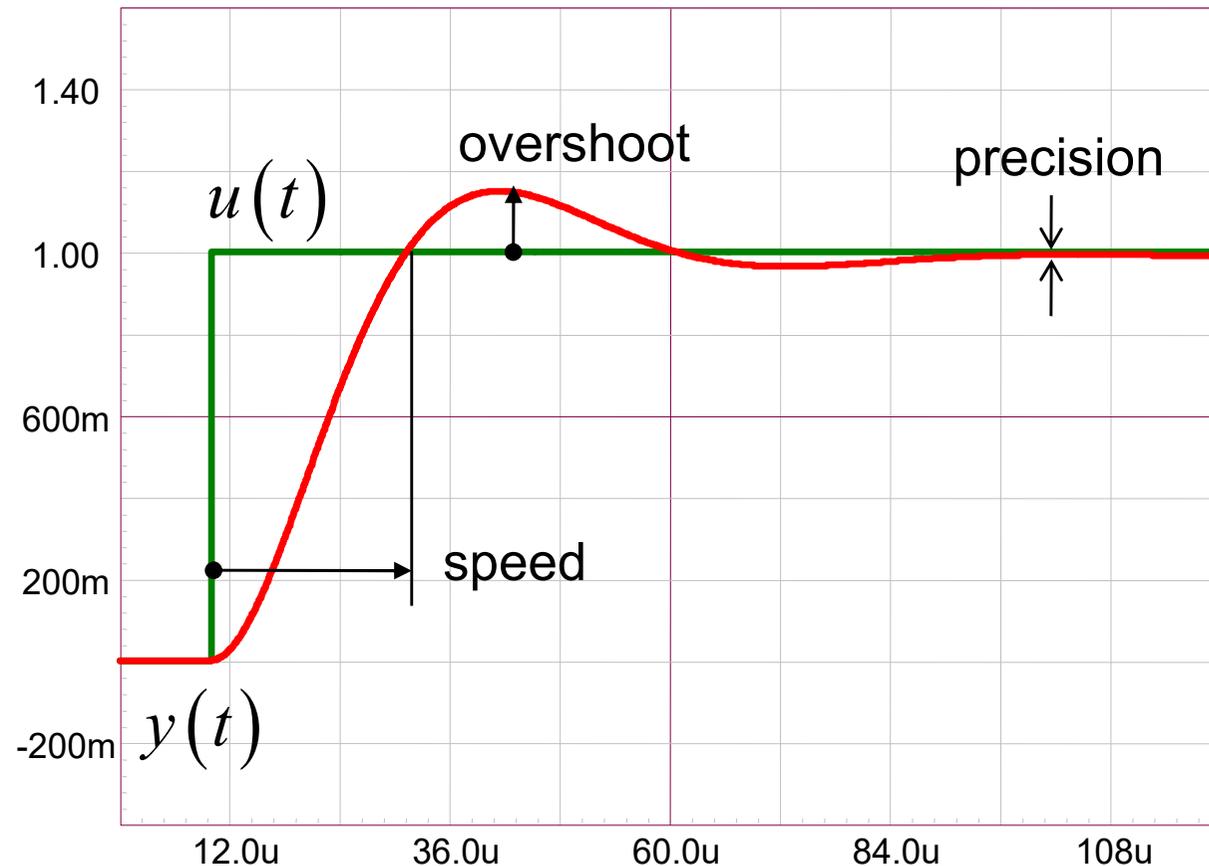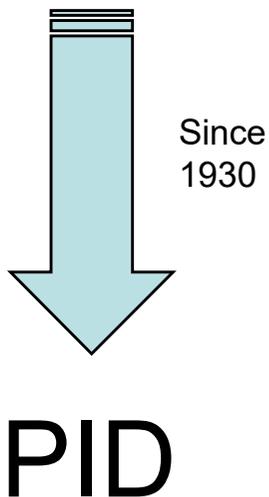

PID = **P**roportional **I**ntegral **D**erivative

Combine Three Terms for a PID

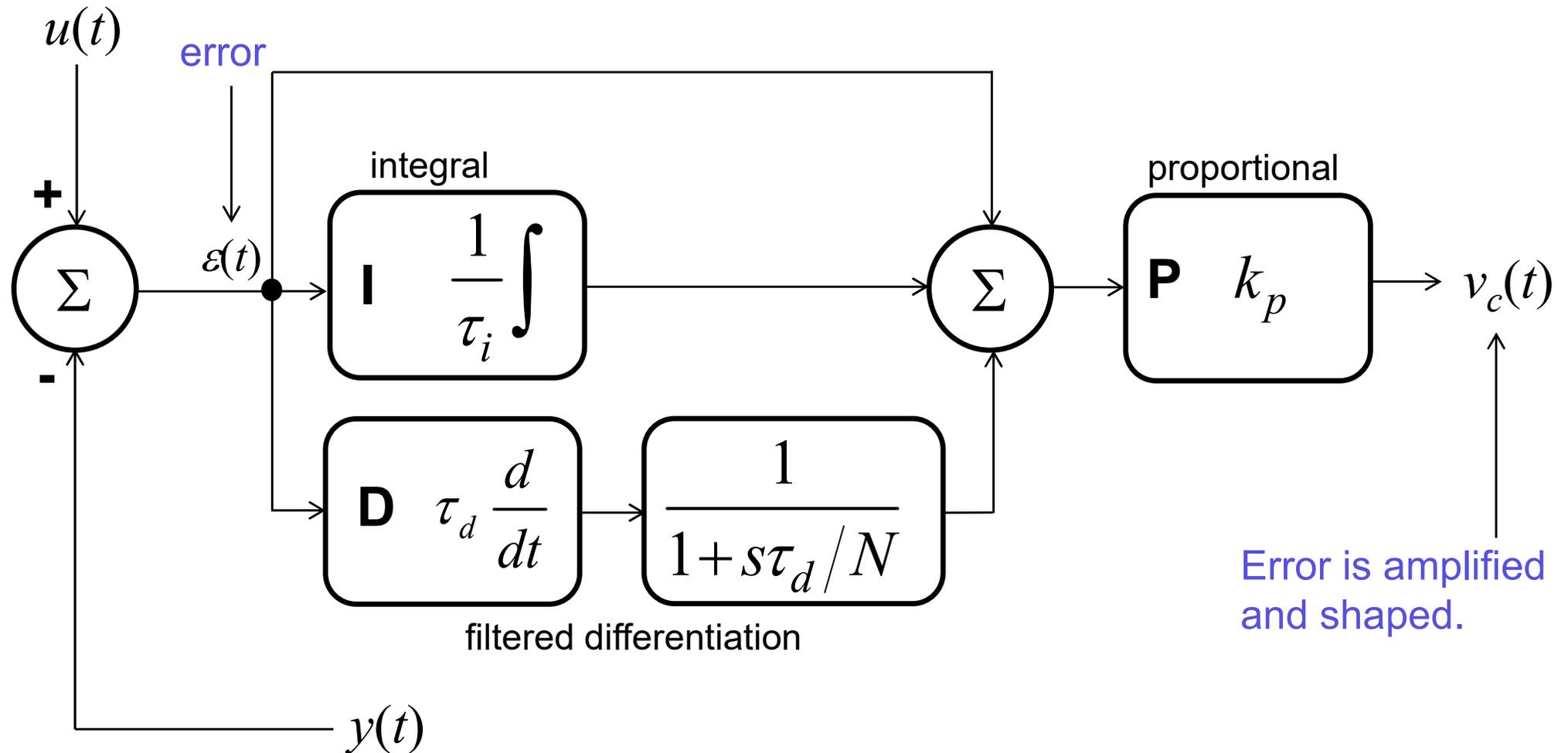- This is the filtered standard form of the PID




How do You Implement the PID?

- The compensator is the place where you apply corrections




The compensator: G

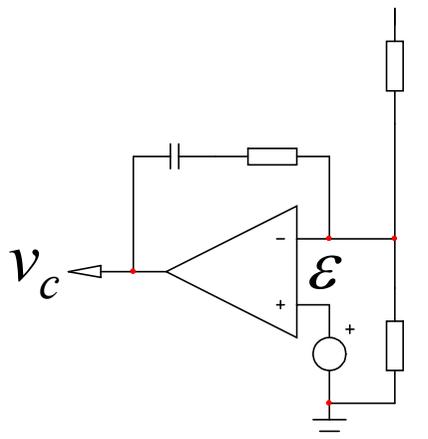
- The compensator is built with an error amplifier:



Op amp

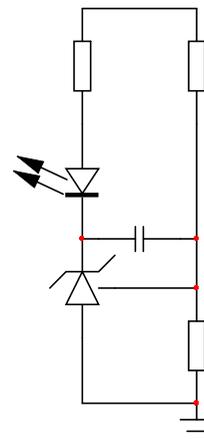


TL431

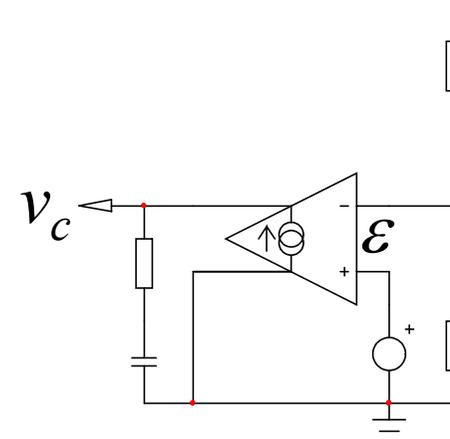

OTA

Build the PID with an Op Amp

- A type 3 compensator is a PID with an extra pole

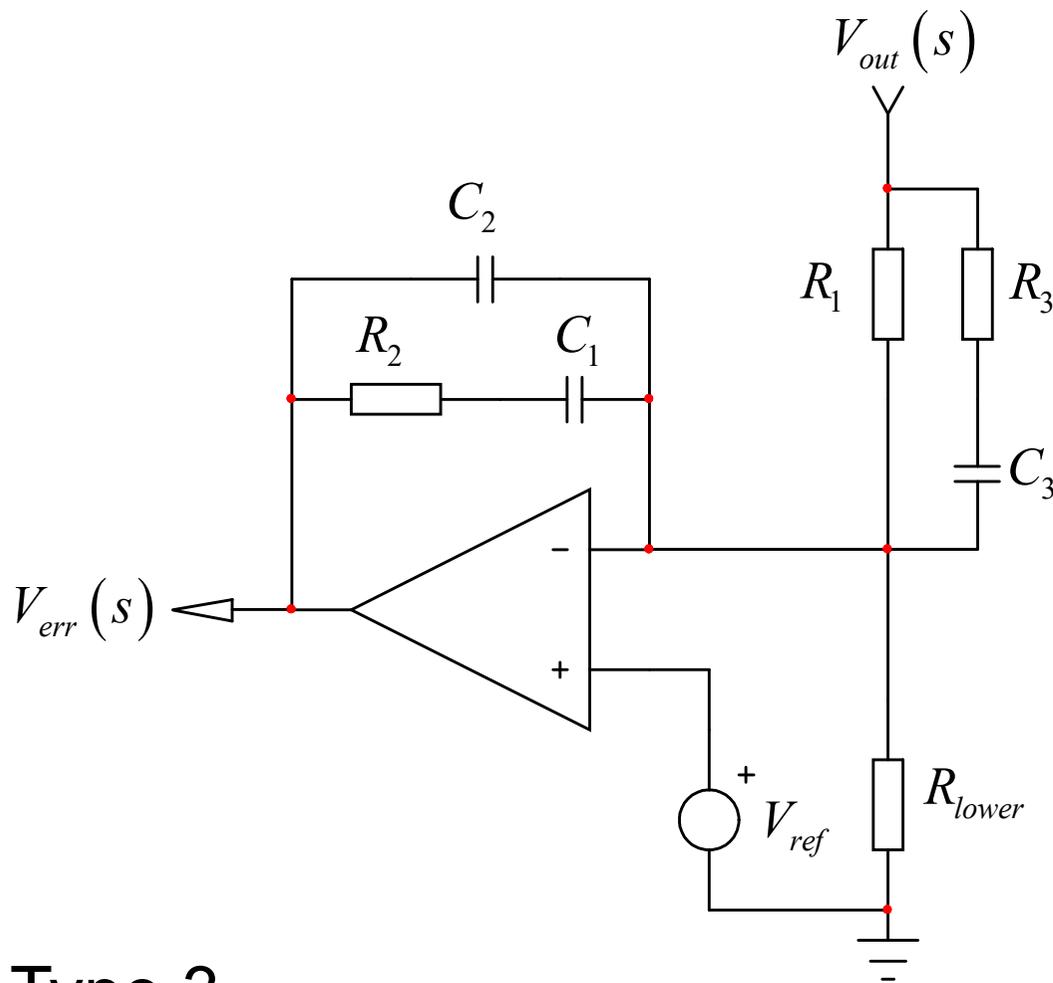

Type 3


$$G(s) = - \frac{1 + s \left(\frac{1}{s_{z_1}} + \frac{1}{s_{z_2}} \right) + s^2 \left(\frac{1}{s_{z_1} s_{z_2}} \right)}{\frac{s}{s_{po}} \left(1 + \frac{s}{s_{p_1}} \right) \left(1 + \frac{s}{s_{p_2}} \right)}$$

PID to type 3 Added pole

$$G(s) = - \frac{\left(1 + \frac{s}{s_{z_1}} \right) \left(1 + \frac{s}{s_{z_2}} \right)}{\frac{s}{s_{po}} \left(1 + \frac{s}{s_{p_1}} \right) \left(1 + \frac{s}{s_{p_2}} \right)}$$

A PI Compensator is Also Useful


- A PI version does not include a differentiation term

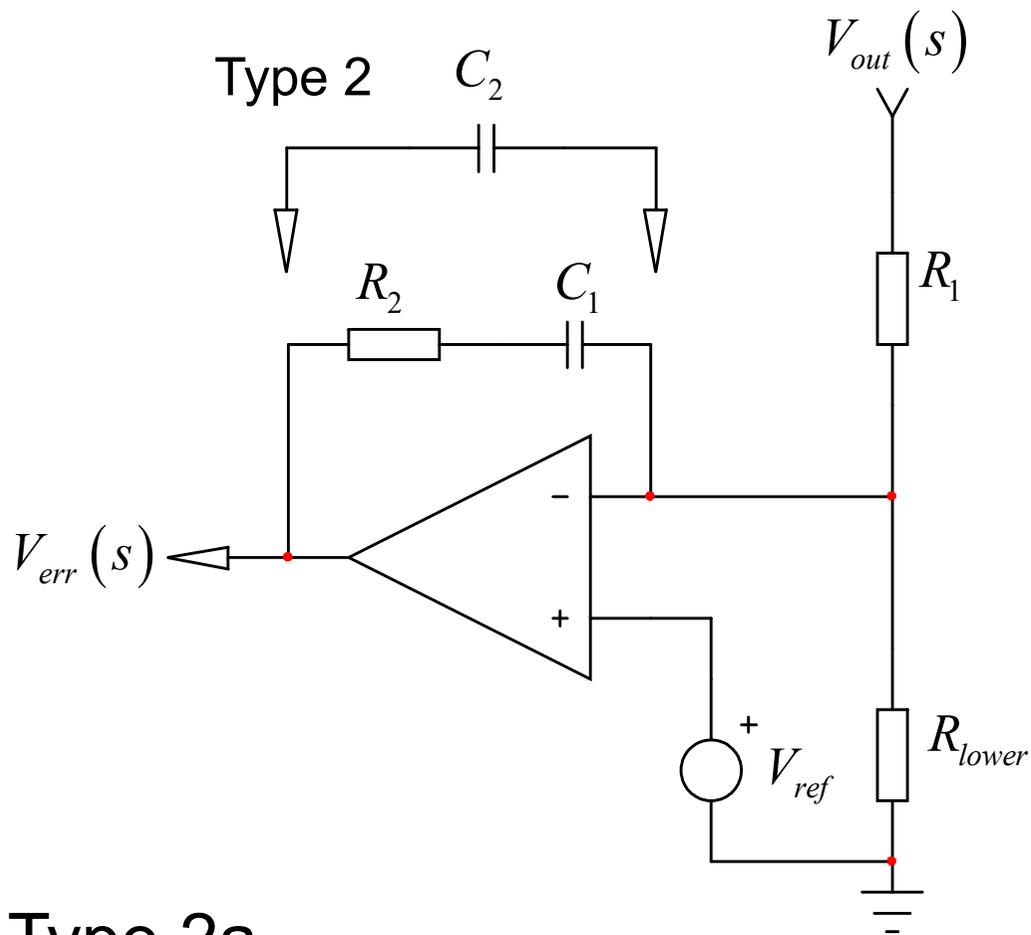

Type 2a


$$G(s) = -k_p \left(\frac{1 + s\tau_i}{s\tau_i} \right)$$

PI to
type 2a

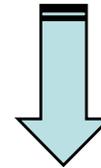

$$G(s) = -\frac{1 + s/s_{z_1}}{s/s_{p_0}}$$


2a to
type 2

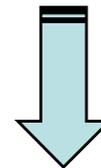

$$G(s) = -\frac{1 + s/s_{z_1}}{s/s_{p_0} (1 + s/s_{p_1})}$$

Compensation Strategy

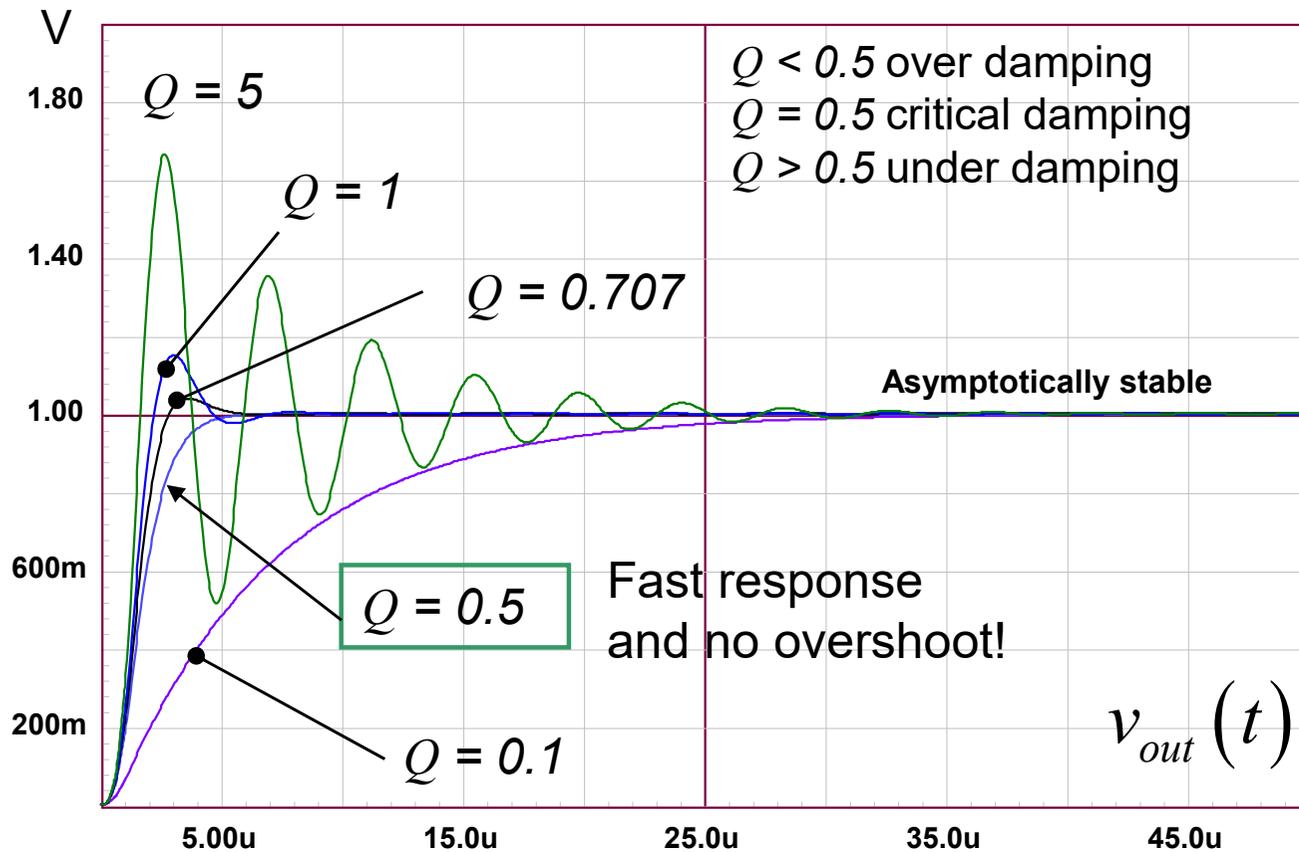1. Force crossover at the selected frequency f_c
2. Build phase margin at crossover
3. Ensure robustness with gain margin




Impact transient response

$$H(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$



Phase Margin Affects the Response

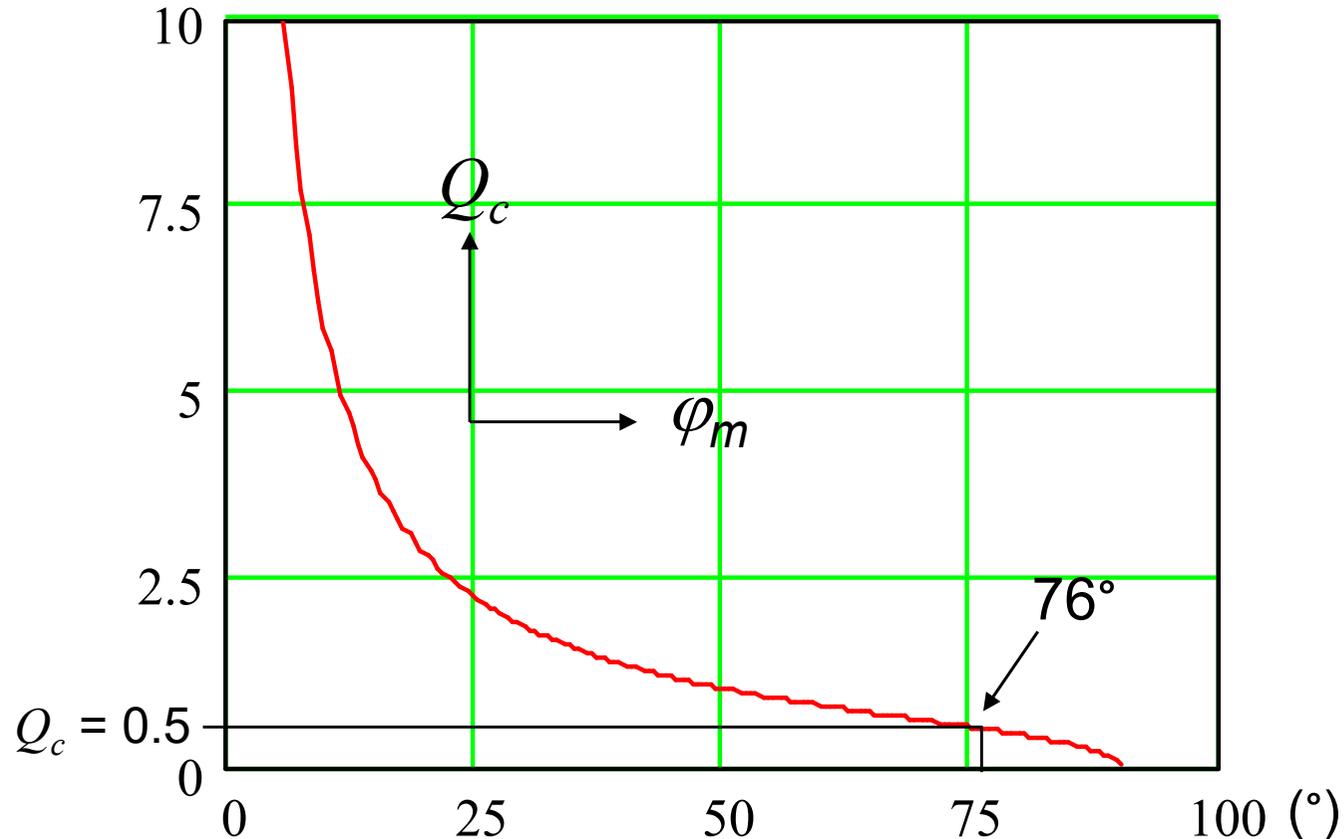
- Open-loop phase margin affects closed-loop response



- Select the phase margin based on the response you want

Imposing Crossover Frequency

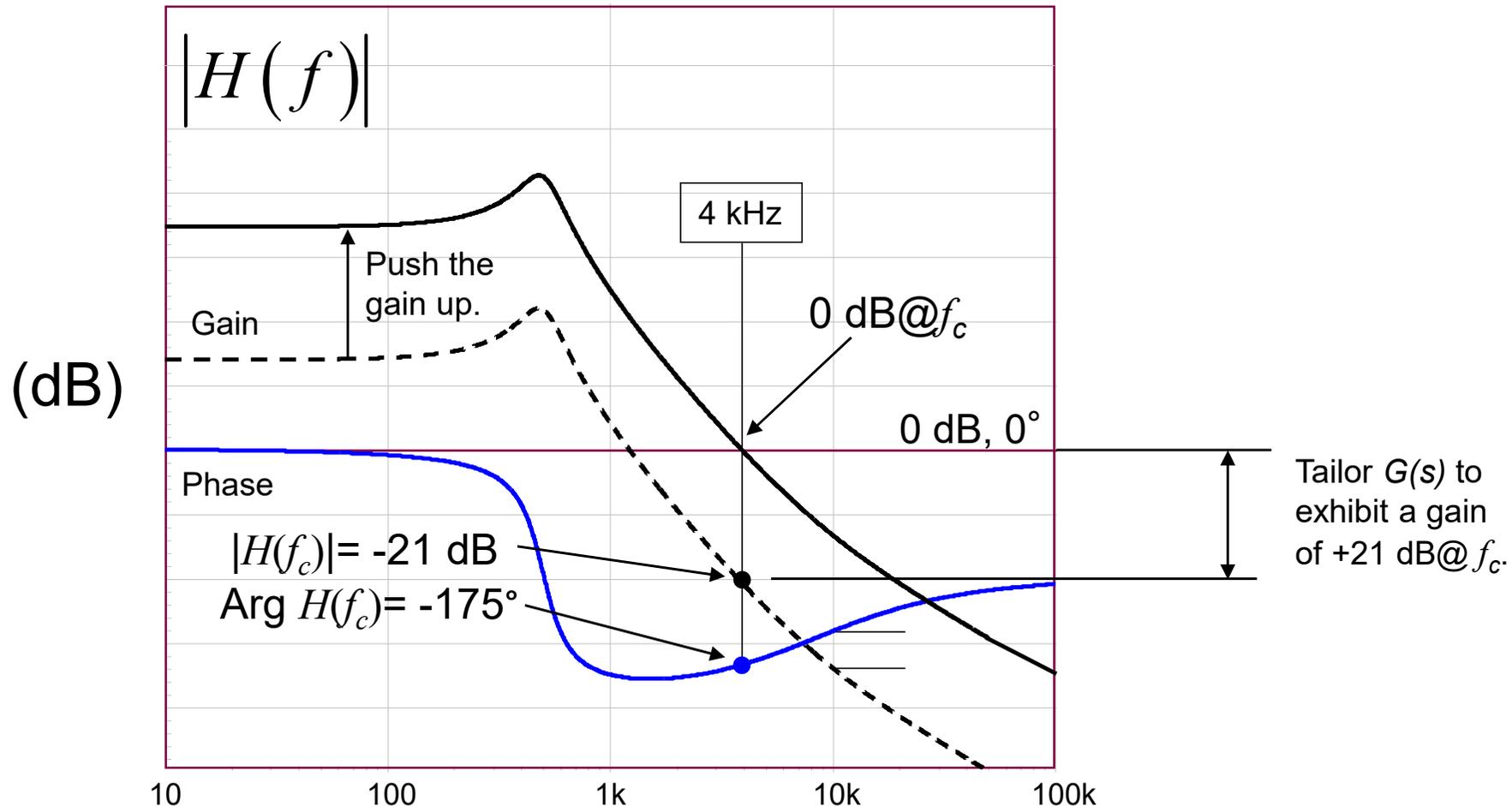- Compensate power stage gain excess or attenuation at f_c



- Tailor the compensator to provide attenuation at crossover

Combine Poles and Zeros to Boost Phase

- An transfer function where a pole and a zero are combined looks like

$$G(s) = \frac{\left(1 + \frac{s}{s_{z_1}}\right)}{\left(1 + \frac{s}{s_{p_1}}\right)} = \frac{N(s)}{D(s)}$$


- The argument of a quotient is: $\arg N - \arg D$

$$\arg G(f) = \arctan\left(\frac{f}{f_{z_1}}\right) - \arctan\left(\frac{f}{f_{p_1}}\right)$$

- Where does the phase peak (the boost) occur?

$$\frac{d\left(\arctan\left(\frac{f}{f_{z_1}}\right) - \arctan\left(\frac{f}{f_{p_1}}\right)\right)}{df} = 0$$


Max boost
occurs at:

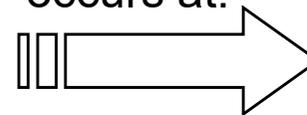

$$f = \sqrt{f_{z_1} f_{p_1}}$$

Split Poles and Zeros to Boost Phase

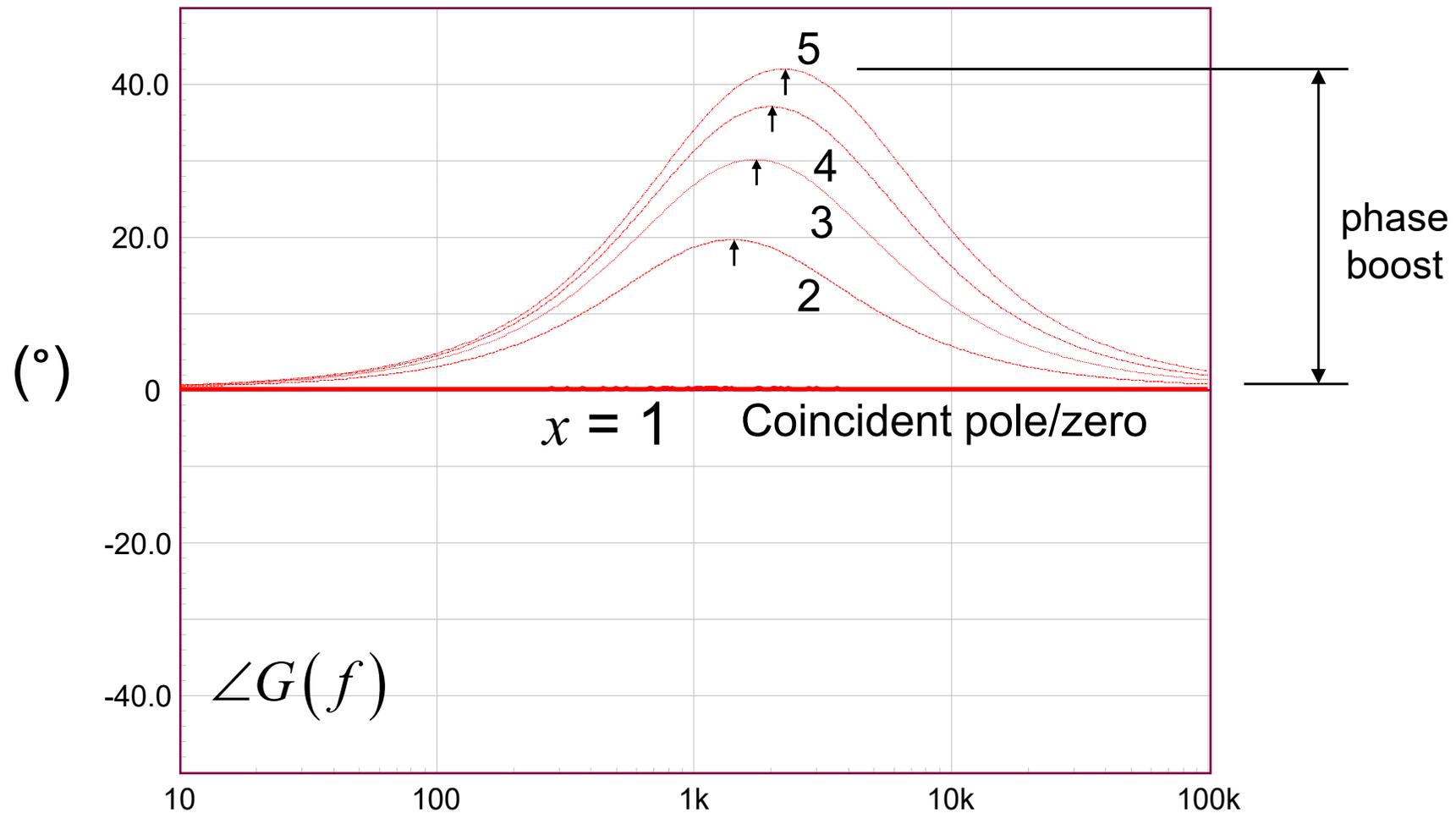
- A pole and zero are linked by $f_p = x \cdot f_z$



- Phase boost grows as pole(s) and zero(s) spread apart


Boost the Phase to Create Margin at f_c

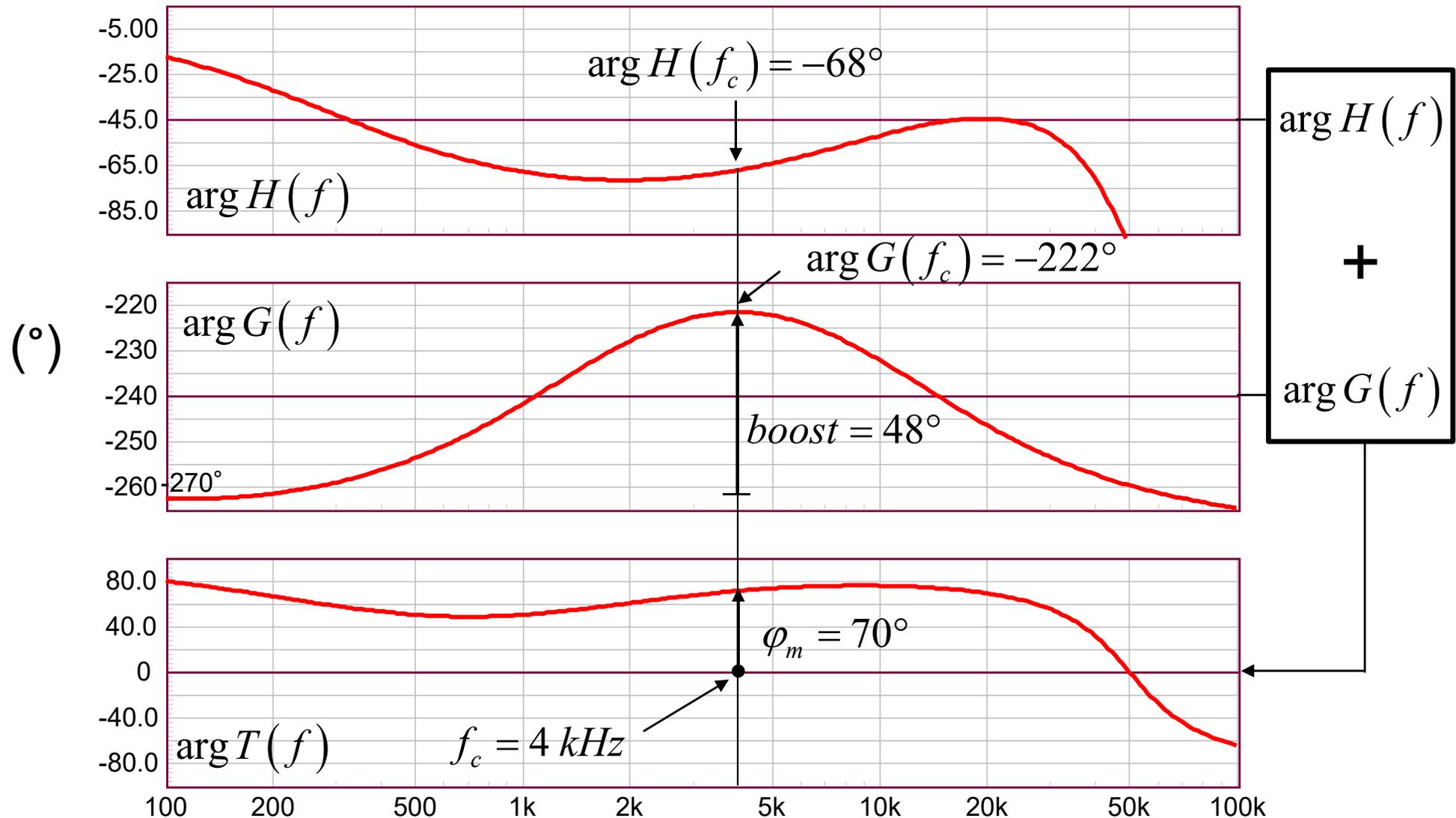- The pole has been placed at 10.4 kHz and the zero at 1.5 kHz




Three Compensator Types Exist

□ Boost the phase from 0 to 180° with 3 different filters

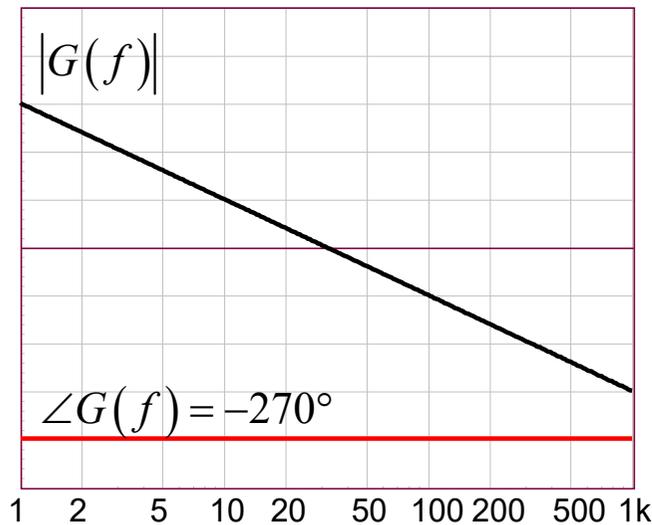


Type 1 – no boost

$$G_1(s) = -\frac{1}{\frac{s}{\omega_{po}}}$$

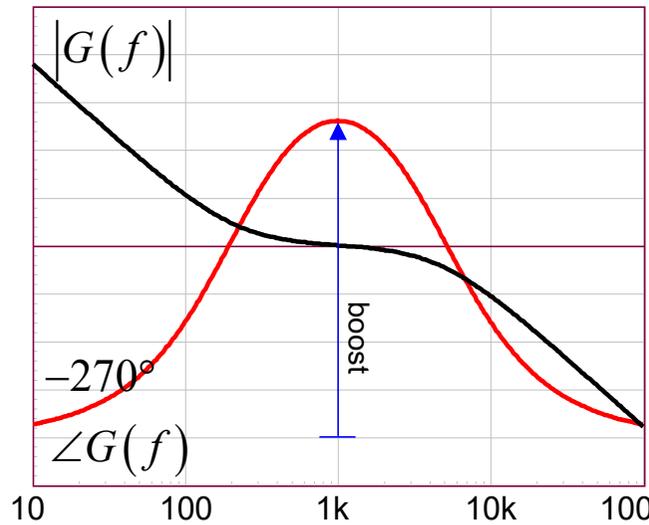

Type 2 – up to 90°

$$G_2(s) = -G_0 \frac{1 + \frac{s}{s_{z_1}}}{1 + \frac{s}{s_{p_1}}}$$

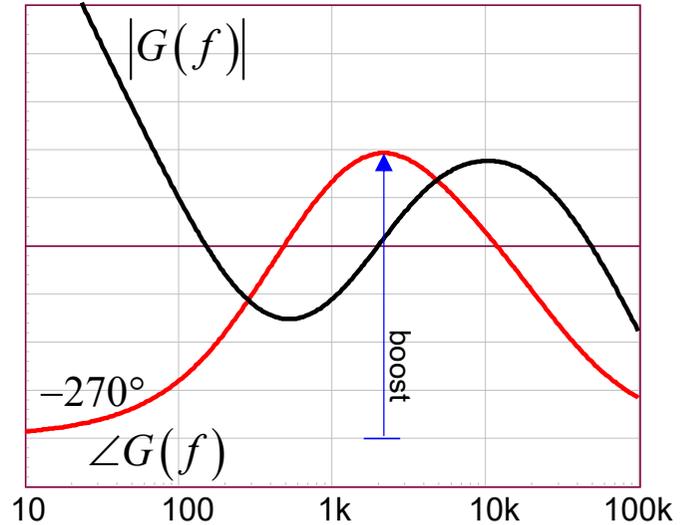

Type 3 – up to 180°

$$G_3(s) = -G_0 \frac{\left(1 + \frac{s}{s_{z_1}}\right) \left(1 + \frac{s}{s_{z_2}}\right)}{\left(1 + \frac{s}{s_{p_1}}\right) \left(1 + \frac{s}{s_{p_2}}\right)}$$


Course Agenda

- Control System Basics
- Operational Amplifier and Low-Frequency Pole**
- Gain-Bandwidth Impact on Phase Boost
- Op Amp Slew Rate Effects in Loop Control
- Start-Up Sequence and Auxiliary Supply
- Characterizing the Optocoupler Pole
- Dealing with the Fast Lane
- Going Around the TL431 Fast Lane



The Operational Amplifier

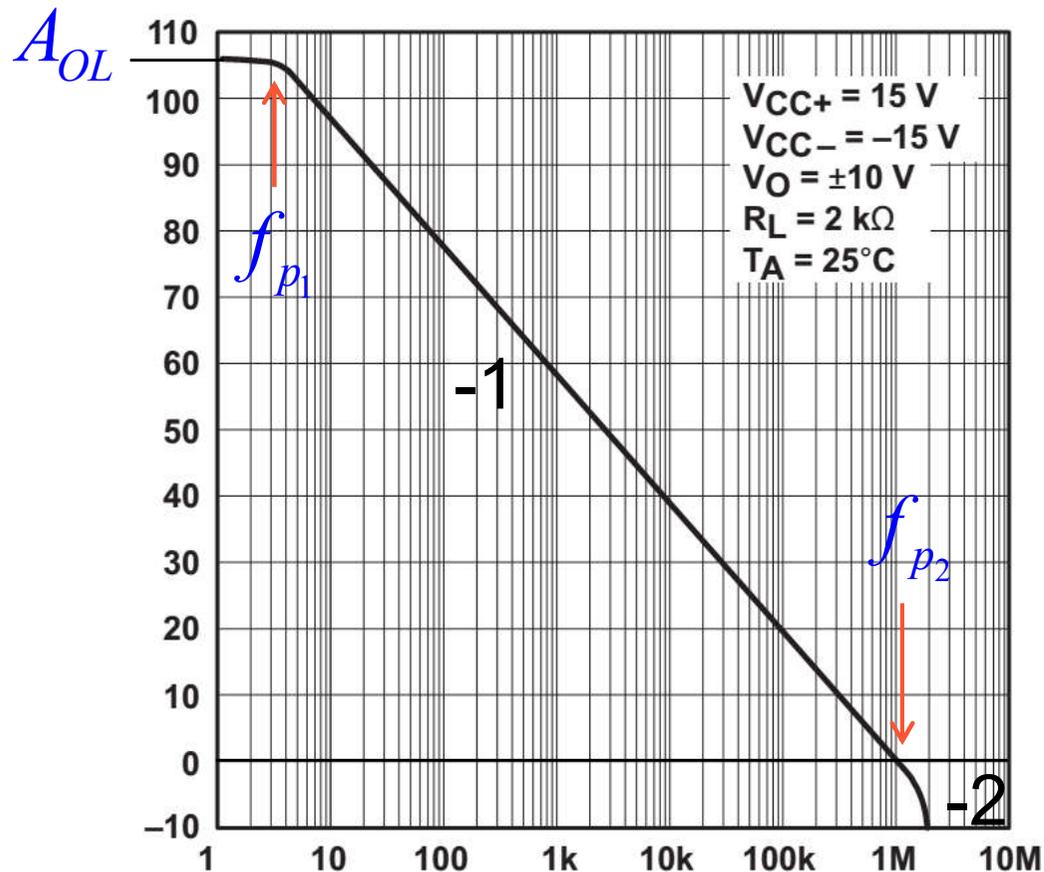
- ❑ For high bandwidth systems, compensators use op amps
- ❑ Op amps are affected by an open-loop gain and two poles



- ❑ How do these variables affect compensator performance?

Op Amp Simplified Internals

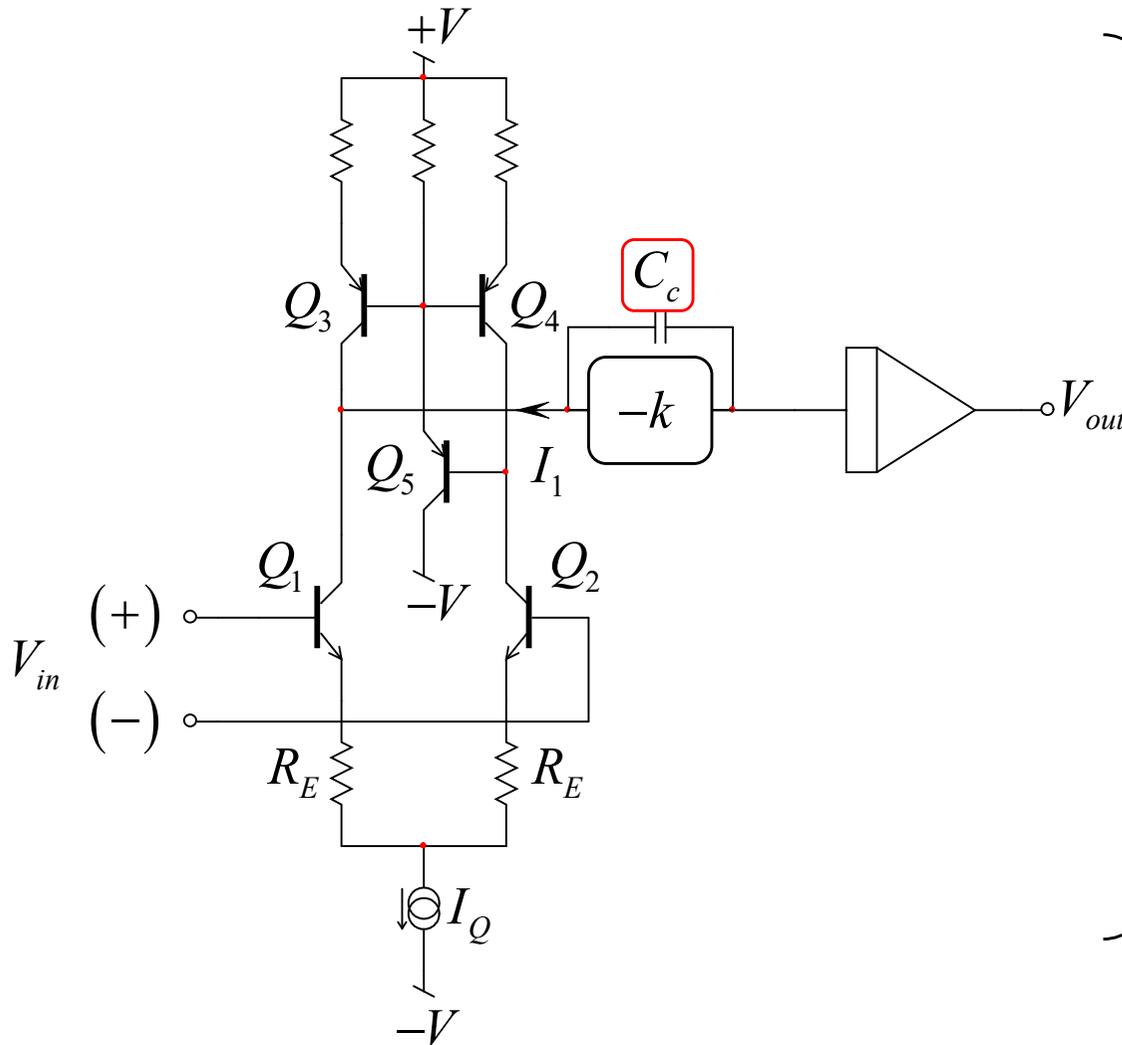- Capacitor C_c is key as compensating element



$$G(s) = \frac{A_{OL}}{1 + \frac{s}{\omega_{p1}}}$$

$$A_{OL} = \frac{k \cdot R_{eq}}{r_{\pi} + R_E}$$



$$\omega_{p1} = \frac{1}{(1+k) C_c R_{eq}}$$

↑
Miller effect

M. Leach, "Introduction to Electroacoustics and Audio Amplifier Design", Kendall/Hunt, 2003

Op Amp Gain-Bandwidth Product

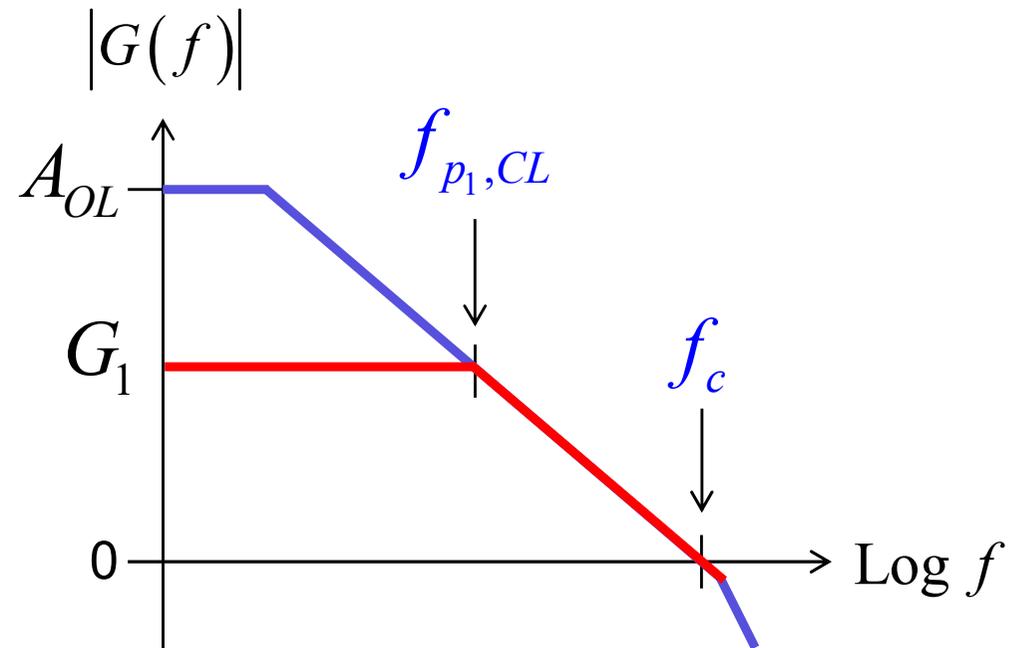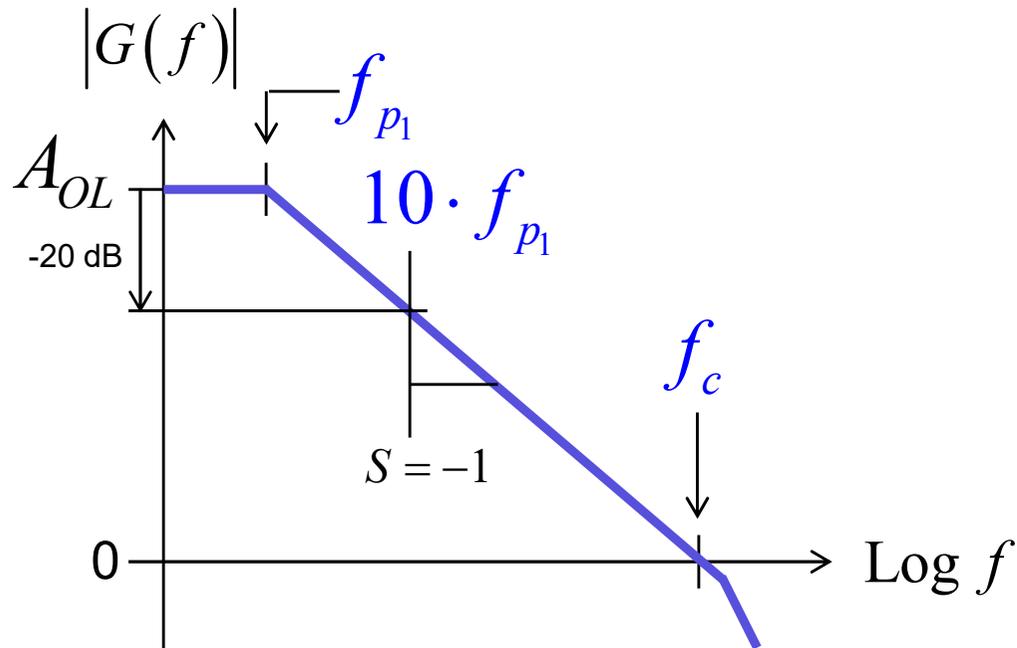- The 0-dB crossover point is at unity-gain frequency or GBW



$$S = \frac{\Delta y}{\Delta x} = \frac{-20 \text{ dB}}{\log\left(\frac{10 f_{p1}}{f_{p1}}\right)} = -20 \text{ dB/dec}$$

$$f_c = A_{OL} \times f_{p1} \longrightarrow \text{GBW}$$

$$\longrightarrow f_{p1,CL} = \frac{f_c}{G_1}$$


Accounting for the Open-Loop Gain

- The open-loop gain can vary quite a bit, see $\mu\text{A}741$ below

A_{VD}	Large-signal differential voltage amplification	$R_L \geq 2\text{k}\Omega$	25°C	20 200	50 200	V/mV
		$V_O = \pm 10\text{ V}$	Full range	15	25	

- ❖ How does it impact our compensator transfer function?

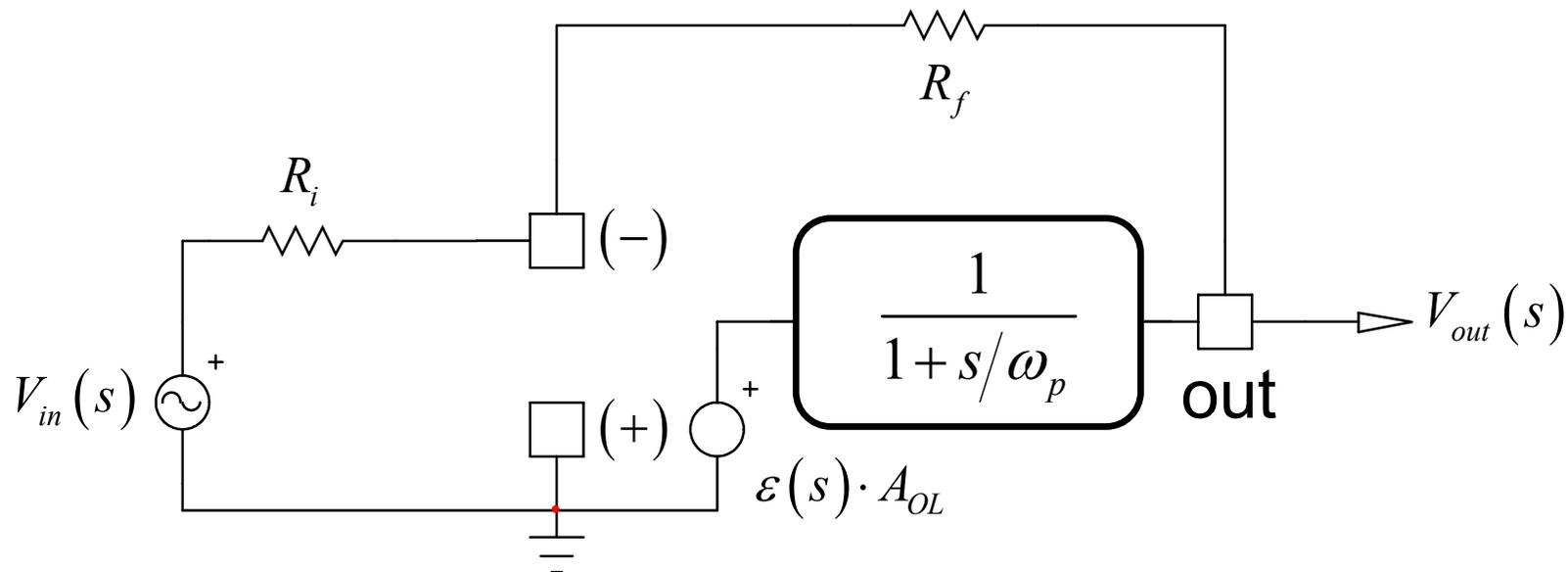- Let's take a simple inverting case, a proportional gain



C. Basso, "Designing Control Loops for Linear and Switching Power Supplies", Artech House, 2012

The Low-Frequency Pole Moves

□ The transfer function follows the form

$$G(s) = -\frac{R_f}{R_i + \frac{R_f + R_i}{A_{OL}}} \frac{1}{1 + s \frac{R_i + R_f}{\omega_p (R_f + R_i + A_{OL} R_i)}} = -G_0 \frac{1}{1 + \frac{s}{\omega_{eq}}}$$

□ The equivalent pole expression can be re-arranged


$$\omega_{eq} = \omega_p \frac{R_f + R_i + A_{OL} R_i}{R_f + R_i} \longrightarrow \frac{R_f}{R_i} \approx G \longrightarrow R_f \approx R_i G$$

$$\omega_{eq} = \omega_p \frac{R_i G + R_i + A_{OL} R_i}{R_i G + R_i} = \omega_p \frac{1 + G + A_{OL}}{1 + G} \quad \text{Factor } 1 + G \text{ and simplify}$$

$$\omega_{eq} = \omega_p \left(1 + \frac{A_{OL}}{1 + G} \right) \approx \frac{\omega_p A_{OL}}{1 + G} \quad \longrightarrow \quad \omega_{eq} \approx \frac{GBW}{1 + G}$$


What is the Impact on Transfer Function?

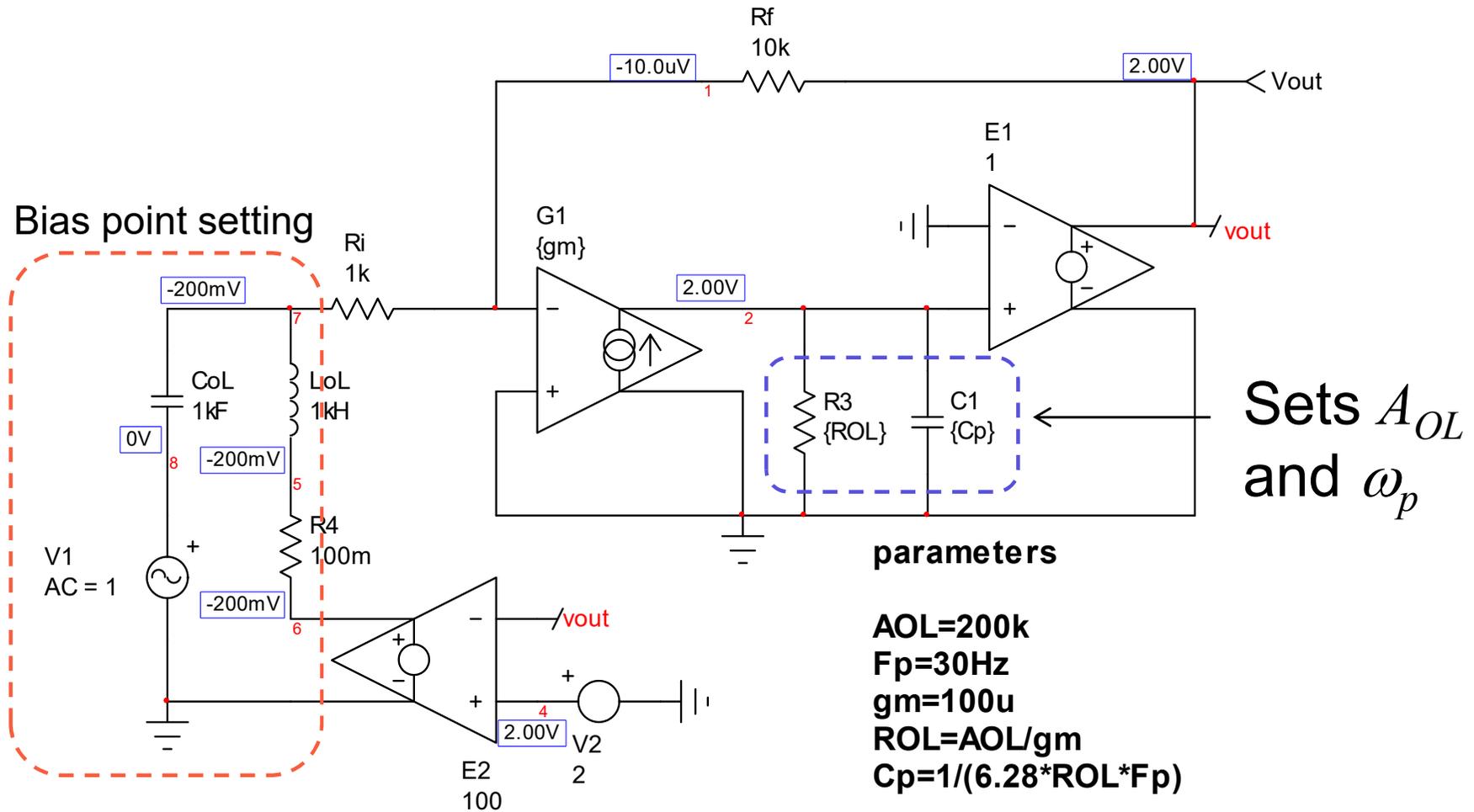- ❑ You need a wide-bandwidth voltage buffer – $A_{OL} = 200k$



Closed-Loop Bandwidth vs Gain

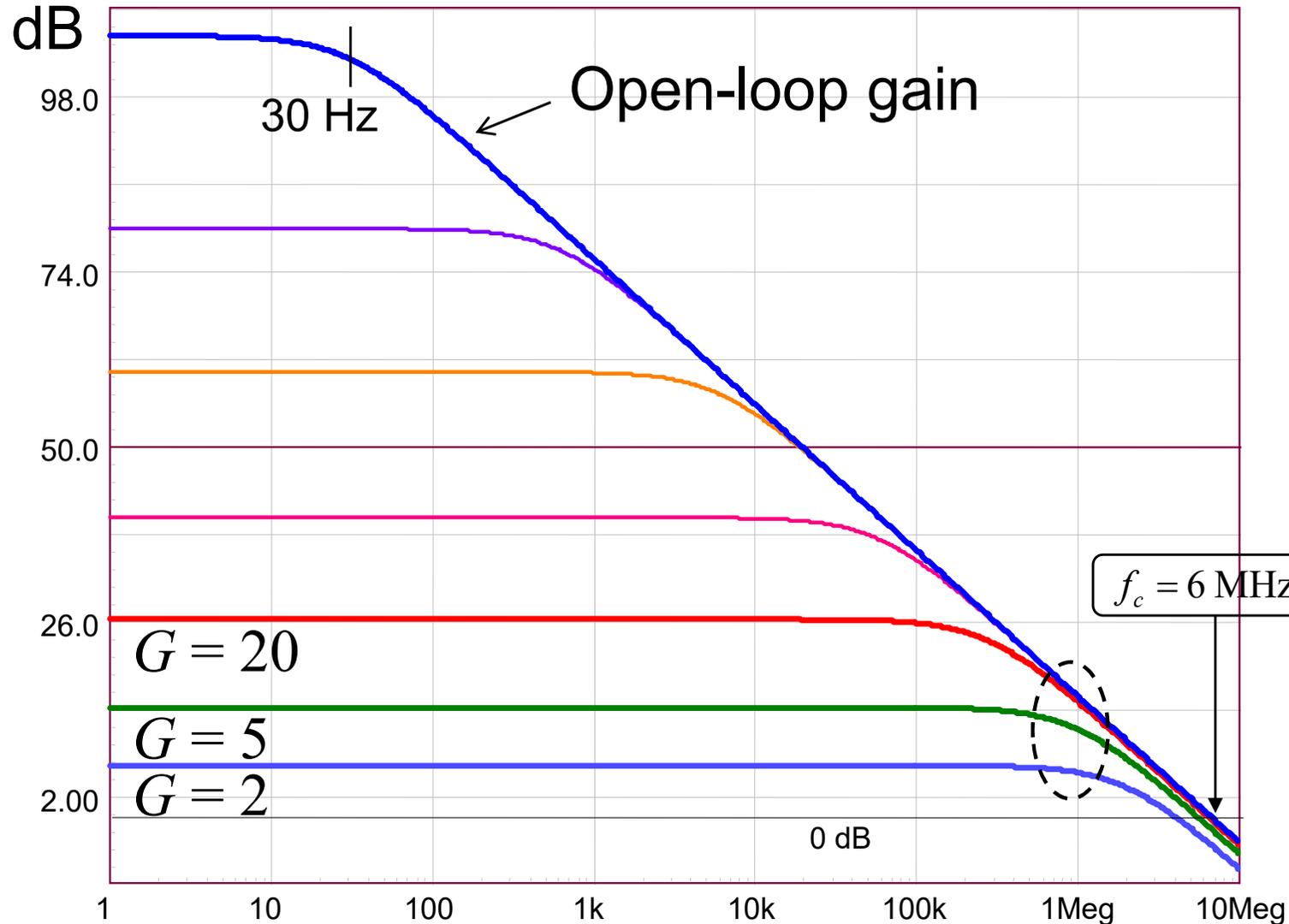- ❑ You need a wide-bandwidth voltage buffer – $A_{OL} = 200k$



$$f_{p1,CL} \approx \frac{f_c}{G_1}$$



$$f_{p1,CL} = \frac{f_c}{G_1 + 1}$$

Log f



Low-Frequency Pole Moves

- ❑ Too wide an open-loop gain dispersion brings additional lag

$$A_{OL} = 200k \text{ (106 dB)}$$

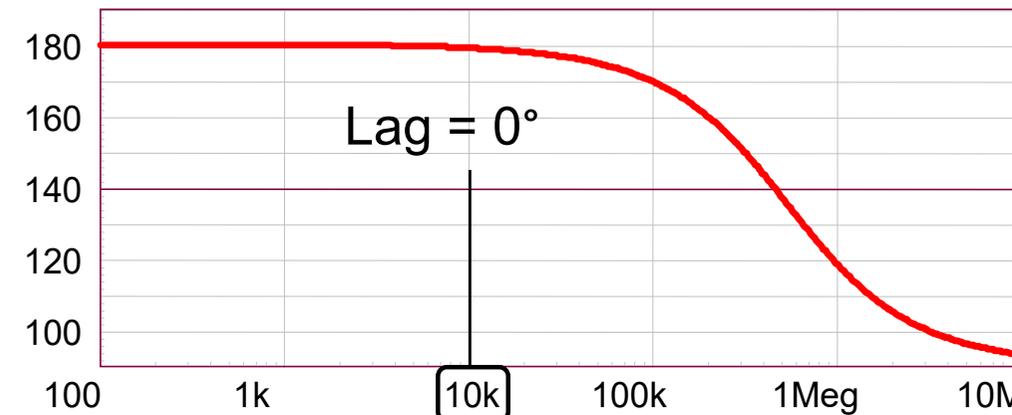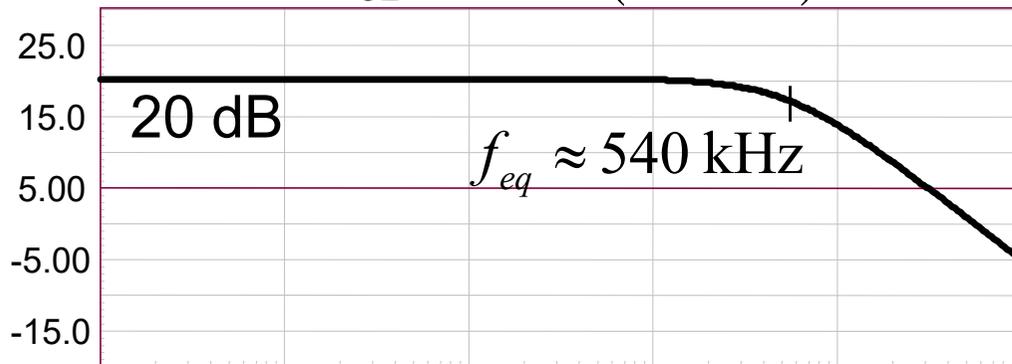

$$A_{OL} = 20k \text{ (86 dB)}$$

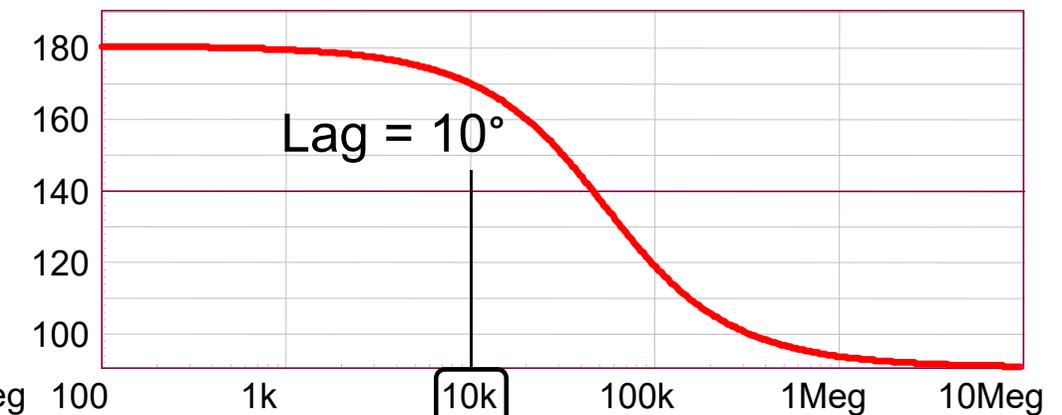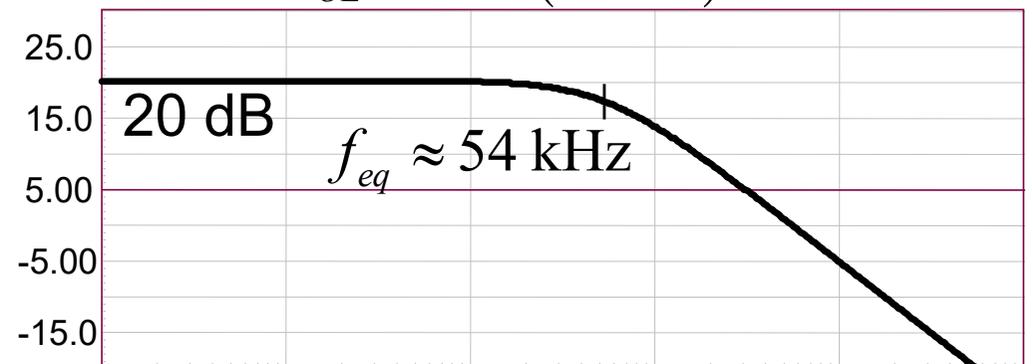

- ❑ A 20-dB difference in the open-loop gain divides BW by 10

Course Agenda

- ❑ Control System Basics
- ❑ Operational Amplifier and Low-Frequency Pole
- ❑ **Gain-Bandwidth Impact on Phase Boost**
- ❑ Op Amp Slew Rate Effects in Loop Control
- ❑ Start-Up Sequence and Auxiliary Supply
- ❑ Characterizing the Optocoupler Pole
- ❑ Dealing with the Fast Lane
- ❑ Going Around the TL431 Fast Lane




What Gain-Bandwidth is Needed?

- Assume a type III design for 130° boost and 25 dB at 200 kHz

parameters
Rupper=10k
fc=200k
pm=70
Gfc=-25
ps=-150

$G=10^{(-Gfc/20)}$
boost=pm-(ps)-90
 $\pi=3.14159$
 $K=(\tan((\text{boost}/4+45)*\pi/180))^2$
 $C2=1/(2*\pi*fc*G*Rupper)$
 $C1=C2*(K-1)$
 $R2=\text{sqrt}(k)/(2*\pi*fc*C1)$
 $R3=Rupper/(k-1)$
 $C3=1/(2*\pi*fc*\text{sqrt}(k)*R3)$

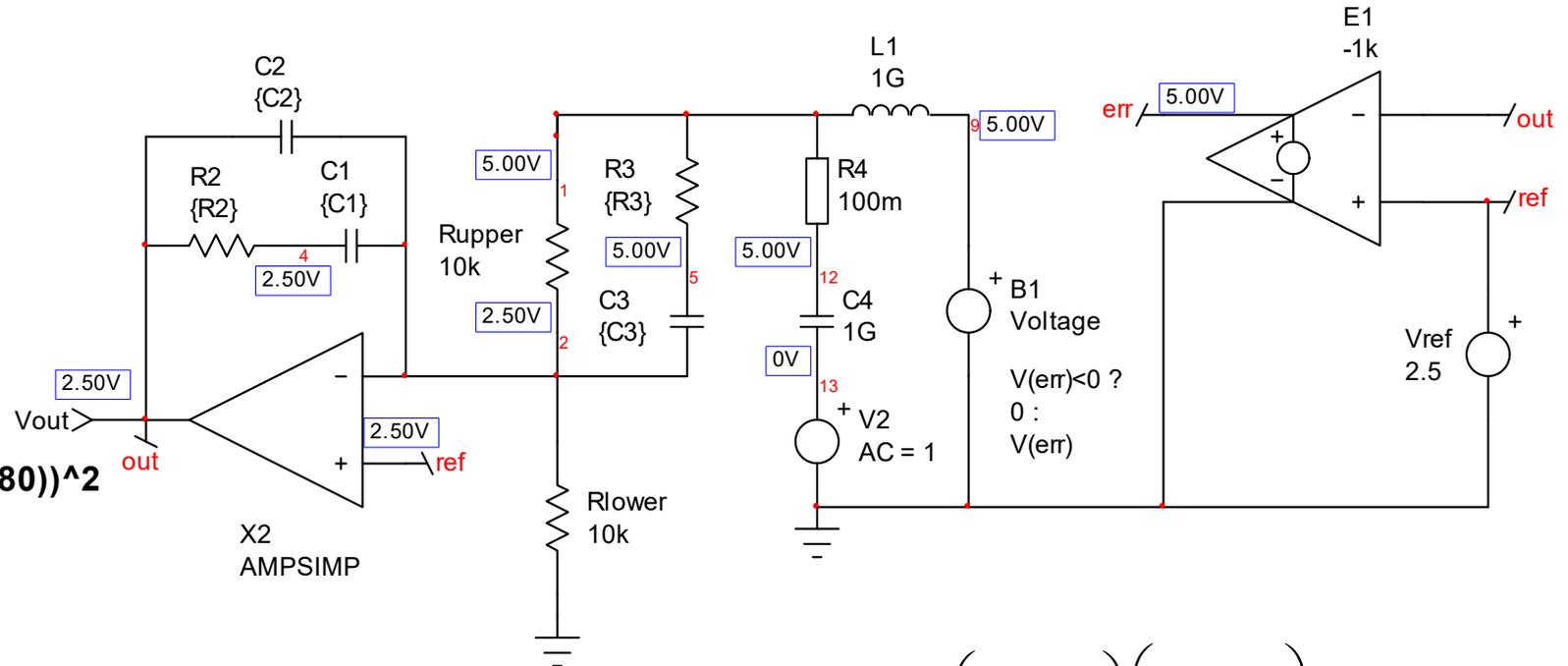
$fp1=1/(2*\pi*R2*C2)$
 $fp2=1/(2*\pi*R3*C3)$
 $fz1=1/(2*\pi*R2*C1)$
 $fz2=1/(2*\pi*Rupper*C3)$



$$G(s) = -G_0 \frac{\left(1 + \frac{s}{z_1}\right) \left(1 + \frac{s}{s_{z_2}}\right)}{\left(1 + \frac{s}{s_{p_1}}\right) \left(1 + \frac{s}{s_{p_2}}\right)}$$


Type III Response with a Perfect Op Amp

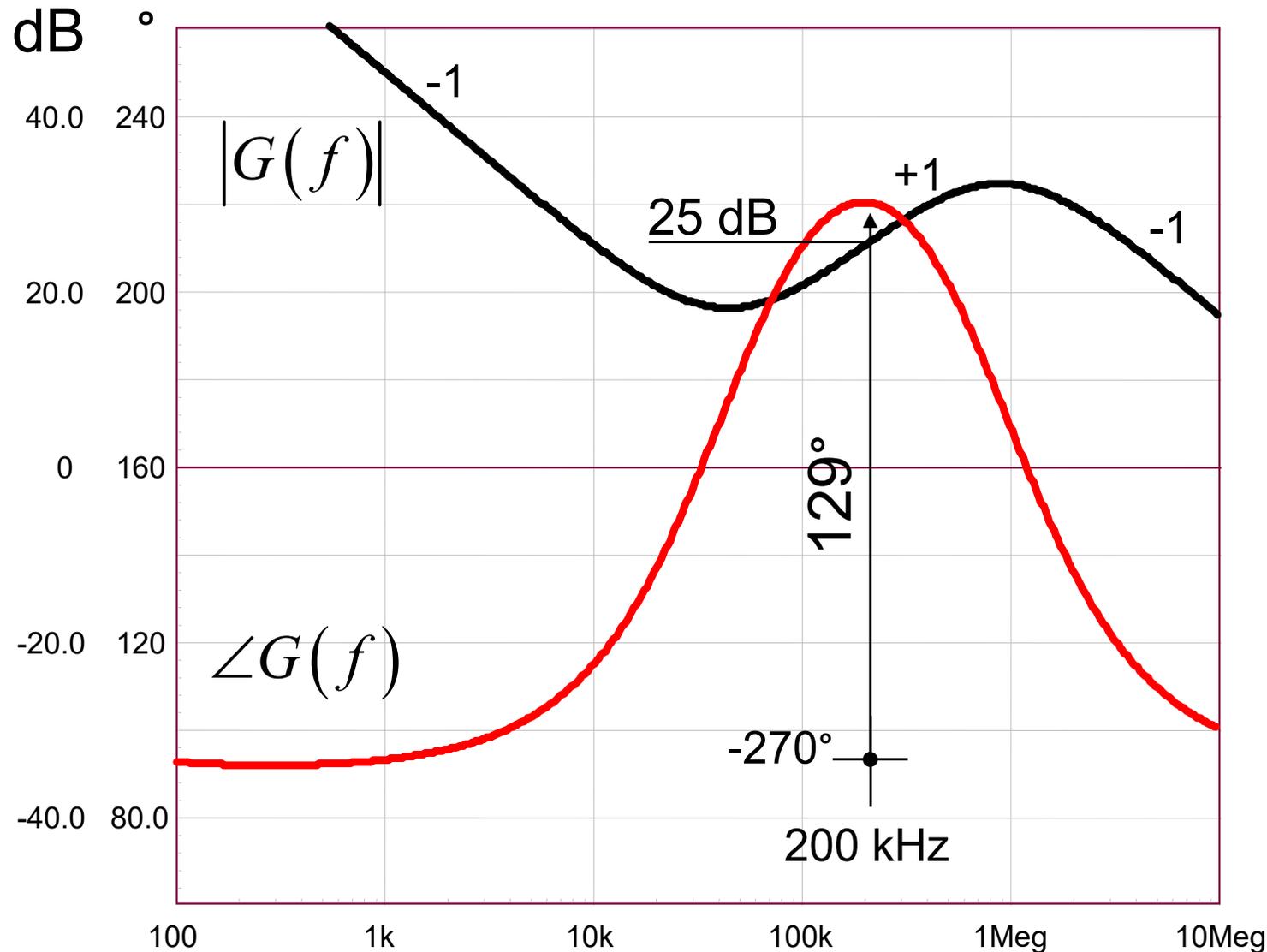- Excellent ac response at 200 kHz with a perfect op amp




True Op Amp Degrades Phase Boost

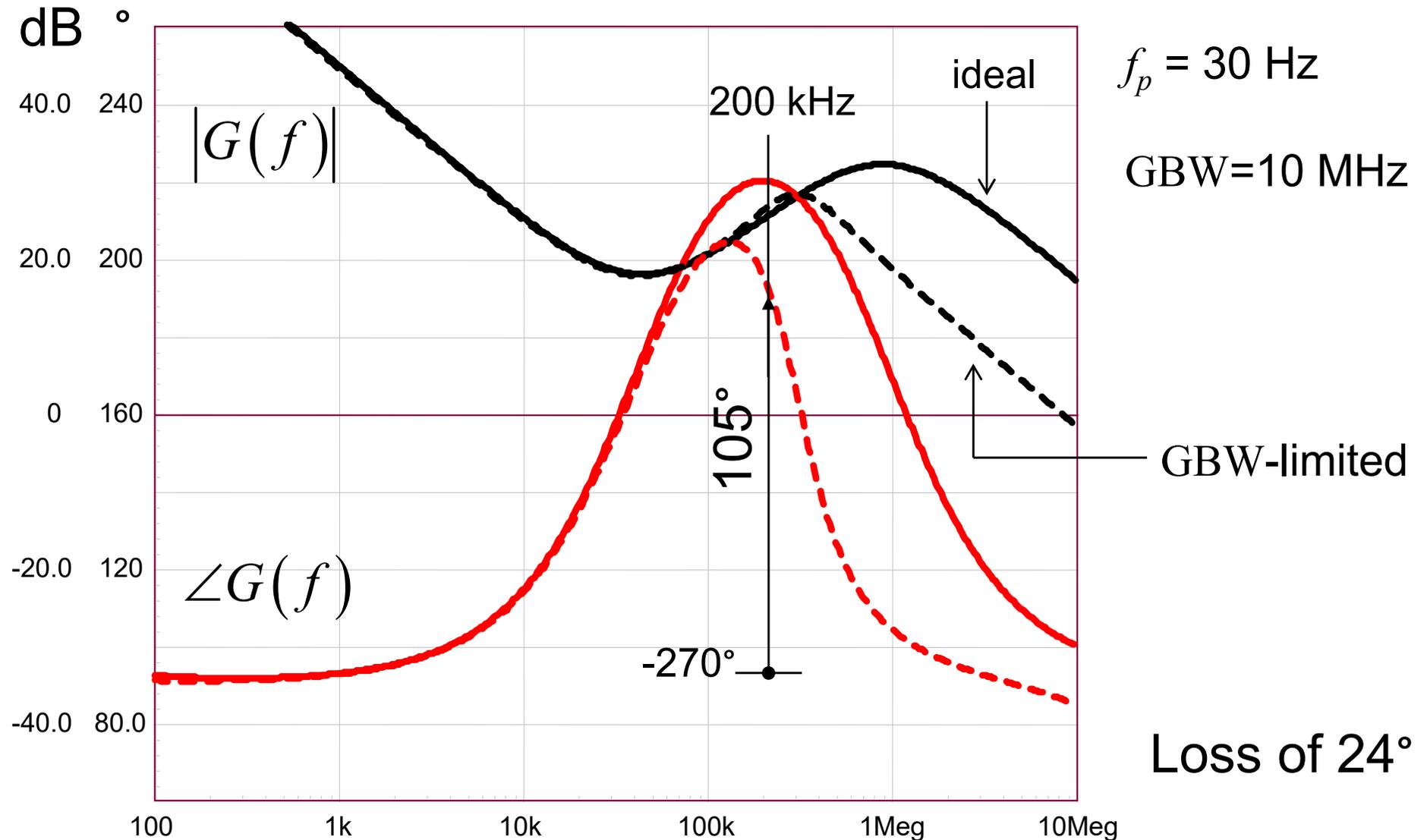- Phase boost is affected by a 10-MHz gain bandwidth product




Superimpose the Op Amp Ac Response

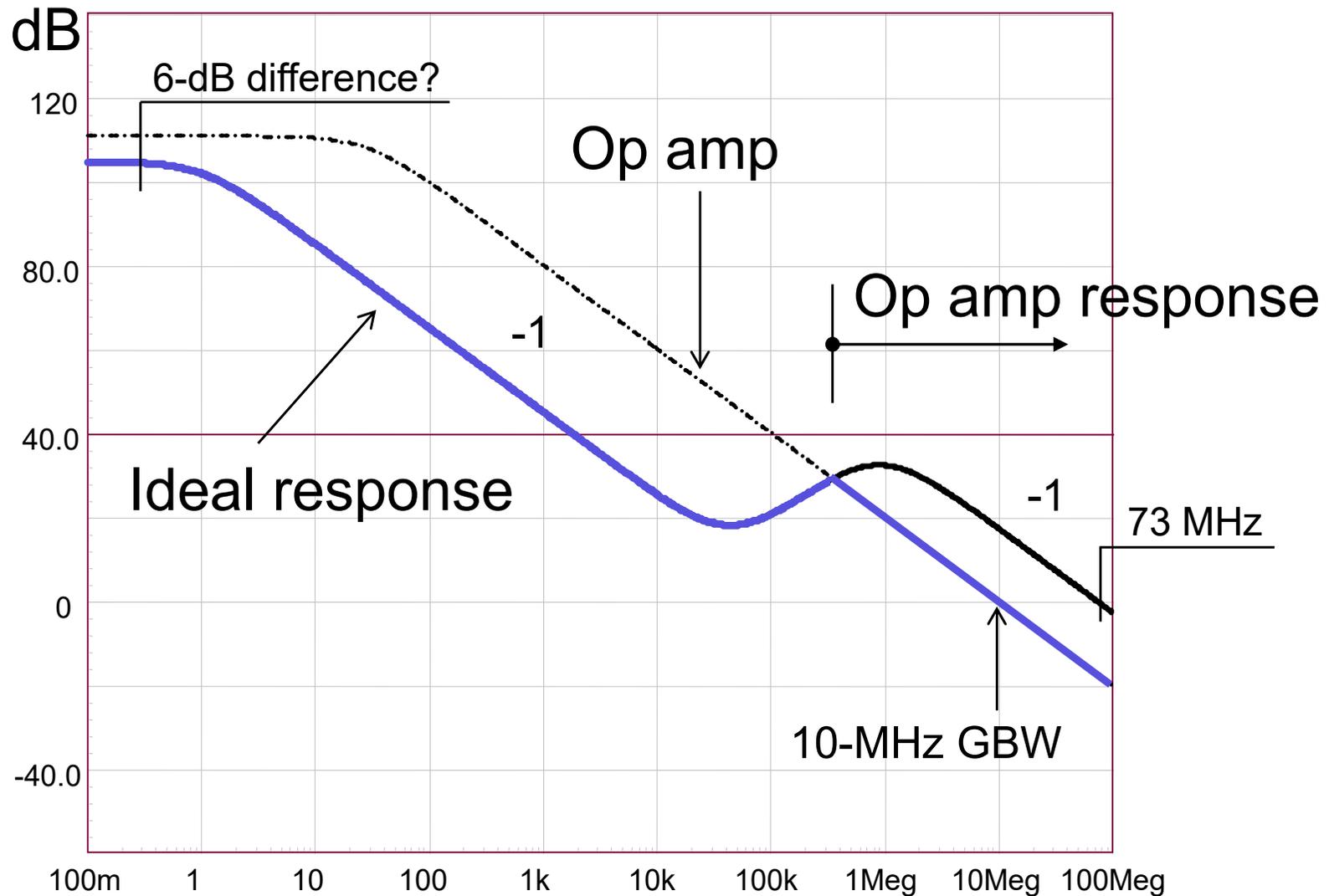- The selected op amp GBW leads response at high frequency



Why is there a Change in the Dc Gain?

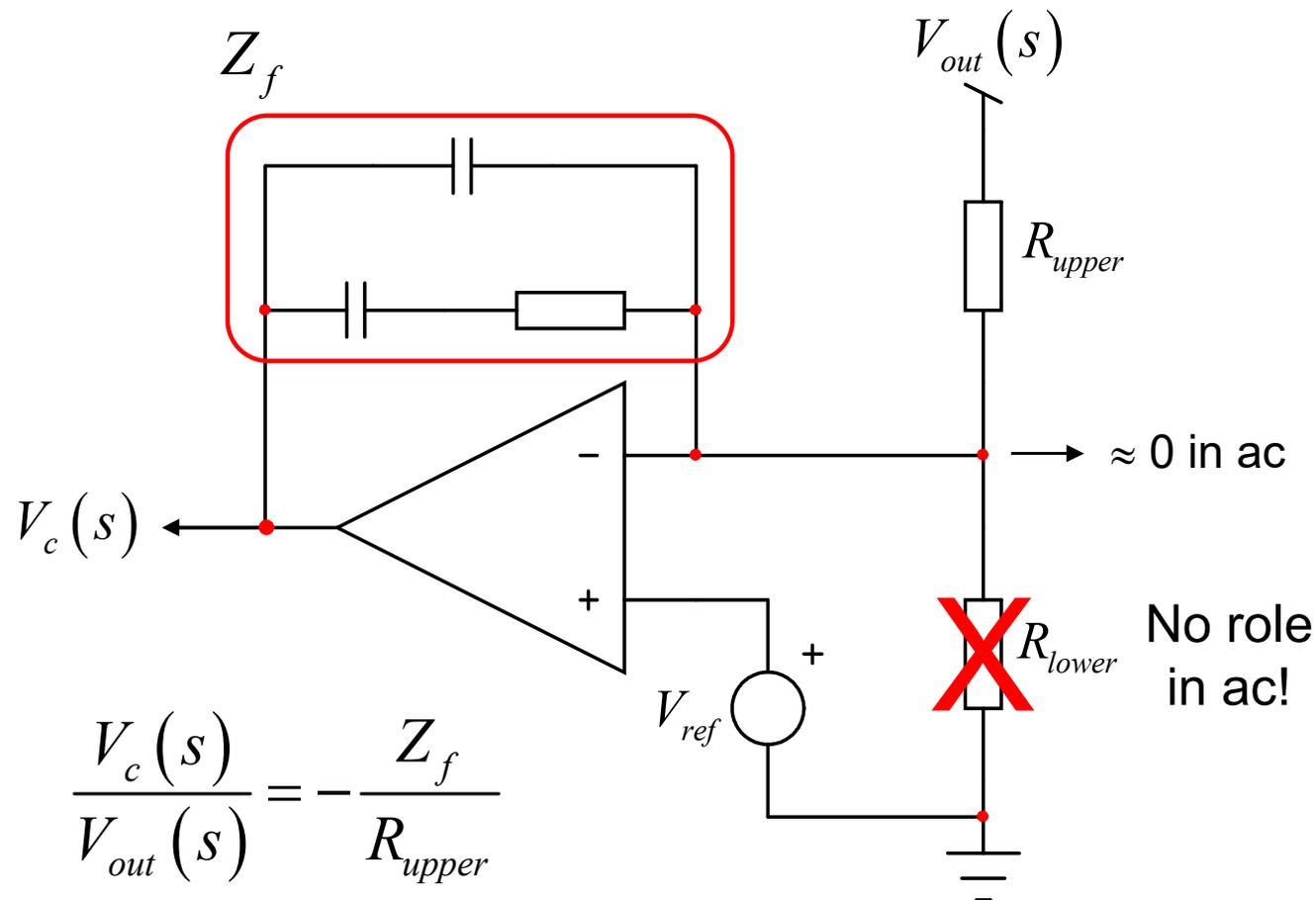
- Because of local feedback, the op amp builds a virtual ground



- The virtual ground excludes the lower resistor R_{lower}

The Divider Ratio is Back in Dc

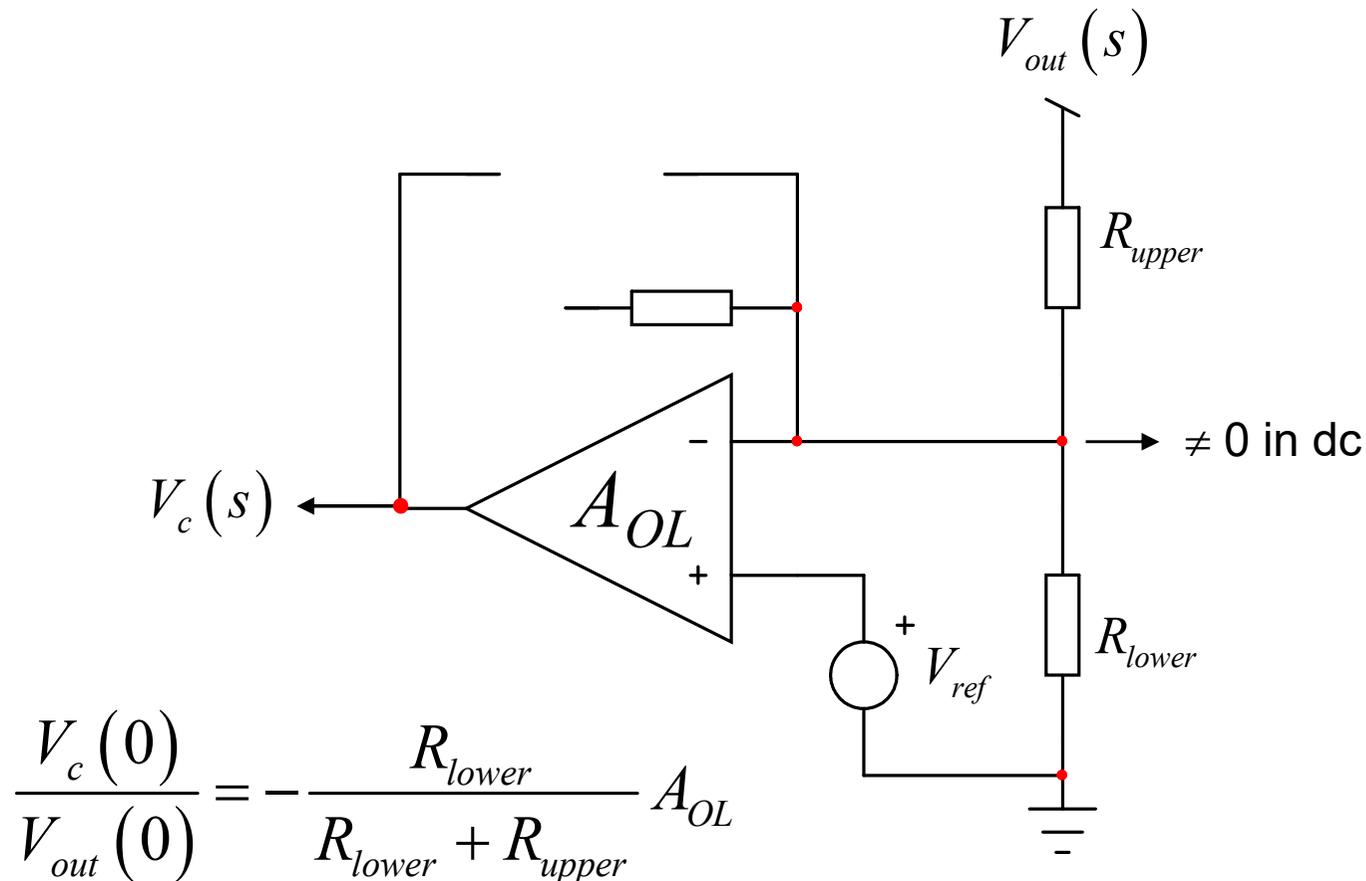
- In a type 1, 2 or 3, the local feedback is lost for $s = 0$



- The 0-Hz gain is indeed changed but not f_c !


The Division Ratio Affects the Dc Gain Alone

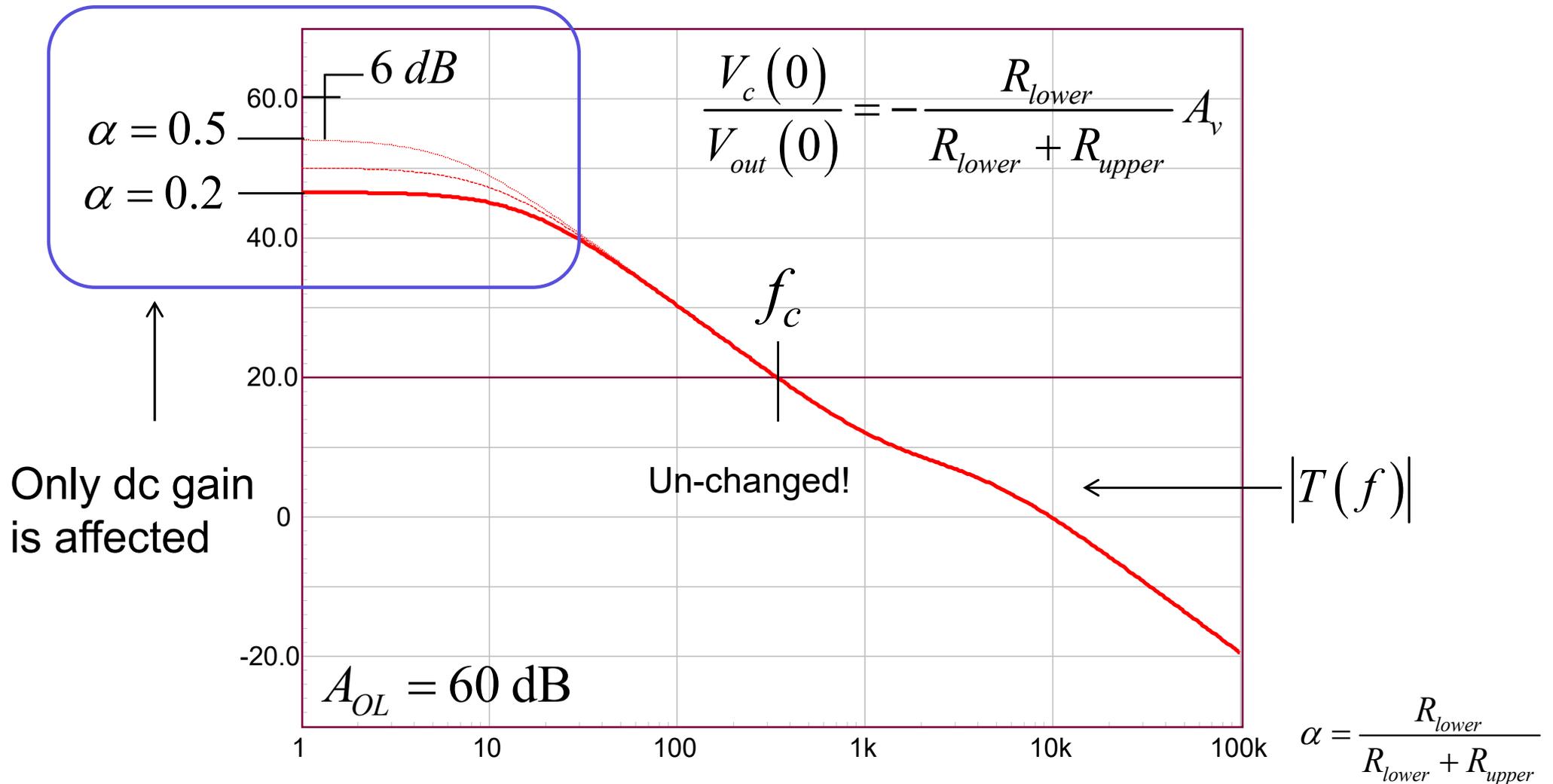- The division ratio is changed to adjust V_{out} : f_c is unchanged



Select Higher GBW Op Amplifiers

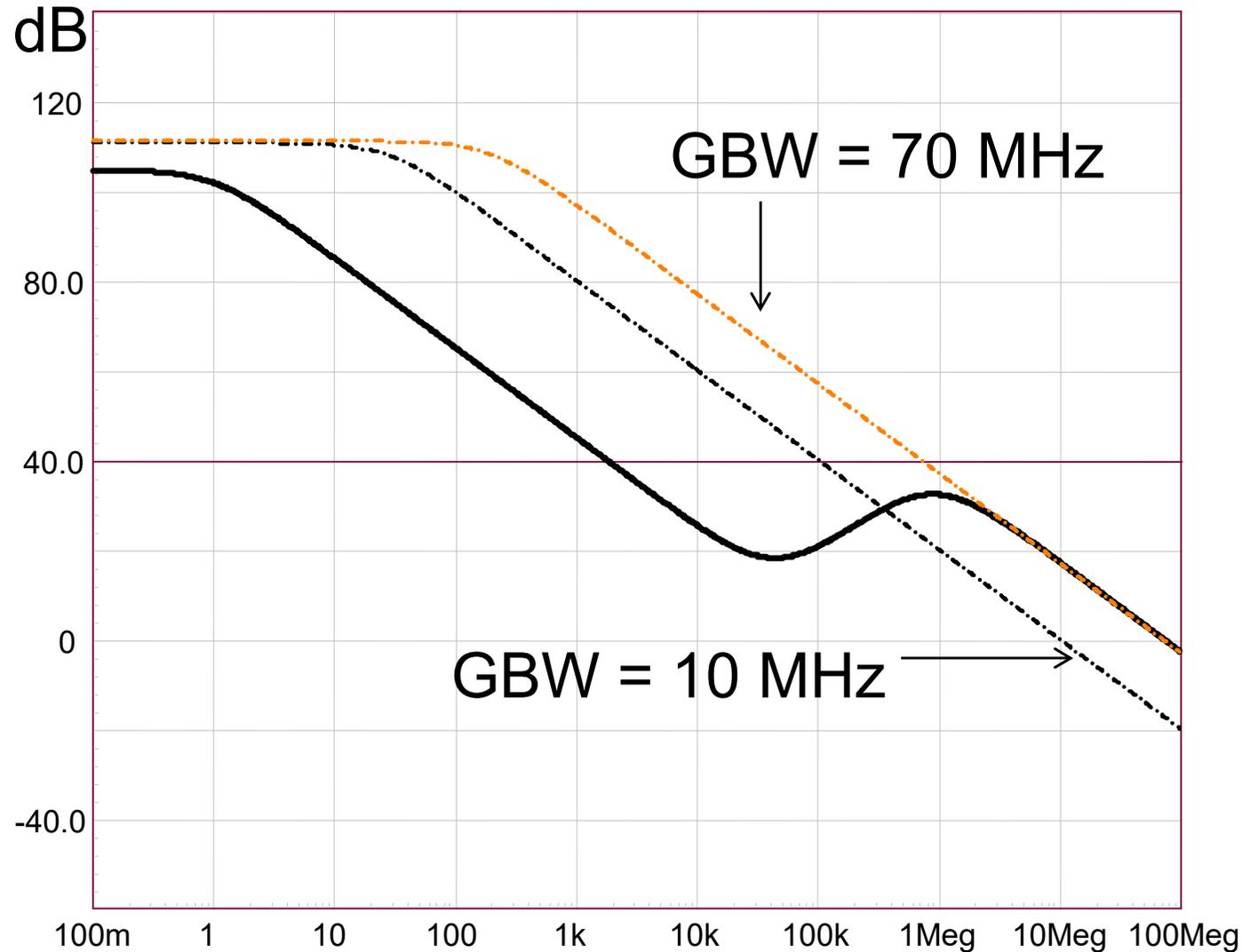
- Choose an op amp whose GBW is the type 3 0-dB f_c



T. Hegarty, "Error Amp. Limitations in High Performance Regulator Applications", AN-1997, Texas Inst.

Final Phase Distortion is Low

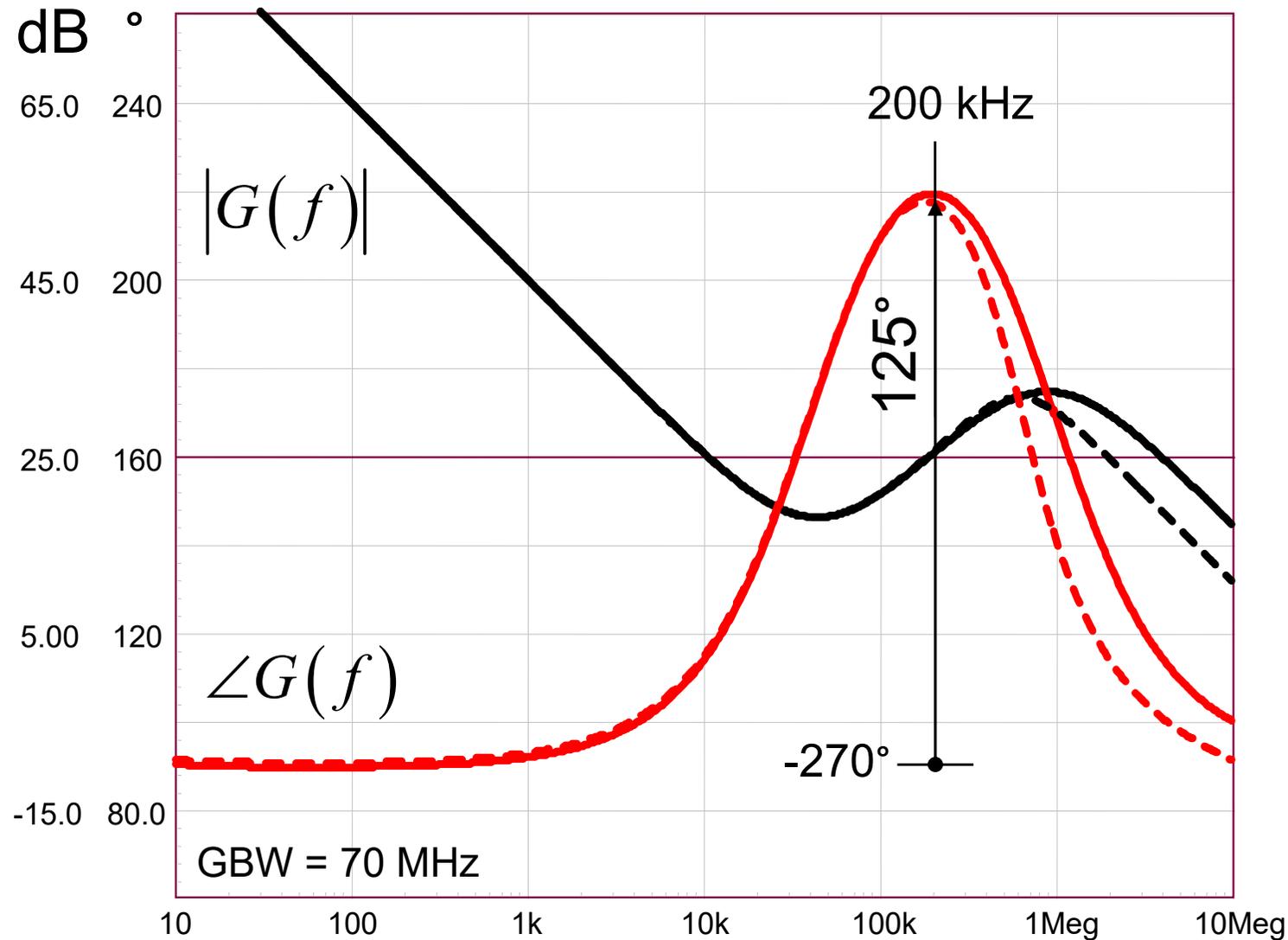- With the right GBW, impact on the final phase boost is low




Course Agenda

- Control System Basics
- Operational Amplifier and Low-Frequency Pole
- Gain-Bandwidth Impact on Phase Boost
- Op Amp Slew Rate Effects in Loop Control**
- Start-Up Sequence and Auxiliary Supply
- Characterizing the Optocoupler Pole
- Dealing with the Fast Lane
- Going Around the TL431 Fast Lane




Slew Rate in an Op Amp

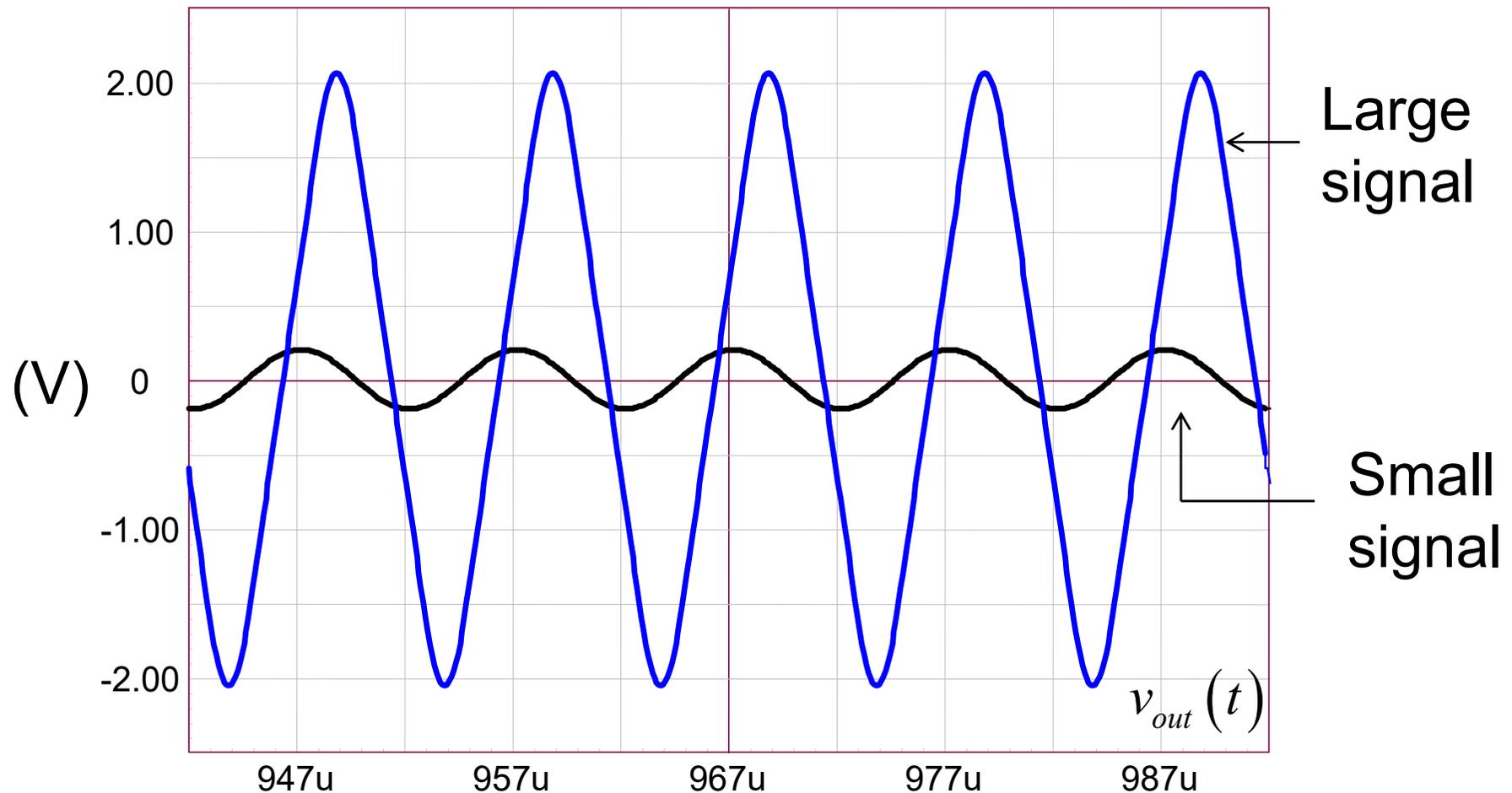- ❑ Small-signal analysis implies small output dynamics
- ❑ Step load response often involves large-signal behavior



Why Does the Op Amp Slew?

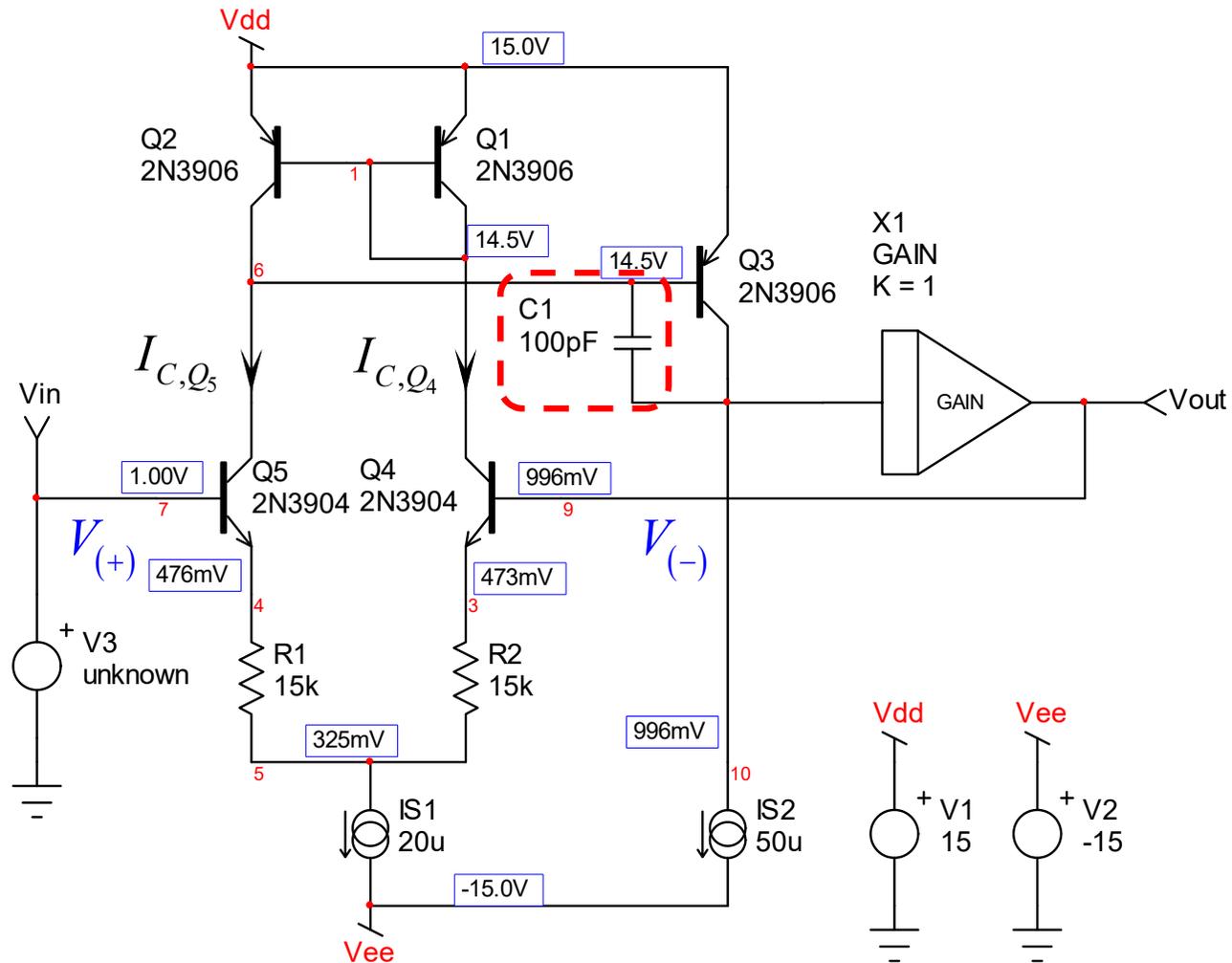- SR limit occurs if differential input stage equilibrium is lost




$$I_{C,Q5} \neq I_{C,Q4}$$

<http://www.edn.com/electronics-blogs/the-signal/4415482/Slew-Rate-the-op-amp-speed-limit>

Capacitor C_1 Limits the Output Slew Rate

□ The Miller capacitor is charged/discharged by 20- μ A

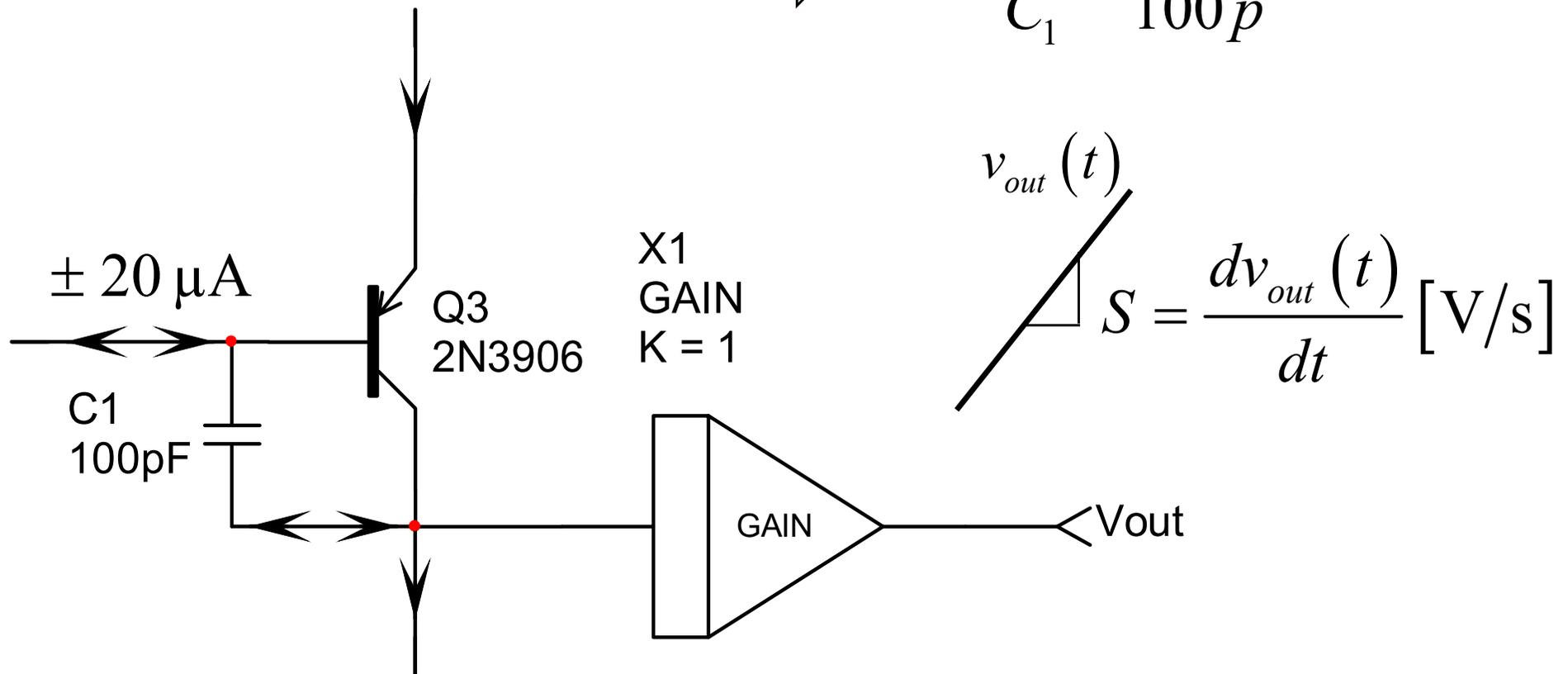
□ Neglecting base currents $\Rightarrow SR = \frac{I_{S_1}}{C_1} = \frac{20\mu}{100p} = 200 \text{ mV}/\mu\text{s}$



□ The slew rate is the maximum rate of change you can get


Miller Capacitor Charging/Discharging

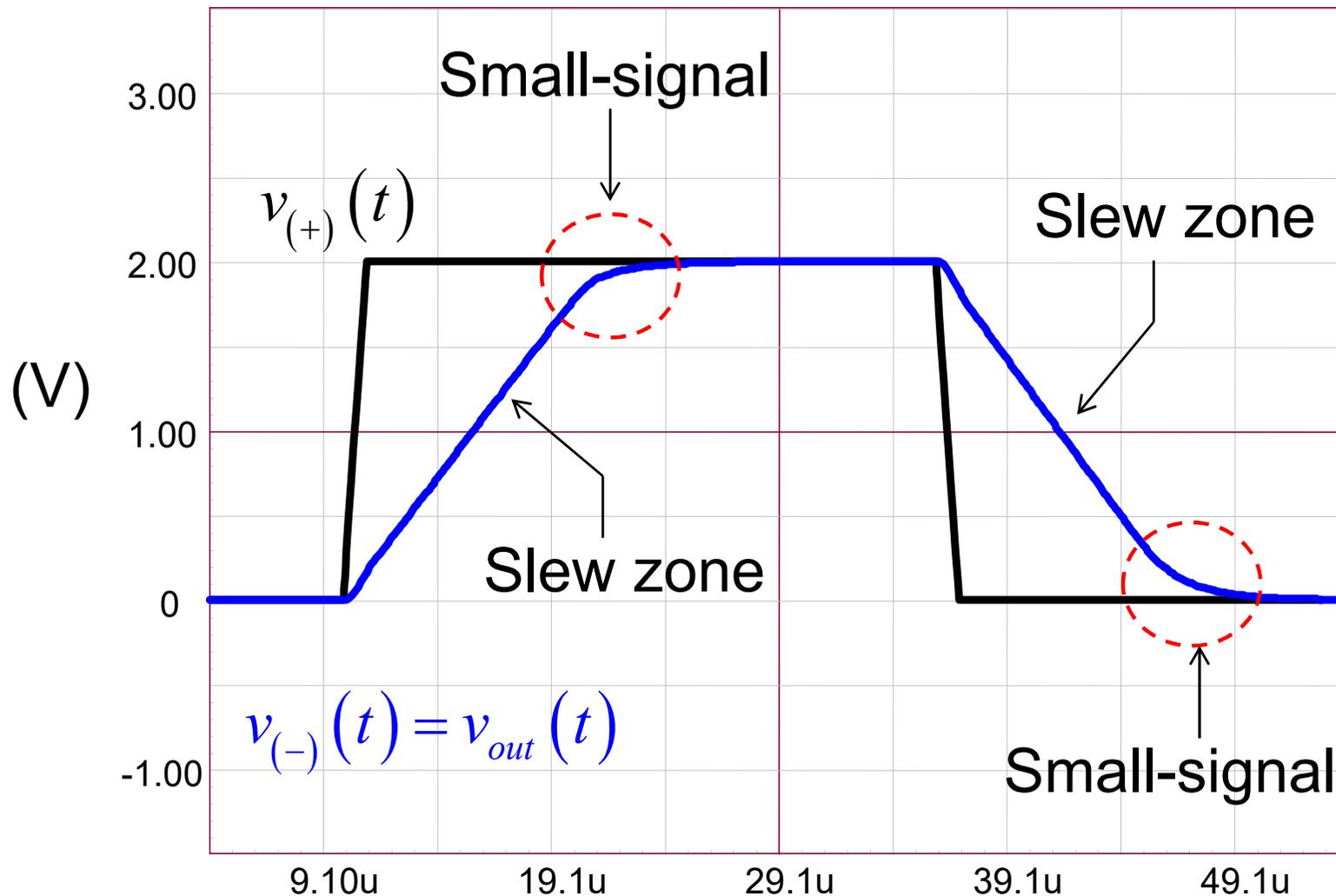- ❑ The op amp output cannot keep up the change: slewing



Duty Ratio Modulator

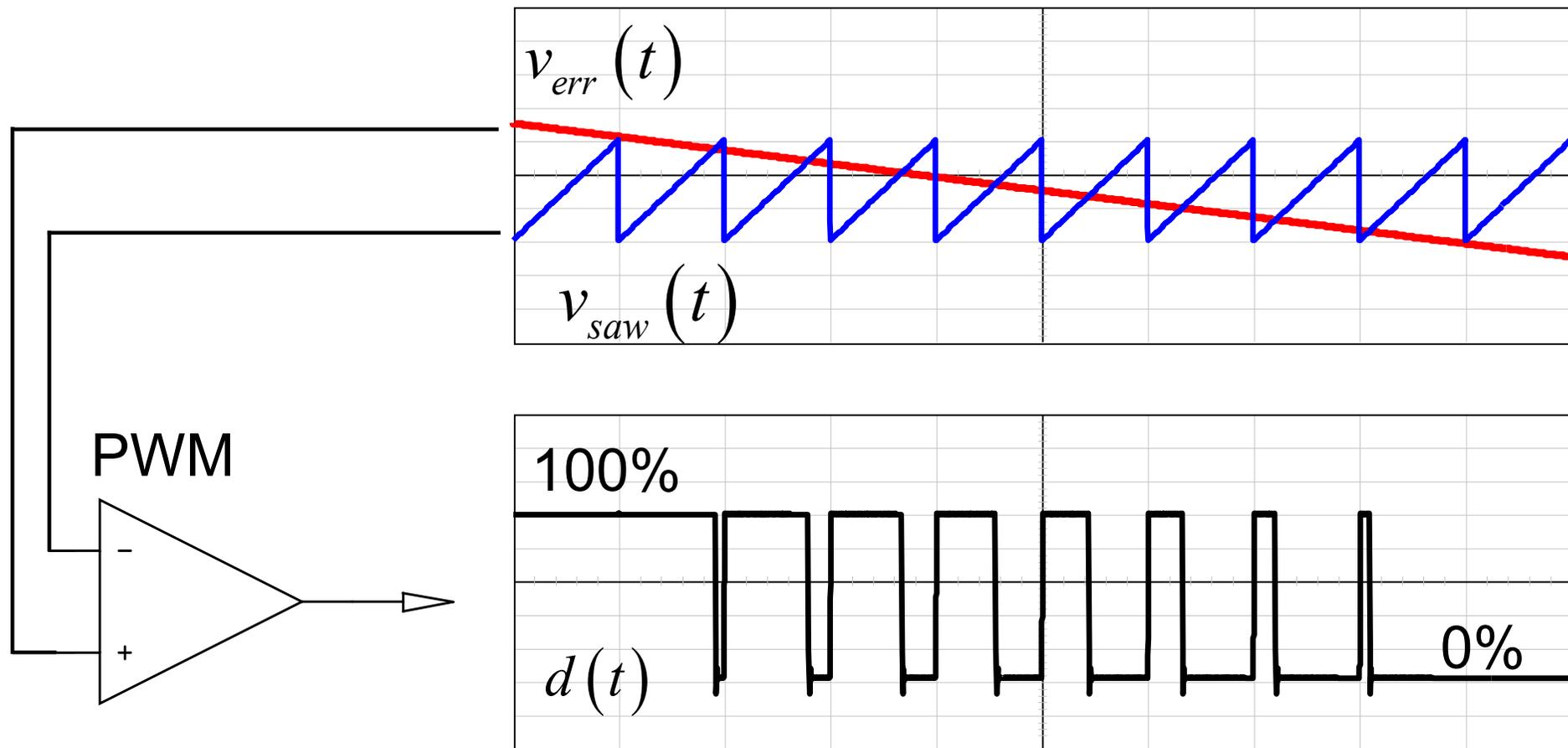- ❑ The duty ratio can change from 0 to 100%



- ❑ What if the op amp slews while the loop asks for a change?

Slew-Rate Impact on a Buck Regulator

□ This converter switches at 1 MHz and features a 200-kHz f_c

parameters

Rupper=38k
 $f_c=200k$
 $G_{fc}=-30$

$G=10^{-(G_{fc}/20)}$
 $\pi=3.14159$

$f_{z1}=10k$
 $f_{z2}=5k$
 $f_{p1}=50k$
 $f_{p2}=500k$

$C3=1/(2*\pi*f_{z1}*R_{upper})$
 $R3=1/(2*\pi*f_{p2}*C3)$


$C1=1/(2*\pi*f_{z2}*R2)$
 $C2=1/(2*\pi*(f_{p1})*R2)$

$a=f_c^4+f_c^2*f_{z1}^2+f_c^2*f_{z2}^2+f_{z1}^2*f_{z2}^2$
 $c=f_{p2}^2*f_{p1}^2+f_c^2*f_{p2}^2+f_c^2*f_{p1}^2+f_c^4$

$R2=\sqrt{c/a}*G*fc*R3/f_{p1}$


GBW=10Meg
 LFP=30
 $AOL=20*LOG(GBW/LFP)$
 SR=0.1

↑ SR adjustment

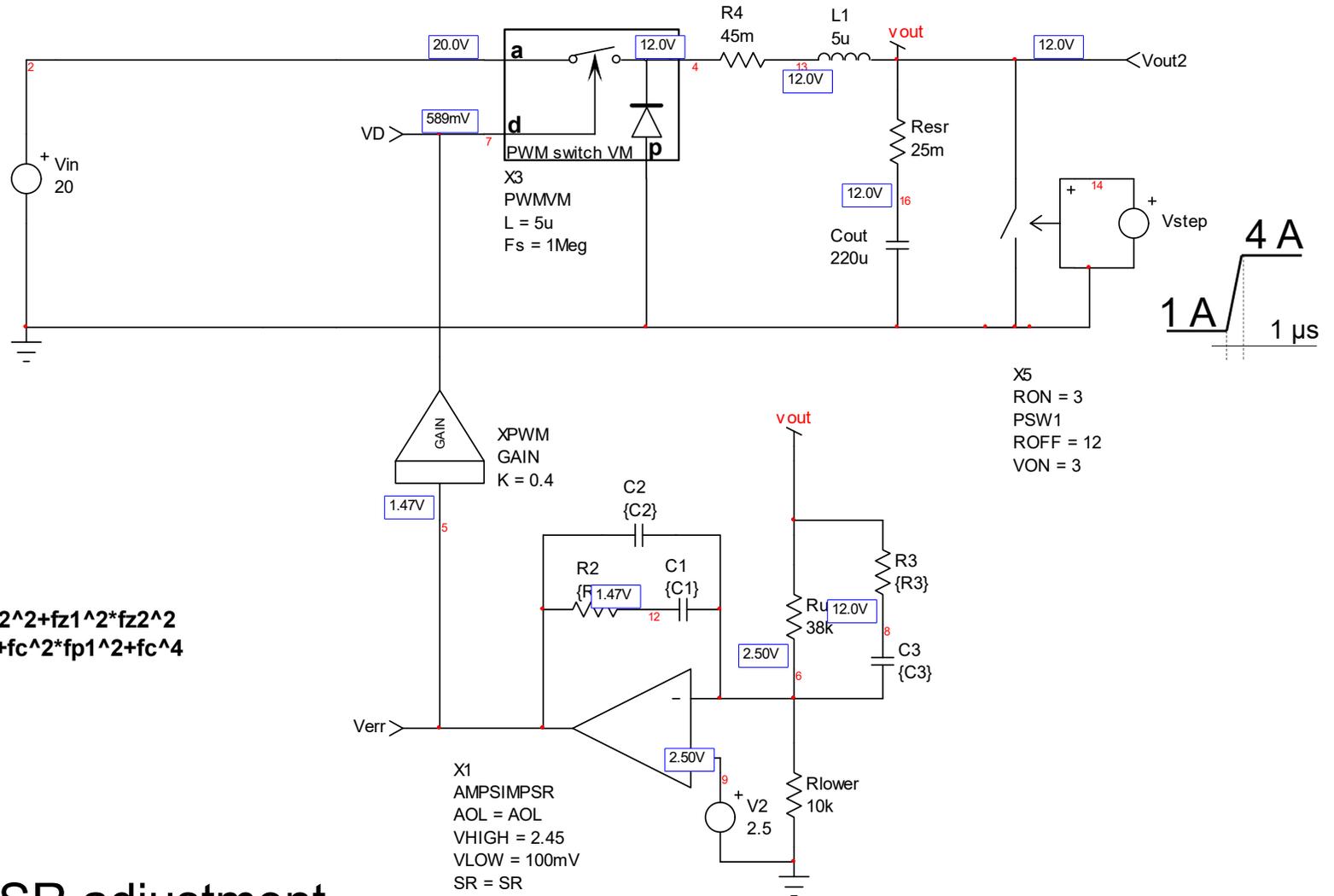


Too Low a Slew-Rate Brings Oscillations

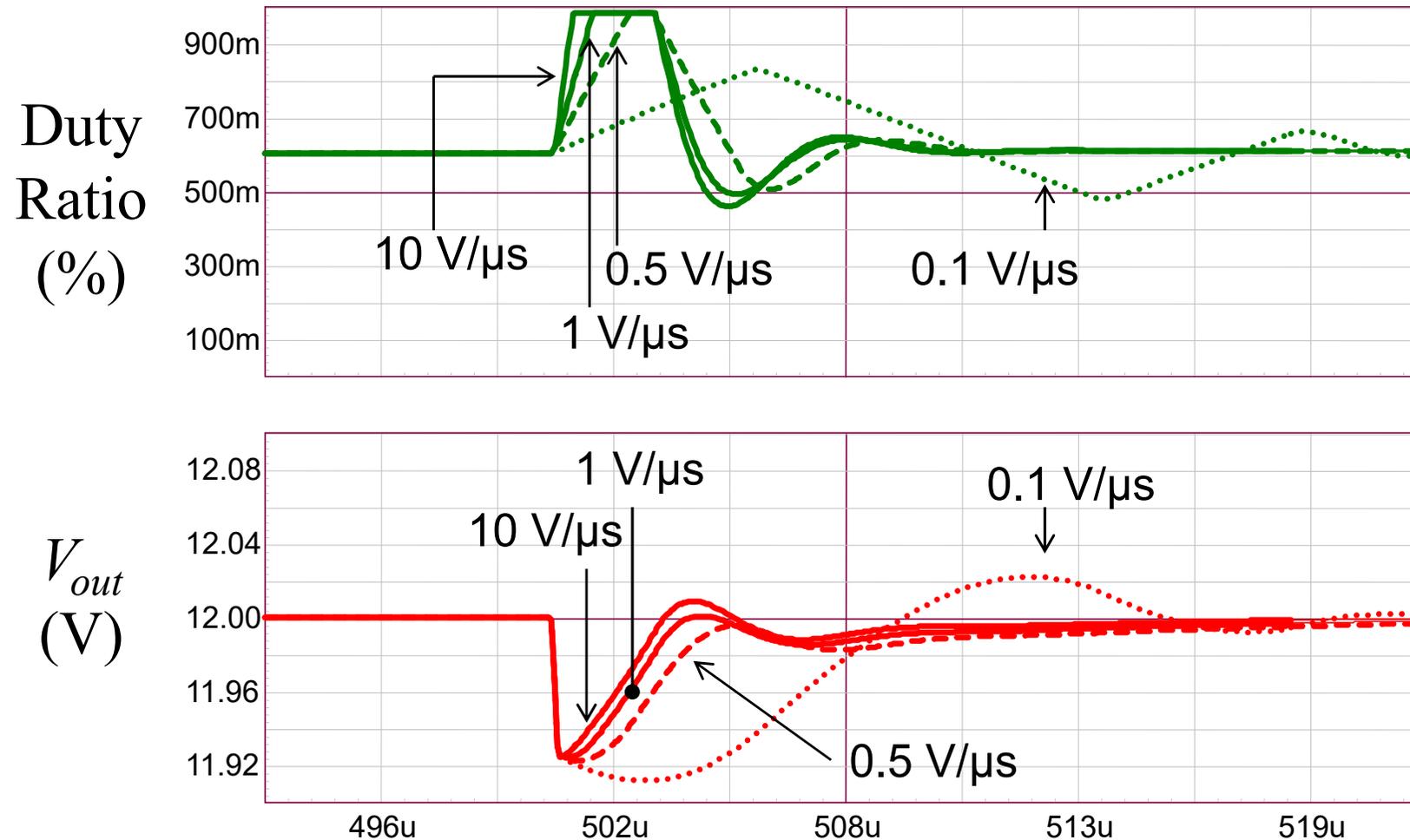- Changing the op amp slew-rate affects transient response



Controlling the Slew-Rate in SPICE

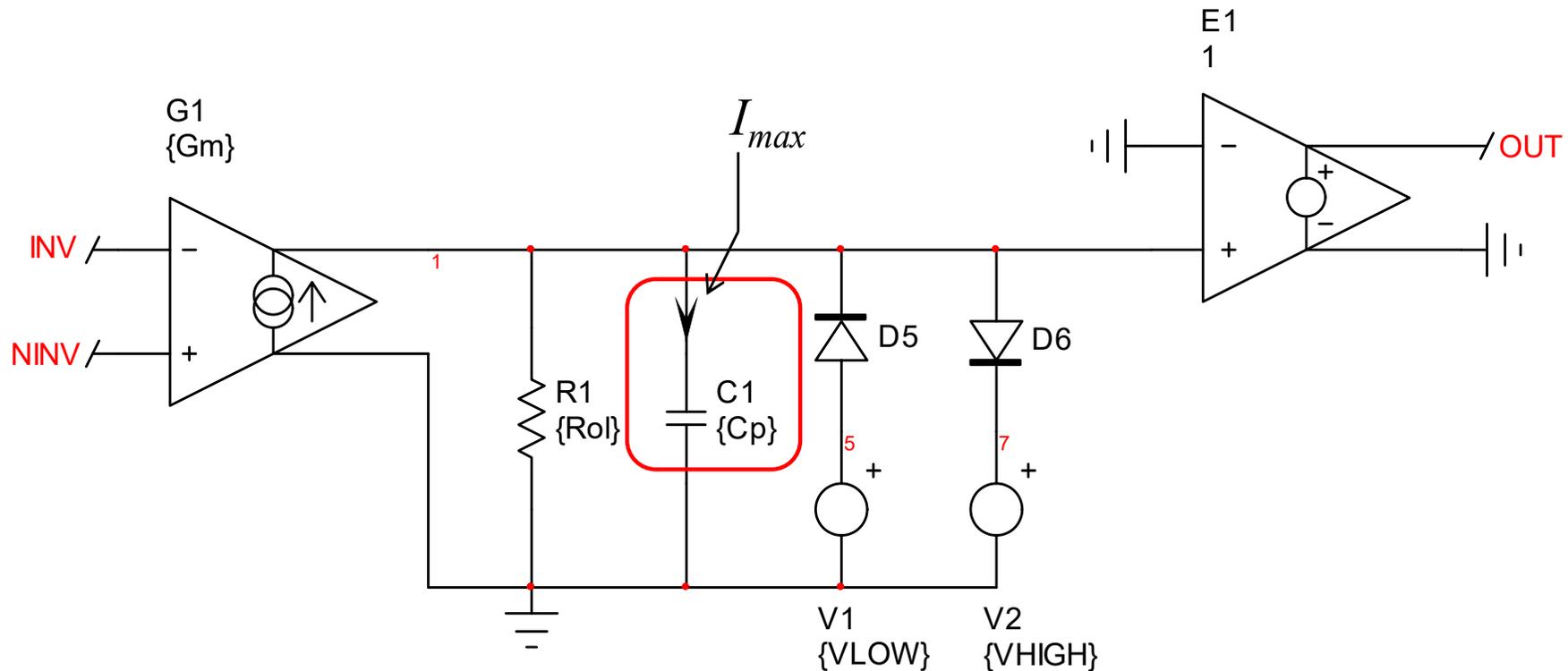
- What defines slew-rate in an op amp model?



- The current charging capacitor C_1 limits the slew-rate
- How do we clamp the current through C_1 ?

A Diode Bridge as a Current Clamp

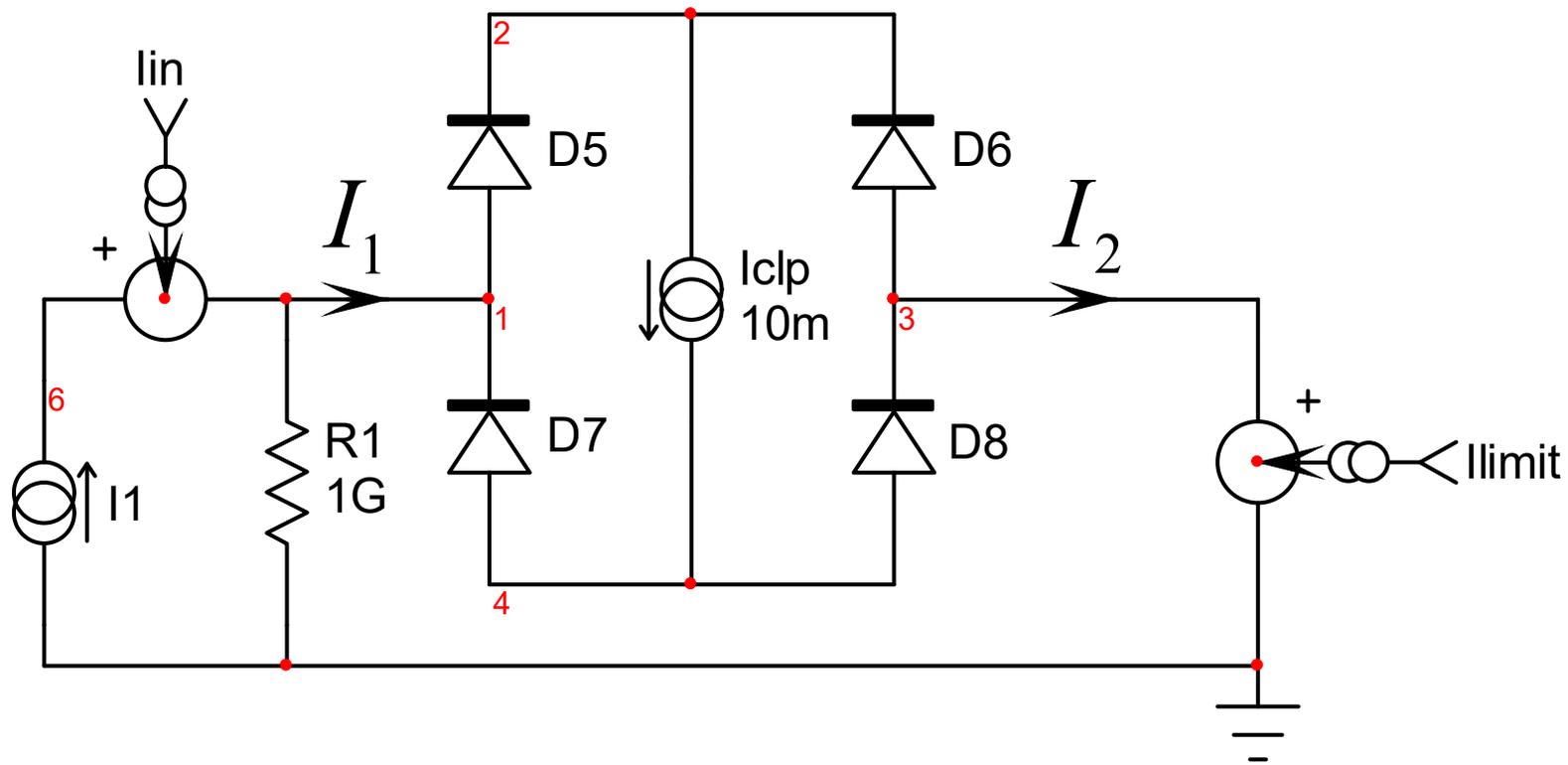
- A diode bridge is used as a current clamp



- When current source I_1 is less than 10 mA, $I_2 = I_1$
- How does the current split between diodes?

Current Source Equally Splits

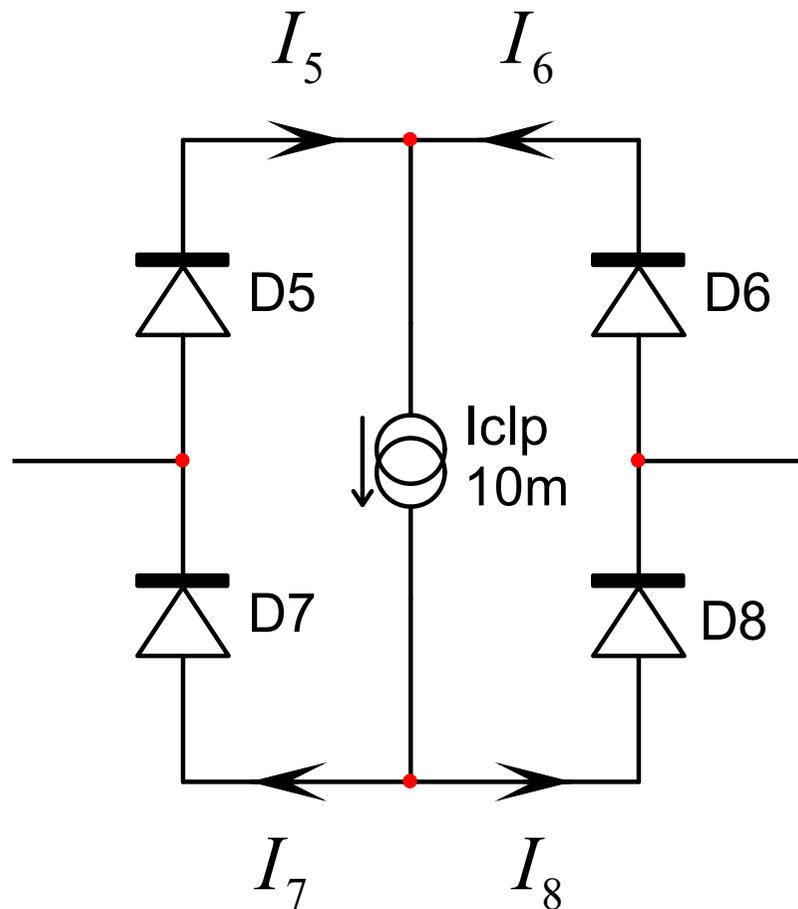- ❑ The trick is to assume all diodes are always biased
- ❑ All diodes are of similar characteristics, same V_f and r_d




$$I_5 = I_6 = \frac{I_{clp}}{2} = 5 \text{ mA}$$

$$I_7 = I_8 = \frac{I_{clp}}{2} = 5 \text{ mA}$$

Splitting and Adding Currents

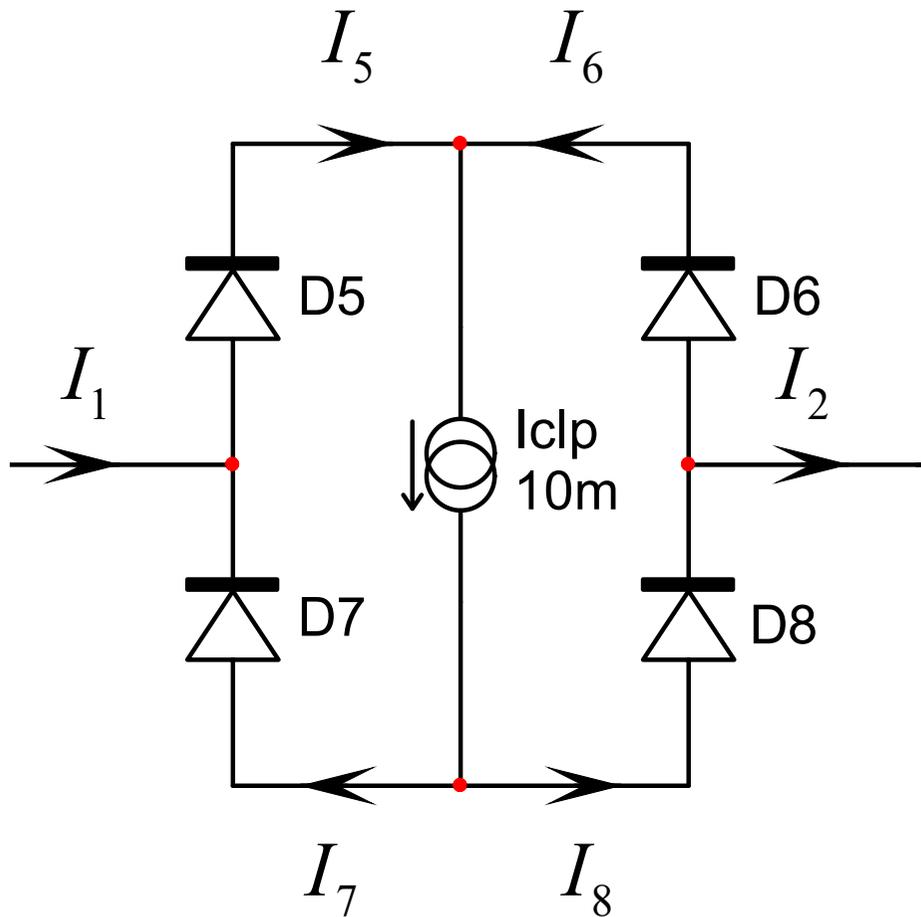- Write KCL considering conducting diodes



$$I_5 + I_6 = I_{clp}$$

$$I_7 + I_8 = I_{clp}$$

$$I_7 + I_1 = I_5 \quad I_2 + I_6 = I_8$$

subtract


$$I_7 + I_1 - I_2 - I_6 = I_5 - I_8$$

$$I_1 - I_2 = \underbrace{I_5 + I_6}_{I_{clp}} - \underbrace{(I_8 + I_7)}_{I_{clp}} = 0$$

$$I_1 = I_2$$

Input Current Goes to the Output

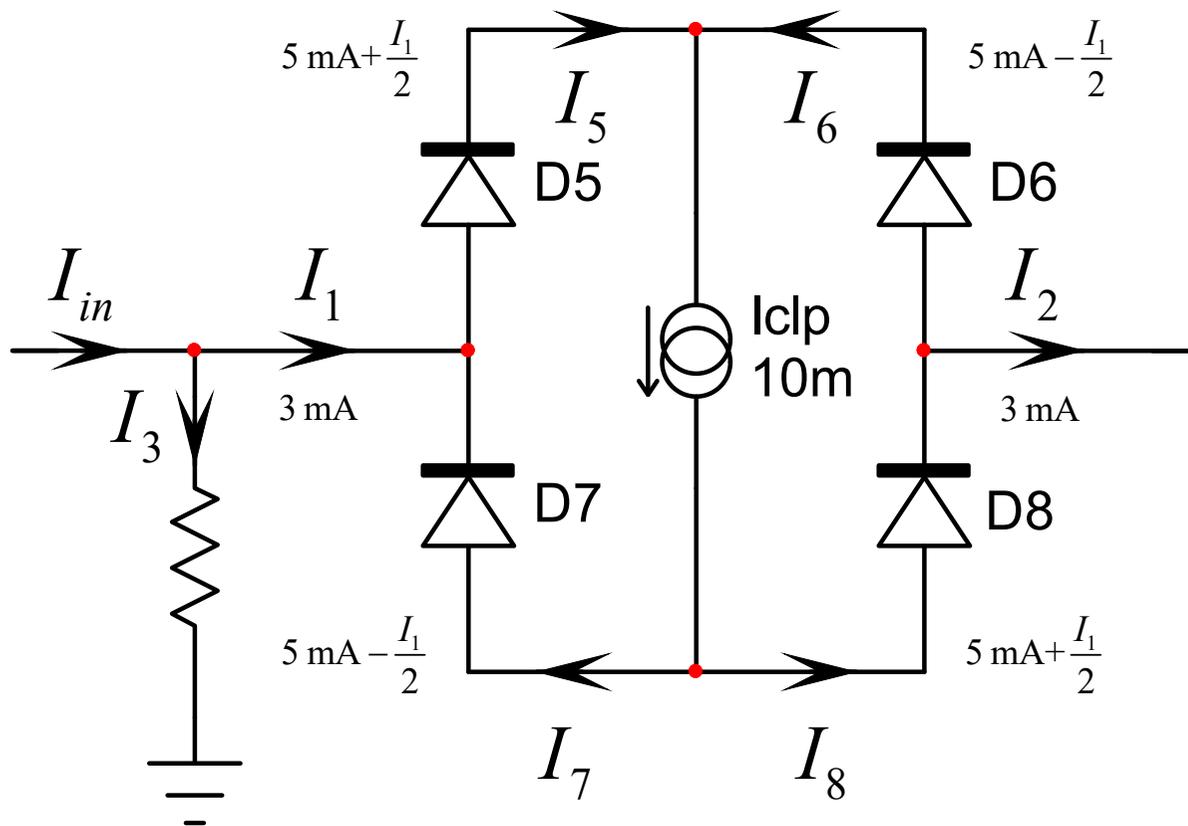- Diodes are always forward-biased and imply $I_1 = I_2$



$$I_1 = 3 \text{ mA}$$

↓

$$10 \text{ mA} \left\{ \begin{array}{l} I_5 = 6.5 \text{ mA} \\ I_7 = 3.5 \text{ mA} \end{array} \right.$$

$$10 \text{ mA} \left\{ \begin{array}{l} I_8 = 6.5 \text{ mA} \\ I_6 = 3.5 \text{ mA} \end{array} \right.$$


↓

$$I_2 = 3 \text{ mA}$$

- When diodes block, I_1 and I_2 are clamped to 10 mA
- I_3 is the excess current in clamped state

Clamp Circuit at Work

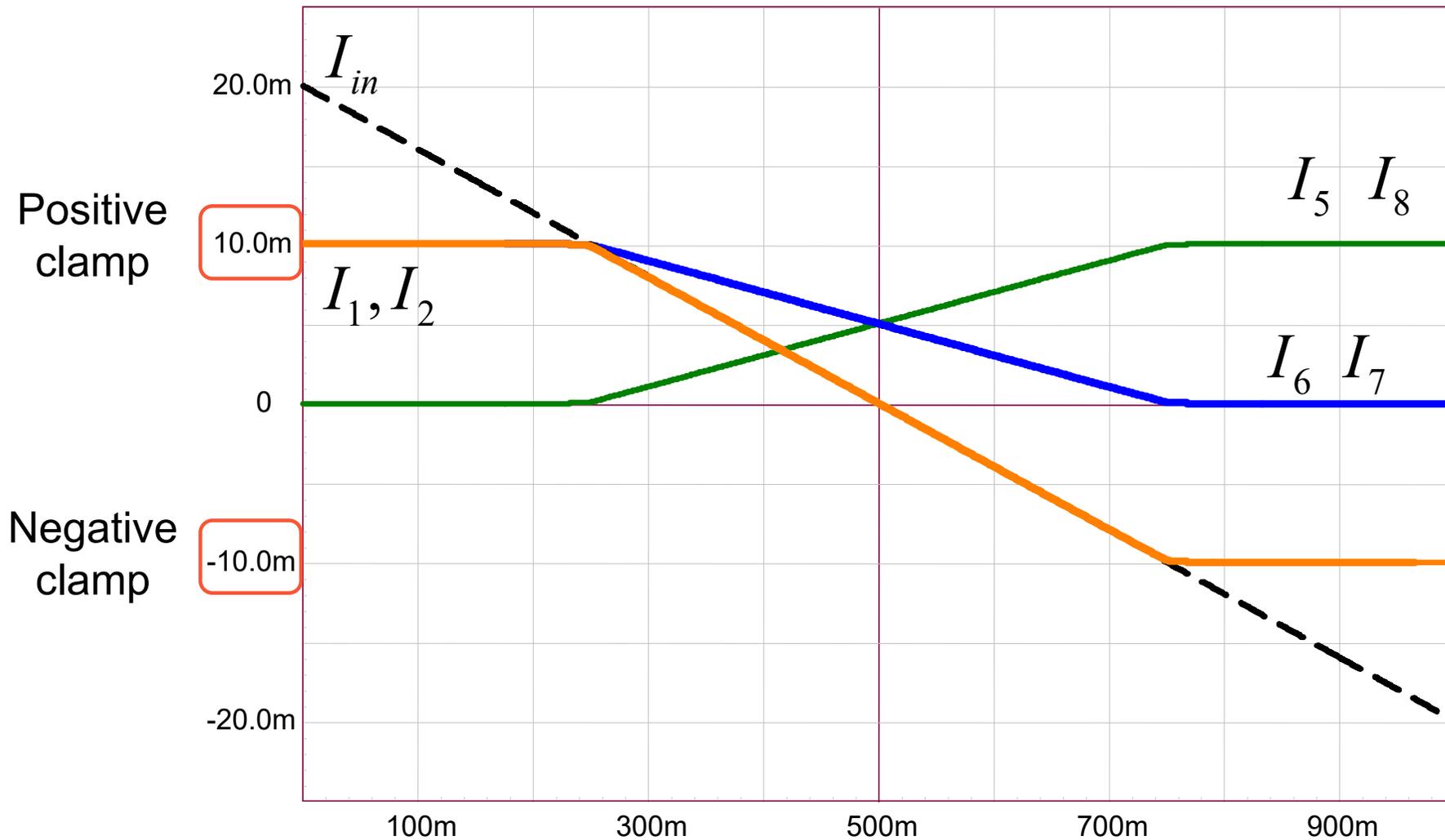
- ❑ Output current is clamped to 10 mA regardless of polarity



Slow-Down Low Frequency Pole Charging

- ❑ Create SR limit by clamping the capacitor charging current
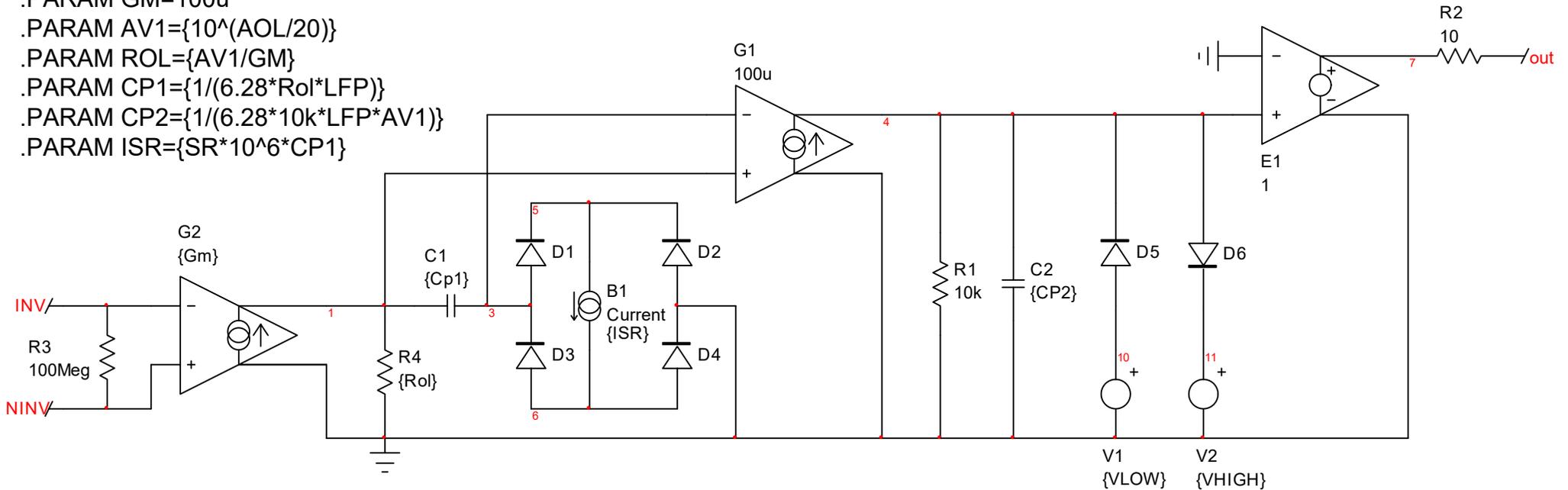
```
.PARAM GM=100u
.PARAM AV1={10^(AOL/20)}
.PARAM ROL={AV1/GM}
.PARAM CP1={1/(6.28*RoI*LFP)}
.PARAM CP2={1/(6.28*10k*LFP*AV1)}
.PARAM ISR={SR*10^6*CP1}
```



- ❑ Complete op amp macro model featuring SR and 2nd pole


- ❑ The slope (slew rate) is I_{SR} / C_{p1}

$$\Rightarrow I_{SR} = C_{p1} \text{SR} \times 10^{-6} \text{ V}/\mu\text{s}$$



When the Op Amp Slews

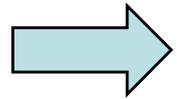❑ The slewing op amp distorts the input signal



Check expected slope is always smaller than max SR

❖ What is the highest slope of a sinusoidal signal?

$$S(t) = \frac{d}{dt} V_p \sin(\omega t) = V_p \cdot \omega \cdot \cos(\omega t)$$

$$\frac{d}{dt} S(t) = 0$$



$$-V_p \omega^2 \sin(\omega t) = 0$$




$$\omega t = 0$$

$$SR = V_p 2\pi f$$


50 kHz
9 V peak

$$SR = 2.8 \text{ V}/\mu\text{s}$$

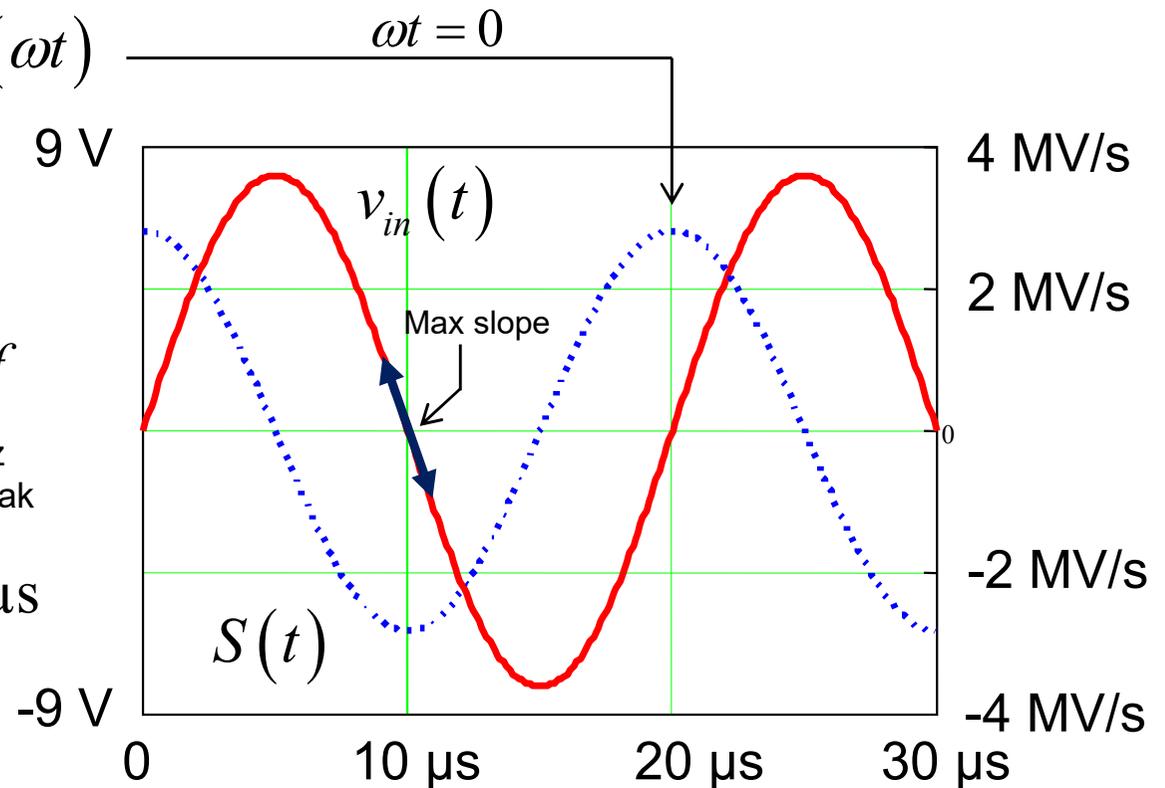

Testing the Model in Transient

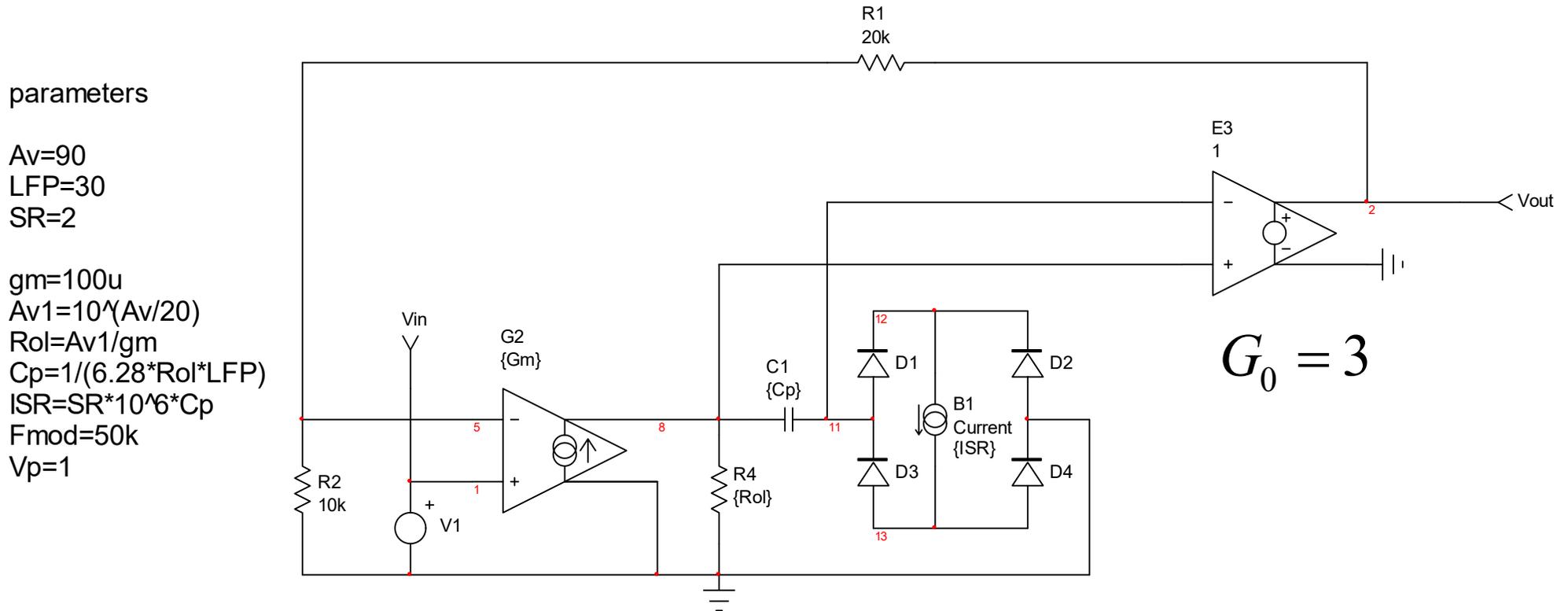- A 50-kHz 1-V_{peak} waveshape drives an SR-limited op amp




- The signal max SR is: $SR(V_{in}) = V_p 2\pi f = 1 \times 6.28 \times 50k \approx 0.3 \text{ V}/\mu\text{s}$

$G_0 = 3$


→ $SR(V_{out}) = V_p 2\pi f = 3 \times 6.28 \times 50k \approx 1 \text{ V}/\mu\text{s}$

Slewing in Action

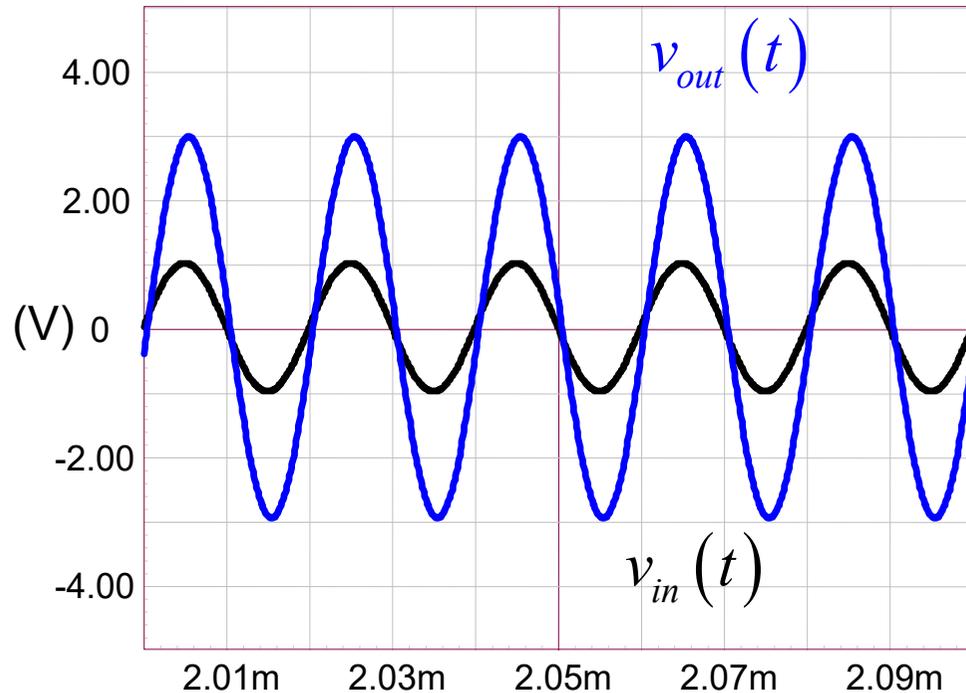- ❑ The slew-rate is adjusted while the output is monitored



$$SR = 2 \text{ V}/\mu\text{s}$$

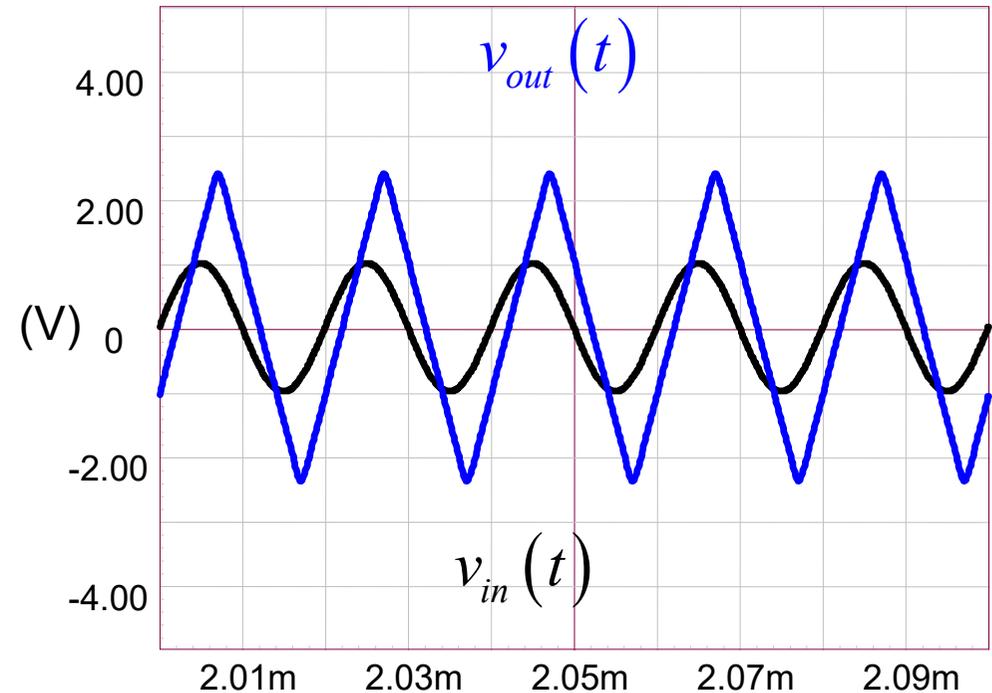


$$SR = 0.5 \text{ V}/\mu\text{s}$$

- ❑ If the op amp slews, it cannot track the input signal

Adding a Low-Frequency Pole

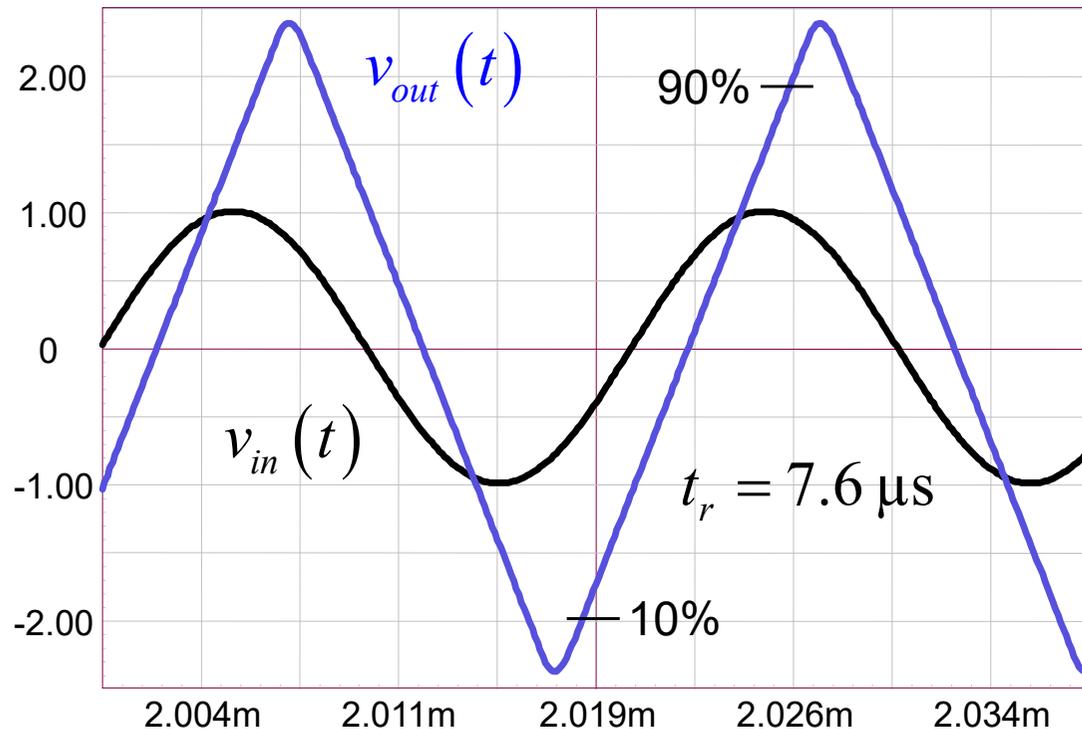- A slewing op amp behaves like adding a low-frequency pole



For a 1st-order system:


$$f_p \approx \frac{0.35}{t_r} = \frac{0.35}{7.6\mu} = 46 \text{ kHz}$$

- A new pole is added to the system

➡ Phase margin degradation, oscillatory response

Slew Rate and Pulse Width Modulation (1)

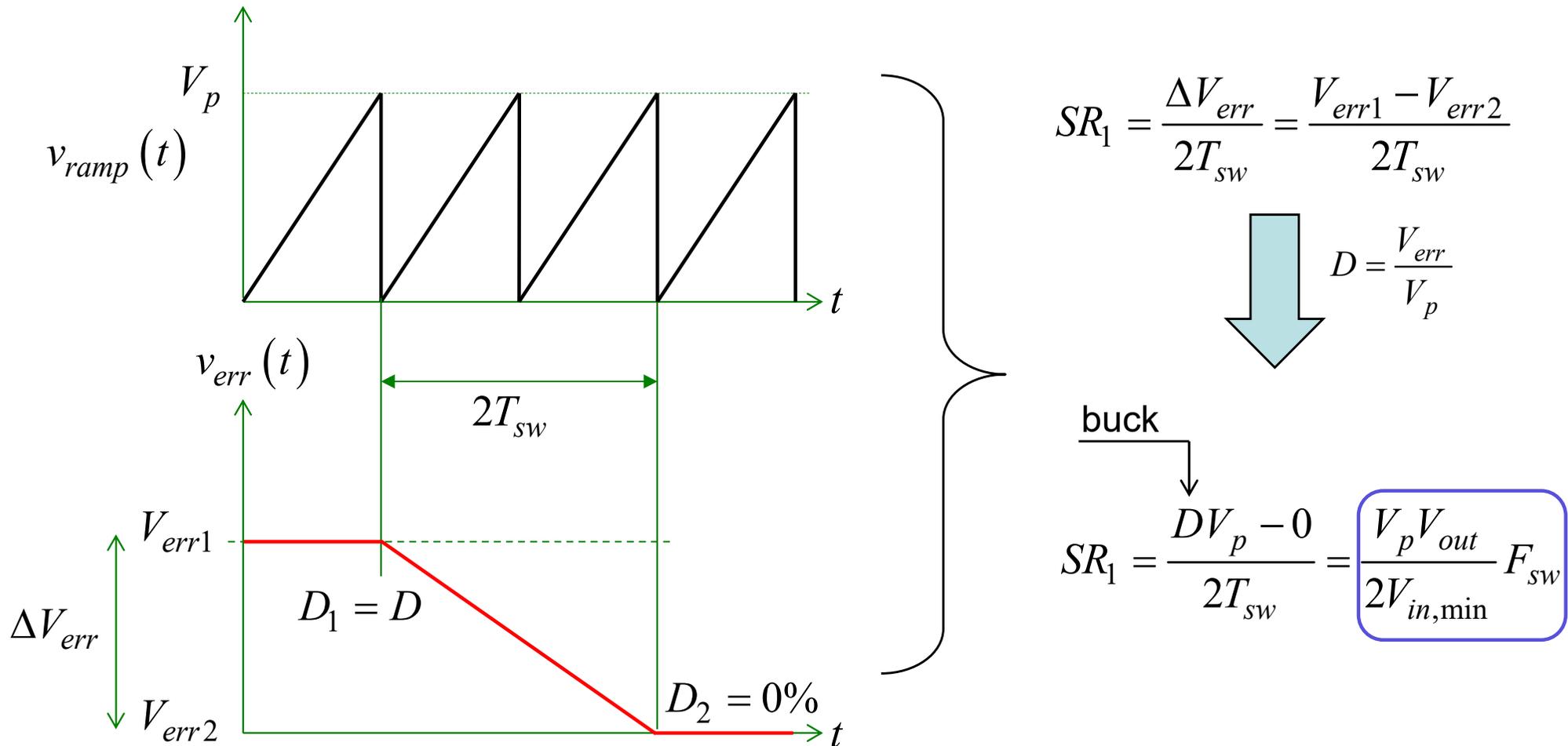
□ 1st case, the load is released and duty ratio drops



M. Jovanović et al. "Design Considerations for Low-Voltage On-Board Dc-Dc Modules", IEEE Transactions on Power Electronics, Vol. 11, no 2, March 1996

Slew Rate and Pulse Width Modulation (2)

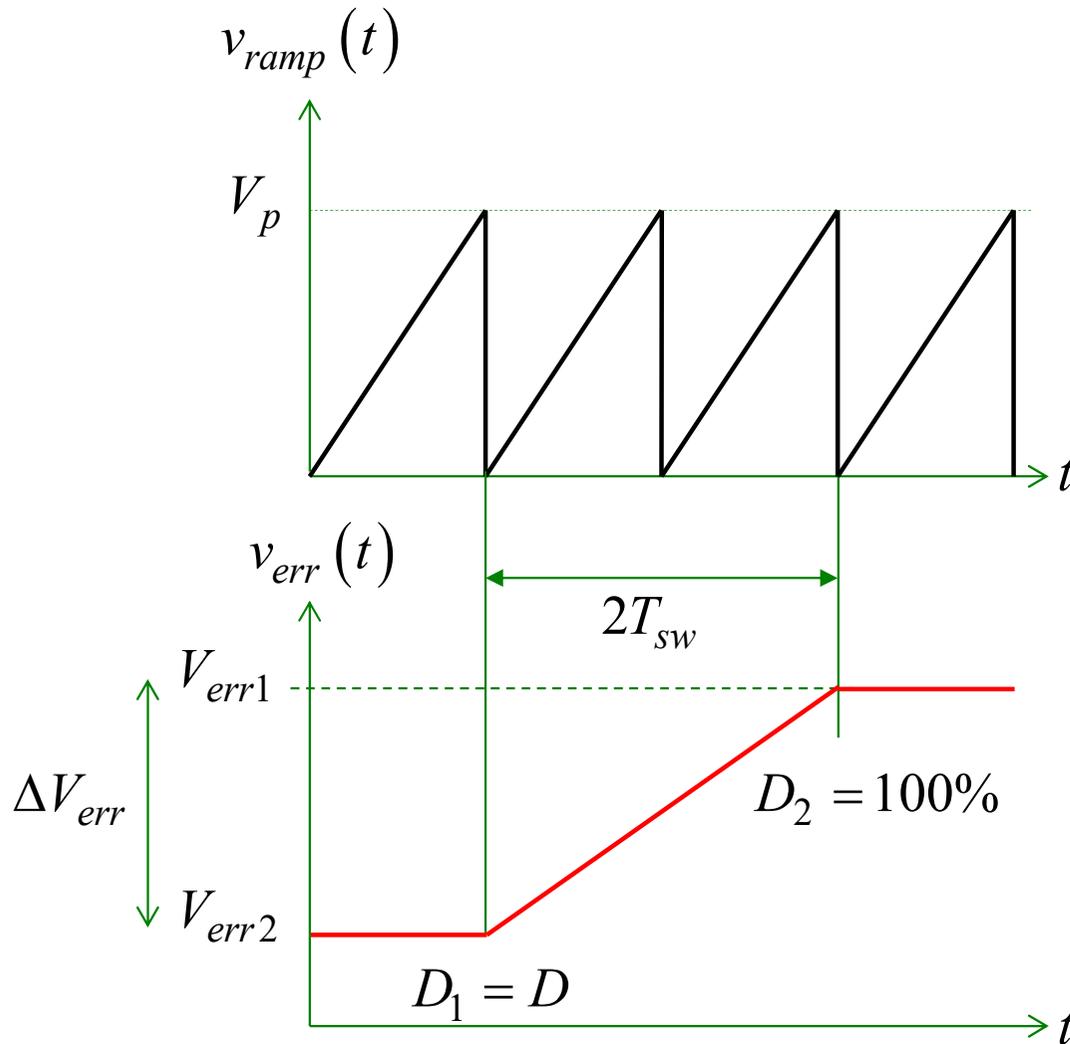□ 2nd case, the load is connected and duty ratio jumps high



$$SR_2 = \frac{\Delta V_{err}}{2T_{sw}} = \frac{V_{err1} - V_{err2}}{2T_{sw}}$$

$$D = \frac{V_{err}}{V_p}$$

buck

$$SR_2 = \frac{V_p - DV_p}{2T_{sw}} = \frac{V_p(1-D)}{2T_{sw}}$$

$$SR_2 = \frac{V_p}{2} \left(1 - \frac{V_{out}}{V_{in,max}} \right) F_{sw}$$

Slew Rate Selection Example

- Take the highest result and select the op amp SR

$$V_{in} = 20 \text{ V} \quad V_{out} = 12 \text{ V} \quad F_{sw} = 1 \text{ MHz} \quad V_p = 2.5 \text{ V}$$

$$SR_1 = \frac{V_p V_{out}}{2V_{in}} F_{sw} = \frac{2.5 \times 12}{2 \times 20} 10^6 = 750 \text{ kV/s} = 0.75 \text{ V}/\mu\text{s}$$

$$SR_2 = \frac{V_p}{2} \left(1 - \frac{V_{out}}{V_{in}} \right) F_{sw} = \frac{2.5}{2} \left(1 - \frac{12}{20} \right) 10^6 = 500 \text{ kV/s} = 0.5 \text{ V}/\mu\text{s}$$




Select an op amp with a SR at least equal to 1 V/ μ s

		TLV271				
Slew Rate at Unity Gain	SR	$V_{O(pp)} = V_{DD}/2, R_L = 10 \text{ k}\Omega, C_L = 50 \text{ pF}$	$V_{DD} = 2.7 \text{ V}$	1.35	2.1	V/ μ S
		$T_A = -40^\circ\text{C to } +105^\circ\text{C}$		1		
	$V_{O(pp)} = V_{DD}/2, R_L = 10 \text{ k}\Omega, C_L = 50 \text{ pF}$	$V_{DD} = 5 \text{ V}$	1.45	2.3		
	$T_A = -40^\circ\text{C to } +105^\circ\text{C}$		1.2			
	$V_{O(pp)} = V_{DD}/2, R_L = 10 \text{ k}\Omega, C_L = 50 \text{ pF}$	$V_{DD} = \pm 5 \text{ V}$	1.8	2.6		
	$T_A = -40^\circ\text{C to } +105^\circ\text{C}$		1.3			

- Watch for SR variations depending on op amp configuration!


Look at the Open-Loop Bode Plot

- The system exhibits gain up to 200 kHz

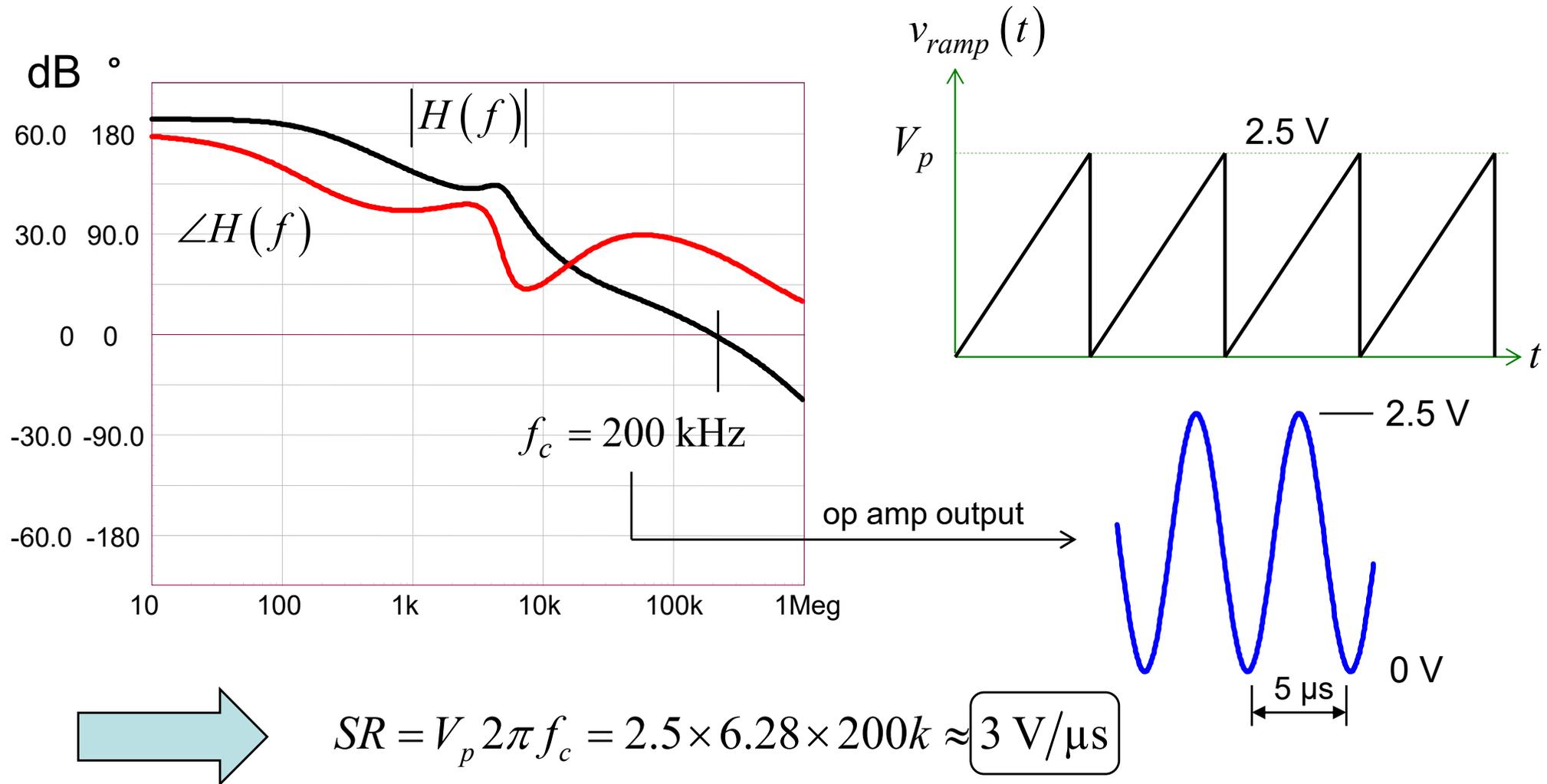

Slew Rate Depends on Architecture

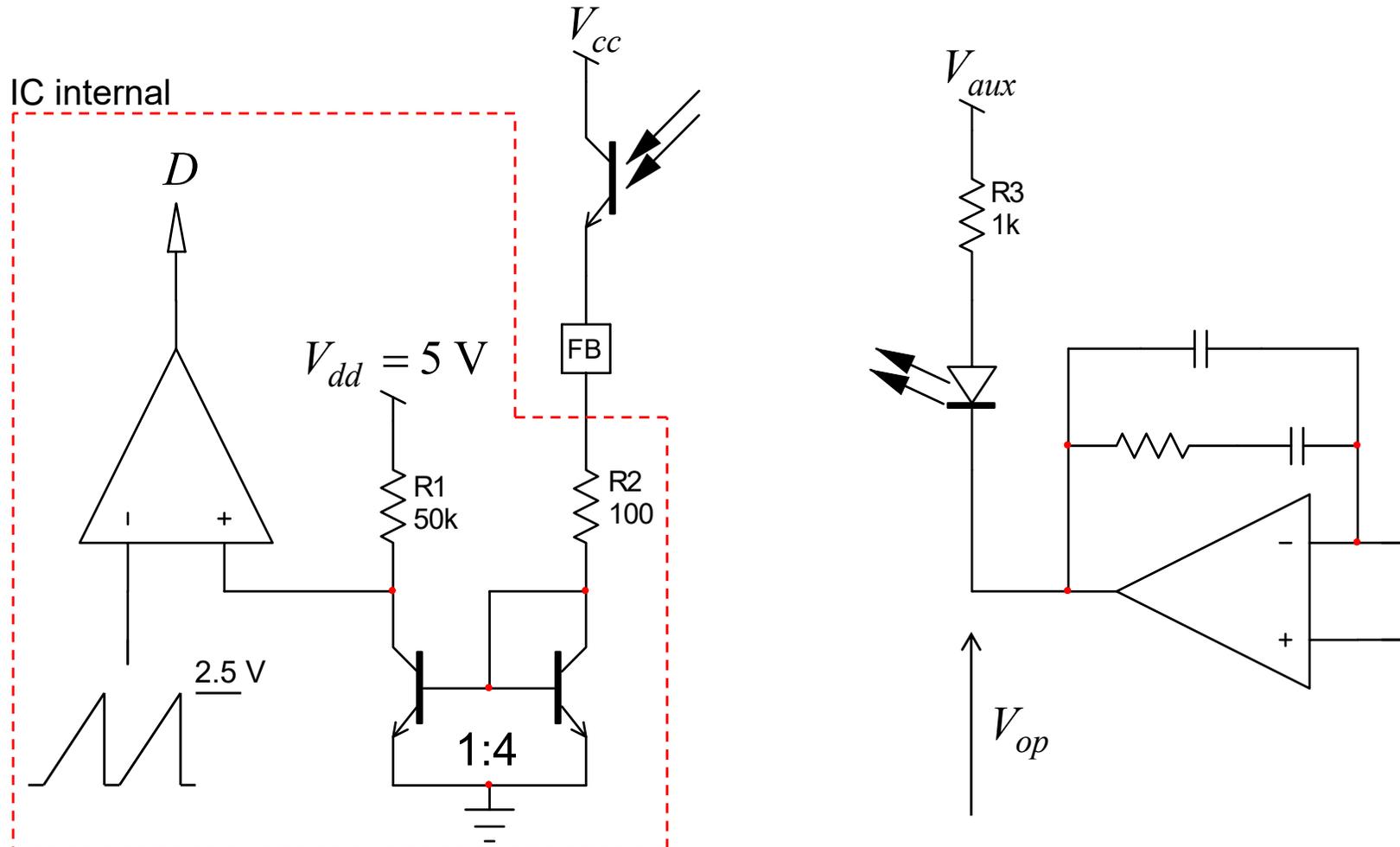- ❑ For opto-isolated dc-dc, op amp dynamics is reduced



- ❑ What is the op slew rate to sweep the 2.5-V ramp?

NCP1565 – Active Clamp Controller

A Lower SR for the Opto-Isolated Version

- ❑ The 2.5-V ramp must be swept from 0 to 2.5 V
- ❑ An external resistor adjusts the maximum duty ratio

$$I_{R_1} = \frac{V_{dd} - V_{CE,sat}}{50k} \approx 100 \mu A \quad \xrightarrow[1:4]{\text{mirror}} \quad I_{FB} \approx 400 \mu A$$

- ❑ Considering a 60% CTR worst case, the LED current is

$$I_{LED} \approx 670 \mu A$$

- ❑ Across the 1-k Ω resistor, it induces a voltage swing of

$$V_{op,ac} = 670u \times 1k = 670 \text{ mV}$$

- ❑ If we adopt 0.67 V, then for a 200-kHz crossover

$$SR = V_p 2\pi f_c = 0.67 \times 6.28 \times 200k \approx 0.84 \text{ V}/\mu s$$

 Select an op amp with a 1-V/ μ s slew rate



Course Agenda

- ❑ Control System Basics
- ❑ Operational Amplifier and Low-Frequency Pole
- ❑ Gain-Bandwidth Impact on Phase Boost
- ❑ Op Amp Slew Rate Effects in Loop Control
- ❑ **Start-Up Sequence and Auxiliary Supply**
- ❑ Characterizing the Optocoupler Pole
- ❑ Dealing with the Fast Lane
- ❑ Going Around the TL431 Fast Lane



Start Up Characteristics for Dc-Dc Bricks

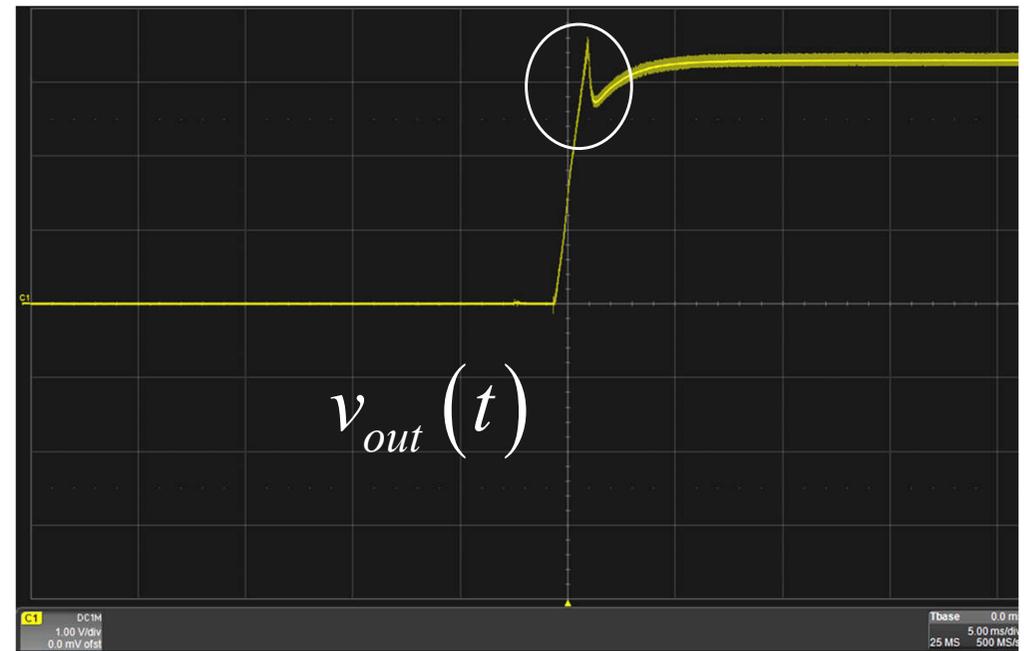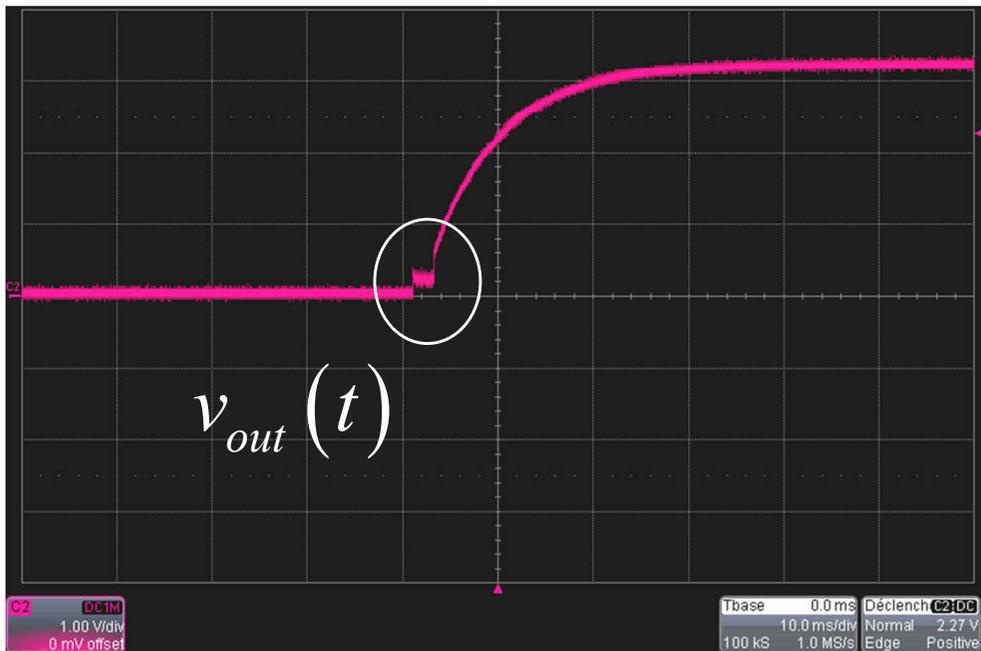
- ❑ Monotonicity of V_{out} at start-up is important:
 - ❖ no hiccup or glitch while V_{out} ramps up
 - ❖ no negative slope at any time during start up
 - ❖ no overshoot of any kind, smooth V_{out} landing




- ❑ How do you prevent these from happening?

Controlling V_{out} at Start Up

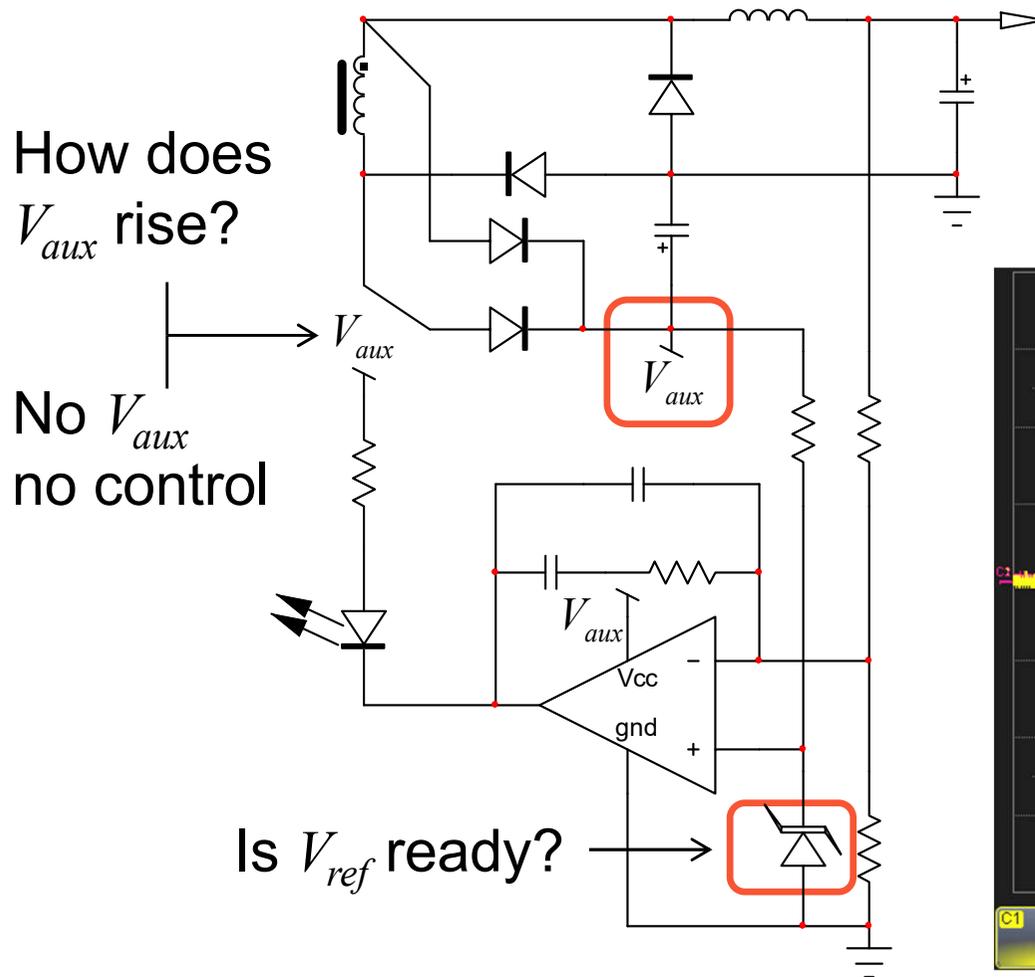- ❑ In a power supply, the loop at start-up is blind to V_{out}
- ❖ Output control must occur at the very first switching cycles




Typical ugly start up

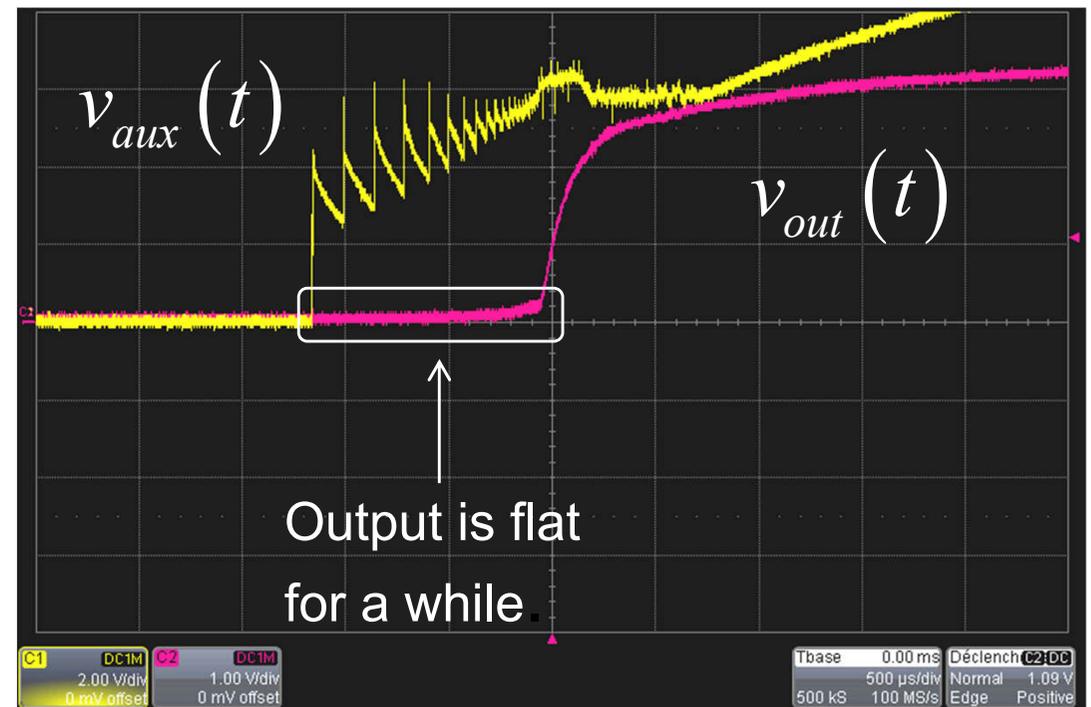


A Two-Loop System

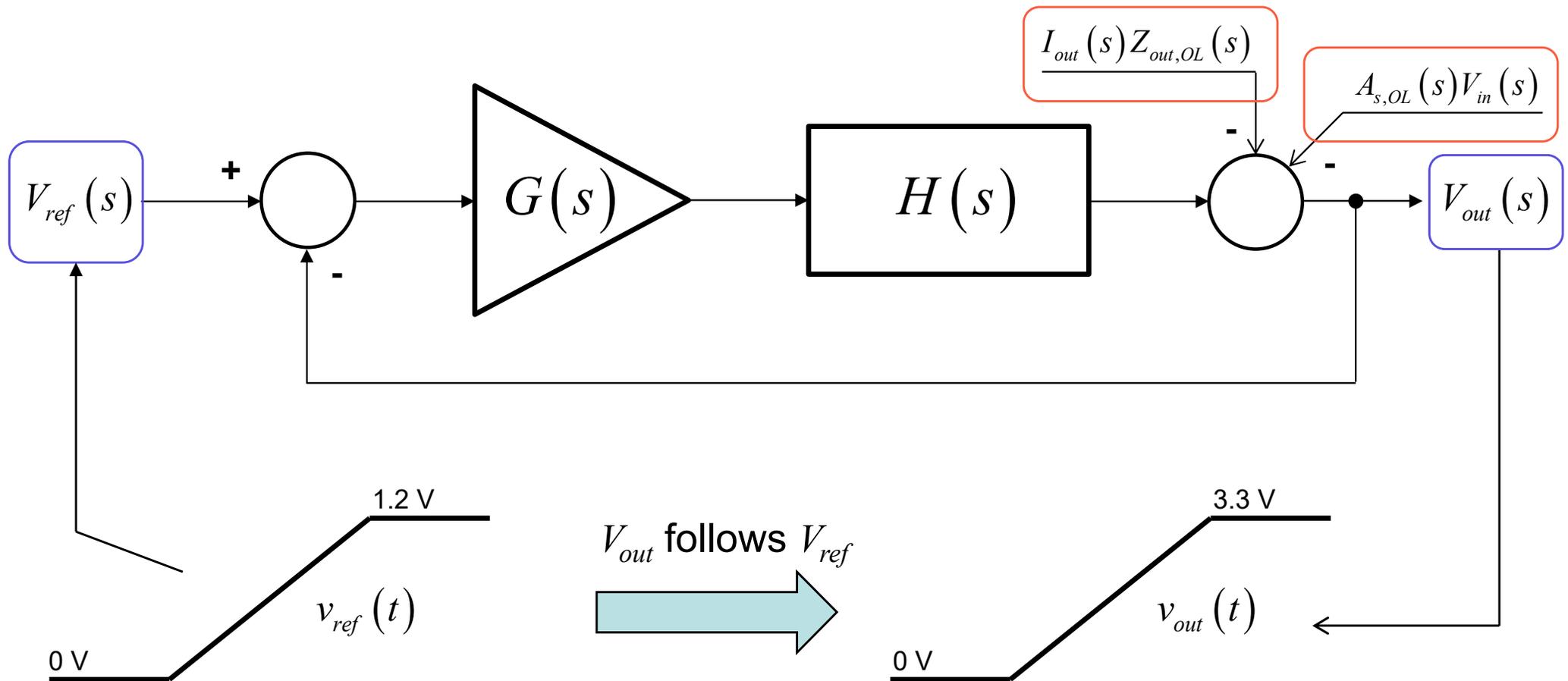- ❑ At power up, V_{ref} takes over and V_{out} follows it
- ❑ When target is reached, loop observes V_{out} only




Immediate Auxiliary Voltage Availability

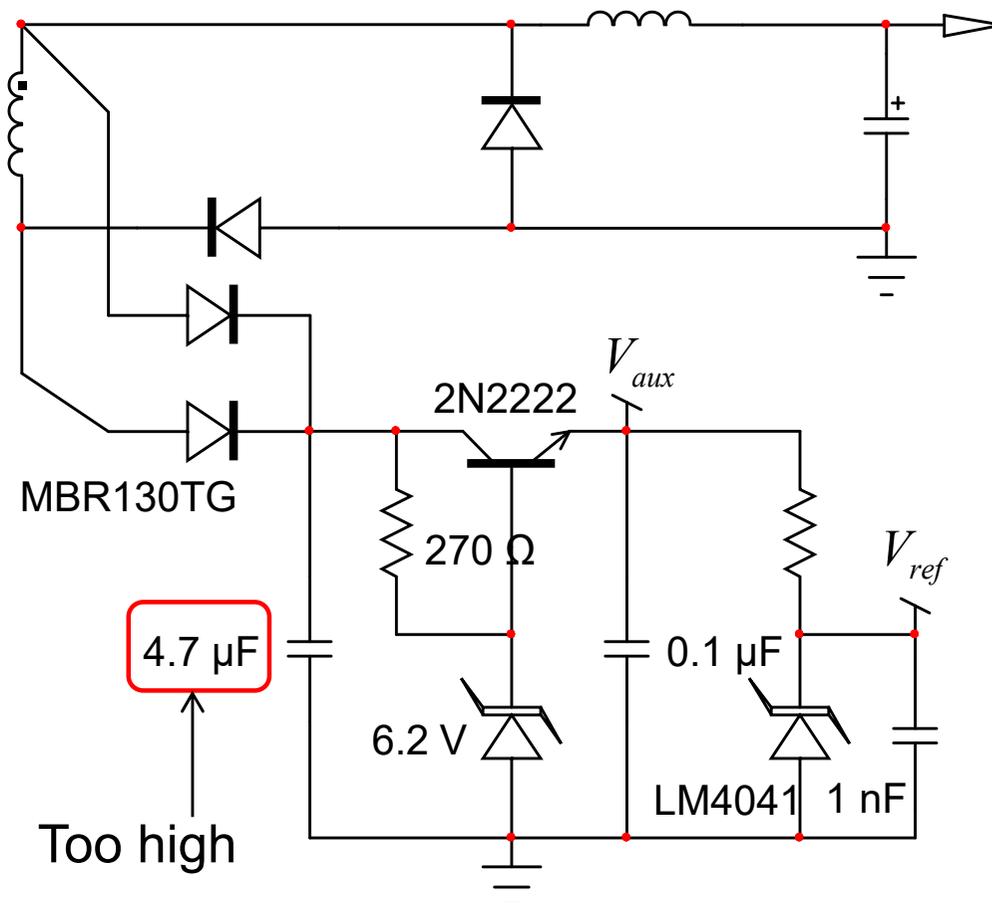- ❑ The key is to have V_{aux} showing up immediately
- ❖ V_{ref} and the op amp are biased
- ❖ Control current exists to take the lead




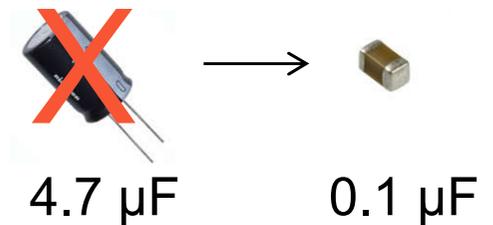If decoupling capacitors are too big, V_{aux} slugs!




Optimum Capacitor Value

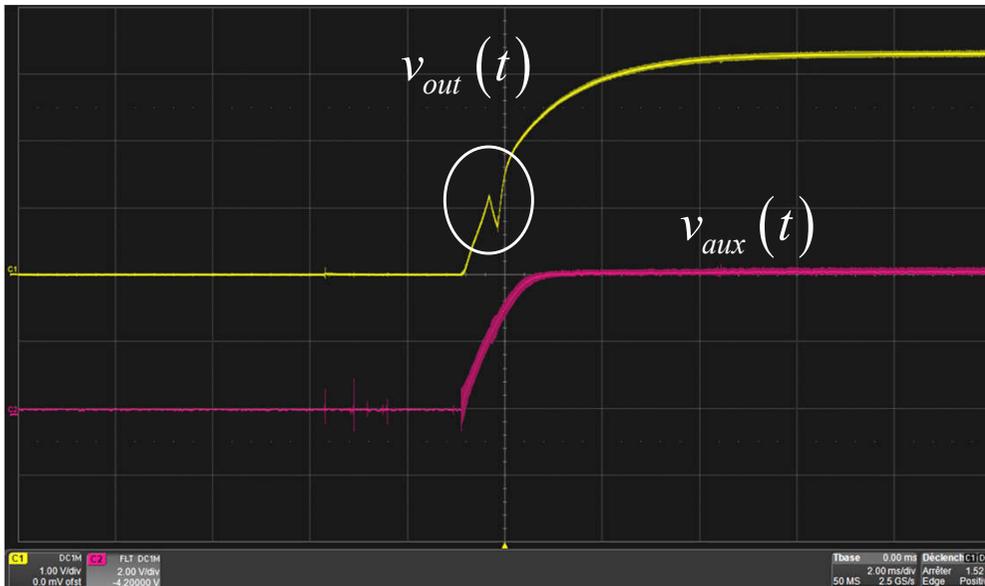- The auxiliary voltage has to come up immediately



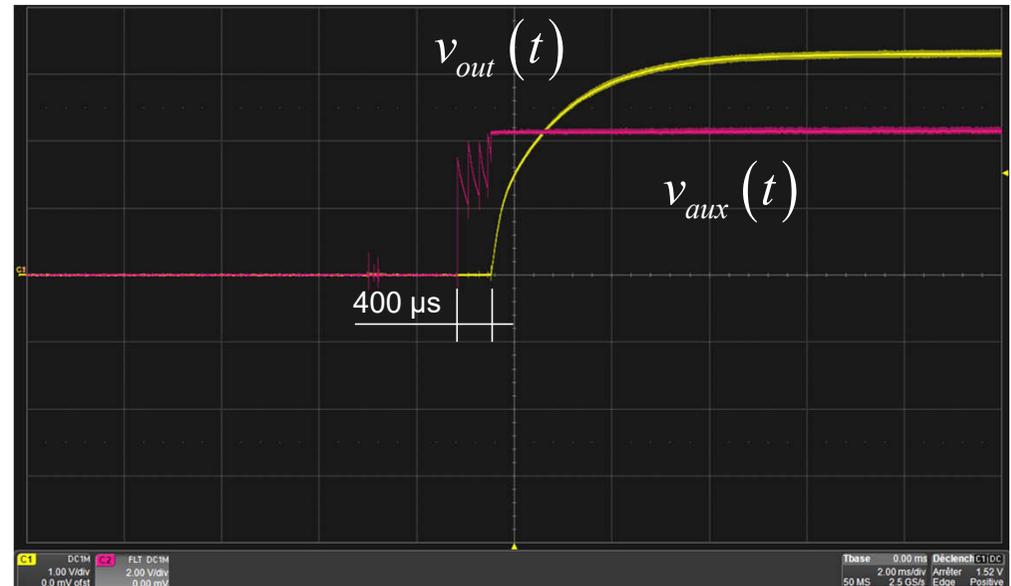V_{aux} is late, discontinuity
 $C = 4.7 \mu\text{F}$




V_{aux} is immediate, no discontinuity
 $C = 0.1 \mu\text{F}$

- The secondary side must take the lead: V_{out} follows V_{ref}

Too Much Soft Start Brings Overshoot


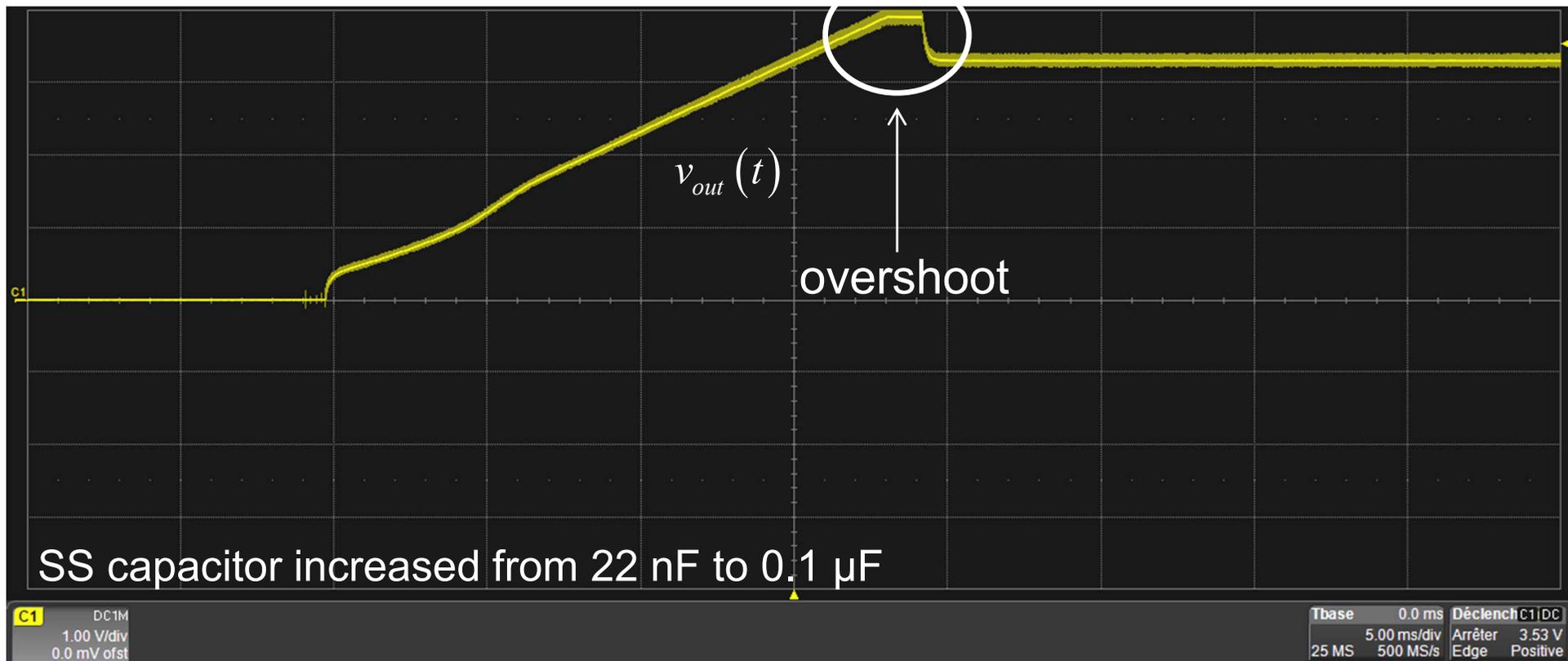
- ❑ Primary-side duty ratio soft start must not be oversized



- ❑ Compensation capacitors impose op amp recovery time

Soft-Started V_{ref} is Key to Smooth Start-Up

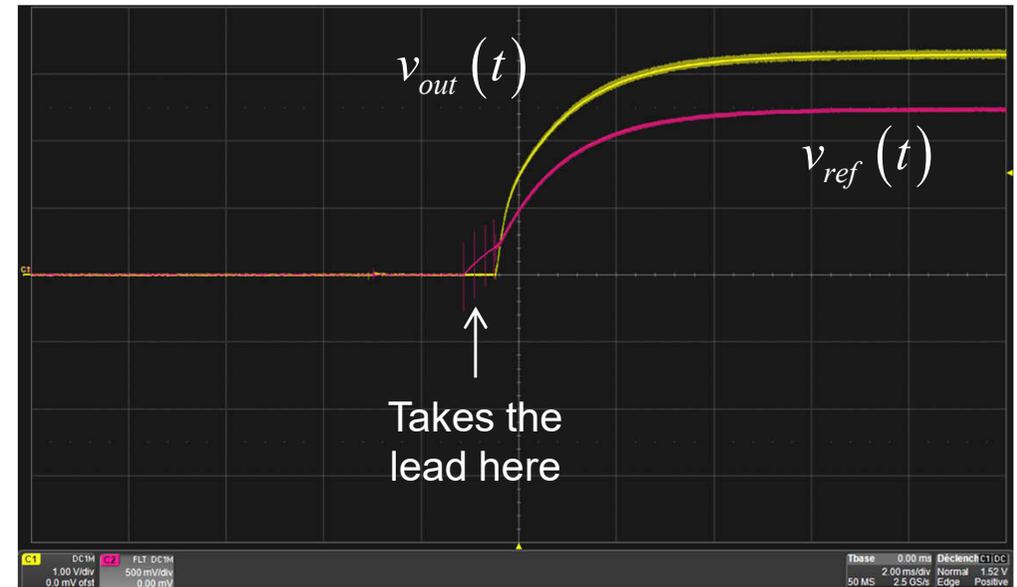
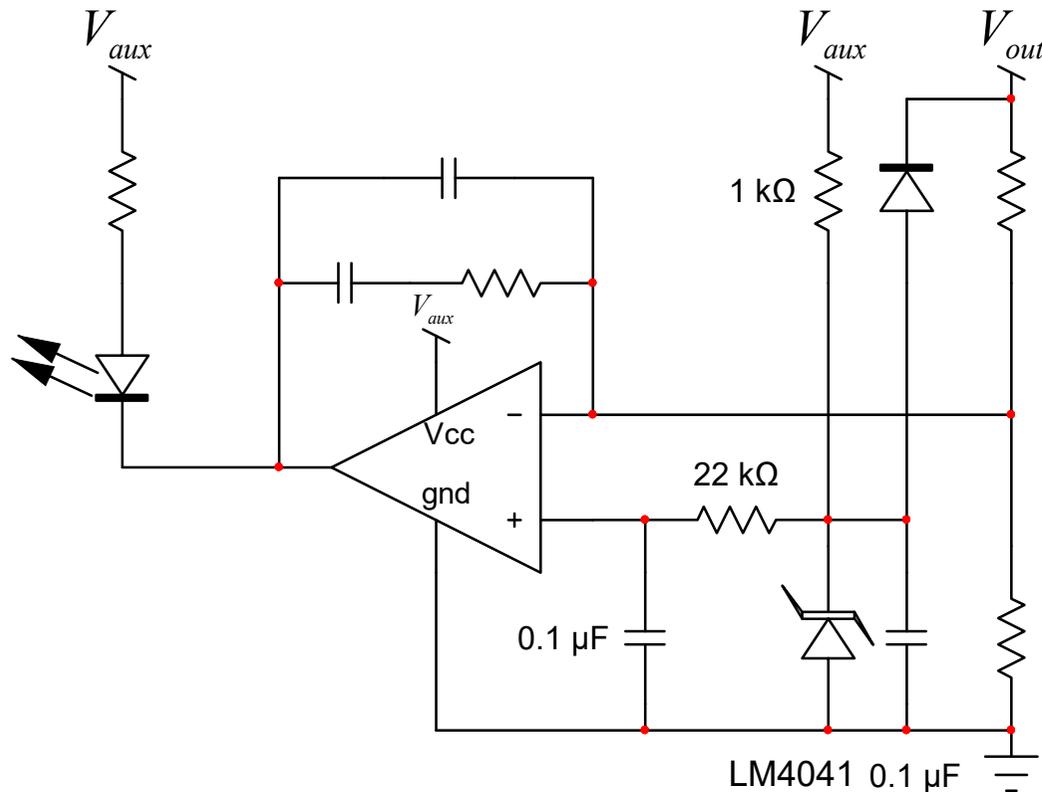
- ❑ Monotonic output is obtained when V_{ref} is soft-started





- ❑ The diode is important to discharge the SS cap. at power off

Clean Start-Up Sequences

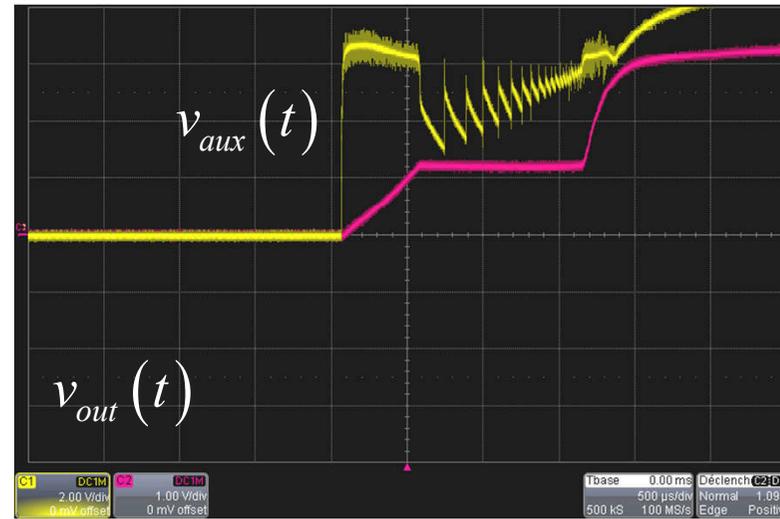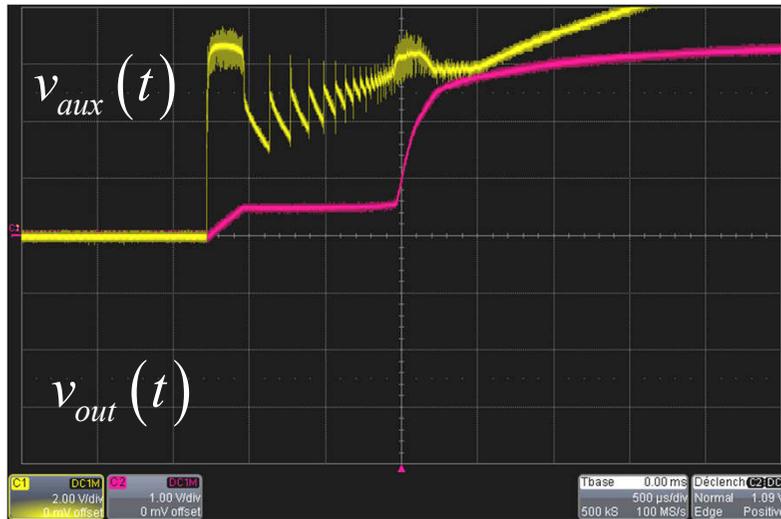- Apply these rules to a prototype and see immediate changes!



Raw
results

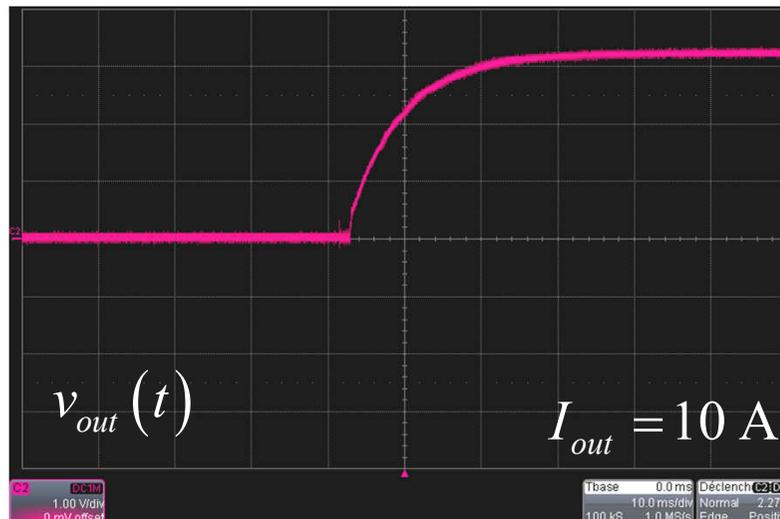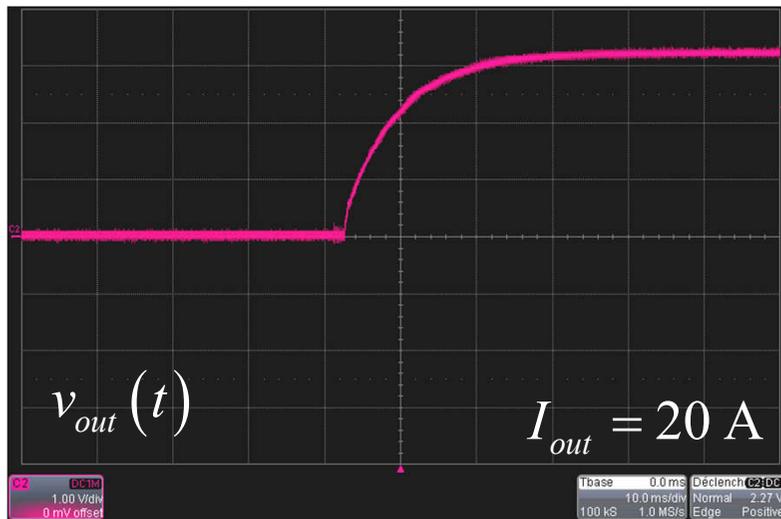

After
optimization

Course Agenda

- ❑ Control System Basics
- ❑ Operational Amplifier and Low-Frequency Pole
- ❑ Gain-Bandwidth Impact on Phase Boost
- ❑ Op Amp Slew Rate Effects in Loop Control
- ❑ Start-Up Sequence and Auxiliary Supply
- ❑ **Characterizing the Optocoupler Pole**
- ❑ Dealing with the Fast Lane
- ❑ Going Around the TL431 Fast Lane





Isolated Switching Converters



- ❑ The transformer ensures isolation from source to load



Utility

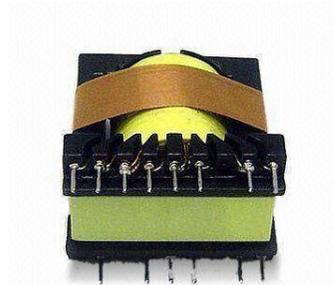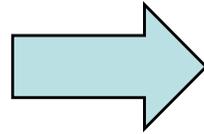



Transformer

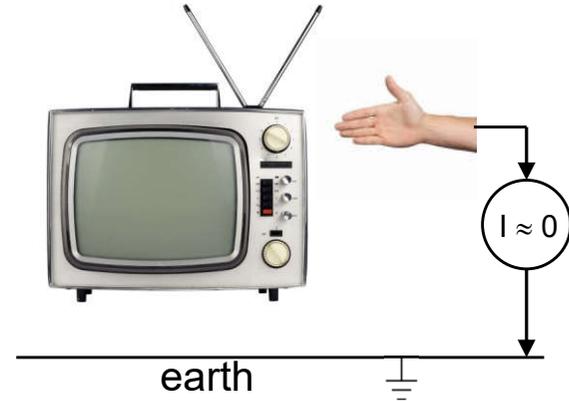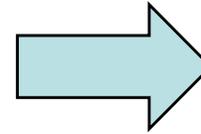

- ❑ In closed-loop systems, the information must be fed back


- ❖ Optocoupler
- ❖ Digital CMOS isolator
- ❖ Transformer

To control circuit

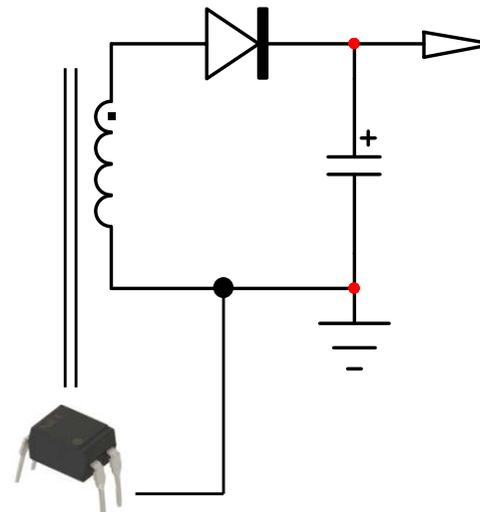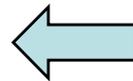


Emitting and Receiving Light

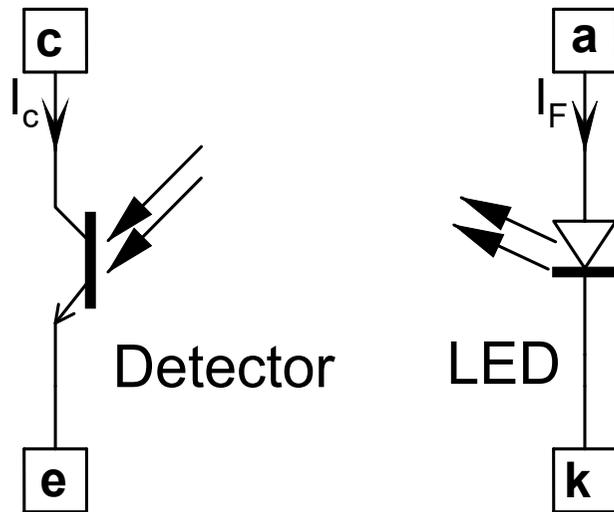- ❑ You need galvanic isolation between the prim. and the sec.
- ❑ An optocoupler transmits light only, no electrical link



$$CTR = \frac{I_c}{I_F} \times 100$$


Current Transfer Ratio

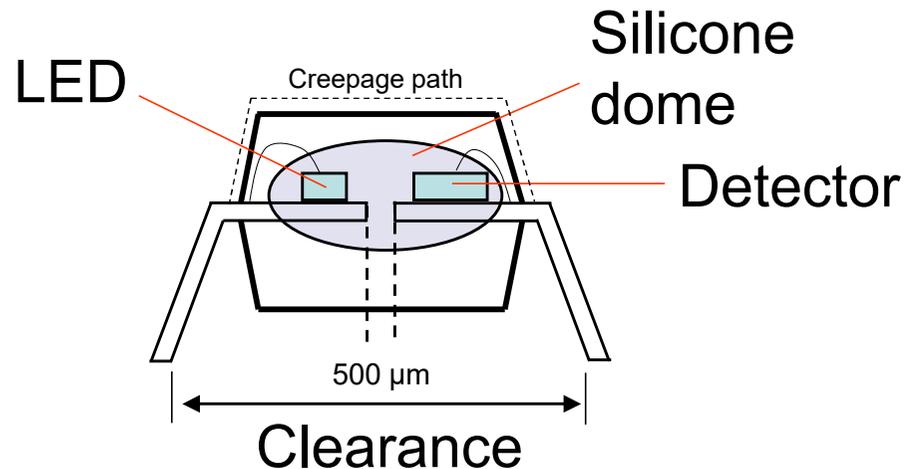

Luigi Galvani, 1737-1798
Italian physician and physicist




French specimen →

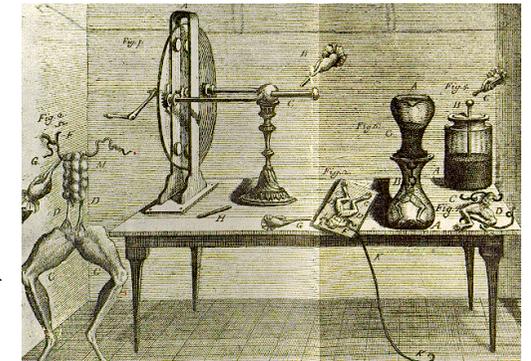

The Optocoupler Corrupts the Return Path

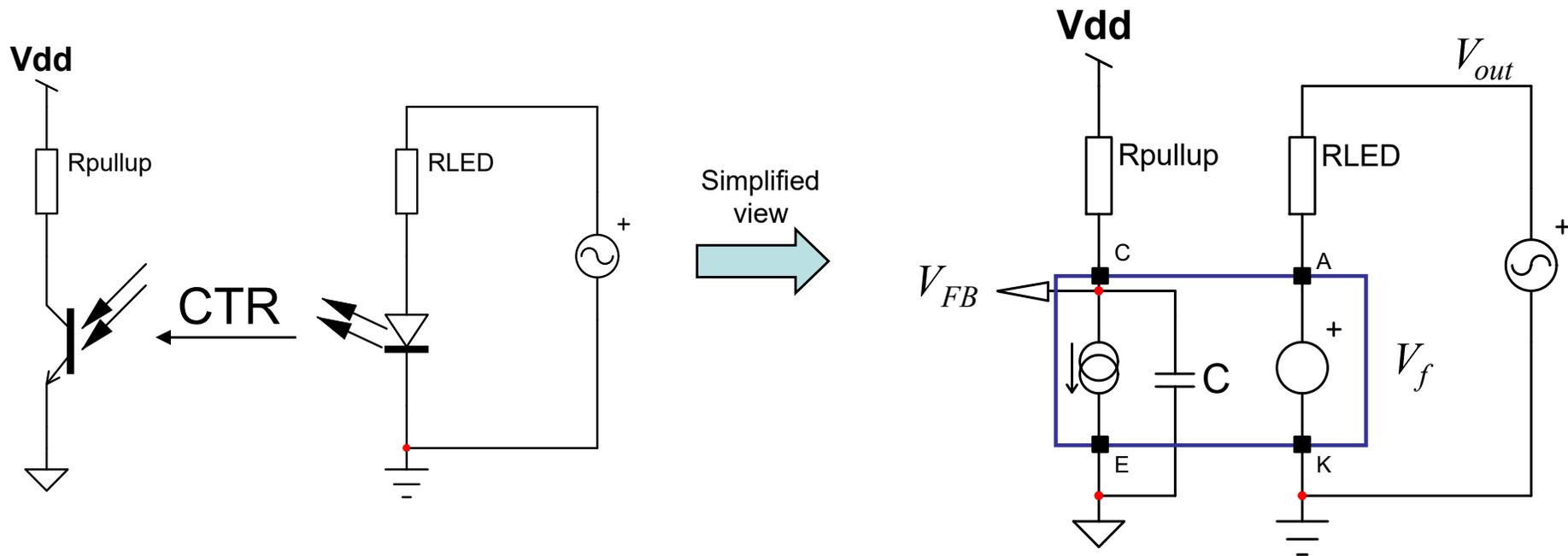- ❑ Photons are collected by a collector-base area
- ❑ This area brings a large CE parasitic capacitance



$$\frac{V_{FB}(s)}{V_{out}(s)} = -\frac{R_{pullup} CTR}{R_{LED}} \frac{1}{1 + sR_{pullup} C}$$

If f_p is well above f_c , its effect is negligible
 If f_p is close to f_c , phase margin degradation

Assess the CTR variations


- ❑ CTR changes with the operating current
- ❑ Try to select collector bias currents around 2-5 mA

Current Transfer Ratio (I_C/I_F at $V_{CE}=5.0$ V) and Collector-emitter Leakage Current

SFH-615

Parameter	-1	-2	-3	-4	-12	-23	-34	-13	-24	-14	Unit
I_C/I_F ($I_F=10$ mA)	40–80	63–125	100–200	160–320	40–125	63–200	100–320	40–200	63–320	40–320	%
I_C/I_F ($I_F=1.0$ mA)	30(>13)	45(>22)	70(>34)	90(>56)	30(>13)	45(>22)	70(>34)	30(>13)	45(>22)	30(>13)	
Collector-Emitter Leakage Current, I_{CEO} , $V_{CE}=10$ V	2.0(≤ 50)	2.0(≤ 50)	5.0(≤ 100)	5.0(≤ 100)	2.0(≤ 50)	5.0(≤ 100)	nA				

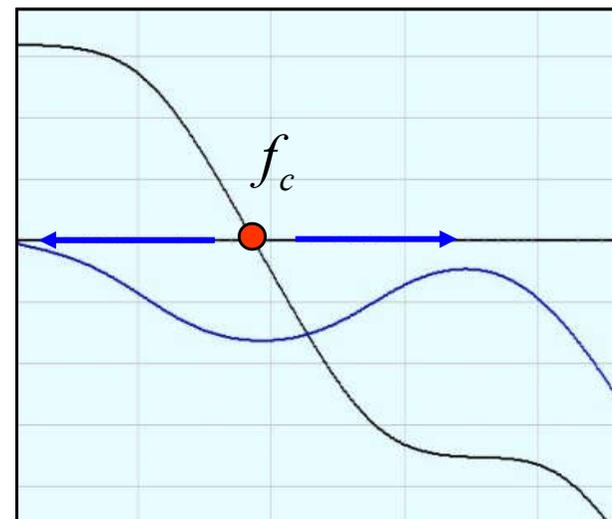CTR between 0.63 and 1.25
 Normalized to 1 (0 dB)
 0.63 gives -4 dB
 1.25 gives +1.9 dB



Watch out for crossover frequency changes and phase margin at CTR extremes!

Selecting the Right Optocoupler


- ❑ High temperature shortens the optocoupler lifetime
- ❑ Low LED currents:
 - expand lifetime
 - CTR dispersion increases
- ❑ Low CTR optocouplers have low internal capacitance
 - Select them for high-bandwidth applications
- ❑ Higher drive currents improve speed but:
 - Shorten lifetime
 - Degrade standby power



Understand the optocoupler impact on your design!

LED Photons Emission Suffers with Age

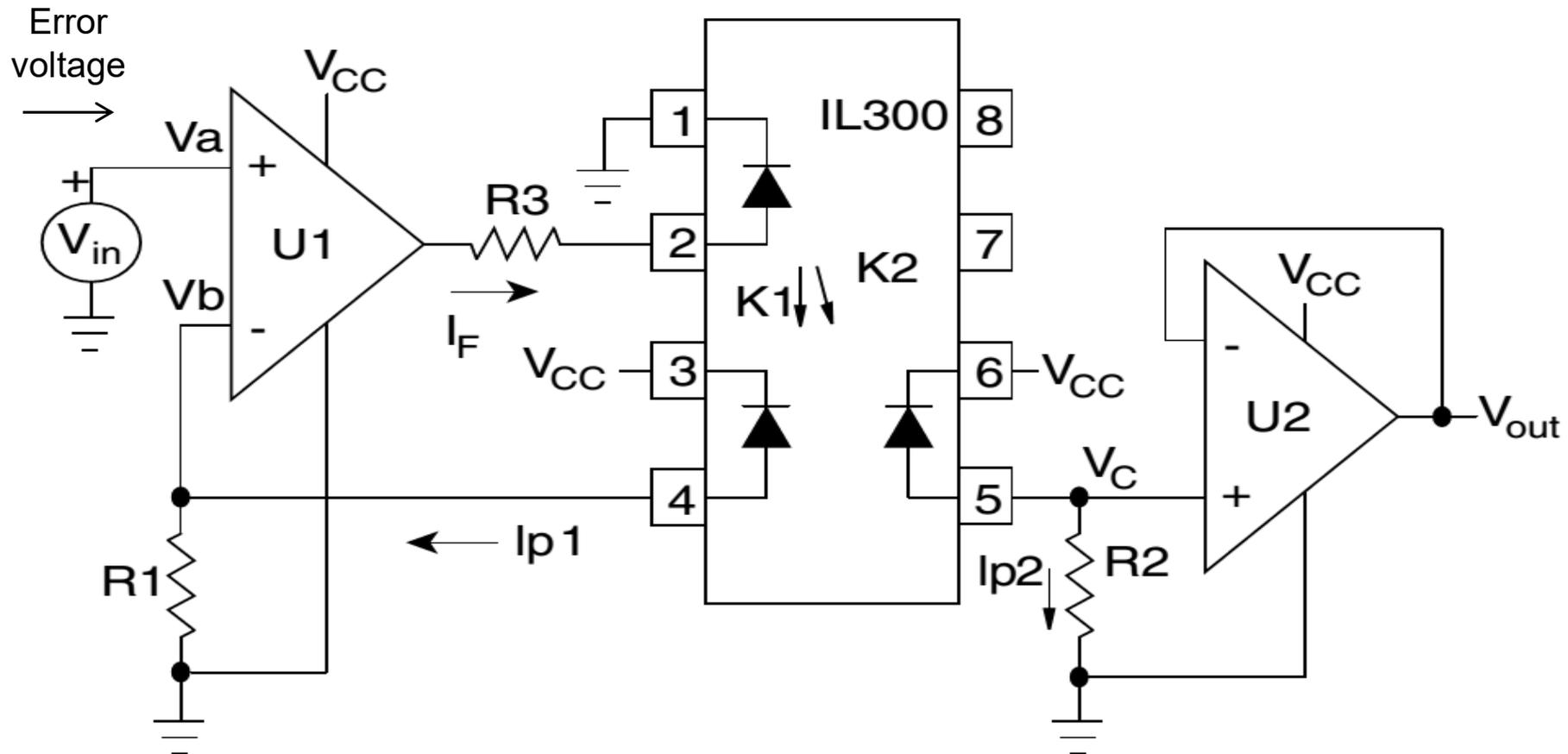- ❑ For long-life applications, compensate for LED degradation




- ❑ IL300 senses the LED light and adjusts driving current

<http://www.vishay.com/docs/83622/il300.pdf>



Where is the Pole?

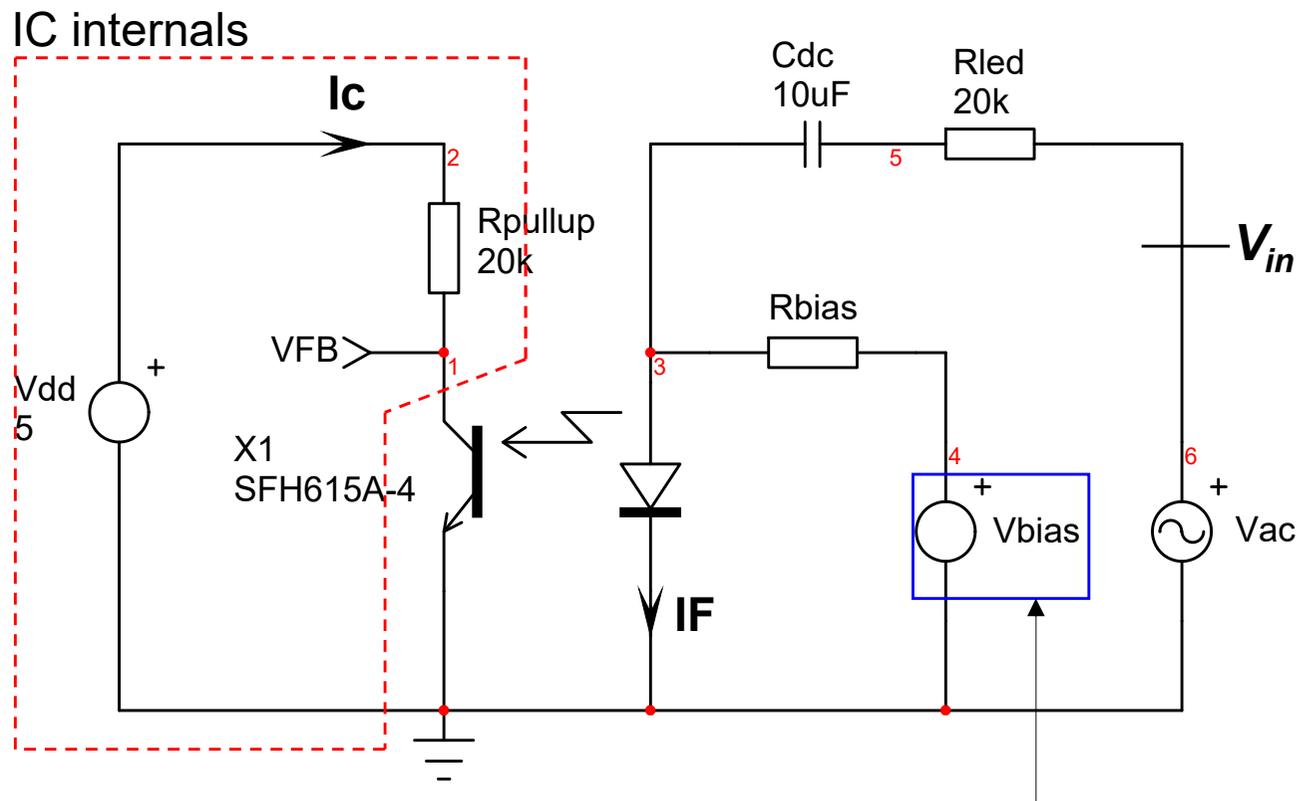
- Once your optocoupler is selected, characterize it



- Adjust V_{bias} to $V_{FB} = 2.5 \text{ V}$ (or $V_{dd}/2$) then ac sweep
- Observe V_{FB} with a scope or a network analyzer

No Need for a Network Analyzer

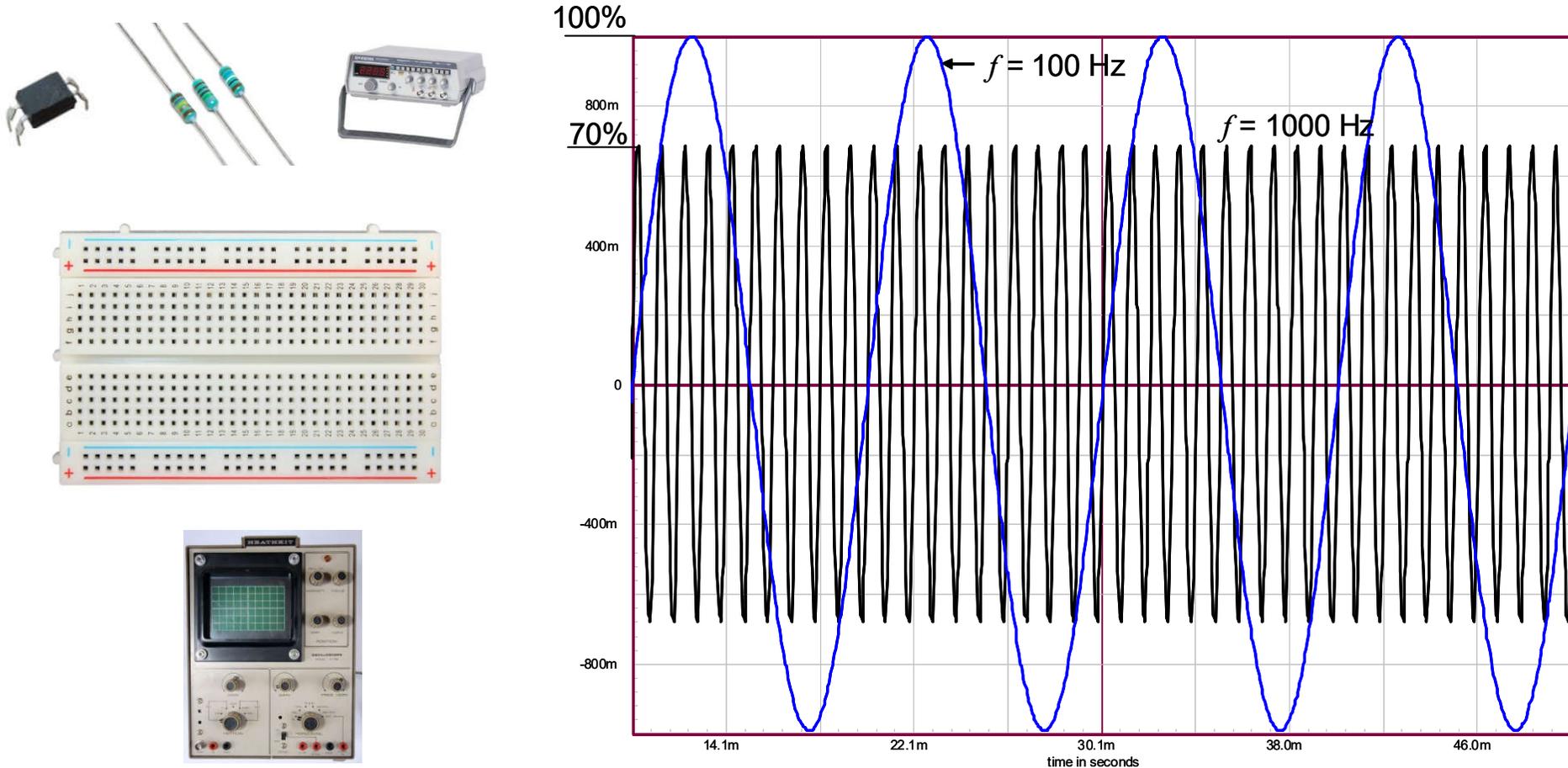
- Pole extraction can also be done with an oscilloscope



- 10 division is the low-frequency reference, 7 divisions is f_p

Adapt the Bias Point to Your Circuit

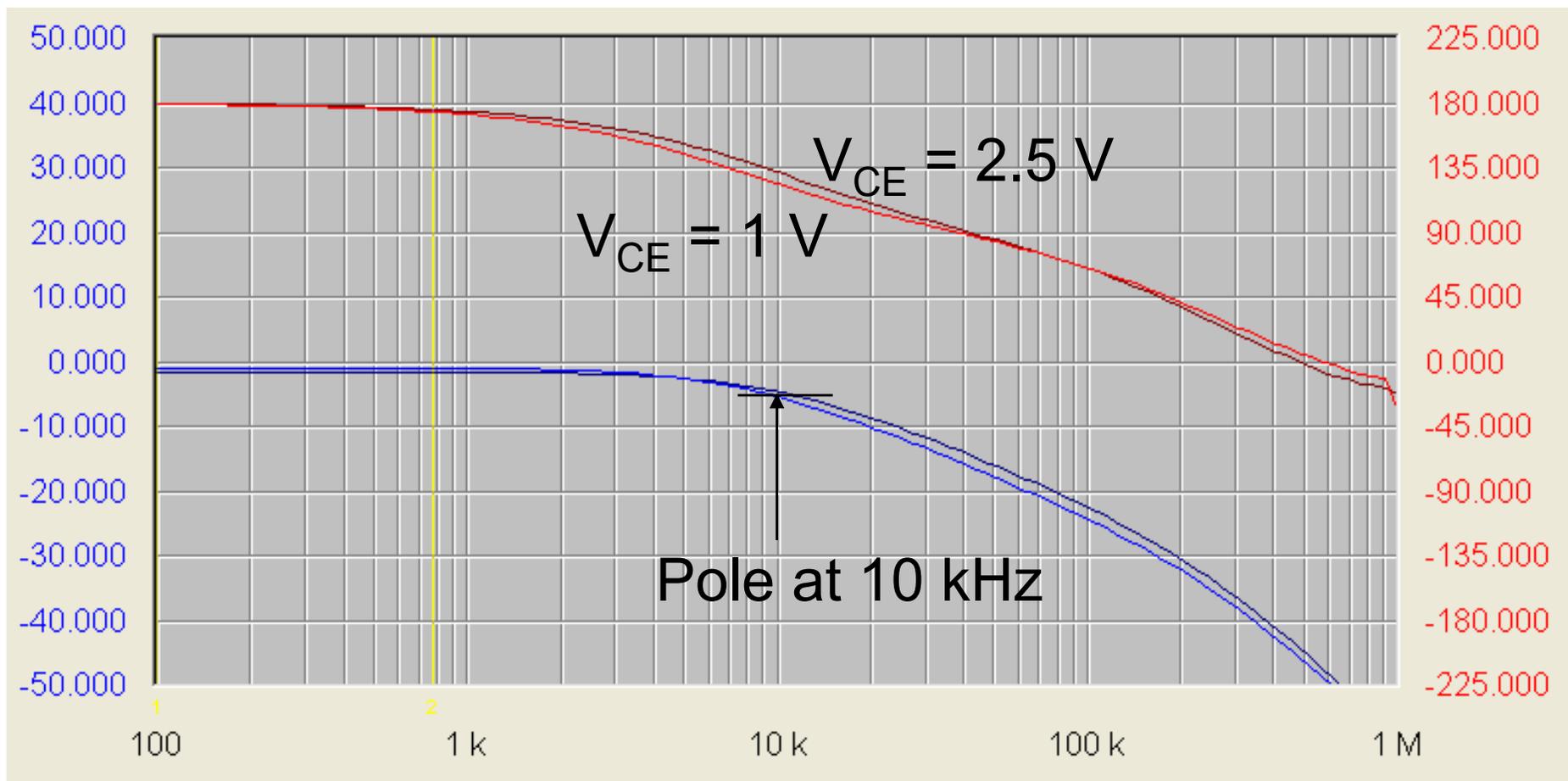- The dc bias does not change the pole position






$$R_{pullup} = 4.7\text{ k}\Omega$$

SFH615A-2

The Pull-Up Resistor Affects the Pole

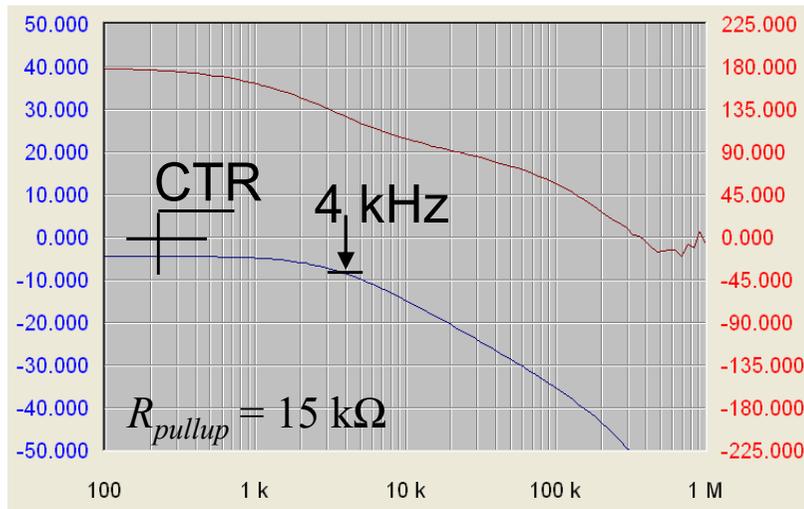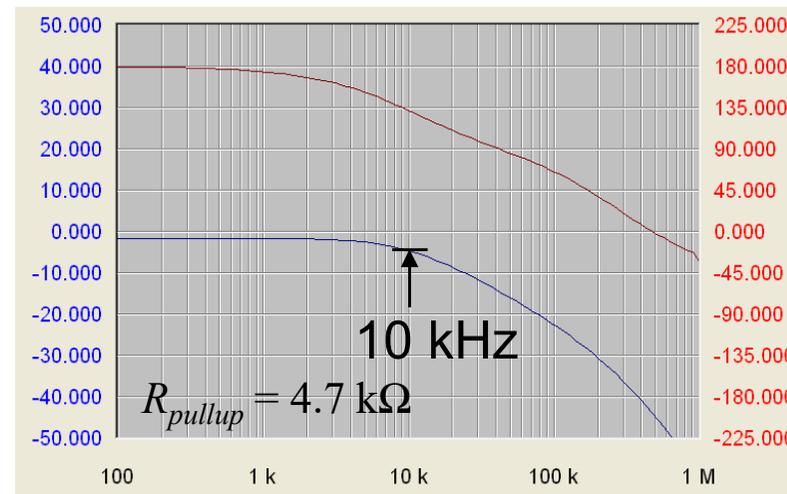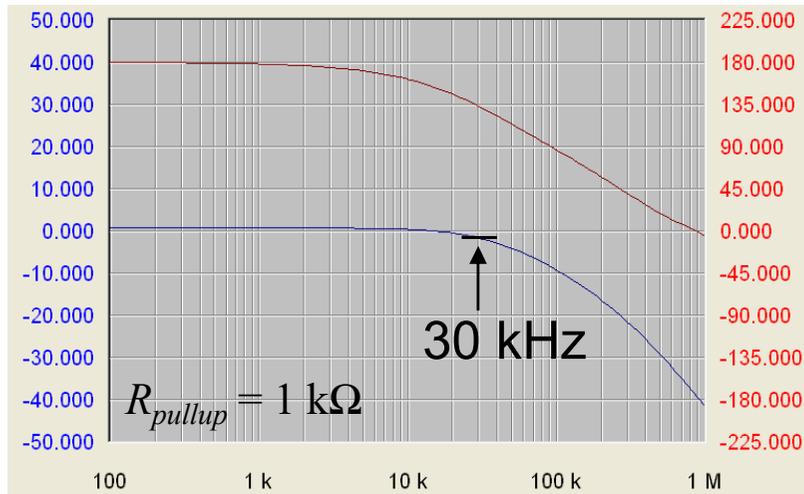- A low value pull-up resistor offers better bandwidth!



- Changing the bias point affects the CTR


$$\frac{V_{FB}(s)}{V_{out}(s)} = -\frac{R_{pullup}}{R_{LED}} \text{CTR}$$

- Low resistor values degrade standby

SFH615A-2


What is the Application Circuit?

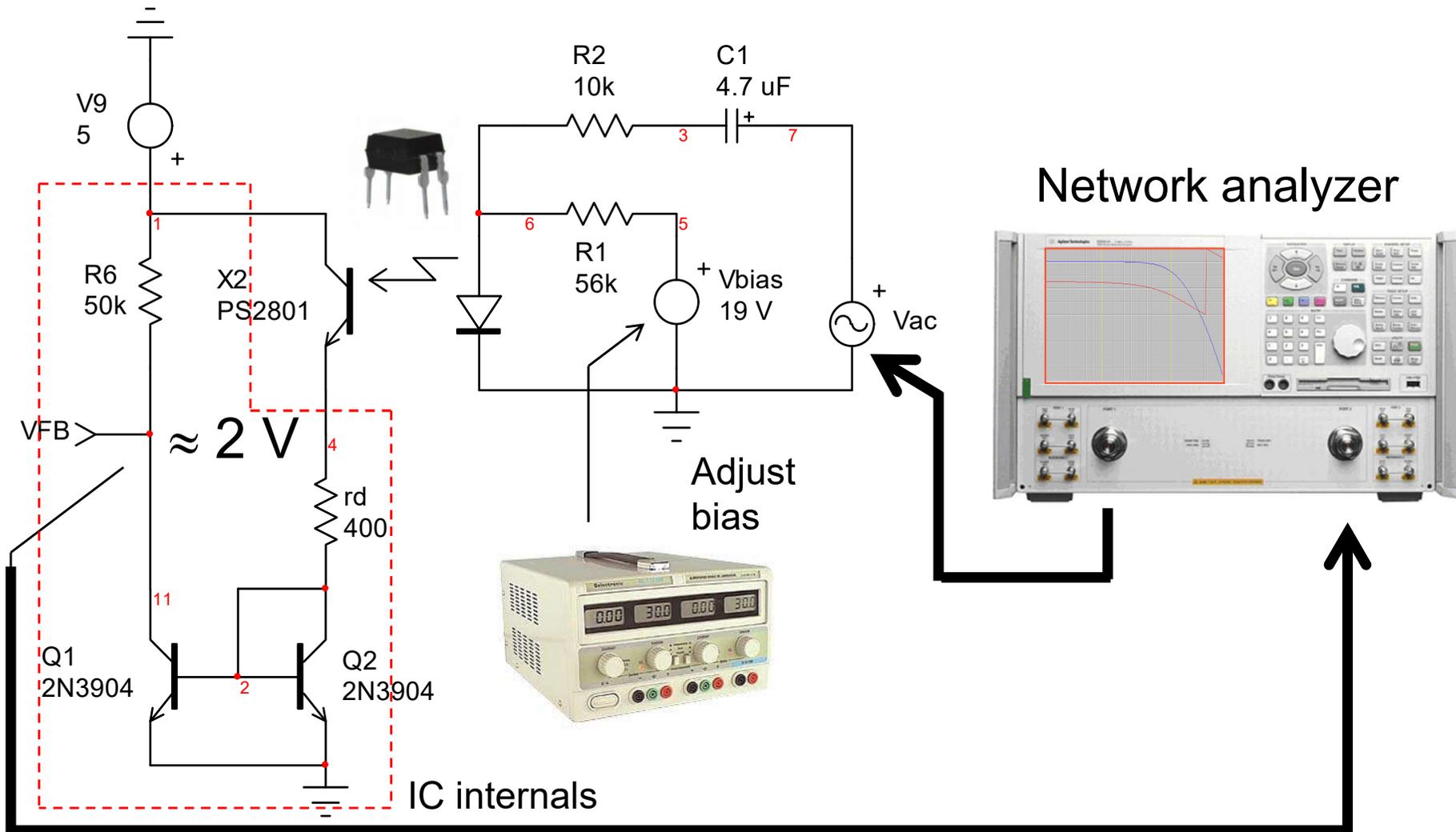- ❑ You need to recreate the optocoupler biasing conditions




Pole Will Stress the Phase at Crossover

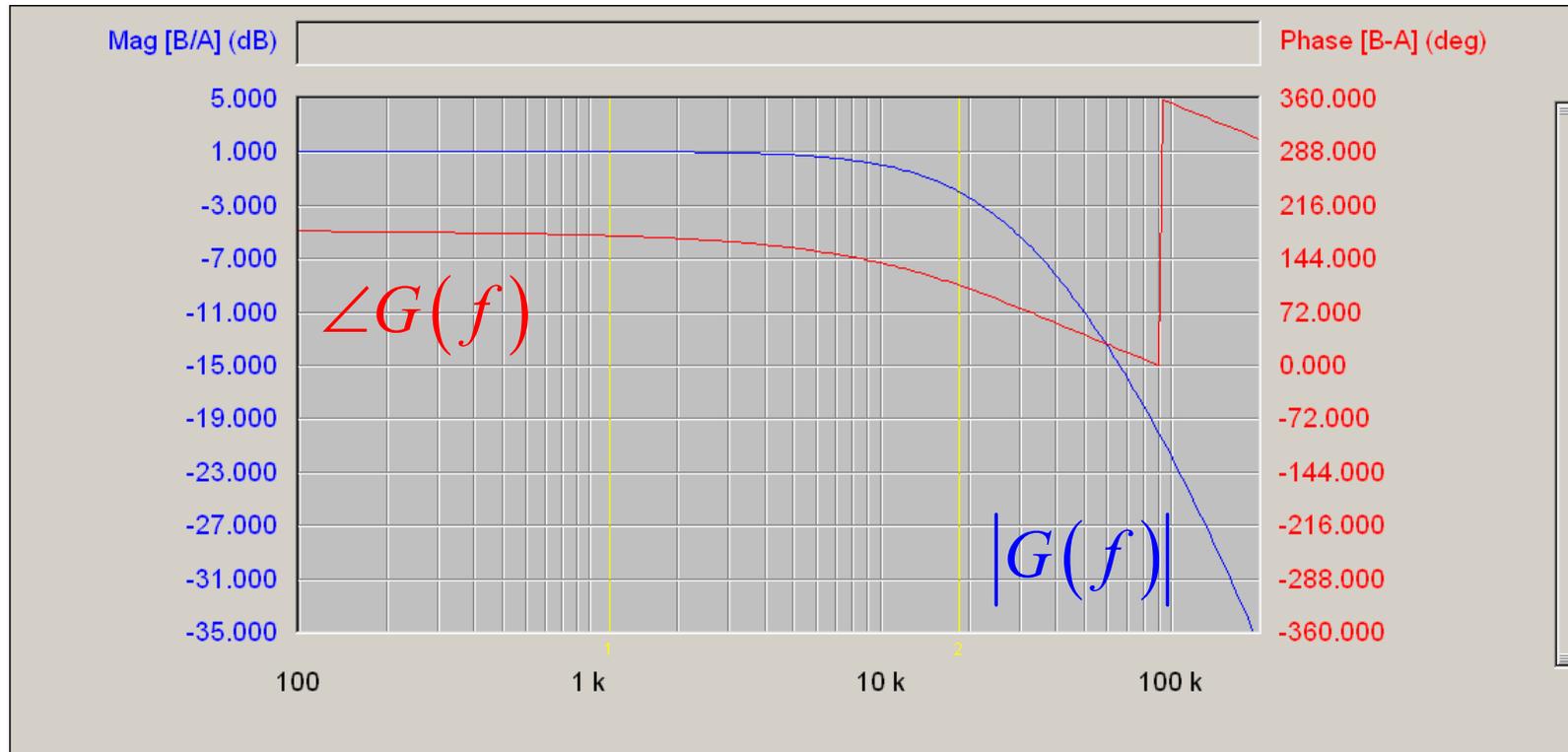- The pole is located at 17.5 kHz, R_d is 400 Ω




- ❖ Phase lag can potentially bother compensation

Compensating the Optocoupler Poke

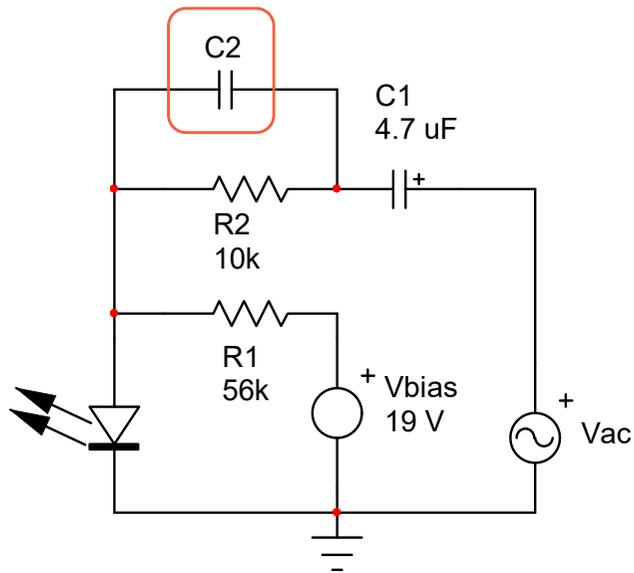



□ A zero compensates the pole
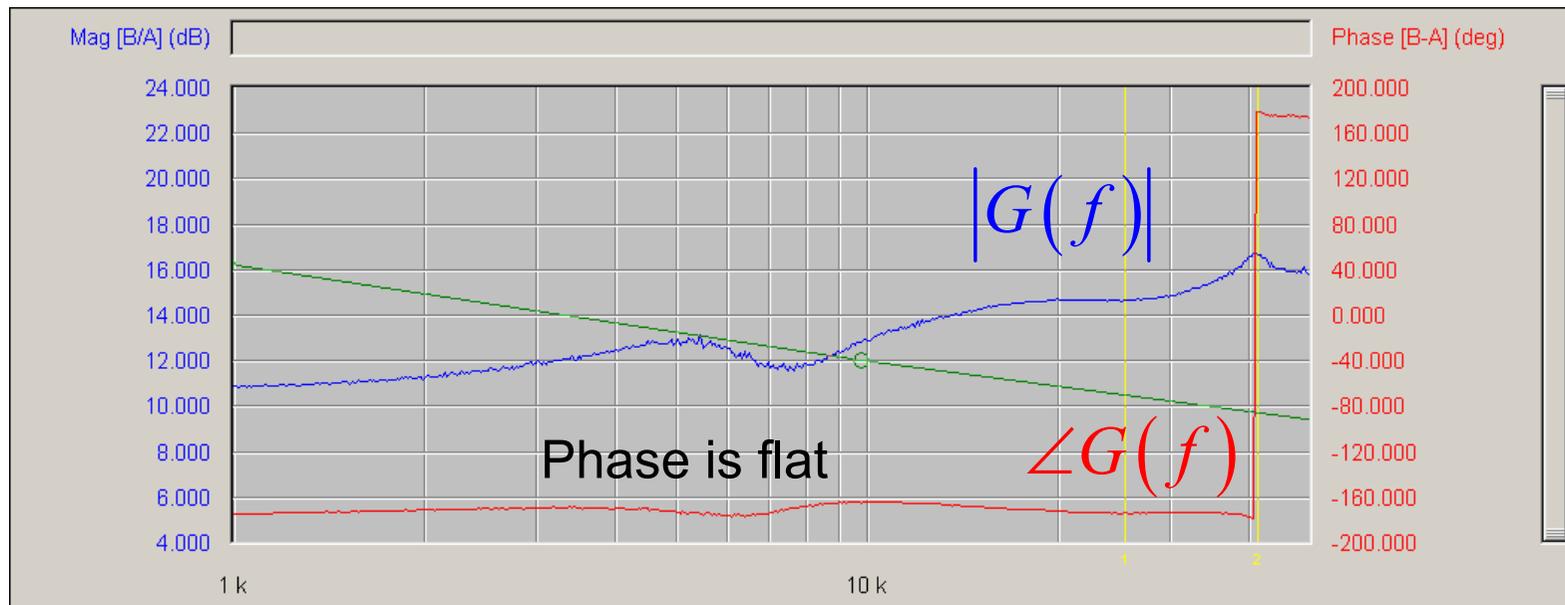
$$C_2 = \frac{1}{2\pi f_{pole} R_2} \approx 870 \text{ pF}$$



Push the Pole Farther with a Cascode


- ❑ The cascode fixes the optocoupler collector potential
- ❑ It neutralizes the Miller capacitance in the optocoupler

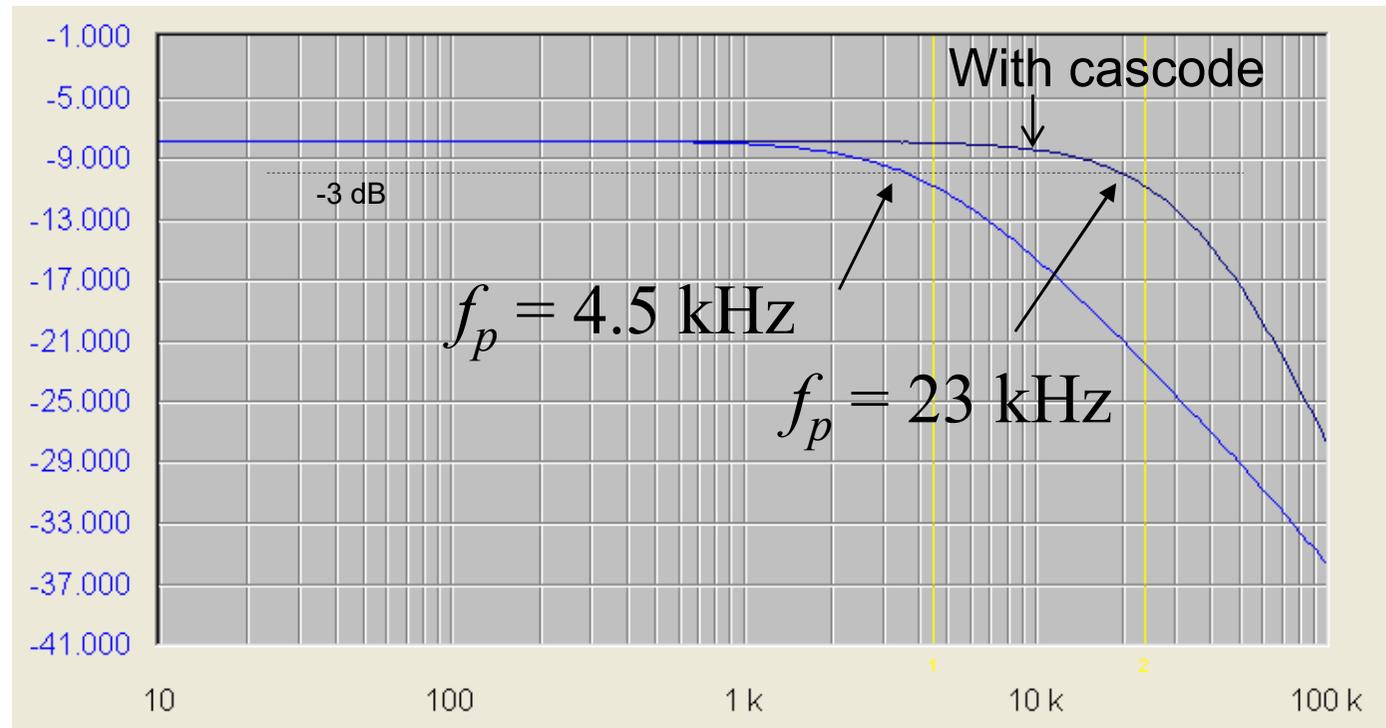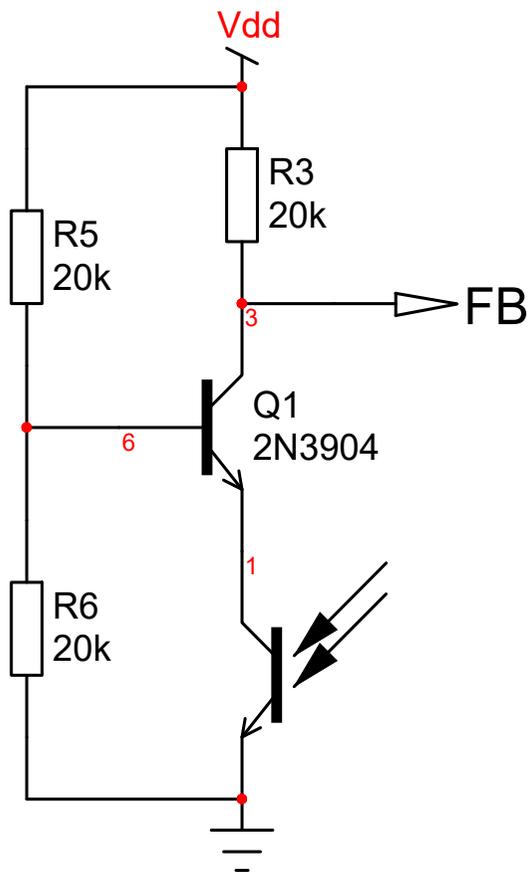

SFH615A-2

A Simple Optocoupler Model

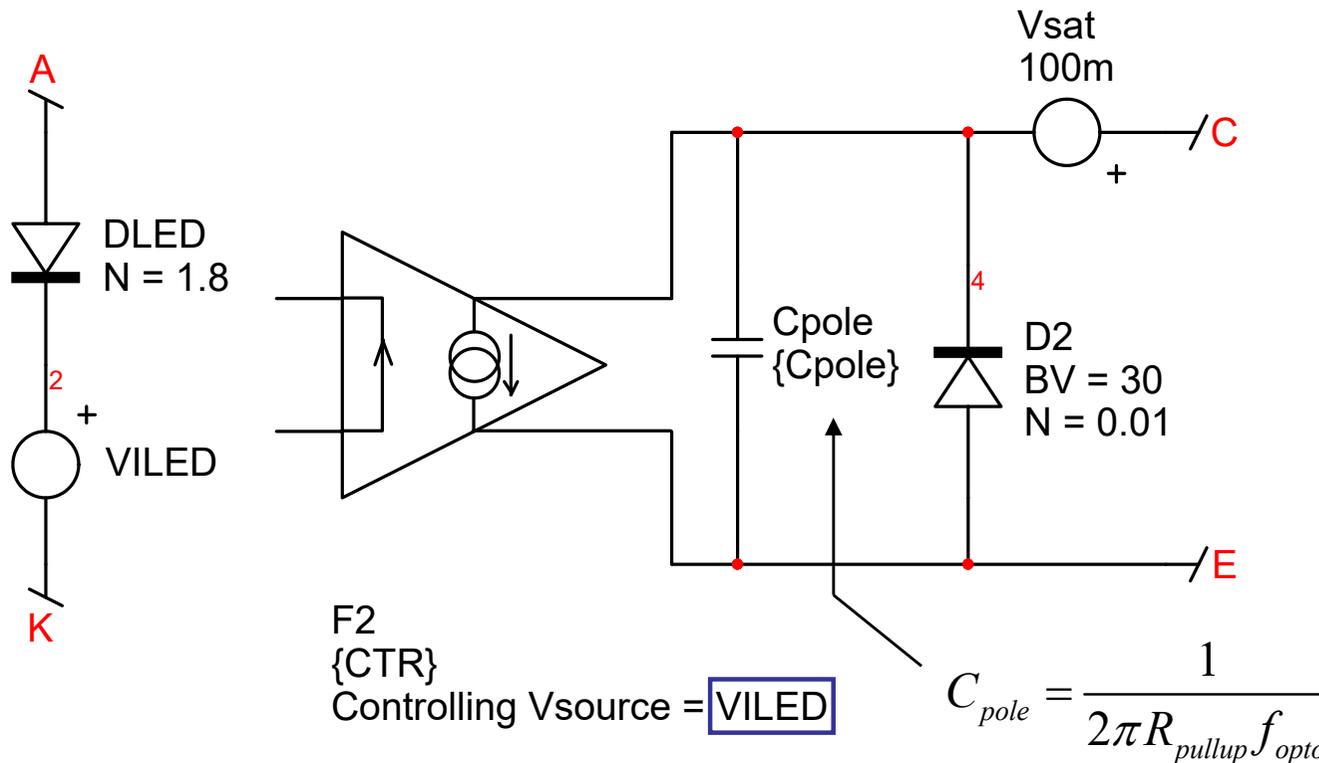- ❑ Read the pole position and the CTR value
- ❑ Adjust the internal capacitor value to fix the pole



- ❑ Ok for low-frequency exploration, no 2nd-order effects


Course Agenda

- Control System Basics
- Operational Amplifier and Low-Frequency Pole
- Gain-Bandwidth Impact on Phase Boost
- Op Amp Slew Rate Effects in Loop Control
- Start-Up Sequence and Auxiliary Supply
- Characterizing the Optocoupler Pole
- Dealing with the Fast Lane**
- Going Around the TL431 Fast Lane



A Single Current Path

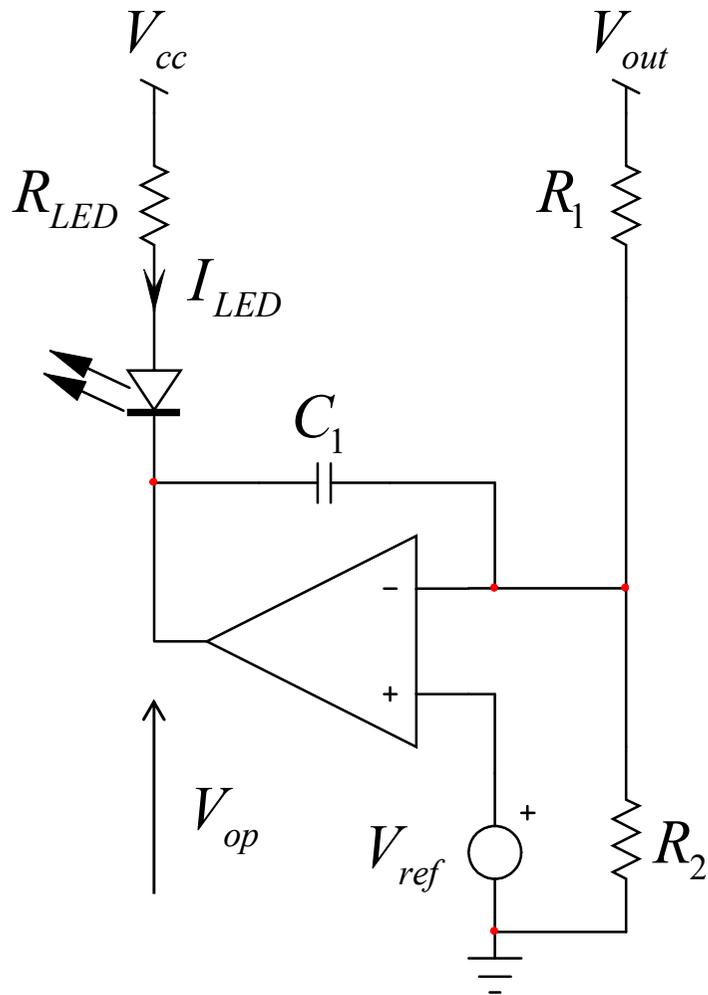- There is a single ac path which defines the LED current: V_{out}



$$I_{LED}(s) = \frac{\cancel{V_{cc}} - V_{op}(s)}{R_{LED}} = -\frac{V_{op}(s)}{R_{LED}}$$


$$V_{op}(s) = -\frac{1}{sC_1} = -\frac{1}{sR_1C_1} = -\frac{1}{s\omega_{po}}$$

➔
$$I_{LED}(s) = \frac{1}{R_{LED}} \frac{1}{s\omega_{po}}$$

Integrator, single pole

A Second Path Creates the Fast Lane

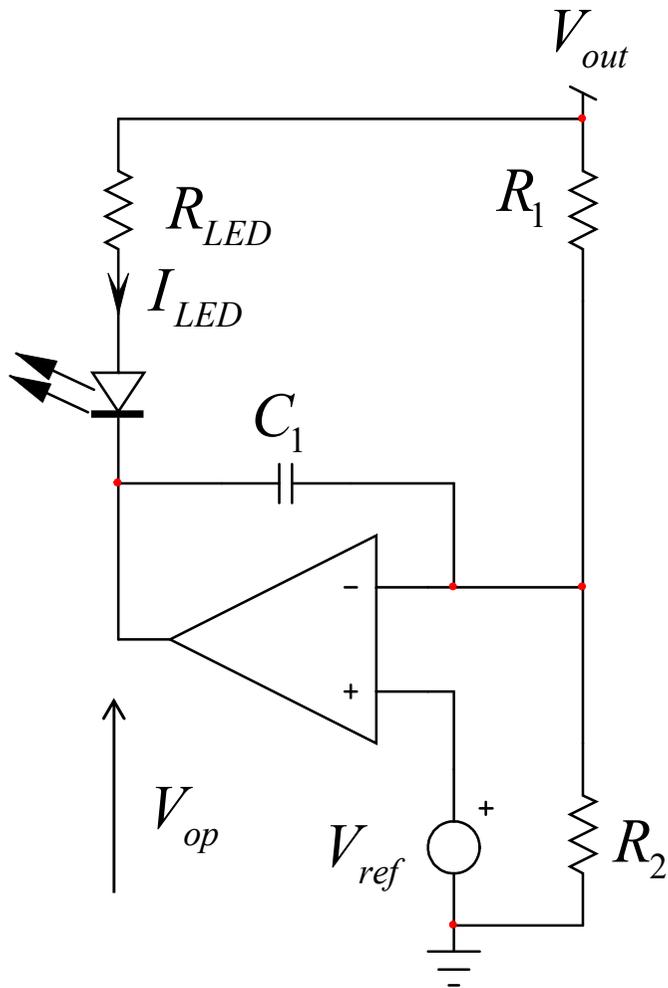- The optocoupler current now depends on V_{out} via two paths



$$I_{LED}(s) = \frac{V_{out}(s) - V_{op}(s)}{R_{LED}}$$

$$V_{op}(s) = -\frac{sC_1}{R_1} = -\frac{1}{sR_1C_1}$$


$$I_{LED}(s) = \frac{1}{R_{LED}} \left(1 + \frac{1}{sR_1C_1} \right)$$

$$= \frac{1}{R_{LED}} \left(\frac{1 + sR_1C_1}{sR_1C_1} \right) = \frac{1}{R_{LED}} \left(\frac{1 + \boxed{s/\omega_z}}{\frac{s}{\omega_{po}}} \right)$$

➔ Integrator plus a zero

The Fast Lane Prevents Gain Roll-off


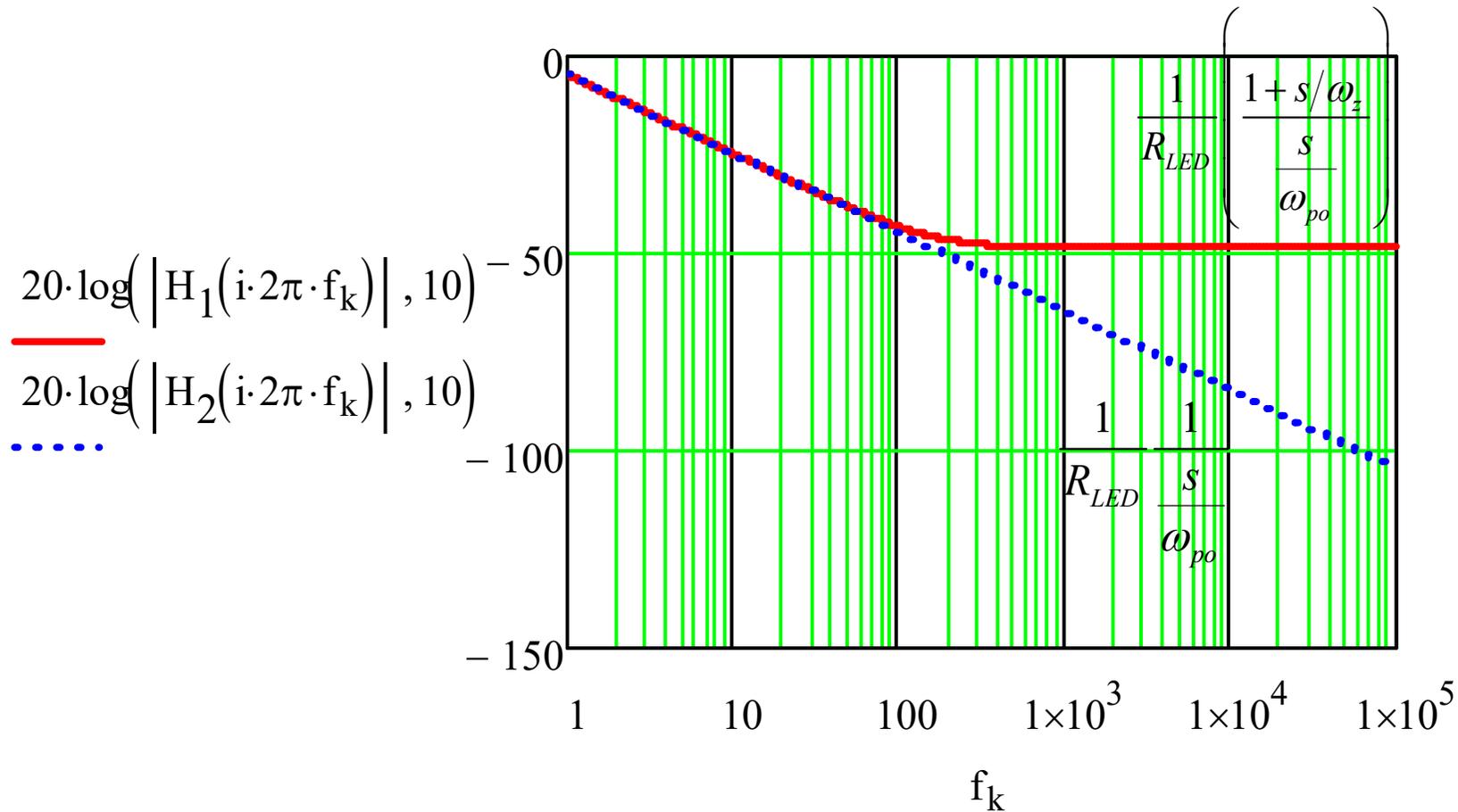
- With the fast lane presence, you cannot roll off the gain



- The zero imposes a fixed gain as s approaches infinity

Disconnect the Fast Lane!

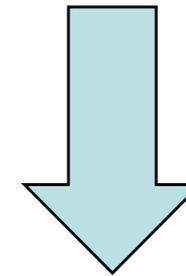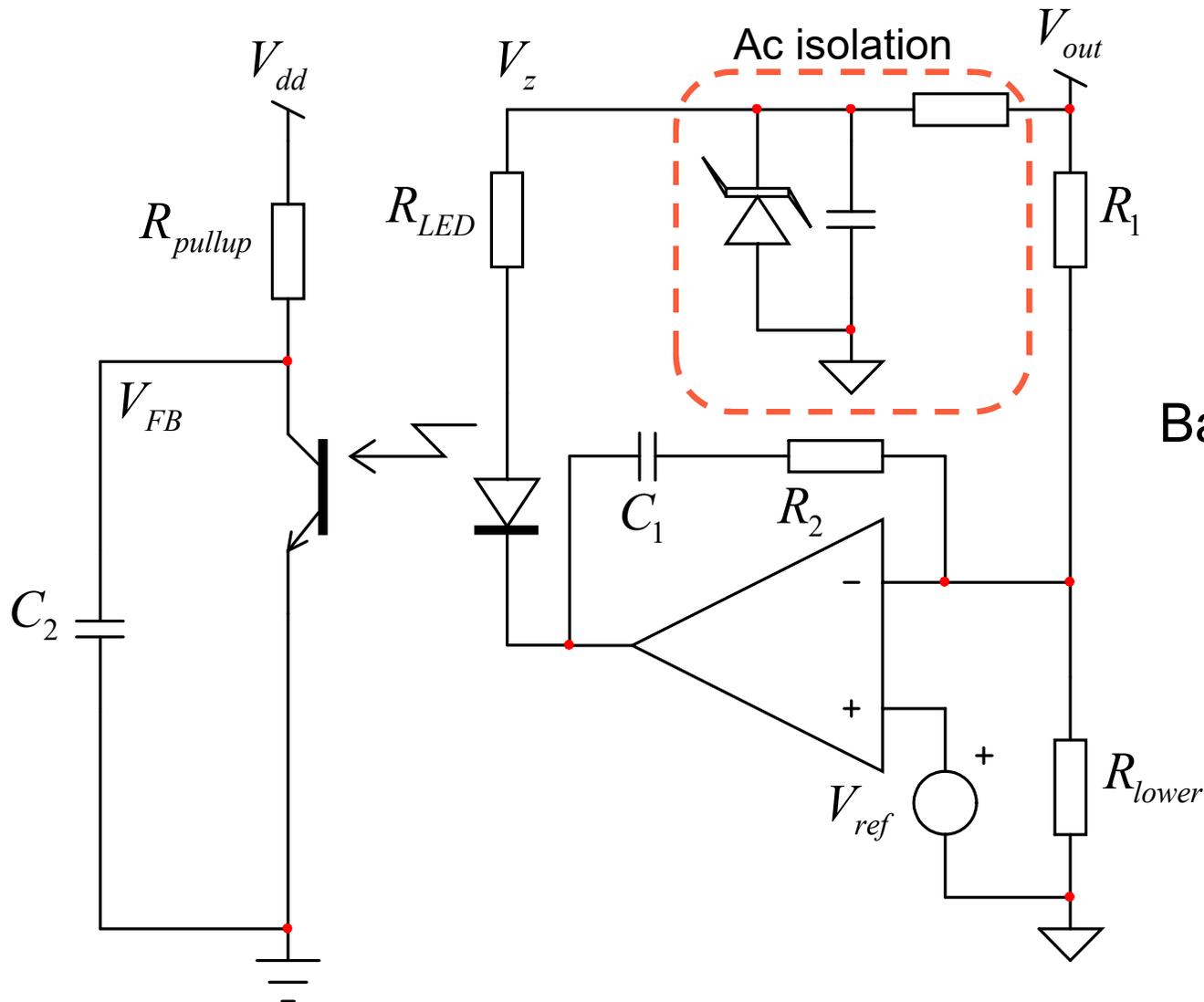
- ❑ One solution is to get rid of the fast lane via ac isolation



Back to an open-collector configuration

Same Issue with a TL431

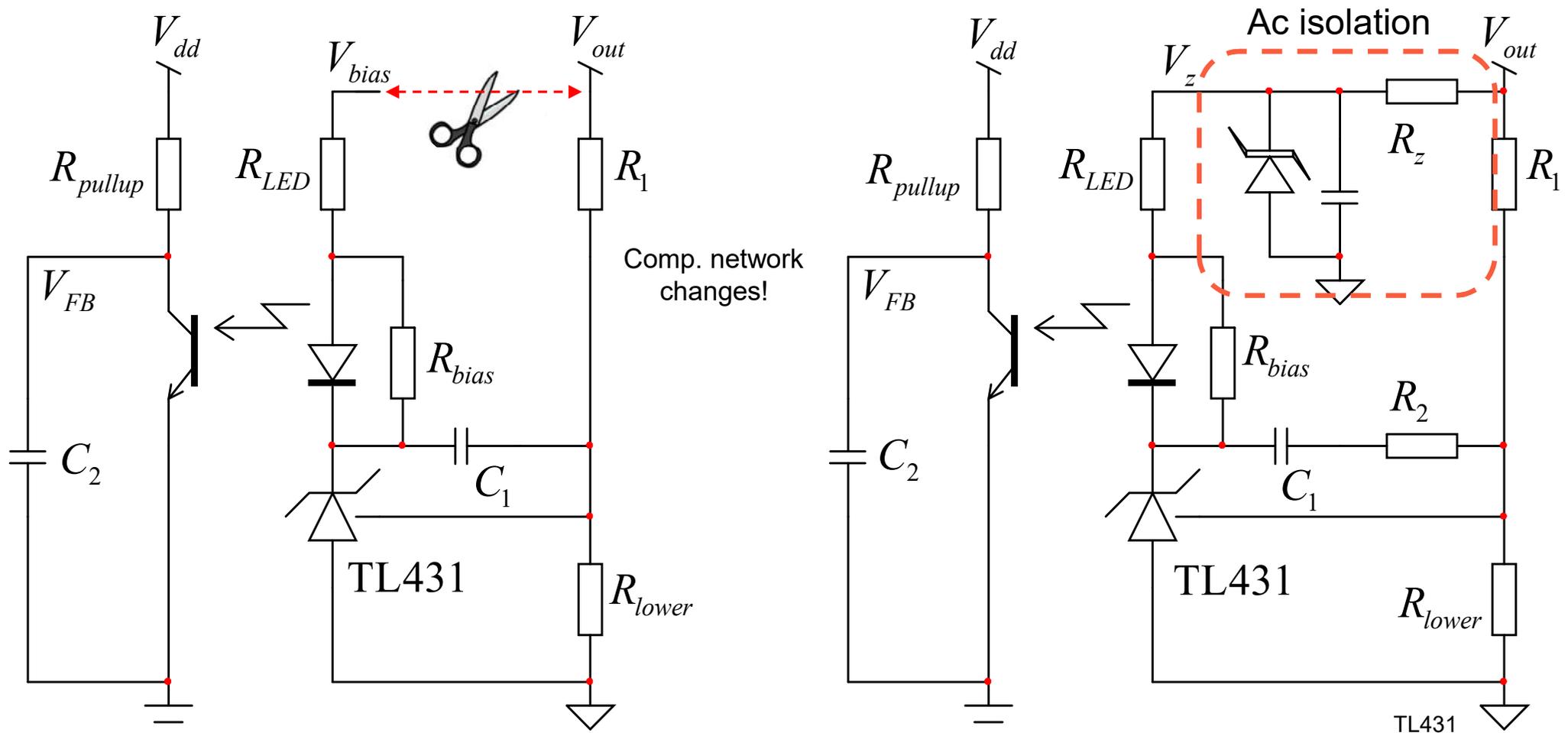- ❑ The TL431 exhibits exactly the same fast lane problem



- ❑ The solution is to also ac-isolate the fast lane from V_{out}

What is the Impact on Compensator?

- ❑ A poor ac-isolation will corrupt the compensator response

parameters

$R_{pullup}=1k$
 $F_{opto}=15k$
 $C_{opto}=1/(2*\pi*R_{pullup}*F_{opto})$
 $CTR=0.8$
 $G=10^{-(G_{fc}/20)}$


$R_{LED}=R_{max}*0.8$
 $R_{LED1}=910$

$G_1=R_{pullup}*CTR/R_{LED}$
 $G_2=G/G_1$

$C_1=1/(2*\pi*f_{z1}*R_2)$
 $C_3=(f_{p2}-f_{z2})/(2*\pi*R_1*f_{p2}*f_{z2})$
 $R_3=R_1*f_{z2}/(f_{p2}-f_{z2})$

$a=\sqrt{(f_c^2/f_{p1}^2)+1}$
 $b=\sqrt{(f_c^2/f_{p2}^2)+1}$
 $c=\sqrt{(f_{z1}^2/f_c^2)+1}$
 $d=\sqrt{(f_c^2/f_{z2}^2)+1}$

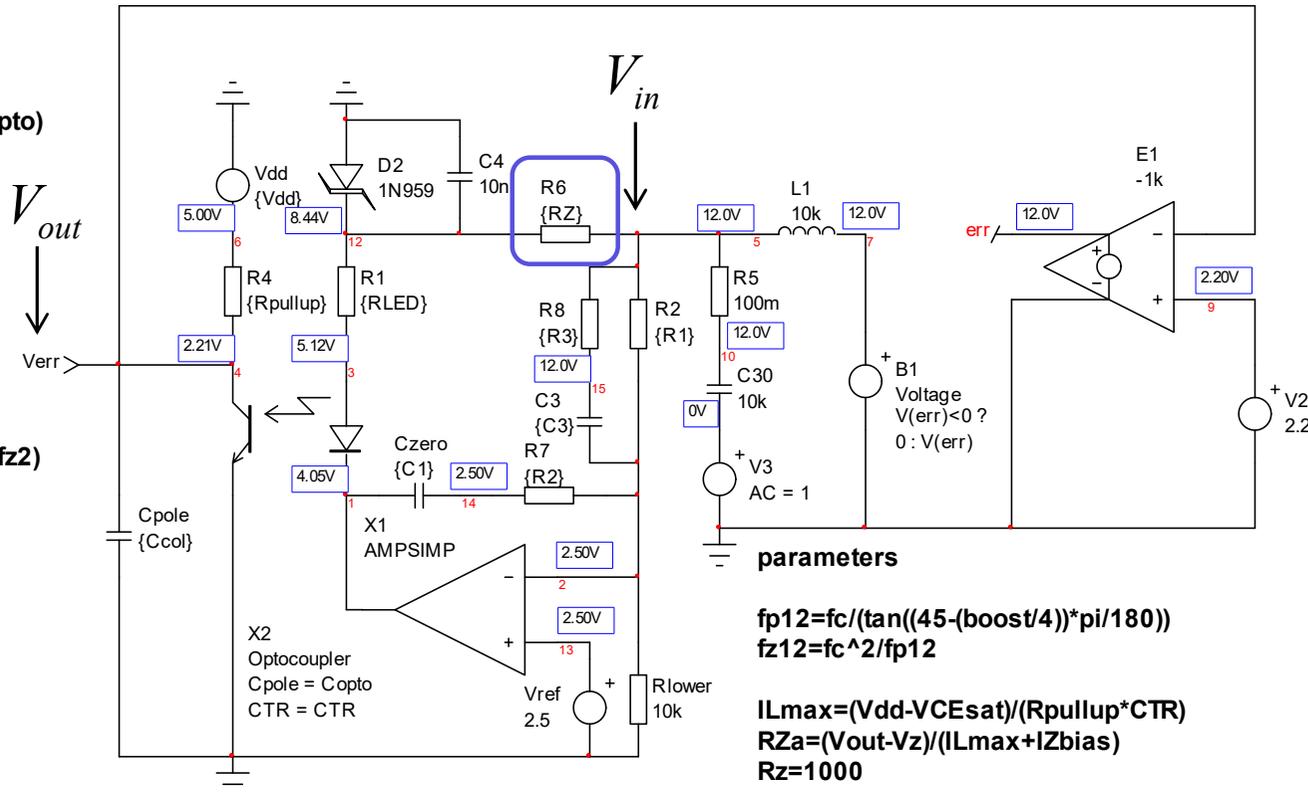$R_2=(a*b/(c*d))*R_1*G_2$
 $C_2=1/(2*\pi*f_{p1}*R_{pullup})$
 $C_{col}=C_2-C_{opto}$



parameters

$V_{out}=12V$
 $R_1=38k$
 $f_c=1.8k$
 $G_{fc}=10$
 $boost=150$
 $G=10^{-(G_{fc}/20)}$
 $\pi=3.14159$

$f_{z1}=f_{z12}$
 $f_{z2}=f_{z12}$
 $f_{p1}=f_{p12}$
 $f_{p2}=f_{p12}$

$V_{OL}=0.2$
 $V_{CEsat}=0.3$
 $V_{dd}=5$
 $V_z=8.2$
 $V_f=1$

$I_{Zbias}=1m$
 $AA=V_z-V_f-V_{OL}$
 $BB=V_{dd}-V_{CEsat}$
 $R_{max}=(AA/BB)*R_{pullup}*CTR$

parameters


$f_{p12}=f_c/(\tan((45-(boost/4))*\pi/180))$
 $f_{z12}=f_c^2/f_{p12}$

$I_{Lmax}=(V_{dd}-V_{CEsat})/(R_{pullup}*CTR)$
 $R_{Za}=(V_{out}-V_z)/(I_{Lmax}+I_{Zbias})$
 $R_z=1000$

- ❑ The Zener diode bias point is changed by adjusting R_6


Poor Isolation Corrupts Phase Boost

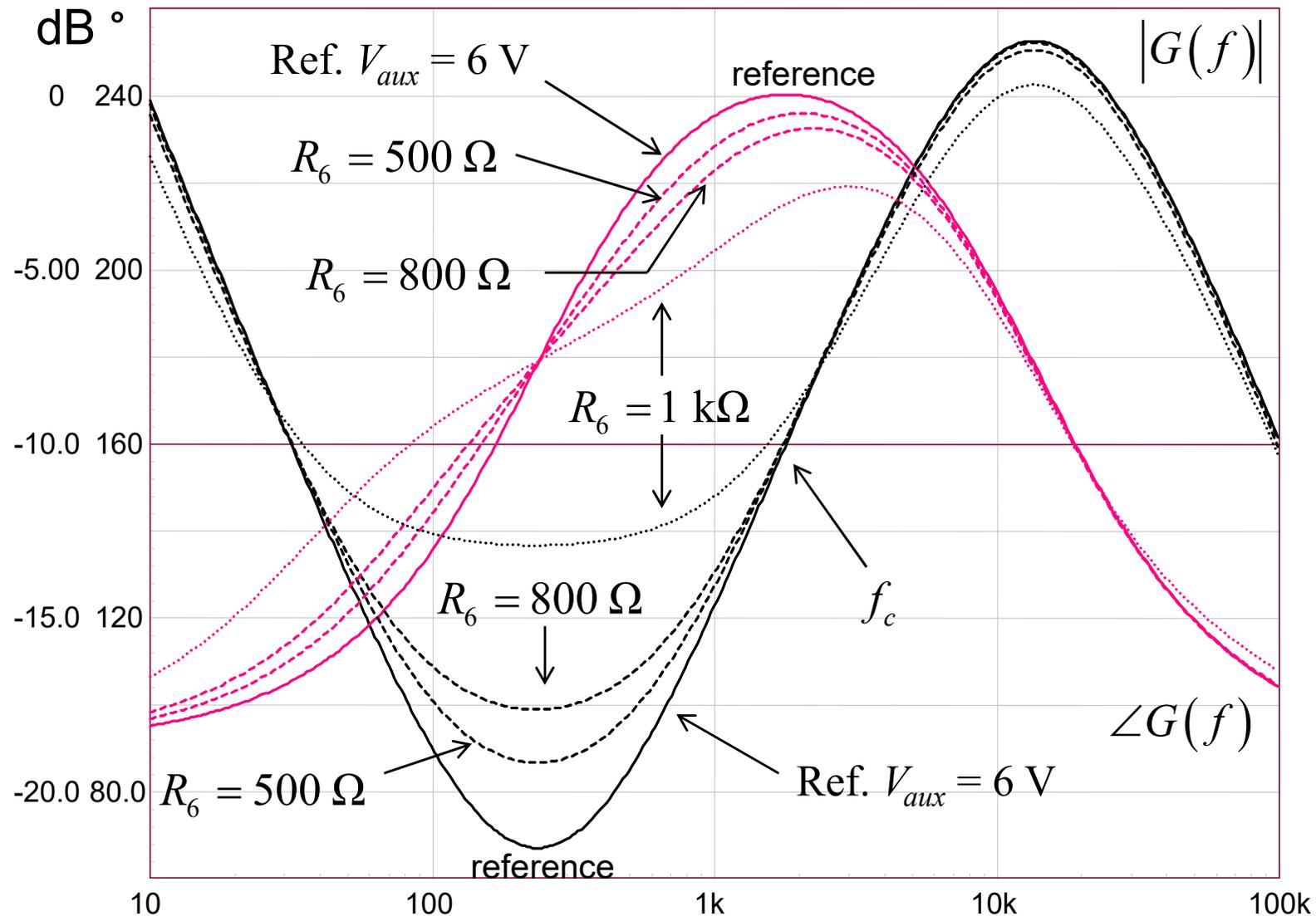- As dynamic resistance changes, ac response degrades






Practical Experimentation Around the Zener

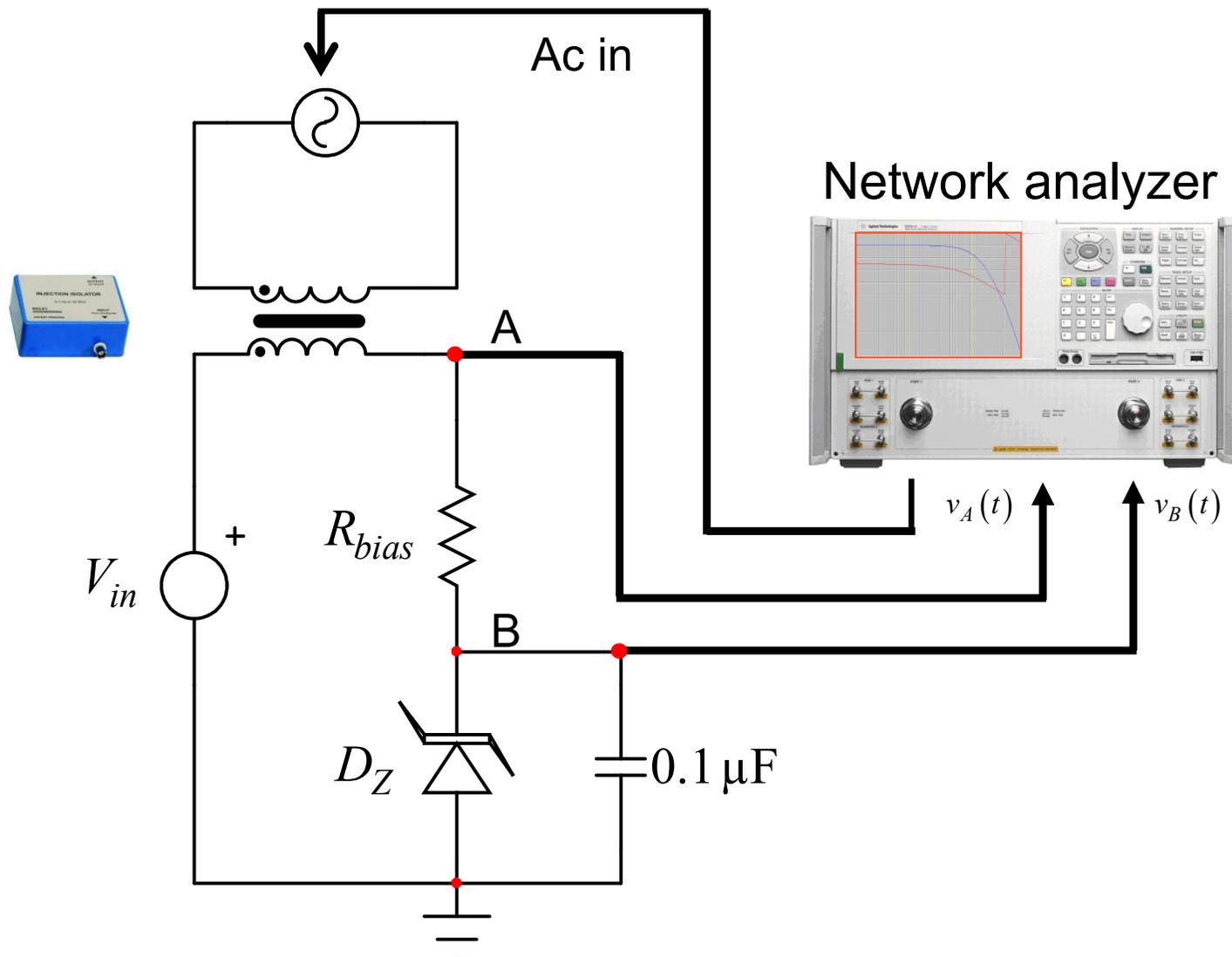- How much isolation does a biased Zener diode provide?



Check Zener Isolation Capability


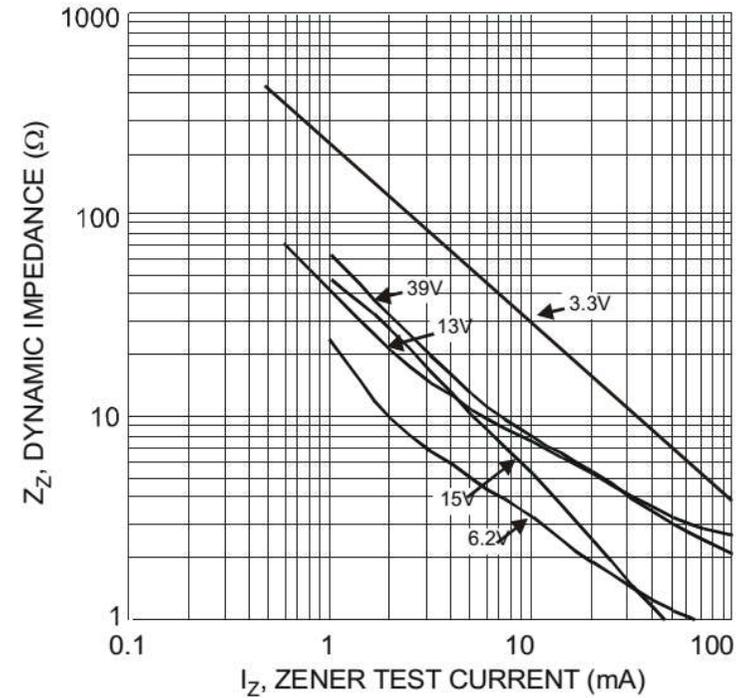
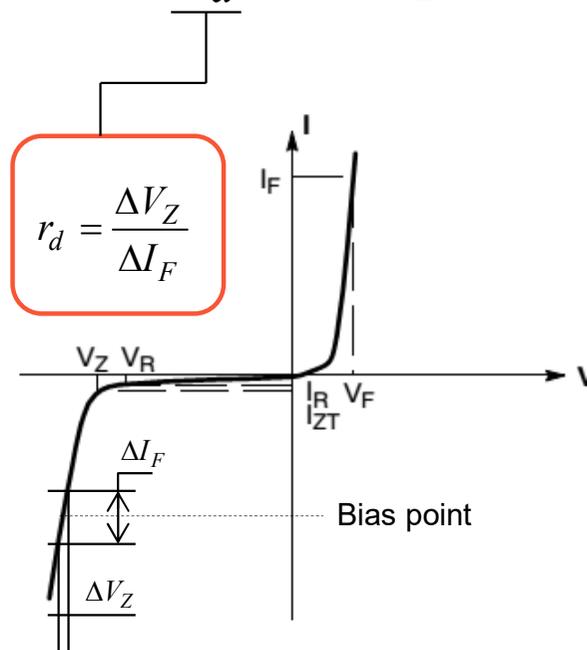
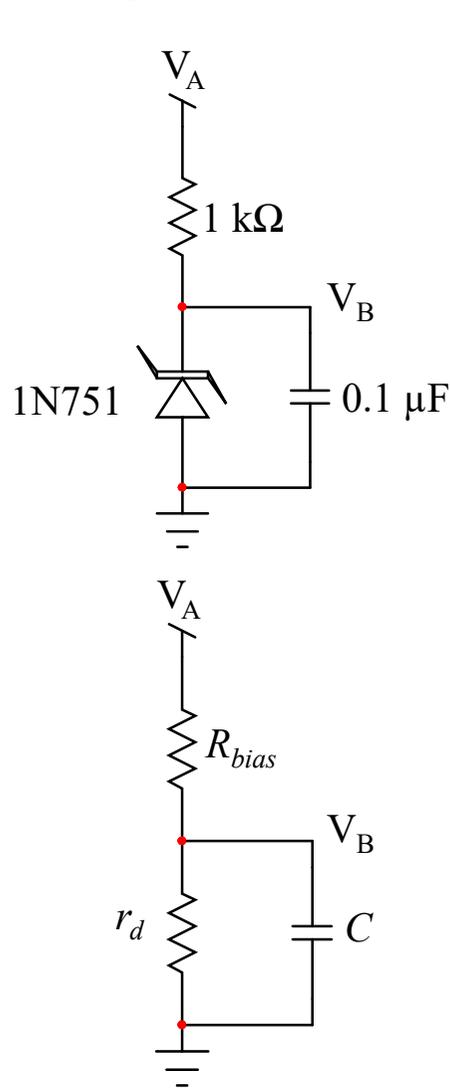
- Dynamic resistance r_d changes as bias conditions move



$$H(s) = \frac{V_B(s)}{V_A(s)} = \frac{r_d}{r_d + R_{bias}} \frac{1}{1 + s(r_d \parallel R_{bias})C}$$





The Dc Bias Affects the Resistor Drop

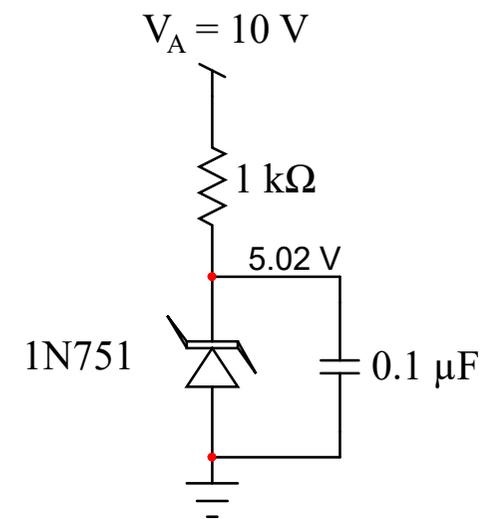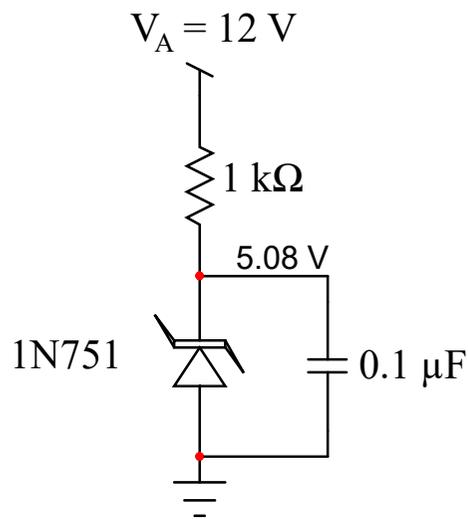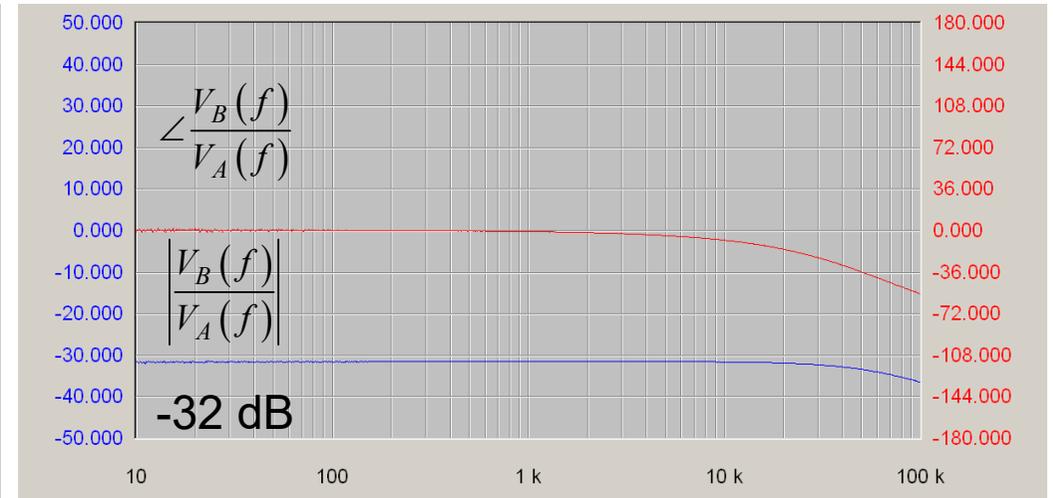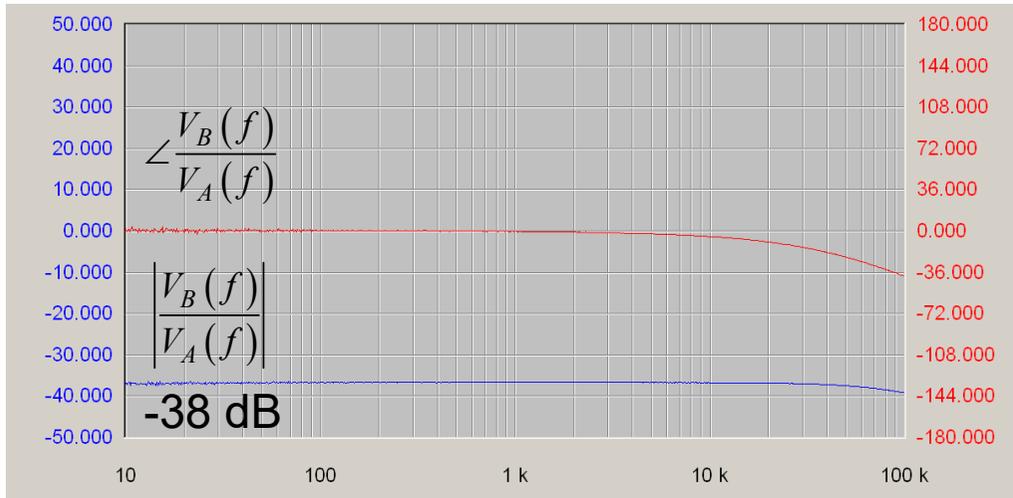- Attenuation degrades as dc bias reduces





Decoupling Helps at High Frequency

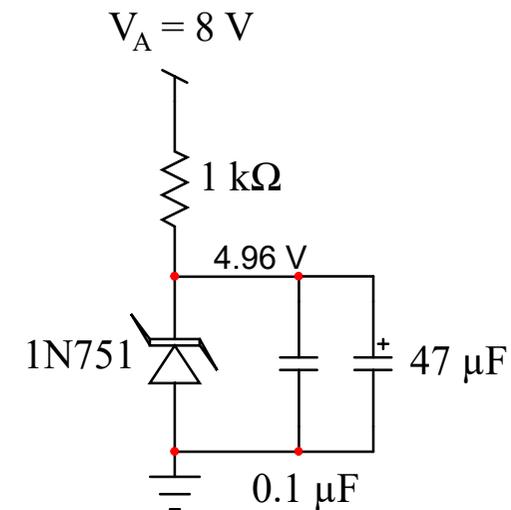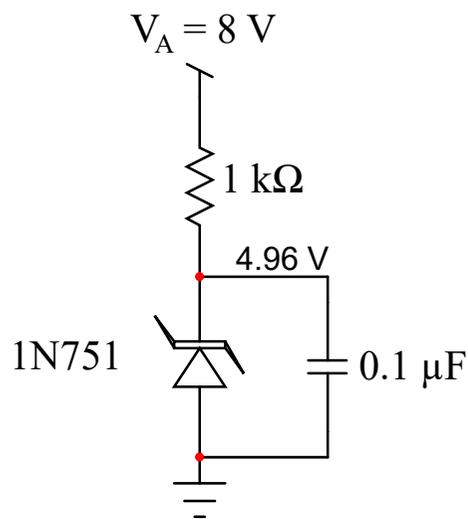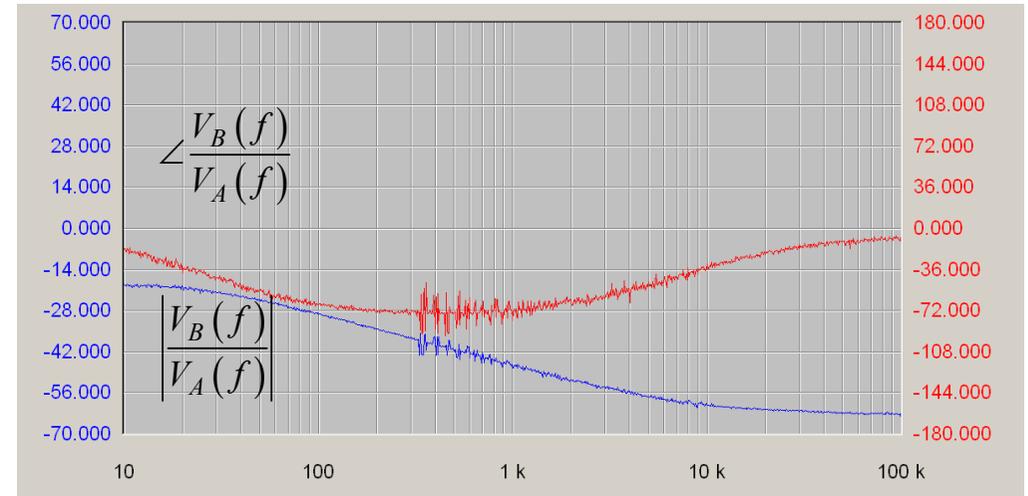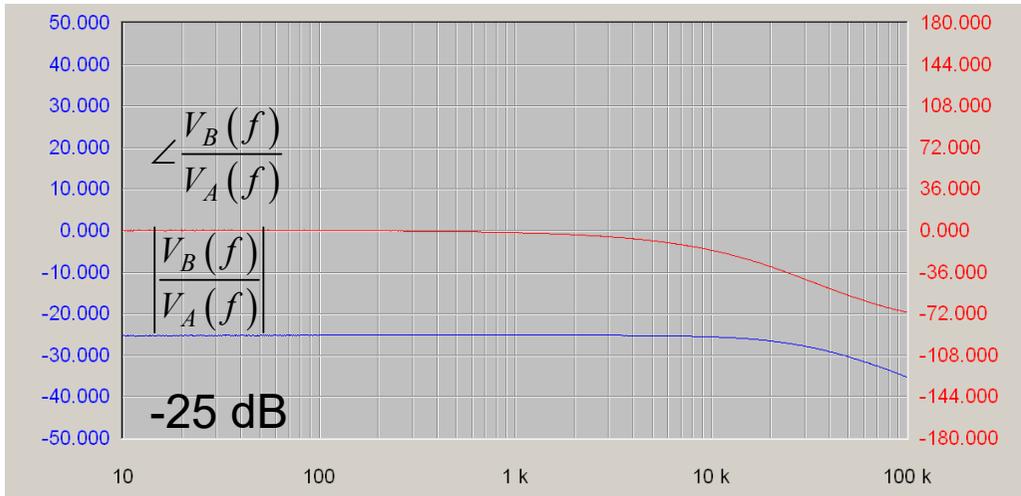- A larger capacitor helps but not enough at low frequency



Calling an Active Zener Diode



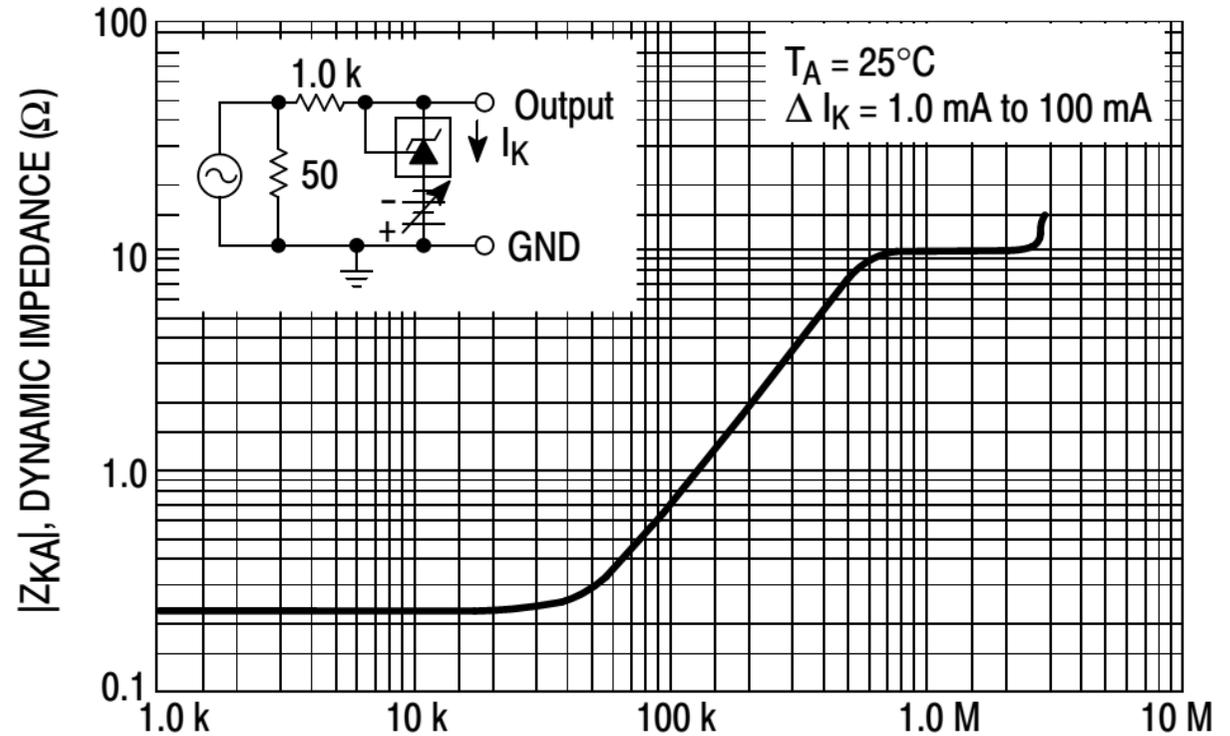
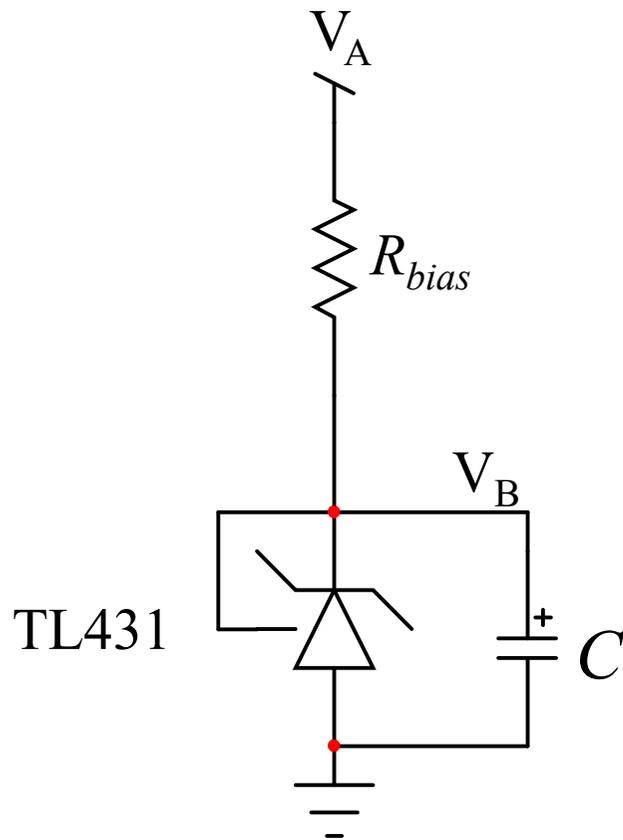
- ❑ Why not using a programmable Zener diode?



- ❑ The TL431 exhibits an excellent dynamic impedance





Dc-Bias Changes with the Active Zener

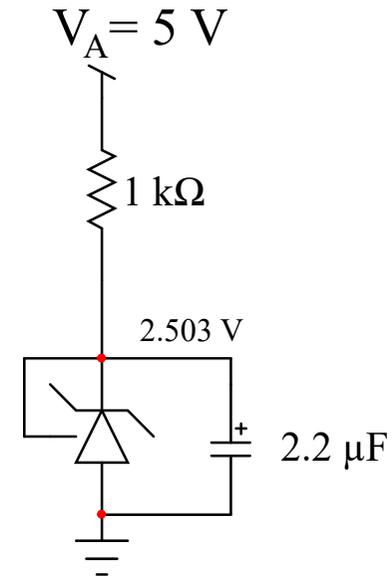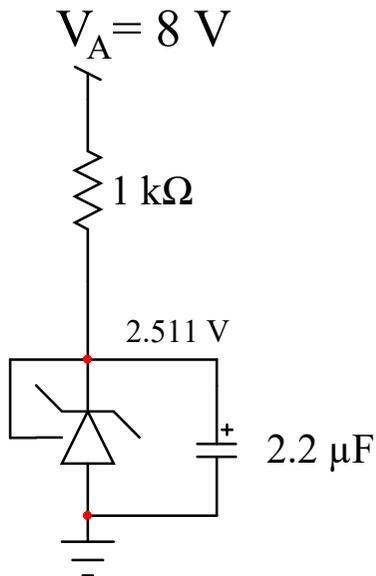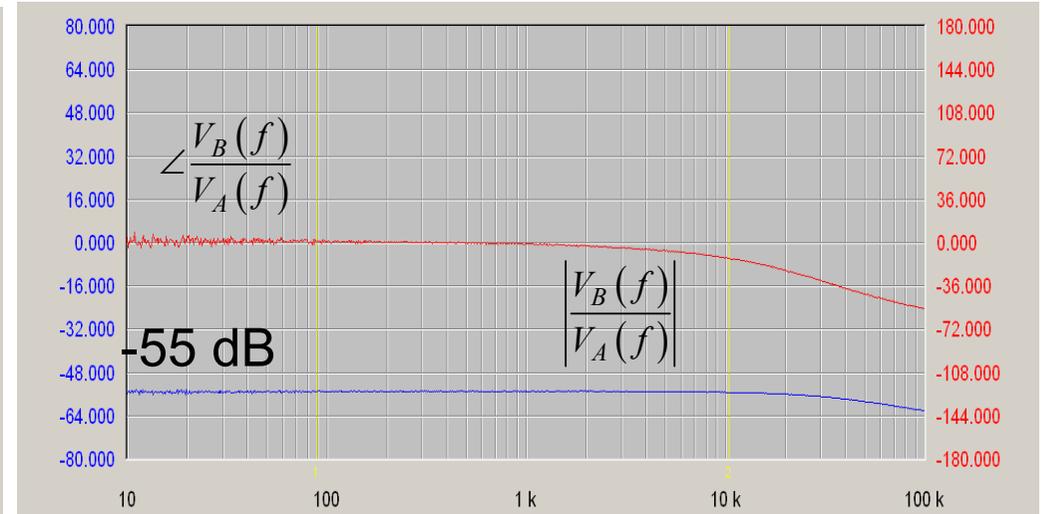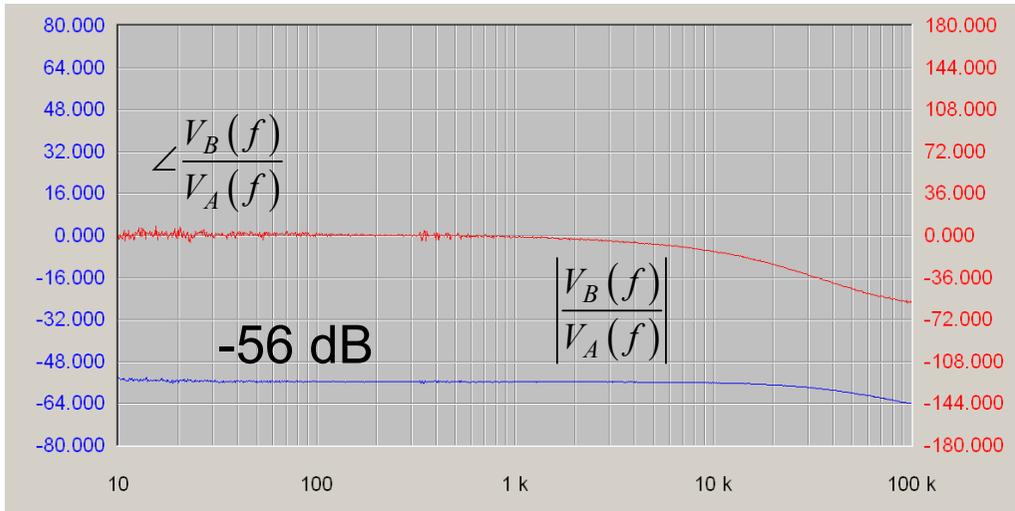- The change in dc bias is not that dramatic with TL431







Watch Out for the Bias Resistor Selection

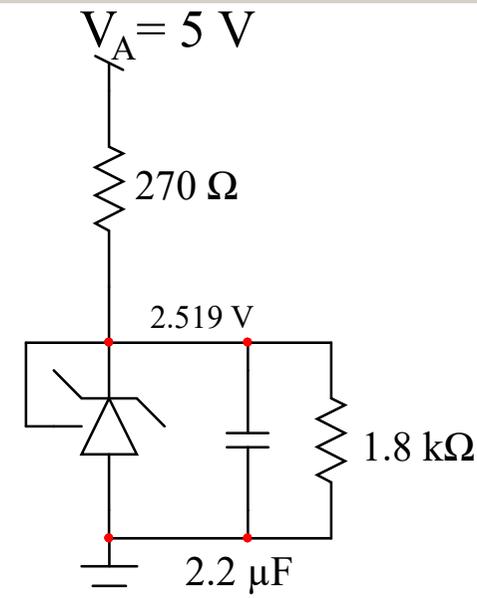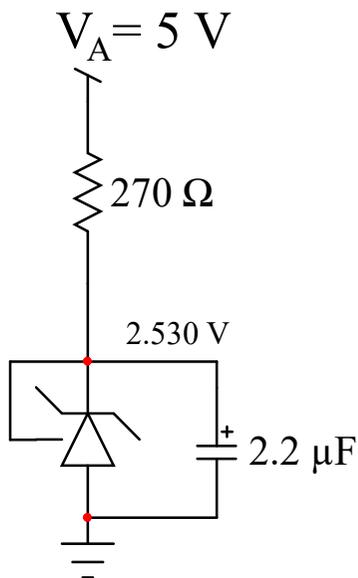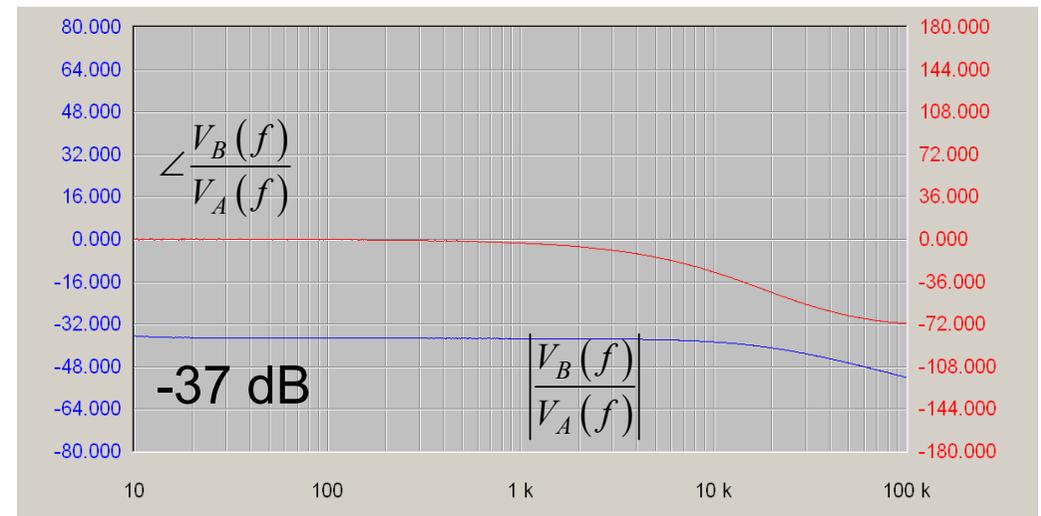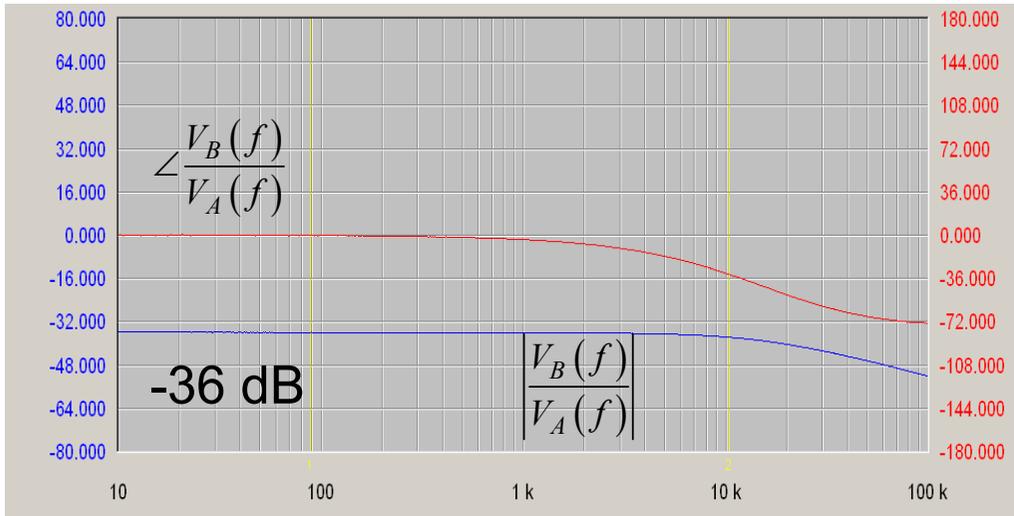- ❑ Reducing the dropping resistor degrades rejection ratio






A Bipolar Also Brings Isolation

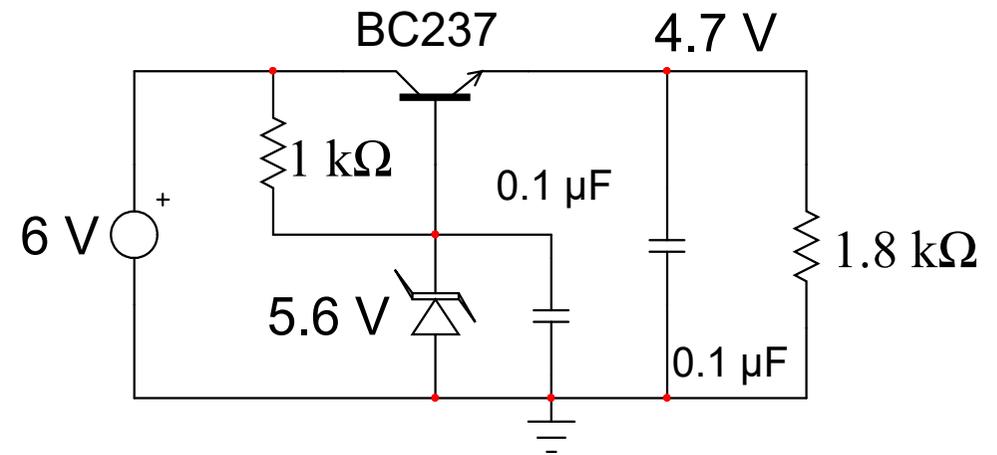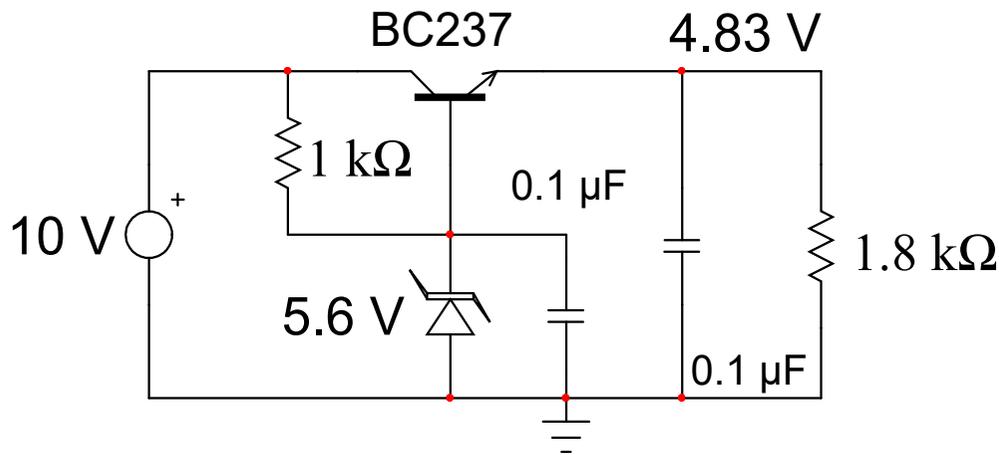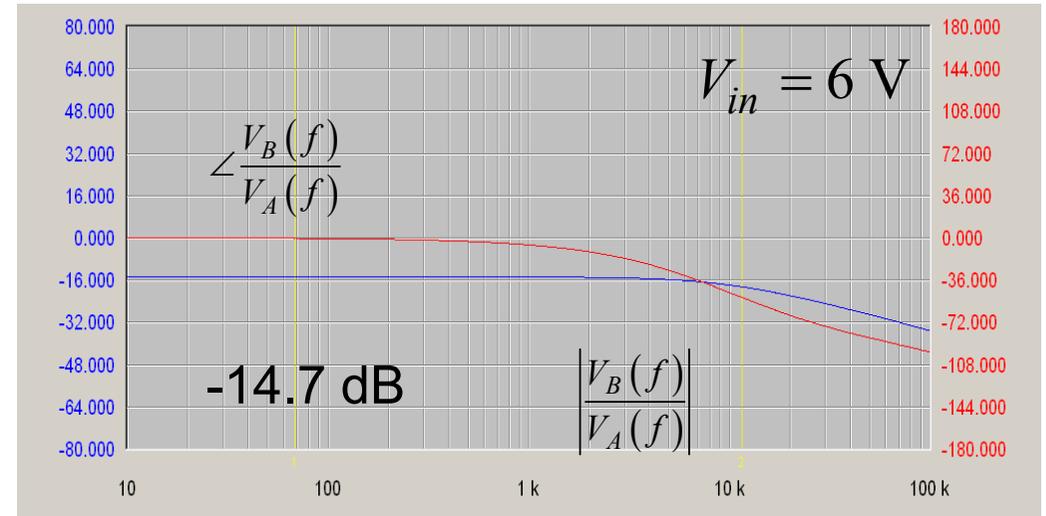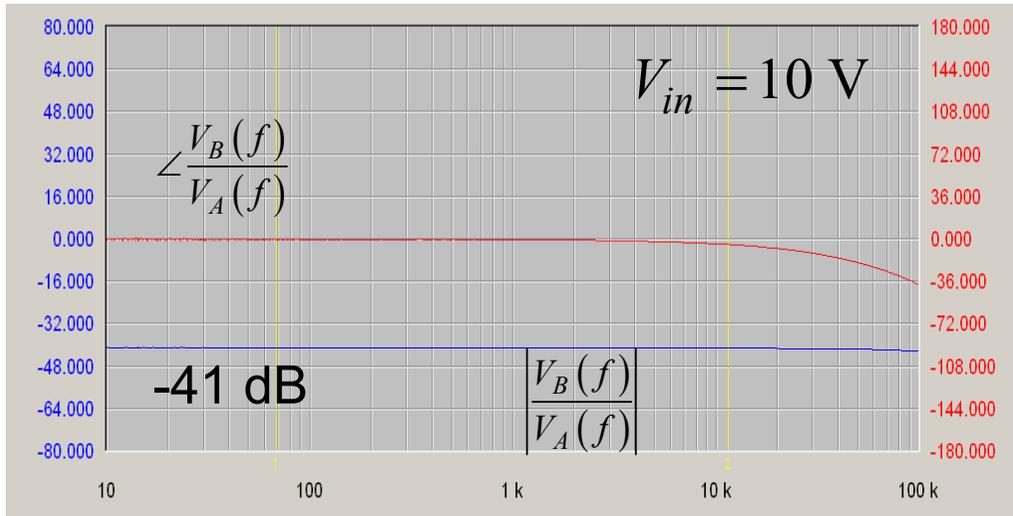- A series transistor is slightly better but sensitive to V_{in}



Regulators Can Also Do the Job

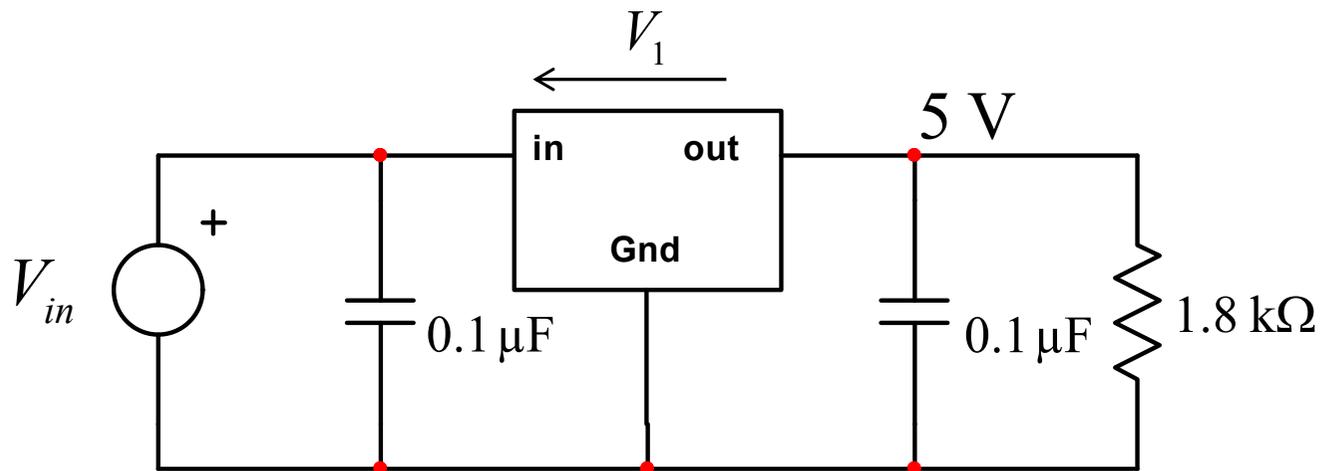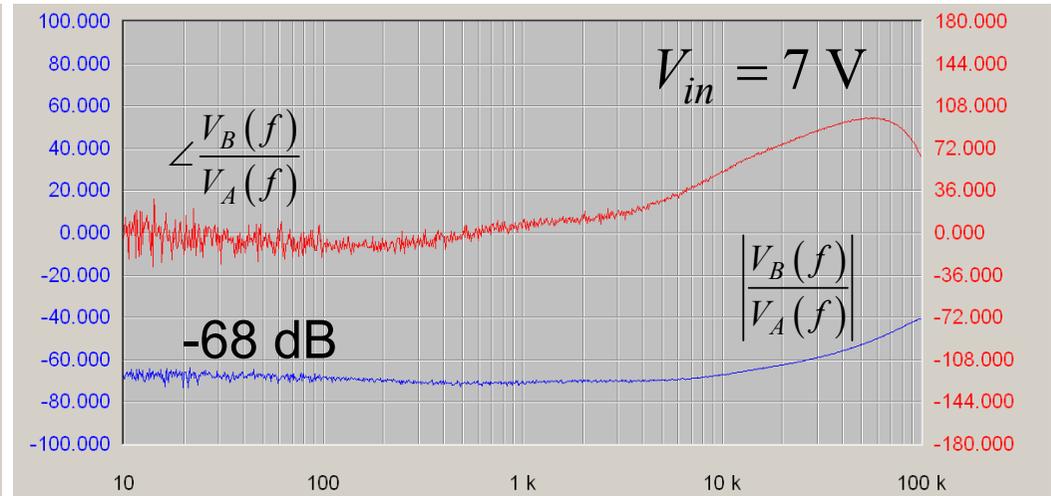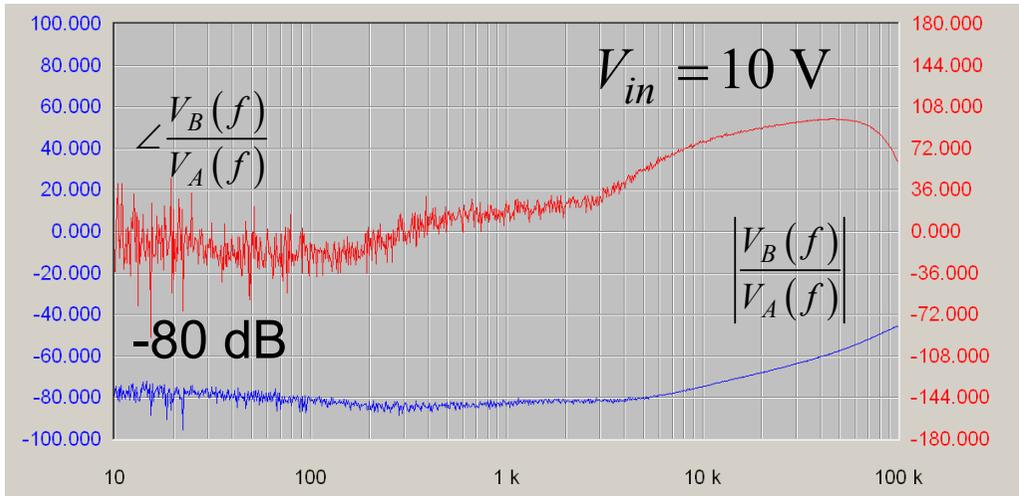- ❑ Good rejection from a 78L05. Expect poor start-up behavior





MC78L05



- ❑ Rejection depends on regulator dropout voltage V_1

Best Combination

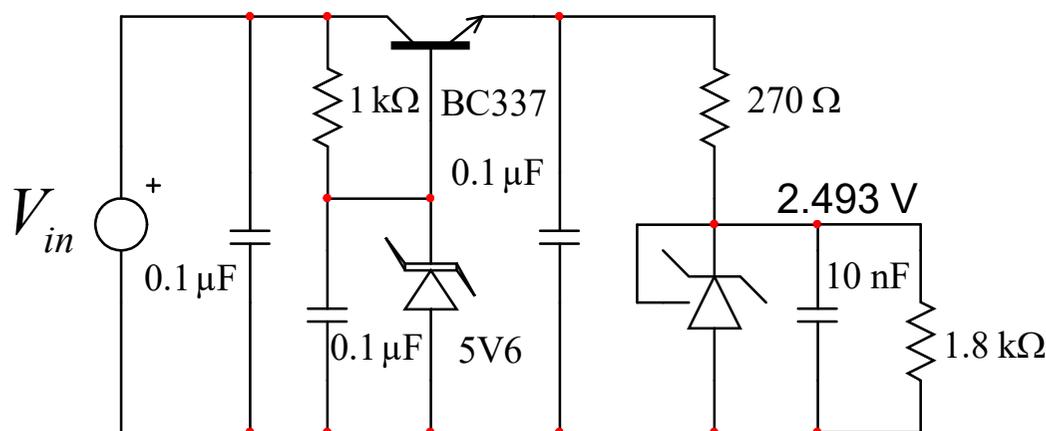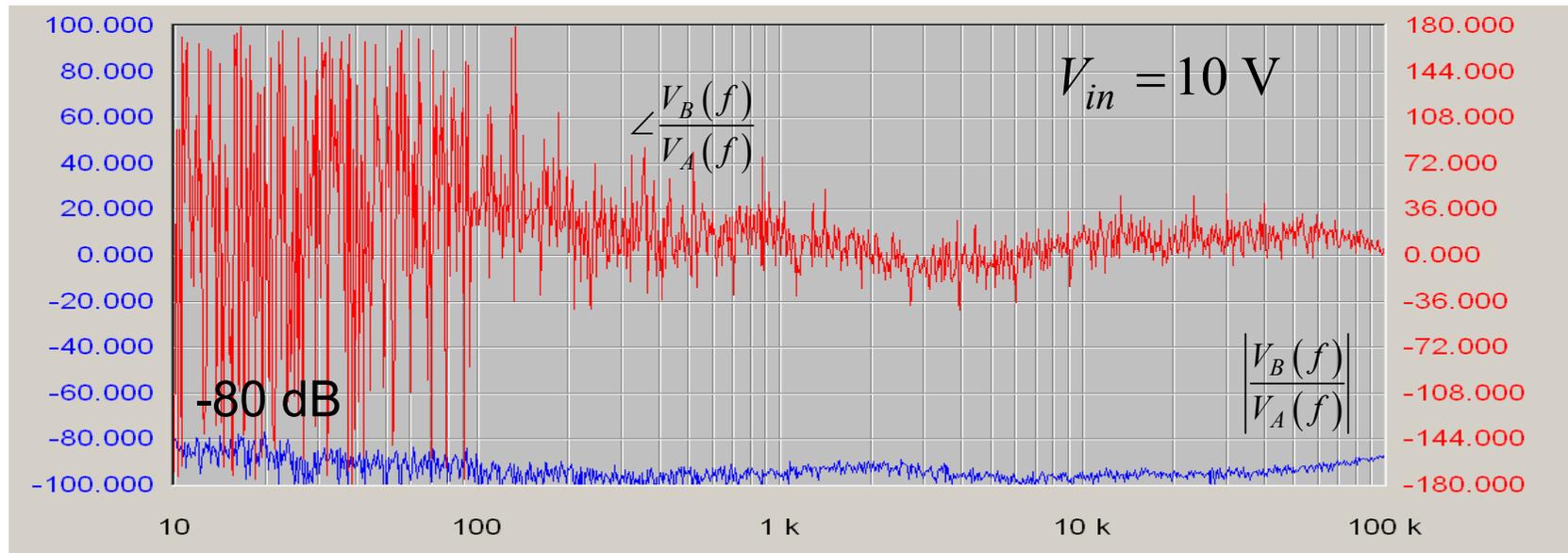
- The strongest rejection is obtained by cascading stages



Low V_{out} is ok
with op amp and
LED connection


Practical Implementation

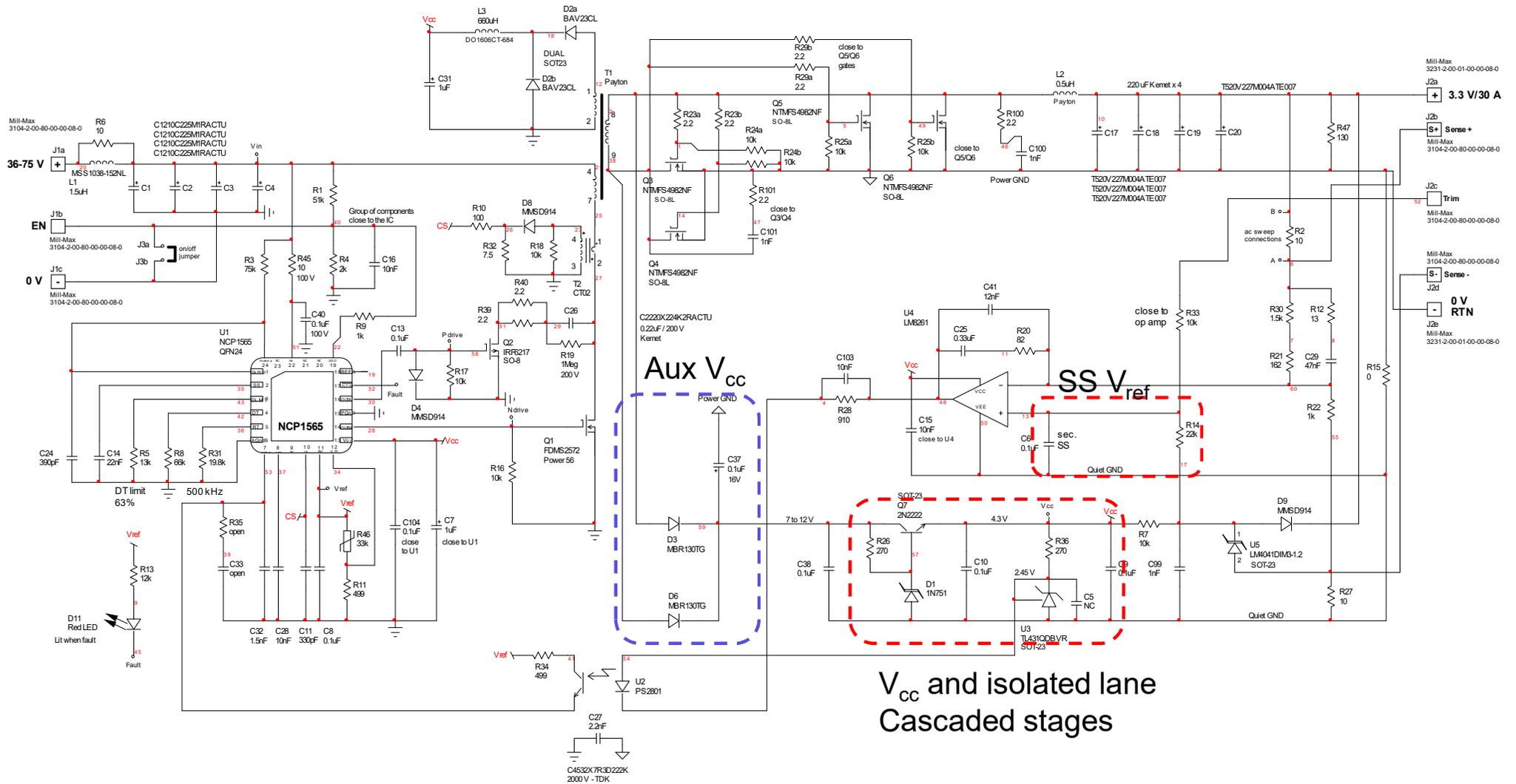□ Stabilizing a 3.3-V/20-A Active Clamp Forward converter



Check the Compensated Loop Response

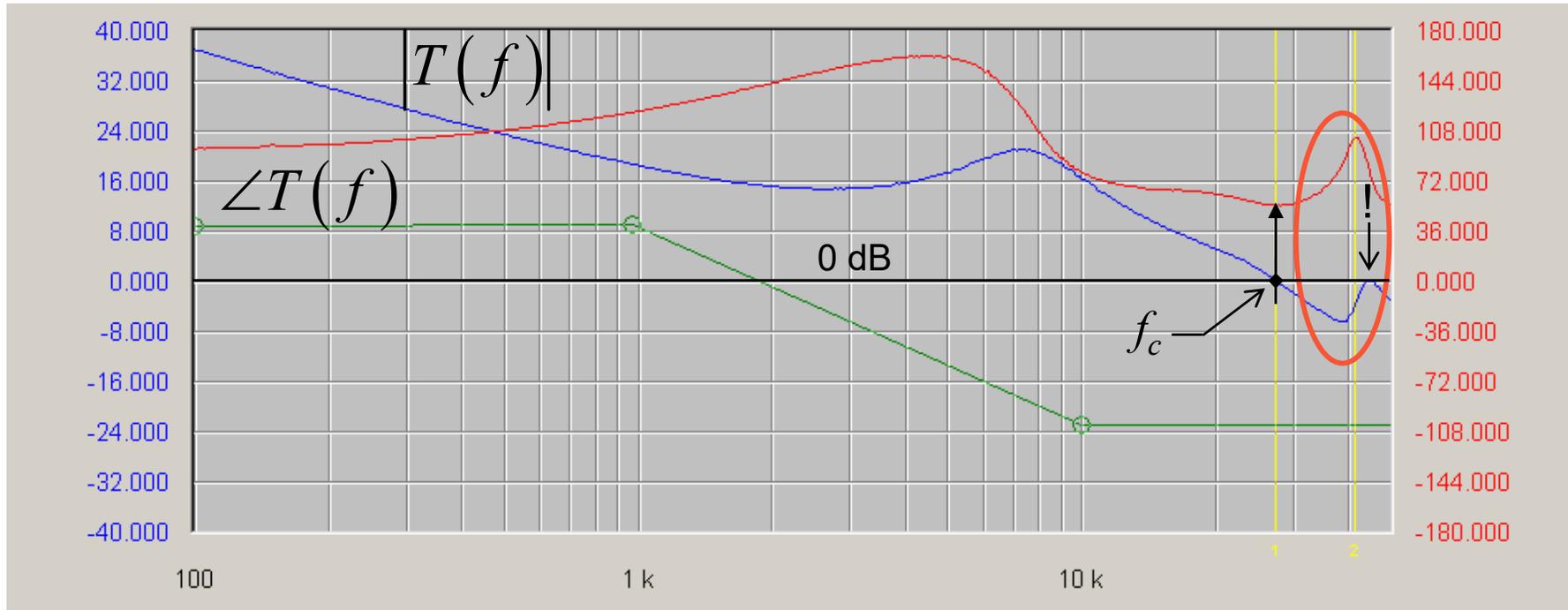- Open-loop Bode plot shows good phase margin at 27-kHz f_c




$V_{in} = 36 \text{ V}$, 110-m Ω constant-resistance load

- Resonance in the upper spectrum is linked to the EMI filter

➔ Apply damping



Damping Filter Helps Removing the Glitch

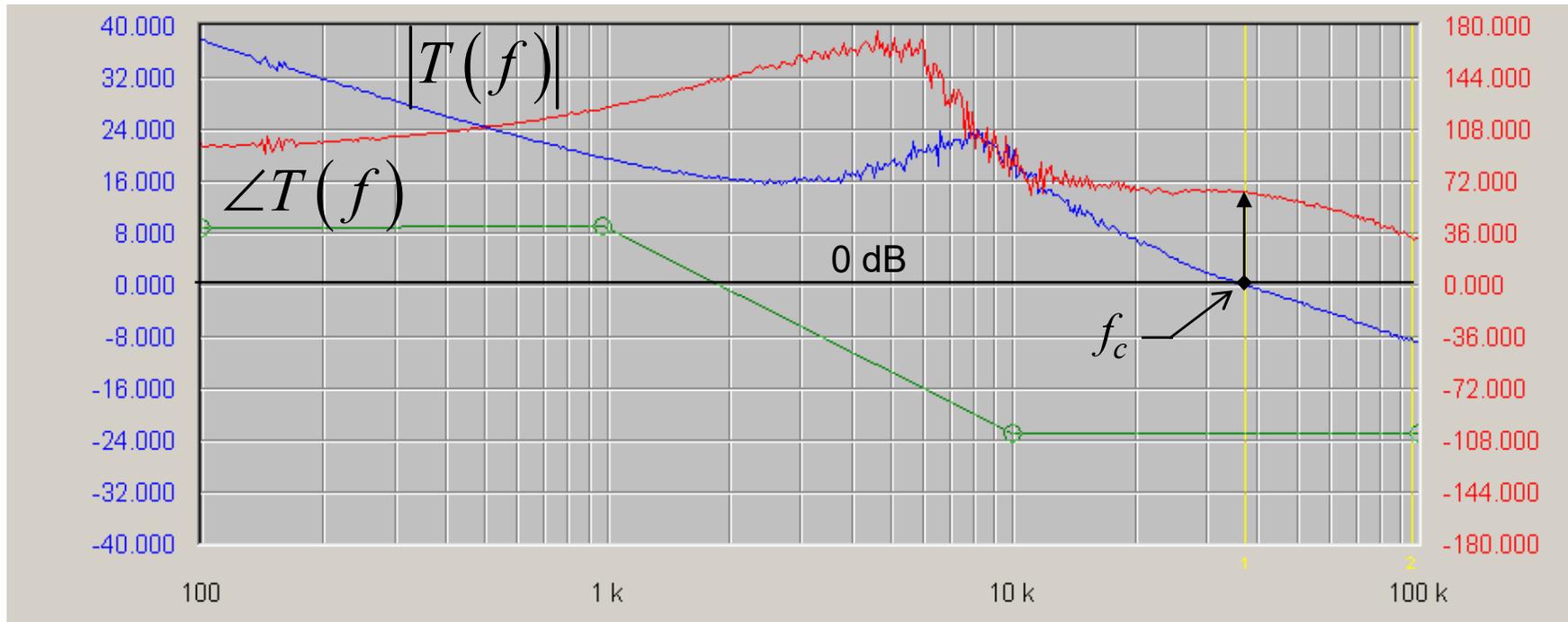- Damping removes glitches and improves f_c to 35 kHz



$V_{in} = 36 \text{ V}$, 110-m Ω constant-resistance load

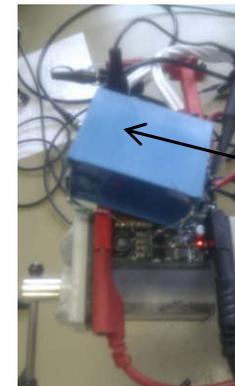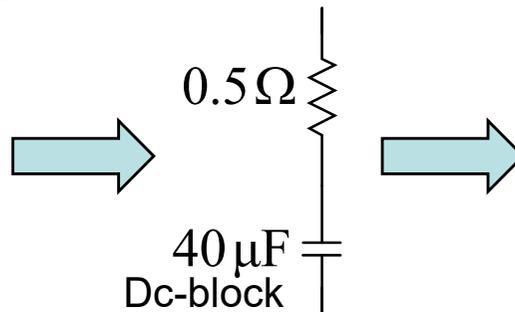
$$R_{damp} := R_{in} \cdot \frac{L_1 + C_{tot} \cdot r_C \cdot r_L - \frac{r_L}{\omega_0}}{-2 \cdot R_{in} \cdot C_{tot} \cdot r_L + \frac{R_{in}}{\omega_0} + L_1 + C_{tot} \cdot r_L \cdot r_C - \frac{r_C}{\omega_0}} = 0.422 \Omega$$



40 μF
(couldn't find bigger!)

Comparing Filter Effects on Loop Gains

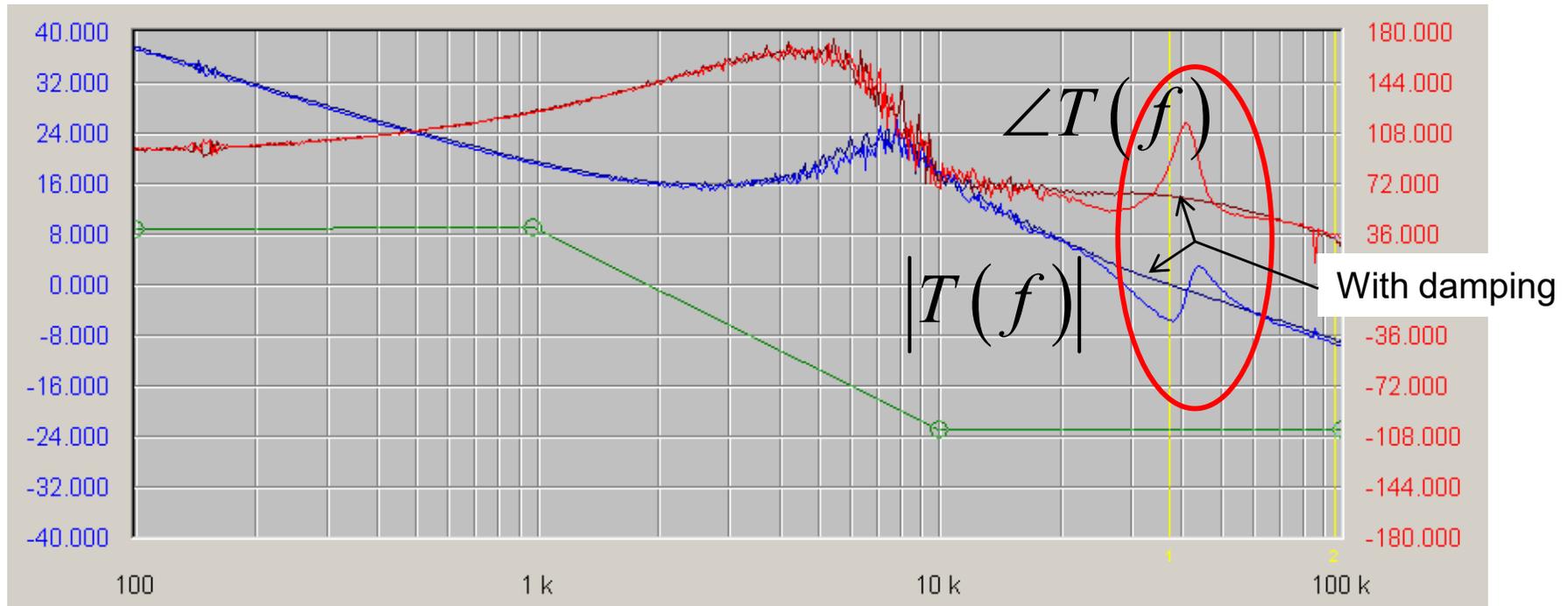- EMI filter resonance degrades open-loop response




- Damping means increased losses per cycles

- An electrolytic cap. features an ESR






Naturally lossy cap.

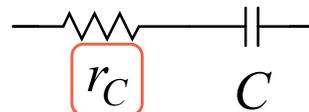


Run Transient Tests

- Final test, run start-up sequences and transient steps

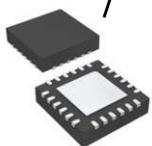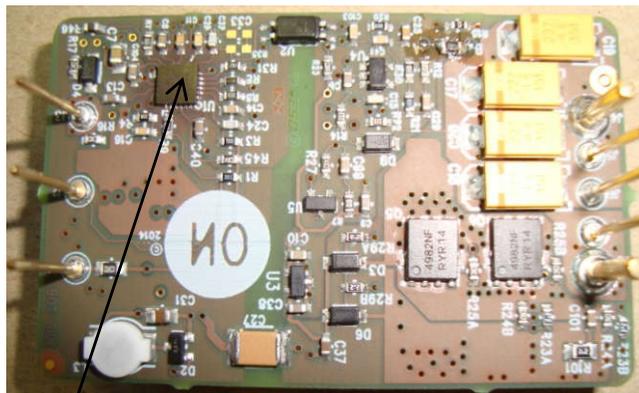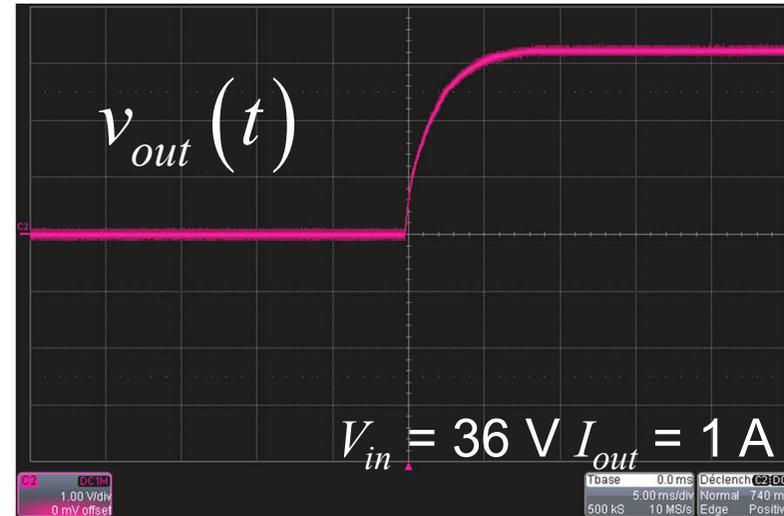

NCP1565

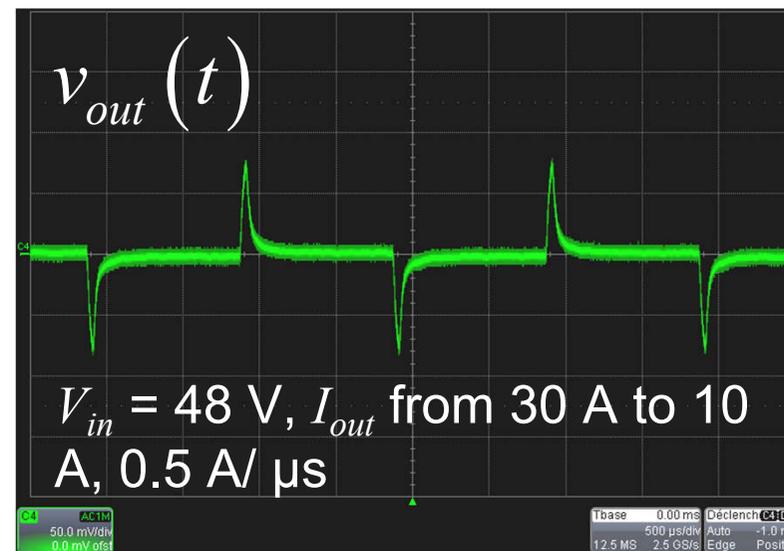




Course Agenda

- Control System Basics
- Operational Amplifier and Low-Frequency Pole
- Gain-Bandwidth Impact on Phase Boost
- Op Amp Slew Rate Effects in Loop Control
- Start-Up Sequence and Auxiliary Supply
- Characterizing the Optocoupler Pole
- Dealing with the Fast Lane
- Going Around the TL431 Fast Lane**



The TL431 Programmable Zener

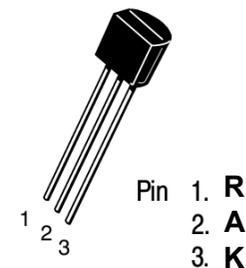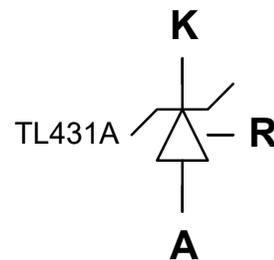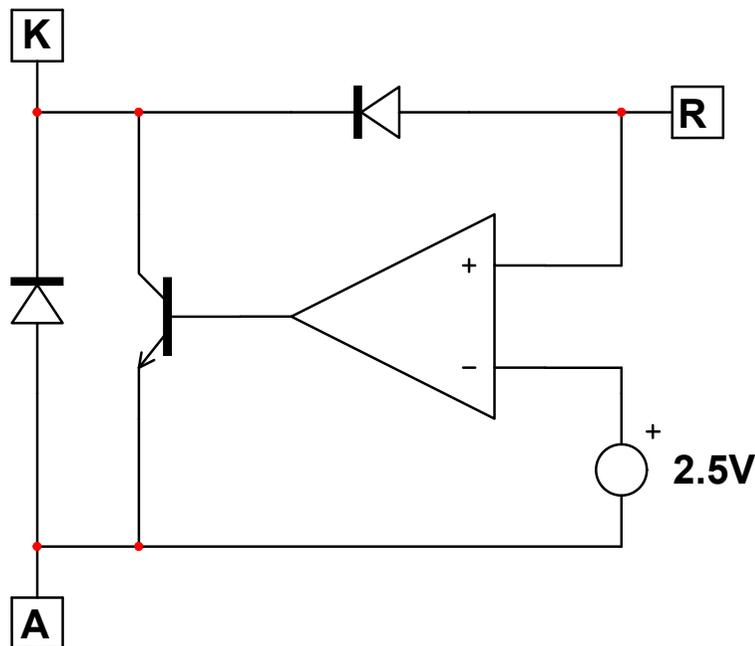
- ❑ The TL431 is the most popular choice in nowadays designs
- ❑ It associates an open-collector op amp and a reference voltage
- ❑ The internal circuitry is self-supplied from the cathode current
- ❑ When the R node exceeds 2.5 V, it sinks current from its cathode



- ❑ The TL431 is a shunt regulator

Two Lanes to Drive the LED

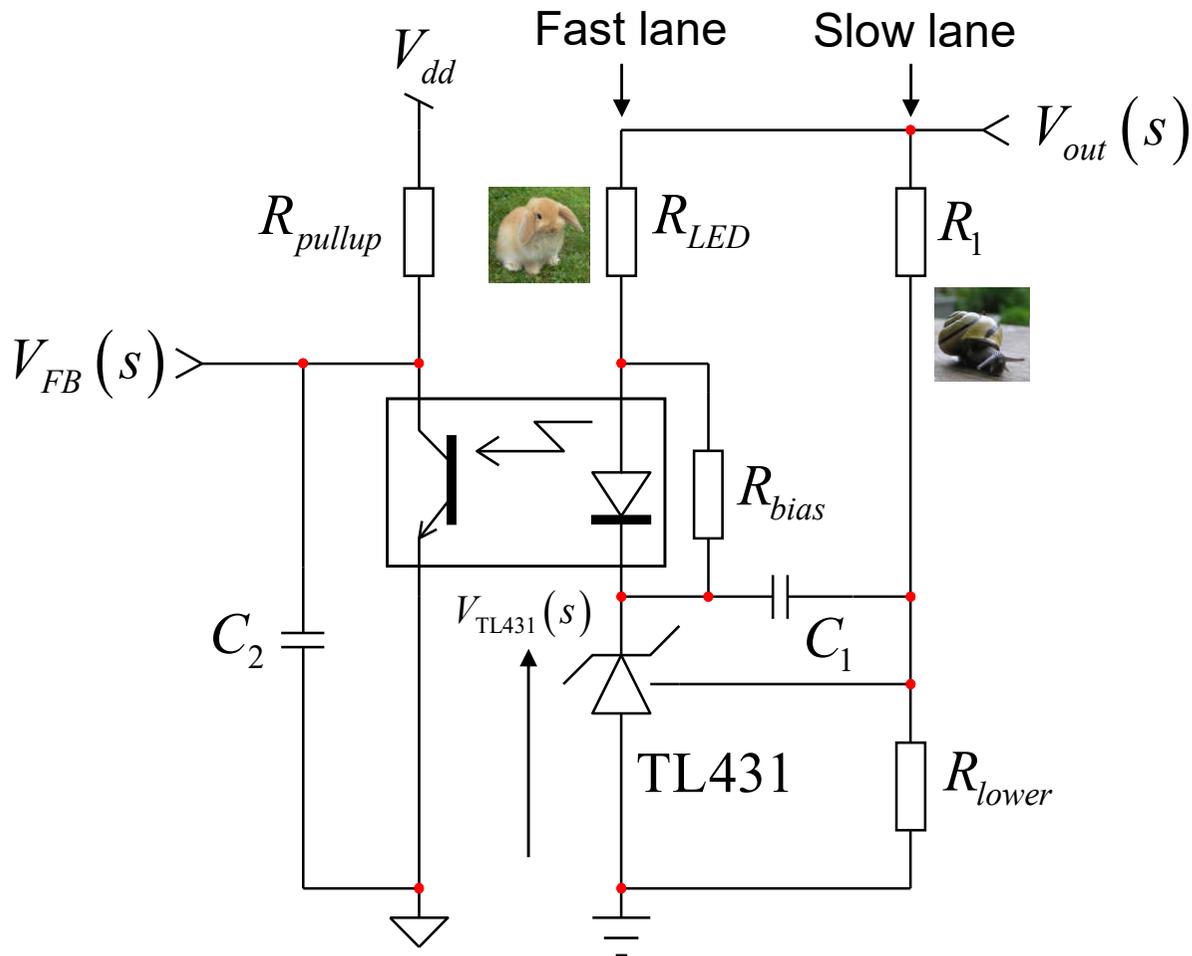- The TL431 lends itself very well to optocoupler control




$$I_{LED}(s) = \frac{V_{out}(s) - V_{TL431}(s)}{R_{LED}}$$

$$I_{LED}(s) = \underbrace{\frac{V_{out}(s)}{R_{LED}}}_{\text{Fast lane}} - \underbrace{\frac{V_{TL431}(s)}{R_{LED}}}_{\text{Slow lane}}$$

- R_{LED} connected to V_{out} offers a direct path to the LED: fast lane!

Bias Conditions Set an Upper Limit

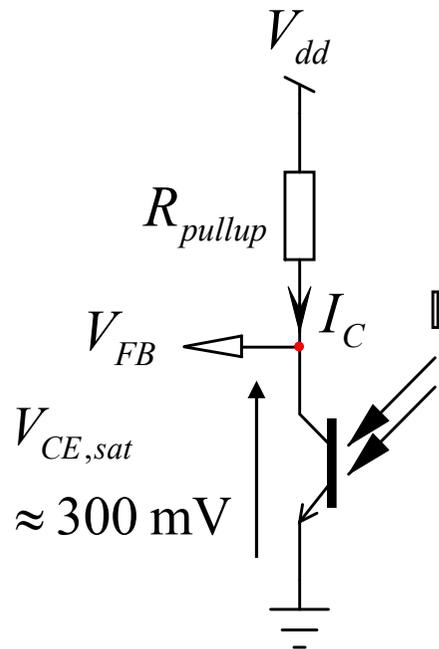
- ❑ R_{LED} cannot exceed a certain value because of bias limits
- ❑ V_{FB} must swing between $V_{CE,sat}$ and V_{dd}



$$I_{C,max} = \frac{V_{cc} - V_{CE,sat}}{R_{pullup}}$$

$$I_{1,max} = \frac{V_{dd} - V_{CE,sat}}{R_{pullup} CTR_{min}} + I_{bias}$$

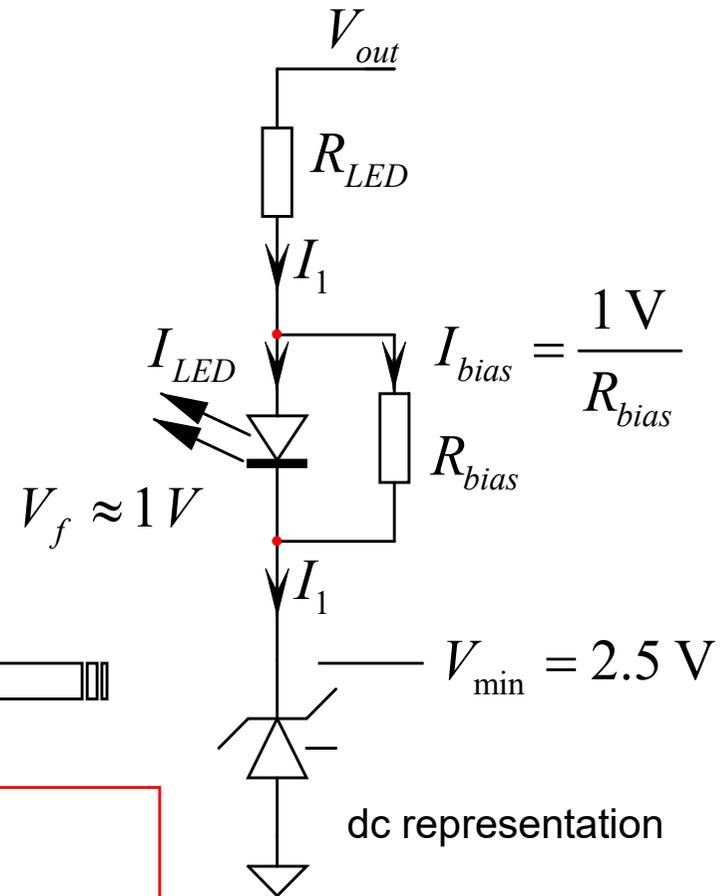
$$I_{1,max} = \frac{V_{out} - V_f - V_{TL431,min}}{R_{LED}}$$



$$R_{LED,max} = \frac{V_{out} - V_f - V_{TL431,min}}{V_{dd} - V_{CE,sat} + I_{bias} CTR_{min}} R_{pullup} CTR_{min}$$

The Gain is Affected by Bias Limits

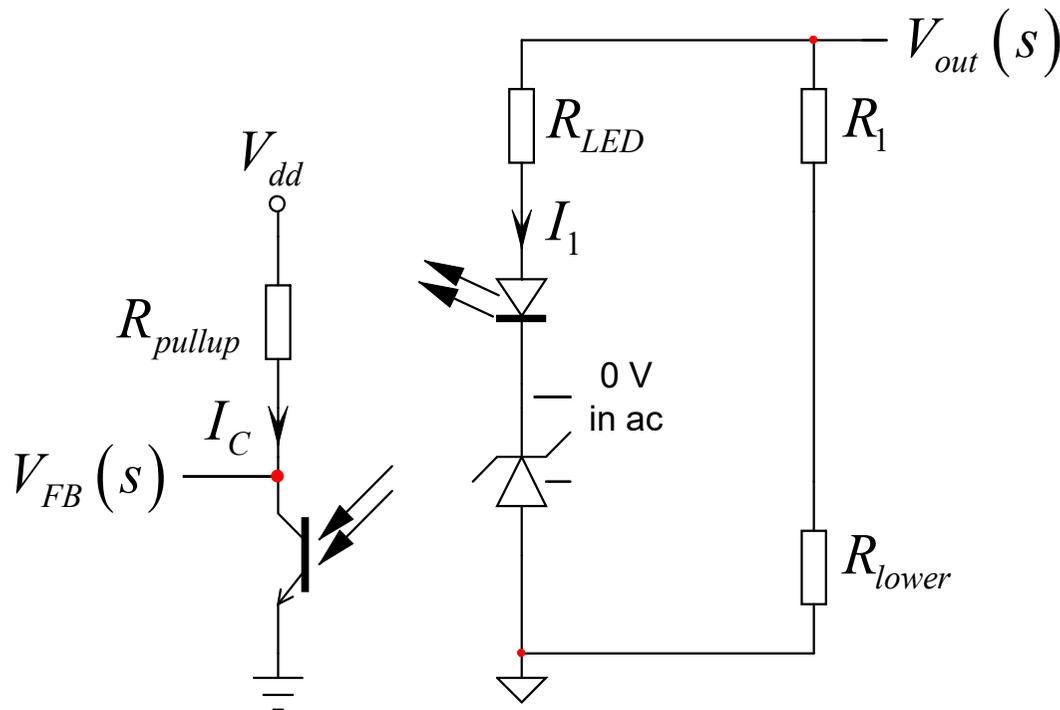- ❑ At high frequencies, the TL431 ac output is zero, C_1 is a short-circuit
- ❑ R_{LED} alone fixes the fast-lane gain



$$V_{FB}(s) = -CTR \cdot R_{pullup} \cdot I_1$$

$$I_1 = \frac{V_{out}(s)}{R_{LED}}$$

$$\frac{V_{FB}(s)}{V_{out}(s)} = -CTR \frac{R_{pullup}}{R_{LED}}$$

- ❑ R_{LED} must also leave headroom to bias the TL431: upper limit!

A Quick Design Example

□ Assume the following design:

$$V_{out} = 5 \text{ V}$$

$$V_f = 1 \text{ V}$$

$$V_{TL431, \min} = 2.5 \text{ V}$$

$$V_{dd} = 4.8 \text{ V}$$


$$V_{CE, \text{sat}} = 300 \text{ mV}$$

$$I_{bias} = 1 \text{ mA}$$

$$\text{CTR}_{\min} = 0.3$$

$$R_{pullup} = 20 \text{ k}\Omega$$
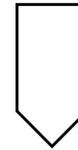
$$R_{LED, \max} \leq \frac{5 - 1 - 2.5}{4.8 - 0.3 + 1\text{m} \times 0.3 \times 20\text{k}} \times 20\text{k} \times 0.3$$



$$R_{LED, \max} \leq 857 \Omega$$




$$G_0 > \text{CTR} \frac{R_{pullup}}{R_{LED}} > 0.3 \frac{20}{0.857} > 7 \text{ or } \approx 17 \text{ dB}$$

□ In designs where R_{LED} fixes the gain, G_0 cannot be below 17 dB

⇒ You cannot “amplify” by less than 17 dB



Crossover Frequency Choices are Limited

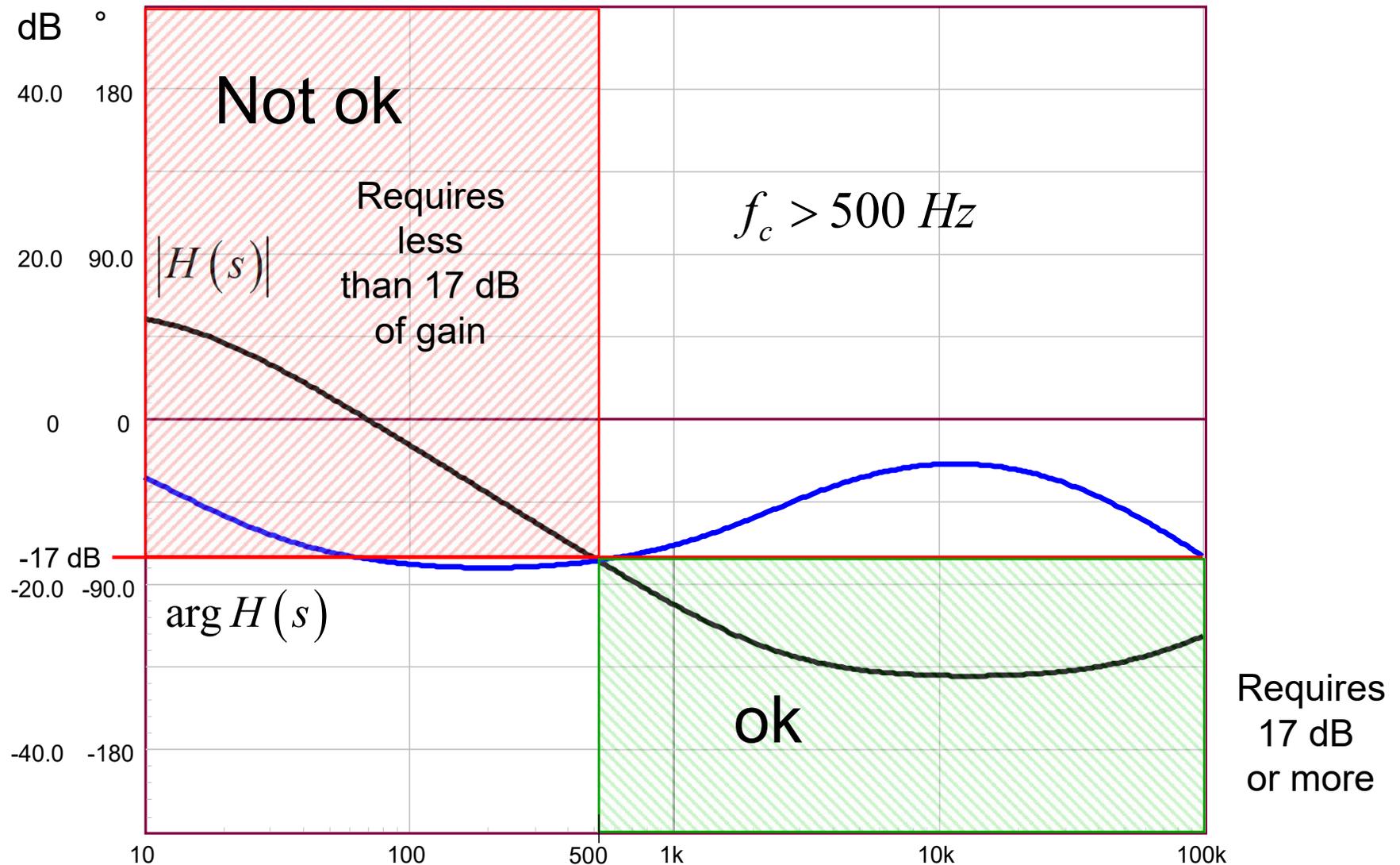- ❑ You must identify areas where crossover is possible



Going Around the Bias Limit

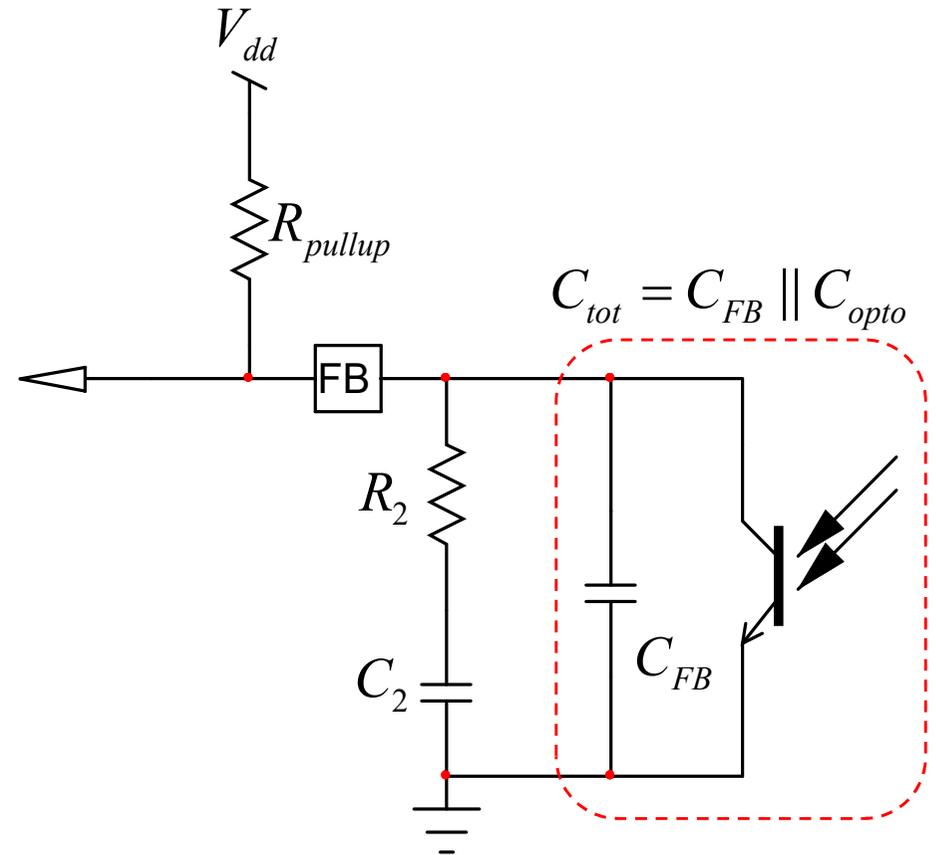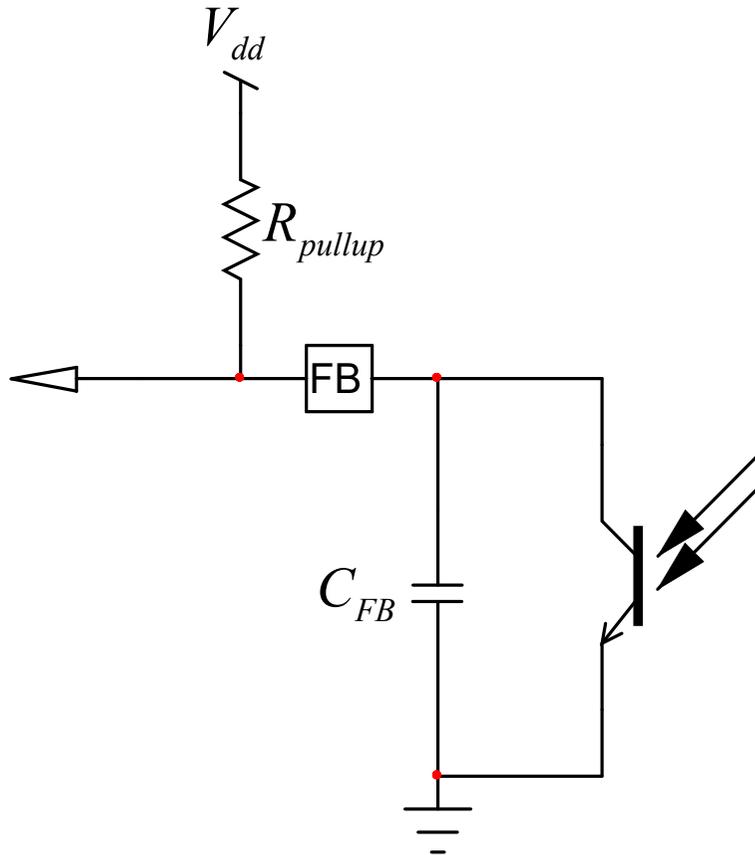- ❑ The pull-up resistor is internal and cannot be altered
- ❑ One way to modify the mid-band gain is by adding an RC circuit




- ❑ The capacitance at the FB pin involves the optocoupler parasitics

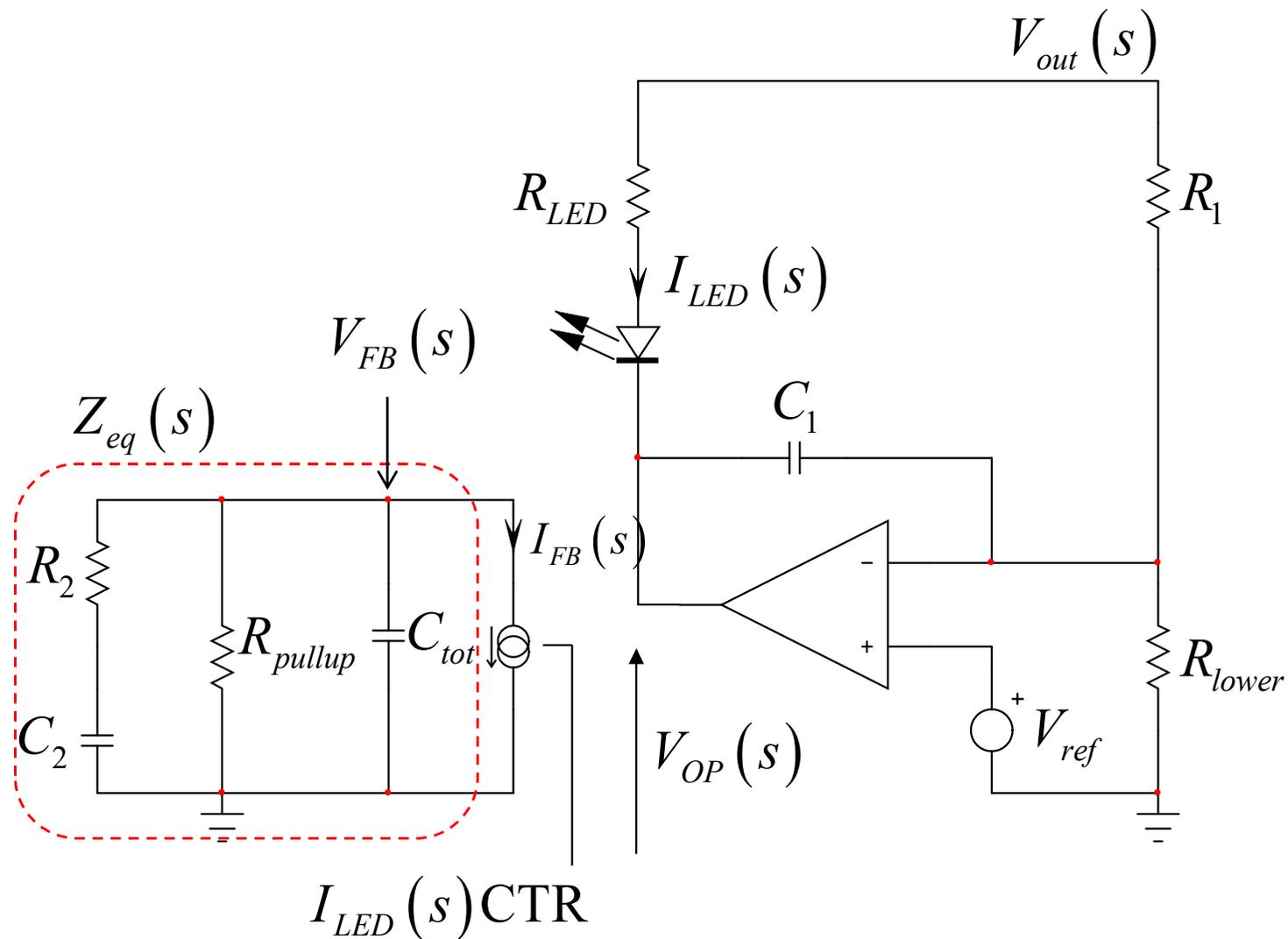C. Richardson, <http://www.powerguru.org/a-simple-low-cost-technique-for-compensating-isolated-converters/>

An Equivalent Small-Signal Model

- The new small-signal circuit includes the extra R_2C_2 circuit



Define the LED Current

- The LED current can be defined by

$$I_{LED}(s) = \frac{V_{out}(s) - V_{op}(s)}{R_{LED}} \quad \leftarrow \quad V_{op}(s) = -\frac{V_{out}(s)}{sR_1C_1}$$

- Rearrange and factor

$$I_{LED}(s) = \frac{V_{out}(s)}{R_{LED}} \left(1 + \frac{1}{sR_1C_1} \right) = \frac{V_{out}(s)}{R_{LED}} \left(\frac{1 + sR_1C_1}{sR_1C_1} \right) = \frac{V_{out}(s)}{R_{LED}} \frac{1 + \frac{s}{s_{z_1}}}{\frac{s}{s_{po}}}$$

- Rearrange and factor to unveil $V_{FB}(s)$

$$I_{FB}(s) = I_{LED}(s) \text{CTR}$$


$$V_{FB}(s) = -I_{LED}(s) Z_{eq}(s) \text{CTR}$$

$$\omega_{po} = \omega_{z_1} = \frac{1}{R_1C_1}$$



A 2nd-Order Impedance

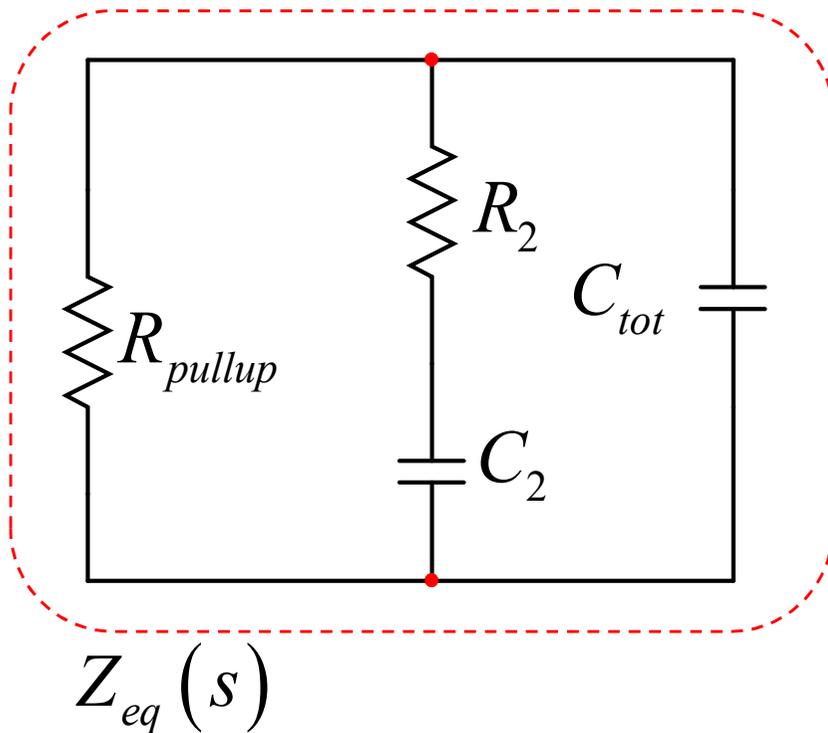- ❑ The equivalent impedance Z_{eq} is a second-order network
- ❑ It's time to call the FACTs!



You apply brute-force analysis...

$$Z_{eq}(s) = \left(R_{pullup} \parallel \frac{1}{sC_{tot}} \right) \parallel \left(R_2 + \frac{1}{sC_2} \right)$$

or use FACTs for a low-entropy result


$$Z_{eq}(s) = R_0 \frac{1 + \frac{s}{z_1}}{1 + a_1s + a_2s^2}$$

- ❑ There are two storage elements, this is a 2nd-order system

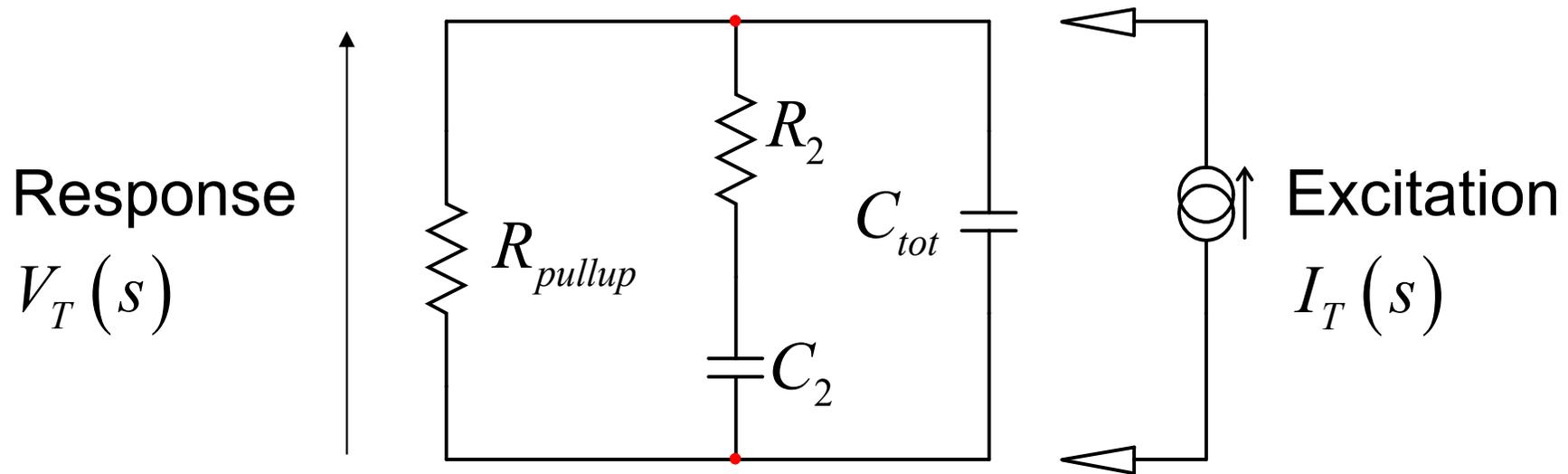V. Vorpérian, "Fast Analytical Techniques for Electrical and Electronic Circuits", Cambridge Press 2004

Identify Stimulus and Response

- ❑ The circuit is driven by a current source, the excitation
- ❑ The voltage is the response




- ❑ The impedance is the ratio of V_T over I_T


$$Z_{eq}(s) = \frac{V_T(s)}{I_T(s)} \quad \begin{array}{l} \longleftarrow \text{response} \\ \longleftarrow \text{stimulus} \end{array}$$

Start by the Circuit Examined in Dc

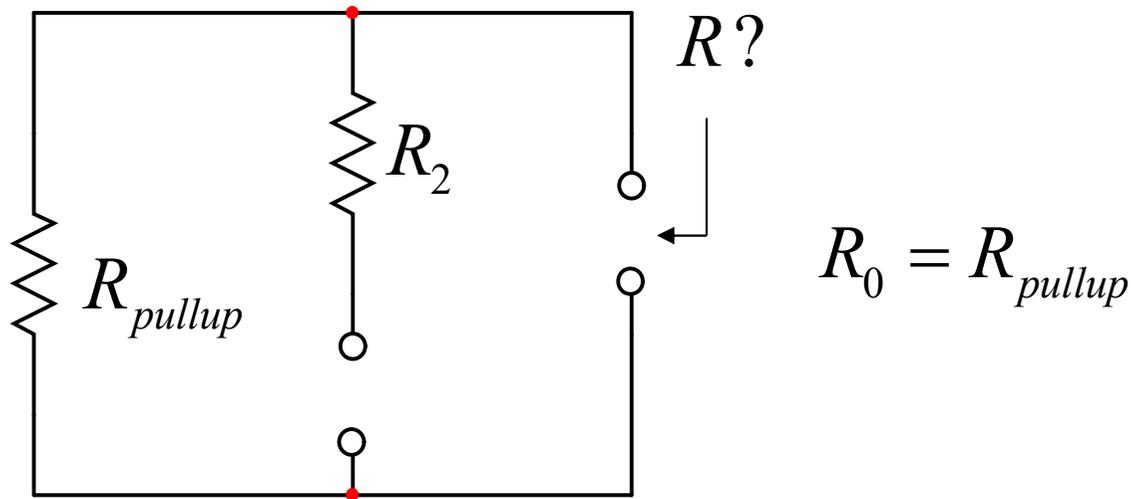- For $s = 0$, open the capacitors and define R_0




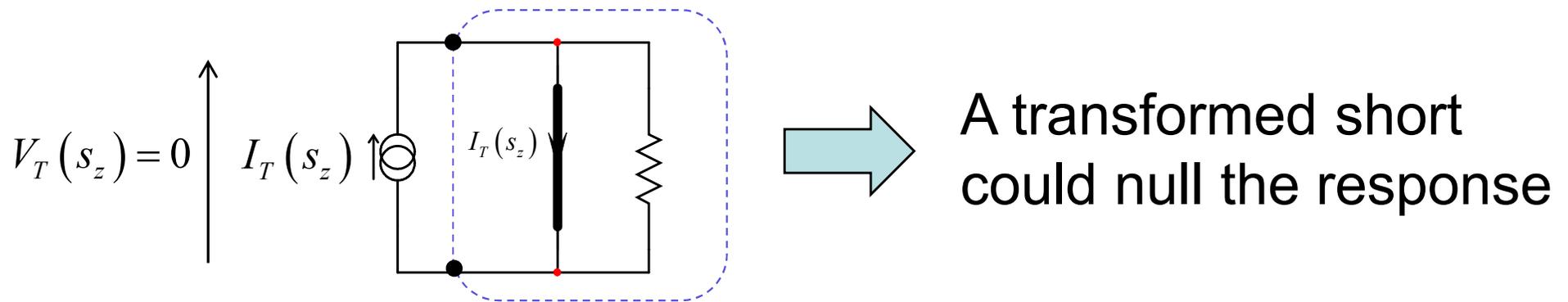- Examine circuit conditions that could lead to $V_{out} = 0$ at $s = s_z$



Examine the Transformed Circuit

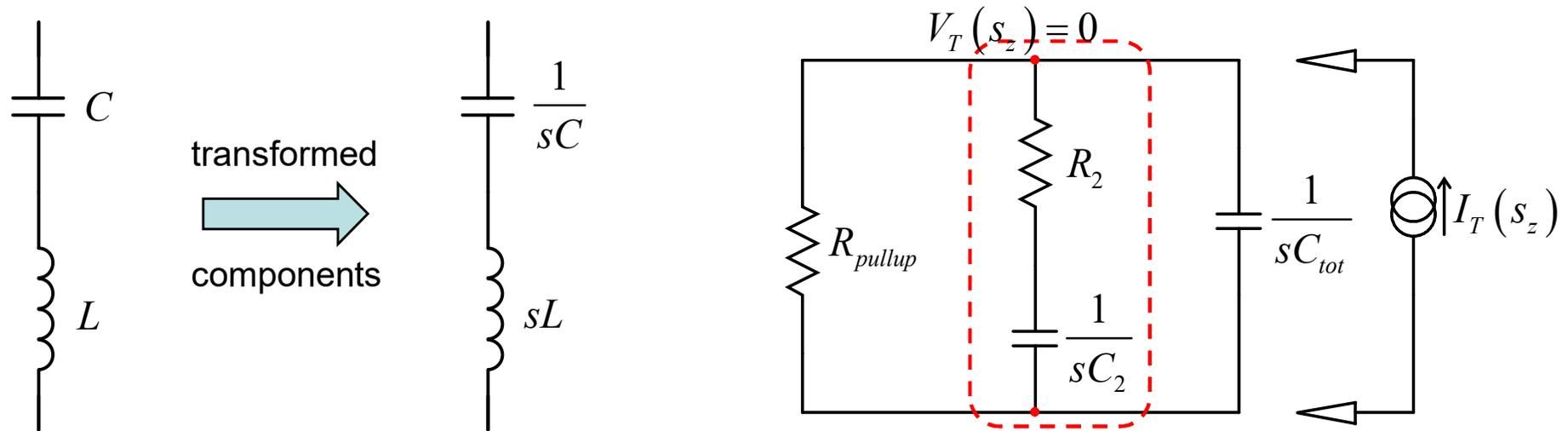- A transformed circuit associates C and L impedances




- A transformed short circuit brings the response to a null

$$R_2 + \frac{1}{sC_2} = \frac{1 + sR_2C_2}{sC_2} = 0 \longrightarrow 1 + sR_2C_2 = 0 \longrightarrow s_{z_2} = -\frac{1}{R_2C_2}$$


$$\implies \omega_{z_2} = \frac{1}{R_2C_2}$$

Calculate Time Constants

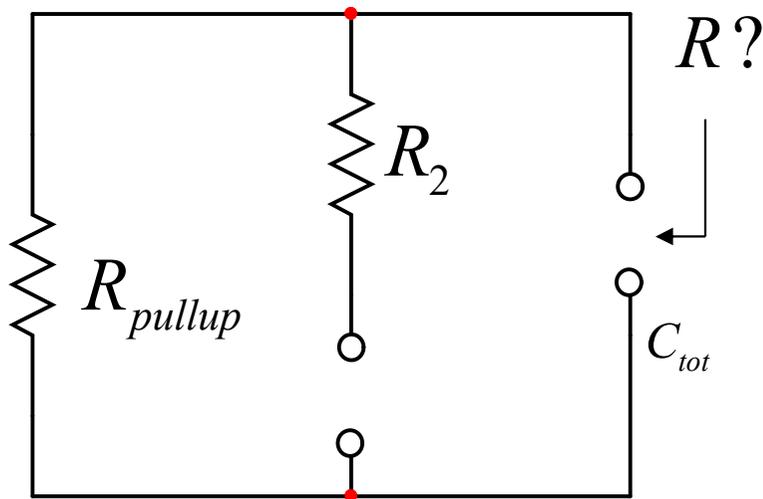- A transformed circuit associates C and L impedances



$$\tau_2 = R_{pullup} C_{tot}$$

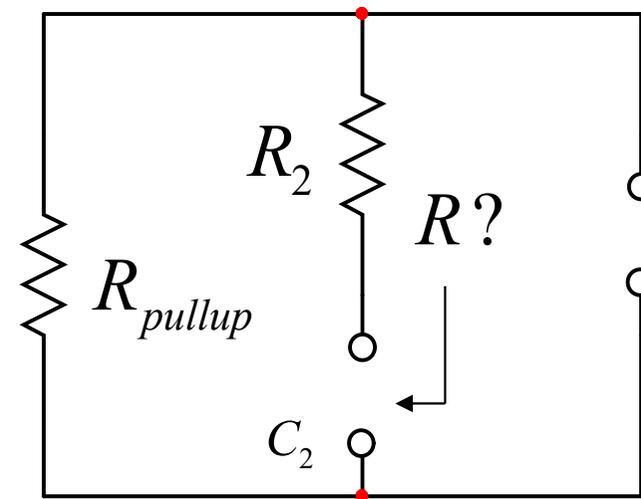

$$\tau_1 = (R_{pullup} + R_2) C_2$$

- The denominator is unitless

$$D(s) = 1 + a_1 s + a_2 s^2 \left. \begin{array}{l} a_1 [s] \\ a_2 [s^2] \end{array} \right\}$$




$$a_1 = \tau_1 + \tau_2$$

$$a_2 = \tau_1 \tau_2 = \tau_2 \tau_1$$

Calculate Higher Order Time Constants

- Set one of the capacitor in its high-frequency state

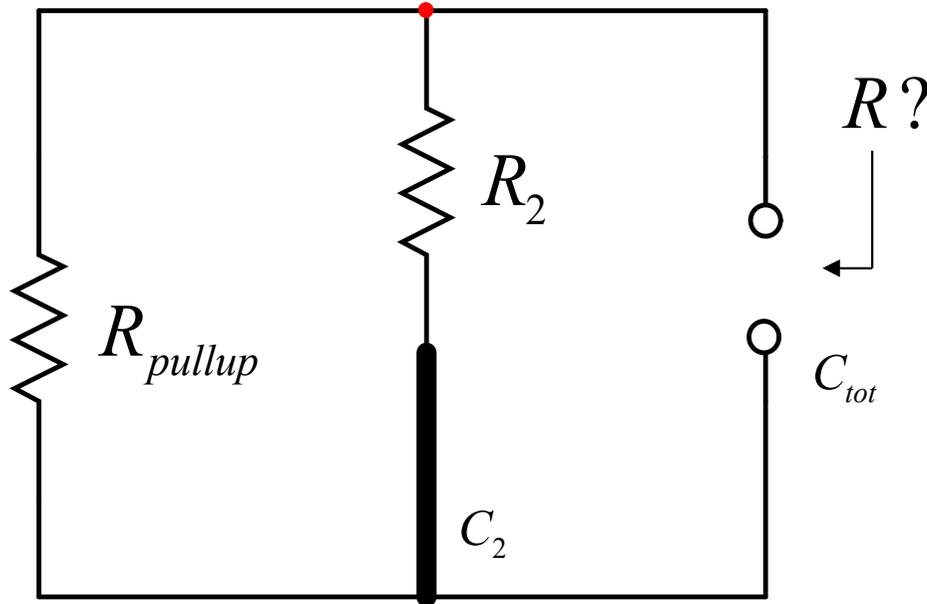τ_2^1 → Put storage element involved in τ_1 in HF
 τ_2 ← Look at driving resistance of element involved in τ_2




$$\tau_2^1 = C_{tot} (R_2 \parallel R_{pullup})$$

$$a_2 = \tau_1 \tau_2^1 = (R_{pullup} + R_2) C_2 (R_2 \parallel R_{pullup}) C_{tot}$$

Calculate Higher Order Time Constants

- Check if the second combination brings a simpler result

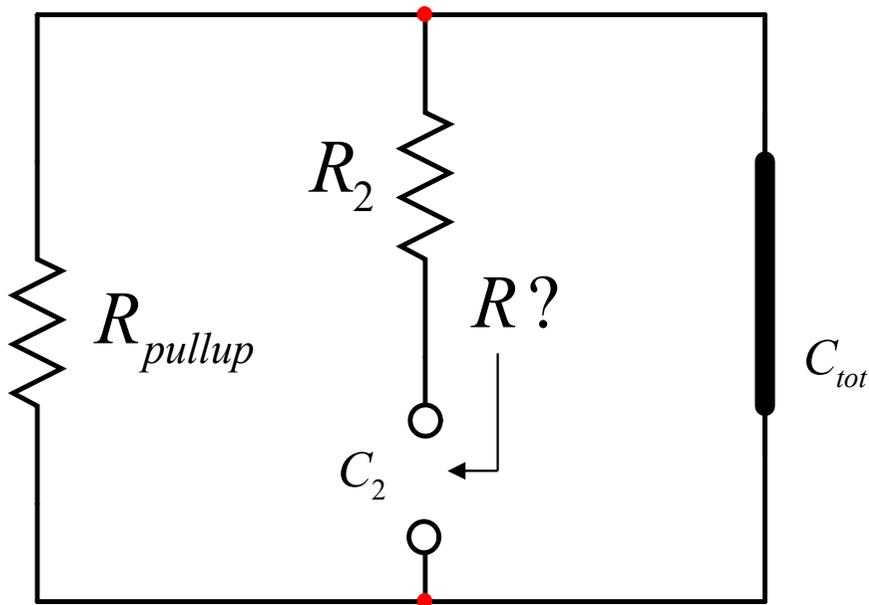τ_1^2 → Put storage element involved in τ_2 in HF
 ↑
 Look at driving resistance of element involved in τ_1



$$\tau_1^2 = R_2 C_2$$

$$a_2 = \tau_2 \tau_1^2 = R_{pullup} C_{tot} R_2 C_2 \quad \leftarrow \text{Much simpler definition for } a_2$$

Rewrite Denominator with Cascaded Poles

- Identify variables in the second-order polynomial

$$D(s) = 1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2 \quad \longrightarrow \quad \begin{aligned} a_1 &= \frac{1}{\omega_0 Q} & a_2 &= \frac{1}{\omega_0^2} \\ \omega_0 &= \frac{1}{\sqrt{a_2}} & Q &= \frac{\sqrt{a_2}}{a_1} \end{aligned}$$
$$D(s) = 1 + a_1 s + a_2 s^2$$

- You can apply the low- Q approximation to $D(s)$

$$D(s) = 1 + a_1 s + a_2 s^2 \approx \left(1 + \frac{s}{s_{p1}}\right) \left(1 + \frac{s}{s_{p2}}\right) \quad \left| \quad \begin{aligned} \omega_{p1} &= Q \omega_0 = \frac{1}{a_1} \\ \omega_{p2} &= \frac{\omega_0}{Q} = \frac{a_1}{a_2} \end{aligned} \right.$$

Express Poles and Zeros

□ C_{tot} is a few nF while C_2 will be around the μF : $C_{tot} \ll C_2$

$$\omega_{p_1} = \frac{1}{R_{pullup} C_{tot} + (R_{pullup} + R_2) C_2} \quad f_{p_1} = \frac{1}{2\pi [R_{pullup} C_{tot} + (R_{pullup} + R_2) C_2]}$$

$$f_{p_1} \approx \frac{1}{2\pi (R_{pullup} + R_2) C_2} \longrightarrow \text{Low-frequency pole}$$

□ The second pole involves the optocoupler capacitor C_{tot}

$$\omega_{p_2} = \frac{R_{pullup} C_{tot} + (R_{pullup} + R_2) C_2}{R_{pullup} C_{tot} R_2 C_2} = \frac{1}{R_2 C_2} + \frac{1}{C_{tot} (R_2 \parallel R_{pullup})}$$

$$\longrightarrow f_{p_2} = \frac{1}{2\pi \left[\frac{1}{R_2 C_2} + \frac{1}{C_{tot} (R_2 \parallel R_{pullup})} \right]} \quad f_{p_2} \approx \frac{1}{2\pi C_{tot} (R_2 \parallel R_{pullup})}$$

Assembling Poles and Zeros

- Assemble gain, poles and zeros to form the transfer function

$$V_{FB}(s) = -I_{LED}(s) Z_{eq}(s) CTR$$

$$V_{FB}(s) = -\frac{V_{out}(s) CTR}{R_{LED}} R_0 \frac{1 + \frac{s}{s_{z_1}}}{\frac{s}{s_{po}}} \frac{1 + \frac{s}{s_{z_2}}}{\left(1 + \frac{s}{s_{p_1}}\right) \left(1 + \frac{s}{s_{p_2}}\right)}$$

→ $G(s) = -\frac{CTR}{R_{LED}} R_{pullup} \frac{(1 + sR_1C_1)(1 + sR_2C_2)}{sR_1C_1 \left[1 + (R_{pullup} + R_2)C_2\right] \left[1 + sC_{tot} (R_2 \parallel R_{pullup})\right]}$

- Factor sR_1C_1 in the numerator

$$G(s) = -\frac{CTR}{R_{LED}} R_{pullup} \frac{\cancel{sR_1C_1} \left(1 + \frac{1}{sR_1C_1}\right) (1 + sR_2C_2)}{\cancel{sR_1C_1} \left[1 + (R_{pullup} + R_2)C_2\right] \left[1 + sC_{tot} (R_2 \parallel R_{pullup})\right]}$$

Simplify Final Transfer Function

- Rearrange the low-frequency pole and zero

$$G(s) = -\frac{CTR}{R_{LED}} R_{pullup} \frac{1 + \frac{1}{sR_1C_1}}{1 + sC_{tot} (R_2 \parallel R_{pullup})} \frac{1 + sR_2C_2}{1 + s(R_{pullup} + R_2)C_2} \leftarrow \text{Factor}$$


$$G(s) = -\frac{CTR}{R_{LED}} R_{pullup} \frac{\cancel{sR_2C_2}}{s\cancel{(R_{pullup} + R_2)C_2}} \frac{1 + \frac{1}{sR_1C_1}}{1 + sC_{tot} (R_2 \parallel R_{pullup})} \frac{1 + \frac{1}{sR_2C_2}}{1 + \frac{1}{s(R_{pullup} + R_2)C_2}}$$

$$\frac{1 + \frac{1}{sR_2C_2}}{1 + \frac{1}{s(R_{pullup} + R_2)C_2}} \approx 1 \quad \Rightarrow \quad G(s) = -\frac{R_{pullup} \parallel R_2}{R_{LED}} CTR \frac{1 + \frac{1}{sR_1C_1}}{1 + sC_{tot} (R_2 \parallel R_{pullup})}$$

New mid-band gain


Validating the Transfer Function

- Compare both expressions with Mathcad®

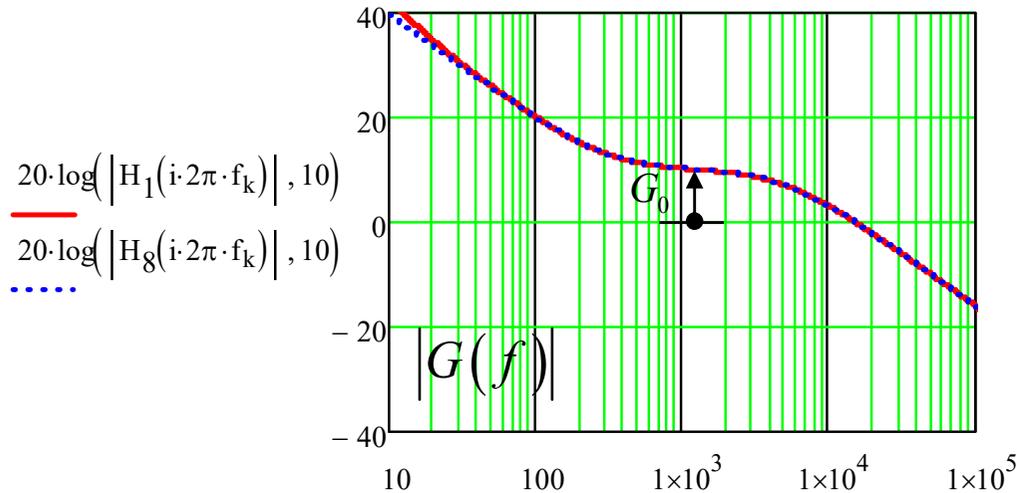

Full formula
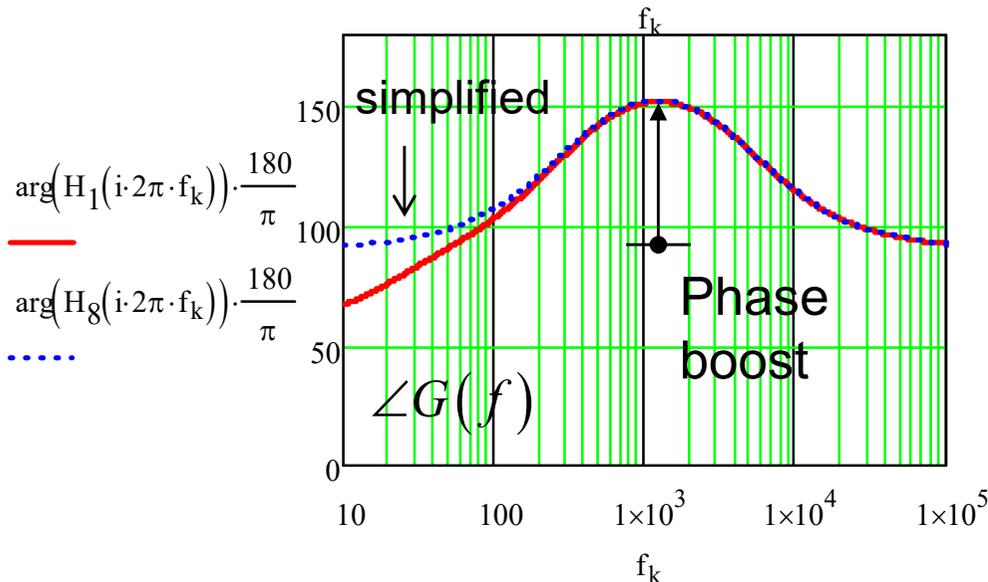
$$G(s) = -\frac{CTR}{R_{LED}} R_{pullup} \frac{(1 + sR_1C_1)(1 + sR_2C_2)}{sR_1C_1 [1 + (R_{pullup} + R_2)C_2] [1 + sC_{tot}(R_2 \parallel R_{pullup})]}$$




Simplified formula

$$G(s) = -\frac{R_{pullup} \parallel R_2}{R_{LED}} CTR \frac{1 + \frac{1}{sR_1C_1}}{1 + sC_{tot}(R_2 \parallel R_{pullup})}$$

Comparing SPICE and Mathcad®


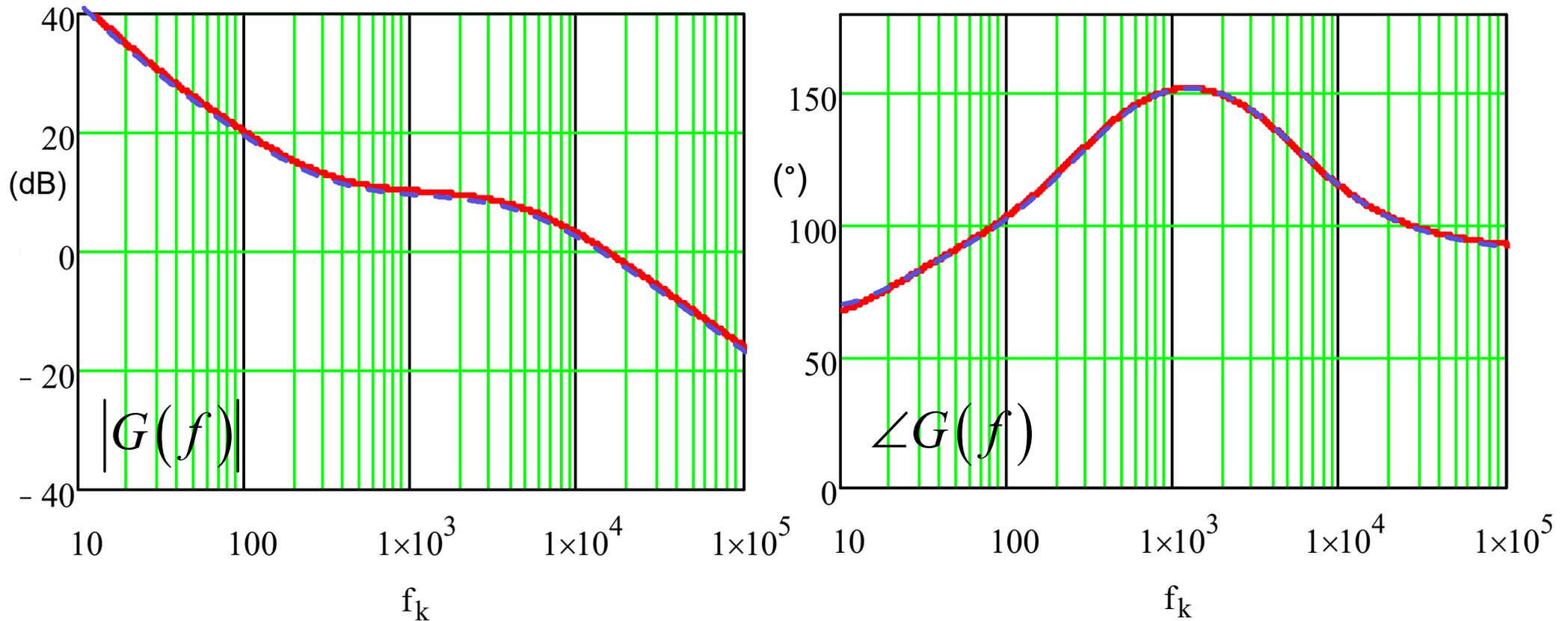
- The simulation matches analytical results



- Let's exercise these formulas in a practical example

A Typical Design Case

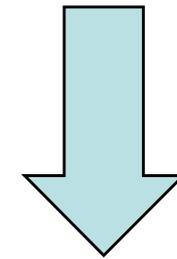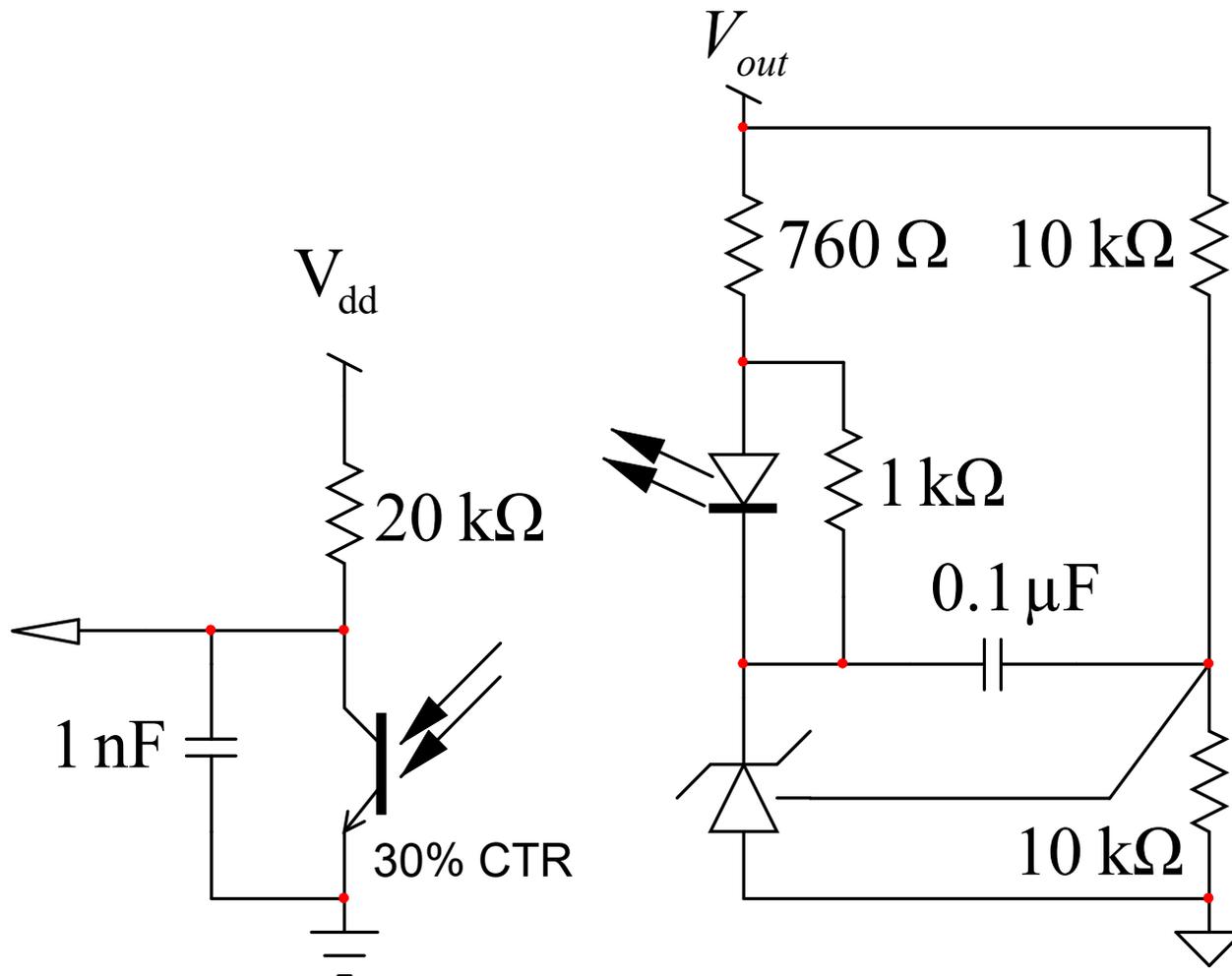- ❑ Assume a 5-V power supply, crossover requires a **10-dB** gain
- ❑ R_{LED} max is computed to 840 Ω



Minimum gain is

$$\begin{aligned}
 G_0 &= \text{CTR} \frac{R_{pullup}}{R_{LED}} \\
 &= 0.3 \times \frac{20}{0.840} \\
 &= 7.2 \text{ or } \approx \mathbf{17 \text{ dB}}
 \end{aligned}$$

Reducing the Mid-Band Gain


- ❑ The LED resistor is selected with margins to satisfy bias
- ❑ The extra resistor is computed based on the required gain

$$G_0 = \frac{R_{pullup} \parallel R_2}{R_{LED}} \text{CTR} \longrightarrow R_2 = \frac{G_0 R_{LED} R_{pullup}}{\text{CTR} \cdot R_{pullup} - G_0 R_{LED}}$$

- ❑ A 10-dB gain means G_0 equals 3.16


$$R_2 = \frac{3.16 \times 760 \times 20k}{0.3 \cdot 20k - 3.16 \times 760} = 13.3 \text{ k}\Omega$$

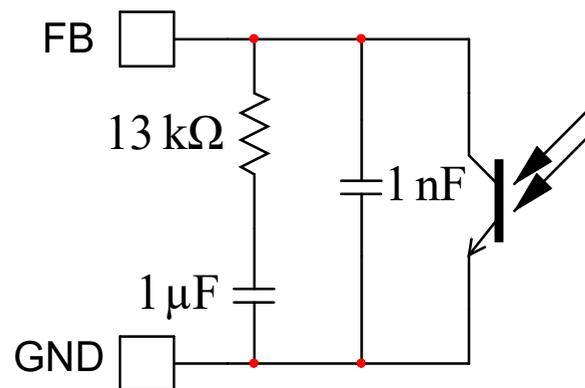- ❑ Select a high-value capacitor for C_2 , 1 μF



SPICE Simulation of Compensator

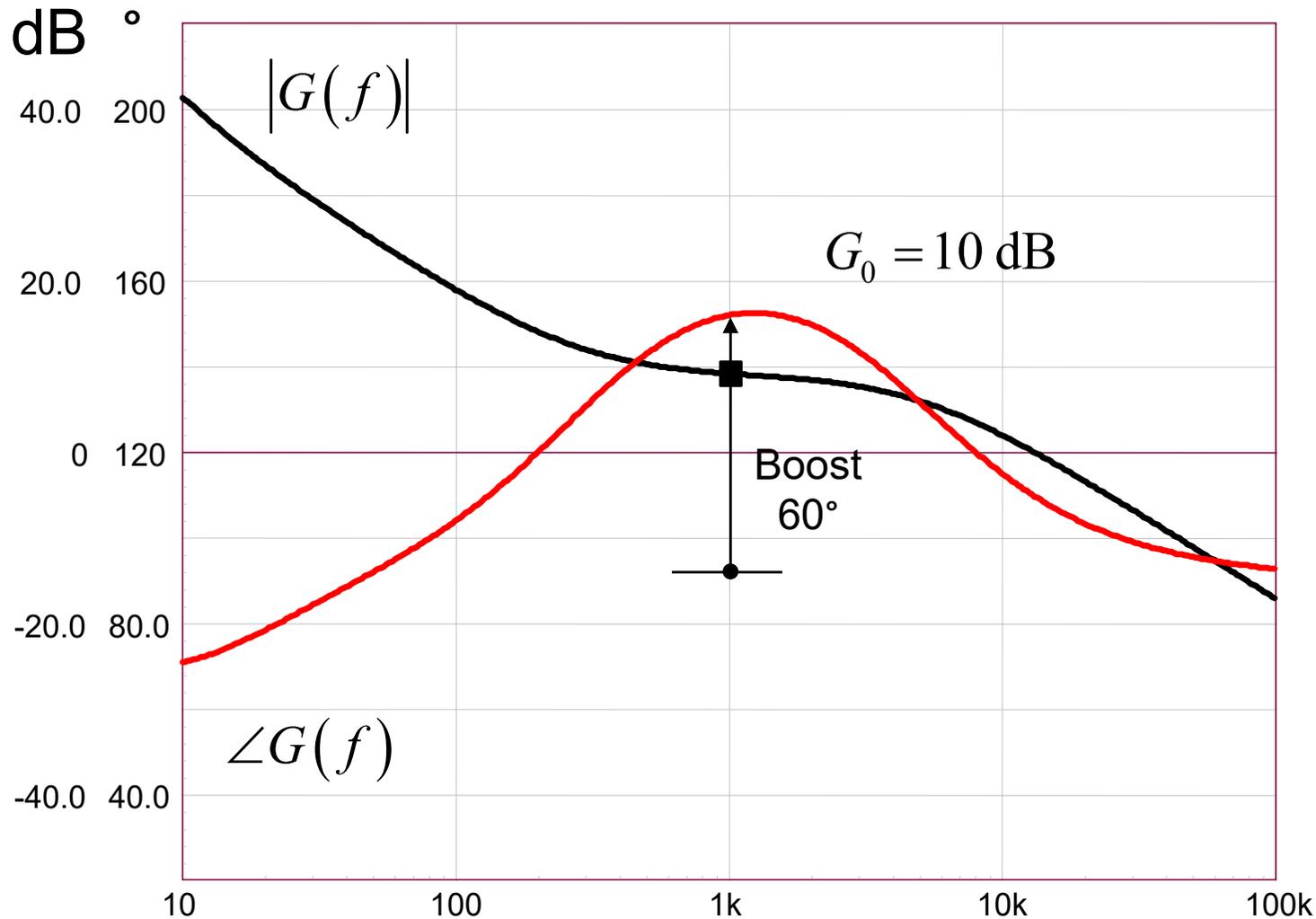- Simulation results confirm calculations



Conclusion

- ❑ It is important to consider non-ideal components in studies
- ❑ Models show the impact of op amps imperfections
- ❑ Simulation helps assess contribution of parasitics
- ❑ Optocoupler is key in isolated designs and must be characterized
- ❑ The fast lane affects optocoupler-based return paths
- ❑ Dc-dc bricks control require soft-start from the secondary side
- ❑ Analysis, simulation and bench are recipes for success!



Merci !
Thank you!
Xiè-xie!

