



ON Semiconductor®

Introduction to Fast Analytical Techniques: Application to Small-Signal Modeling

Christophe Basso – Technical Fellow
IEEE Senior Member



Course Agenda

- What is a Transfer Function?
- Why do We Need New Analytical Techniques?
- Time Constants and Poles
- Identifying the Zeros
- The Null Double Injection
- 2nd-Order Networks
- The PWM Switch Model
- A CCM Buck in Voltage Mode
- A CCM Buck-Boost in Voltage Mode



Course Agenda

- What is a Transfer Function?**
- Why do We Need New Analytical Techniques?
- Time Constants and Poles
- Identifying the Zeros
- The Null Double Injection
- 2nd-Order Networks
- The PWM Switch Model
- A CCM Buck in Voltage Mode
- A CCM Buck-Boost in Voltage Mode



Definition of Transfer Functions

□ What is a *transfer function*?




“A transfer function is a mathematical relationship linking a response to an excitation”

$$H(s) = \frac{V_{out}(s) \text{ response}}{V_{in}(s) \text{ excitation}}$$


Six Types of Transfer Functions

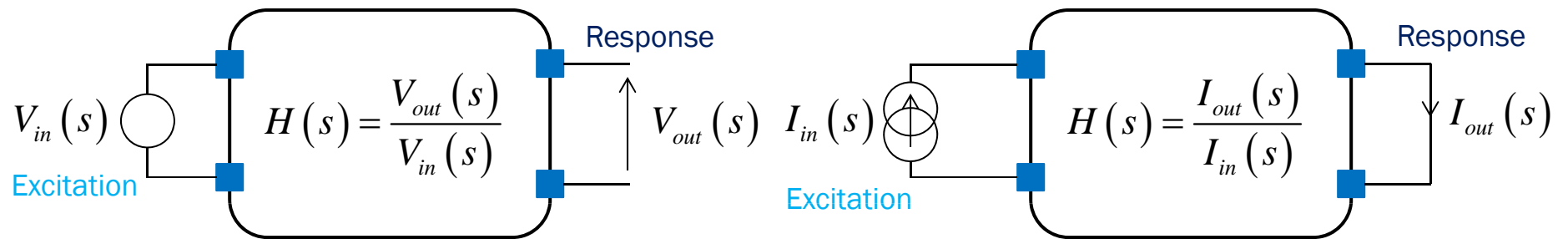- Transfer function can involve signals at different places



Voltage gain

Current gain

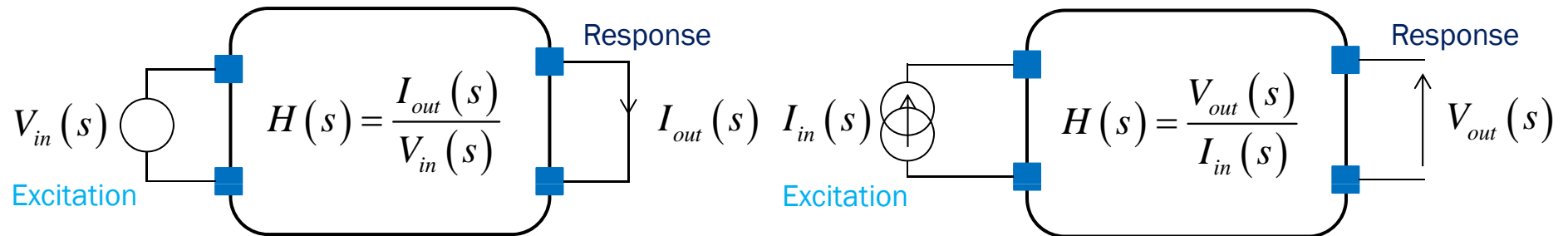


Transfer admittance
or *transadmittance*


Transimpedance

Driving Point Impedance - DPI

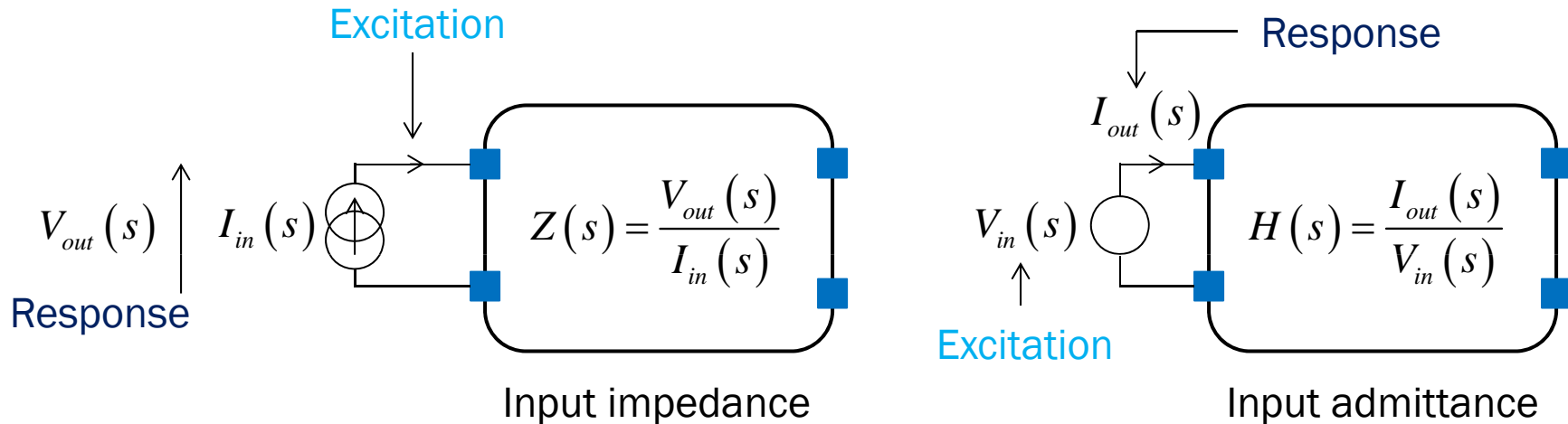- Waveforms can also be observed at the same terminals



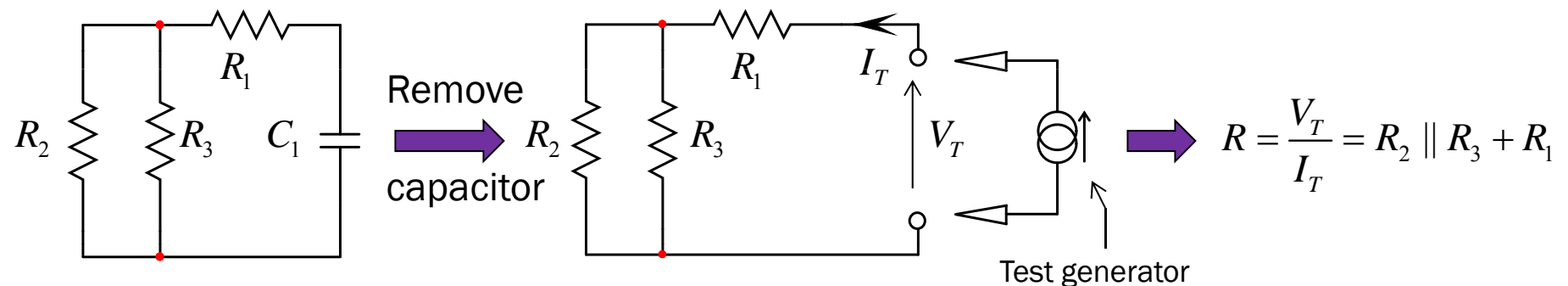- Determining the resistance at reactance's terminals: DPI



Writing Transfer Functions

- How to write a transfer function the right way?
- ✓ A leading term (if any) with the same unit as the function
- ✓ A numerator $N(s)$: its roots are the *zeros* $|H(s_z)| = 0$
- ✓ A denominator $D(s)$: its roots are the *poles* $|H(s_p)| \rightarrow \infty$

gain	$\begin{array}{c} \text{unitless} \\ \downarrow \\ H(s) = H_0 \frac{N(s)}{D(s)} \end{array}$	$\begin{array}{c} \text{unitless} \\ \downarrow \\ H(s) = H_0 \frac{N(s)}{D(s)} \end{array}$	$\begin{array}{c} [\Omega] \\ \downarrow \\ Z(s) = R_0 \frac{N(s)}{D(s)} \end{array}$	$\begin{array}{c} [\Omega] \\ \downarrow \\ Z(s) = R_0 \frac{N(s)}{D(s)} \end{array}$	$\begin{array}{c} \text{unitless} \\ \downarrow \\ \frac{N(s)}{D(s)} \end{array}$	impedance
gain	$\begin{array}{c} \uparrow \\ G(s) = G_\infty \frac{N(s)}{D(s)} \\ \uparrow \\ [V]/[V] \end{array}$	$\begin{array}{c} \uparrow \\ G(s) = G_\infty \frac{N(s)}{D(s)} \\ \uparrow \\ [V]/[V] \end{array}$	$\begin{array}{c} \uparrow \\ Y(s) = Y_0 \frac{N(s)}{D(s)} \\ \uparrow \\ [S] \end{array}$	$\begin{array}{c} \uparrow \\ Y(s) = Y_0 \frac{N(s)}{D(s)} \\ \uparrow \\ [S] \end{array}$	admittance	




Course Agenda

- What is a Transfer Function?
- Why do We Need New Analytical Techniques?**
- Time Constants and Poles
- Identifying the Zeros
- The Null Double Injection
- 2nd-Order Networks
- The PWM Switch Model
- A CCM Buck in Voltage Mode
- A CCM Buck-Boost in Voltage Mode



Why a Different Approach?

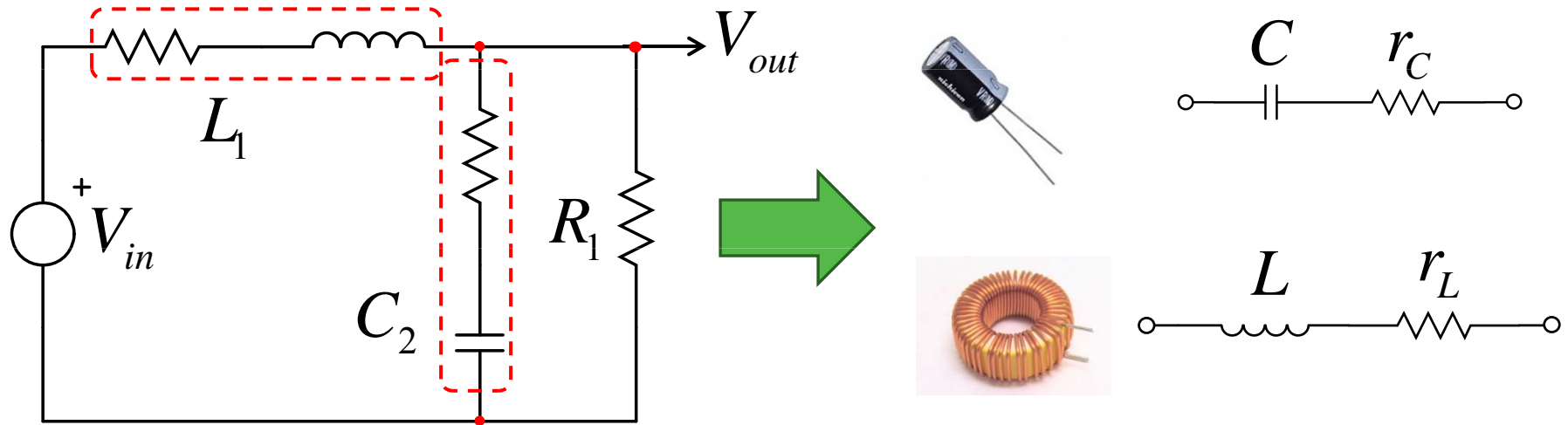- ❑ A buck power stage involves energy-storing elements



- ❖ Energy-storing elements host parasitic contributors
- ❖ They move with production, temperature, age...



They hide in the transfer function
and must be unmasked!

Identifying the Contributors

- ❑ Brute-force algebra complicates analysis

$$H(s) = \frac{\left(\frac{1}{sC_2} + r_C\right) \parallel R_1}{\left(\frac{1}{sC_2} + r_C\right) \parallel R_1 + r_L + sL_1} = \frac{R_1 + sR_1r_C C_2}{R_1 + r_L + sL_1 + sC_2R_1r_C + C_2R_1r_Ls + C_2r_Cr_Ls + C_2L_1R_1s^2 + C_2L_1r_Cs^2}$$

Dc gain? ↓
Zeros? ↙

↑
Poles? ↘

- ❑ More energy is needed to unveil these terms
- ❖ factor and rearrange coefficients
- ❖ simplify numerator and denominator
- Don't make mistakes!



This is a *high-entropy* expression

In thermodynamics, entropy is a measure of disorder, <http://en.wikipedia.org/wiki/Entropy>

Low-Entropy Expressions

- What if you could write the expression in one shot?

$$H(s) = \frac{R_1}{R_1 + r_L} \frac{1 + sr_C C_2}{1 + s \left[\frac{L_1}{r_L + R_1} + C_2 (r_C + r_L \parallel R_1) \right] + s^2 L_1 C_2 \frac{r_C + R_1}{r_L + R_1}}$$

- Naturally reading gains, poles and zeros...

$$H(s) = H_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0} \right)^2}$$

$$\left. \begin{aligned} \omega_z &= \frac{1}{r_C C_2} & \omega_0 &= \frac{1}{\sqrt{L_1 C_2}} \sqrt{\frac{r_C + R_1}{r_L + R_1}} \\ Q &= \frac{r_L + R_1}{L_1 + C_2 [r_C r_L + R_1 (r_C + r_L)]} \frac{1}{\omega_0} \end{aligned} \right\}$$




This is a *low-entropy* expression

R. D. Middlebrook, "Methods of Design-Oriented Analysis: Low Entropy Expressions", New Approaches to Undergraduate Education, July 1992

Starting with a Simple Example

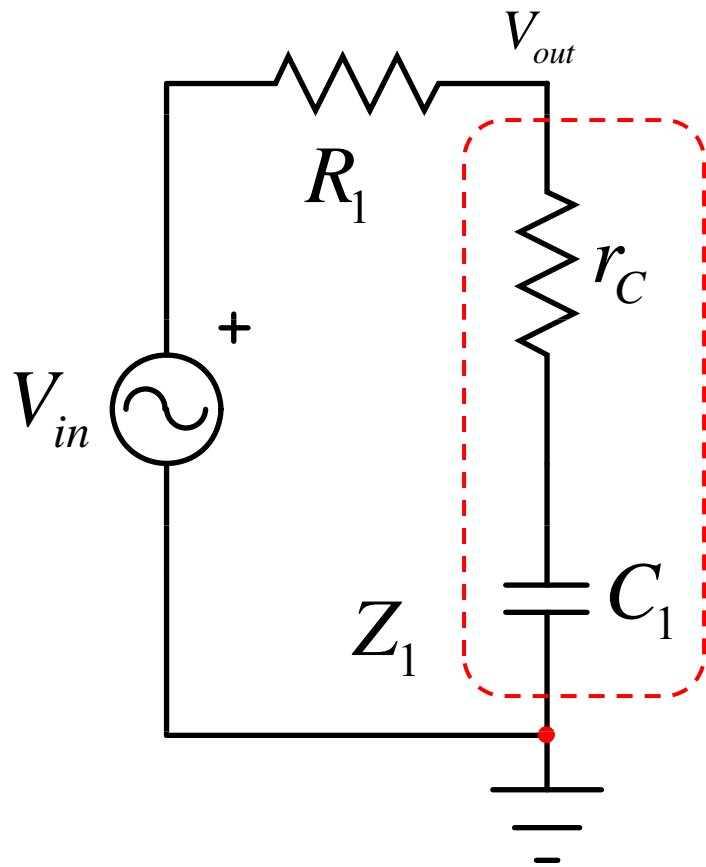- What is the transfer function of the below circuit?





$$Z_1(s) = r_c + \frac{1}{sC_1} = \frac{1 + sr_c C_1}{sC_1}$$

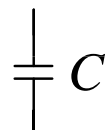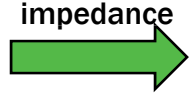
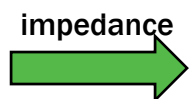
$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{\frac{1 + sr_c C_1}{sC_1}}{\frac{1 + sr_c C_1}{sC_1} + R_1}$$

- Is there any easier and faster way to go?

Two Different Stages

- Consider dc and high-frequency states for L and C

 C		$Z_C = \frac{1}{sC}$	Dc state	$Z_C = \infty$	Cap. is an open circuit
			HF state	$Z_C = 0$	Cap. is a short circuit

 L		$Z_L = sL$	Dc state	$Z_L = 0$	Inductor is a short circuit
			HF state	$Z_L = \infty$	Inductor is an open circuit

- Change the circuit depending on s




Fast Analytical Techniques at a Glance

□ Look at the circuit for $s = 0$

➤ Capacitors are open circuited

➤ Inductors are short circuited

} SPICE operating point calculation

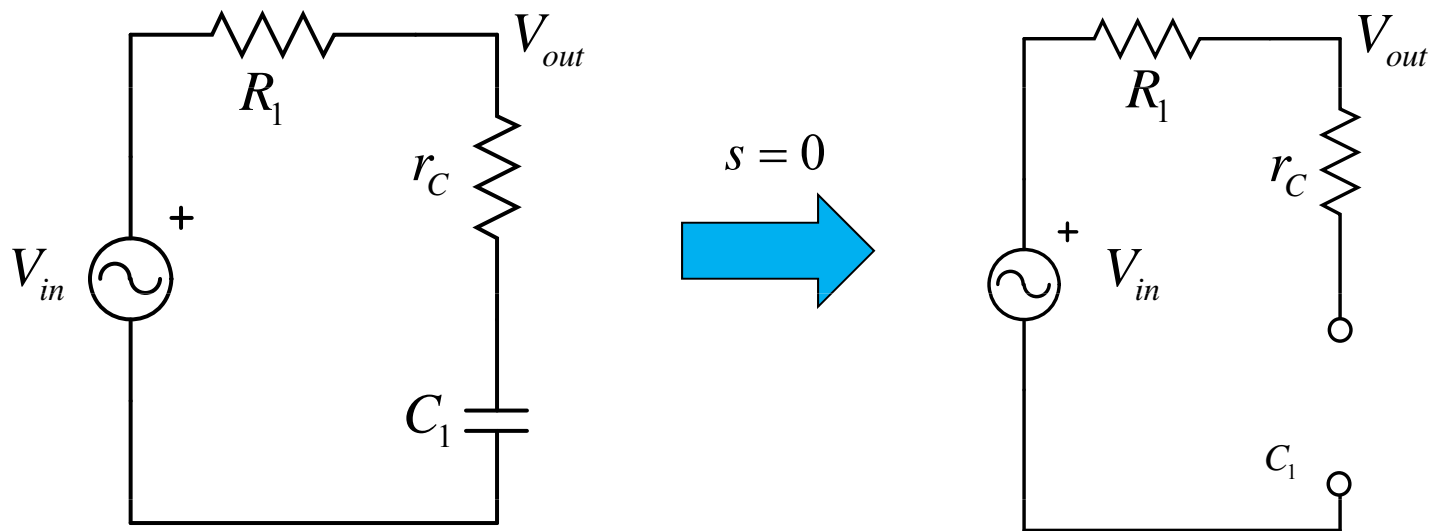


□ Determine the gain in this condition

$$H_0 = V_{out} / V_{in} = 1$$

Fast Analytical Techniques at a Glance

□ Look at the resistance driving the storage element

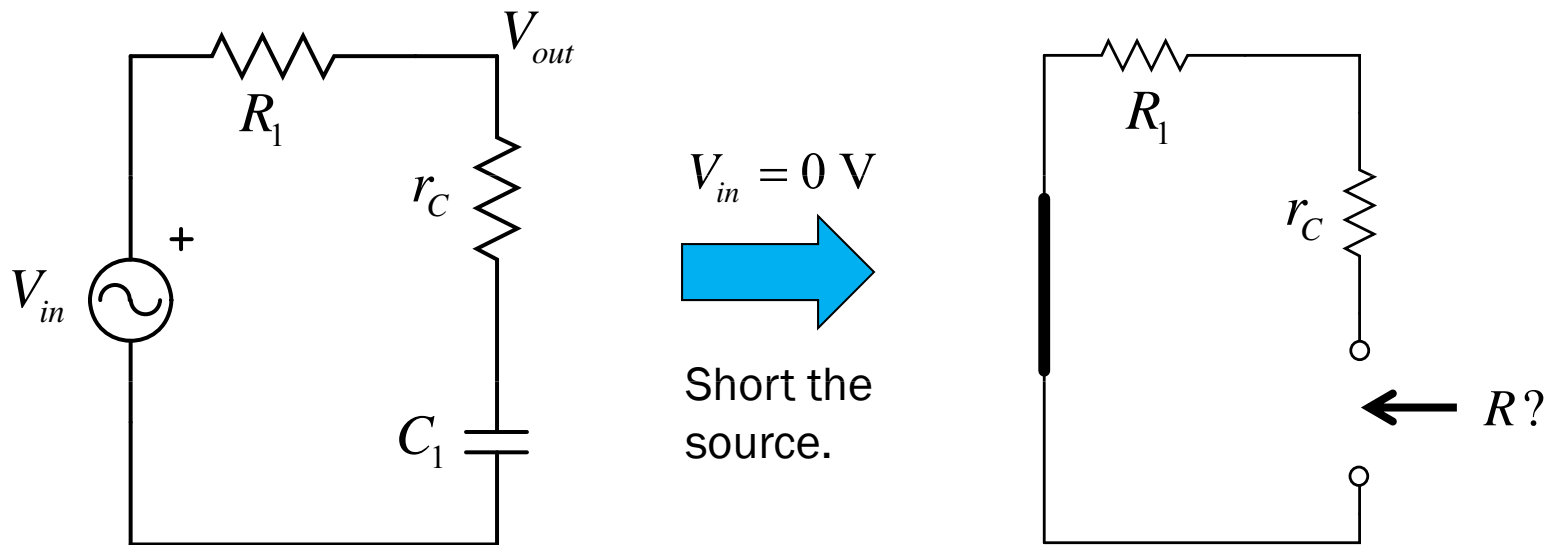1. When the excitation is turned off, $V_{in} = 0$ V




□ Remove the capacitor and look into its terminals

➤ The first time constant is $\tau_1 = (r_C + R_1)C_1$

Fast Analytical Techniques at a Glance

□ Look at the resistance driving the storage element

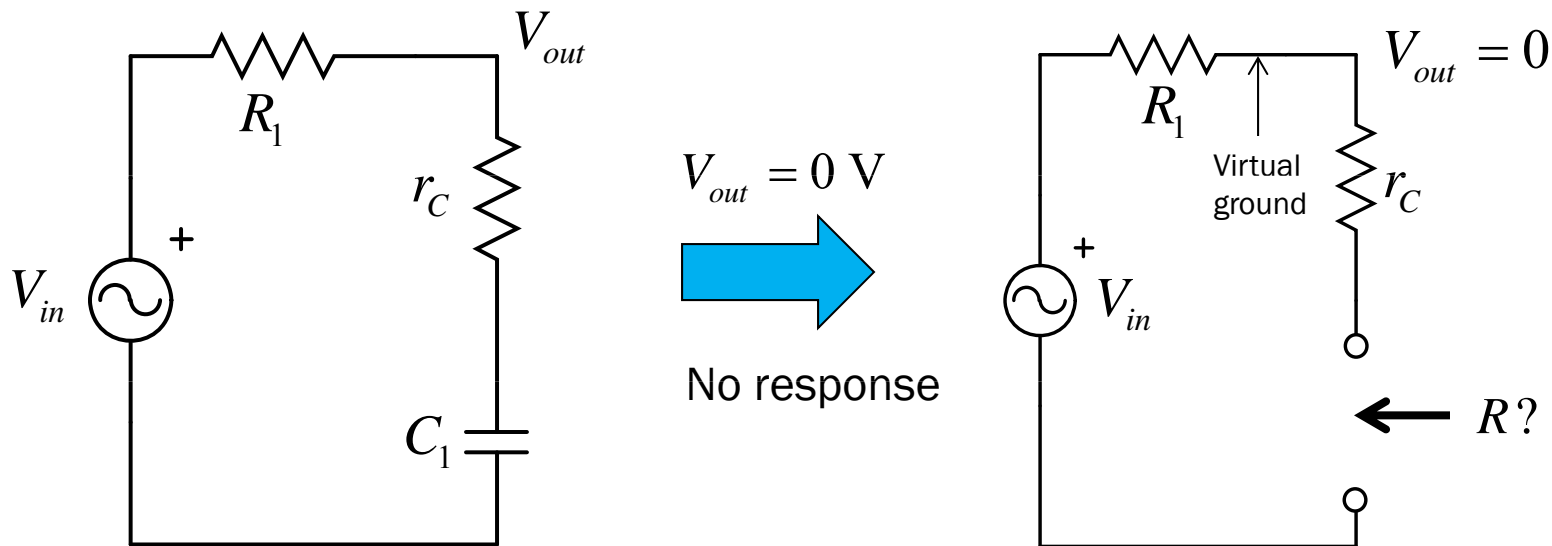1. When the excitation is back but $V_{out} = 0$ V



□ Remove the capacitor and look into its terminals

➤ The second time constant is $\tau_2 = r_C C_1$

Combining Time Constants

- By combining times constants, we have

$$H(s) = H_0 \frac{1 + s\tau_2}{1 + s\tau_1} = \frac{1 + sr_C C_1}{1 + s(r_C + R_1)C_1}$$


- Rearrange the equation to unveil a pole and a zero

$$H(s) = H_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \left. \vphantom{H(s)} \right\} \begin{aligned} \omega_z &= \frac{1}{r_C C_1} & H_0 &= 1 \\ \omega_p &= \frac{1}{(r_C + R_1)C_1} \end{aligned}$$

- This is a *low-entropy* expression

Another Example

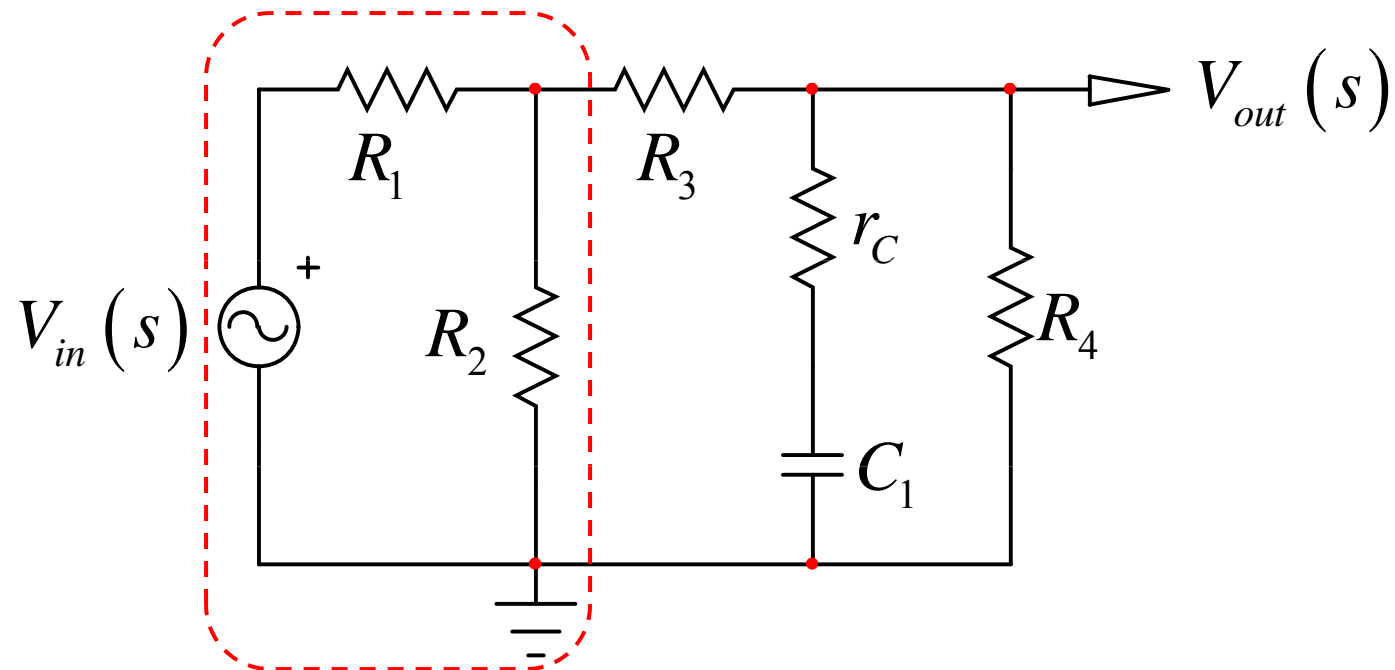
- How would you calculate V_{out} / V_{in} ?



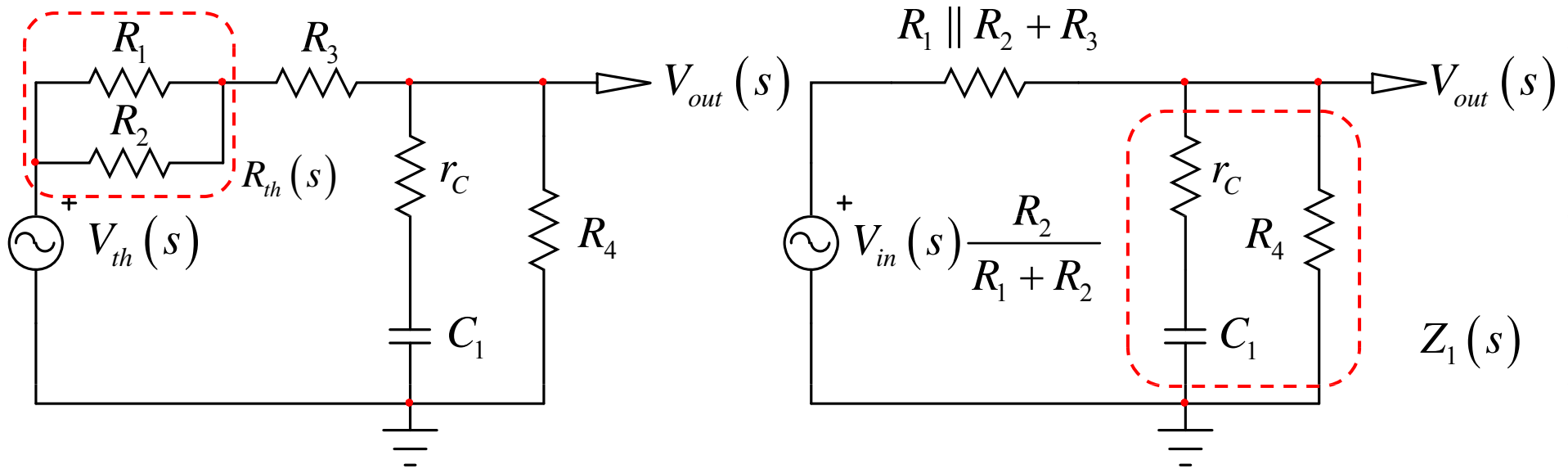1. Transform the circuit with a Thévenin generator
2. Apply impedance divider involving C_1

Apply Impedance Divider

- Reduce circuit complexity with Thévenin



- Apply impedance divider involving Z_1 and R_{th}

$$R_{th}(s) = R_1 \parallel R_2 + R_3$$

$$Z_1(s) = R_4 \parallel \left(r_c + \frac{1}{sC_1} \right)$$

$$H(s) = \frac{Z_1(s)}{Z_1(s) + R_{th}(s)} \frac{R_2}{R_1 + R_2}$$



“Who you gonna call?”


M

High-Entropy Expression

□ How do you make use of this result?

$$H_2(s) := \frac{R_2 \cdot R_4 \cdot (C_1 \cdot r_C \cdot s + 1)}{R_1 \cdot R_2 + R_1 \cdot R_3 + R_1 \cdot R_4 + R_2 \cdot R_3 + R_2 \cdot R_4 + C_1 \cdot R_1 \cdot R_2 \cdot R_4 \cdot s + C_1 \cdot R_1 \cdot R_3 \cdot R_4 \cdot s + C_1 \cdot R_2 \cdot R_3 \cdot R_4 \cdot s + C_1 \cdot R_1 \cdot R_2 \cdot r_C \cdot s + C_1 \cdot R_1 \cdot R_3 \cdot r_C \cdot s + C_1 \cdot R_1 \cdot R_4 \cdot r_C \cdot s + C_1 \cdot R_2 \cdot R_3 \cdot r_C \cdot s + C_1 \cdot R_2 \cdot R_4 \cdot r_C \cdot s}$$

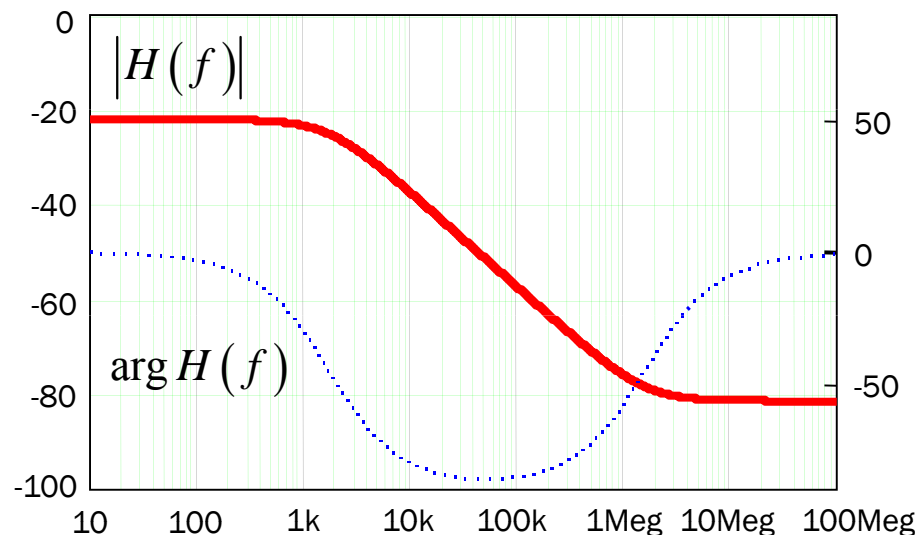
- ❖ what is the pole/zero position?
- ❖ what affects the quasi-static gain for $s = 0$?



You can plot the ac response but it yields no insight on what drives poles and zeros!

Applying FACTs Now

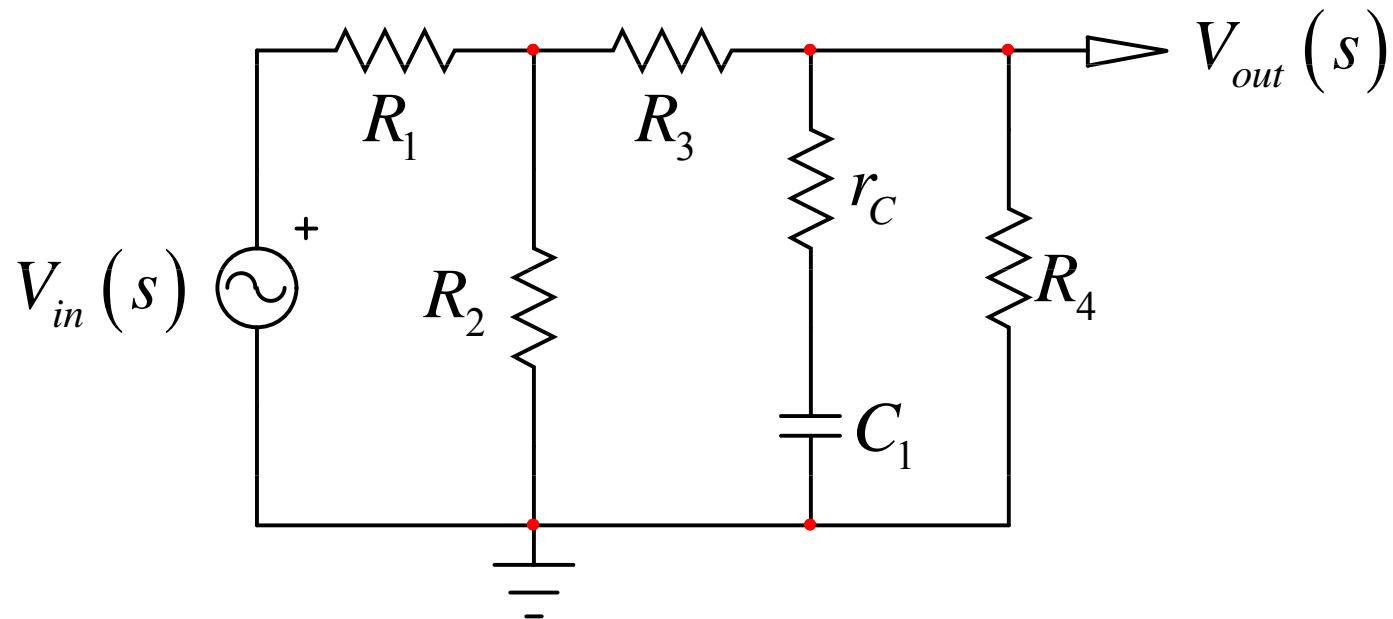- What is the gain when V_{in} is a dc voltage?




- The capacitor is open circuited, read the schematic!

$$H_0 = \frac{R_2}{R_1 + R_2} \frac{R_4}{R_1 \parallel R_2 + R_3 + R_4}$$

Fast Analytical Circuits Techniques – FACTs, V. Vorperian

Determine the First Time Constant

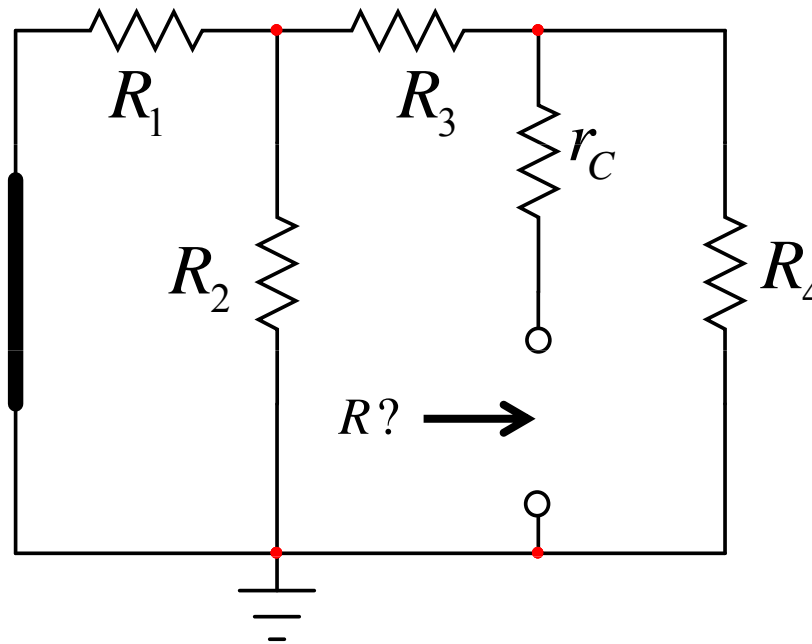
- Look at the resistance driving the storage element
1. When the excitation is turned off, $V_{in} = 0$ V



$$\tau_1 = \left[r_C + (R_1 \parallel R_2 + R_3) \parallel R_4 \right] C_1$$

Determine the Second Time Constant

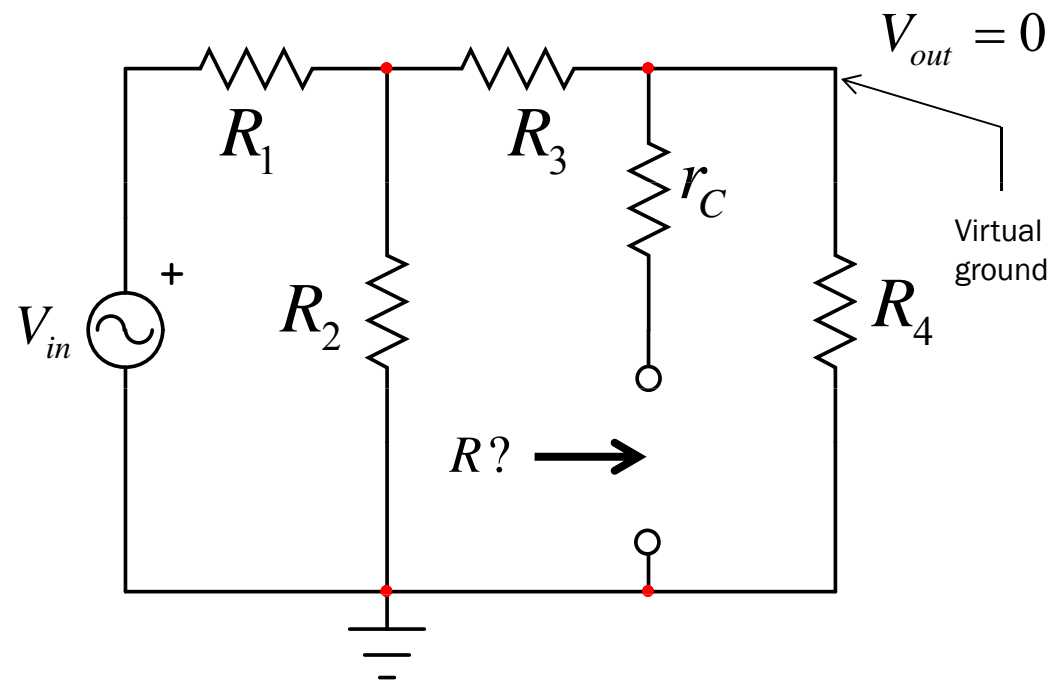- Look at the resistance driving the storage element
- 1. When the excitation is back but $V_{out} = 0$ V



$$\tau_2 = r_C C_1$$

Assemble the Terms

- You immediately have a *low-entropy* form

$$H(s) = H_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \left| \begin{array}{l} H_0 = \frac{R_2}{R_1 + R_2} \frac{R_4}{R_1 \parallel R_2 + R_3 + R_4} \\ \omega_p = \frac{1}{\left[r_C + (R_1 \parallel R_2 + R_3) \parallel R_4 \right] C_1} \\ \omega_z = \frac{1}{r_C C_1} \end{array} \right.$$

Way cool!



- We did not write a single line of algebra!

Use Mathcad[®] to Check Results

$$R_1 := 1\text{k}\Omega \quad R_2 := 22\text{k}\Omega \quad r_C := 0.1\Omega \quad R_3 := 150\Omega \quad R_4 := 100\Omega$$

$$\|(x, y) := \frac{x \cdot y}{x + y} \quad C_1 := 1\mu\text{F}$$

$$H(s) = \frac{\frac{R_4 \cdot \left(r_C + \frac{1}{s \cdot C_1} \right)}{R_4 + r_C + \frac{1}{s \cdot C_1}} \cdot \frac{R_2}{R_1 + R_2}}{\frac{R_4 \cdot \left(r_C + \frac{1}{s \cdot C_1} \right)}{R_4 + r_C + \frac{1}{s \cdot C_1}} + \frac{R_1 \cdot R_2}{R_1 + R_2} + R_3}$$

$$H_2(s) := \frac{R_2 \cdot R_4 \cdot (C_1 \cdot r_C \cdot s + 1)}{R_1 \cdot R_2 + R_1 \cdot R_3 + R_1 \cdot R_4 + R_2 \cdot R_3 + R_2 \cdot R_4 + C_1 \cdot R_1 \cdot R_2 \cdot R_4 \cdot s + C_1 \cdot R_1 \cdot R_3 \cdot R_4 \cdot s + C_1 \cdot R_2 \cdot R_3 \cdot R_4 \cdot s + C_1 \cdot R_1 \cdot R_2 \cdot r_C \cdot s + C_1 \cdot R_1 \cdot R_3 \cdot r_C \cdot s + C_1 \cdot R_1 \cdot R_4 \cdot r_C \cdot s + C_1 \cdot R_2 \cdot R_3 \cdot r_C \cdot s + C_1 \cdot R_2 \cdot R_4 \cdot r_C \cdot s}$$


$$\tau_2 := C_1 \cdot \left[r_C + (R_1 \parallel R_2 + R_3) \parallel R_4 \right] = 91.812 \mu\text{s}$$

$$\tau_1 := C_1 \cdot r_C = 100 \text{ ns}$$

$$H_0 := \frac{R_4}{R_4 + R_1 \parallel R_2 + R_3} \cdot \frac{R_2}{R_1 + R_2} = 0.079$$

$$H_1(s) := H_0 \cdot \frac{1 + s \cdot \tau_1}{1 + s \cdot \tau_2}$$

$$\begin{aligned} & \text{---} 20 \cdot \log(|H_1(i \cdot 2\pi \cdot f_k)|, 10) \\ & \text{---} 20 \cdot \log(|H_2(i \cdot 2\pi \cdot f_k)|, 10) \\ & \text{---} \end{aligned}$$

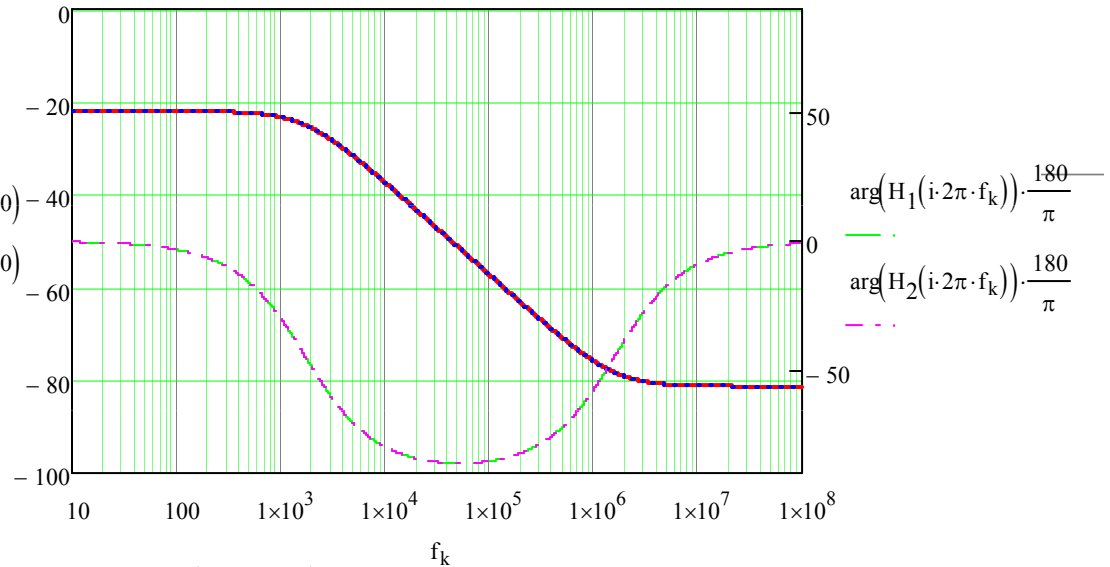

Superimposing both transfer functions, matching should be perfect. If not, there is mistake.


Course Agenda

- What is a Transfer Function?
- Why do We Need New Analytical Techniques?
- Time Constants and Poles**
- Identifying the Zeros
- The Null Double Injection
- 2nd-Order Networks
- The PWM Switch Model
- A CCM Buck in Voltage Mode
- A CCM Buck-Boost in Voltage Mode




Time Constants

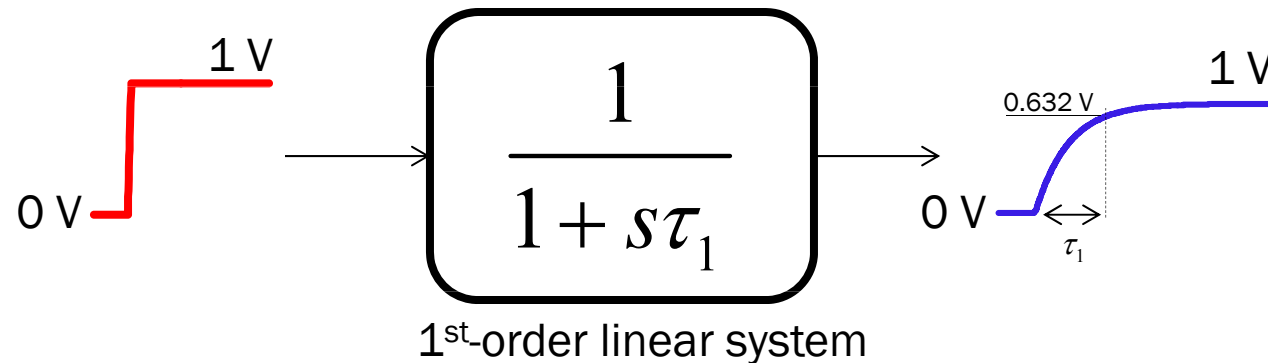- Response to a step input is described by a time constant



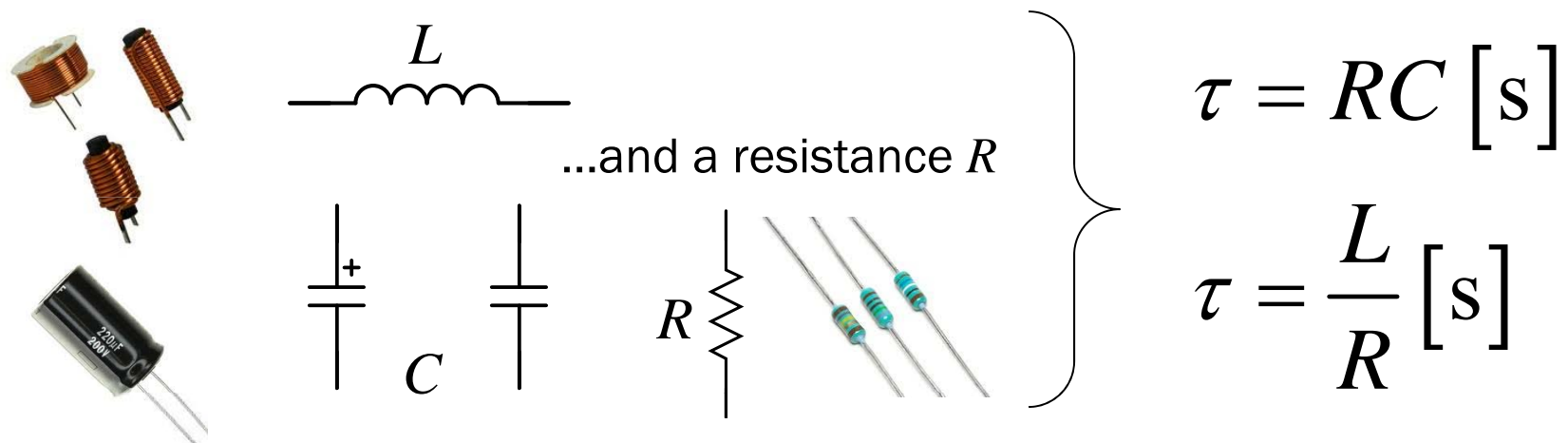- A time constant “tau” is associated with a reactance





Time-Domain Response

- The time-domain response $y(t)$ of a linear system is

$$y(t) = r_f(t) + r_n(t)$$



↑ ↑
Forced response Natural response

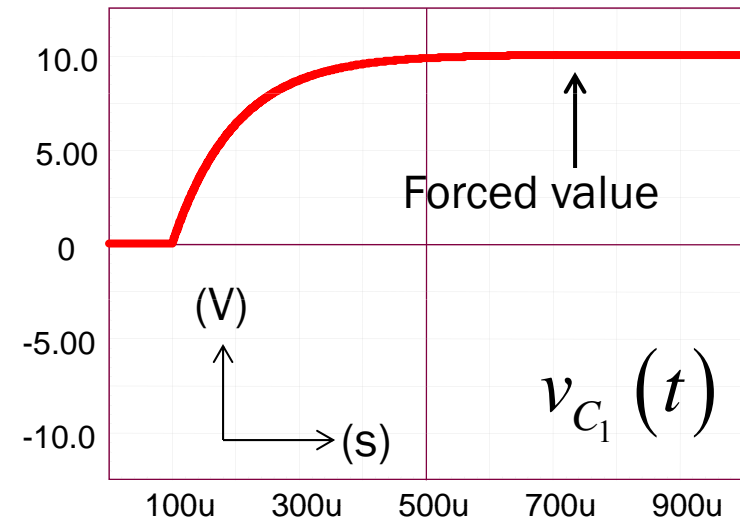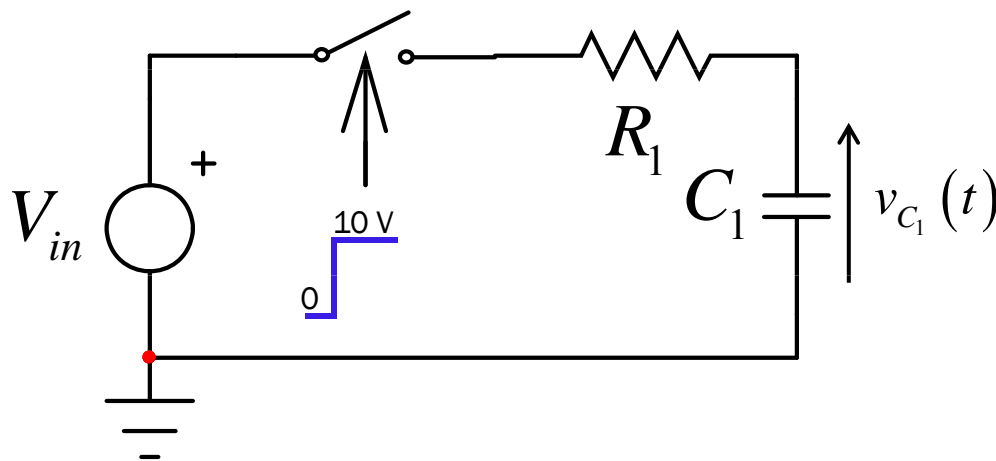- The first term depends on the excitation – the force



Natural Response

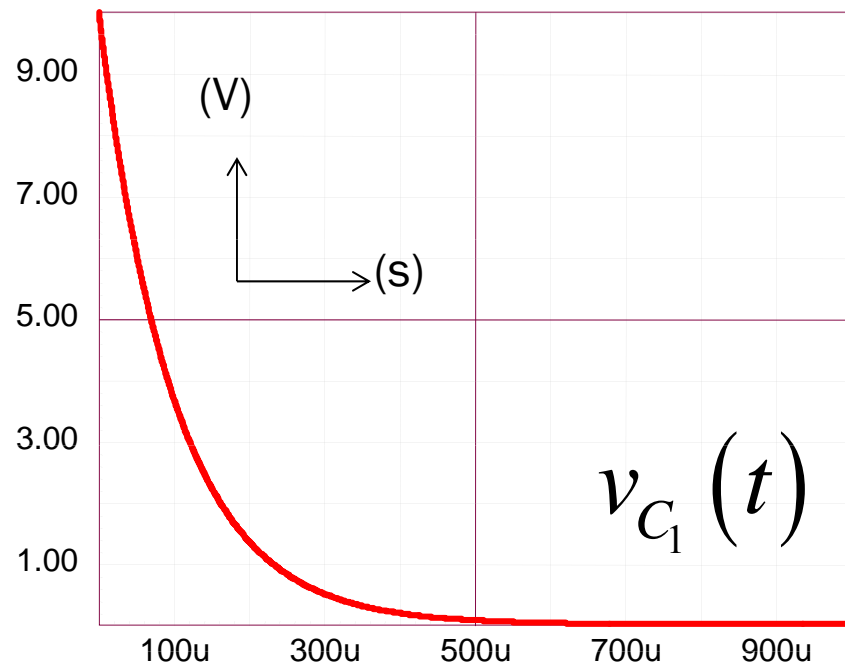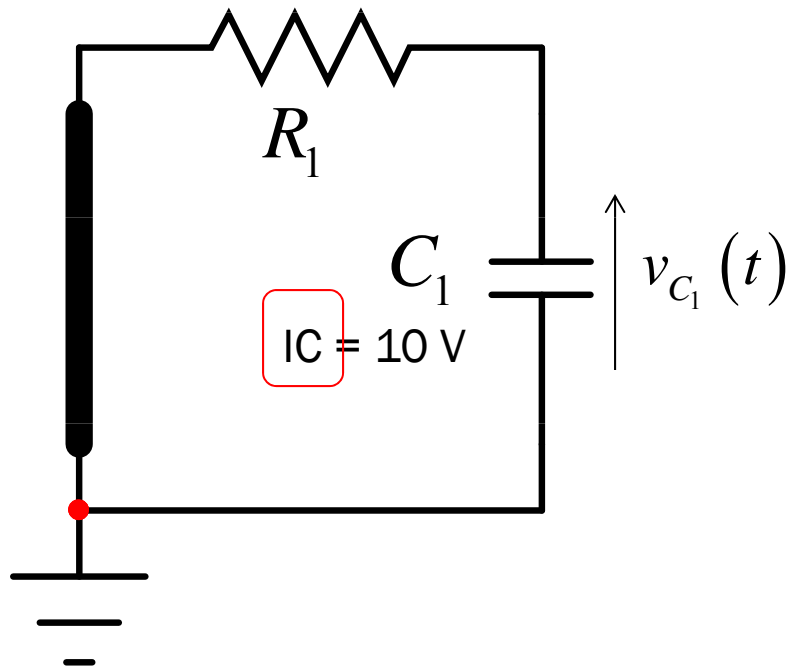
- Natural response solely involves initial conditions



➔ You don't need a source for the natural response

Time Constant Involving a Capacitor

- Assume a simple low-pass RC filter

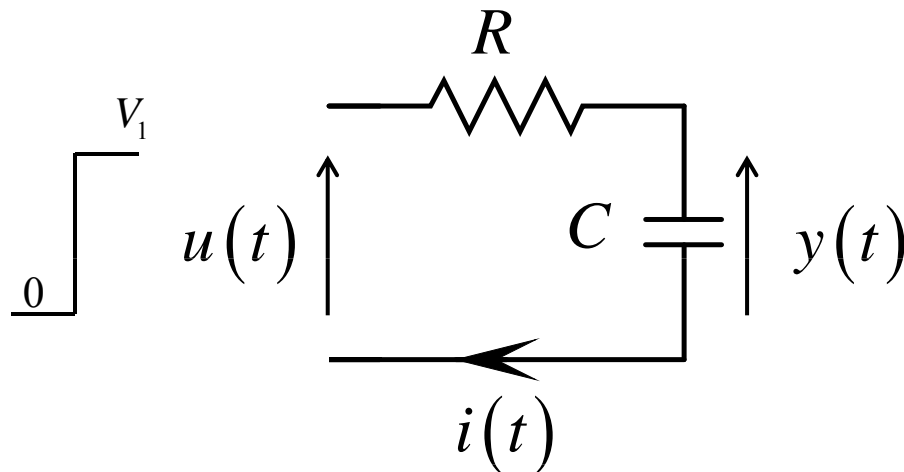

$$u(t) = Ri(t) + y(t)$$

$$i(t) = C \frac{dv_c(t)}{dt}$$

Initial capacitor voltage is V_0

$$y(t) = u(t) - RC \frac{dv_c(t)}{dt} = u(t) - RC \frac{dy(t)}{dt}$$

- The state variable associated with C is its voltage, x_2

Time Domain to Laplace

- Take the Laplace transform of the time-domain equation

$$Y(s) = \mathcal{L}\{y(t)\} = U(s) - RC(sY(s) - V_0)$$

$$Y(s) = \frac{U(s)}{1 + sRC} + \frac{RCV_0}{1 + sRC}$$

→ $\tau = RC$ time constant

- Considering 0-V initial conditions, $v_C(0) = 0$

$$Y(s) = \frac{U(s)}{1 + sRC} + \frac{RCV_0}{1 + sRC} \Rightarrow \frac{Y(s)}{U(s)} = \frac{1}{1 + s\tau}$$

$\tau = RC$
 $=0$

1st-order transfer function

Forced and Natural Responses

- Assume that input voltage U is a step function

$$\mathcal{L}^{-1}\{Y(s)\} = \mathcal{L}^{-1}\left\{\frac{V_1}{s} \frac{1}{1+sRC}\right\} + \mathcal{L}^{-1}\left\{\frac{RCV_0}{1+sRC}\right\} \quad \tau = RC$$

- Use inverse Laplace-transform tables to obtain

$$y(t) = V_1 \left(1 - e^{-\frac{t}{\tau}}\right) + V_0 e^{-\frac{t}{\tau}} \quad \Rightarrow \quad y(t) = r_f(t) + r_n(t)$$


Forced response
No initial conditions

Natural response
No source contribution

Time constant

Time Constant Involving an Inductor

- Assume a simple low-pass LR filter

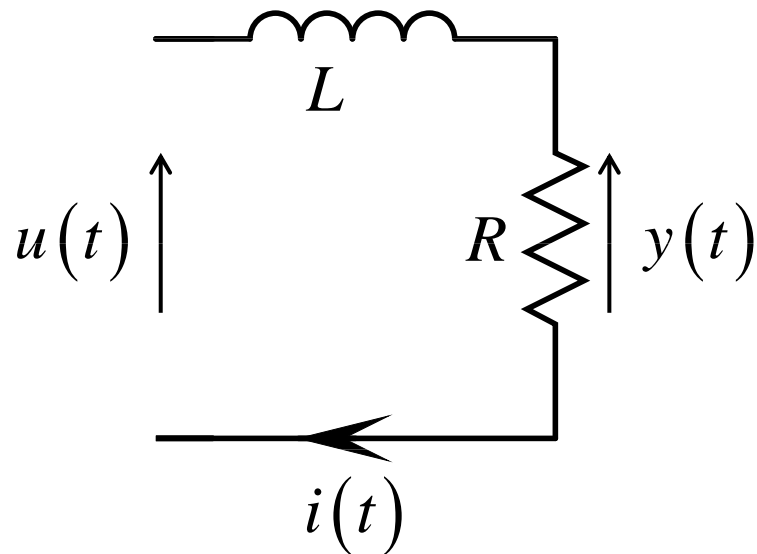

$$u(t) = L \frac{di(t)}{dt} + y(t)$$

$$y(t) = Ri(t)$$

Initial inductor current is I_0

$$y(t) = u(t) - L \frac{di(t)}{dt}$$

- The state variable associated with L is its current, x_1

Laplace Transform

- Take the Laplace transform of the time-domain equation

$$Y(s) = \mathcal{L}\{y(t)\} = U(s) - L(sI(s) - I_0) \quad I(s) = \frac{Y(s)}{R}$$

$$Y(s) = U(s) - L\left(s \frac{Y(s)}{R} - I_0\right) \quad Y(s) = \frac{U(s)}{1 + s \frac{L}{R}} + \frac{LI_0}{1 + s \frac{L}{R}}$$

- Considering 0-A initial conditions, $i_L(0) = 0$

$$Y(s) = \frac{U(s)}{1 + s \frac{L}{R}} + \frac{LI_0}{1 + s \frac{L}{R}} \quad \Rightarrow \quad \frac{Y(s)}{U(s)} = \frac{1}{1 + s\tau}$$

$\tau = \frac{L}{R}$
 Time constant

1st-order transfer function



Response to an Input Step

□ Now assume that input voltage U is a step function

$$U(s) = \frac{V_1}{s}$$

$$\mathcal{L}^{-1}\{Y(s)\} = \mathcal{L}^{-1}\left\{\frac{V_1}{s} \frac{1}{1 + s \frac{L}{R}}\right\} + \mathcal{L}^{-1}\left\{\frac{LI_0}{1 + s \frac{L}{R}}\right\} \quad \tau = \frac{L}{R}$$

$$y(t) = V_1 \left(1 - e^{-\frac{t}{\tau}}\right) + LI_0 e^{-\frac{t}{\tau}}$$


Forced response
No initial conditions

Natural response
No source contribution

Time constant

Natural Time Constant


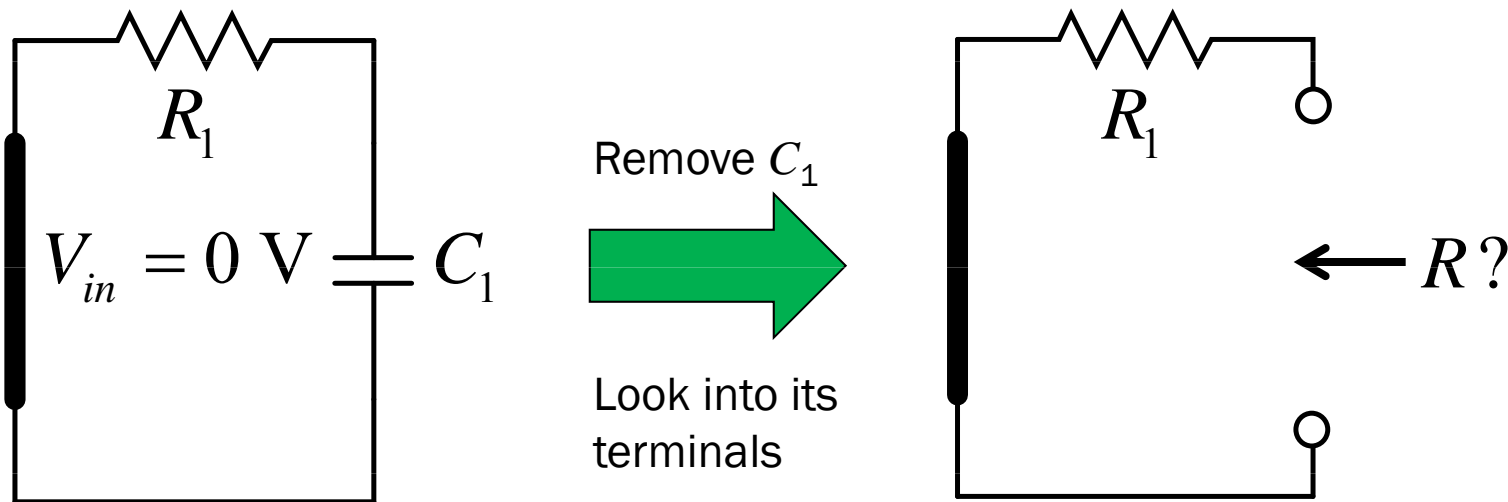
- ❑ The time constant τ plays a role in r_f and r_n
- ❑ How can we determine τ in the simplest way?
- ❖ Look at natural response circuit where V_{in} is off



- ❑ What resistance do you see? R_1 then $\tau = R_1 C_1$


Setting the Excitation to Zero

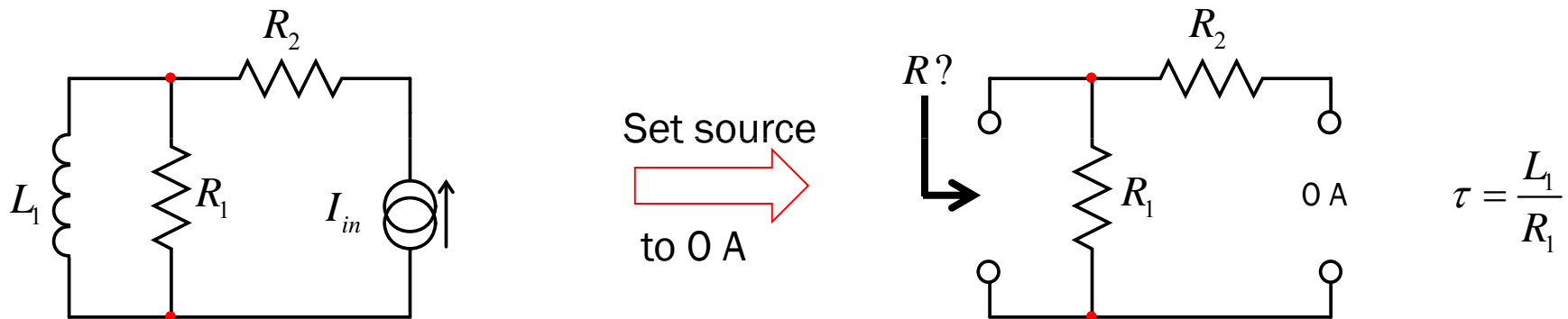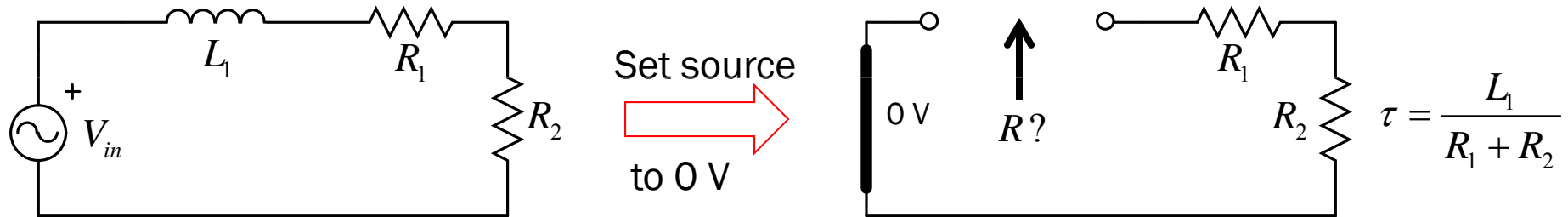- Turning the excitation off means
 - ❖ A 0-V source becomes a short circuit
 - ❖ A 0-A generator is an open circuit and disappears





Excitation Plays no Role

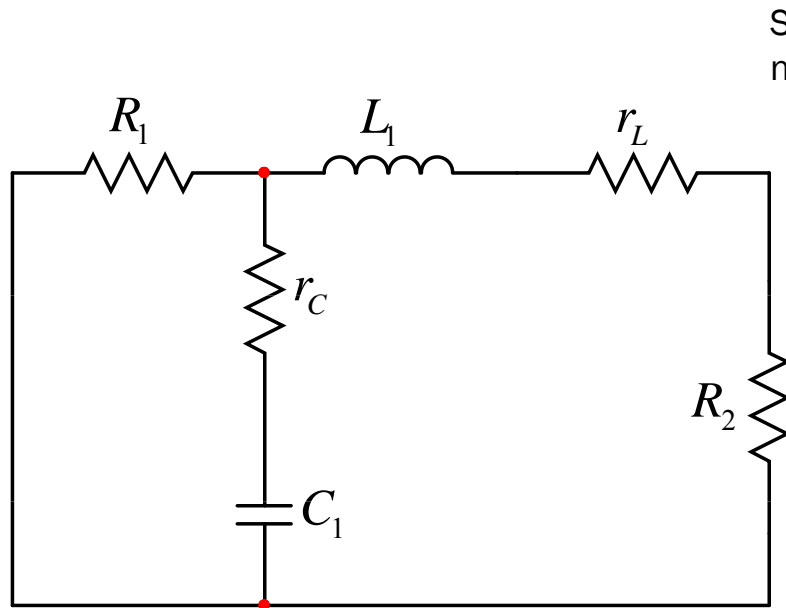- Time constants are part of the network structure



Natural network structure


Set V_{in} to 0 V:
no change

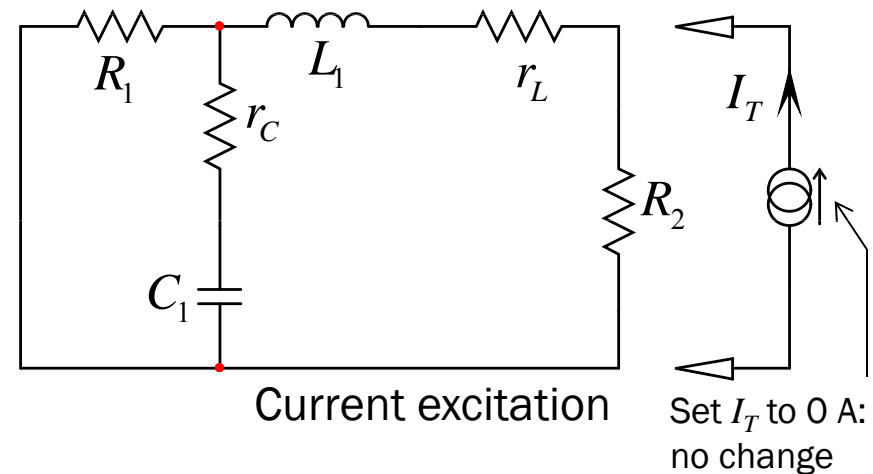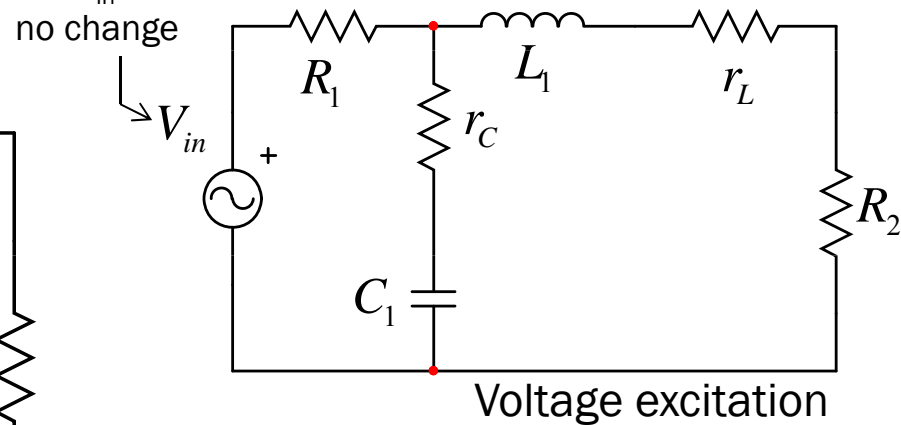

- When excitation is off, the structure remains the same


Does Excitation Change the Structure?

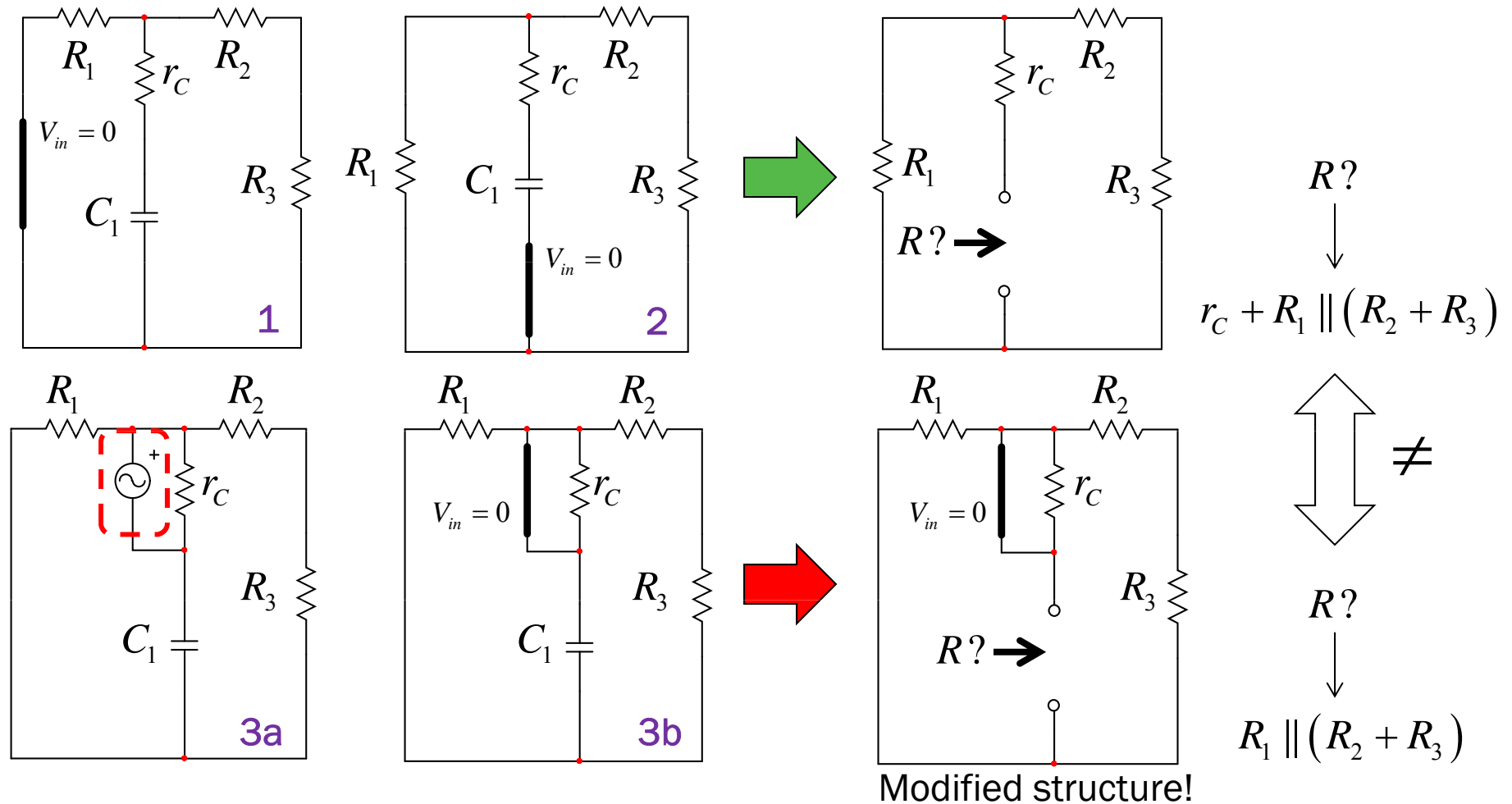❑ The time constant does not change for $V_{in} = 0$ V




Probing Does not Affect Time Constants

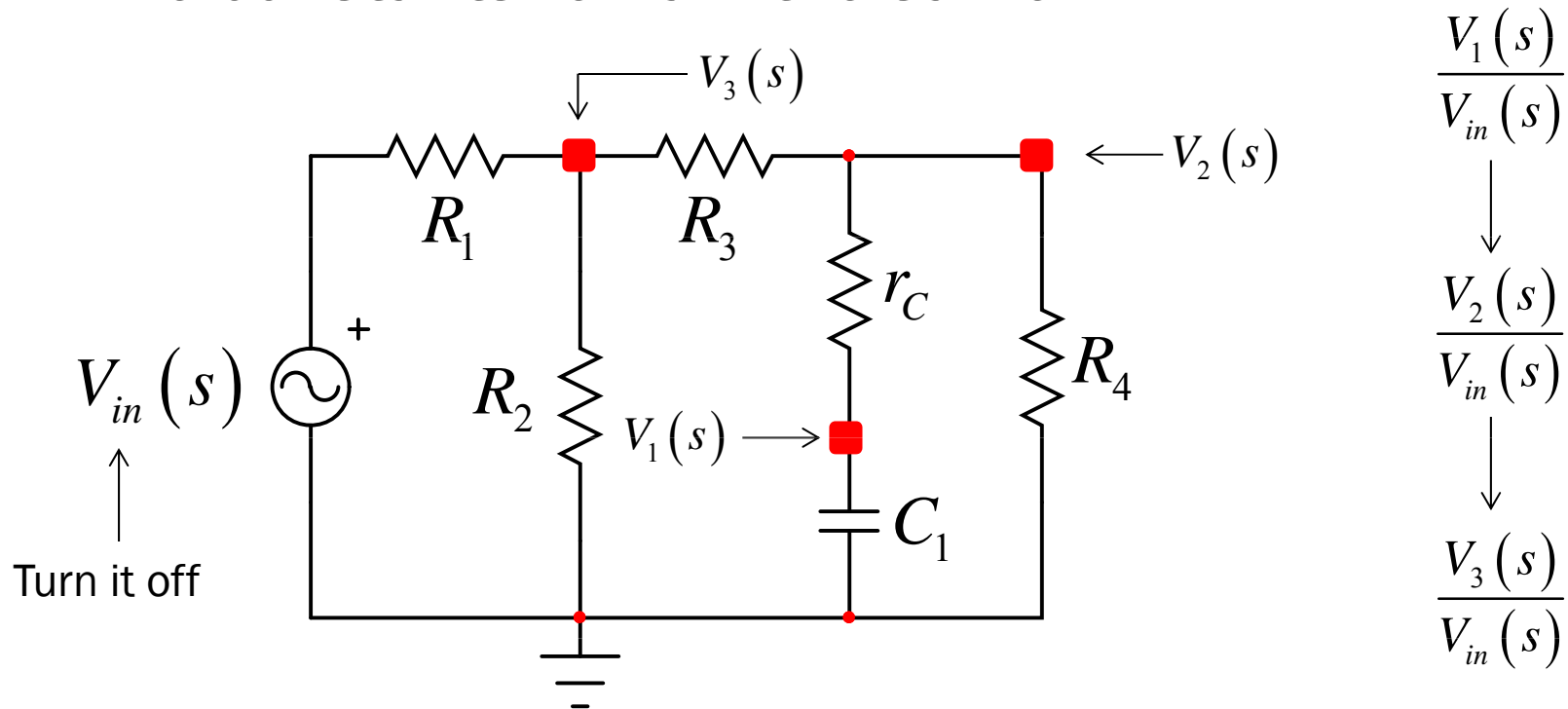- You can observe the response at any place
- ❖ Time constants remain the same



$$\frac{V_1(s)}{V_{in}(s)} \rightarrow \frac{V_2(s)}{V_{in}(s)} \rightarrow \frac{V_3(s)}{V_{in}(s)}$$

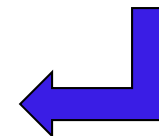- The resistance seen by C_1 is the same!



Denominator and Time Constants

- The response of a SISO system is given by:

$$y(t) = r_n(t) + r_f(t) = \sum_{i=1}^n C_i e^{p_i t} + r_f(t)$$

C are the exponential terms coefficients

n is the system order

p are the poles of the systems

- Assume the following 3rd-order transfer function:

$$H(s) = \frac{N(s)}{D(s)} = \frac{\left[(s+2)^2 + 4 \right] s - 1}{\left[(s+1)^2 + 1 \right] s + 3} \quad H(0) = \frac{\left[(2)^2 + 4 \right] (-1)}{\left[(1)^2 + 1 \right] 3} = -\frac{4}{3}$$

3rd order denominator, 3 poles: $p_3 = -3$ $p_{1,2} = \pm j - 1$

SISO: single-output single-input



SISO Response to a Step Input

- Multiply the transfer function by a step input

$$Y(s) = \frac{1}{s} H(s) \longrightarrow \begin{array}{c} 1\text{ V} \\ \text{---} \\ 0 \end{array}$$


- Extract the time-domain response

$$\mathcal{L}_s^{-1}\{Y(s)\} = y(t) = \underbrace{\frac{4}{3} e^{-3t} + \cos(t) e^{-1t} + 3 \sin(t) e^{-1t}}_{r_n(t)} - \underbrace{\frac{4}{3}}_{r_f(t)}$$


- Poles appear in the exponential power terms

Poles and Natural Time Constants

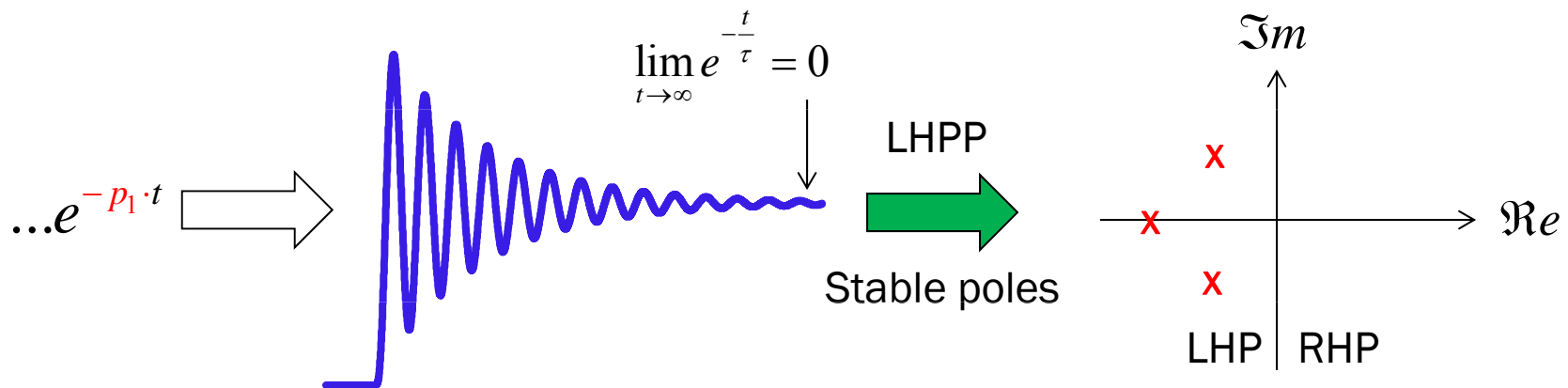- A negative sign implies a decaying term



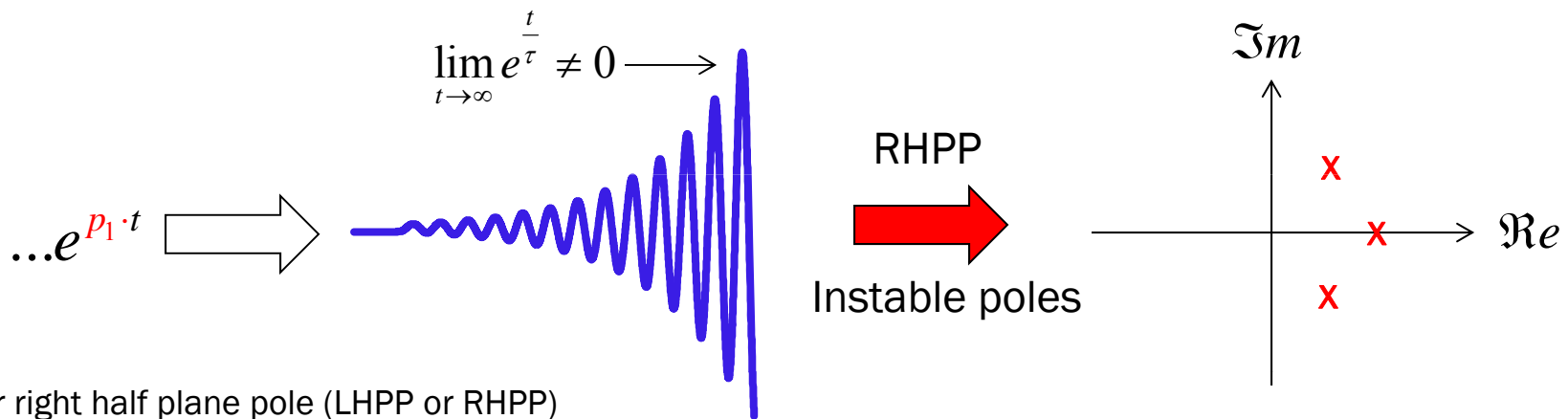
- A positive sign means it is an increasing term



Left or right half plane pole (LHPP or RHPP)


Time Constant and Pole – 1st Order

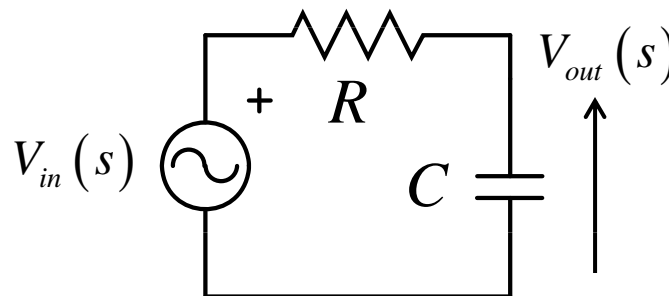□ In 1st-order systems, a pole is the inverse of the time constant



A circuit diagram showing an input voltage source $V_{in}(s)$ connected in series with a resistor R and a capacitor C . The output voltage $V_{out}(s)$ is measured across the capacitor. A blue arrow points from the circuit to the transfer function.
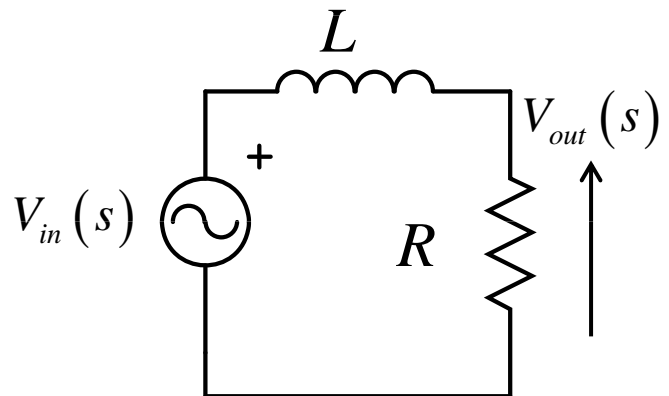
$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + sRC} = \frac{1}{1 + s\tau} = \frac{1}{1 + \frac{s}{\omega_p}}$$
$$\omega_p = \frac{1}{RC} = \frac{1}{\tau}$$




A circuit diagram showing an input voltage source $V_{in}(s)$ connected in series with an inductor L and a resistor R . The output voltage $V_{out}(s)$ is measured across the resistor. A blue arrow points from the circuit to the transfer function.


$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + s\frac{L}{R}} = \frac{1}{1 + s\tau} = \frac{1}{1 + \frac{s}{\omega_p}}$$
$$\omega_p = \frac{R}{L} = \frac{1}{\tau}$$

Determining the Time Constant

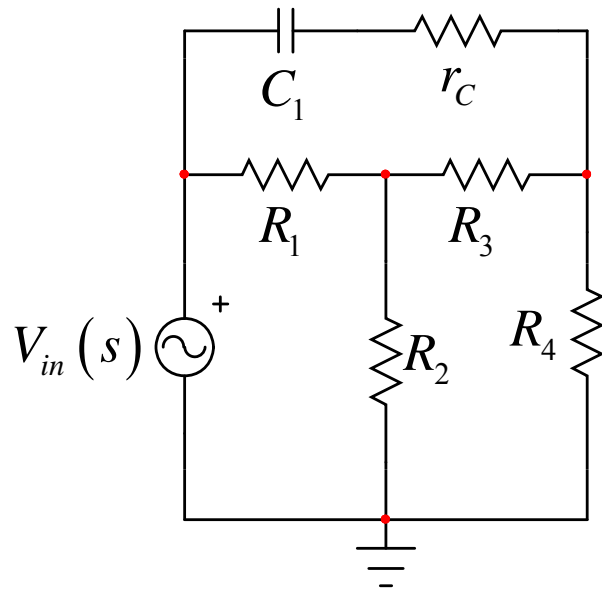- Find the time constant to obtain the pole



Set V_{in}
to 0 V

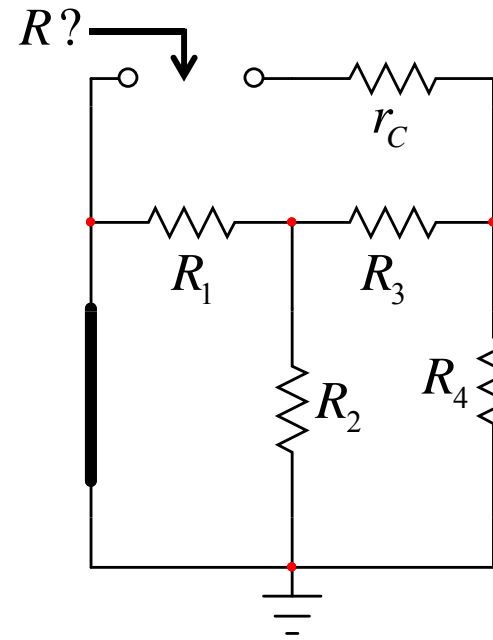


$$\tau = C_1 \left[r_c + (R_1 \parallel R_2 + R_3) \parallel R_4 \right]$$

$$D(s) = 1 + s\tau = 1 + \frac{s}{\omega_p}$$

$$\omega_p = \frac{1}{C_1 \left[r_c + (R_1 \parallel R_2 + R_3) \parallel R_4 \right]}$$

Same Denominator for Z_{out}

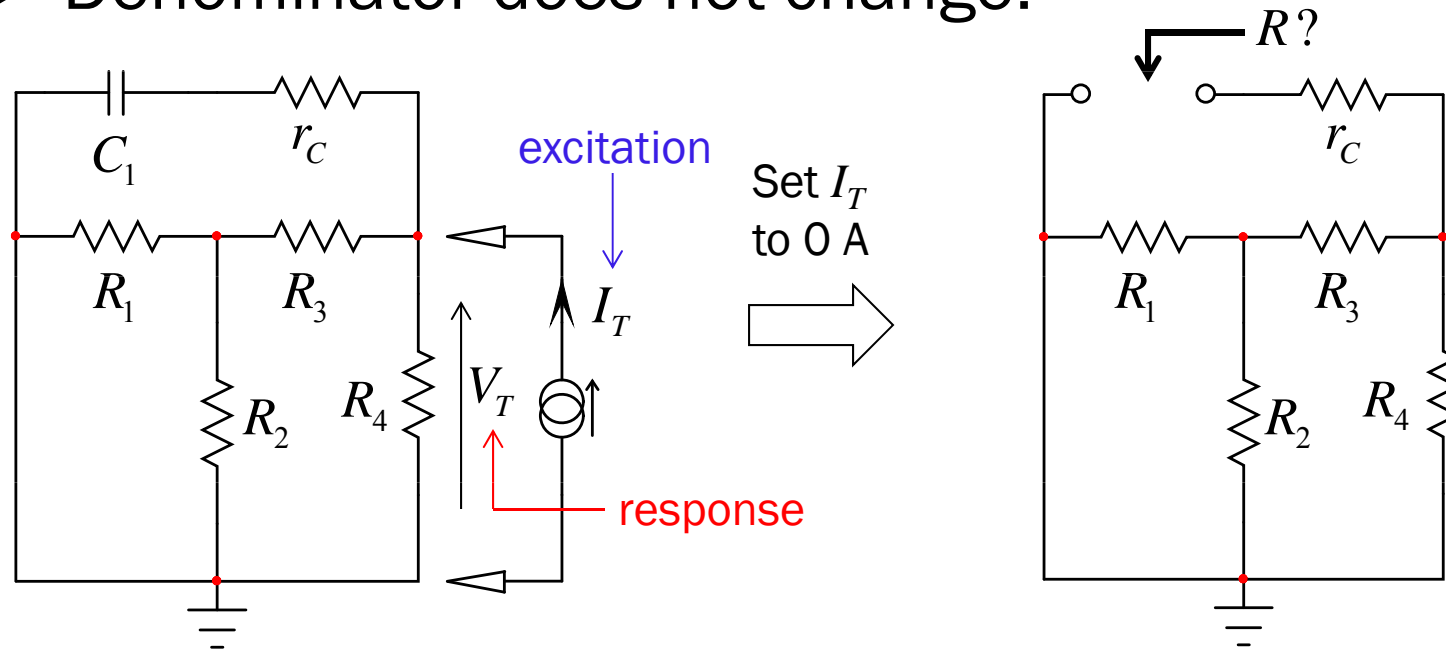- ❑ A current generator does not alter the structure
- Denominator does not change!




- ❑ Transfer function keeps the same denominator

$$D(s) = 1 + sC_1 \left[r_c + (R_1 \parallel R_2 + R_3) \parallel R_4 \right]$$

Denominator Changes for Z_{in}

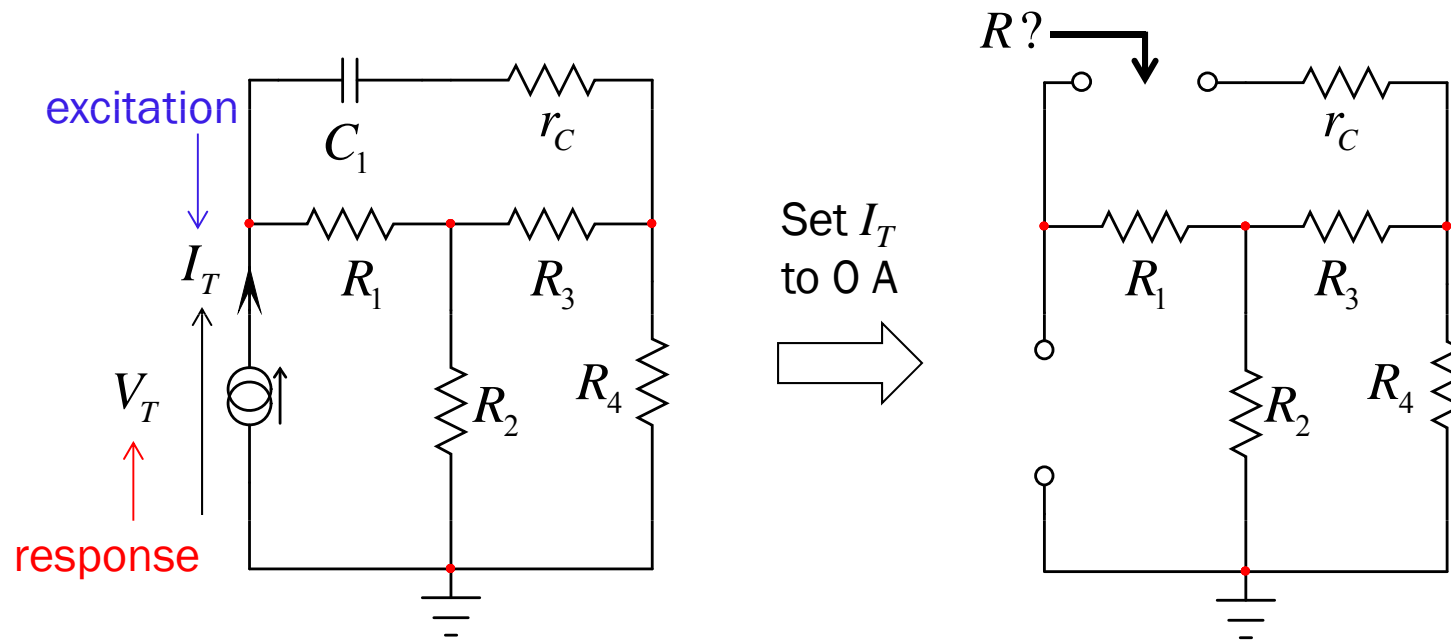- Series insertion of current source alters the structure





- Time constant is changed, cannot reuse $D(s)$

$$\tau = C_1 \left[r_C + R_1 + R_3 \parallel (R_2 + R_4) \right] \quad \omega_p = \frac{1}{C_1 \left[r_C + R_1 + R_3 \parallel (R_2 + R_4) \right]}$$

Find the Time Constants

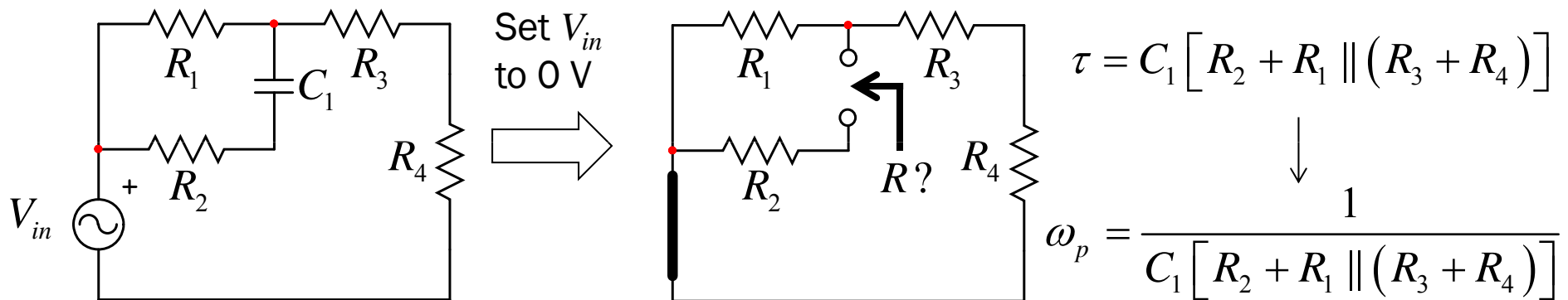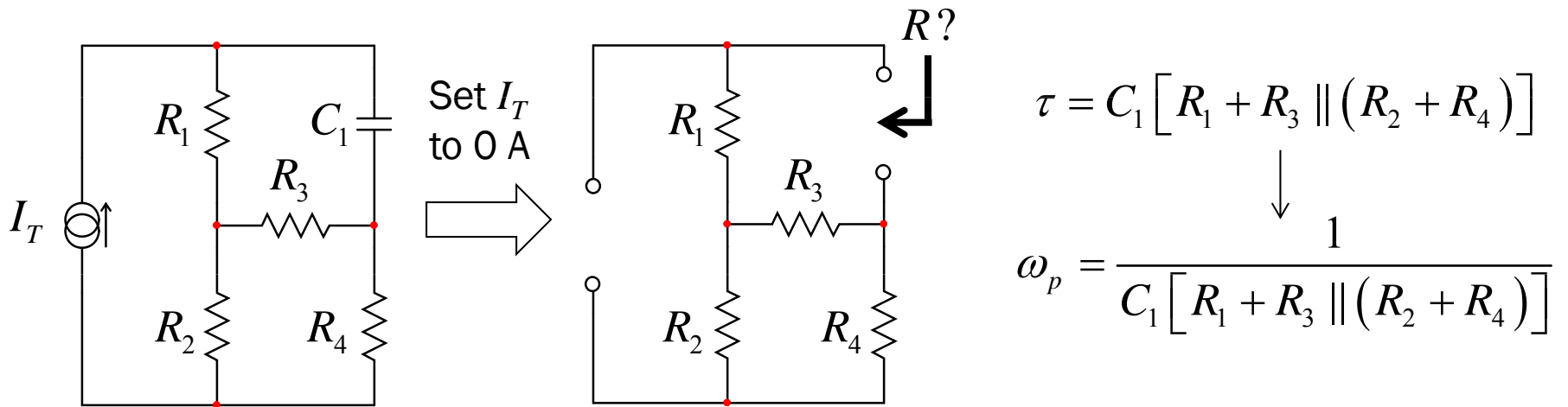□ Find the time constants when excitation is set to 0




Course Agenda

- What is a Transfer Function?
- Why do We Need New Analytical Techniques?
- Time Constants and Poles
- Identifying the Zeros**
- The Null Double Injection
- 2nd-Order Networks
- The PWM Switch Model
- A CCM Buck in Voltage Mode
- A CCM Buck-Boost in Voltage Mode



Zero: the Mathematical Definition

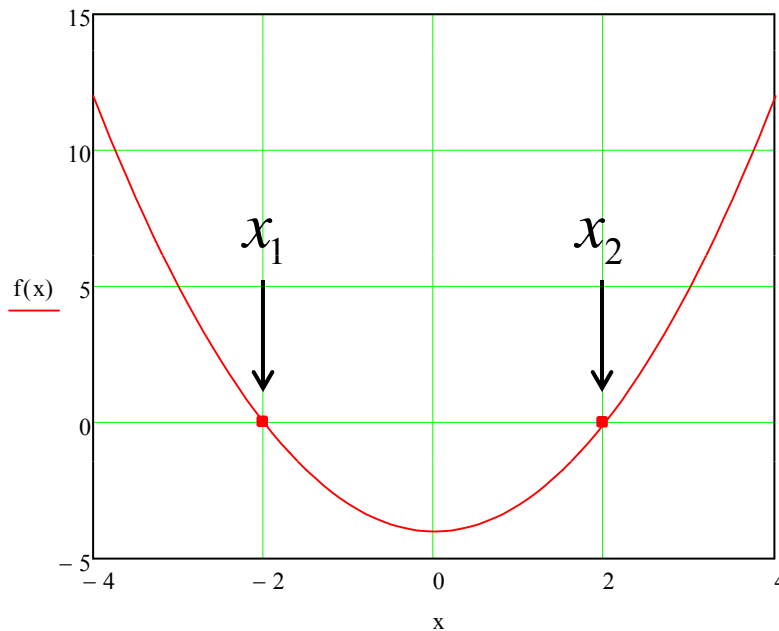- A zero is the root of the equation $f(x) = 0$



$$f(x) = x^2 - 4$$

$$f(x) = 0$$



$$x_1 = -2$$

$$x_2 = 2$$

- Transfer function zeros are the numerator roots

$$N(s) = 0 \longrightarrow s_{z_1}, s_{z_2} \dots$$

Nulling the Response

- If the numerator is 0, then the response is also 0




- What is happening in the box when $s = s_z$?


➔ The excitation does not generate a response

How Does the Response Disappear?

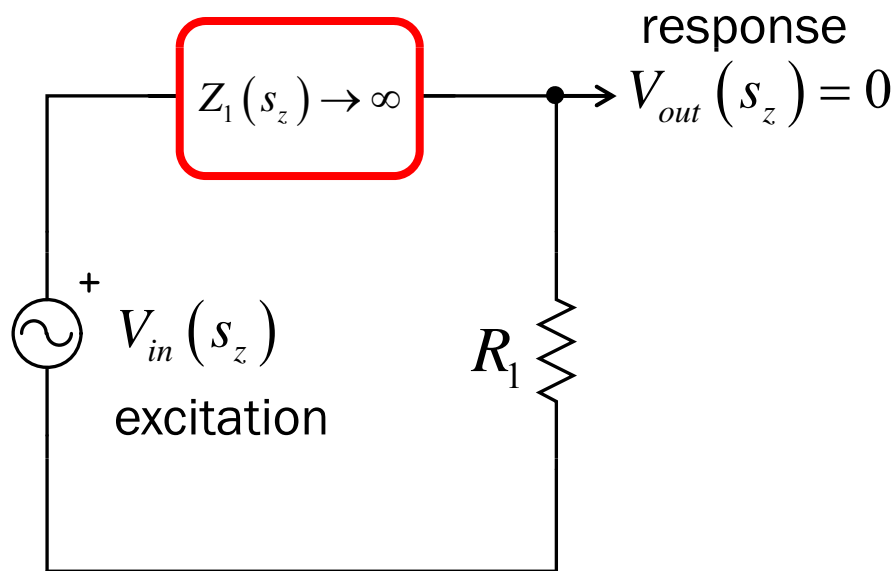- The signal is lost in the *transformed* network



A series impedance becomes infinite.

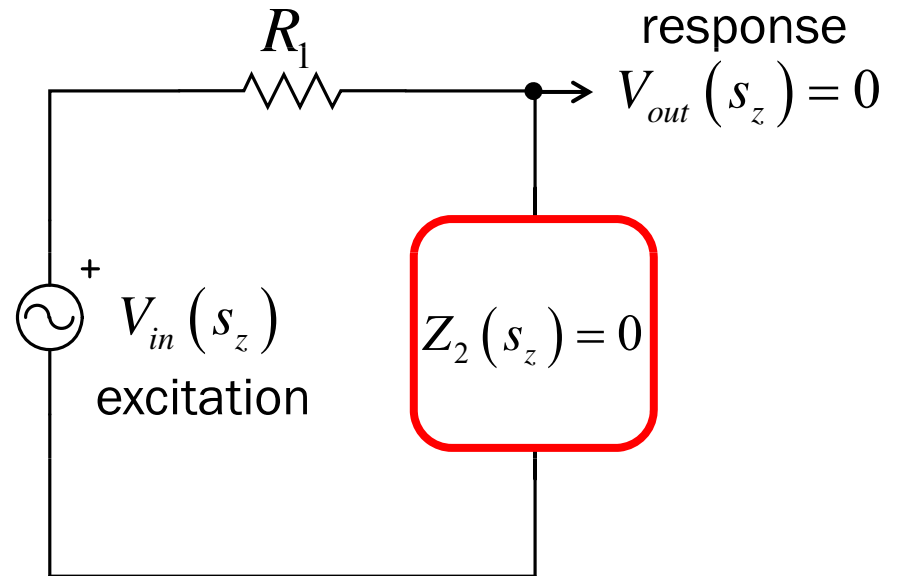


A parallel impedance shorts the path to ground

- What is a *transformed* network?

The Transformed Network

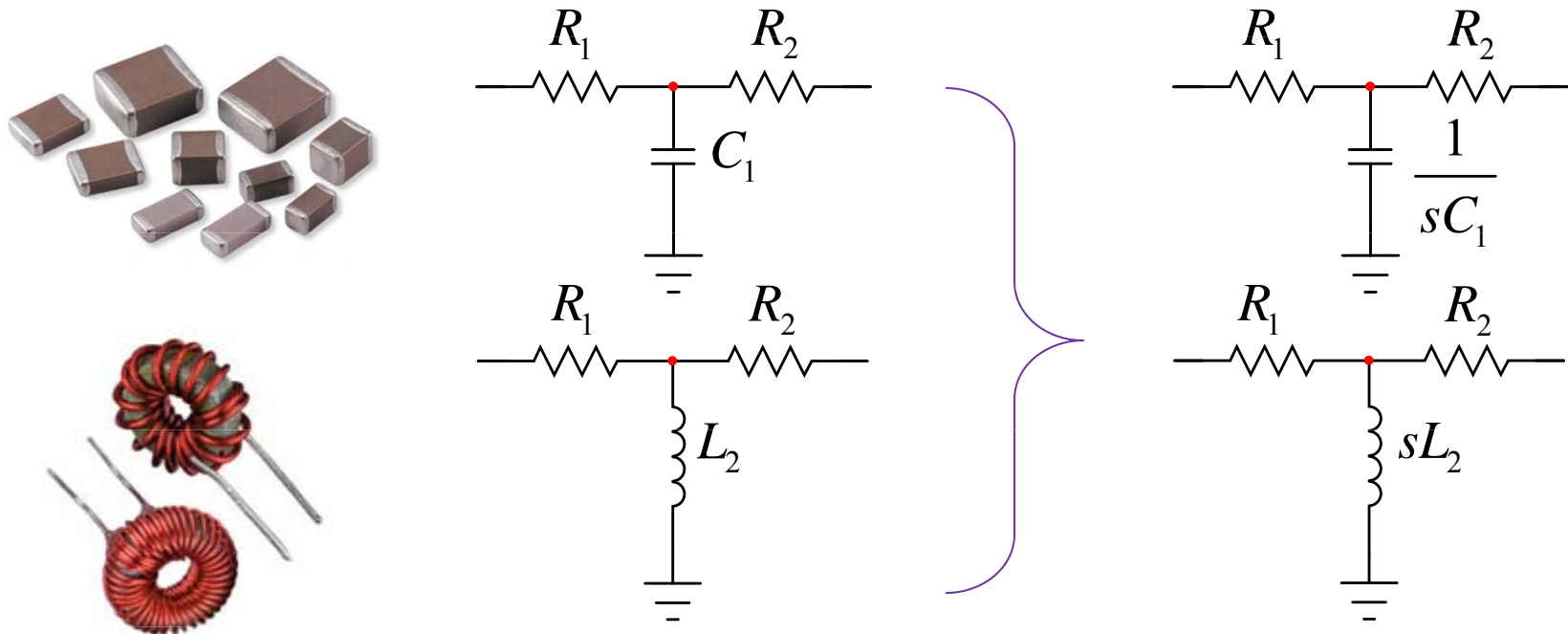
- Reactances are replaced by their Laplace expression



- The circuit is then observed at the zero frequency


Harmonic Analysis

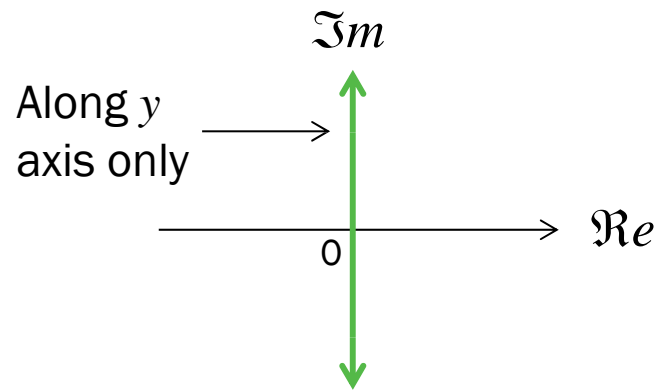- Harmonic analysis is performed for $s = j\omega$



- ❖ imaginary frequencies only
- ❖ no real negative frequencies

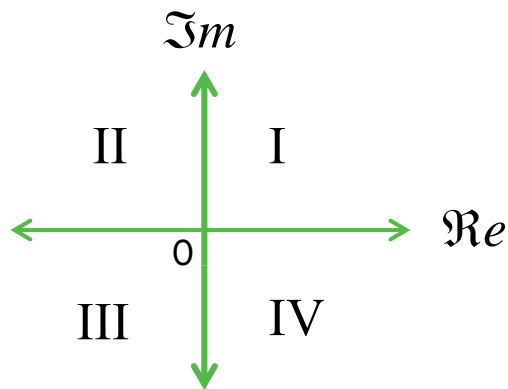- In the transformed network, consider $s = \sigma + j\omega$




The four quadrants are considered!

- ❖ negative angular frequencies
- ❖ real or imaginary ang. frequencies


- There is no physical meaning: mathematical abstraction!

Considering a Negative Frequency

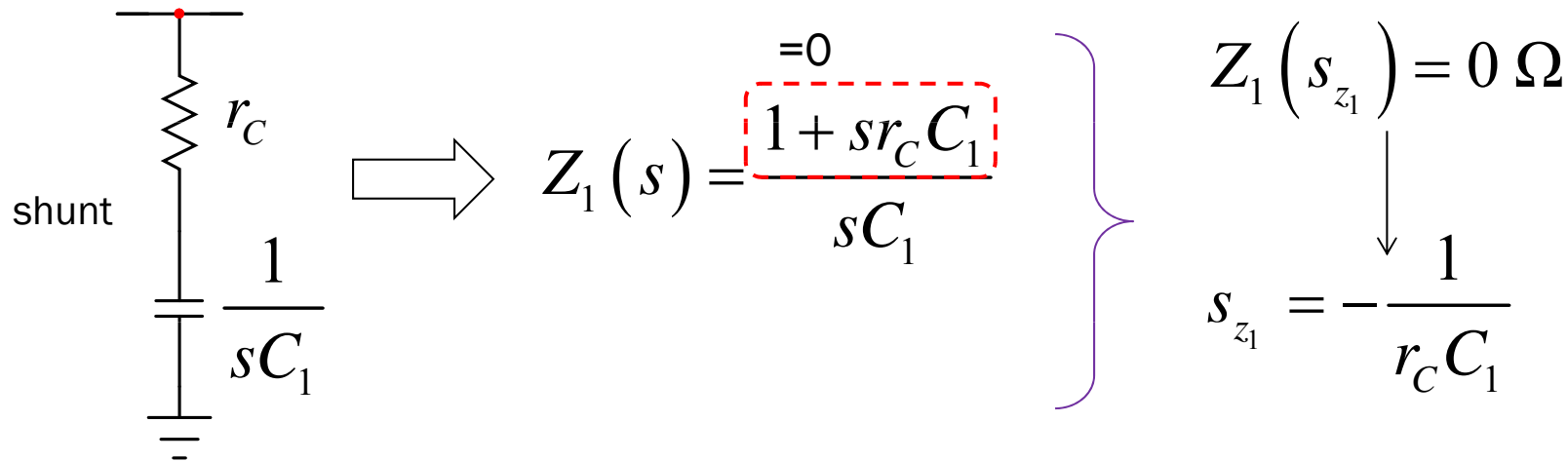- For $s = s_{z1}$, the RC impedance is a short circuit




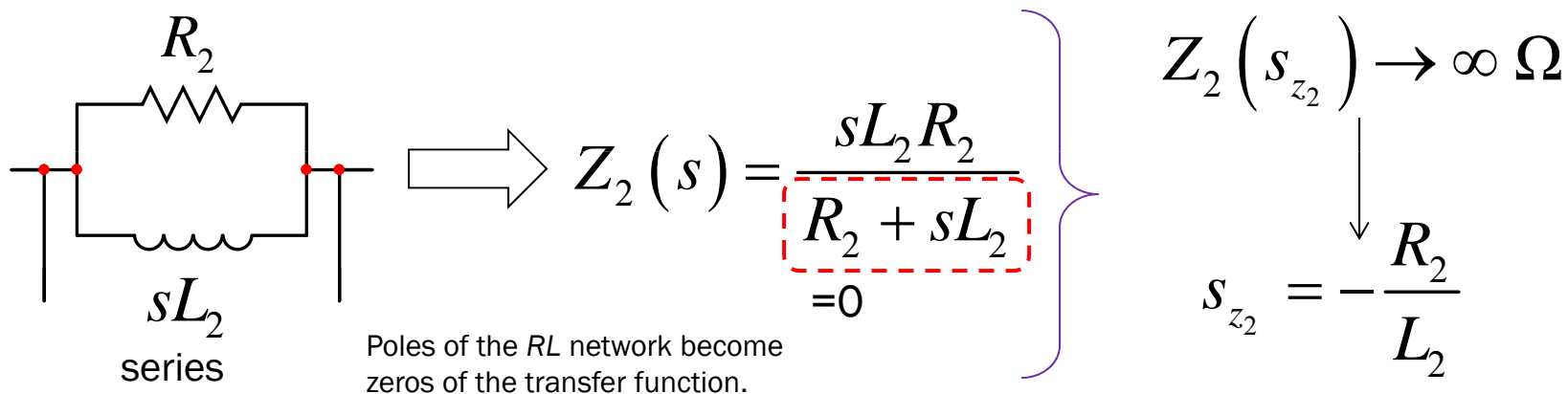
- For $s = s_{z2}$, the RL impedance is infinite



Zeros by Inspection

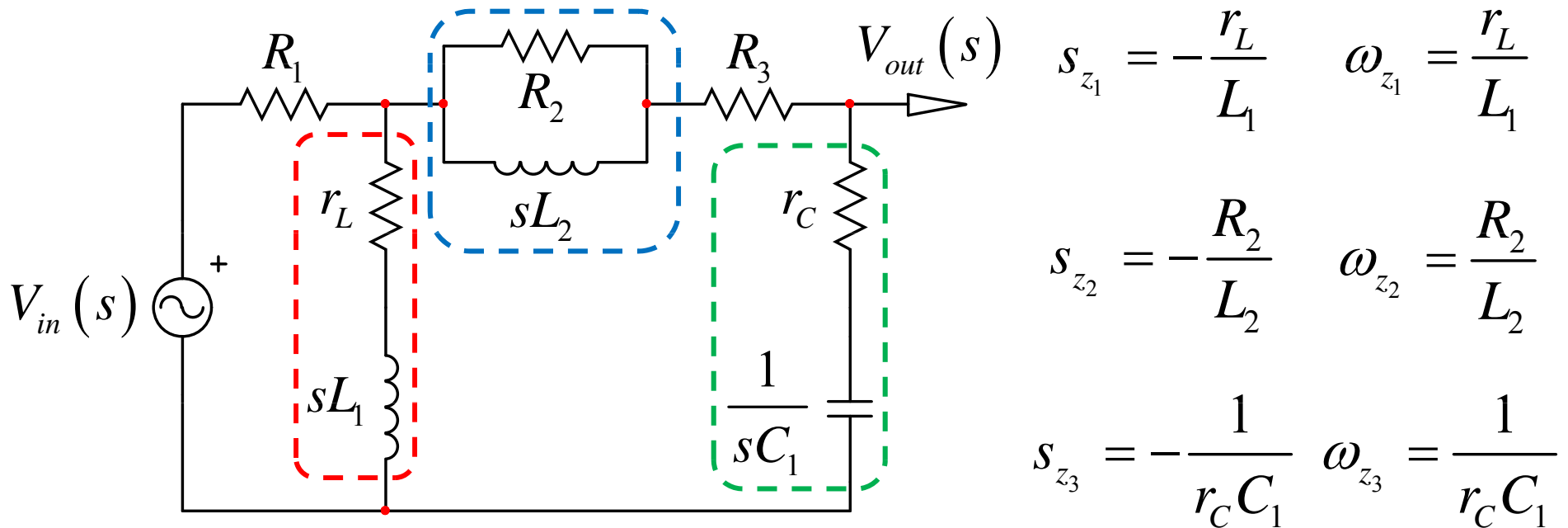- Identify *transformed* open circuits/short circuits






$$N(s) = \left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 + \frac{s}{\omega_{z_2}}\right) \left(1 + \frac{s}{\omega_{z_3}}\right)$$

No equations!




A Zero in the Laboratory


❑ Can you observe a zero in the lab?



$T = 2\pi r_C C_1$

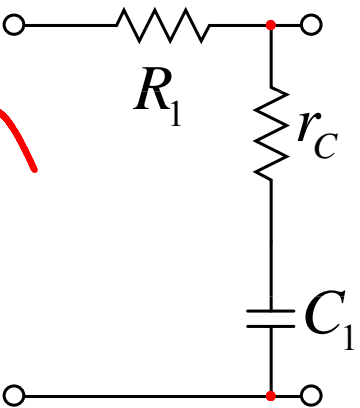



response is non-zero

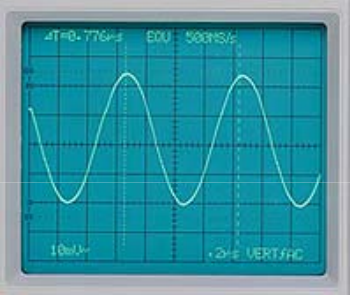

❑ No, because this is a harmonic analysis $s = j\omega$

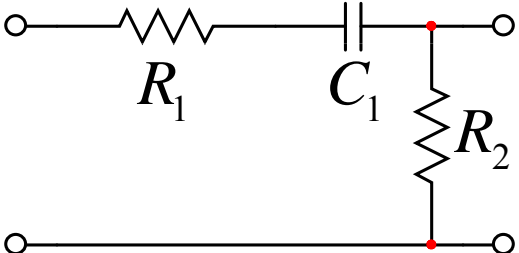
✓ It works for a zero at the origin: dc block




$V_{out}(0 \text{ Hz}) = 0 \text{ V}$

A Notch Truly Nulls the Response

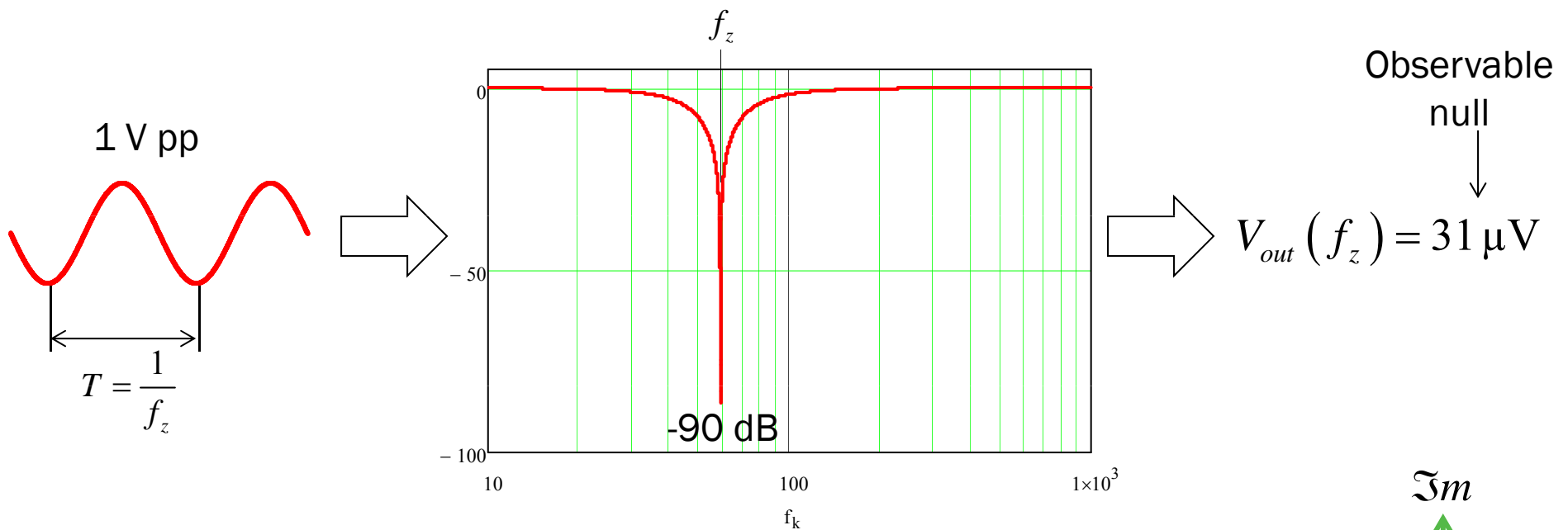- When Q approaches infinity, zeros become imaginary




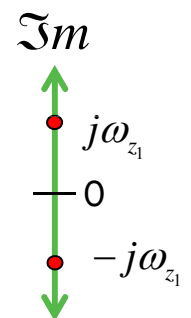- Build a high- Q notch and you can observe the null
- Roots are along the y axis: harmonic analysis



Find the Zeros by Inspection

□ When does the response disappear?

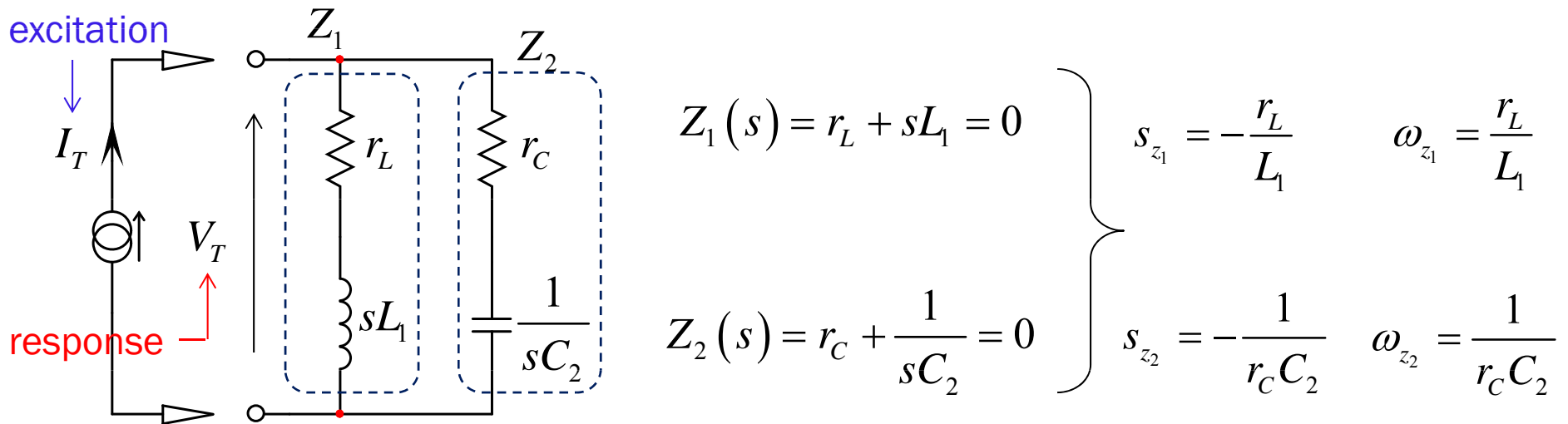

□ The numerator is obtained without algebra

$$N(s) = \left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 + \frac{s}{\omega_{z_2}}\right)$$



Inspection gives the simplest expressions


Course Agenda

- What is a Transfer Function?
- Why do We Need New Analytical Techniques?
- Time Constants and Poles
- Identifying the Zeros
- The Null Double Injection**
- 2nd-Order Networks
- The PWM Switch Model
- A CCM Buck in Voltage Mode
- A CCM Buck-Boost in Voltage Mode




The Null Double Injection

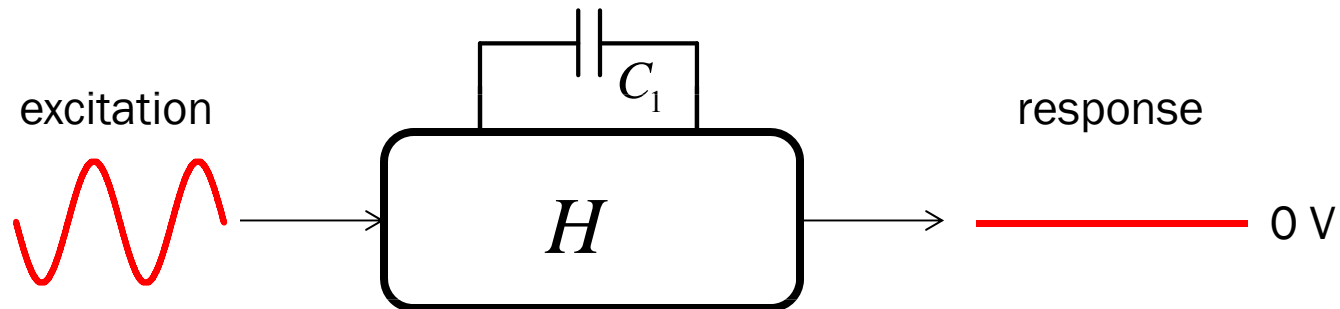- A null implies an injection but no response



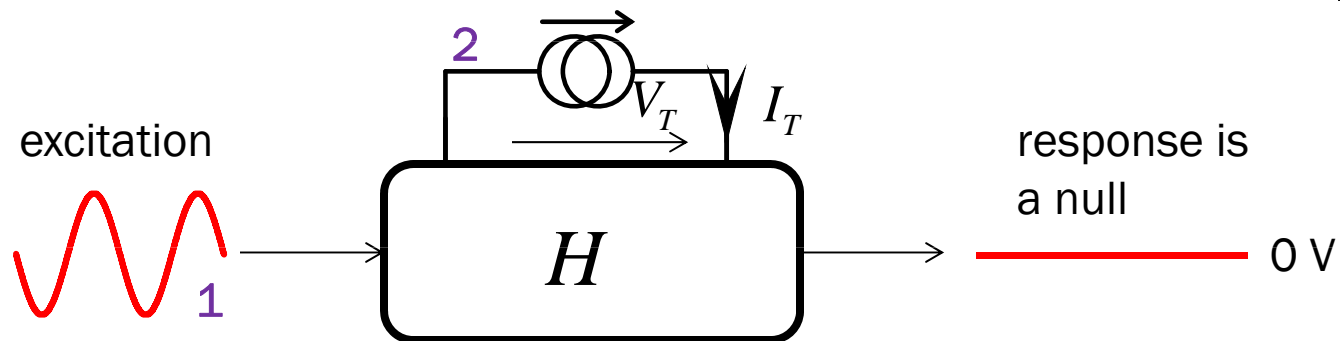
- What is the time constant in this mode? $\tau = \frac{V_T}{I_T} C_1$



- Double injection with a nulled response (NDI)

What is a Null in the Response?

- No current circulates in the load

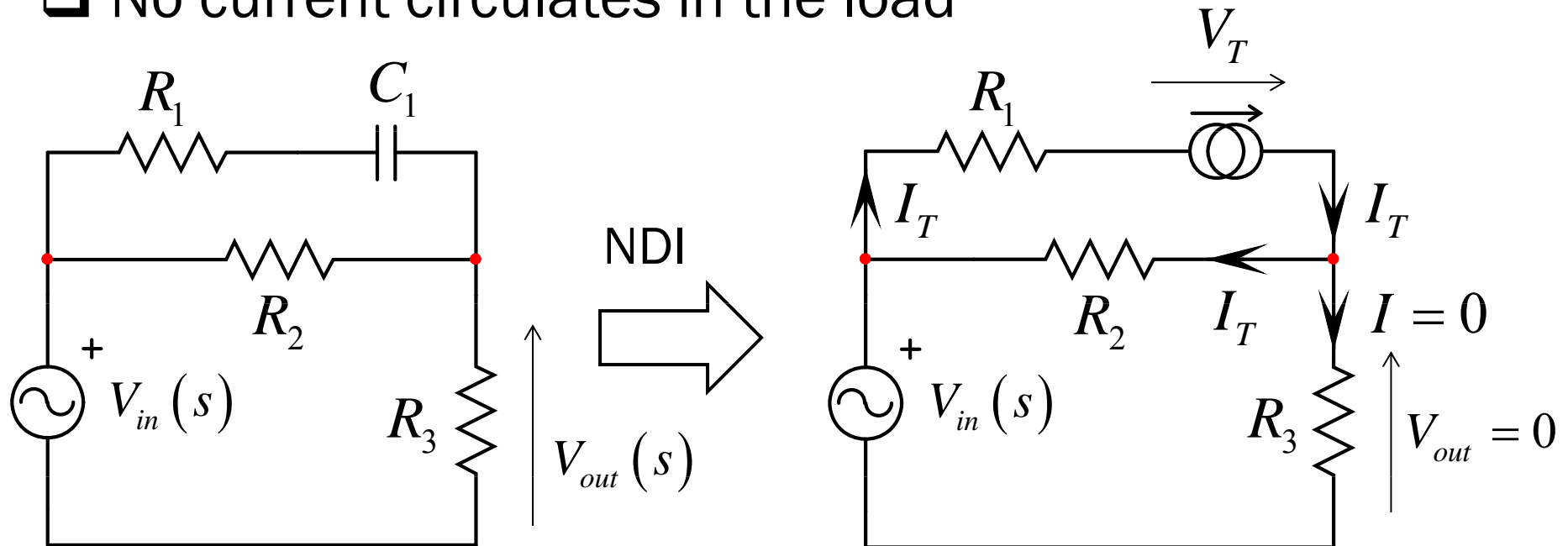


- In this configuration, the resistance is $R_1 + R_2$

➔ $\tau = (R_1 + R_2)C_1$ and $N(s) = 1 + s(R_1 + R_2)C_1$

Does it Have a Physical Meaning?

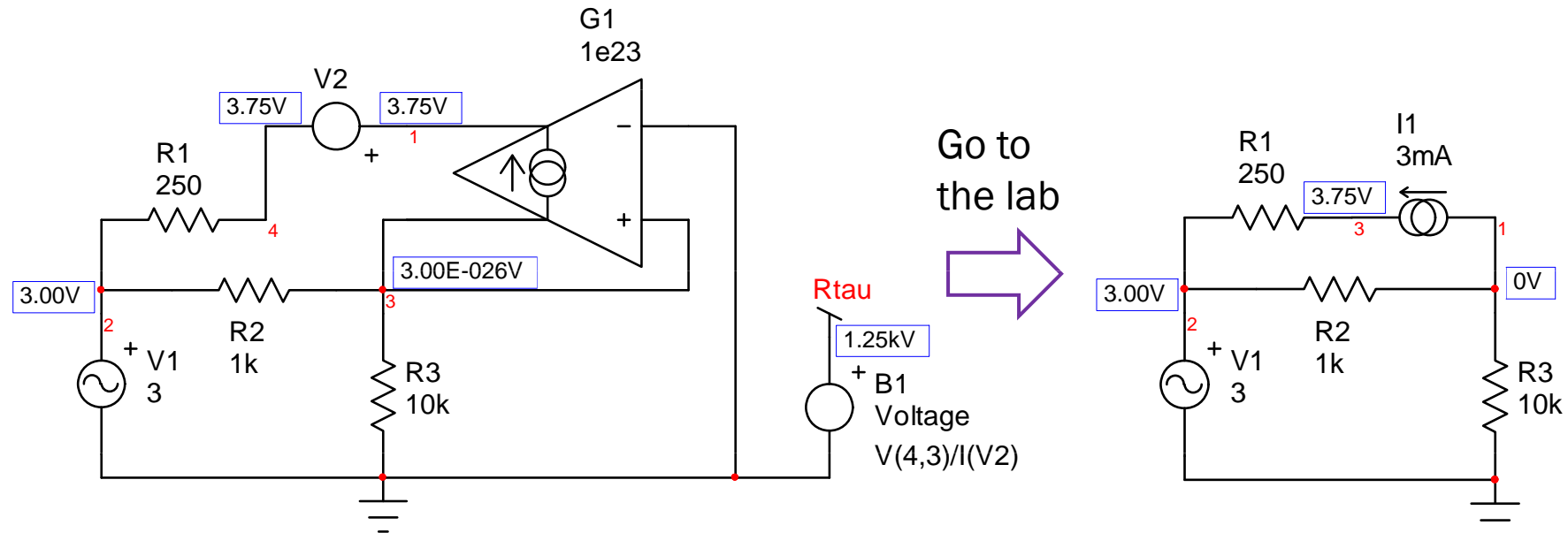- A certain combination of V and I cancels the response




- The current source G_1 adjusts to set V_{out} to 0 V: NDI

$$\rightarrow R = \frac{V_T}{I_T} = \frac{3.75 \text{ V}}{3 \text{ mA}} = 1250 \Omega \longrightarrow R_1 + R_2$$

Inspection Would Work Here as Well

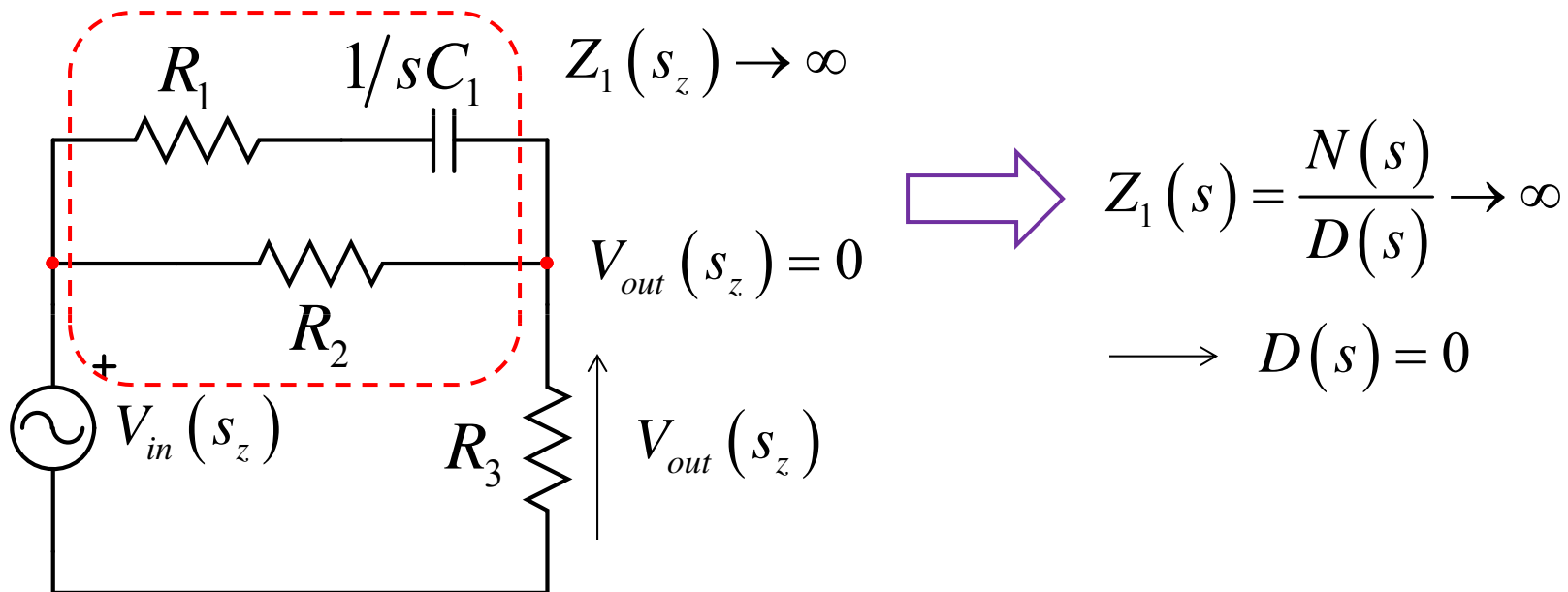- ❑ What prevents the excitation from building a response?




- ❑ What is the denominator of Z_1 ? Look at R driving C_1

$$R = R_1 + R_2 \longrightarrow D(s) = 1 + sC_1(R_1 + R_2) \longrightarrow \omega_p = \frac{1}{C_1(R_1 + R_2)}$$


❖ Z_1 's pole is H 's zero

A Null is Not a Short Circuit

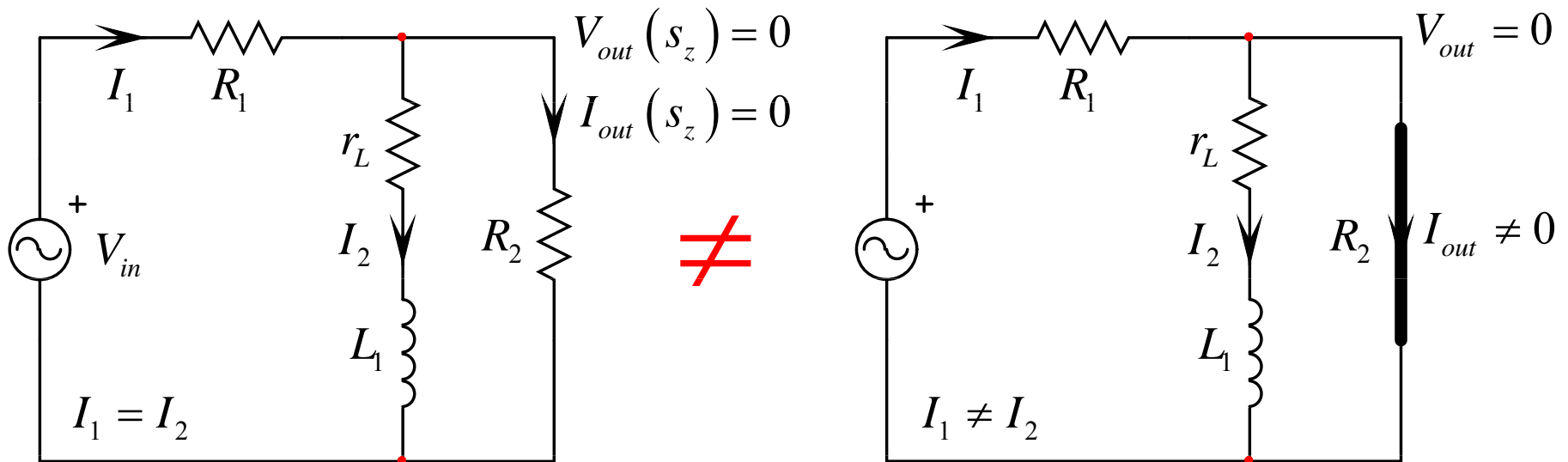- See the output null as a virtual ground: no short!




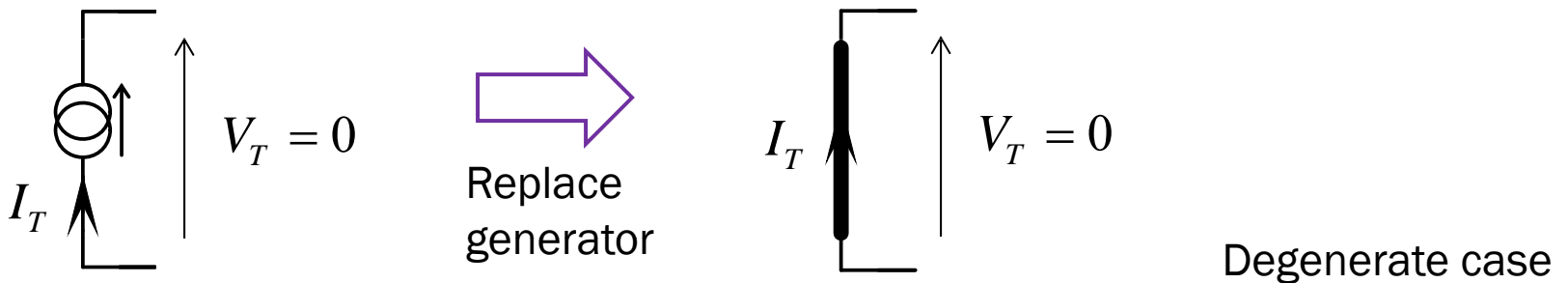- 0 V across a current generator is a true short circuit




Degenerate Case Applied to Impedance

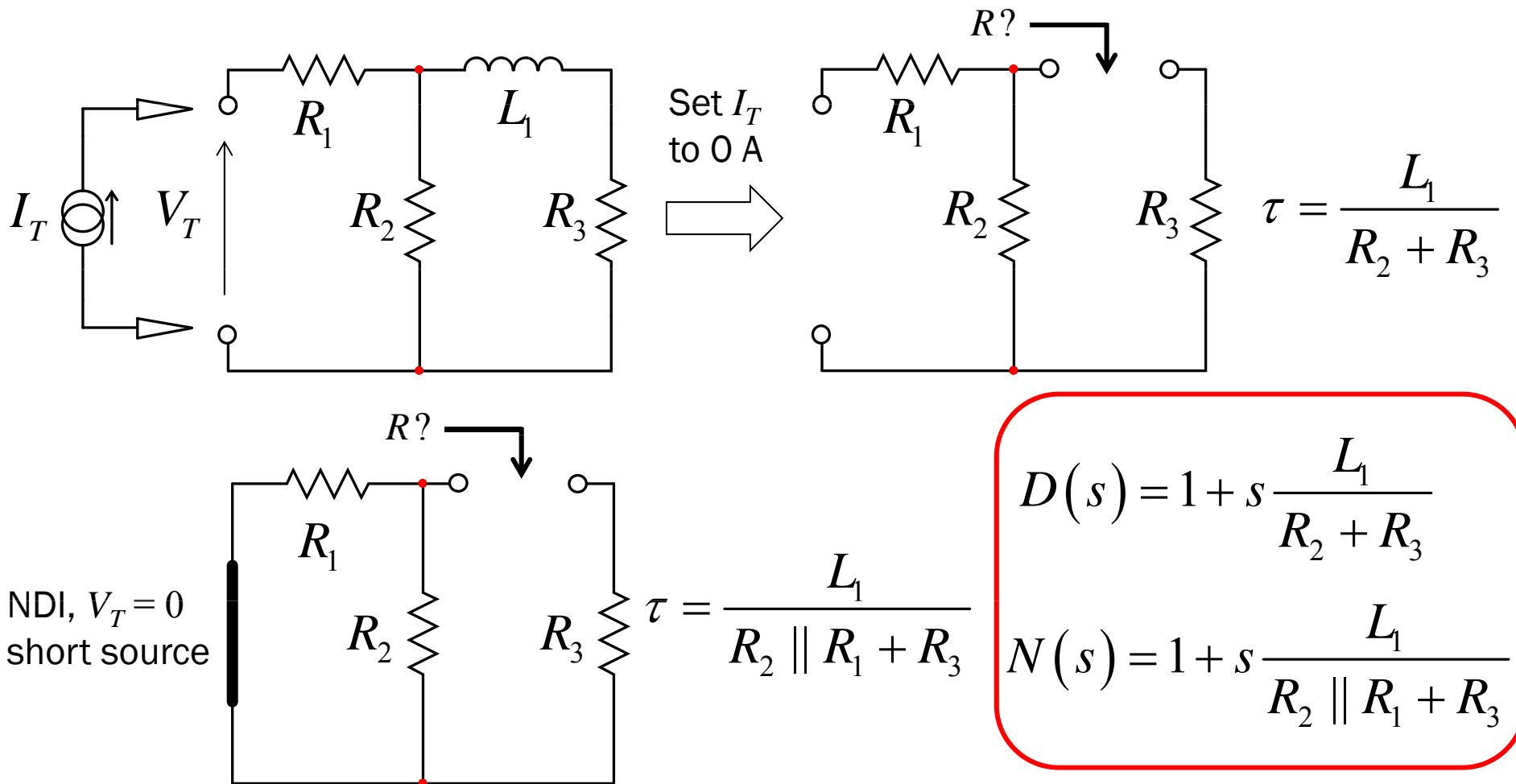- Determine the input impedance of this circuit



Three Steps for the Transfer Function

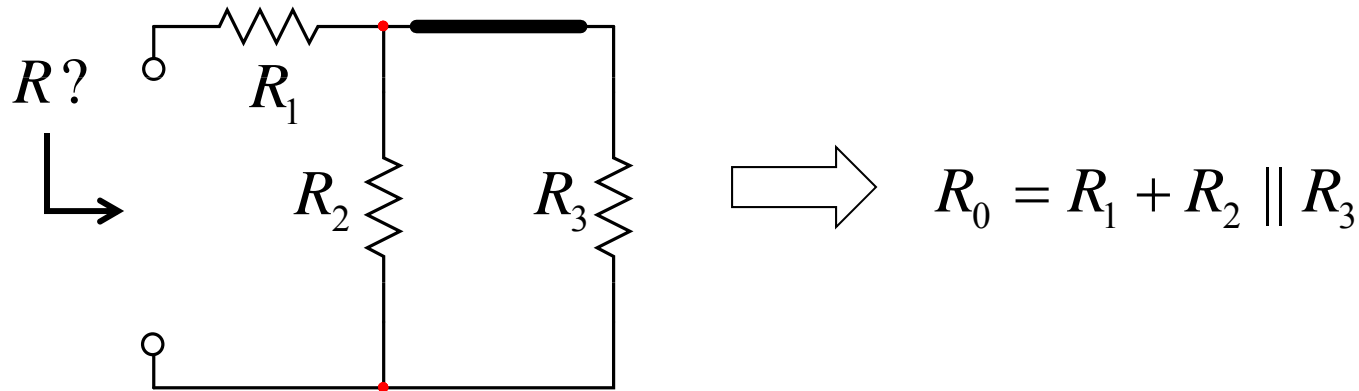- For $s = 0$, replace the inductor by a short circuit



- Result is well ordered and obtained without KVL/KCL

$$Z(s) = R_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \quad R_0 = R_1 + R_2 \parallel R_3 \quad \omega_p = \frac{R_2 + R_3}{L_1} \quad \omega_z = \frac{R_2 \parallel R_1 + R_3}{L_1}$$

Summary for 1st-order Systems - I

- Observe the circuit for $s = 0$
 - ❖ short inductor, open capacitor
 - ✓ You have H_0

- Turn the excitation off
 - ❖ voltage source is replaced by a short circuit
 - ❖ current source is open-circuited

- Remove the energy storage element
- Determine the resistance R_D looking into its terminals

⇒ $\tau_D = R_D C$ or $\tau_D = \frac{L}{R_D}$

Summary for 1st-order Systems - II

- ❑ Bring excitation source back in place
- ❑ Null the output, $V_{out} = 0$ V and $I_{out} = 0$ A
- ❑ Determine R_N driving the energy-storage component

$$\Rightarrow \tau_N = R_N C \quad \text{or} \quad \tau_N = \frac{L}{R_N}$$


- ❑ Combine time constants and dc gain

$$H(s) = H_0 \frac{1 + s\tau_N}{1 + s\tau_D} = H_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$

\Rightarrow If possible, use inspection: simplest possible form

What if dc Gain Does not Exist?

- If you have a series capacitor

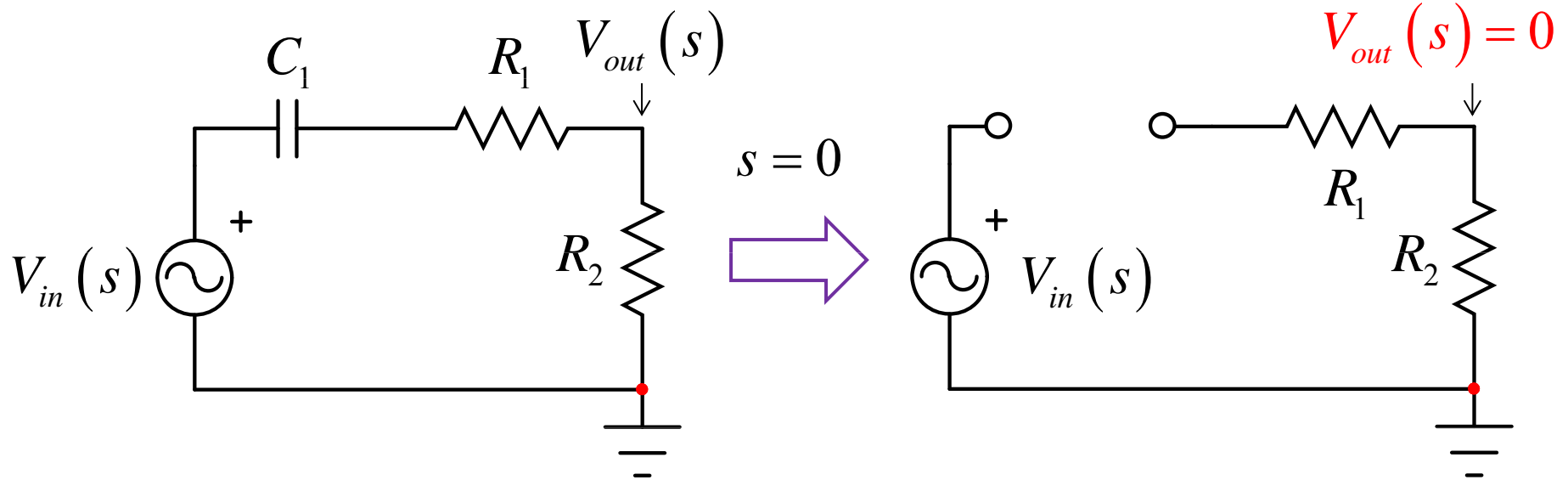


- The dc or quasi-static gain is 0


$$H_0 = 0 \quad \xrightarrow{\text{No longer applies}} \quad H(s) = H_0 \frac{1 + s\tau_N}{1 + s\tau_D}$$

Consider High-Frequency Model

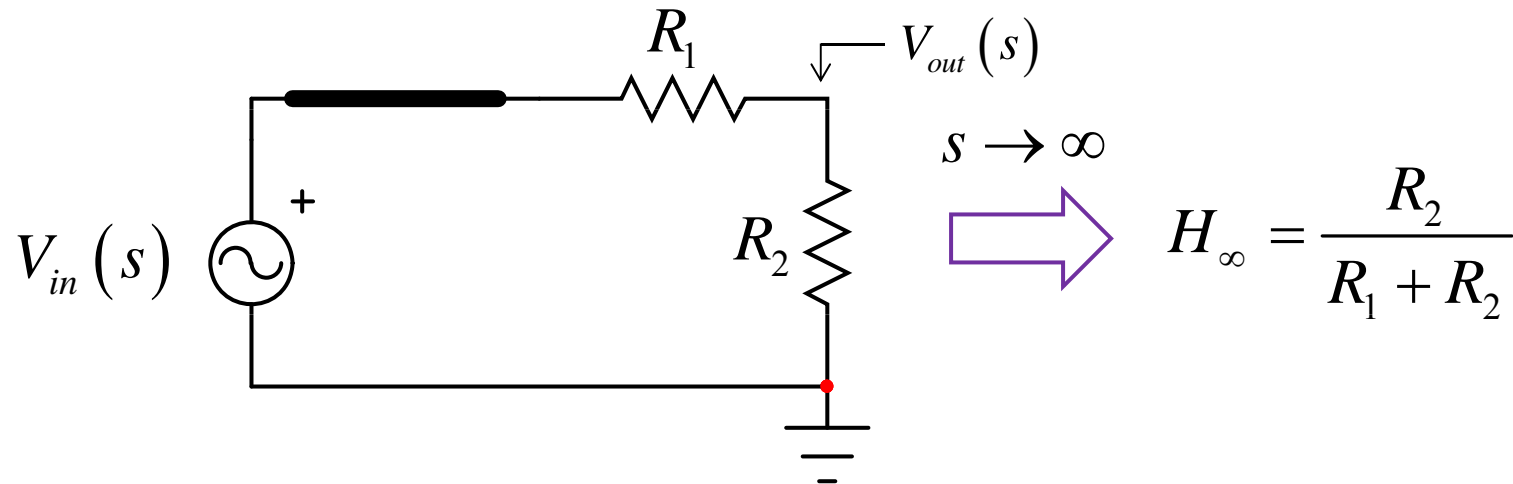- Rather than considering s at 0, consider $s \rightarrow \infty$




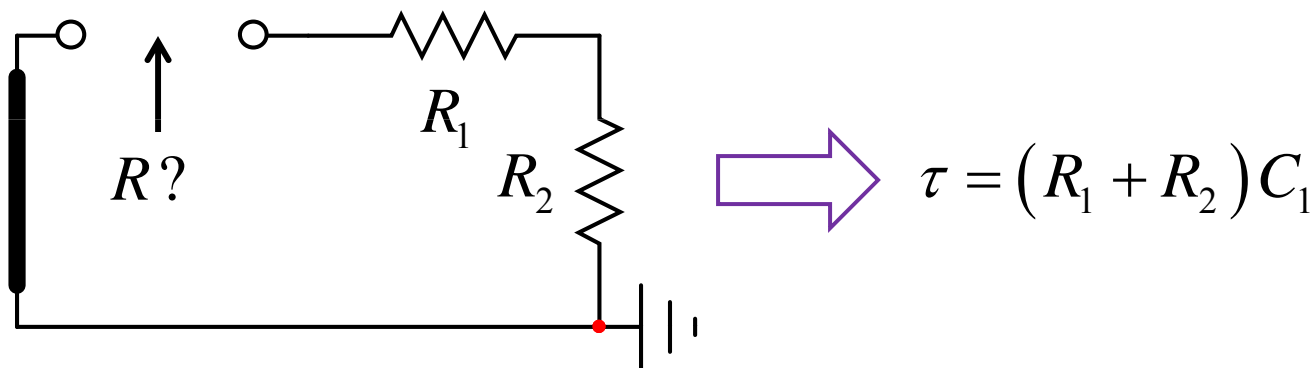- Look at the resistance driving C while excitation is off



Null the Response to Get the Zero

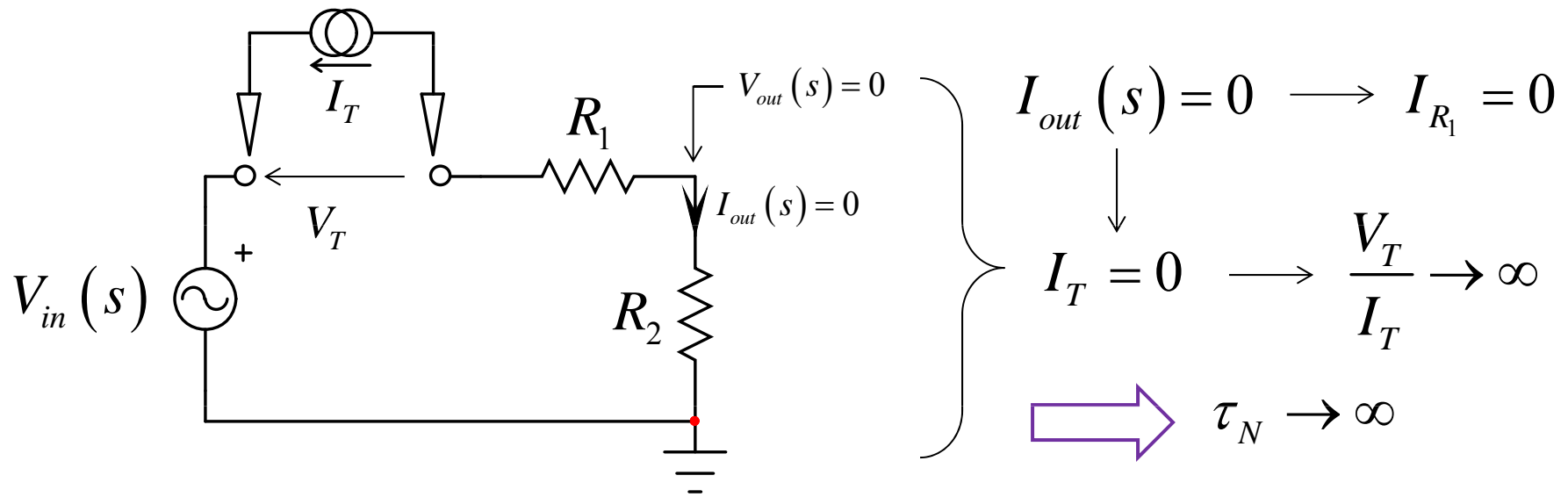□ Is there a zero other than at the origin?



□ We have a high-frequency gain and two time constants

$$H_\infty = \frac{R_2}{R_1 + R_2} \quad \tau_D = (R_1 + R_2)C_1 \quad \tau_N \rightarrow \infty$$

Two Formulas for the Same Function

□ The Extra Element Theorem shows that

$$H(s) = H_0 \frac{1 + s\tau_N}{1 + s\tau_D} \text{ is equivalent to } H(s) = H_\infty \frac{1 + \frac{1}{s\tau_N}}{1 + \frac{1}{s\tau_D}}$$

□ Time constants are similar in both expressions


$$H(s) = \frac{R_2}{R_1 + R_2} \frac{1 + \frac{1}{s \cdot \infty}}{1 + \frac{1}{sC_1(R_1 + R_2)}} = \frac{R_2}{R_1 + R_2} \frac{1}{1 + \frac{1}{sC_1(R_1 + R_2)}}$$

□ It is a low-entropy form featuring an inverted pole


R. D. Middlebrook, "Null Double Injection and the Extra Element Theorem", IEEE Transactions on Education, Vol. 32, NO. 3, August 1989.

Another Example

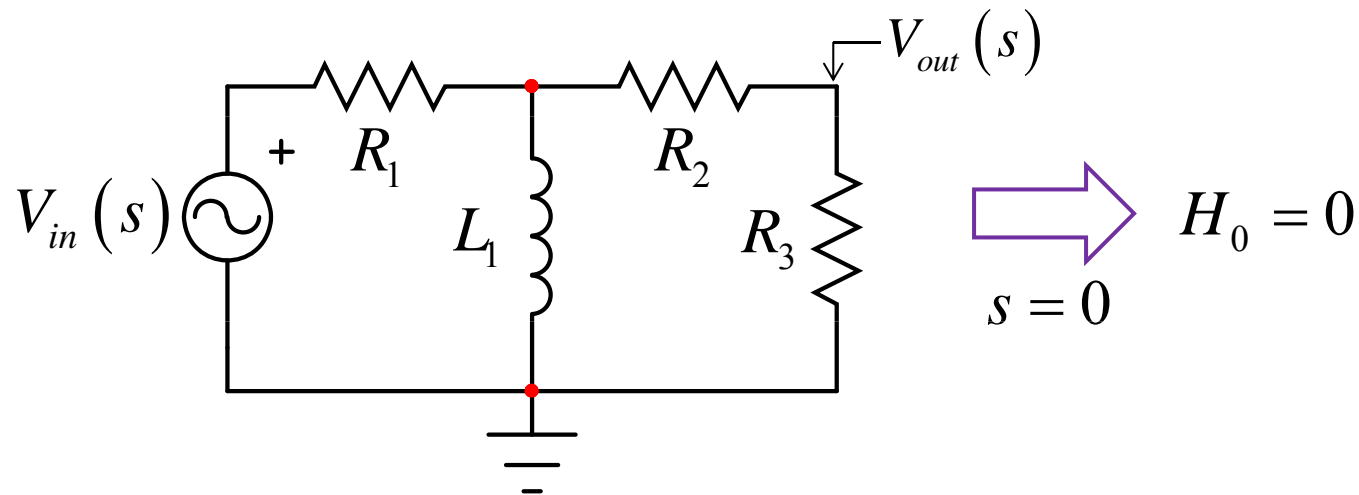- The inductance is a short circuit in dc





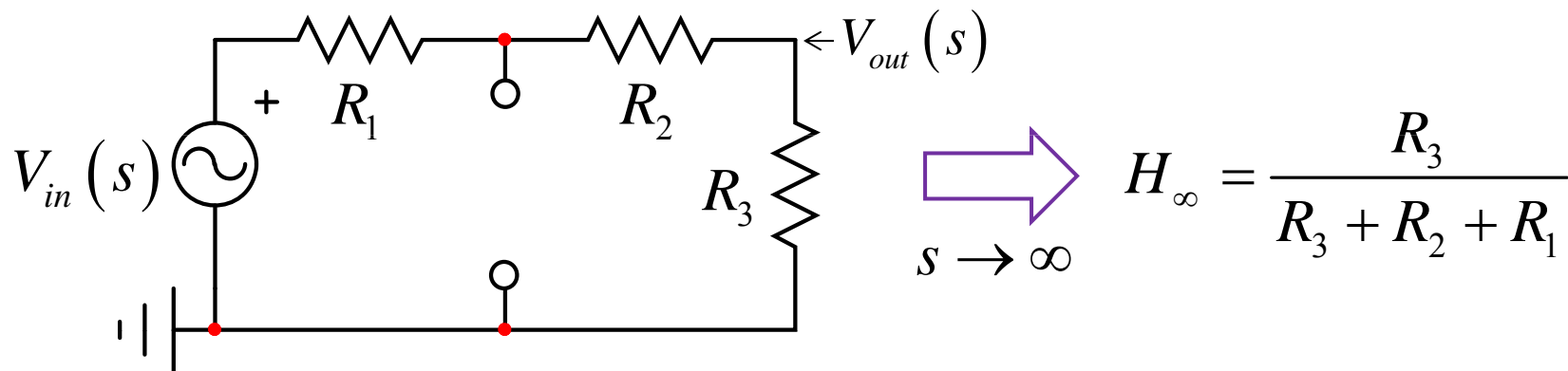- Consider the circuit at high frequency instead




Time Constant Involving Inductor

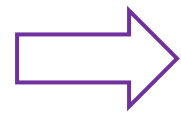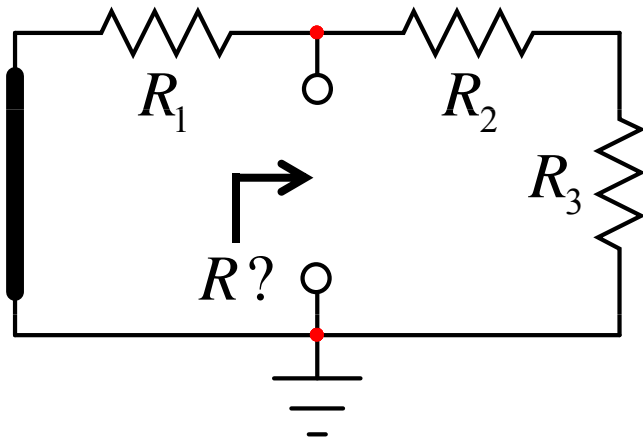- Look at the inductor time constant while V_{in} is 0 V



$$\tau_D = \frac{L_1}{R_1 \parallel (R_2 + R_3)}$$

- Now consider a null output voltage

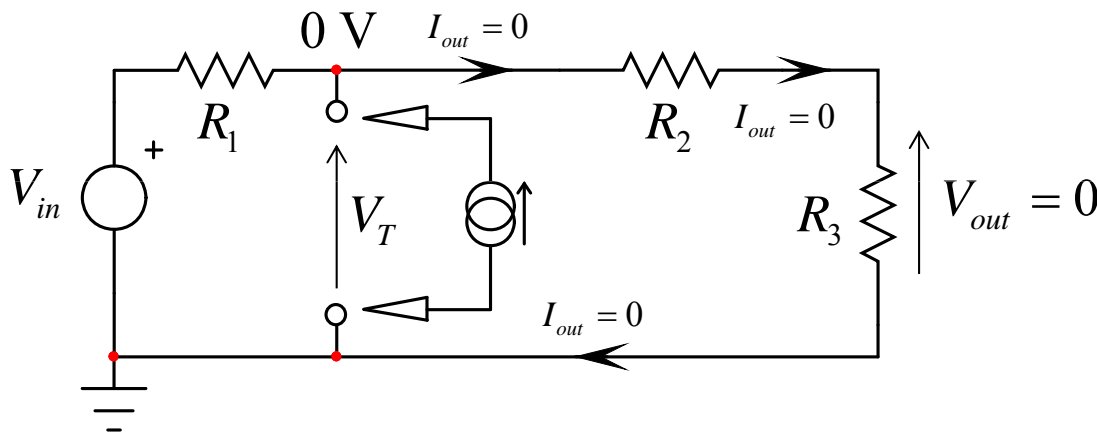

$$\frac{V_T}{I_T} = \frac{0}{I_T} = 0$$




$$\tau_N = \frac{L_1}{R} \rightarrow \infty$$



Determining the Zero

- Check with SPICE if a doubt exists

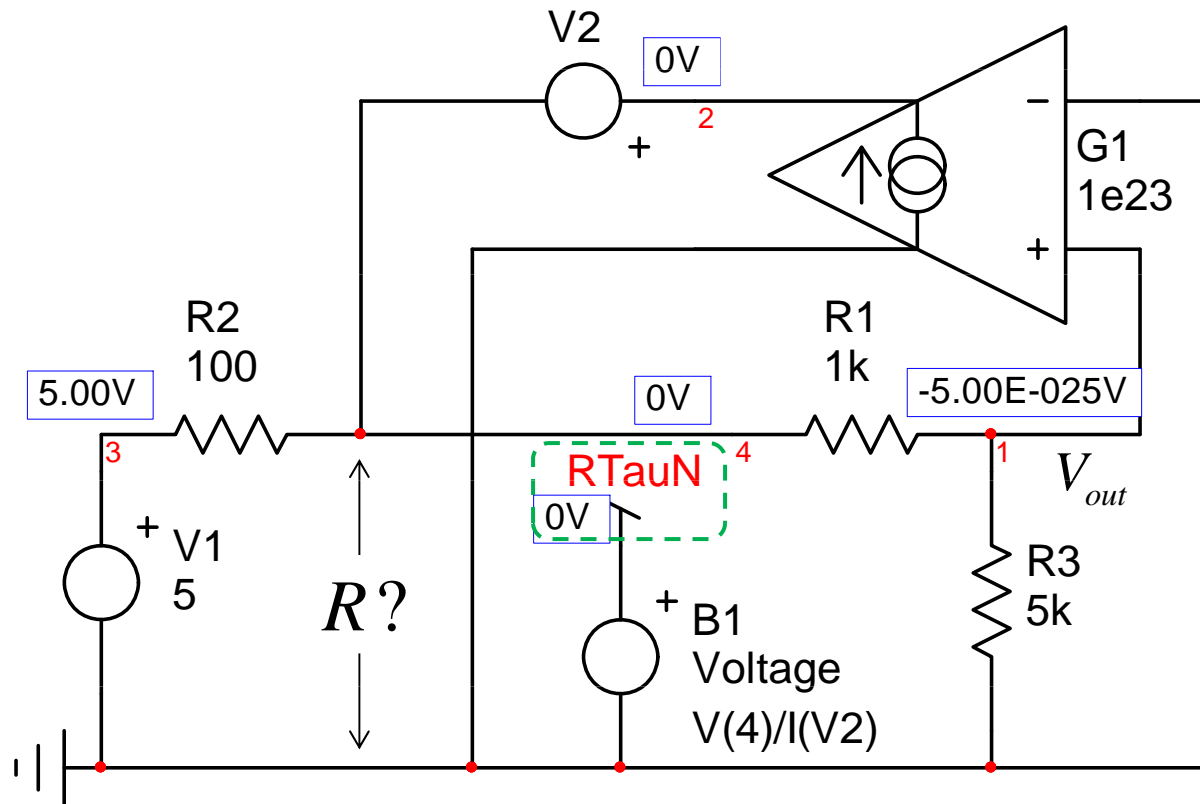

$$R = 0$$

↓

$$\tau_N = \frac{L_1}{R} \rightarrow \infty$$

- G_1 injects a current to maintain V_{out} at 0: NDI

Final Transfer Function

- Assemble time constants to form $H(s)$

$$H(s) = \frac{R_3}{R_3 + R_2 + R_1} \frac{1 + \frac{1}{s \cdot \infty}}{1 + \frac{1}{s \frac{L_1}{R_1 \parallel (R_2 + R_3)}}} = \frac{R_3}{R_3 + R_2 + R_1} \frac{1}{1 + \frac{1}{s \frac{L_1}{R_1 \parallel (R_2 + R_3)}}}$$

- Rewrite the expression in a compact form




$$H(s) = H_\infty \frac{1}{1 + \frac{\omega_p}{s}} \quad H_\infty = \frac{R_3}{R_3 + R_2 + R_1} \quad \omega_p = \frac{R_1 \parallel (R_2 + R_3)}{L_1}$$

Check with Mathcad and SPICE

$$R_1 := 100\Omega \quad R_2 := 1k\Omega \quad R_3 := 5k\Omega \quad L_1 := 1mH \quad \|(x,y) := \frac{x \cdot y}{x + y}$$


$$\tau_D := \frac{L_1}{R_1 \|(R_2 + R_3)} = 10.167\mu s \quad H_{inf} := \frac{R_3}{R_1 + R_2 + R_3} = 0.82$$
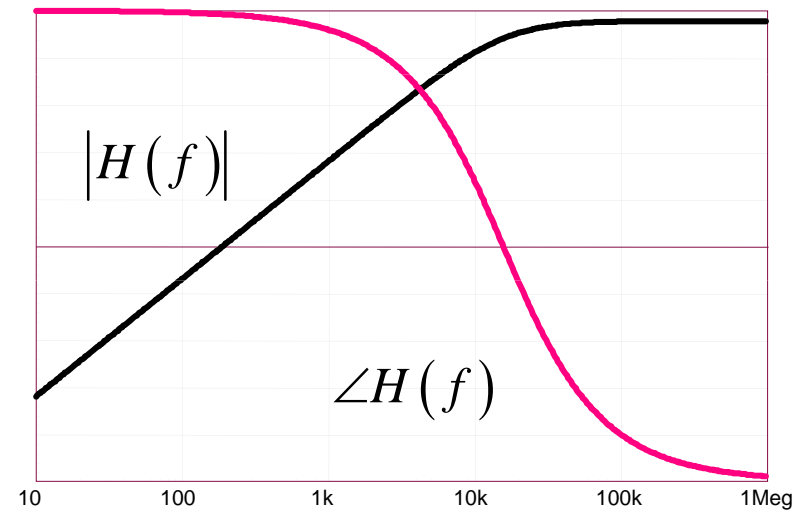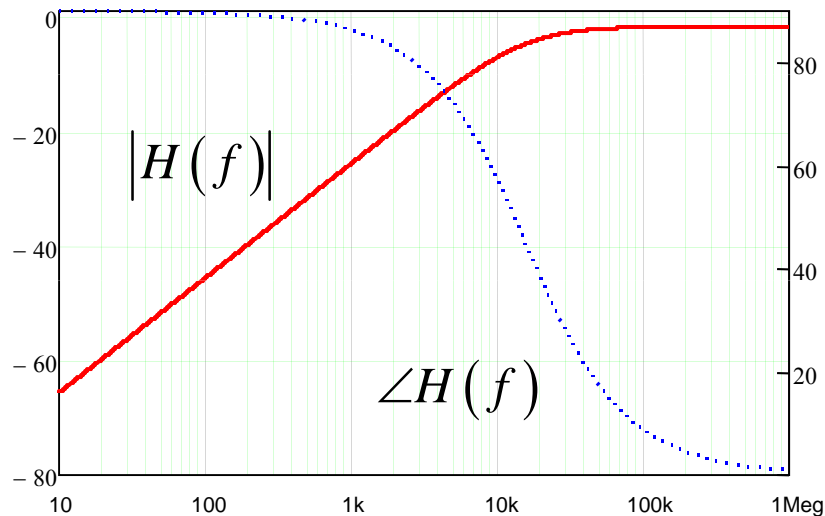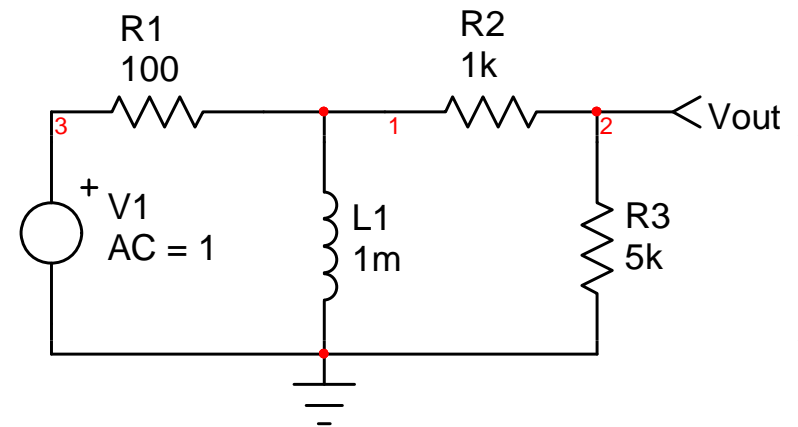
$$H_1(s) := H_{inf} \frac{1}{1 + \frac{1}{s \cdot \tau_D}} \quad f_p := \frac{1}{2\pi \cdot \tau_D} = 15.655kHz$$



Checking for a Zero

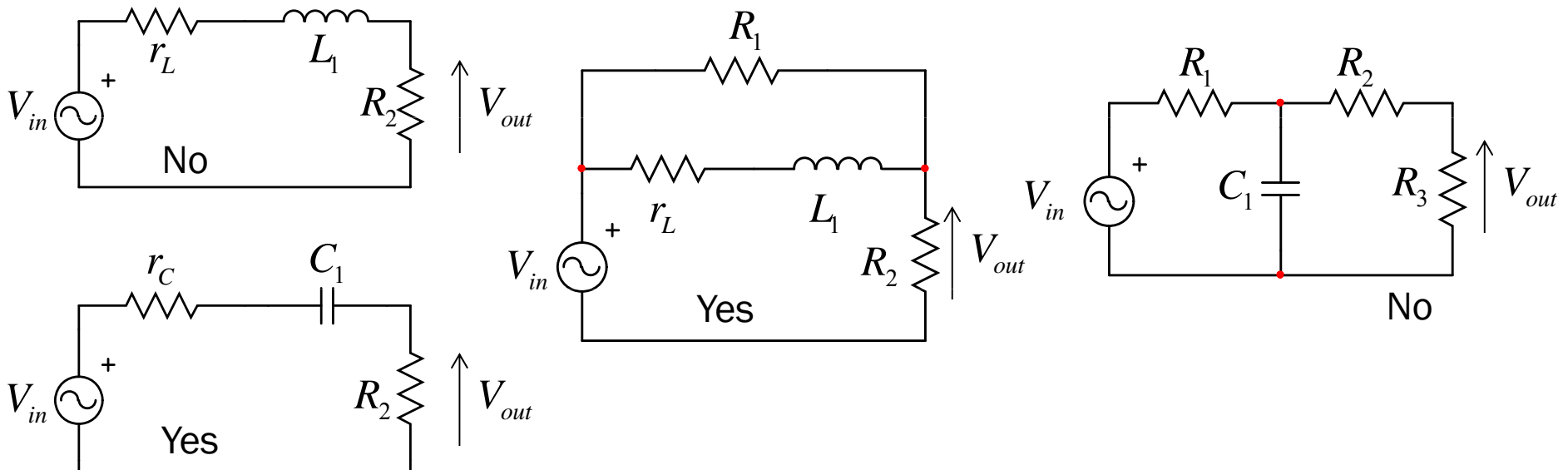- ❑ Is there a quick way to check if there is a zero?
- Yes! Put the reactance in its high-frequency state
- Check if the response is still there
- ✓ If yes, there is a zero associated with the reactance
- ✓ If not, there is no zero in the circuit



Course Agenda

- What is a Transfer Function?
- Why do We Need New Analytical Techniques?
- Time Constants and Poles
- Identifying the Zeros
- The Null Double Injection
- 2nd-Order Networks**
- The PWM Switch Model
- A CCM Buck in Voltage Mode
- A CCM Buck-Boost in Voltage Mode



Fractions and Dimensions

□ A 1st-order system follows the form

$$H(s) = \frac{N(s)}{D(s)} = \frac{a_0 + a_1 s}{b_0 + b_1 s} \xrightarrow{\text{factoring}} H(s) = \frac{a_0}{b_0} \frac{1 + \frac{a_1}{a_0} s}{1 + \frac{b_1}{b_0} s}$$

□ Leading term (if any) carries the unit

$$\begin{array}{ccc}
 \begin{array}{c} \uparrow \\ [\Omega] \end{array} & Z(s) = R_0 & \begin{array}{c} \uparrow \\ [\Omega] \end{array} \\
 & & \boxed{\frac{1 + \frac{a_1}{a_0} s}{1 + \frac{b_1}{b_0} s}} \\
 & & \text{Unitless}
 \end{array}
 \quad \Rightarrow \quad
 \begin{array}{c}
 1 + \frac{a_1}{a_0} s \\
 \updownarrow \\
 1 + \frac{b_1}{b_0} s \\
 \text{Unitless}
 \end{array}
 \left. \vphantom{\begin{array}{c} 1 + \frac{a_1}{a_0} s \\ \updownarrow \\ 1 + \frac{b_1}{b_0} s \end{array}} \right\}
 \begin{array}{l}
 \frac{a_1}{a_0} \rightarrow [s] \rightarrow \tau_N \\
 \frac{b_1}{b_0} \rightarrow [s] \rightarrow \tau_D
 \end{array}$$

2nd-Order System

□ A 2nd-order system follows the form

$$H(s) = \frac{\alpha_0 + \alpha_1 s + \alpha_2 s^2}{\beta_0 + \beta_1 s + \beta_2 s^2} \xrightarrow[\text{Factoring } \beta_0]{\text{Factoring } \alpha_0} H(s) = H_0 \frac{1 + a_1 s + a_2 s^2}{1 + b_1 s + b_2 s^2} \text{ Unitless}$$

↑
Carries the unit

□ The second fraction is unitless

$$a_1 = \frac{\alpha_1}{\alpha_0} \rightarrow [s] \rightarrow \tau_{1N} + \tau_{2N}$$

sum

$$a_2 = \frac{\alpha_2}{\alpha_0} \rightarrow [s^2] \rightarrow \tau_{1N} \tau_{2N}^1 \text{ or } \tau_{2N} \tau_{1N}^2$$

product

$$b_1 = \frac{\beta_1}{\beta_0} \rightarrow [s] \rightarrow \tau_{1D} + \tau_{2D}$$


↑ ↑
reactance 1 reactance 2

$$b_2 = \frac{\beta_2}{\beta_0} \rightarrow [s^2] \rightarrow \tau_{1D} \tau_{2D}^1 \text{ or } \tau_{2D} \tau_{1D}^2$$




Alternating the Reactance States

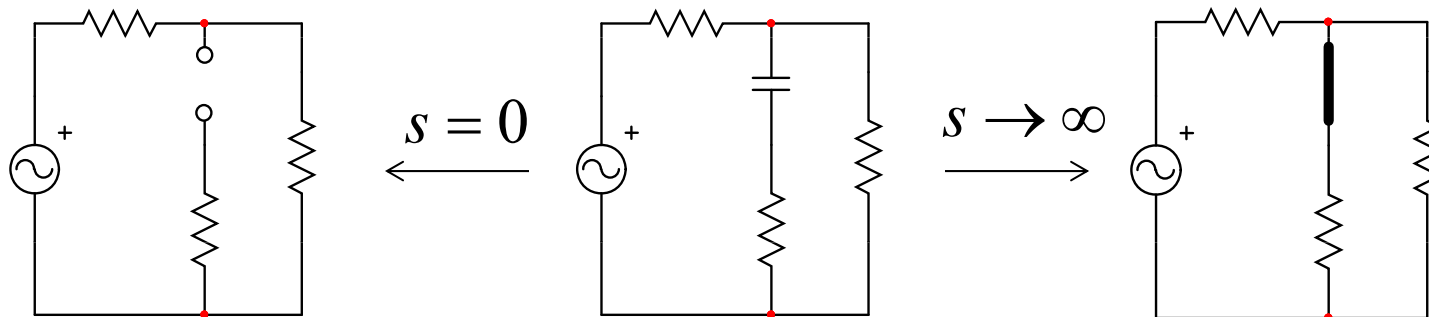- In a 1st-order circuit, there is one reactance
- ❖ it is either in a high-frequency state or in a dc state





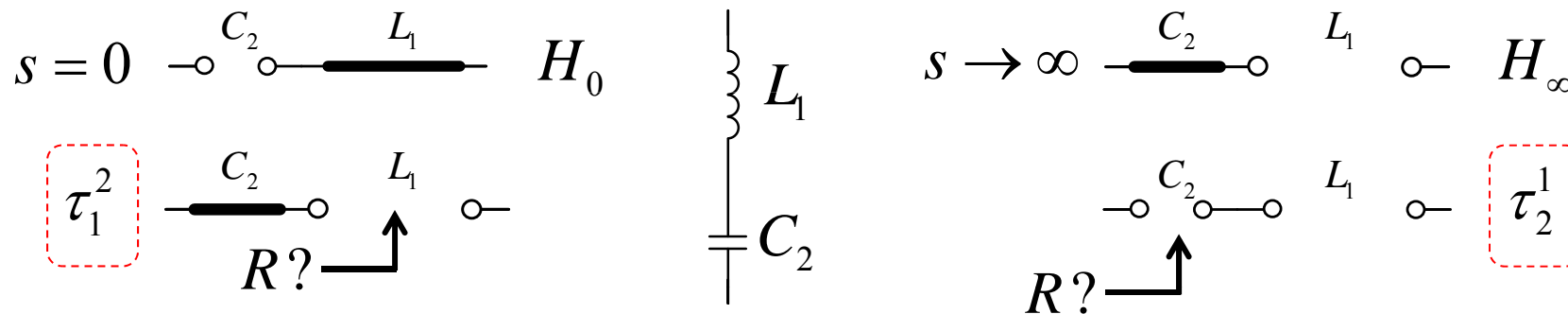- In a 2nd-order circuit, there are two reactances
- ❖ we can consider individual states



Introducing the Notation

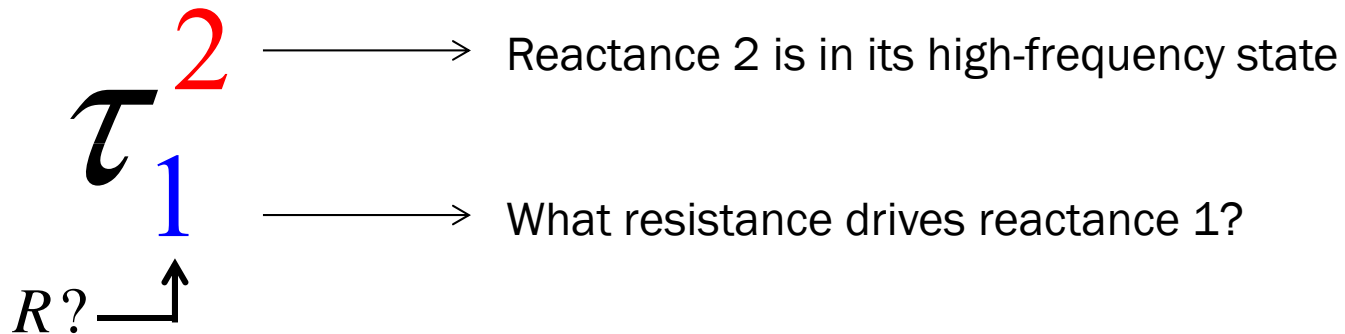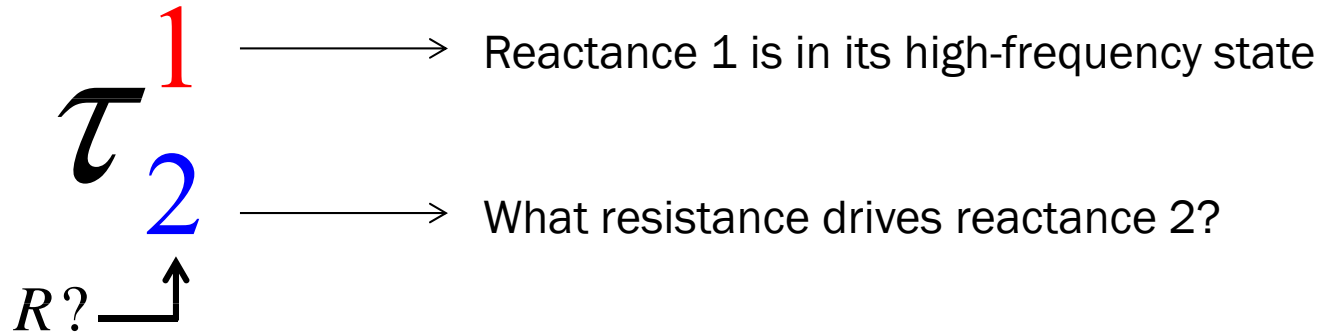- Set one reactance into its high-frequency state




- There is redundancy: pick the simplest result


$$b_2 = \tau_1 \tau_2^1 \iff b_2 = \tau_2 \tau_1^2$$

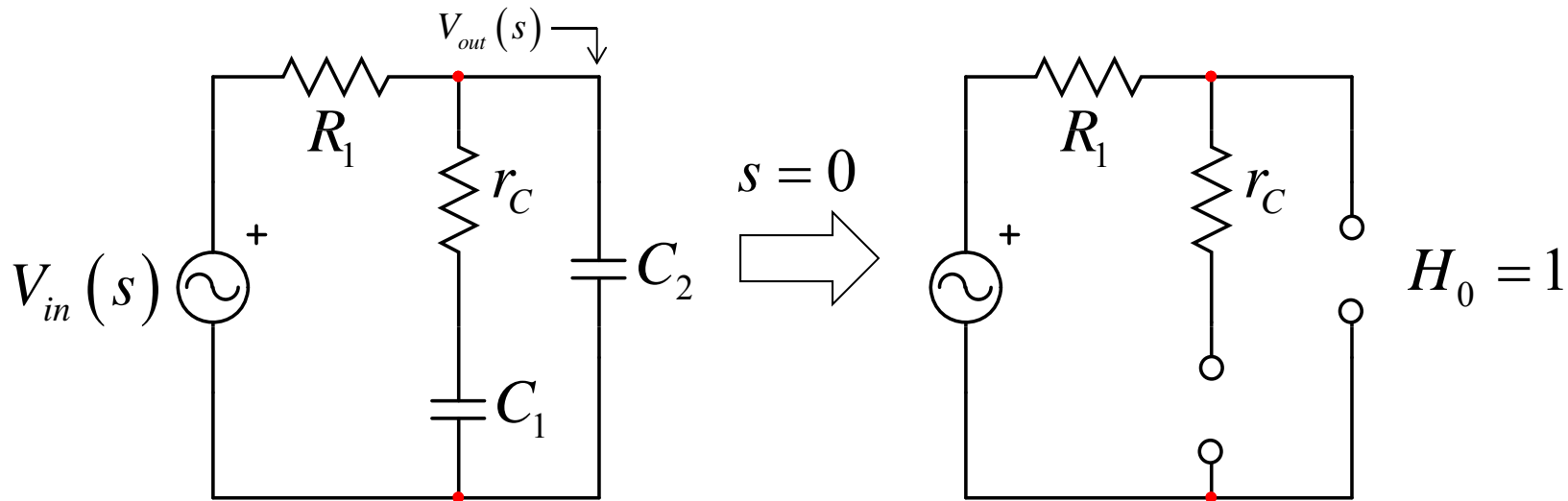Example with Capacitors

- Assume the following 2-capacitor circuit




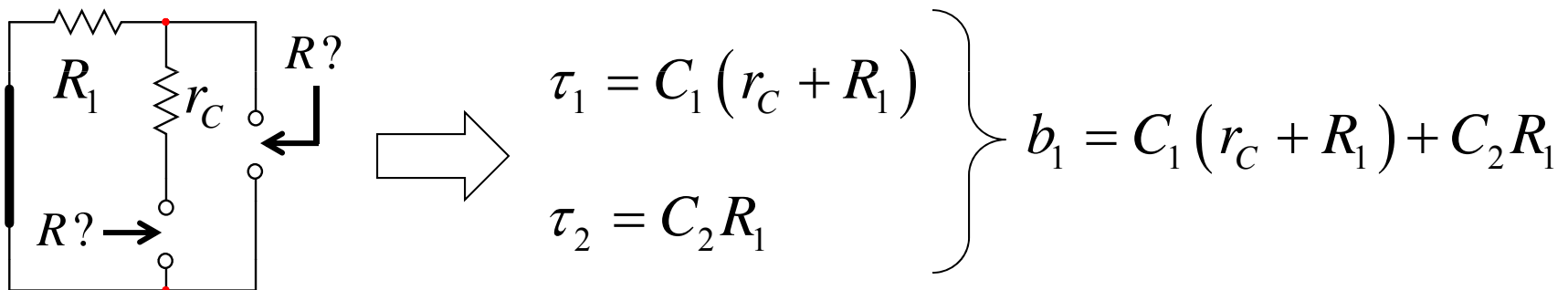- Determine the two time constants while V_{in} is 0 V




Determining the Higher-Order Term

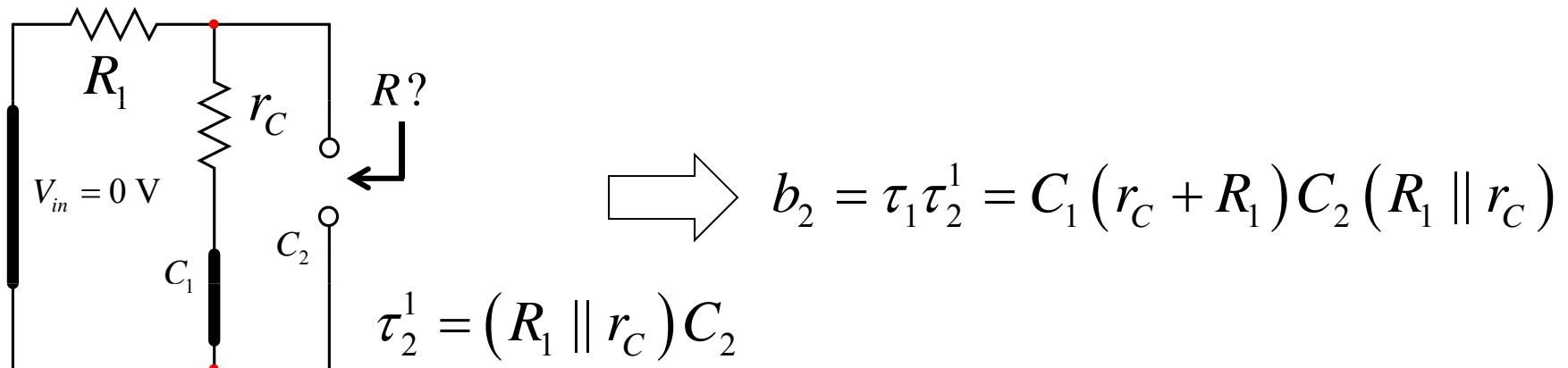- Place C_1 in its high-frequency and look into C_2



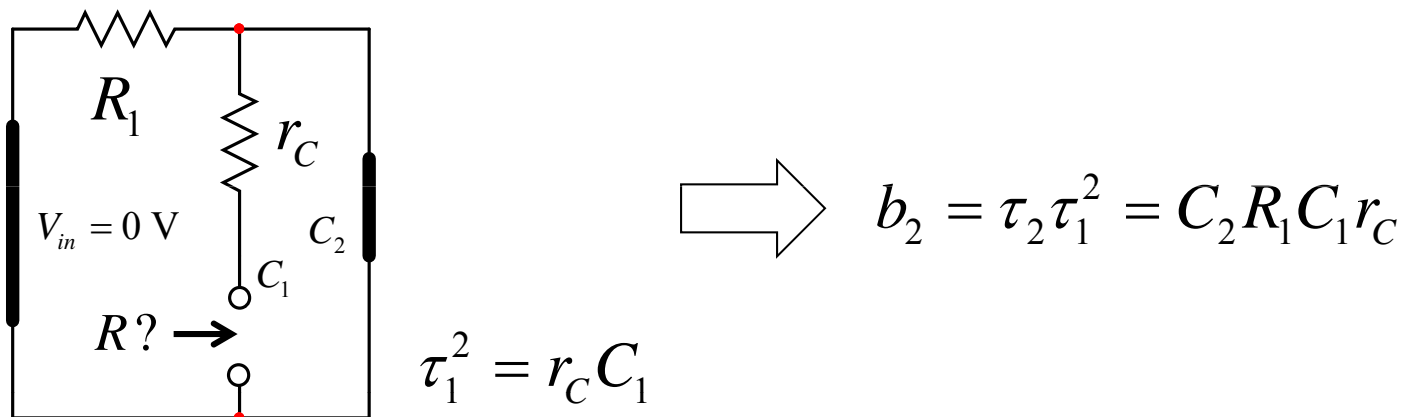- Place C_2 in its high-frequency state and look into C_1




Denominator is Completed

- The denominator can be assembled

$$D(s) = 1 + b_1s + b_2s^2 = 1 + [C_1(r_c + R_1) + C_2R_1]s + C_2R_1C_1r_c s^2$$

- Is there a zero in this network?

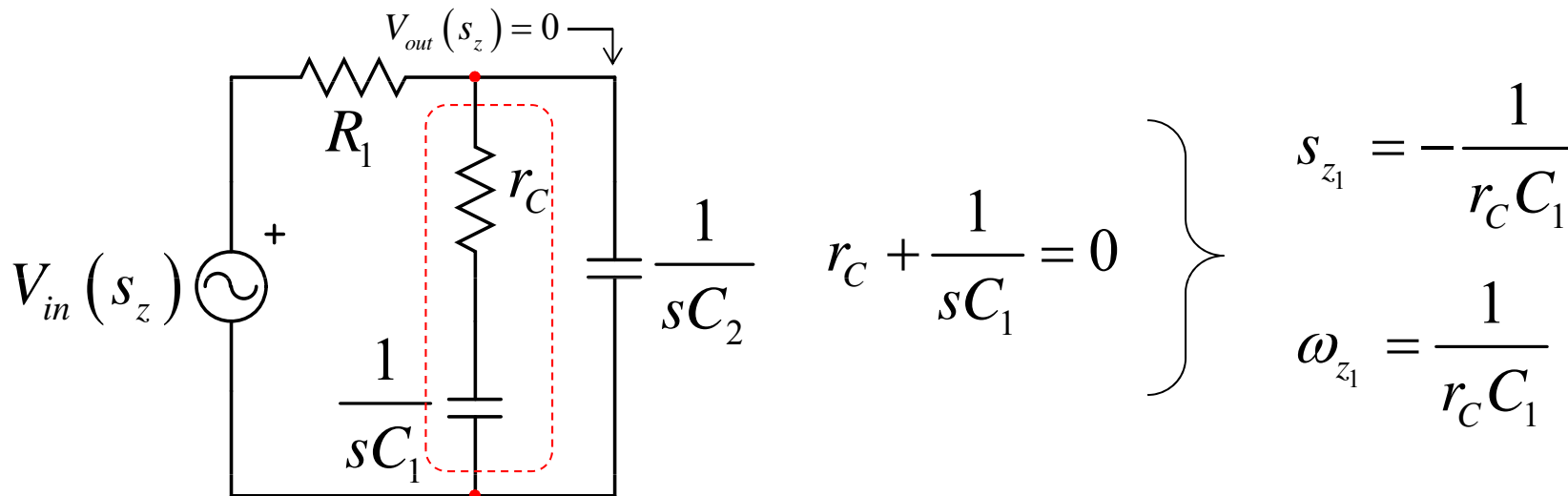

$$H(s) = \frac{1 + sr_c C_1}{1 + [C_1(r_c + R_1) + C_2R_1]s + C_2R_1C_1r_c s^2}$$

No algebra!

You Can Rework the Denominator

- Considering a low quality factor Q (roots are spread)

$$D(s) = 1 + b_1 s + b_2 s^2 = 1 + \underbrace{\frac{s}{\omega_0 Q}}_{\text{Low-frequency}} + \underbrace{\left(\frac{s}{\omega_0}\right)^2}_{\text{High-frequency}} \approx (1 + b_1 s) \left(1 + \frac{b_2}{b_1} s\right)$$

$$H(s) \approx \frac{1 + sr_C C_1}{\left[1 + s(C_1(r_C + R_1) + C_2 R_1)\right] \left(1 + s \frac{C_2 R_1 C_1 r_C}{C_1(r_C + R_1) + C_2 R_1}\right)}$$

$$H(s) = \frac{1 + \frac{s}{\omega_z}}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

$$\omega_z = \frac{1}{r_C C_1} \quad \omega_{p2} = \frac{C_1(r_C + R_1) + C_2 R_1}{C_2 R_1 C_1 r_C}$$

$$\omega_{p1} = \frac{1}{R_1(C_1 + C_2) + r_C C_1}$$

Check with Mathcad

□ It is easy to check results versus a raw expression

$$R_1 := 1k\Omega \quad r_C := 100\Omega \quad C_1 := 10nF \quad C_2 := 5nF \quad \|(x,y) := \frac{x \cdot y}{x + y}$$

$$H_0 := 1 \quad \tau_1 := C_1 \cdot (r_C + R_1) = 11\mu s \quad \tau_2 := C_2 \cdot R_1 = 5\mu s \quad a_1 := \tau_1 + \tau_2 = 16\mu s$$

$$\tau_{12} := C_2 \cdot (R_1 \parallel r_C) = 0.455\mu s \quad \tau_{21} := C_1 \cdot r_C \quad a_2 := \tau_2 \cdot \tau_{21} = 5\mu s^2$$

$$N_1(s) := 1 + s \cdot r_C \cdot C_1 \quad D_1(s) := 1 + a_1 \cdot s + a_2 \cdot s^2$$

$$H_1(s) := H_0 \cdot \frac{N_1(s)}{D_1(s)}$$

$$Z_1(s) := \left(r_C + \frac{1}{s \cdot C_1} \right) \parallel \left(\frac{1}{s \cdot C_2} \right)$$

$$H_2(s) := \frac{Z_1(s)}{R_1 + Z_1(s)}$$

$$\omega_Z := \frac{1}{r_C \cdot C_1}$$

$$\omega_{p1} := \frac{1}{a_1}$$


$$\omega_{p2} := \frac{a_1}{a_2}$$

$$H_3(s) := \frac{1 + \frac{s}{\omega_Z}}{\left(1 + \frac{s}{\omega_{p1}} \right) \cdot \left(1 + \frac{s}{\omega_{p2}} \right)}$$

$$20 \cdot \log(|H_1(i \cdot 2\pi \cdot f_k)|, 10)$$


$$20 \cdot \log(|H_2(i \cdot 2\pi \cdot f_k)|, 10)$$

$$20 \cdot \log(|H_3(i \cdot 2\pi \cdot f_k)|, 10)$$

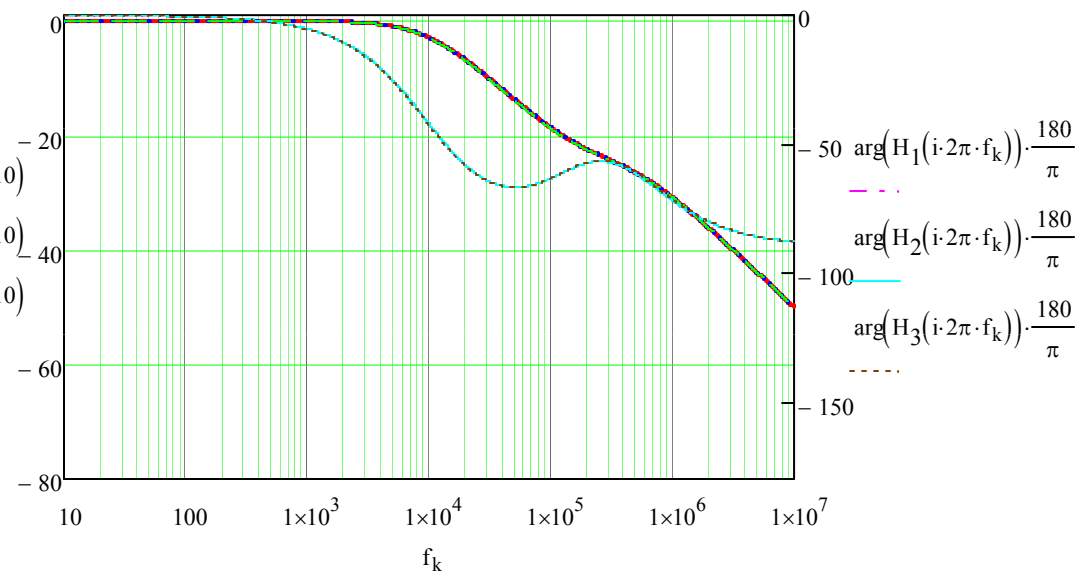


2nd-Order Example

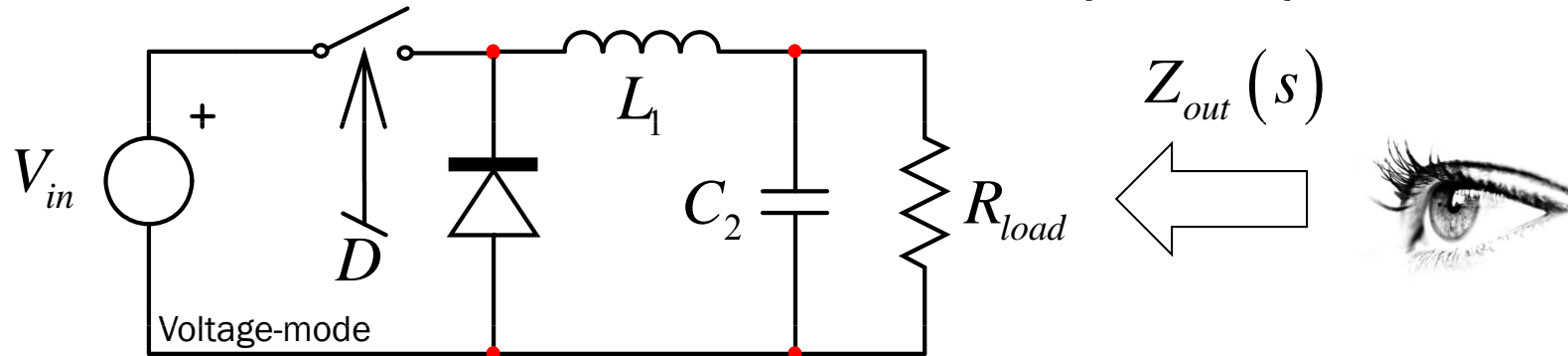- What is the buck converter output impedance?



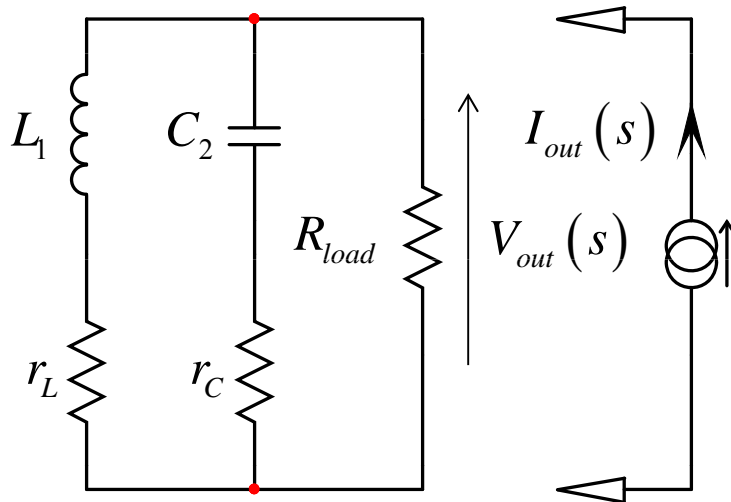- Consider parasitic elements for L and C




$$Z_{out}(s) = \frac{V_{out}(s)}{I_{out}(s)}$$


← response
← excitation

Buck Output Impedance

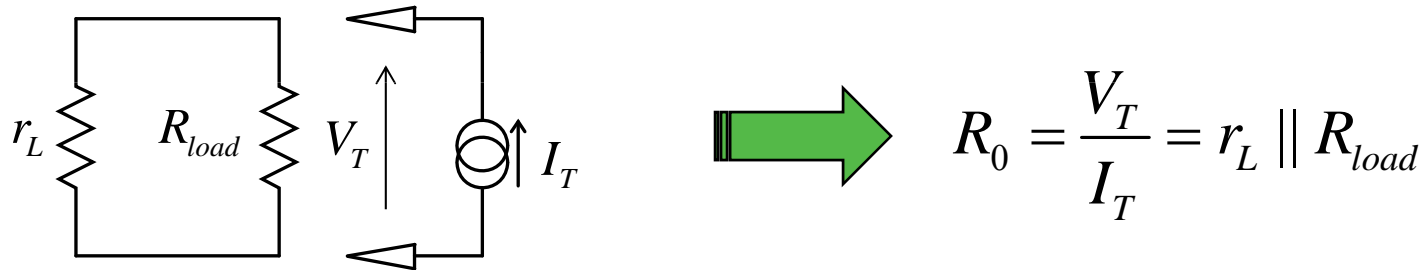- Let's find the term R_0 in dc: open caps, short inductors





- The zeros cancel the response

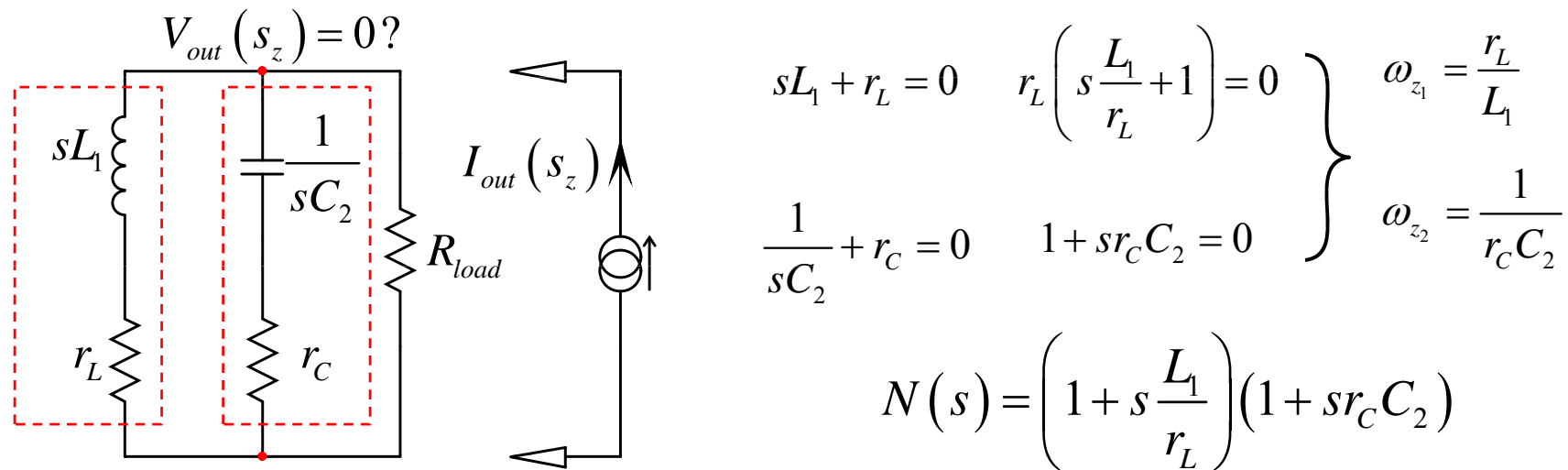

Low-Frequency Time Constants

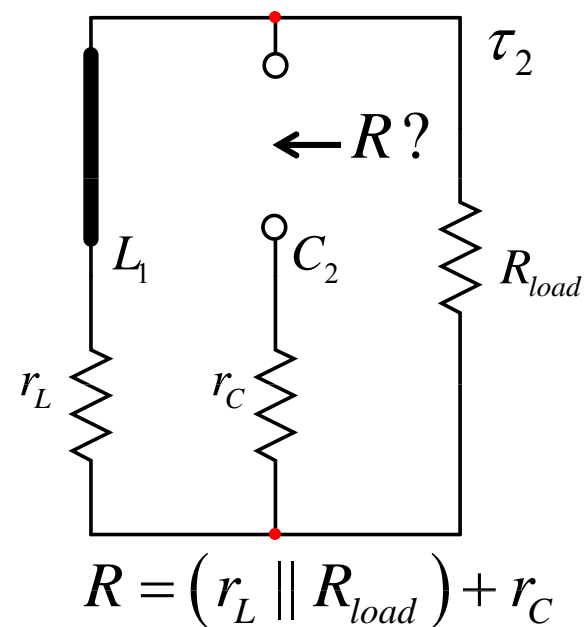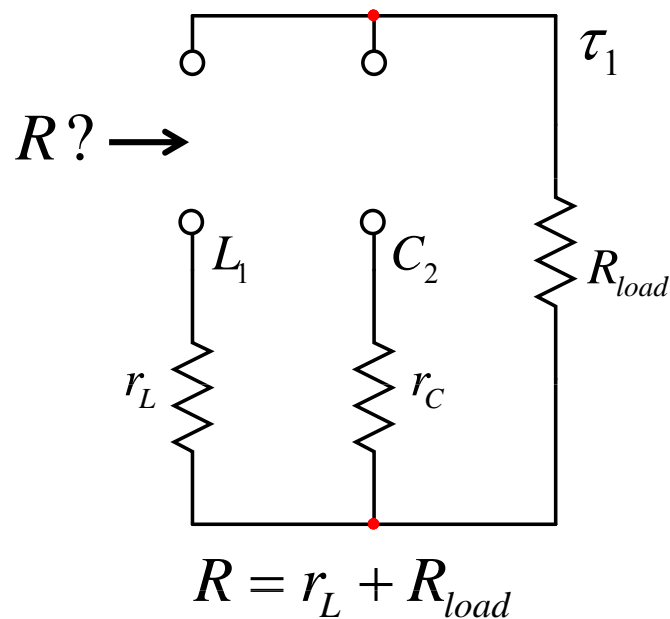
- All elements are in their dc state
- Look at R driving L then R driving C



$$b_1 = \frac{L_1}{r_L + R_{load}} + C_2 \left[(r_L \parallel R_{load}) + r_C \right]$$

High-Frequency Time Constants

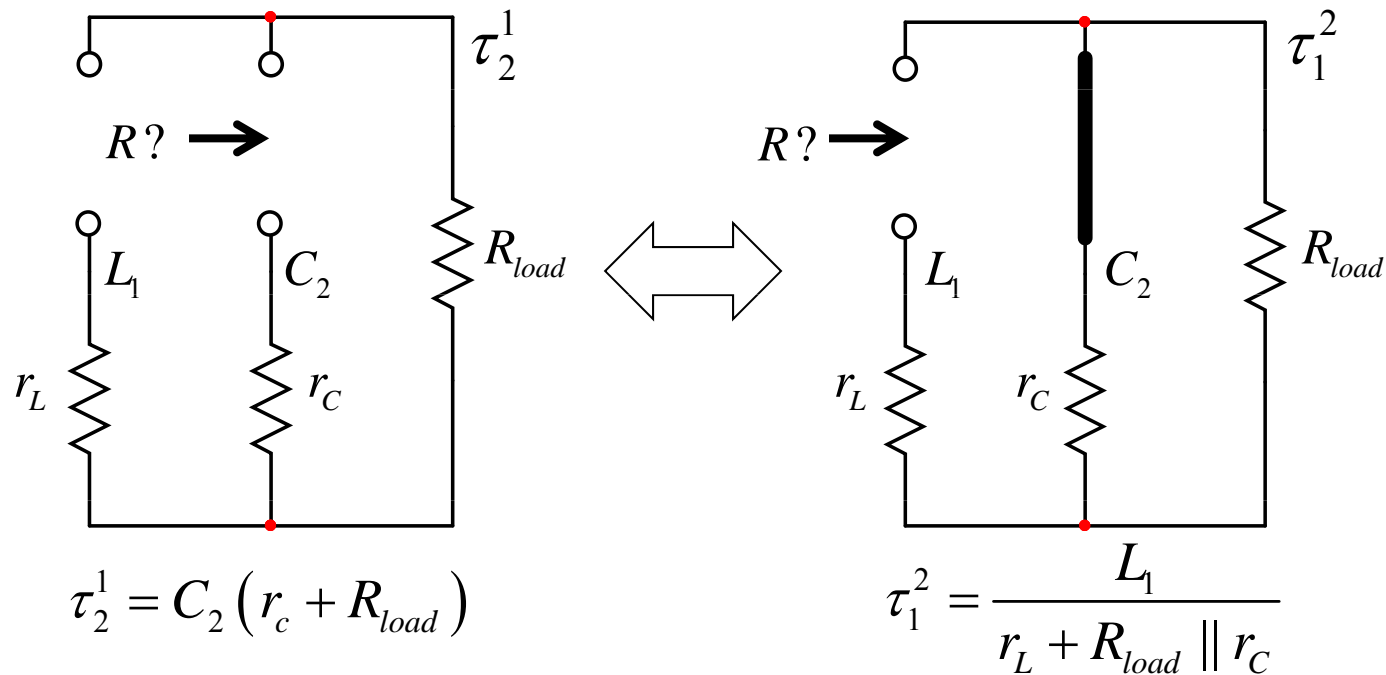- Set L_1 in high frequency state and look at R driving C_2



$$b_2 = \frac{L_1}{r_L + R_{load}} C_2 (r_c + R_{load}) = C_2 \left[(r_L \parallel R_{load}) + r_C \right] \frac{L_1}{r_L + R_{load} \parallel r_C}$$

$$b_2 = \tau_1 \tau_2^1$$

$$b_2 = \tau_2 \tau_1^2$$

Compensating the Buck – Method 1

□ We have our denominator!

$$D(s) = 1 + s \left(\frac{L_1}{r_L + R_{load}} + C_2 \left[(r_L \parallel R_{load}) + r_C \right] \right) + s^2 \left(L_1 C_2 \frac{r_C + R_{load}}{r_L + R_{load}} \right)$$

□ The complete transfer function is now:

$$Z_{out}(s) = (r_L \parallel R_{load}) \frac{\left(1 + s \frac{L_1}{r_L} \right) (1 + s r_C C_2)}{1 + s \left(\frac{L_1}{r_L + R_{load}} + C_2 \left[(r_L \parallel R_{load}) + r_C \right] \right) + s^2 \left(L_1 C_2 \frac{r_C + R_{load}}{r_L + R_{load}} \right)}$$

Compensating the Buck – Method 1

□ It can be put under the following form:

$$Z_{out}(s) = R_0 \frac{(1 + s/\omega_{z_1})(1 + s/\omega_{z_2})}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

□ We can identify the terms:

$$R_0 = r_L \parallel R_{load} \quad \omega_{z_1} = \frac{r_L}{L_1} \quad \omega_{z_2} = \frac{1}{r_C C_2}$$

$$\omega_0 = \frac{1}{\sqrt{L_1 C_2}} \sqrt{\frac{r_L + R_{load}}{r_C + R_{load}}} \quad Q = \frac{L_1 C_2 \omega_0 (r_C + R_{load})}{L_1 + C_2 (r_L r_C + r_L R_{load} + r_C R_{load})}$$



Check Response with Mathcad®

□ Express all time constants independently

$$r_L := 0.1\Omega \quad r_C := 10\Omega \quad C_2 := 10\text{nF} \quad L_1 := 20\mu\text{H} \quad R_L := 5\Omega \quad \|(x,y) := \frac{x \cdot y}{x + y}$$

$$R_0 := r_L \parallel R_L = 0.098\Omega$$

$$\tau_{11} := \frac{L_1}{r_L + R_L} = 3.922\mu\text{s} \quad \tau_{22} := C_2 \cdot (r_L \parallel R_L + r_C) = 100.98\text{ns} \quad a_1 := \tau_{11} + \tau_{22} = 4.023\mu\text{s}$$

$$\tau_{12} := C_2 \cdot (r_C + R_L) = 0.15\mu\text{s} \quad \tau_{21} := \frac{L_1}{r_L + R_L \parallel r_C} = 5.825\mu\text{s} \quad a_2 := \tau_{22} \cdot \tau_{21} = 0.588\mu\text{s}^2$$

$$N_1(s) := \left(1 + s \cdot \frac{L_1}{r_L}\right) \cdot (1 + s \cdot r_C \cdot C_2) \quad D_1(s) := 1 + a_1 \cdot s + a_2 \cdot s^2 \quad Z_1(s) := R_0 \cdot \frac{N_1(s)}{D_1(s)}$$

$$\omega_{z1} := \frac{r_L}{L_1} \quad \omega_{z2} := \frac{1}{r_C \cdot C_2} \quad \omega_0 := \frac{1}{\sqrt{L_1 \cdot C_2}} \cdot \sqrt{\frac{r_L + R_L}{r_C + R_L}} \quad Q := \frac{L_1 \cdot C_2 \cdot \omega_0 \cdot (r_C + R_L)}{L_1 + C_2 \cdot (r_L \cdot r_C + r_L \cdot R_L + r_C \cdot R_L)}$$

$$Z_3(s) := R_0 \cdot \frac{\left(1 + \frac{s}{\omega_{z1}}\right) \cdot \left(1 + \frac{s}{\omega_{z2}}\right)}{1 + \frac{s}{\omega_0 \cdot Q} + \left(\frac{s}{\omega_0}\right)^2}$$

$$Z_a(s) := s \cdot L_1 + r_L \quad Z_b(s) := \frac{1}{s \cdot C_2} + r_C$$


$$Z_2(s) := R_L \parallel (Z_a(s) \parallel Z_b(s))$$

Raw expression

✓ Fault correction is easy!

Derivation is Correct

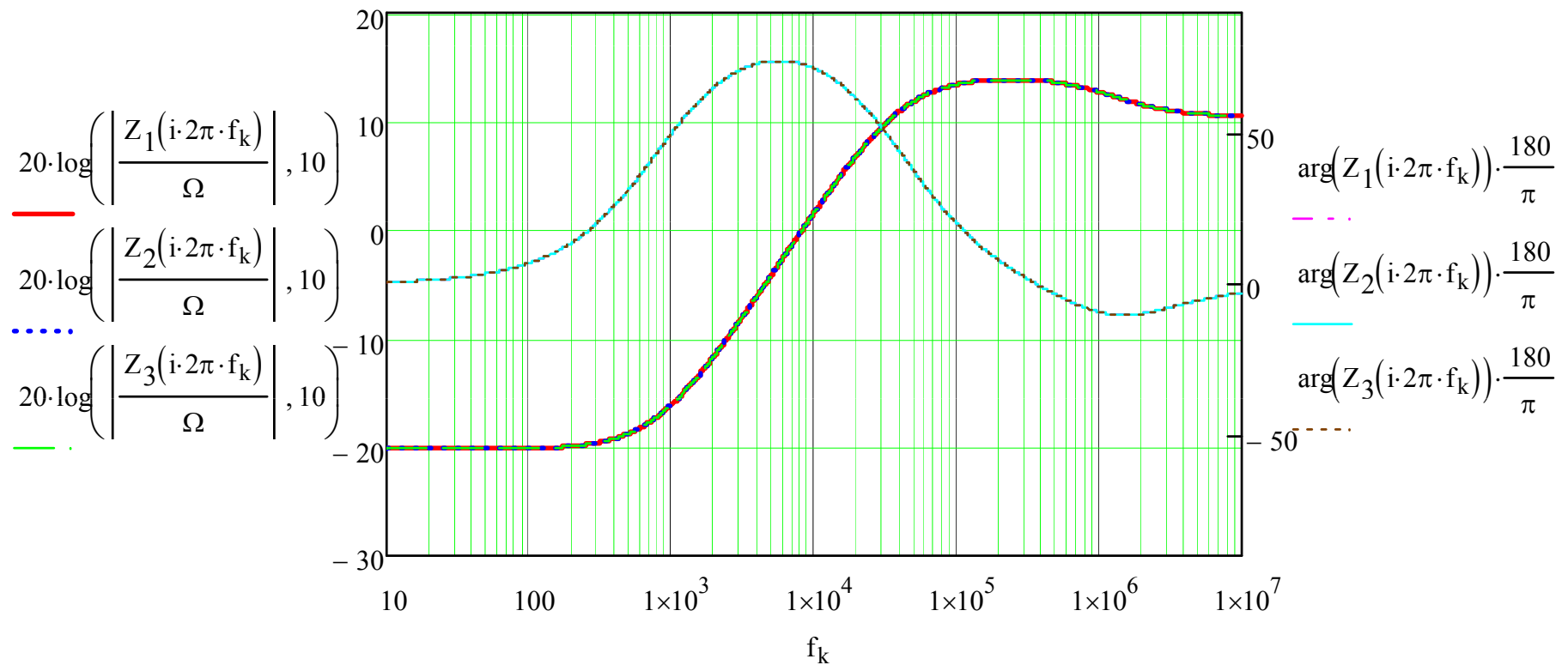
- Magnitude and phase curves perfectly superimpose



- Always verify results with a different expression or SPICE

Checking for Zeros

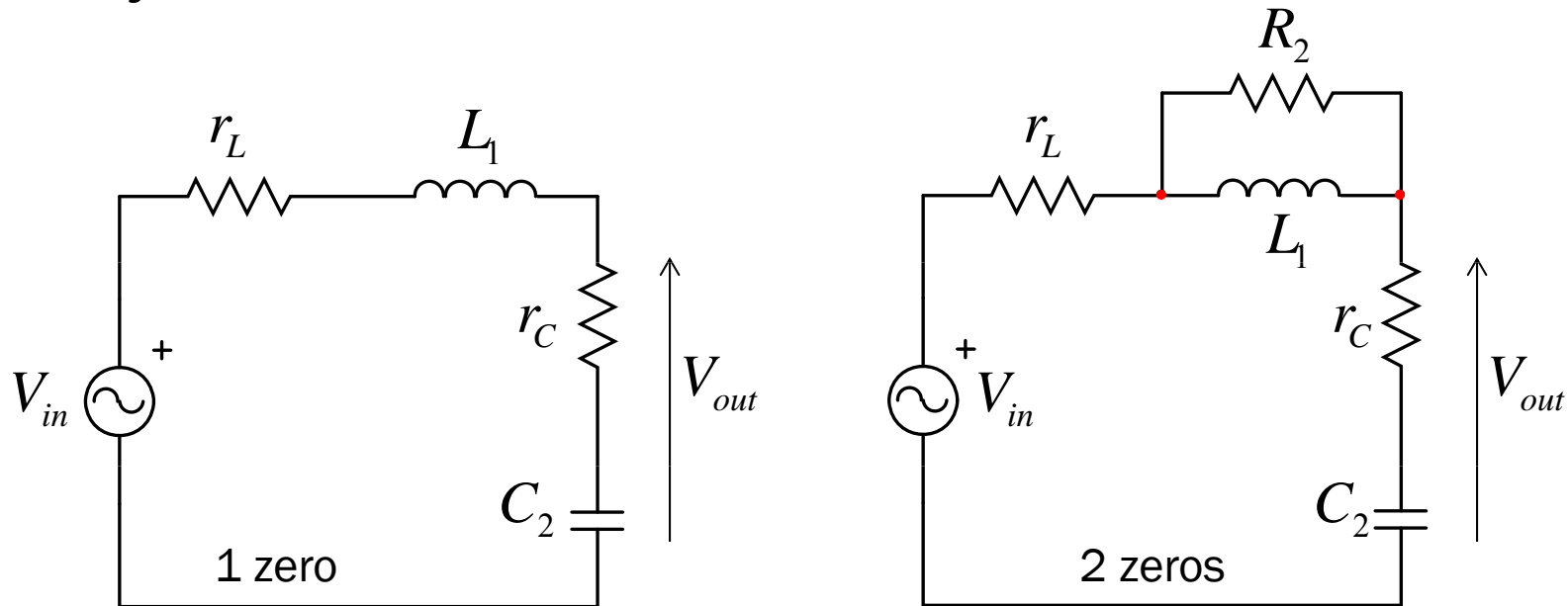- ❑ Is there a quick way to check if there are zeros?
- Yes! Simultaneously put reactances in their HF state
- Check if the response is still there
- ✓ If yes, there are 2 zeros in the circuit




Course Agenda

- What is a Transfer Function?
- Why do We Need New Analytical Techniques?
- Time Constants and Poles
- Identifying the Zeros
- The Null Double Injection
- 2nd-Order Networks
- The PWM Switch Model**
- A CCM Buck in Voltage Mode
- A CCM Buck-Boost in Voltage Mode




The PWM Switch Model in Voltage Mode

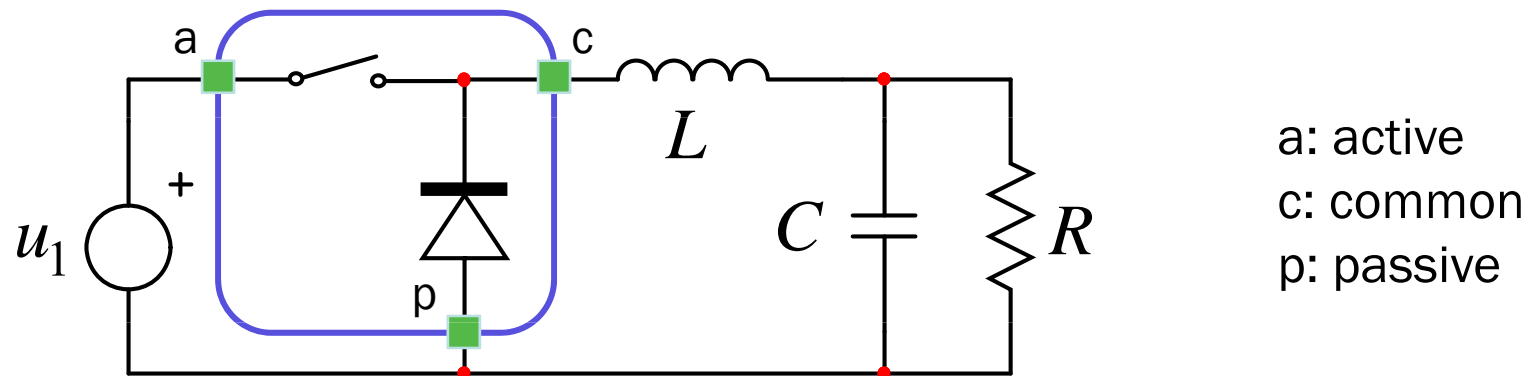- The non-linearity is brought by the switching cell




- Why don't we linearize the cell alone?

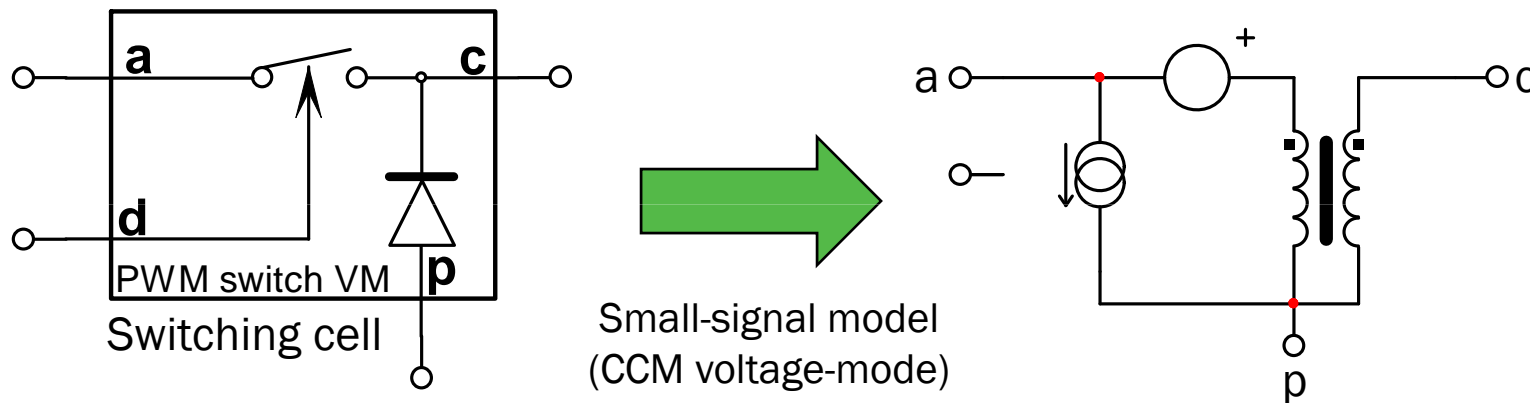

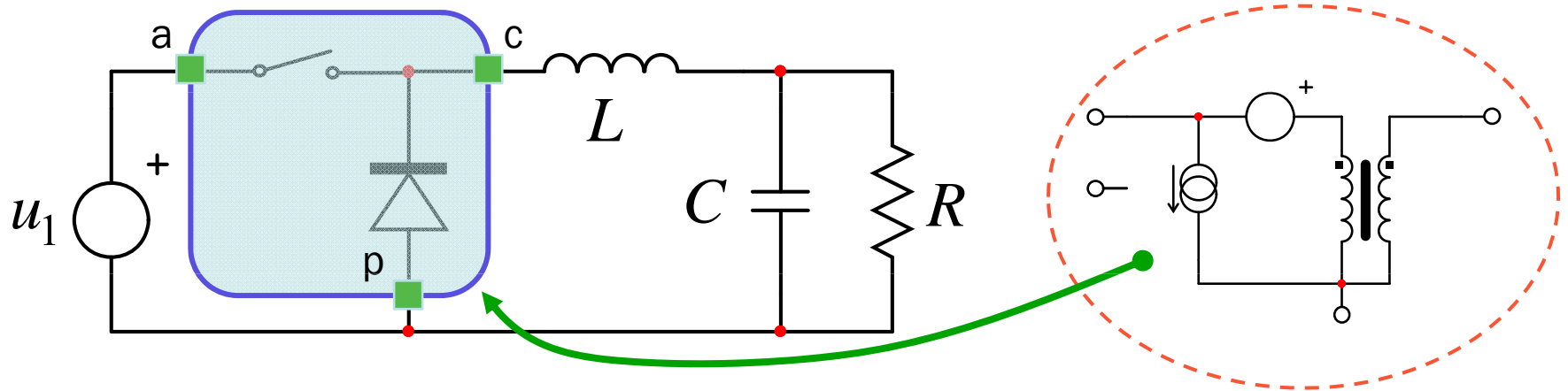V. Vorpérian, "Simplified Analysis of PWM Converters using Model of PWM Switch, parts I and II" IEEE Transactions on Aerospace and Electronic Systems, Vol. 26, NO. 3, 1990


Replace the Switches by the Model

- Like in a bipolar circuit, replace the switching cell...




- ...and solve a set of linear equations!

Small-signal model

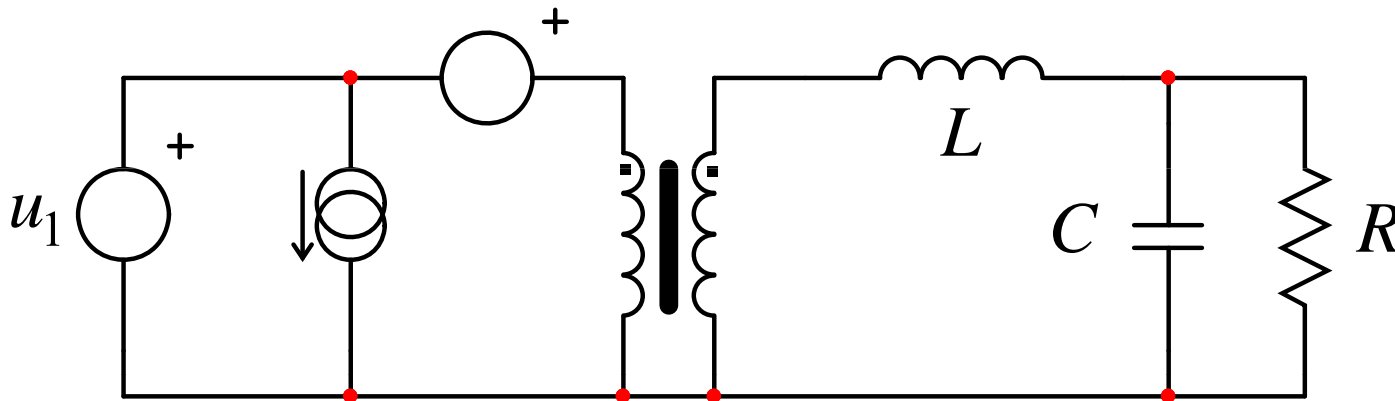


An Invariant Model

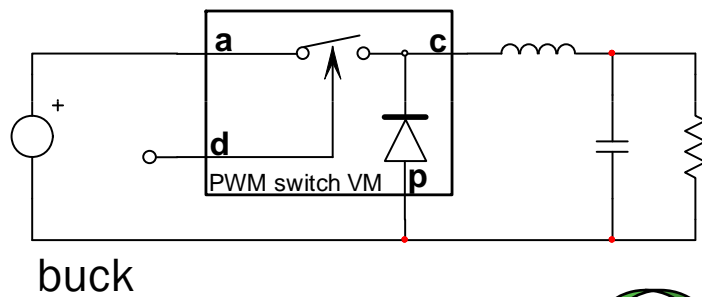
- The switching cell made of two switches is everywhere!




buck

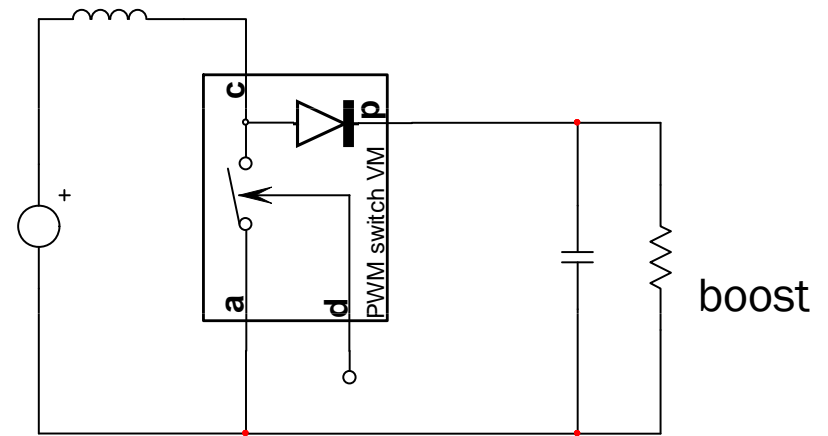

boost

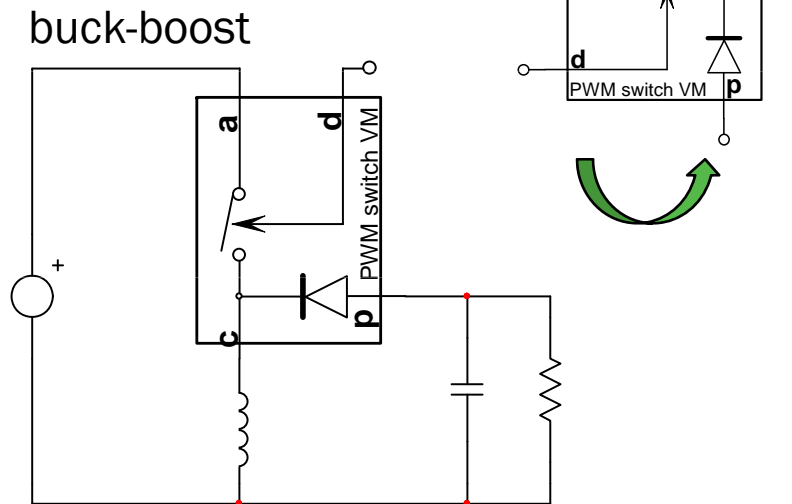


buck-boost

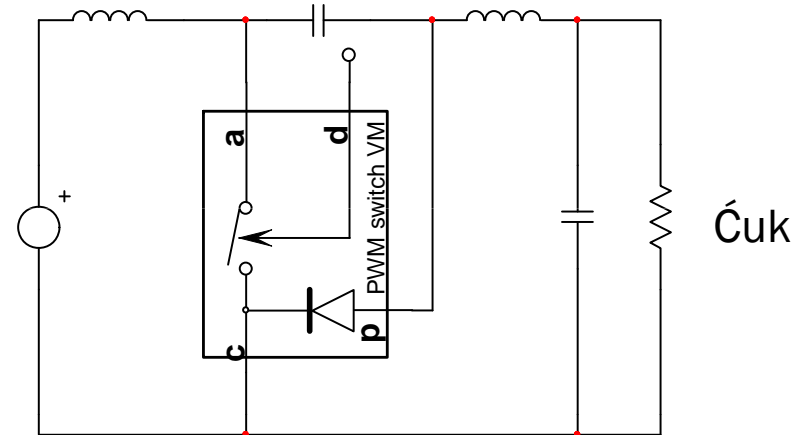


Ćuk

CCM Common Passive Configuration

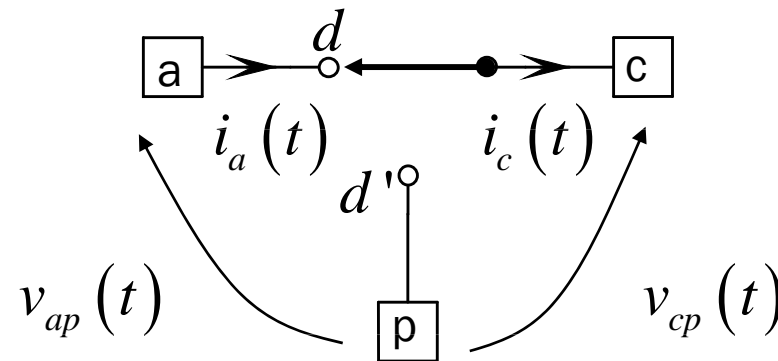- The PWM switch is a single-pole double-throw model




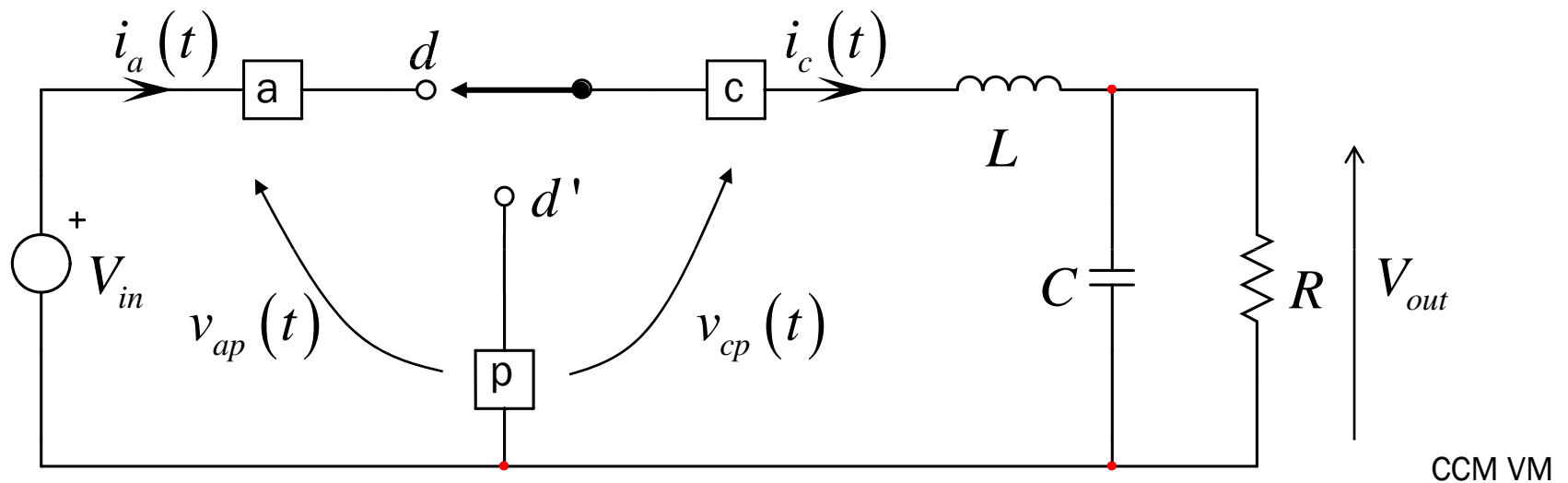- Install it in a buck and draw its terminals waveforms



The Common Passive Configuration

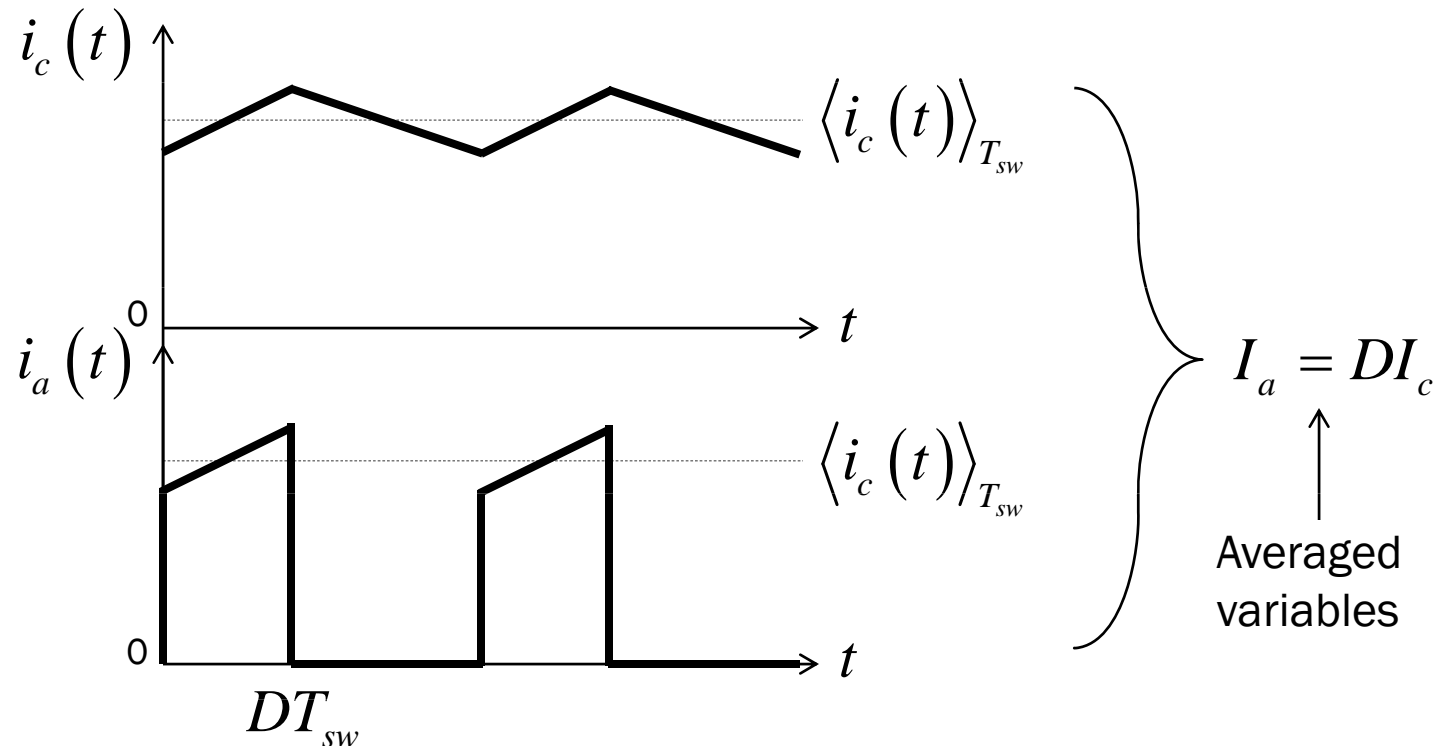- Average the current waveforms across the PWM switch




$$\langle i_a(t) \rangle_{T_{sw}} = I_a = \frac{1}{T_{sw}} \int_0^{DT_{sw}} i_a(t) dt = D \langle i_c(t) \rangle_{T_{sw}} = DI_c$$

CCM VM

The Common Passive Configuration

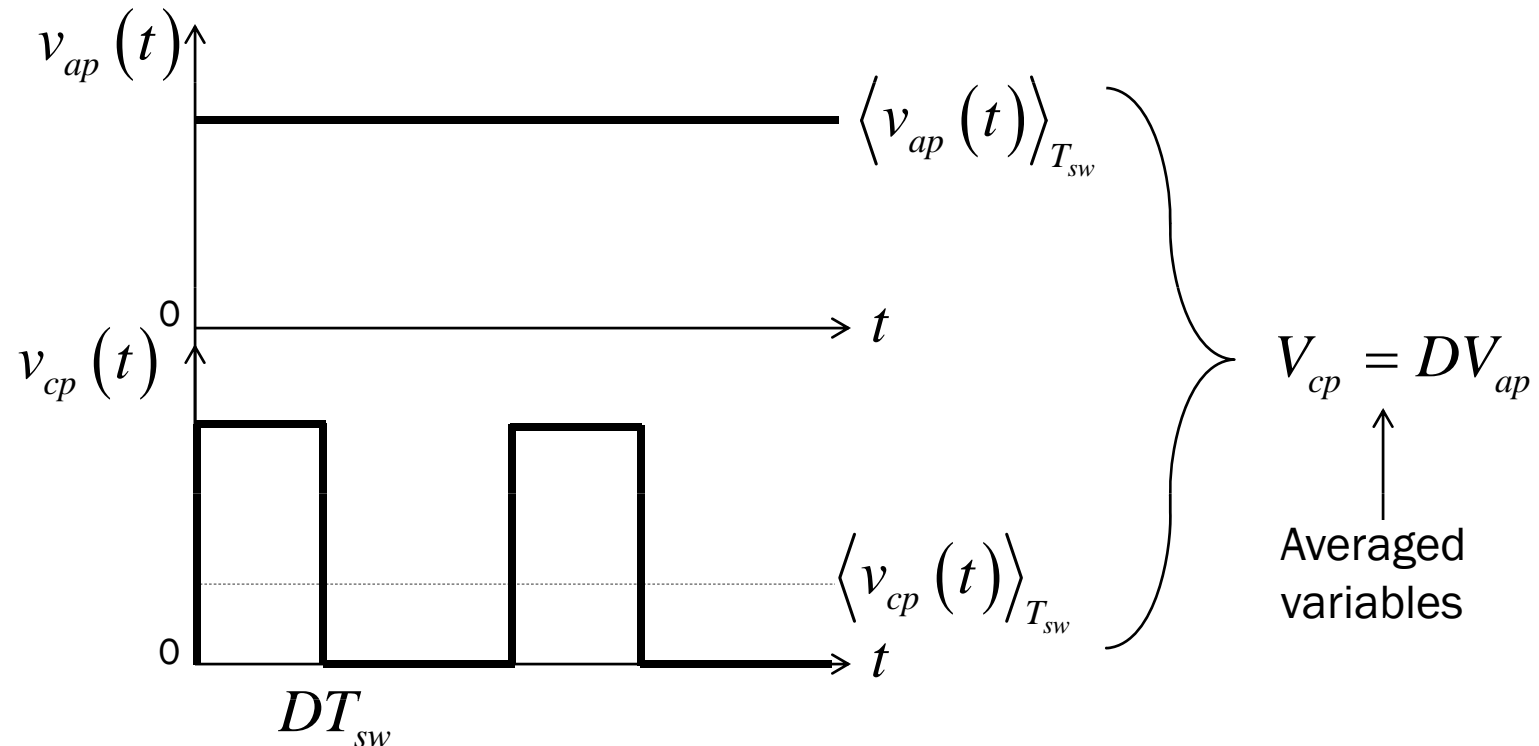- Average the voltage waveforms across the PWM switch




$$\langle v_{cp}(t) \rangle_{T_{sw}} = V_{cp} = \frac{1}{T_{sw}} \int_0^{DT_{sw}} v_{cp}(t) dt = D \langle v_{ap}(t) \rangle_{T_{sw}} = DV_{ap}$$

CCM VM




A Two-Port Representation

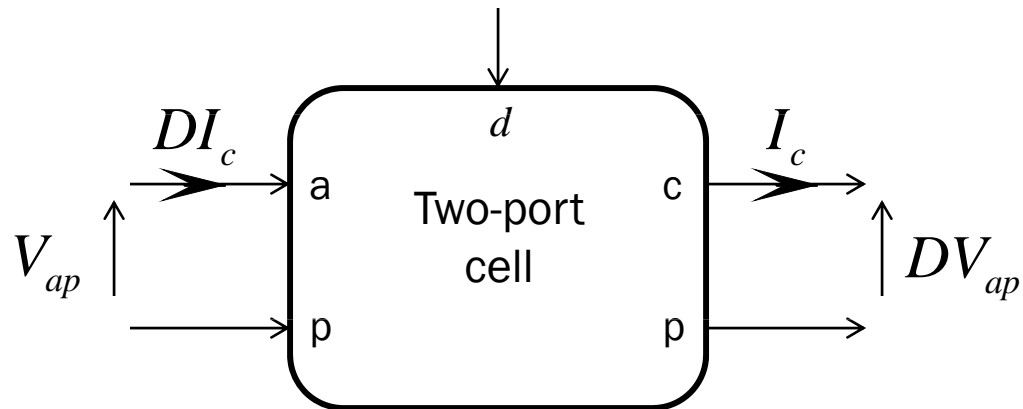- We have a link between input and output variables




- We can involve current and voltage sources

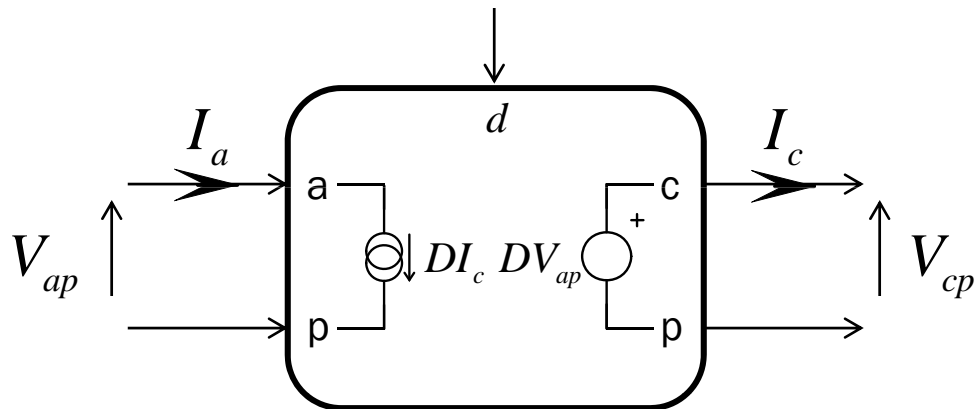

CCM VM

A Dc Transformer Model

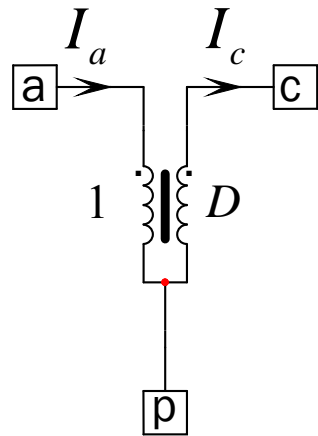- The large-signal model is a dc "transformer"!




$$I_a = DI_c \quad I_c = \frac{I_a}{D}$$

$$V_{ap} = \frac{V_{cp}}{D} \quad V_{cp} = DV_{ap}$$

dc equations!

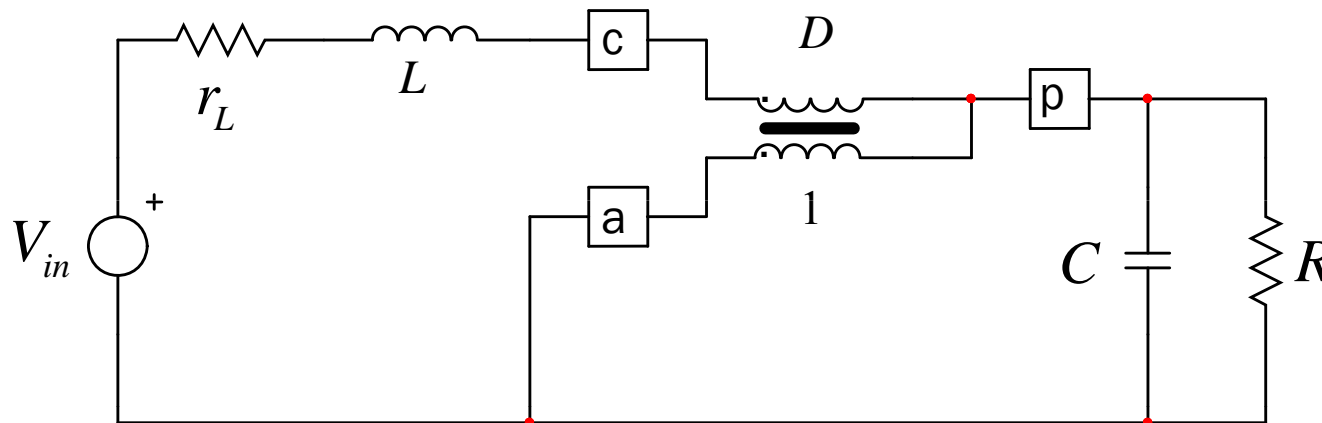- It can be plugged into any 2-switch CCM converter




Dc bias point
Ac response


CCM VM

Simulate Immediately!

- ❑ SPICE can get you the dc bias point

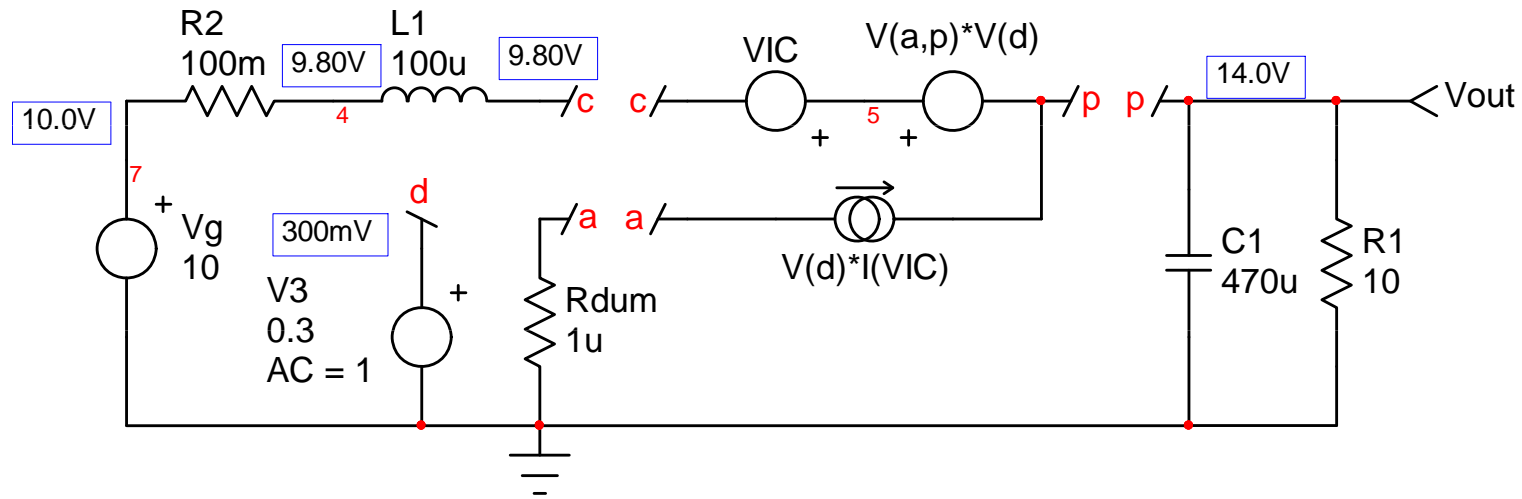

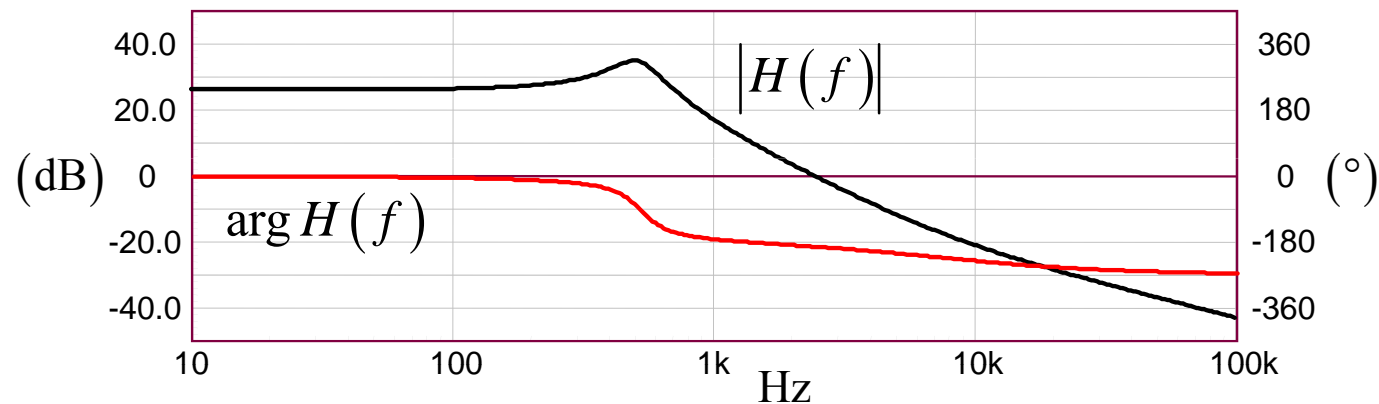
- ❑ ...but also the ac response as it linearizes the circuit





CCM

A Small-Signal Model

- We need a small-signal version to get the ac response
- ❖ Perturb equations or run partial differentiation

I_a  DI_c $\xrightarrow{\text{2 variables}}$ $\hat{i}_a = \frac{\partial f(D, I_c)}{\partial D} \hat{d} + \frac{\partial f(D, I_c)}{\partial I_c} \hat{i}_c \xrightarrow{\hspace{2cm}}$ $\hat{i}_a = I_c \hat{d} + D \hat{i}_c$

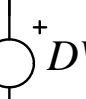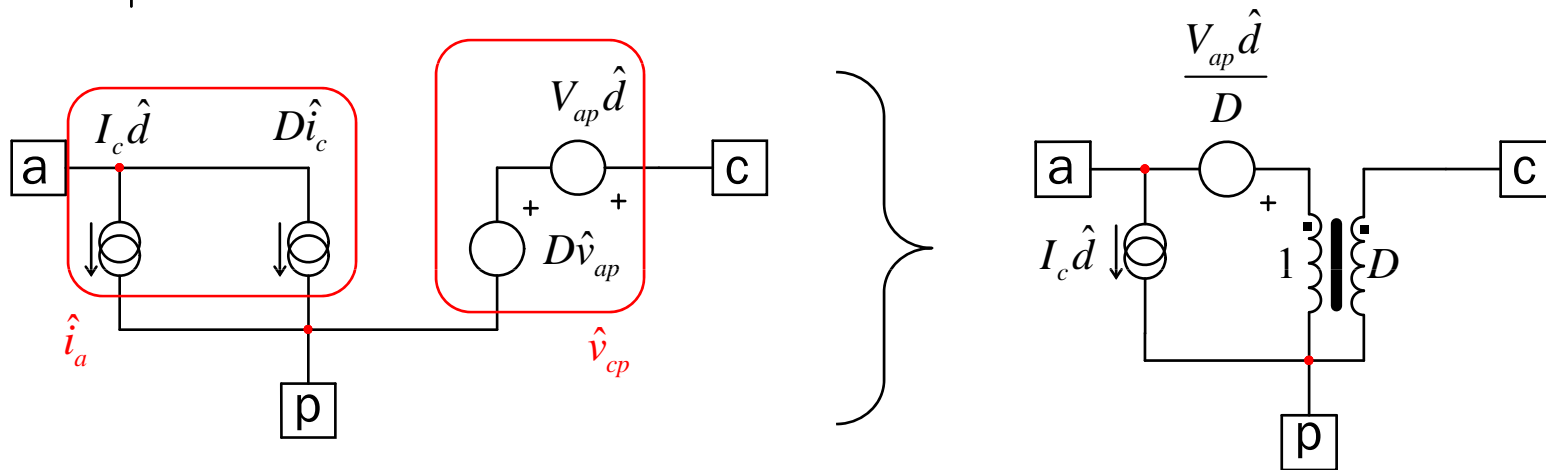V_{cp}  DV_{ap} $\xrightarrow{\text{2 variables}}$ $\hat{v}_{cp} = \frac{\partial f(D, V_{ap})}{\partial D} \hat{d} + \frac{\partial f(D, V_{ap})}{\partial V_{ap}} \hat{v}_{ap} \xrightarrow{\hspace{2cm}}$ $\hat{v}_{cp} = V_{ap} \hat{d} + D \hat{v}_{ap}$



Small-signal model

CCM




Course Agenda

- What is a Transfer Function?
- Why do We Need New Analytical Techniques?
- Time Constants and Poles
- Identifying the Zeros
- The Null Double Injection
- 2nd-Order Networks
- The PWM Switch Model
- A CCM Buck in Voltage Mode**
- A CCM Buck-Boost in Voltage Mode




A Buck Converter

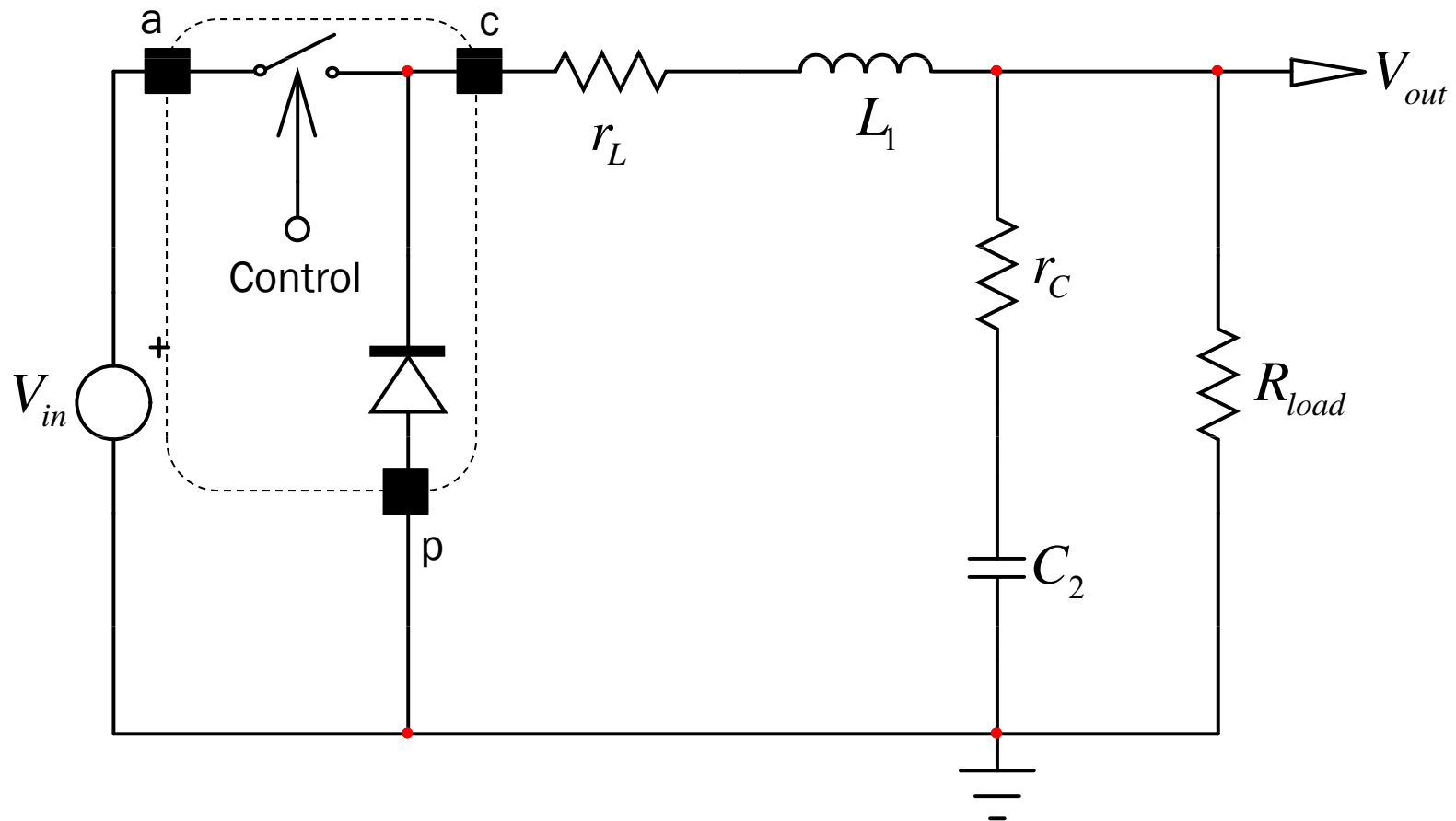- Replace the diode and the switch by the model



Model at Work in a Buck Converter

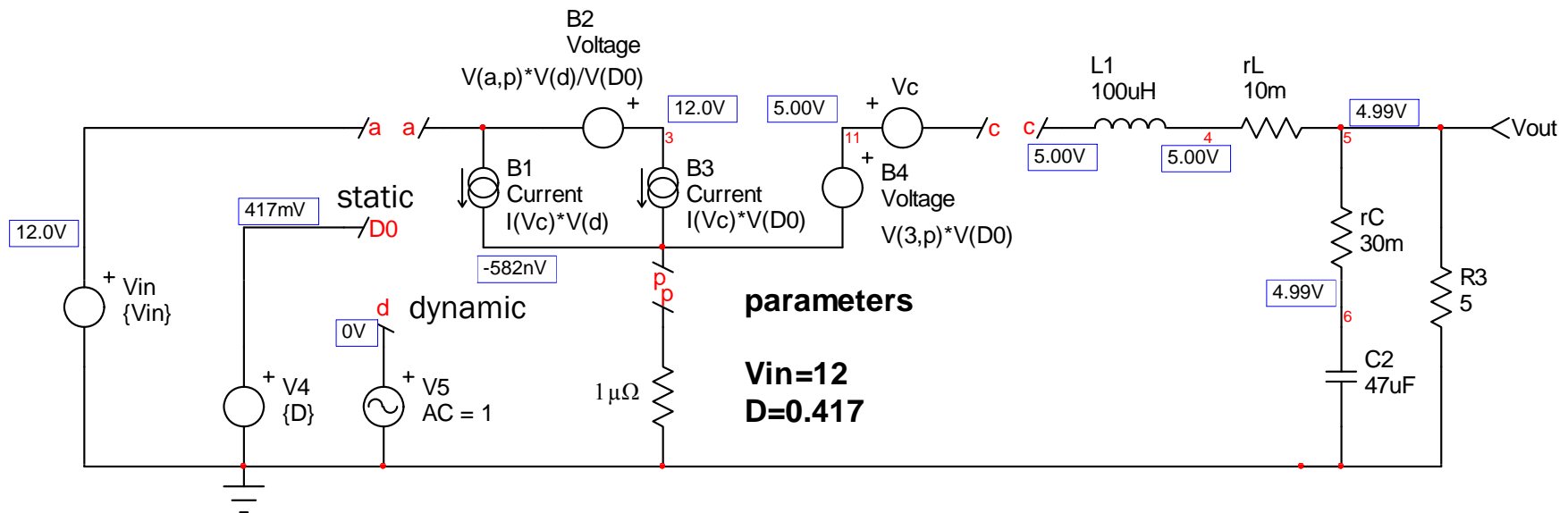- ❑ Plug the invariant small-signal model: all linear!



- ❑ We want the ac control-to-output transfer function


$$\left. \frac{V_{out}(s)}{D(s)} \right|_{\hat{v}_{in}=0}$$

Set node a to 0 V
 Node p is ground
 $V(a, p) = V_{in}$

Simplify schematic

Redraw the Simplified Circuit

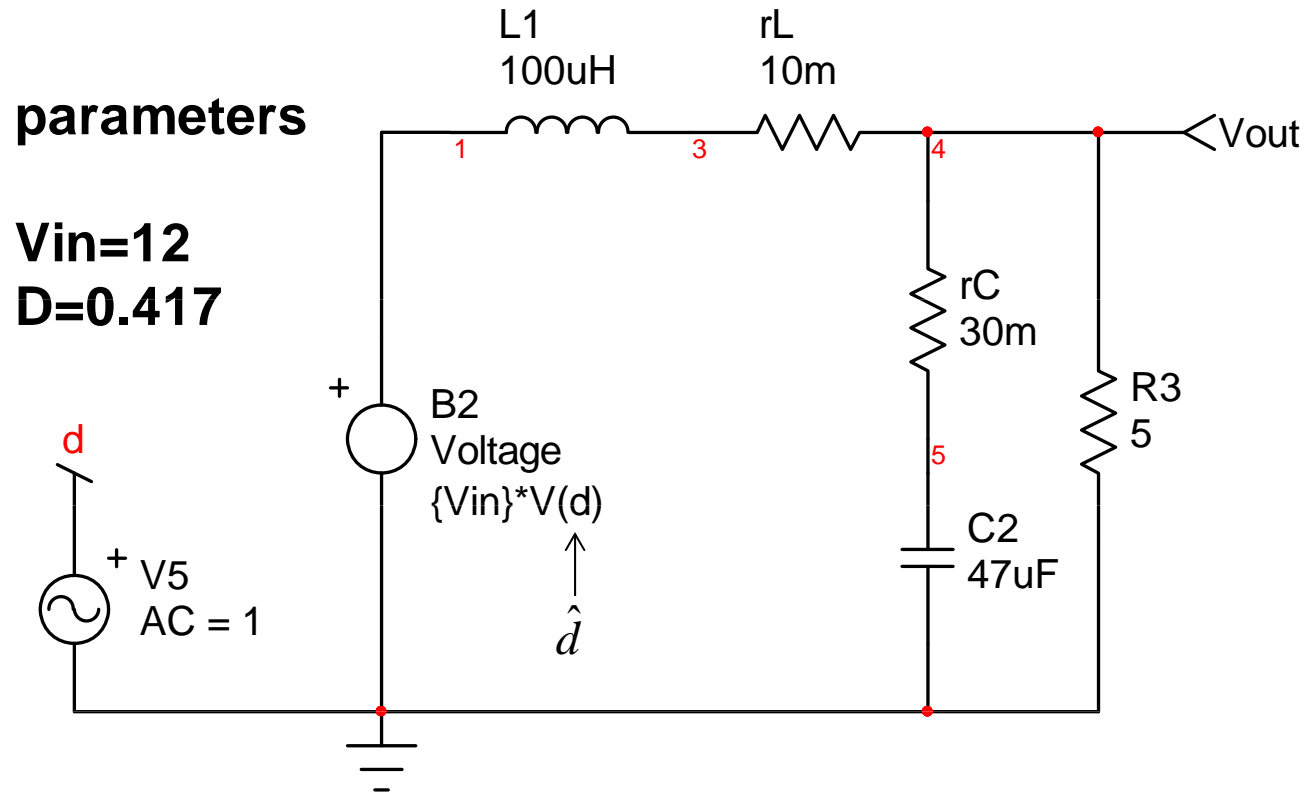- Ac contribution from the input is not the subject





- Setting d to 0 V turns the excitation off

Control-to-output

A Familiar Architecture

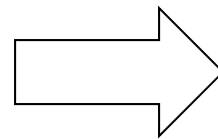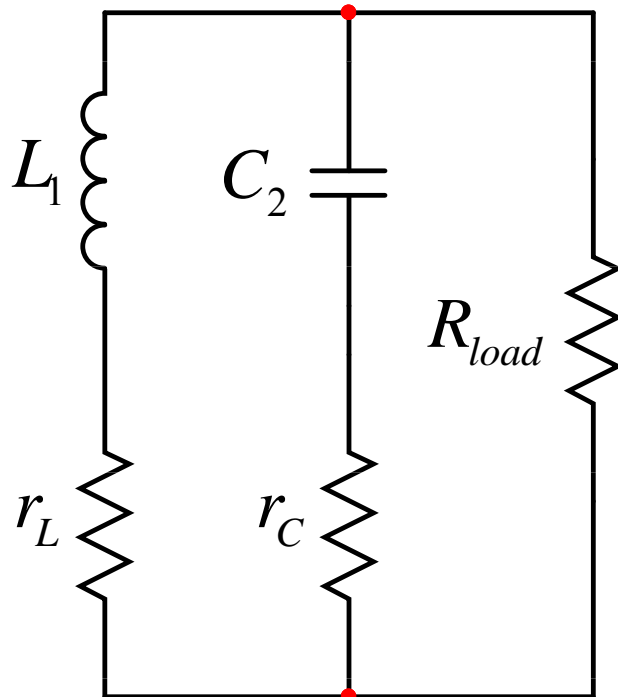- The circuit returns to its natural structure



$$D(s) = 1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0} \right)^2$$

$$\omega_0 = \frac{1}{\sqrt{L_1 C_2}} \sqrt{\frac{r_L + R_{load}}{r_C + R_{load}}}$$

$$Q = \frac{L_1 C_2 \omega_0 (r_C + R_{load})}{L_1 + C_2 (r_L r_C + r_L R_{load} + r_C R_{load})}$$


- You can reuse the denominator previously determined

Control-to-output



Determine the Gain in Dc

- Open the capacitor, short the inductor

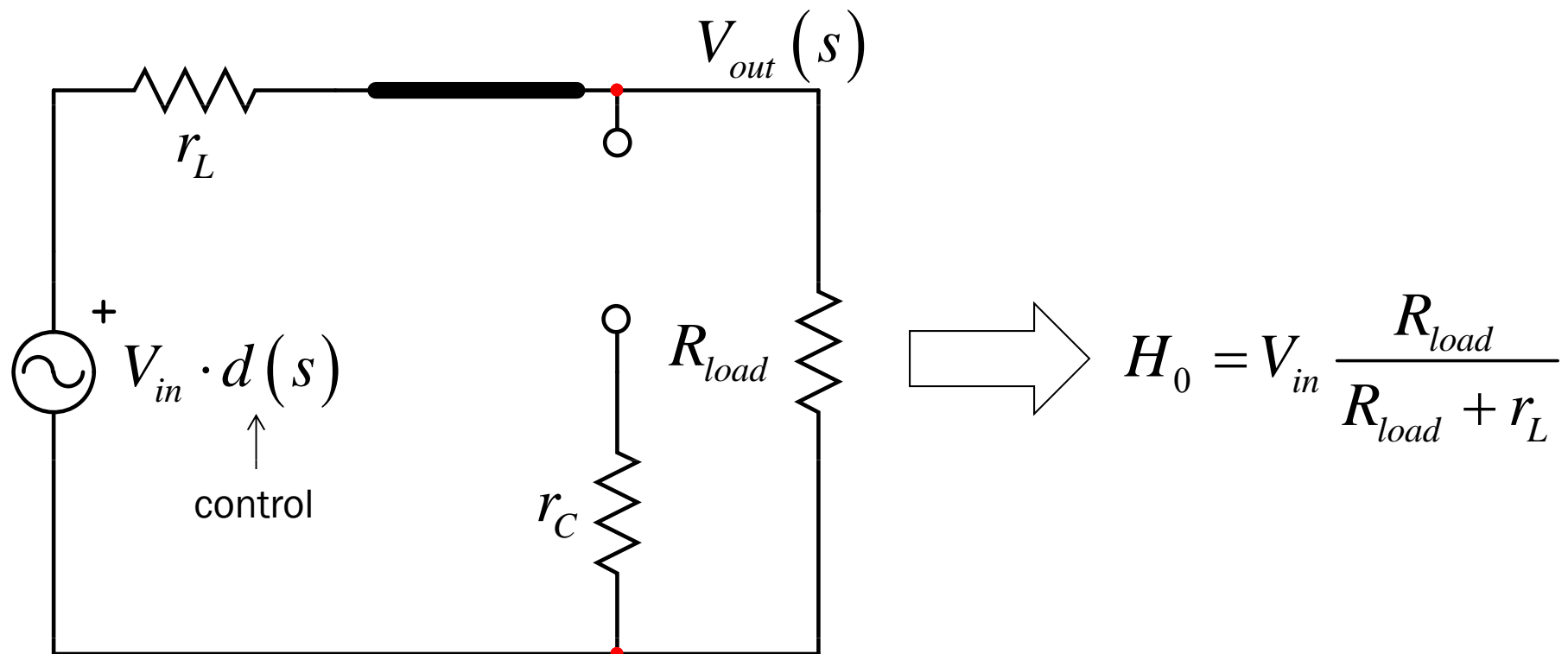


- Losses from the MOSFET and the diode could be added

Control-to-output

Determining the Zeros

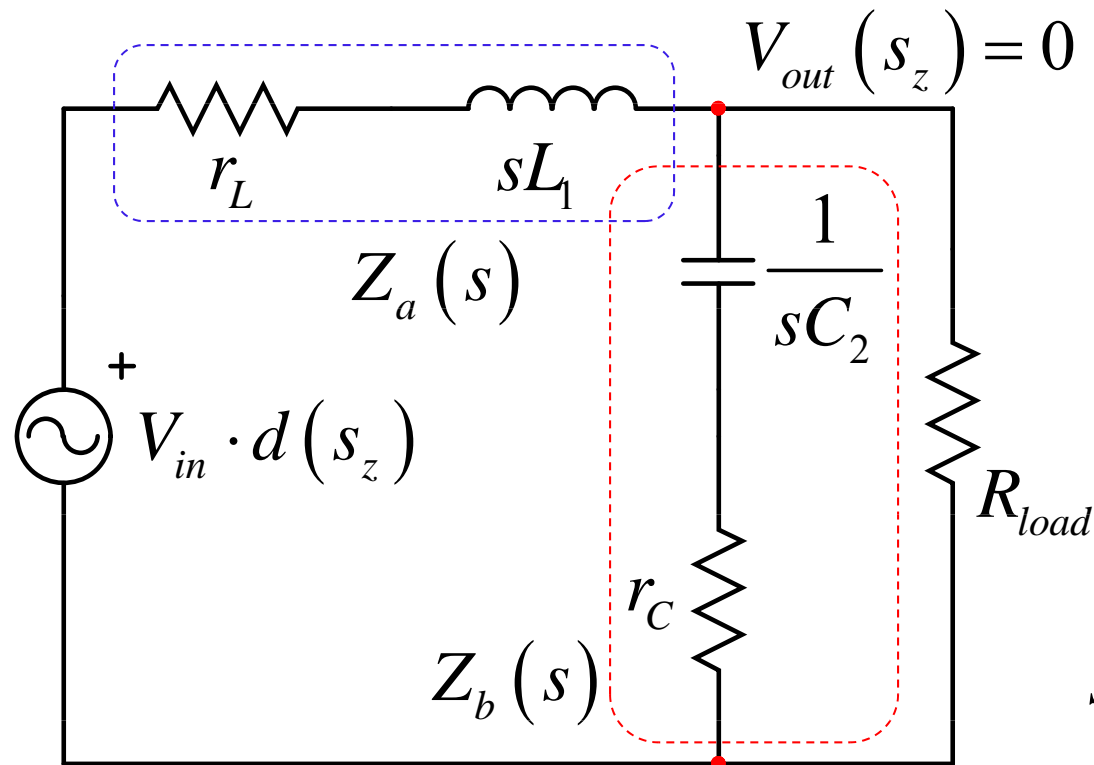- The response is canceled if $Z_2(s_z)$ is a transformed short



$$sL_1 + r_L \rightarrow \infty \quad \text{Non !}$$

$$r_C + \frac{1}{sC_2} = \frac{sr_C C_2 + 1}{sC_2} = 0?$$

↓

Oui !

$$s_z = -\frac{1}{r_C C_2} \quad \omega_z = \frac{1}{r_C C_2}$$

- Observe the transformed network at $s = s_z$

Control-to-output

Final Response

- Assemble the pieces to form $H(s)$

$$\frac{V_{out}(s)}{D(s)} = H_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2} \quad \omega_z = \frac{1}{r_C C_2} \quad H_0 = V_{in} \frac{R_{load}}{R_{load} + r_L}$$

$$\omega_0 = \frac{1}{\sqrt{L_1 C_2}} \sqrt{\frac{r_L + R_{load}}{r_C + R_{load}}} \quad Q = \frac{L_1 C_2 \omega_0 (r_C + R_{load})}{L_1 + C_2 (r_L r_C + r_L R_{load} + r_C R_{load})}$$

- Compare low-entropy form with raw formula

$$H_{ref}(s) = V_{in} \frac{R_L \parallel Z_b(s)}{Z_a(s) + R_L \parallel Z_b(s)}$$

Control-to-output



Test with Mathcad is Simple and Fast

$$r_L := 0.01\Omega \quad r_C := 0.03\Omega \quad C_2 := 47\mu\text{F} \quad L_1 := 100\mu\text{H} \quad R_L := 5\Omega \quad \|(x,y) := \frac{x \cdot y}{x + y}$$

$$V_{in} := 12\text{V} \quad V_p := 1\text{V} \quad H_0 := \frac{V_{in}}{V_p} \cdot \frac{R_L}{R_L + r_L} = 11.976 \quad 20 \cdot \log(H_0) = 21.566$$

$$\tau_1 := \frac{L_1}{r_L + R_L} = 19.96\mu\text{s} \quad \tau_2 := C_2 \cdot (r_L \parallel R_L + r_C) = 1.879 \times 10^3 \cdot \text{ns}$$

$$a_1 := \tau_1 + \tau_2 = 21.839\mu\text{s}$$

$$\tau_{12} := C_2 \cdot (r_C + R_L) = 236.41\mu\text{s} \quad \tau_{21} := \frac{L_1}{r_L + R_L \parallel r_C} = 2.511 \times 10^3 \cdot \mu\text{s}$$

$$a_2 := \tau_1 \cdot \tau_{12} = 4.719 \times 10^3 \cdot \mu\text{s}^2$$


$$N_1(s) := 1 + s \cdot r_C \cdot C_2 \quad D_1(s) := 1 + a_1 \cdot s + a_2 \cdot s^2 \quad H_1(s) := H_0 \cdot \frac{N_1(s)}{D_1(s)}$$

$$\omega_{z2} := \frac{1}{r_C \cdot C_2} \quad \omega_0 := \frac{1}{\sqrt{L_1 \cdot C_2}} \cdot \sqrt{\frac{r_L + R_L}{r_C + R_L}} \quad Q := \frac{L_1 \cdot C_2 \cdot \omega_0 \cdot (r_C + R_L)}{L_1 + C_2 \cdot (r_L \cdot r_C + r_L \cdot R_L + r_C \cdot R_L)}$$


$$H_2(s) := H_0 \cdot \frac{1 + \frac{s}{\omega_{z2}}}{1 + \frac{s}{\omega_0 \cdot Q} + \left(\frac{s}{\omega_0}\right)^2}$$

$$Z_a(s) := s \cdot L_1 + r_L \quad Z_b(s) := \frac{1}{s \cdot C_2} + r_C$$
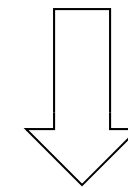
$$H_3(s) := \frac{Z_b(s) \parallel R_L}{Z_a(s) + Z_b(s) \parallel R_L} \cdot \frac{V_{in}}{V_p}$$




All curves
superimpose!

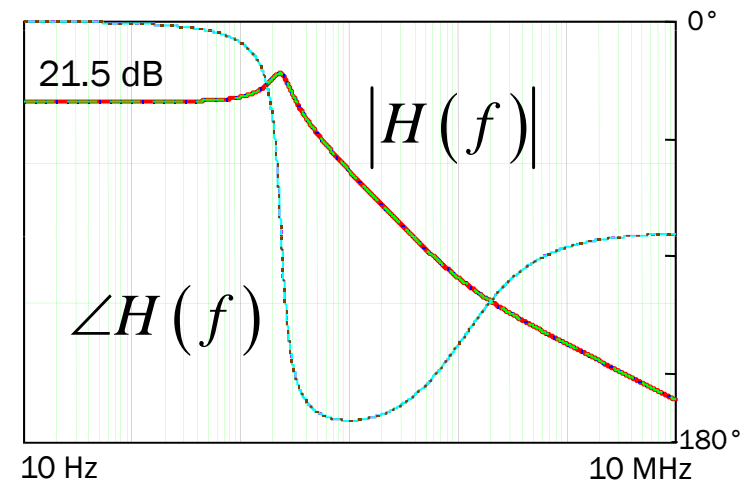


Input to Output Transfer Function

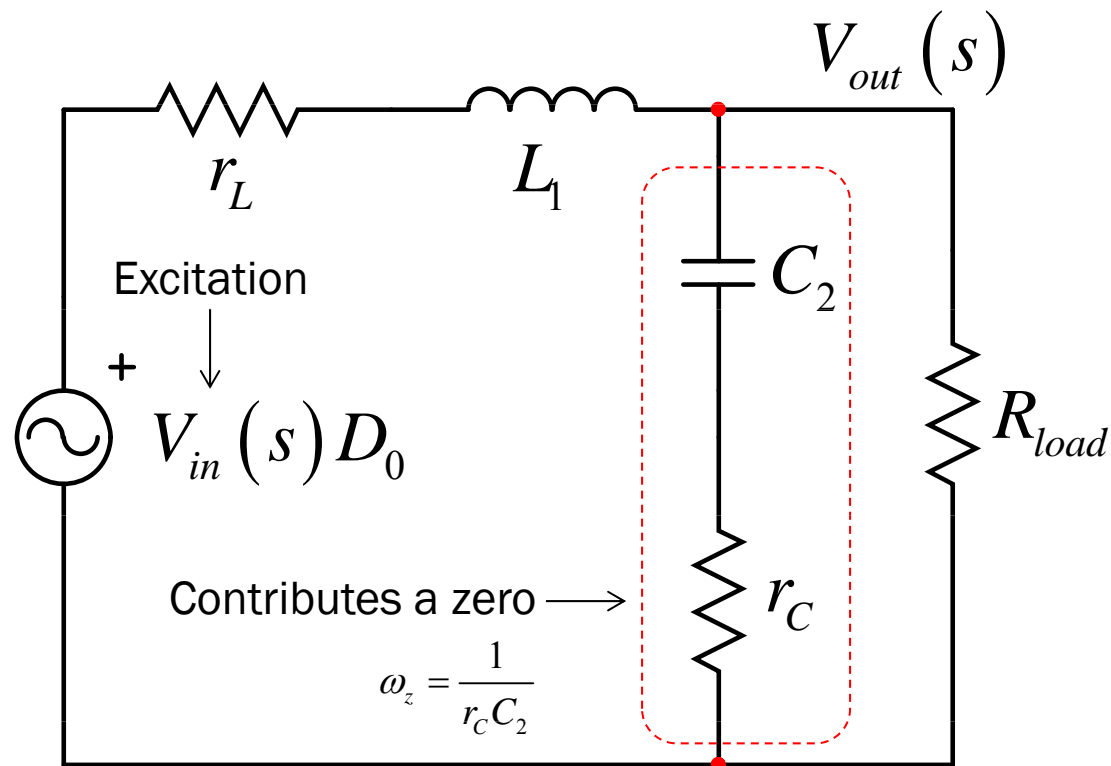- We can set \hat{d} to 0 and check V_{out} to V_{in}



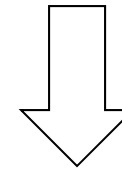Set L_1 as a short circuit
open capacitor C_2



$$H_0 = D_0 \frac{R_{load}}{R_{load} + r_L}$$

- For $V_{in} = 0$, same structure as before, reuse $D(s)$!

Input-to-output

Transfer Function is Immediate


- Reuse existing formula and build transfer function

$$\frac{V_{out}(s)}{V_{in}(s)} = H_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

$$\omega_z = \frac{1}{r_C C_2} \quad H_0 = D_0 \frac{R_{load}}{R_{load} + r_L}$$

$$Q = \frac{L_1 C_2 \omega_0 (r_C + R_{load})}{L_1 + C_2 (r_L r_C + r_L R_{load} + r_C R_{load})}$$
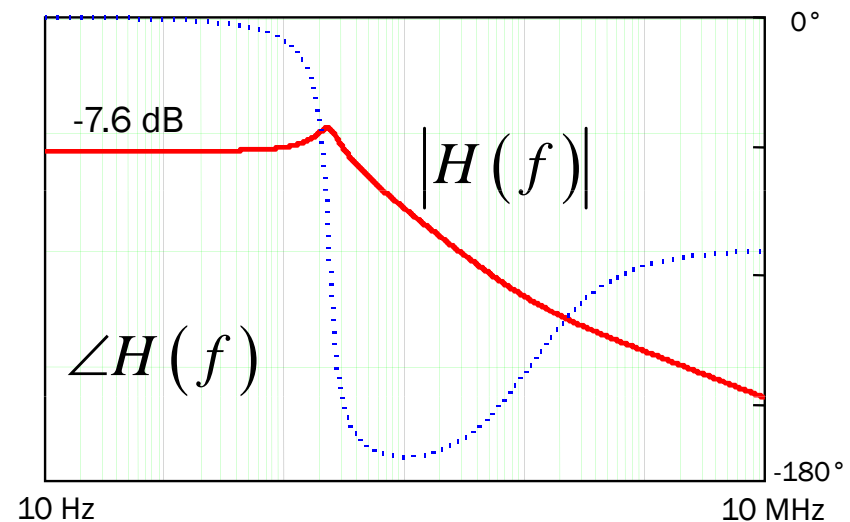
$$\omega_0 = \frac{1}{\sqrt{L_1 C_2}} \sqrt{\frac{r_L + R_{load}}{r_C + R_{load}}}$$




Input-to-output



Buck Input Impedance

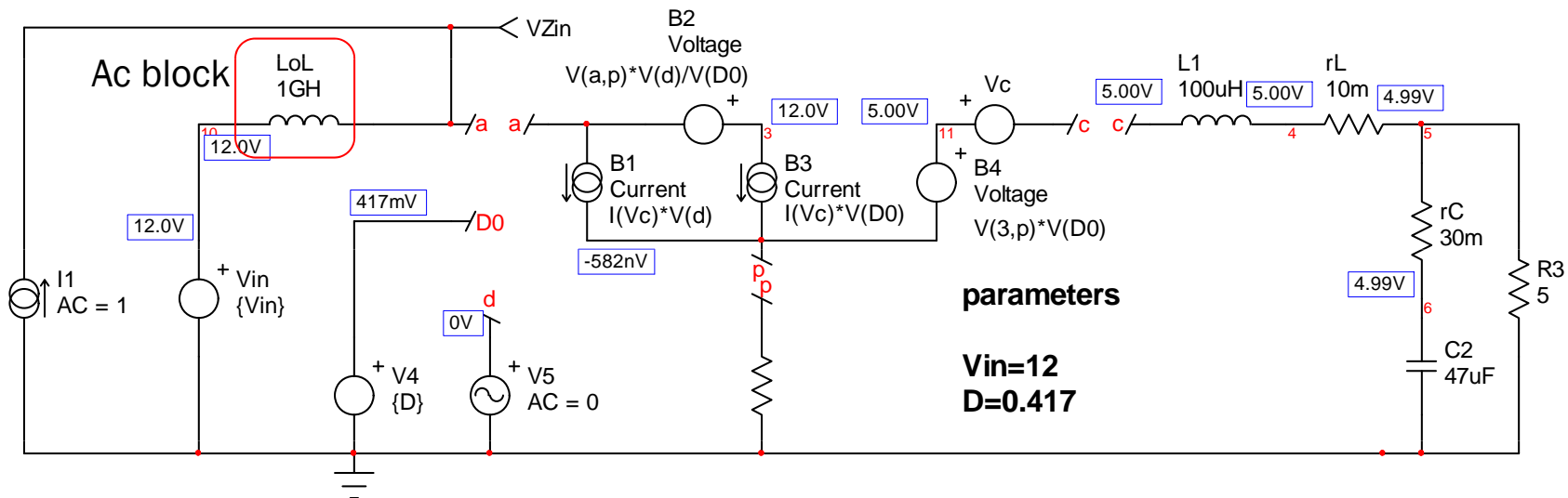- Inductance LoL lets you sweep the input to have Z_{in}



- In this mode, \hat{d} is equal to zero

$$\left. \frac{V_{in}(s)}{I_{in}(s)} \right|_{\hat{d}=0}$$


Source B2 and B1 are zero
Node p is ground
 $V(a, p) = V_{in}$

Simplify schematic
Check ac response

Input impedance


Simplifying and Rearranging is Key

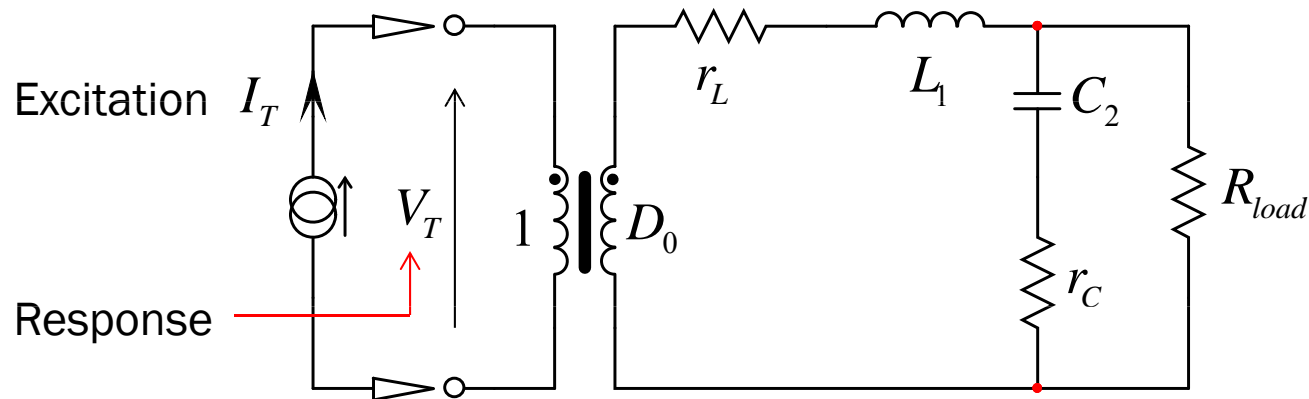- Install the dc transformer to obtain Z_{in}



$$Z_{in}(s) = \frac{V_T(s)}{I_{in}(s)}$$


- Reflect elements to the primary side

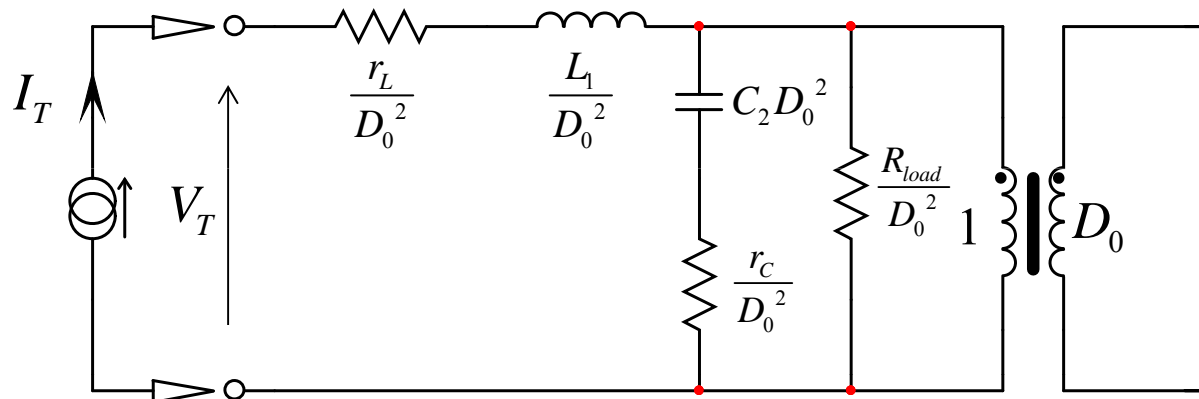



Input impedance

Start with $s = 0$

- Short the inductor, open the capacitor

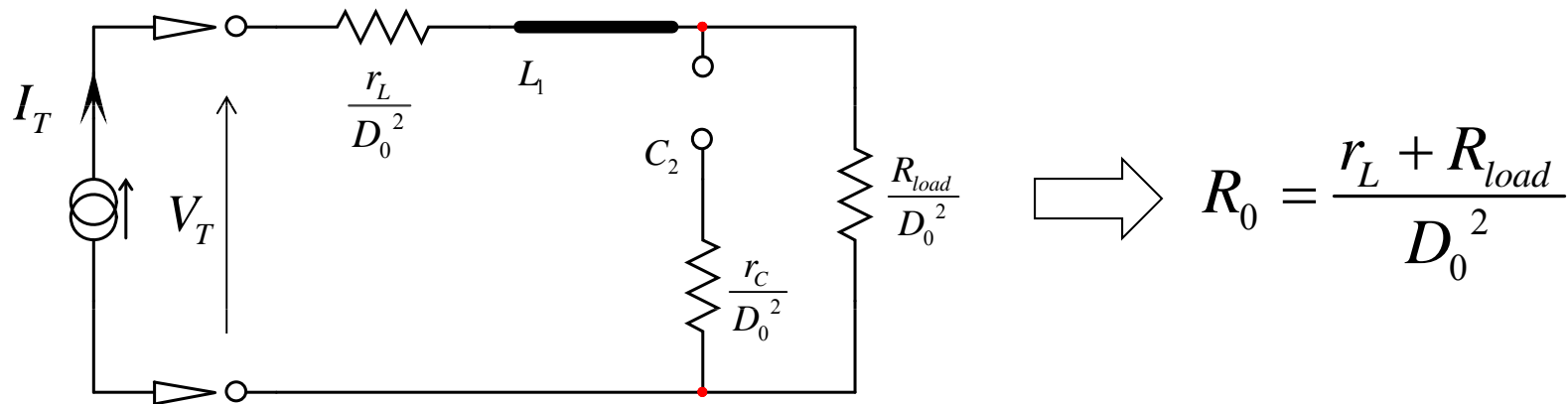

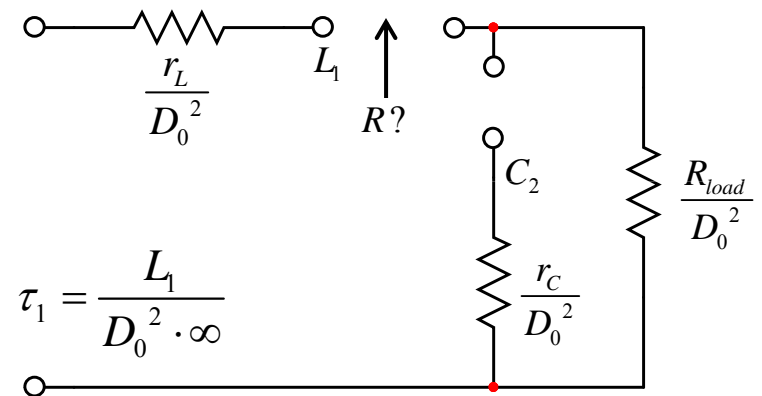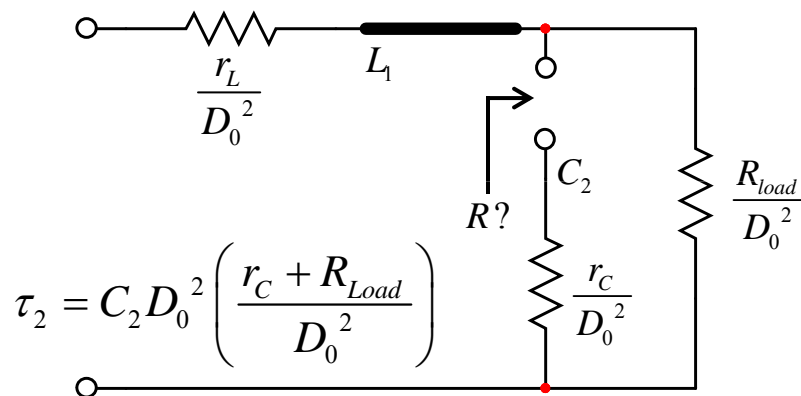- For the time constants, suppress the excitation, $I_T = 0$




Input impedance



Higher Order Coefficients

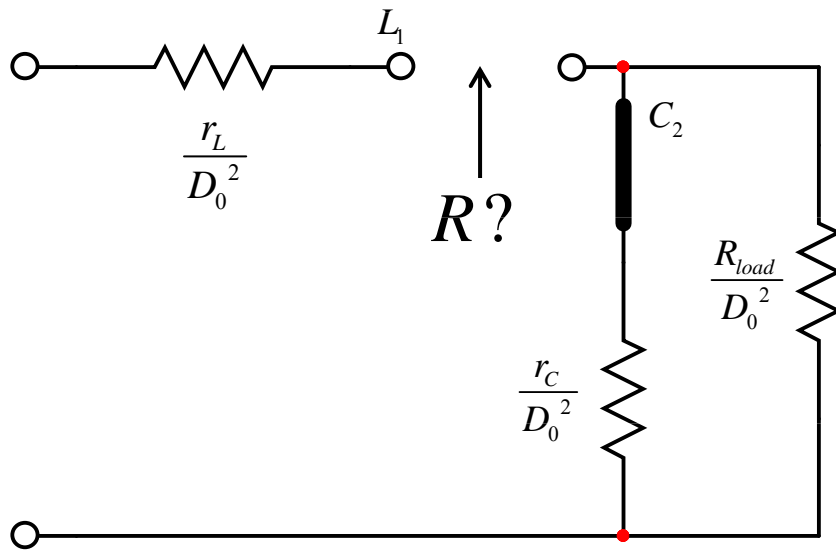- ❑ Avoid indeterminacy with τ_1 : use τ_2 instead
- ❑ Determine τ_1^2



$\tau_1^2 \xrightarrow{\text{High-frequency state}} R?$

$$\tau_1^2 = \frac{L_1}{D_0^2 \cdot \infty}$$

$$\tau_2 \tau_1^2 = C_2 D_0^2 \left(\frac{r_C + R_{Load}}{D_0^2} \right) \frac{L_1}{D_0^2 \cdot \infty} = 0$$


$$\Rightarrow D(s) = 1 + \left[C_2 D_0^2 \left(\frac{r_C + R_{Load}}{D_0^2} \right) + \frac{L_1}{D_0^2 \cdot \infty} \right] s = 1 + s C_2 (r_C + R_{Load})$$

Input impedance

The Numerator is Already Known

□ Null the response across the current source

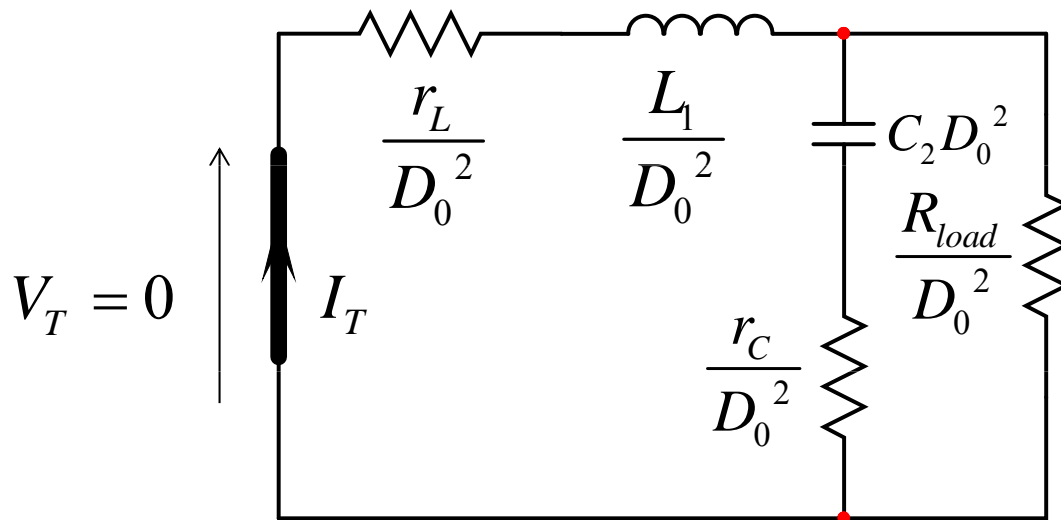→ Degenerate case, short the generator's terminals!



Same network structure as in slide 114!

$$N(s) = 1 + s \left(\frac{L_1}{r_L + R_{load}} + C_2 \left[(r_L \parallel R_{load}) + r_C \right] \right) + s^2 \left(L_1 C_2 \frac{r_C + R_{load}}{r_L + R_{load}} \right)$$

Input impedance

Assemble the Pieces


- The transfer function dimension is now in ohms

$$Z_{in}(s) = R_0 \frac{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}{1 + \frac{s}{\omega_p}}$$

$$\omega_p = \frac{1}{(r_C + R_{Load})C_2} \quad R_0 = \frac{r_L + R_{load}}{D_0^2}$$

$$Q = \frac{L_1 C_2 \omega_0 (r_C + R_{load})}{L_1 + C_2 (r_L r_C + r_L R_{load} + r_C R_{load})}$$
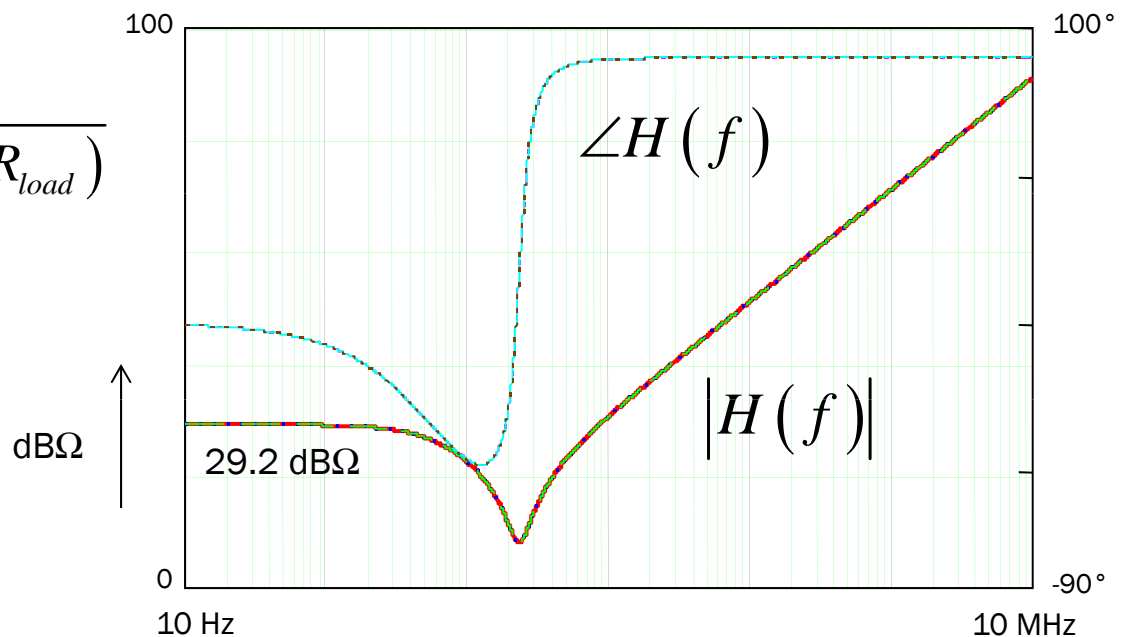
$$\omega_0 = \frac{1}{\sqrt{L_1 C_2}} \sqrt{\frac{r_L + R_{load}}{r_C + R_{load}}}$$




Course Agenda

- What is a Transfer Function?
- Why do We Need New Analytical Techniques?
- Time Constants and Poles
- Identifying the Zeros
- The Null Double Injection
- 2nd-Order Networks
- The PWM Switch Model
- A CCM Buck in Voltage Mode
- A CCM Buck-Boost in Voltage Mode**




A Buck-Boost Converter

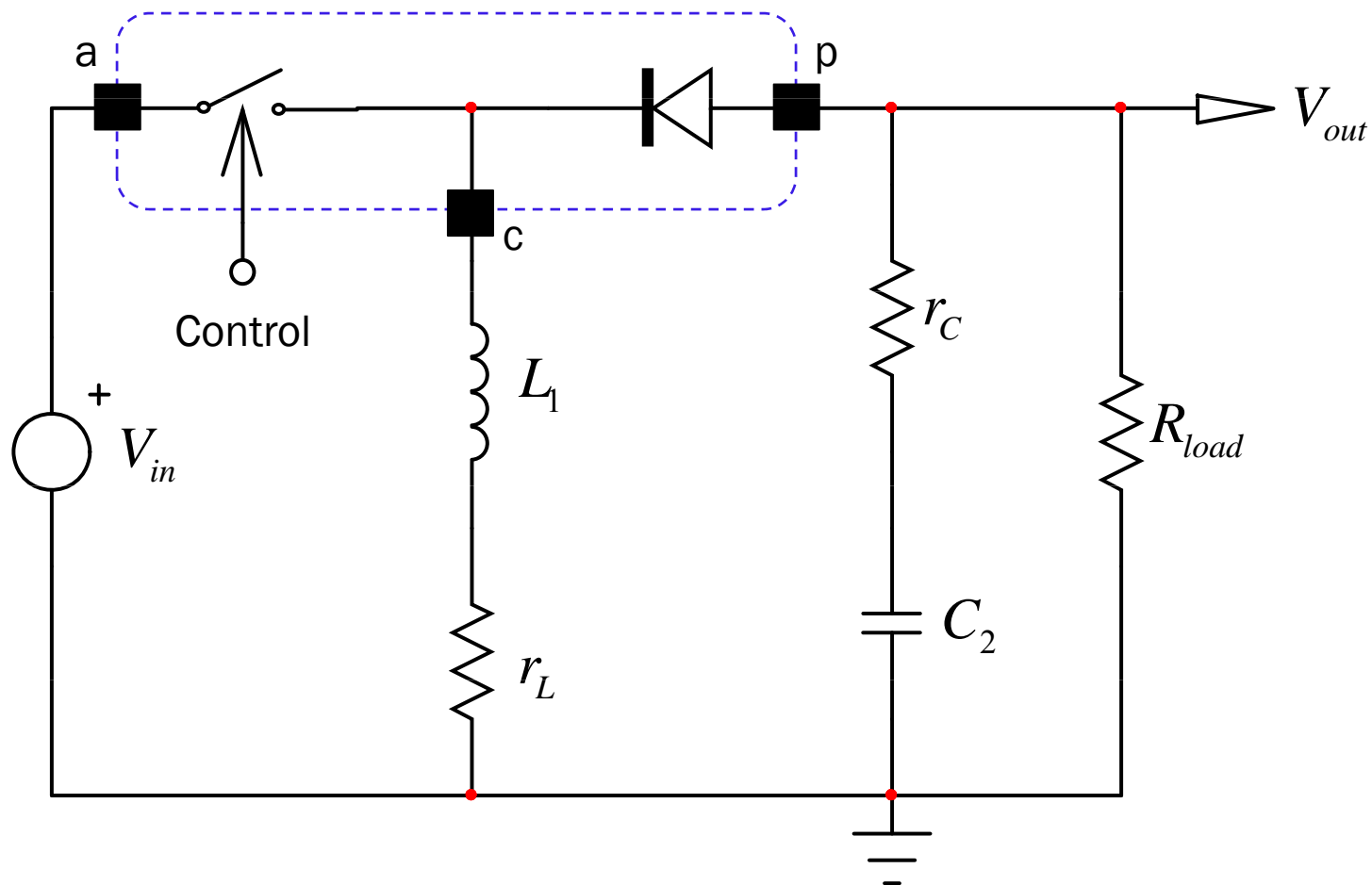- Replace the switch/diode by the PWM switch model



Modeling Switches Only

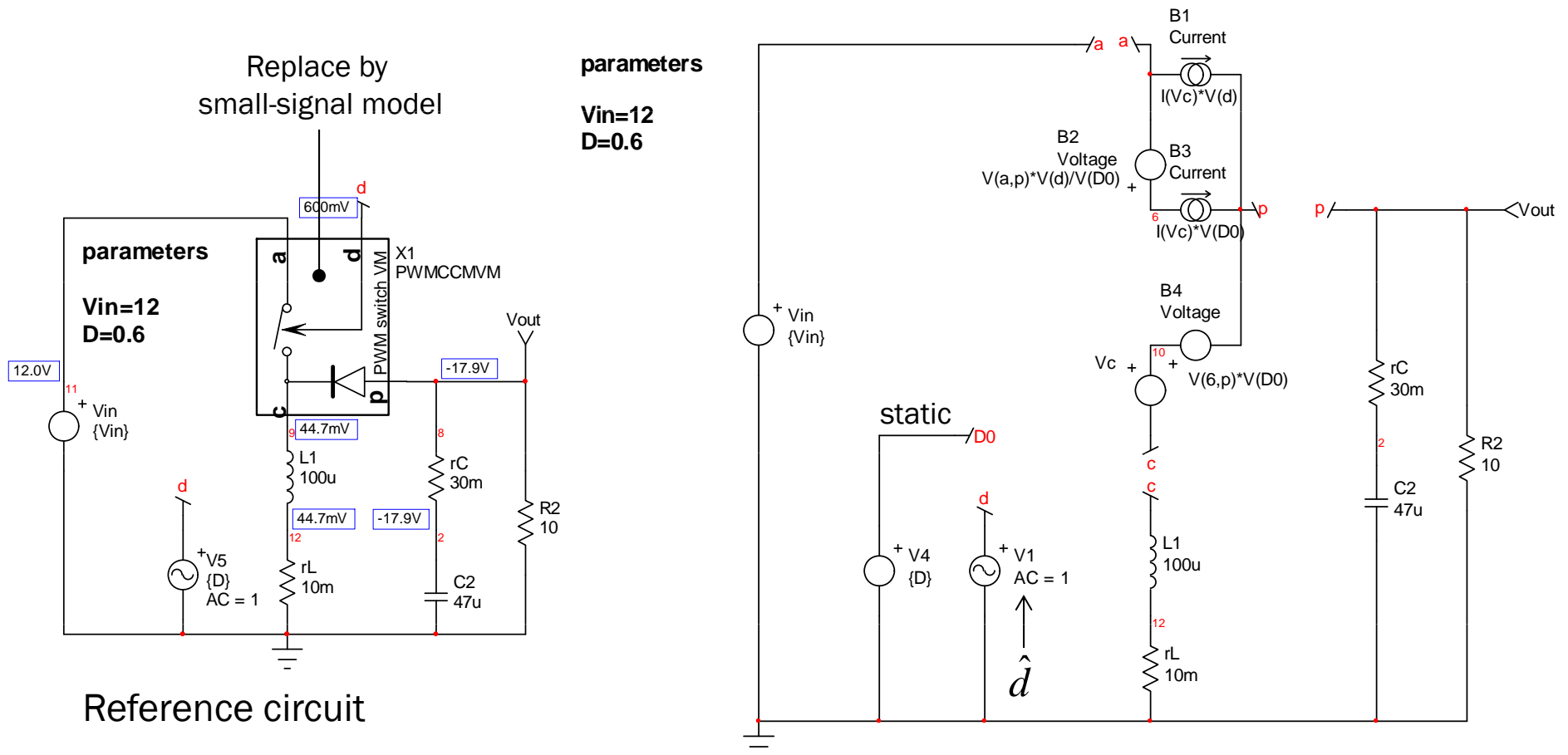- ❑ The PWM switch is invariant in small and large signals



- ❑ Always check simplifications versus reference circuit

Control to Output Transfer Function

- We want the control-to-output transfer function

parameters

$$V_{in}=12$$

$$D=0.6$$


$$V_{out}=-V_{in} \cdot D / (1-D)$$

$$R_L=10$$

$$V_{ap}=V_{in}-V_{out}$$

$$I_c=-V_{out} / (R_L \cdot (1-D))$$

$$\left. \frac{V_{out}(s)}{D(s)} \right|_{\hat{v}_{in}=0}$$

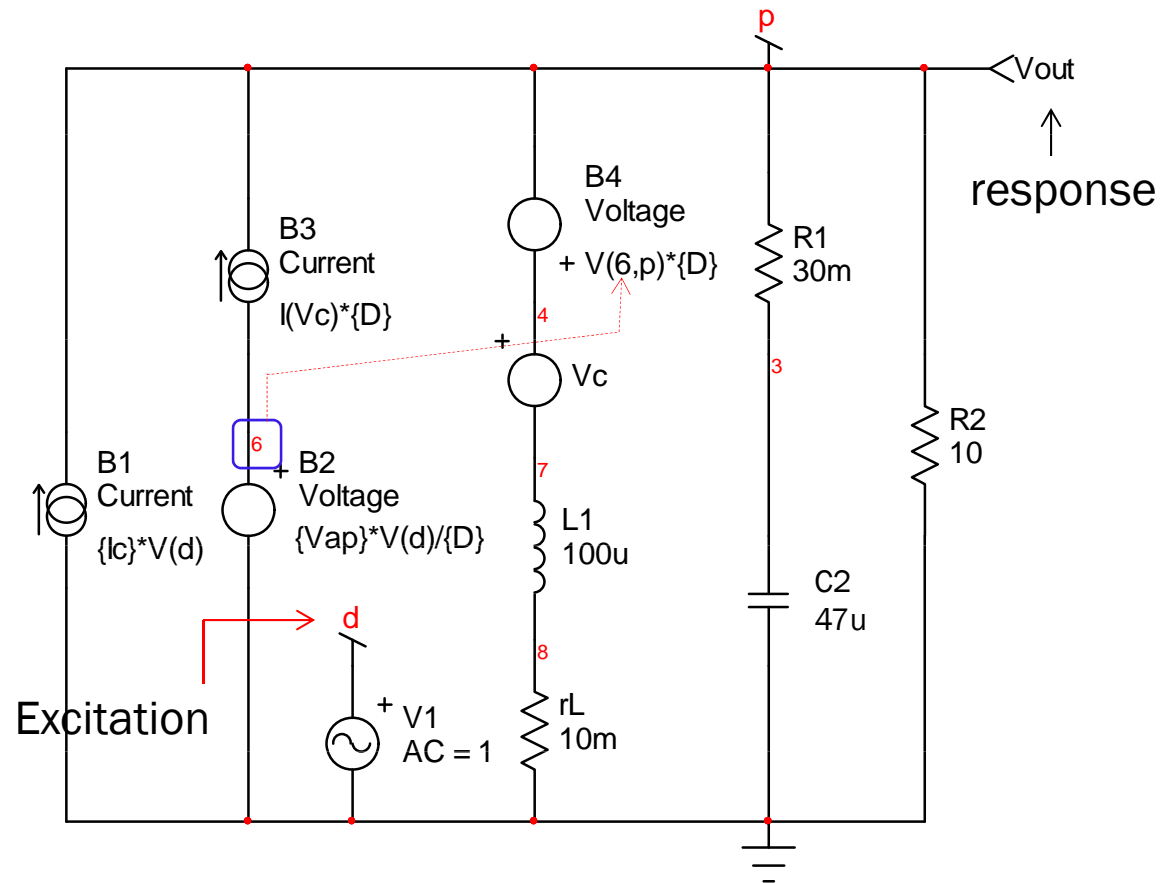

- Simplify circuit and check ac response is unchanged

Control-to-output

Simplify and Rearrange Expressions

- The final schematic is truly compact

parameters

$$V_{in}=12$$

$$D=0.6$$


$$V_{out}=-V_{in} \cdot D / (1-D)$$

$$R_L=10$$

$$V_{ap}=V_{in}-V_{out}$$

$$I_c=-V_{out} / (R_L \cdot (1-D))$$

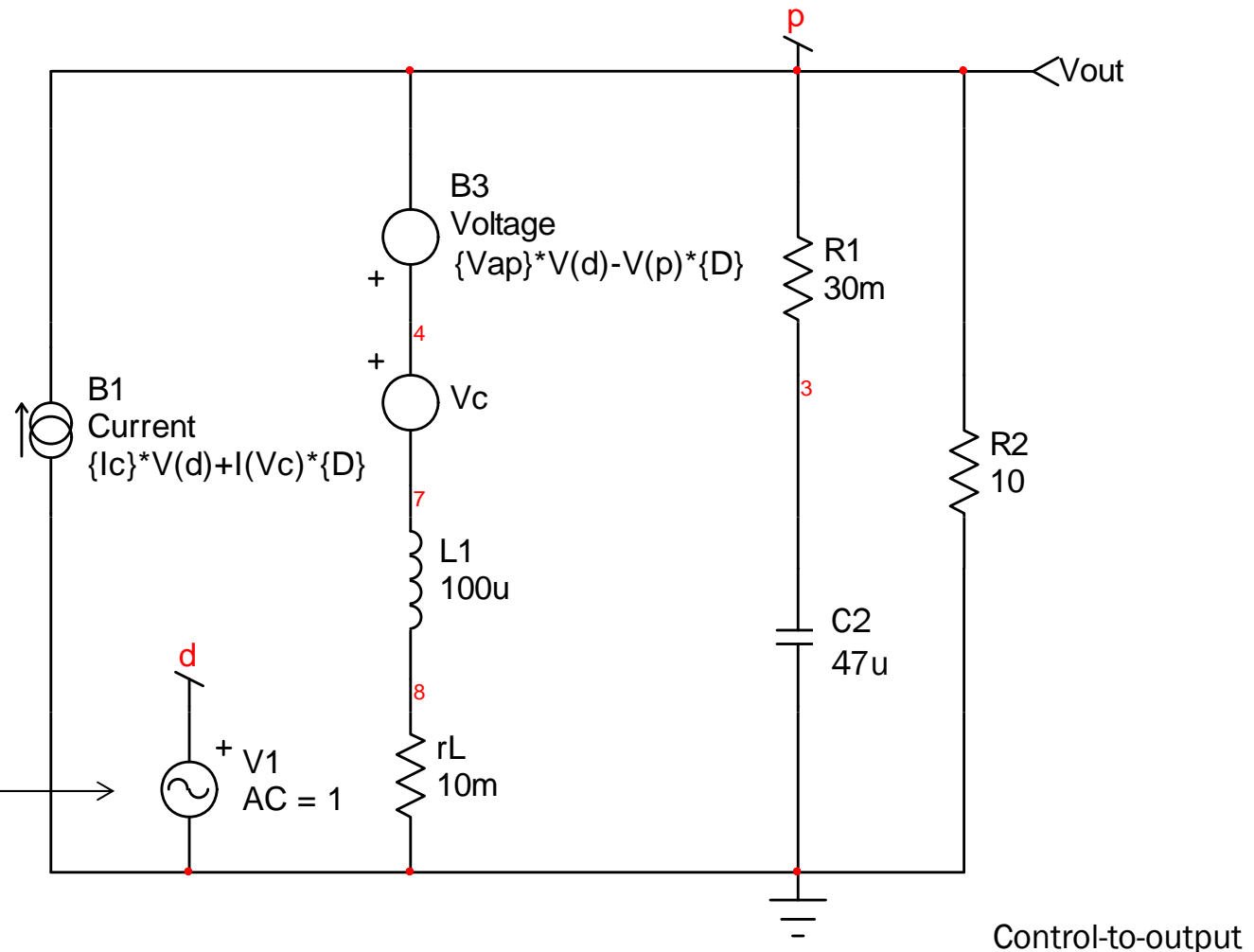response $\rightarrow V_{out}(s)$
 excitation $\rightarrow D(s)$



A Two-Storage Element Circuit

- There are two independent state variables
- This is a 2nd-order network


$$H(s) = H_0 \frac{1 + a_1s + a_2s^2}{1 + b_1s + b_2s^2}$$

1. Determine the dc gain H_0 : open capacitor and short inductor
2. b_1 equals the sum of the time constants when excitation is off
3. b_2 combines time constants product when excitation is off

➔ Assemble $D(s)$

1. Determine the zeros
- NDI or inspection


➔ Assemble $N(s)$

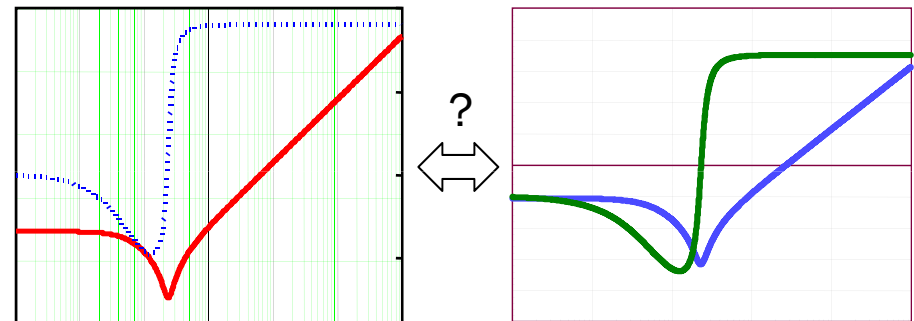

Mathcad[®] and SPICE agree?

Three Equations for the dc Gain

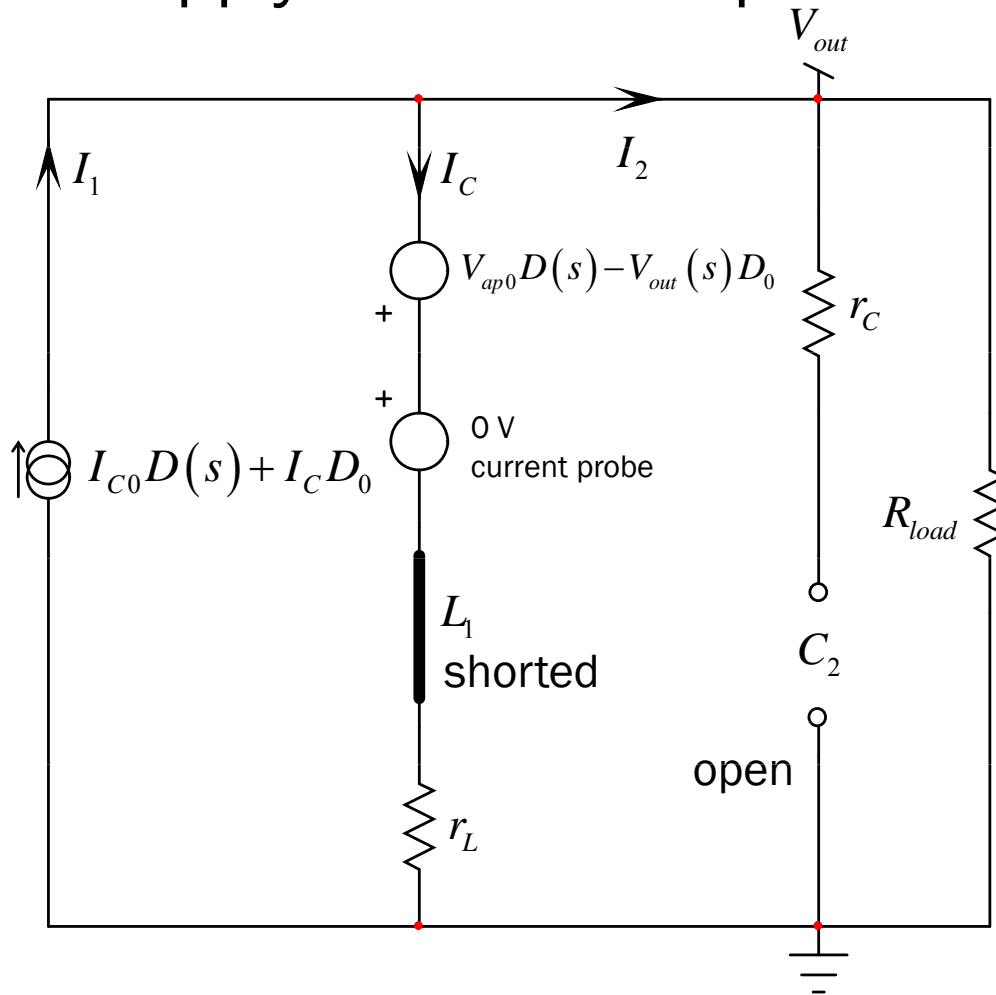- Apply KCL on a simple circuit without reactances, $s = 0$



$$I_C(s) = \frac{V_{out}(s) + V_{ap0}D(s) - V_{out}(s)D_0}{r_L}$$

$$I_2(s) = I_{C0}D(s) + I_C(s)D_0 - I_C(s)$$

$$V_{out}(s) = I_2(s)R_{load} \quad V_{ap0} = V_{in} - V_{out}$$

↓ Substitute
rearrange

$$H_0 = -\left(\frac{1}{1-D_0}\right) \frac{V_{out}r_L + R_{load}(1-D_0)^2(V_{in} - V_{out})}{r_L + R_{load}(1-D_0)^2}$$


↓ $r_L \rightarrow 0, V_{out} = -V_{in} \frac{D_0}{1-D_0}$

$$H_0 \approx -\frac{V_{in}}{(1-D_0)^2}$$

Control-to-output

Excitation is Turned off - τ_1

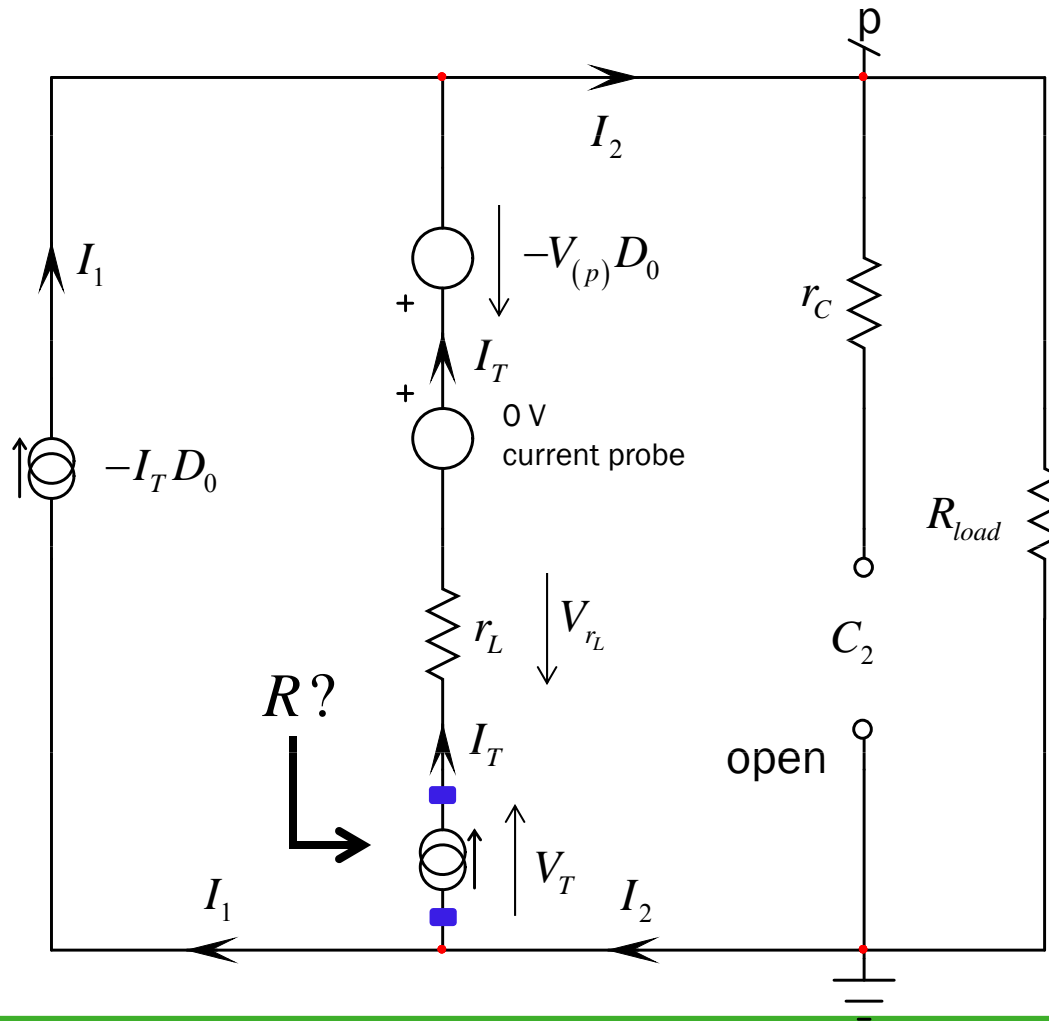- All expressions featuring \hat{d} or $D(s)$ are set to 0



$$V_{(p)} = I_2 R_{load} = (I_1 + I_T) R_{load}$$

$$V_{(p)} = I_T (1 - D_0) R_{load}$$

$$V_T = V_{(p)} - V_{(p)} D_0 + r_L I_T$$

Substitute
rearrange


$$R = \frac{V_T}{I_T} = r_L + (1 - D_0)^2 R_{load}$$

$$\tau_1 = \frac{L_1}{r_L + (1 - D_0)^2 R_{load}}$$

Control-to-output

Excitation is Turned off - τ_2

□ The inductor is now shorted

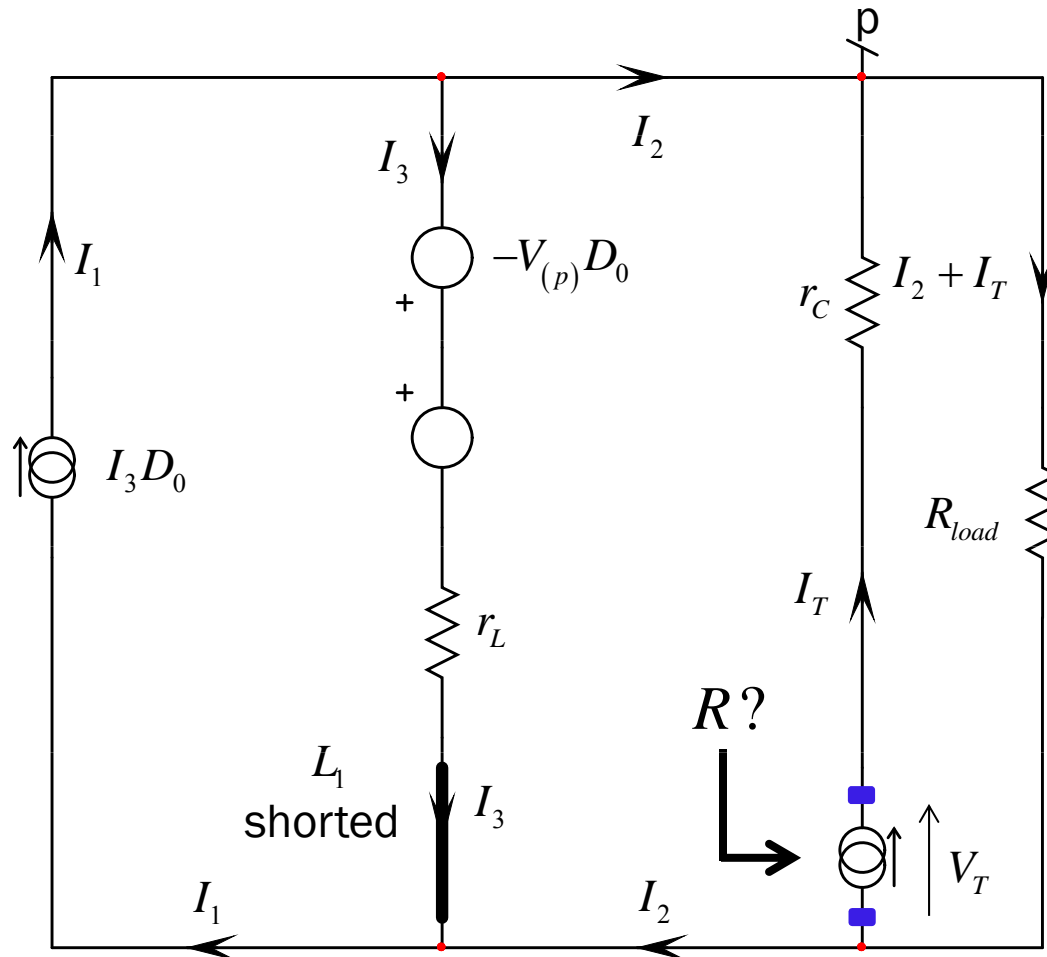

$$I_2 = I_1 - I_3 = I_3 (D_0 - 1)$$

$$I_3 = \frac{V_{(p)} - V_{(p)} D_0}{r_L} = \frac{V_{(p)} (1 - D_0)}{r_L}$$

$$V_{(p)} = R_{load} (I_2 + I_T)$$

$$V_T = I_T r_C + V_{(p)}$$

Substitute
rearrange

$$R = \frac{V_T}{I_T} = r_C + \frac{R_{load} r_L}{R_{load} (1 - D_0)^2 + r_L}$$


↓

$$\tau_2 = C_2 \left(r_C + \frac{R_{load} r_L}{R_{load} (1 - D_0)^2 + r_L} \right)$$

Control-to-output

Which Combination: $\tau_1 \tau_2^1$ or $\tau_2 \tau_1^2$?

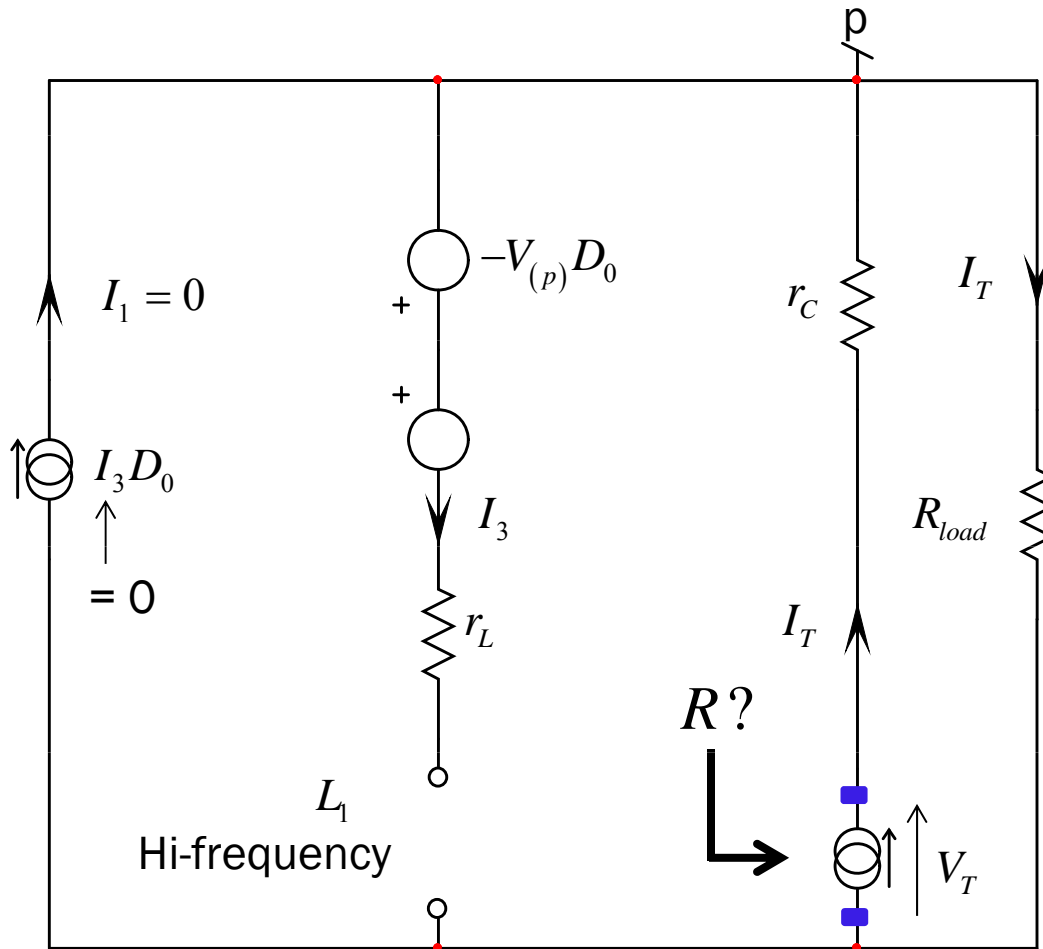- Open the inductor: simplest configuration is τ_2^1



$$\tau_2^1 = C_2 (r_C + R_{load})$$

Combine with
 τ_1

$$\tau_1 = \frac{L_1}{r_L + (1 - D_0)^2 R_{load}}$$

$$b_2 = \tau_1 \tau_2^1 = \frac{L_1}{r_L + (1 - D_0)^2 R_{load}} C_2 (r_C + R_{load})$$

Control-to-output

Denominator Expression

□ The 2nd-order denominator can be formed

$$b_1 = \tau_1 + \tau_2 = \frac{L_1}{r_L + (1 - D_0)^2 R_{load}} + C_2 \left(r_C + \frac{R_{load} r_L}{R_{load} (1 - D_0)^2 + r_L} \right)$$

$$b_2 = \tau_1 \tau_2 = \frac{L_1}{r_L + (1 - D_0)^2 R_{load}} C_2 (r_C + R_{load})$$


$$D(s) = 1 + \left[\frac{L_1}{r_L + (1 - D_0)^2 R_{load}} + C_2 \left(r_C + \frac{R_{load} r_L}{R_{load} (1 - D_0)^2 + r_L} \right) \right] s + \left[\frac{L_1}{r_L + (1 - D_0)^2 R_{load}} C_2 (r_C + R_{load}) \right] s^2$$

⇒ $H(s) = H_0 \frac{N(s)}{1 + b_1 s + b_2 s^2}$ Zeros are missing!


Control-to-output

Determining the Numerator

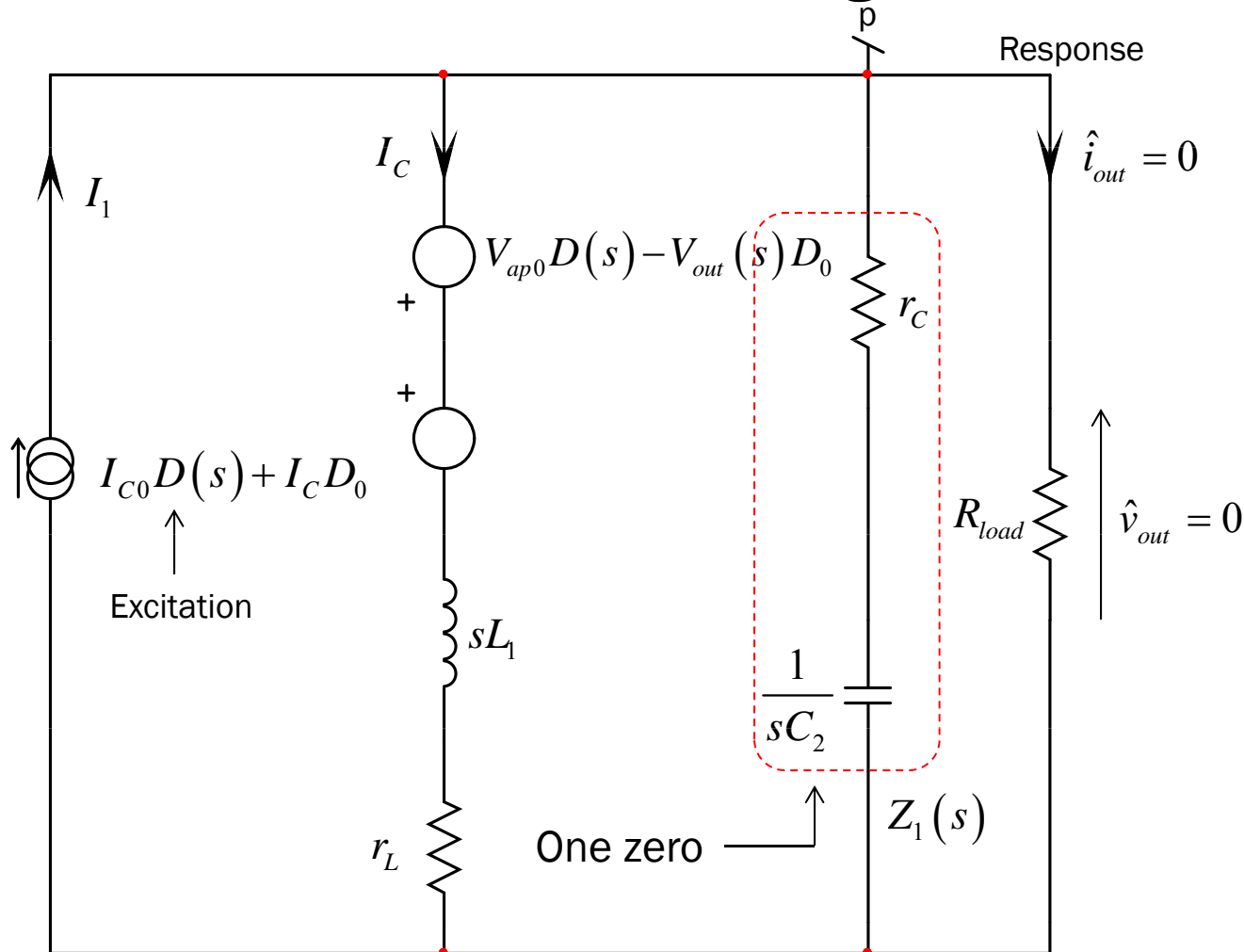□ To determine zeros, bring the excitation back



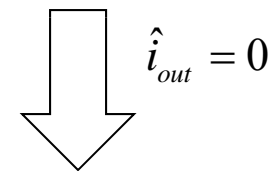“What conditions in the transformed circuit null the response?”



$$Z_1(s) = r_C + \frac{1}{sC_2} = 0$$

$$I_1 = I_C$$

What if L_1 and C_2 are in HF state?

First Zero is Easy

- The equivalent series resistance brings the first zero

$$Z_1(s_z) = r_C + \frac{1}{sC_2} = 0 \quad \longrightarrow \quad Z_1(s_z) = \frac{1 + sr_C C_2}{sC_2} = 0$$

- The negative (LHP) root is simply

$$s_{z_1} = -\frac{1}{r_C C_2} \quad \longrightarrow \quad \omega_{z_1} = \frac{1}{r_C C_2}$$

- Almost there...


$$H(s) = H_0 \frac{\left(1 + \frac{s}{\omega_{z_1}}\right)(\dots)}{1 + b_1 s + b_2 s^2}$$

Control-to-output



Equate Current Expressions

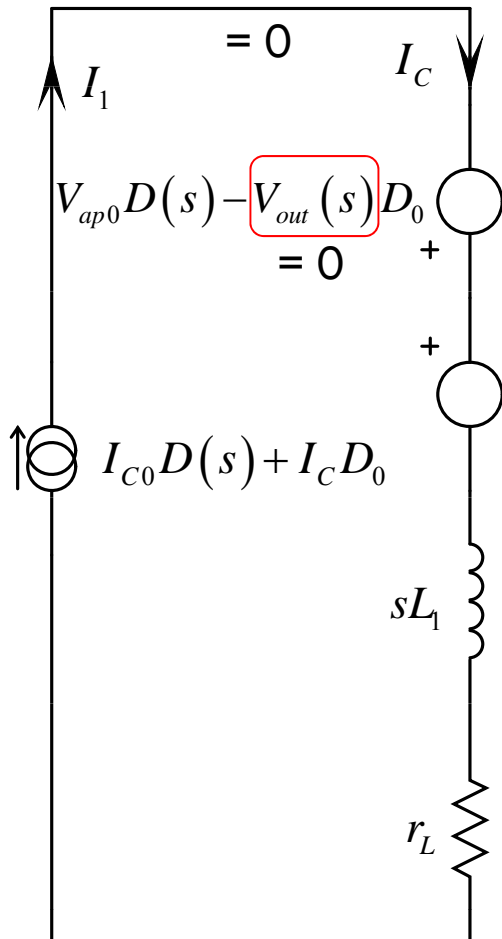□ The output null implies that $\hat{v}_{out} = 0$



$$I_1 - I_C = 0 \quad I_C(s) = \frac{V_{ap0} D(s)}{sL_1 + r_L}$$

$$I_1(s) = I_{C0} D(s) + I_C(s) D_0 \quad \text{Substitute } I_C \text{ in } I_1$$

$$I_{C0} D(s) + \frac{V_{ap0} D(s)}{r_L + sL_1} D_0 - \frac{V_{ap0} D(s)}{r_L + sL_1} = 0$$

Solve for the root

$$s_{z_2} = \frac{(1 - D_0)^2 R_{load} - r_L D_0}{D_0 L_1} \xrightarrow{r_L \ll R_{load}} \omega_{z_2} \approx \frac{(1 - D_0)^2 R_{load}}{D_0 L_1}$$

Positive root, RHPZ!

Control-to-output

Final Expression

□ Assemble the pieces to form the transfer function

$$H_0 = -\left(\frac{1}{1-D_0}\right) \frac{V_{out} r_L + R_{load} (1-D_0)^2 (V_{in} - V_{out})}{r_L + R_{load} (1-D_0)^2} \quad N(s) = (1 + s r_C C_2) \left(1 - s \frac{D_0 L_1}{(1-D_0)^2 R_{load} - r_L D_0} \right)$$

$$D(s) = 1 + \left[\frac{L_1}{r_L + (1-D_0)^2 R_{load}} + C_2 \left(r_C + \frac{R_{load} r_L}{R_{load} (1-D_0)^2 + r_L} \right) \right] s + \left[\frac{L_1}{r_L + (1-D_0)^2 R_{load}} C_2 (r_C + R_{load}) \right] s^2$$

□ Rearrange under a 2nd-order polynomial form

$$\omega_0 = \frac{1}{\sqrt{b_2}} = \frac{1}{\sqrt{\frac{L_1}{r_L + (1-D_0)^2 R_{load}} C_2 (r_C + R_L)}} = \frac{1}{\sqrt{L_1 C_2} \sqrt{\frac{r_C + R_L}{r_L + (1-D_0)^2 R_{load}}}} \approx \frac{1-D_0}{\sqrt{L_1 C_2}}$$

$$Q = \frac{\sqrt{b_2}}{b_1} = \frac{\sqrt{\frac{L_1}{r_L + (1-D_0)^2 R_{load}} C_2 (r_C + R_L)}}{\frac{L_1}{r_L + (1-D_0)^2 R_{load}} + C_2 \left(r_C + \frac{R_{load} r_L}{R_{load} (1-D_0)^2 + r_L} \right)} \approx (1-D_0) R_{load} \sqrt{\frac{C_2}{L_1}}$$

Control-to-output



Plot the Dynamic Response


- Check response versus that of PWM switch model

$$H(s) = H_0 \frac{\left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 - \frac{s}{\omega_{z_2}}\right)}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

$$H_0 = \frac{V_{in}}{(1-D)^2} \quad \omega_{z_1} = \frac{1}{r_C C_2}$$

$$\omega_{z_2} = \frac{(1-D)^2 R_{load}}{D L_1}$$
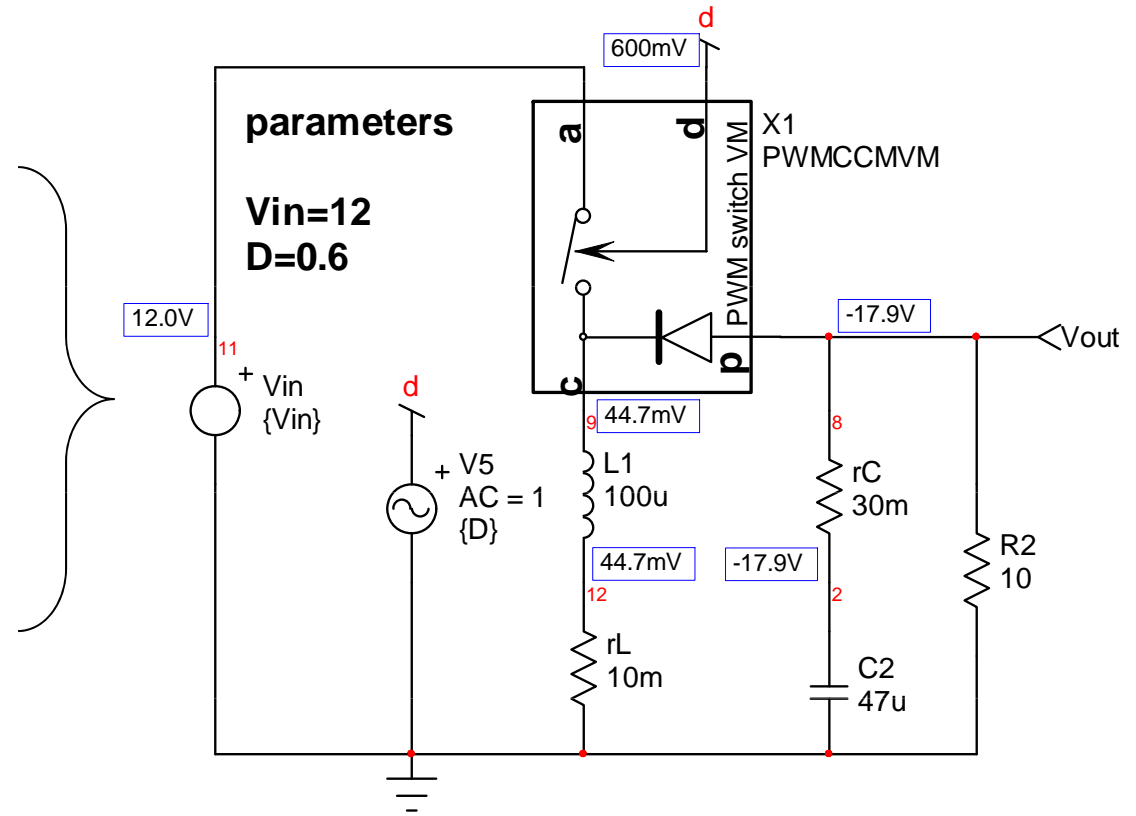
$$\omega_0 = \frac{1-D}{\sqrt{L_1 C_2}} \quad Q = (1-D) R_{load} \sqrt{\frac{C_2}{L_1}}$$




Large-signal PWM switch model

Control-to-output

SPICE and Mathcad® Plots

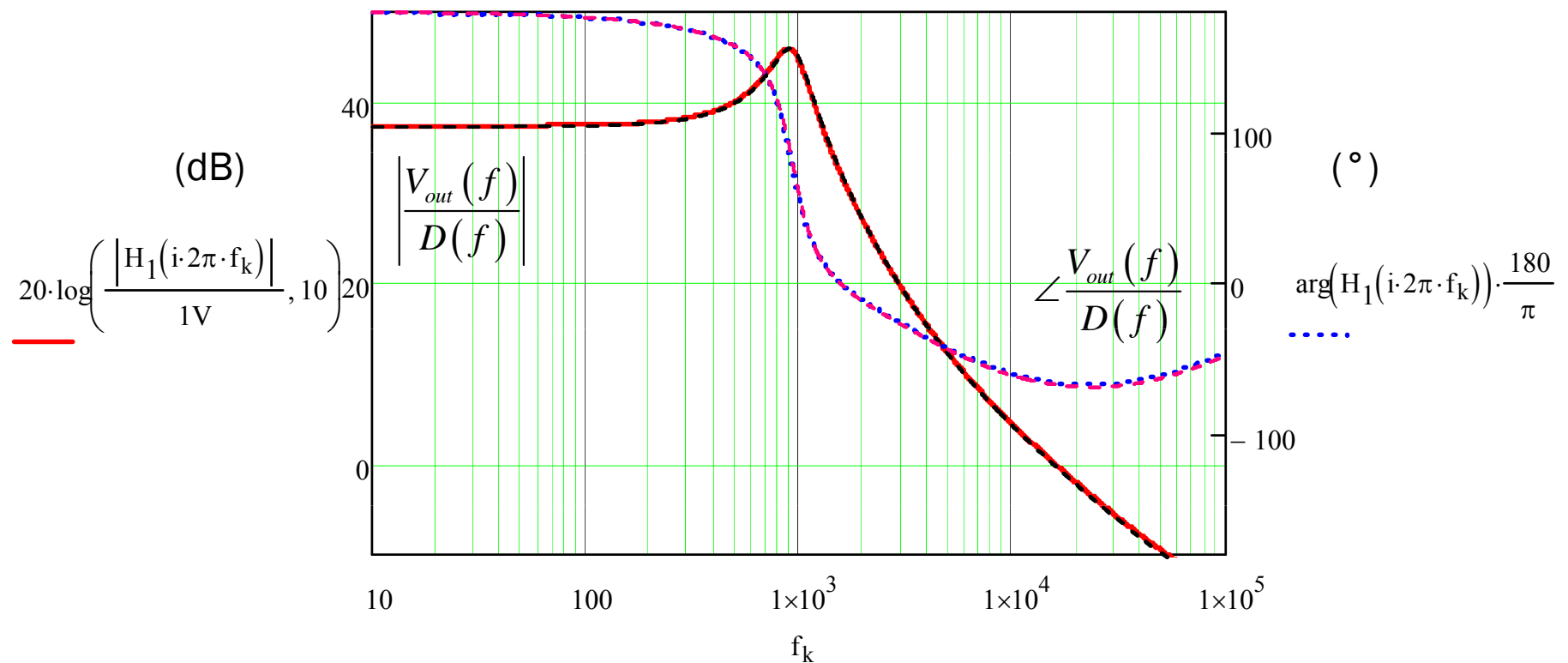
- Curves superimpose: transfer function is correct!



Control-to-output

Input to Output Transfer Function

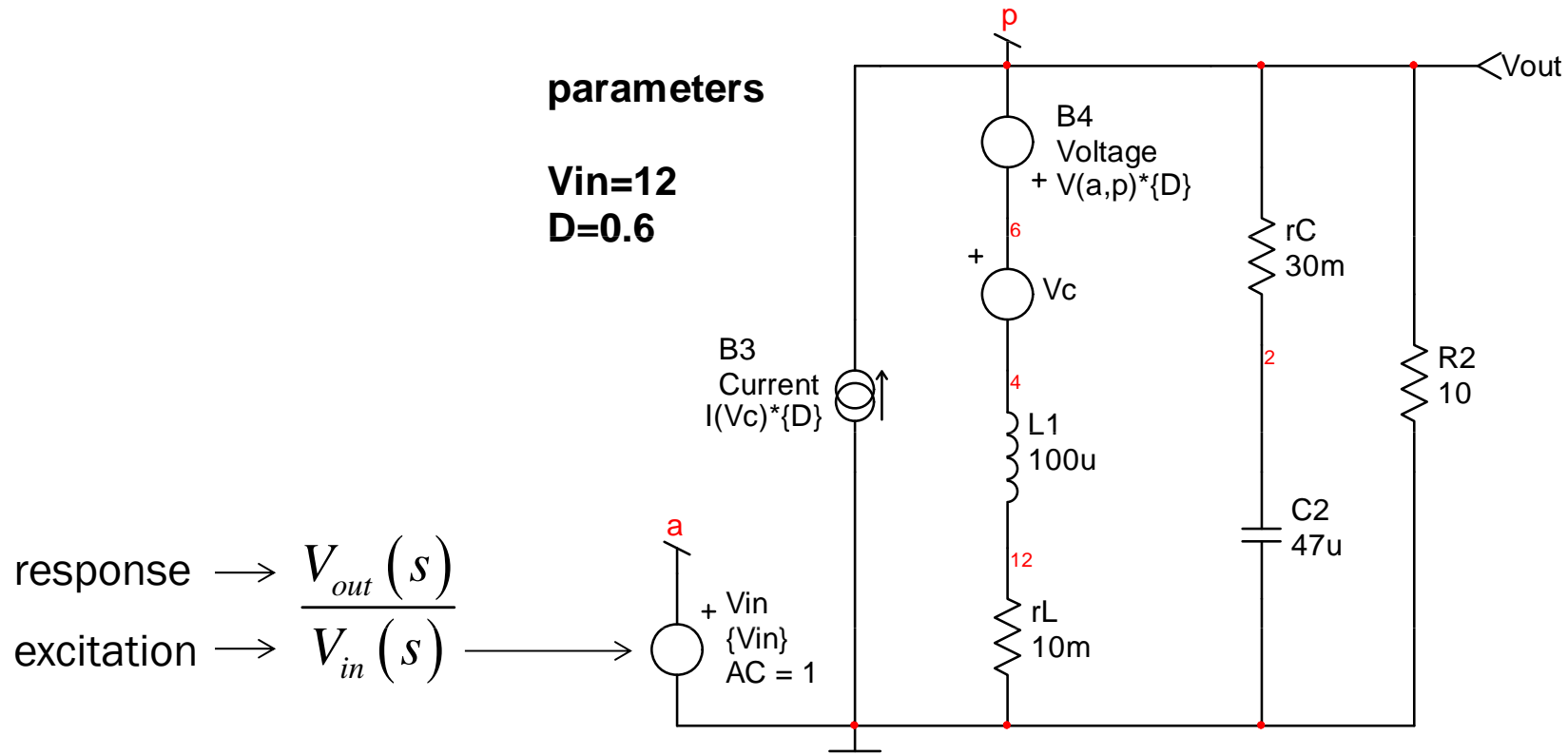- ❑ This time \hat{d} is 0 and V_{in} is now ac-modulated
- ❑ All sources including \hat{d} (d) are set to 0




- ❑ Excitation is 0, structure is unchanged: Reuse $D(s)$!

slide 131

Static Gain - Response for $s = 0$

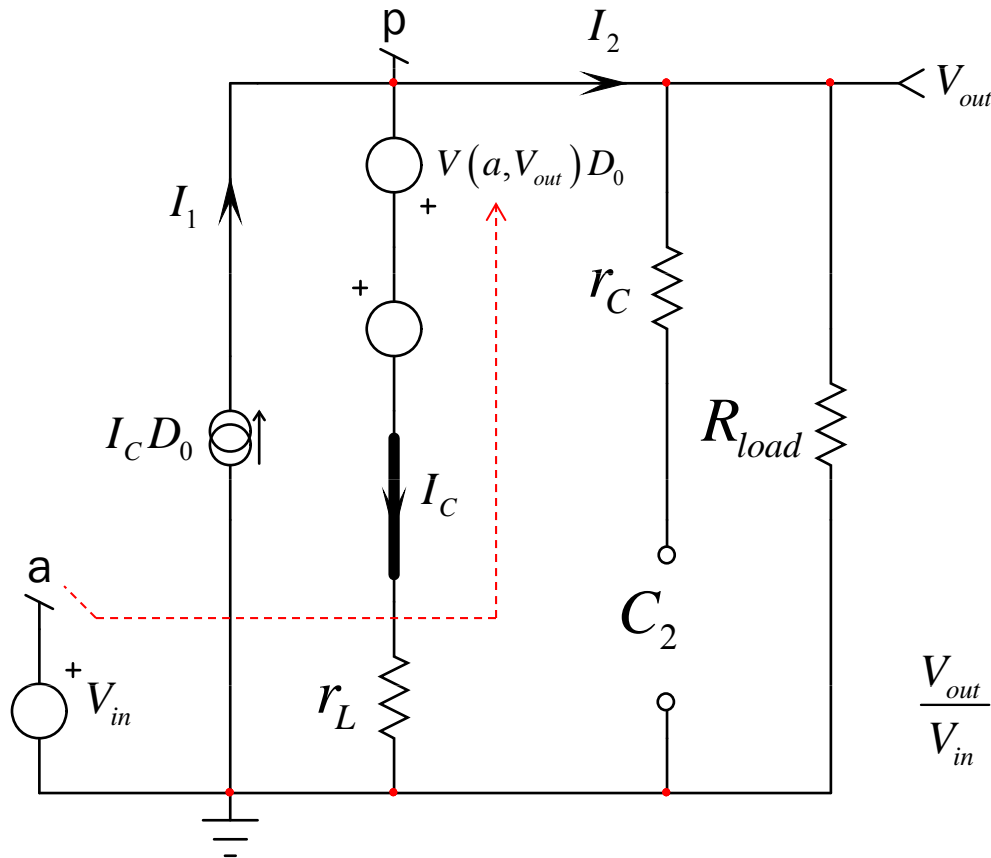
- Open the capacitor and short the inductor



$$I_C = \frac{V_{out} + V_{in} D_0 - V_{out} D_0}{r_L}$$

$$I_1 = \left(\frac{V_{out} + V_{in} D_0 - V_{out} D_0}{r_L} \right) D_0$$

$$V_{out} = (I_1 - I_C) R_{load}$$

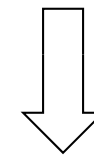


Solve for V_{out}
and rearrange

$$\left. \frac{V_{out}}{V_{in}} \right|_{s=0} = H_0 = -\frac{D(1-D)R_{load}}{(1-D)^2 R_{load} + r_L} \approx -\frac{D}{1-D}$$


Input-to-output

Determining the Numerator: Null V_{out}

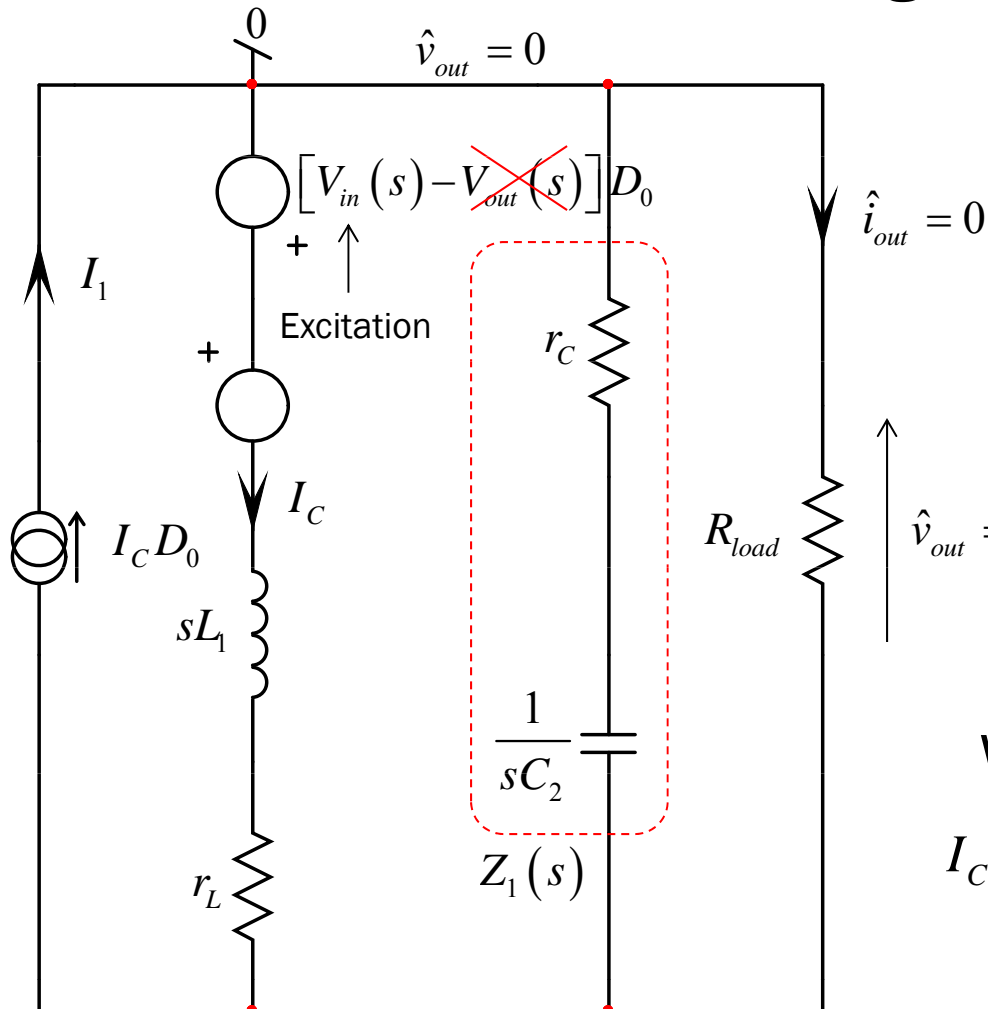□ To determine zeros, bring the excitation back



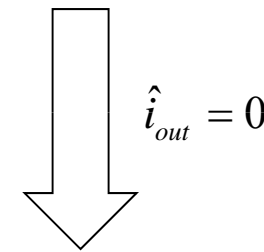“What conditions in the transformed circuit null the response?”



$$Z_1(s) = r_C + \frac{1}{sC_2} = 0 \longrightarrow \omega_{z_1} = \frac{1}{r_C C_2}$$

What if L_1 is set to its HF state?

$$I_C = 0 \longrightarrow I_C D_0 = 0$$

No response, 1 zero only

Input-to-output


Final Transfer Function

□ The transfer function is immediate

$$\frac{V_{out}(s)}{V_{in}(s)} \approx -\left(\frac{D}{1-D}\right) \frac{(1+sr_C C_2)}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

$$\omega_0 \approx \frac{1-D}{\sqrt{L_1 C_2}}$$
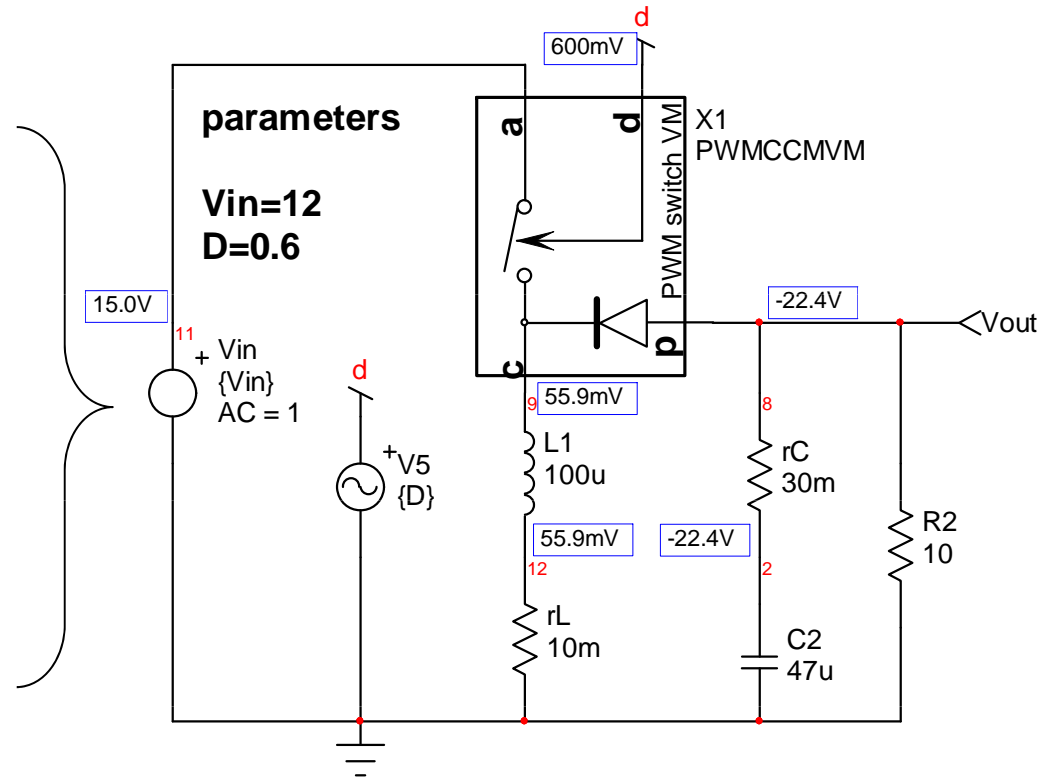
$$Q \approx (1-D) R_{load} \sqrt{\frac{C_2}{L_1}}$$




Large-signal PWM switch model

Input-to-output

SPICE and Mathcad® Plots

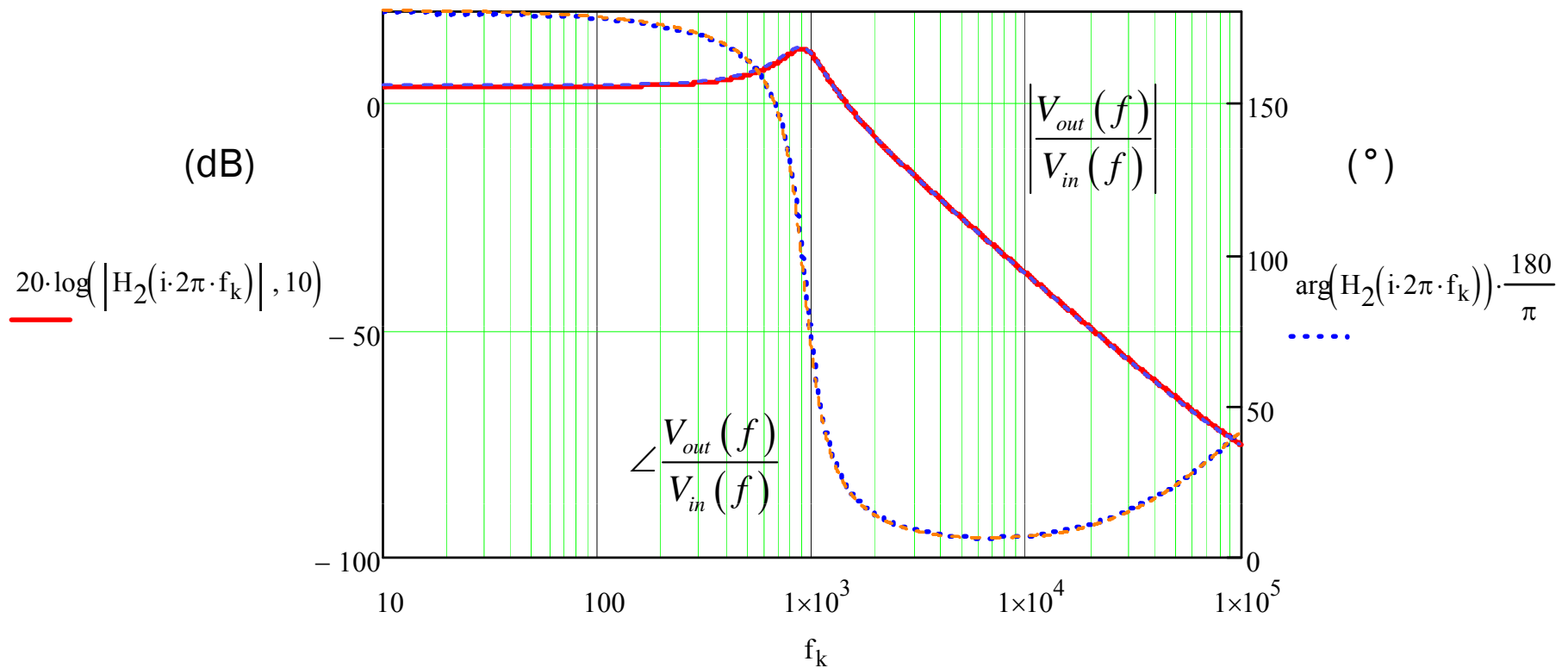- Curves superimpose: transfer function is correct!



Input-to-output

Output Impedance Determination


❑ Install an 1-A ac current source on the output

➤ $\hat{d} = \hat{v}_{in} = 0$

parameters

$V_{in}=12$

$D=0.6$

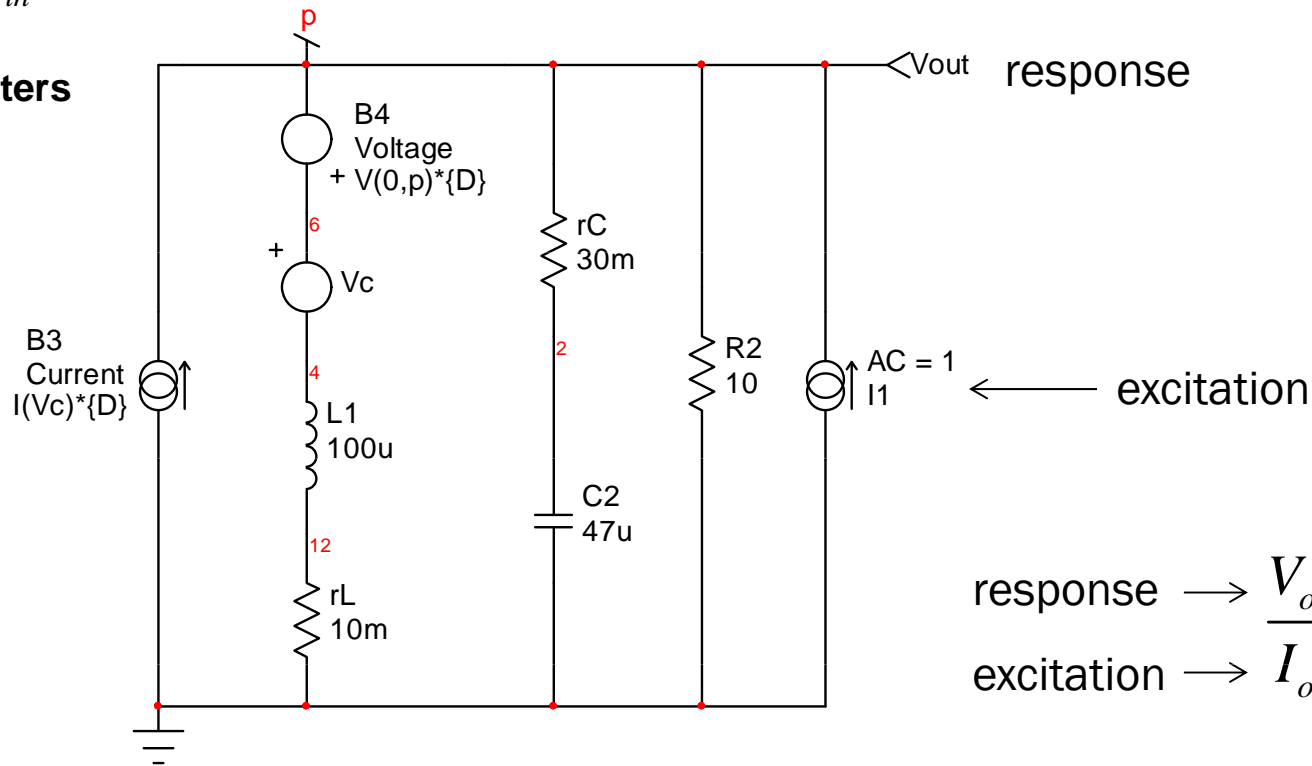


response $\rightarrow \frac{V_{out}(s)}{I_{out}(s)}$
 excitation $\rightarrow I_{out}(s)$

❑ If excitation is 0, structure is unchanged. Same $D(s)$!

→ slide 131

Static Resistance: Response for $s = 0$

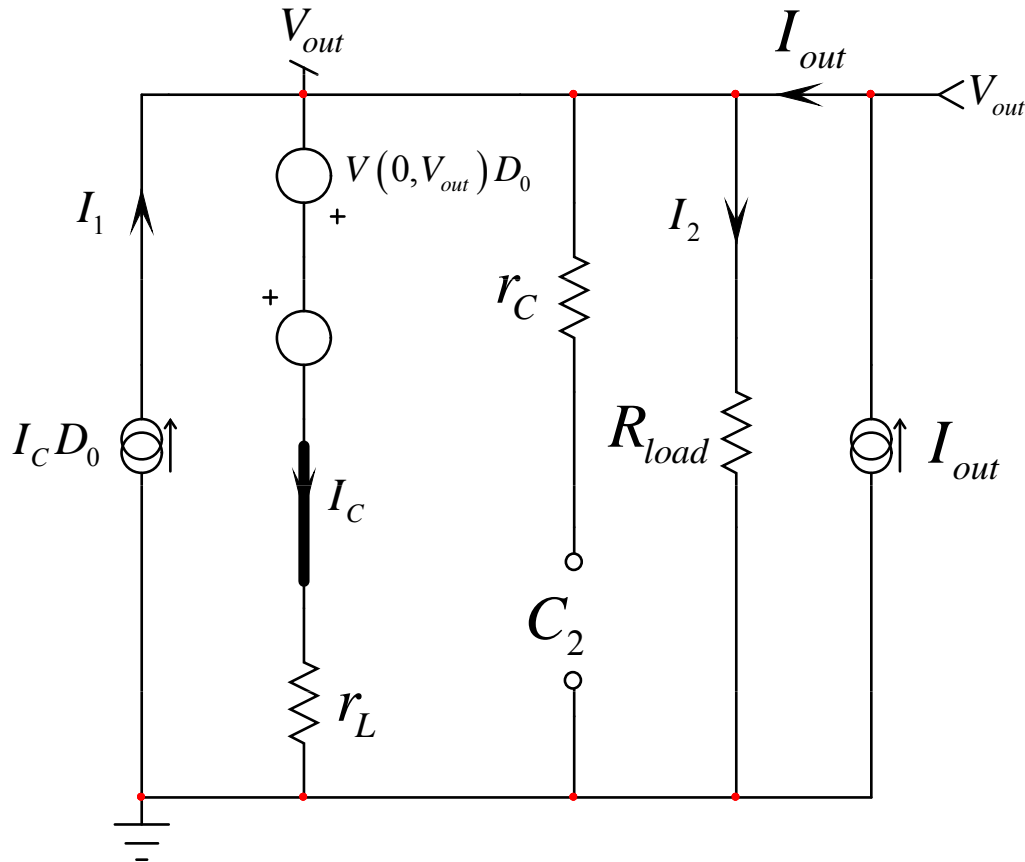
- Open the capacitor and short the inductor



$$I_C = \frac{V_{out} - V_{out} D_0}{r_L} = \frac{V_{out} (1 - D_0)}{r_L}$$

$$I_1 = \left(\frac{V_{out} (1 - D_0)}{r_L} \right) D_0 \quad I_2 = \frac{V_{out}}{R_{load}}$$

$$I_{out} = I_C + I_2 - I_1$$

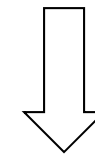

Factor V_{out} and rearrange


$$R_0 = \frac{V_{out}}{I_{out}} = \frac{r_L}{(1 - D_0)^2 + \frac{r_L}{R_{load}}}$$

Output impedance




Determining the Numerator

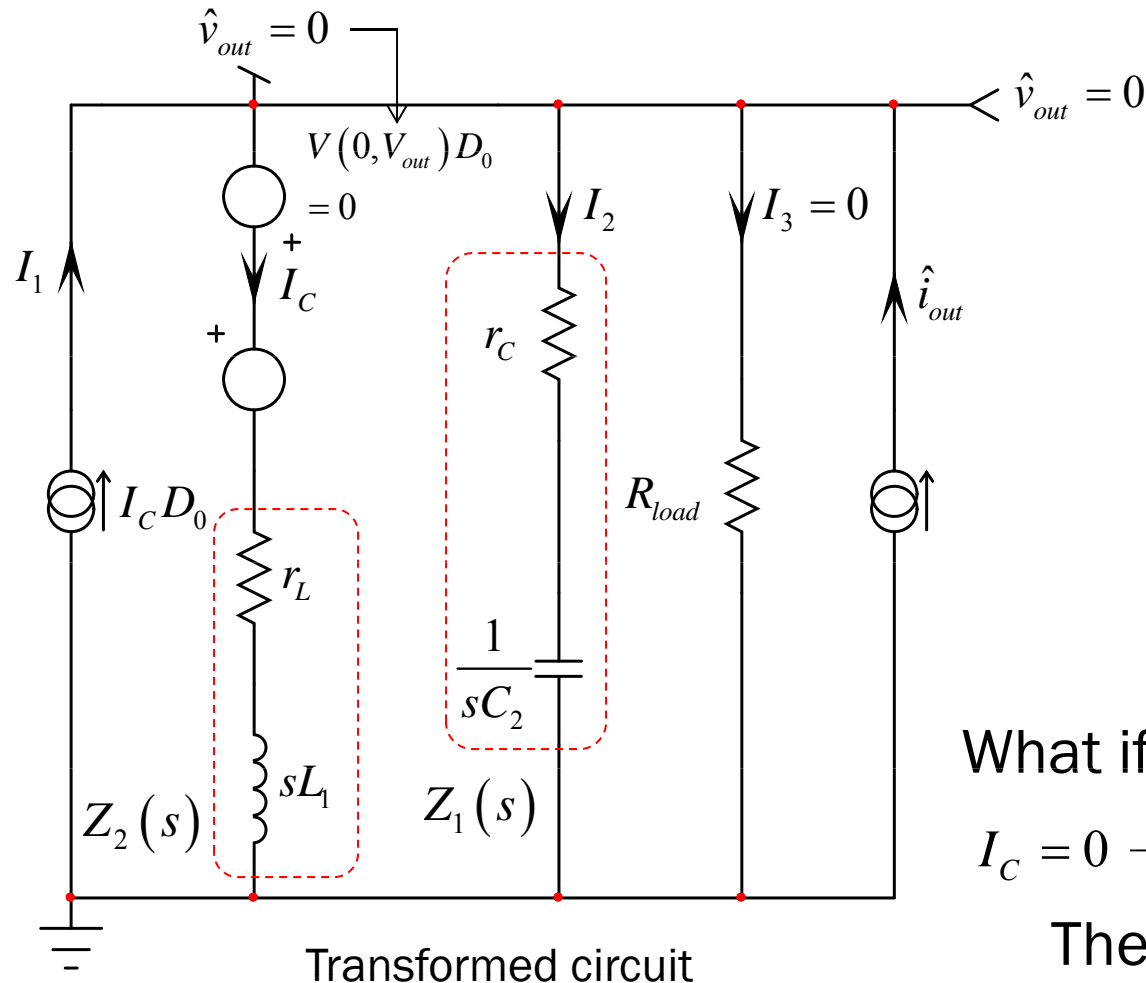- To determine zeros, bring the excitation back



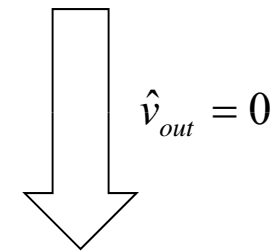“What conditions in the transformed circuit null the response?”



$$Z_1(s) = r_c + \frac{1}{sC_2} = 0$$

What if L_1 and C_2 are in HF state?


$$I_C = 0 \longrightarrow I_C D_0 = 0 \longrightarrow V_{out} = I_{out} R_{load}$$

There is a response: 2 zeros

Output impedance


Two Zeros in the Left Half-Plane

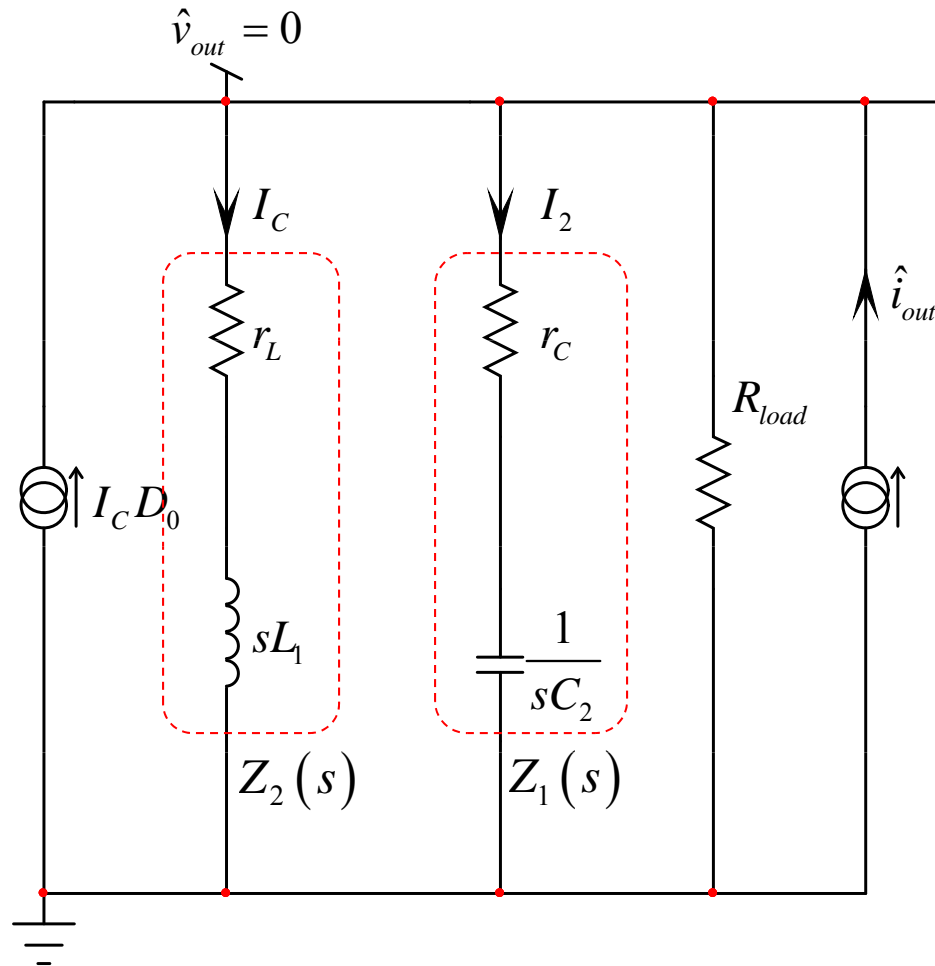- The inductor contributes a zero with r_L



$$Z_1(s) = r_C + \frac{1}{sC_2} = 0 \rightarrow \omega_{z_1} = \frac{1}{r_C C_2}$$
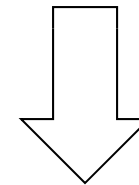
$$Z_2(s) = r_L + sL_1 = 0 \rightarrow \omega_{z_2} = \frac{r_L}{L_1}$$



$$N(s) = \left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 + \frac{s}{\omega_{z_2}}\right)$$

Output impedance


Final Transfer Function

- The transfer function is immediate

$$Z_{out}(s) \approx R_0 \frac{(1 + sr_C C_2) \left(1 + s \frac{L_1}{r_L}\right)}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

$$\omega_0 \approx \frac{1 - D}{\sqrt{L_1 C_2}}$$
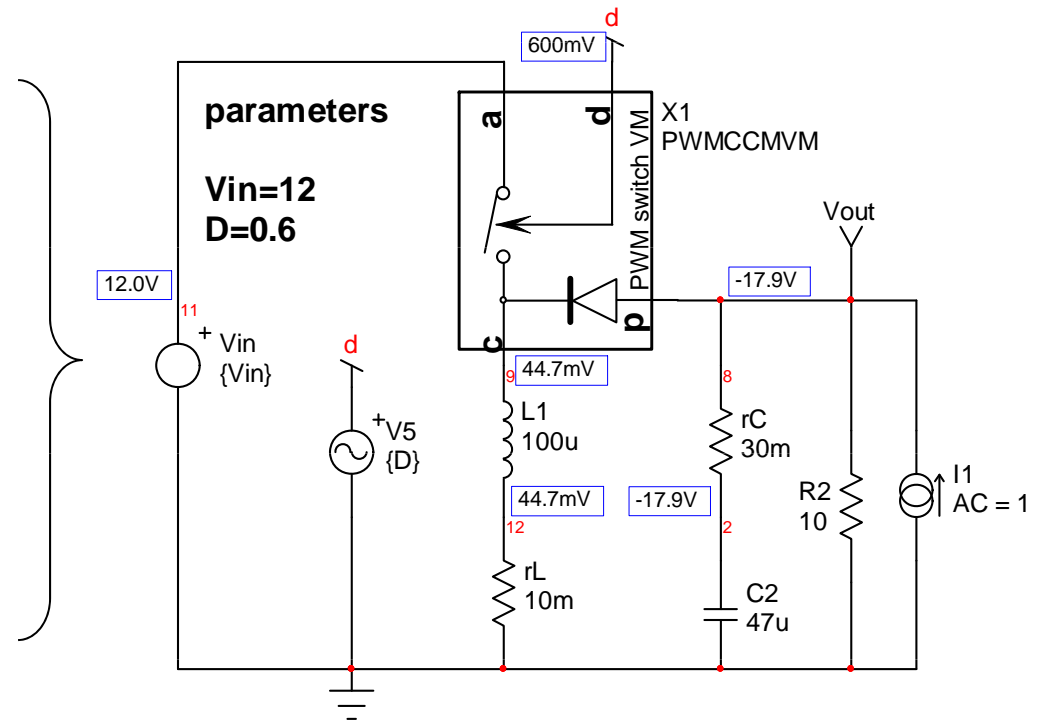
$$Q \approx (1 - D) R_{load} \sqrt{\frac{C_2}{L_1}}$$




Large-signal PWM switch model

Output impedance

SPICE and Mathcad® Plots

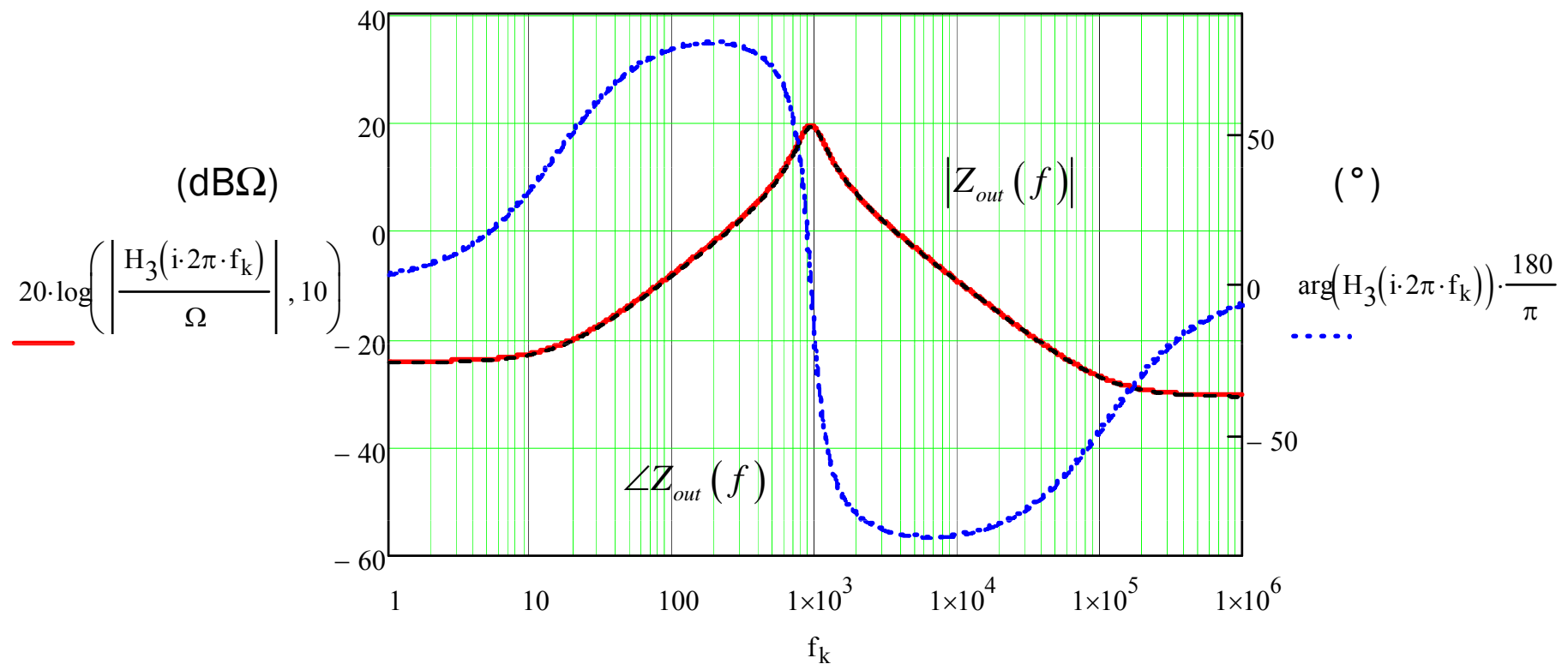
- Curves superimpose: transfer function is correct!



Output impedance

Buck-Boost Input Impedance

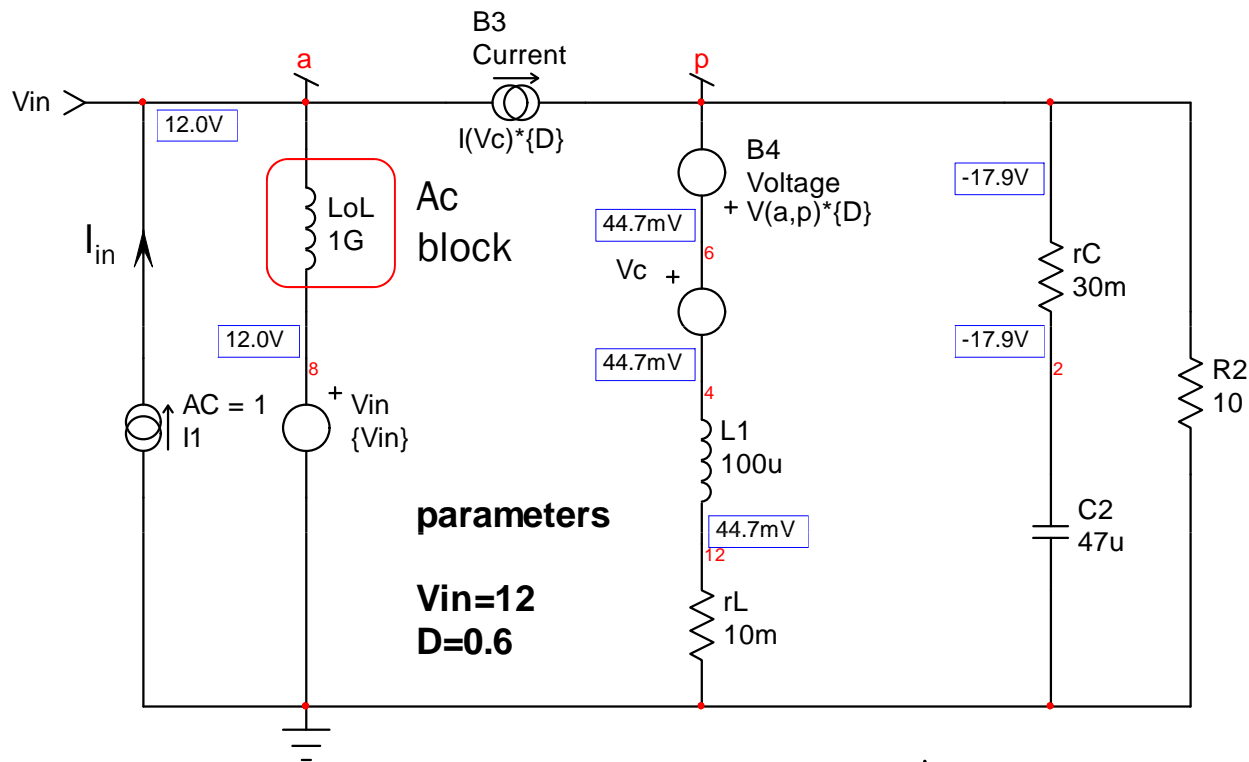- LoL lets you ac-sweep the input to have Z_{in}




$$\begin{aligned} \text{response} &\longrightarrow \left. \frac{V_{in}(s)}{I_{in}(s)} \right|_{\hat{d}=0} \\ \text{excitation} &\longrightarrow \end{aligned}$$

Input impedance



Input Resistance for $s = 0$

- Open capacitor and short the inductor

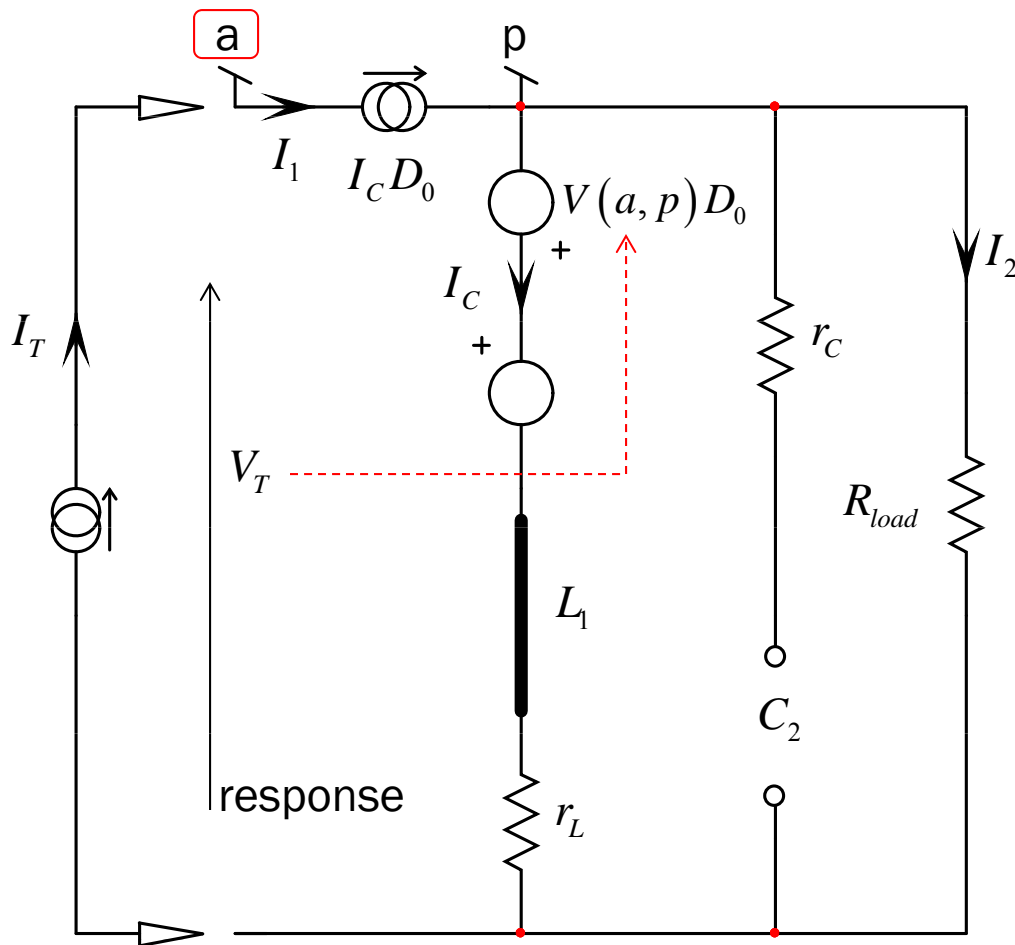

$$I_C D_0 = I_C + I_2 \quad V_{(p)} = I_2 R_{load}$$

$$I_2 = I_C (D_0 - 1) \quad V_{(p)} = I_C (D_0 - 1) R_{load}$$

$$I_C = \frac{V_{(p)} + V_T D_0 - V_{(p)} D_0}{r_L}$$

Substitute $V_{(p)}$

$$I_C = \frac{D_0 V_T}{R_{load} D_0^2 - 2R_{load} D_0 + R_{load} + r_L}$$


$I_T = D_0 I_C$

$$\frac{V_T}{I_T} = R_0 = \frac{(1 - D_0)^2 R_{load} + r_L}{D_0^2}$$

Input impedance

Determine the Denominator, τ_1

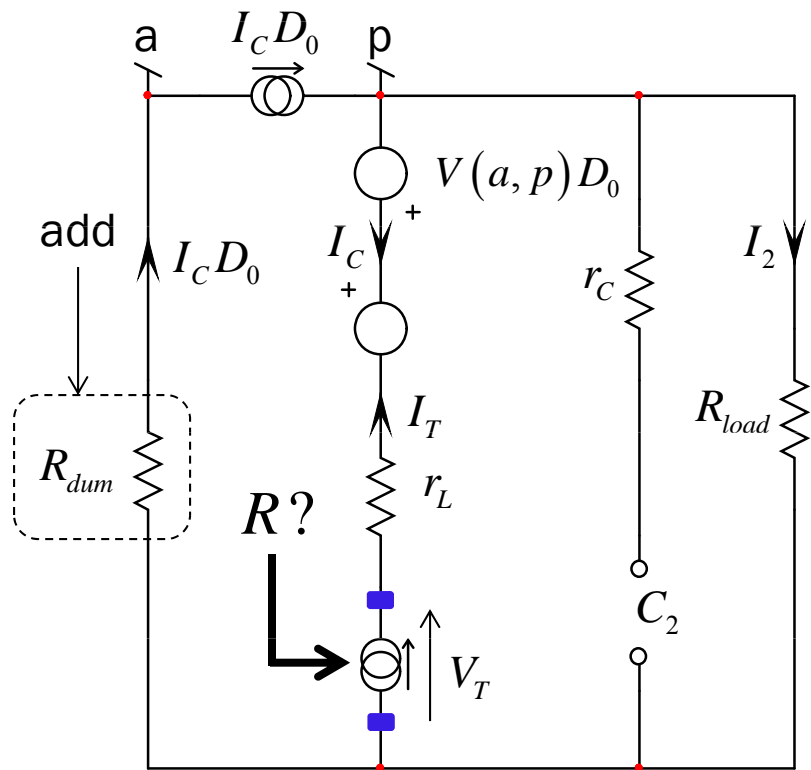- ❑ Turning the excitation off changes the structure
- ❖ You cannot reuse $D(s)$ and node (a) is dangling



$$V_{(a)} = D_0 I_T R_{dum} \quad I_2 = I_C D_0 + I_T \xrightarrow{I_C = -I_T} I_2 = I_T (1 - D_0)$$

$$V_{(p)} = I_2 R_{load} = I_T (1 - D_0) R_{load}$$

$$V_T = I_T (r_L + R_{dum} D_0^2 - (1 - D_0) R_{load} D_0 + (1 - D_0) R_{load})$$

Rearrange

$$\tau_1 = \frac{L_1}{r_L + (1 - D_0) \left(R_{dum} \frac{D_0^2}{1 - D_0} + R_{load} (1 - D_0) \right)}$$


$$\tau_1 \Big|_{R_{dum} \rightarrow \infty} = \frac{L_1}{\infty} = 0$$

- ❑ Install a dummy resistance to build a dc path

Input impedance

Determine the Denominator, τ_2

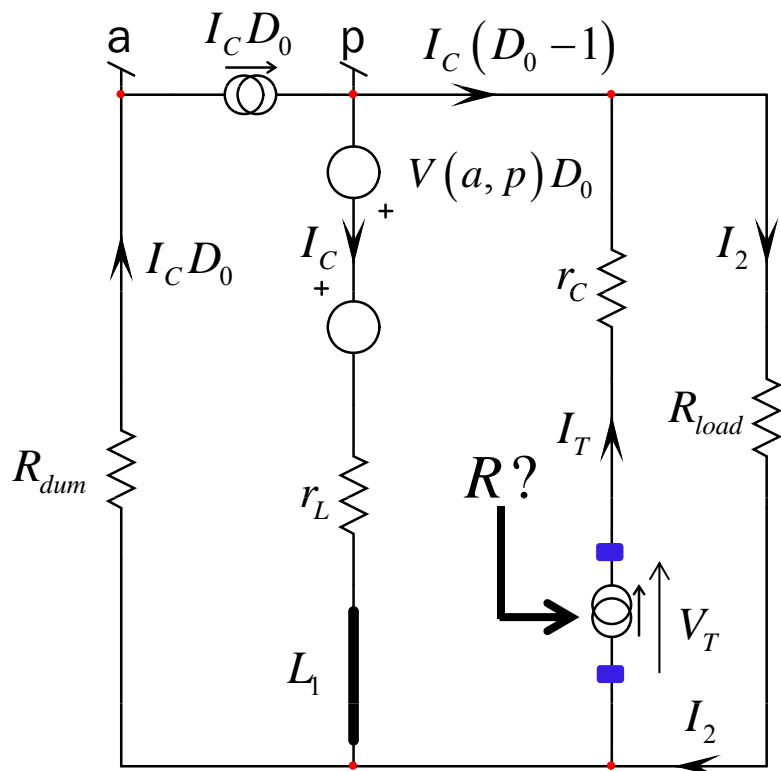
□ Short inductor L_1 and look into C_2 's terminals



$$\tau_2 = (r_C + R_{load}) C_2$$

$$V_{(a)} = -D_0 I_C R_{dum} \quad V_{(p)} = [I_C (D_0 - 1) + I_T] R_{load}$$
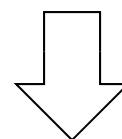
$$V_{(p)} = V_T - I_T r_C \quad I_C = \frac{V_{(p)} + V_{(a)} D_0 - V_{(p)} D_0}{r_L}$$



Substitute and rearrange I_C

$$I_C = \frac{I_T R_{load} (1 - D_0)}{R_{load} + r_L - 2D_0 R_{load} + D_0^2 (R_{dum} + R_{load})}$$

$$V_T - I_T r_C = [I_C (D_0 - 1) + I_T] R_{load}$$


$$R = \frac{V_T}{I_T} = r_C + \frac{R_{dum} \left(R_{load} D_0^2 + \frac{R_{load} r_L}{R_{dum}} \right)}{R_{dum} \left(\frac{R_{load} + r_L - 2D_0 R_{load} + D_0^2 R_{load}}{R_{dum}} + D_0^2 \right)} \xrightarrow{R_{dum} \rightarrow \infty} \approx r_C + R_{load}$$

Input impedance



Determine the Last Term, τ_2^1

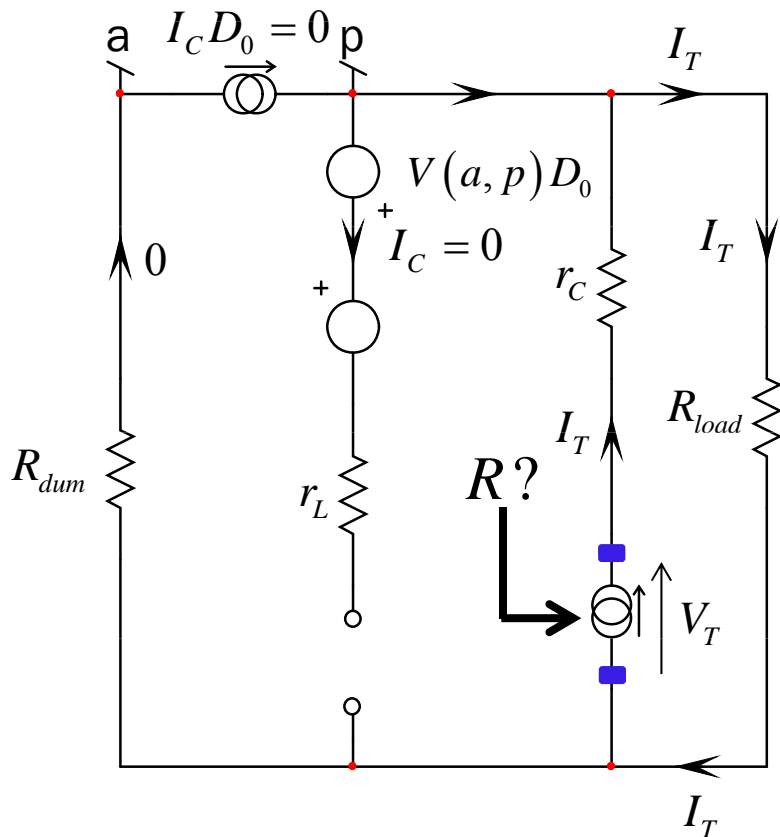- Open the inductor and look through C_2 's terminals



As L_1 is open, current I_C is zero

$$\tau_2^1 = C_2 (r_C + R_{load})$$


$$b_2 = \tau_1 \tau_2^1 = \frac{L_1}{\infty} \cdot C_2 (r_C + R_{load}) = 0$$

$$D(s) = 1 + b_1 s + b_2 s^2 = 1 + s (r_C + R_{load}) C_2$$

Input impedance

Null the response for the denominator

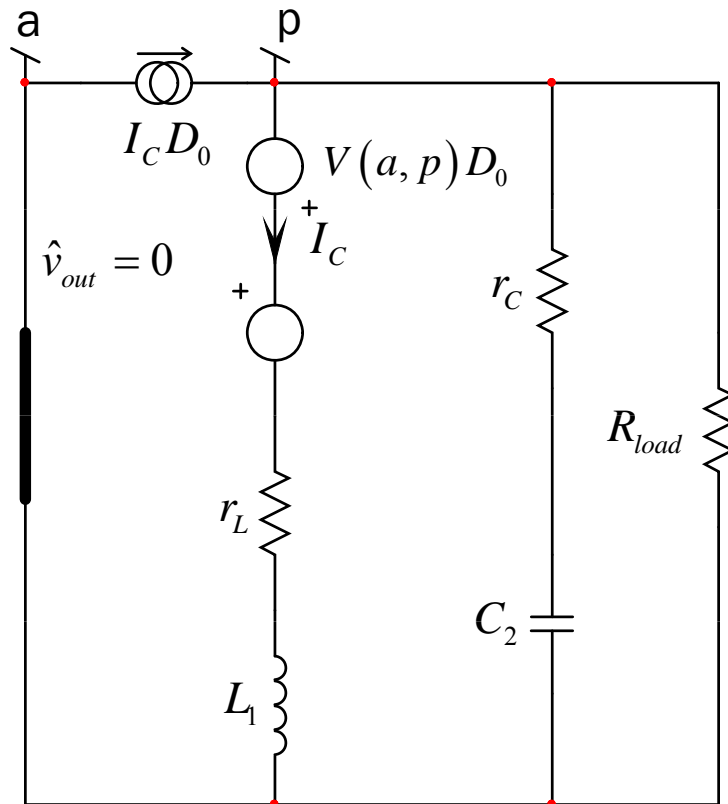- ❑ Short the current source for a null in the response
- ❑ Structure returns to its original state: use D for N !



Determined for Z_{out} and H

$$N(s) = 1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0} \right)^2$$

$$\omega_0 \approx \frac{1-D}{\sqrt{L_1 C_2}} \quad Q \approx (1-D) R_{load} \sqrt{\frac{C_2}{L_1}}$$

→ slide 131

Final Transfer Function


□ The transfer function is immediate

$$Z_{in}(s) \approx R_0 \frac{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}{1 + s(r_C + R_{load})C_2}$$

$$\omega_0 \approx \frac{1-D}{\sqrt{L_1 C_2}}$$

$$Q \approx (1-D) R_{load} \sqrt{\frac{C_2}{L_1}}$$
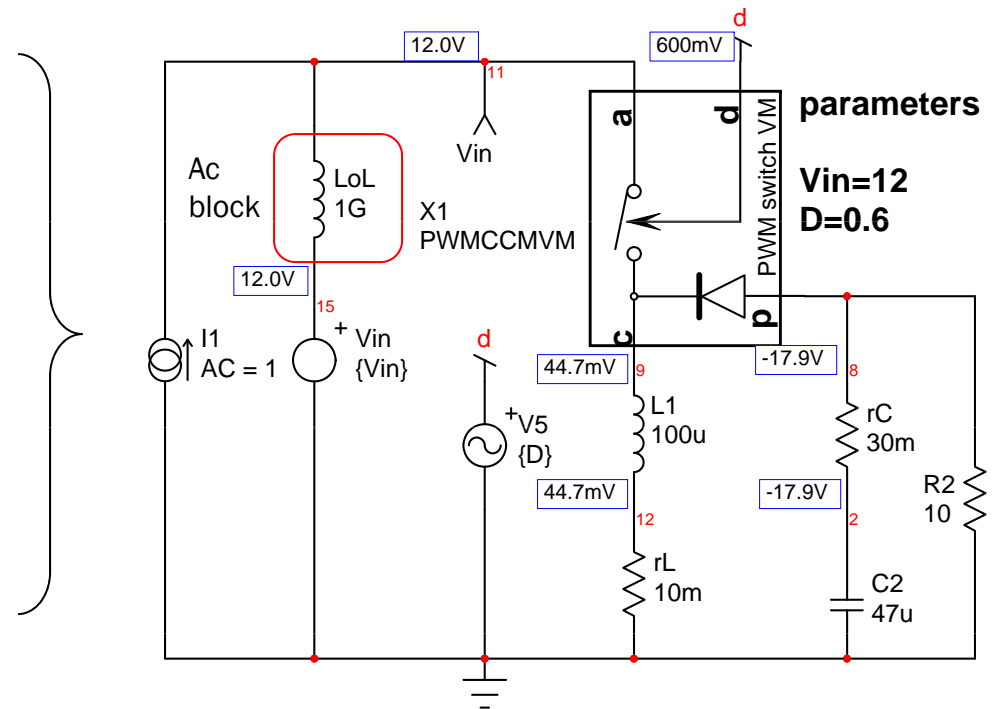
$$R_0 = \frac{(1-D_0)^2 R_{load} + r_L}{D_0^2}$$




Large-signal PWM switch model

Input impedance



SPICE and Mathcad® Plots

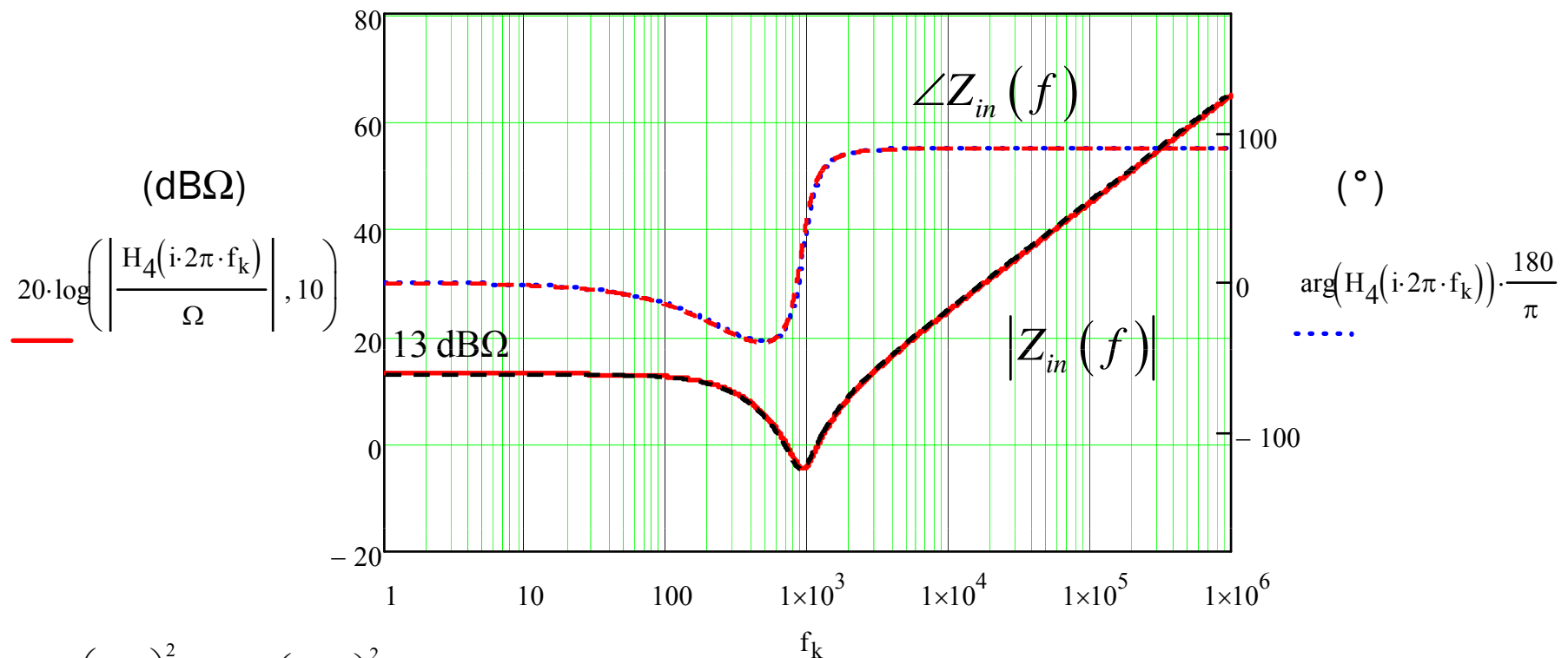- Curves superimpose: transfer function is correct!



$$R_0 = \left(\frac{V_{in}}{V_{out}} \right)^2 R_{load} = \left(\frac{12}{17.9} \right)^2 \times 10 = 4.49 \Omega \rightarrow 13 \text{ dB}\Omega$$

Input impedance



References

- ❑ Middlebrook R.D. “Null Double Injection and The Extra Element Theorem”, IEEE Transactions on Education, Vol. 32, NO 3, August 1989
- ❑ R. D. Middlebrook, V. Vorpérian, J. Lindal, “The N Extra Element Theorem”, IEEE Transactions on Circuits and Systems, vol. 45, NO. 9, September 1998
- ❑ V. Vorpérian, “Fast Analytical Techniques for Electrical and Electronic Circuits”, Cambridge University Press, 978-0-52162-442-8, 2002
- ❑ C. Basso, “Linear Circuit Transfer Functions: A Tutorial Introduction to Fast Analytical Techniques”, Wiley IEEE-press, May 2016



Conclusion

- ❑ Plotting a transfer function is easy with nowadays tools
- ❖ You have no insight on what affects poles or zeros
- ❑ Analytical analysis is important but the form matters
- ❑ A *low-entropy* expression unveils contributors to poles/zeros
- ❑ FACTs naturally lead to *low-entropy* expressions
- ✓ Break the circuit into simple schematics
- ✓ Determine time constants in each configuration
- ❑ Small-signal analysis makes extensive use of FACTs
- ❑ SPICE and Mathcad are useful instruments to track errors
- ❑ Becoming skilled with FACT requires practice and tenacity!



Merci !
Thank you!
Xiè-xie!