



Simulation and Analysis Applied to the Design of Buck Topologies

Christophe Basso – Technical Fellow
IEEE Senior Member

ON Semiconductor®



Course Agenda

- The Buck Converter
- Control Schemes
- Introduction to Modeling
- The PWM Switch in Current-Mode Control
- Introduction to the Fast Analytical Techniques
- The Four Transfer Functions in CCM Current-Mode Control
- Compensation Strategy
- Prototype Measurements



Course Agenda

- ❑ The Buck Converter
- ❑ Control Schemes
- ❑ Introduction to Modeling
- ❑ The PWM Switch in Current-Mode Control
- ❑ Introduction to the Fast Analytical Techniques
- ❑ The Four Transfer Functions in CCM Current-Mode Control
- ❑ Compensation Strategy
- ❑ Prototype Measurements



Input Voltage Reduction: Linear or Switching?

□ How do you step-down the input source?

❖ A linear regulator

- Poor efficiency at high input-output differentials
- Constrained to low input voltages
- ✓ low-noise linear operation

$$\longrightarrow \eta \approx \frac{V_{out}}{V_{in}}$$



❖ A switching regulator


- Noisy operation, requires filtering
- Built with energy-storing components
- ✓ Excellent efficiency
- ✓ Works across a wide input voltage range



The buck converter

Principles of Operation in Voltage-Mode Control

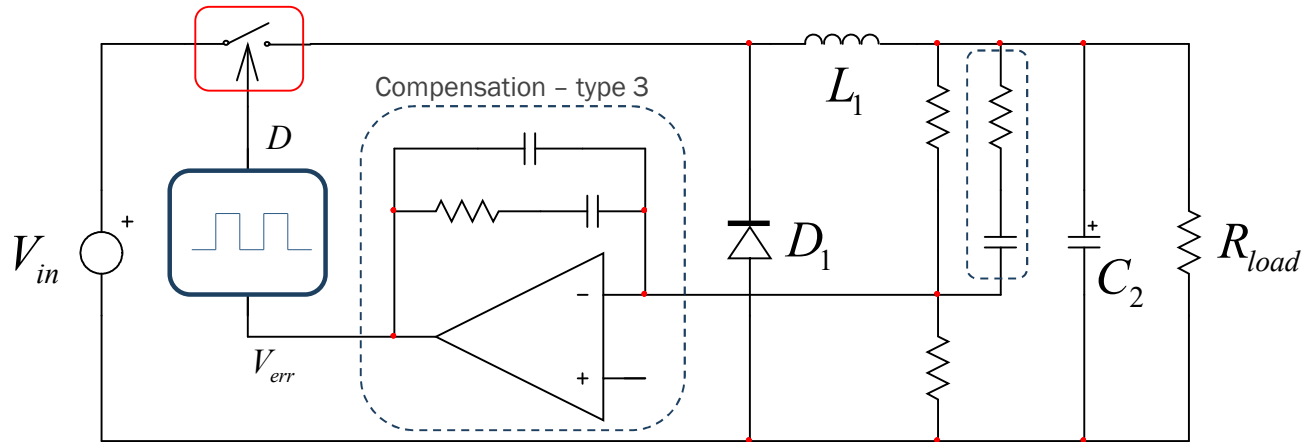- ❑ The buck converter can be operated in voltage-mode control
- Control-to-output transfer function changes between operating modes
- ✓ No need to sense the inductor current*




- ✓ Inherently-low open-loop output impedance
- ❖ Mediocre input line rejection

* Beside over-current protection purposes

Principles of Operation in Current-Mode Control


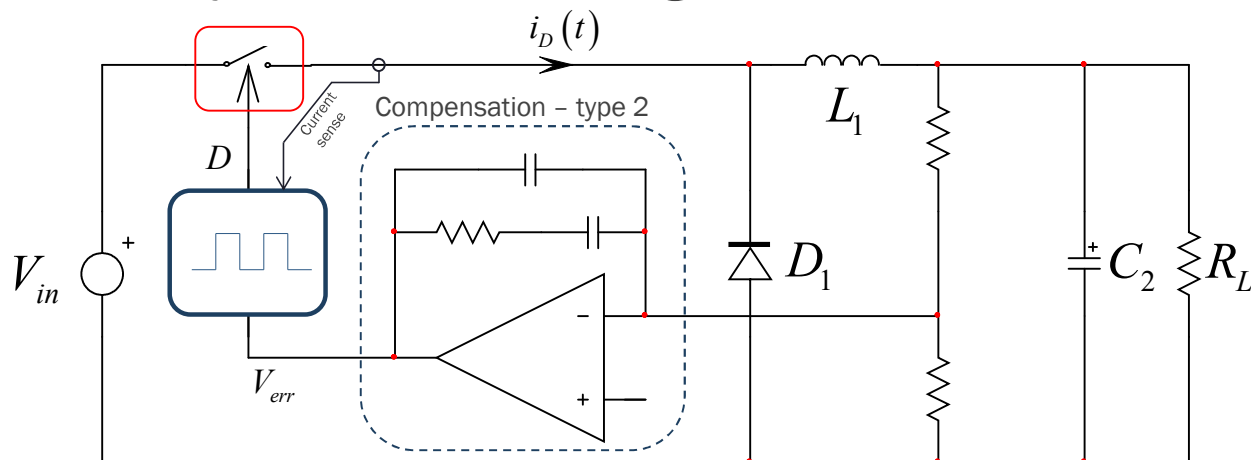
- ❑ The buck converter can be operated in current-mode control
- ✓ 1st-order response in low frequencies whether CCM or DCM operation
- Unstable for duty ratios approaching 50% – CCM needs slope compensation



- Mediocre open-loop output impedance
- ✓ Inherent good input line rejection



The Two Operating Phases of the Buck Converter

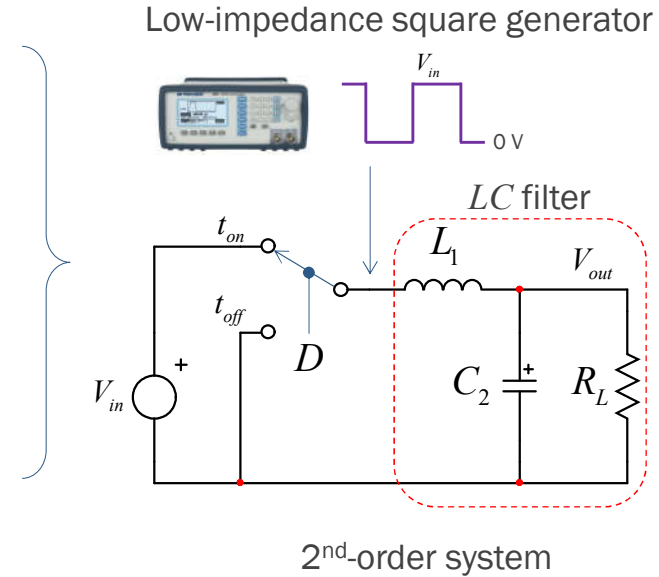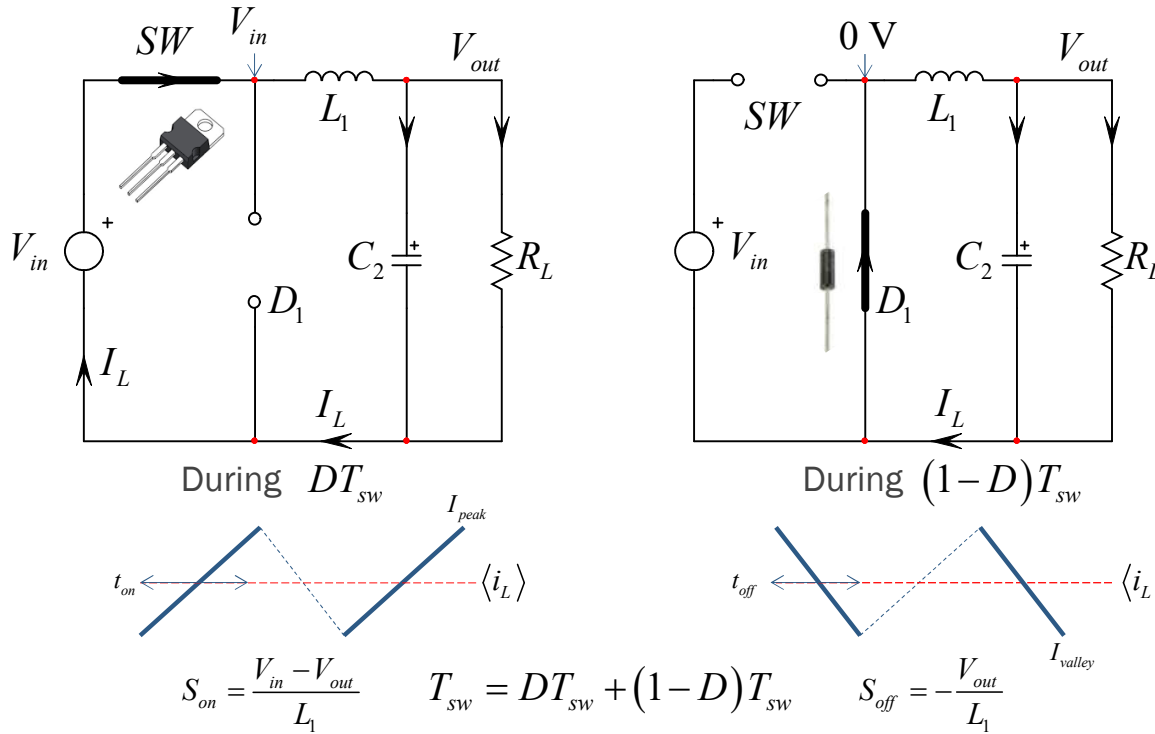□ Neglecting drops, the common $SW-D$ node swings between V_{in} and 0 V



A Third State Exists when the Inductor Depletes

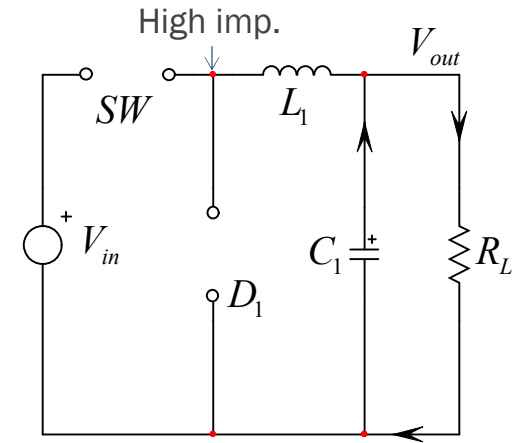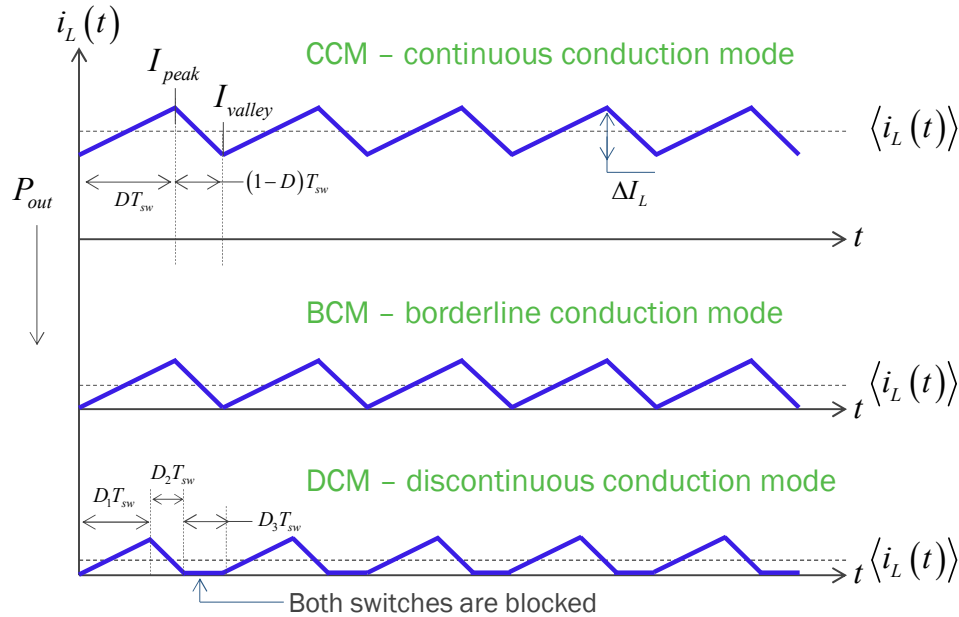□ Observing the inductor current to infer conduction mode




During D_3T_{sw}

$$T_{sw} = t_{on} + t_{off} + D_3T_{sw}$$

❖ Inductive current is in the high-side branch: how to sense?


Challenging Current Sensing for Current Mode

❑ Insert a resistance with L

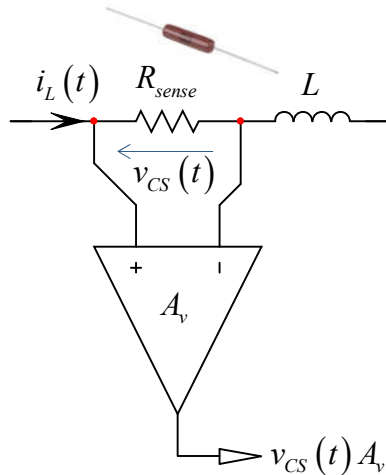

- ✓ Simplest solution
- ✓ Can read I_{out}
- ❖ Efficiency suffers


❑ Use MOSFET $r_{DS(on)}$

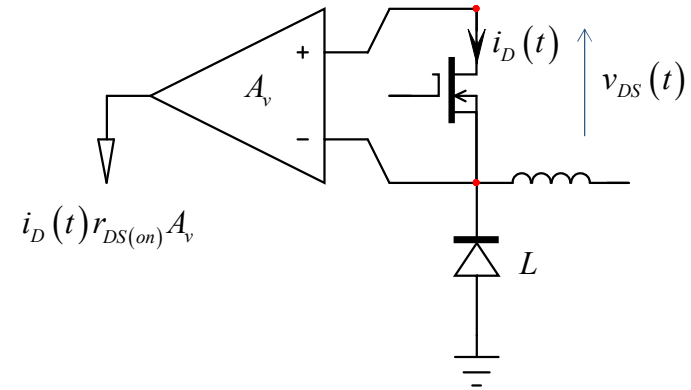

- ✓ No extra sensing element
- ✓ Can be integrated
- ❖ Temperature-dependent values
- ❖ $r_{DS(on)}$ not tested in production

Dc Resistance Inductor Current Sensing

□ Integrate inductor voltage

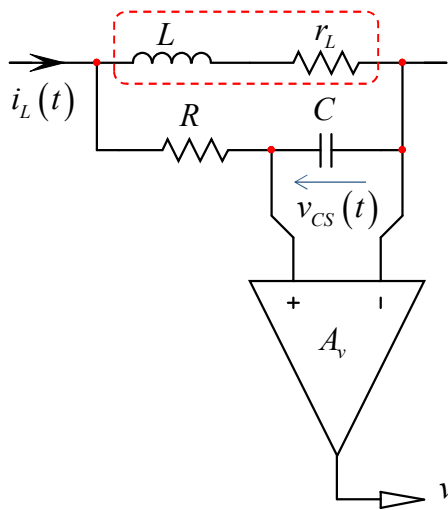

$$V_{CS}(s) \approx I_L(s) r_L \frac{1 + s \frac{L}{r_L}}{1 + sRC}$$

$$V_{CS}(s) = I_L(s) r_L \frac{1 + s\tau_1}{1 + s\tau_2}$$

↓ $\tau_1 = \tau_2$

$$V_{CS}(s) \approx I_L(s) r_L$$


↑
Sensing
resistance

- ✓ Most efficient solution
- ✓ Low cost

❖ Time constant mismatch



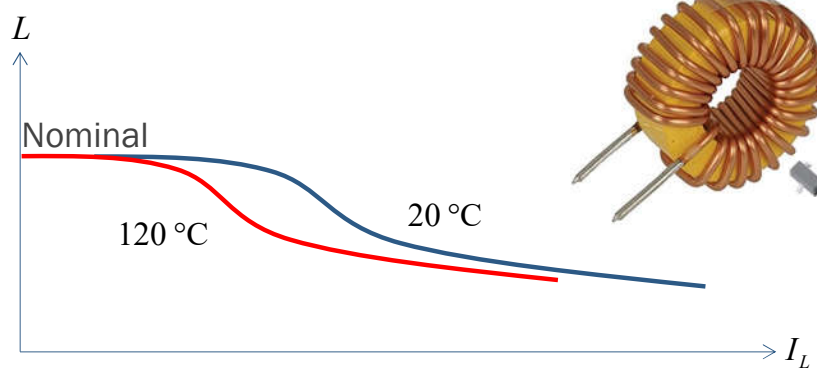- inductance varies with A and °C
- beware of cheap material




T. Hegarty, Inductor DCR Current Sensing With Temperature Compensation, How2Power, November 2013




Sense Transformer for High-Current Applications

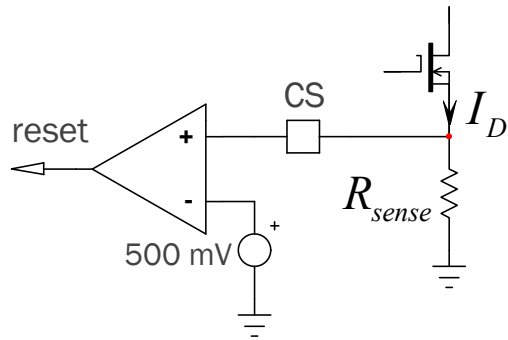- ❑ The transformer references the measured variable to ground
- ❑ Turns ratio N emulates any sense resistance value


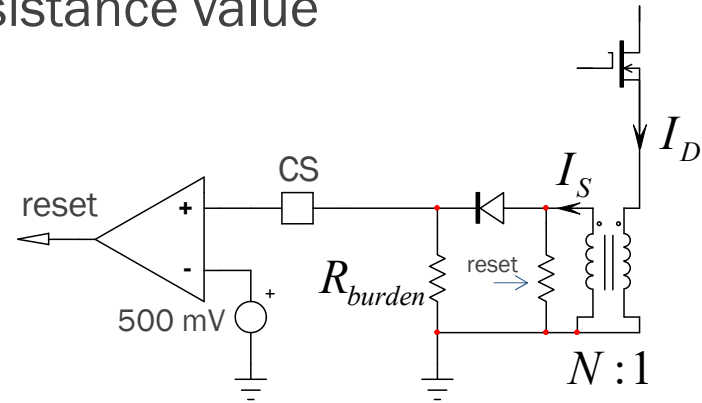
$$R_{sense} = \frac{V_{sense,max}}{I_{D,max}} = \frac{0.5}{30} = 16.6 \text{ m}\Omega$$




$$R_{burden} = \frac{V_{sense,max}}{I_{D,max}} N = \frac{0.5}{30} \times 100 = 1.66 \Omega$$


- ❖ Transformer reset is necessary (e.g. with a Zener diode)
- ❖ Can only sense ac currents

Parasitic Terms Affect Conversion Ratio

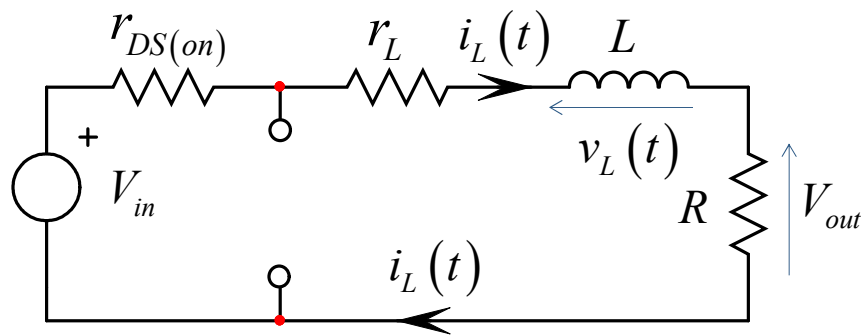□ Apply volt-second balance law*: $\langle v_L(t) \rangle_{T_{sw}} = 0$


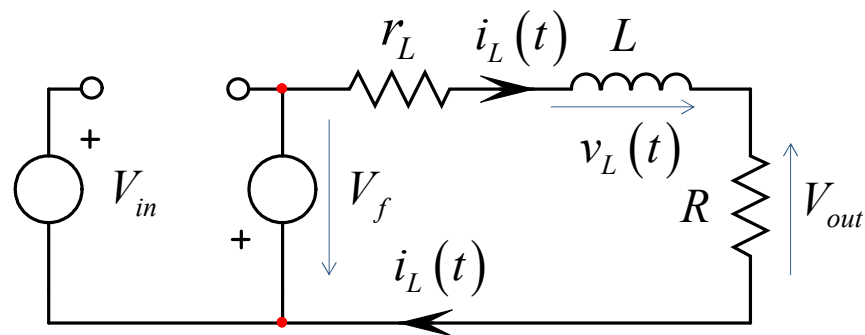
$$\langle v_L(t) \rangle_{t_{on}} = DT_{sw} \left[V_{in} - \frac{V_{out}}{R} (r_{DS(on)} + r_L) - V_{out} \right]$$



$$\langle v_L(t) \rangle_{t_{off}} = (1-D)T_{sw} \left[V_{out} + V_f + \frac{V_{out}}{R} r_L \right]$$

Inductor flux balance implies:

$$\langle v_L(t) \rangle_{t_{on}} - \langle v_L(t) \rangle_{t_{off}} = 0$$

➔
Solve
for M

$$\frac{V_{out}}{V_{in}} = M = D \left[\frac{1}{1 + \frac{r_{DS(on)}}{R} D + \frac{r_L}{R} + \frac{V_f}{V_{out}} D'} \right]$$

* At steady-state


Analyzing the Conversion Ratio Equation

□ Depending on the duty ratio, optimize one of the paths


$$D \left[\frac{1}{1 + \frac{r_{DS(on)}}{R} D + \frac{r_L}{R} + \frac{V_f}{V_{out}} D'} \right]$$

duty ratio scales losses
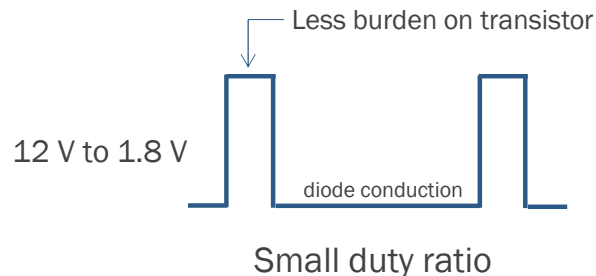
$$D \left[\frac{1}{1 + \frac{r_{DS(on)}}{R} D + \frac{r_L}{R} + \frac{V_f}{V_{out}} D'} \right]$$



Synchronous rectification

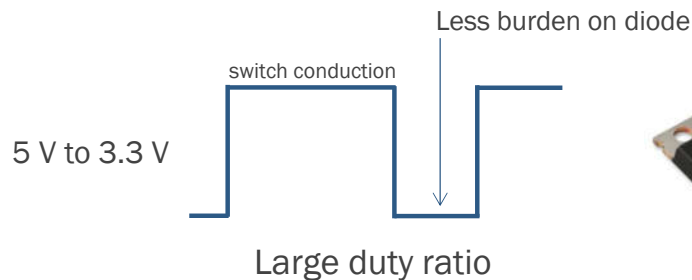

Reduce


$r_{DS(on)}$




Continuous conduction mode (CCM) is assumed

Synchronous Rectification

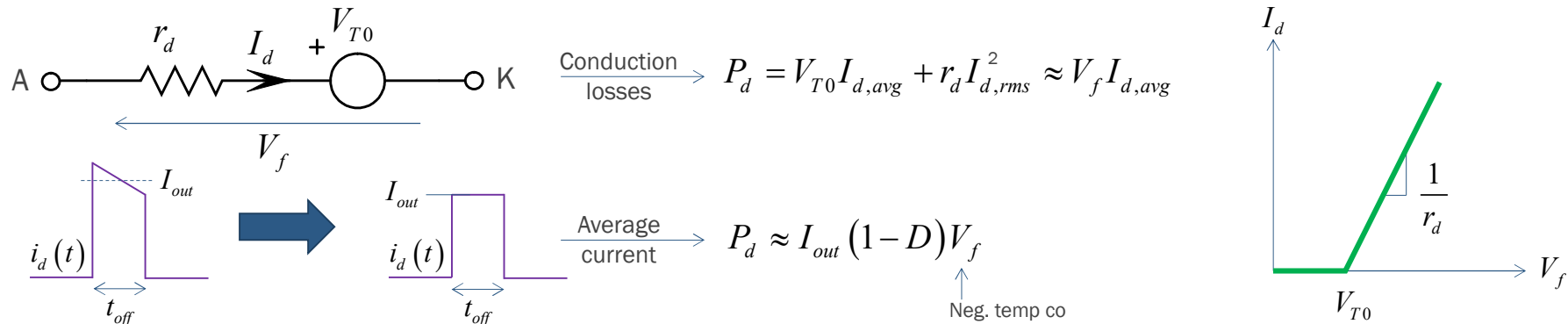- Diode conduction losses depend on average and rms currents
- ❖ As a 1st-order approximation, losses are insensitive to ripple current



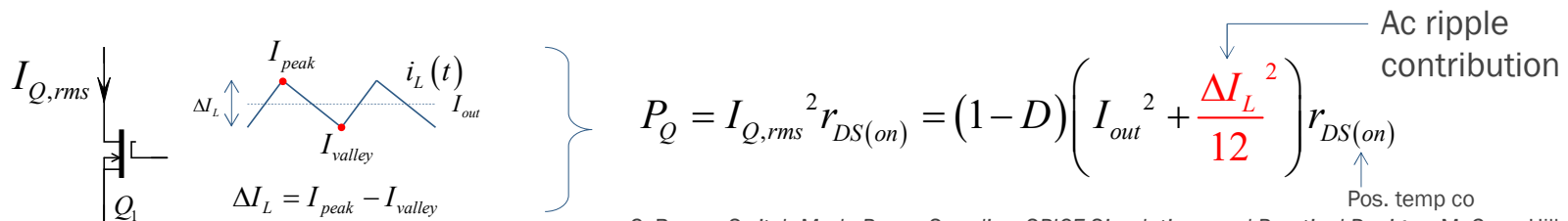
- Replace the diode by a MOSFET and ripple current now matters




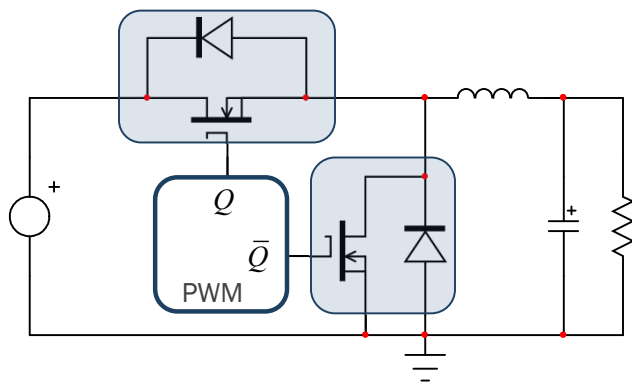
C. Basso, Switch-Mode Power Supplies: SPICE Simulations and Practical Designs, McGraw-Hill, 2nd edition, 2014

Synchronous Rectification Body Diode Conduction


- Limit shoot-through currents by inserting a dead-time



Insert dead-time

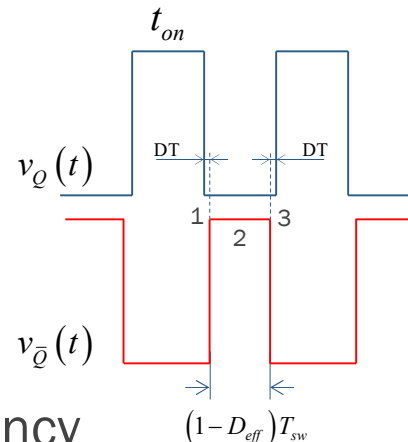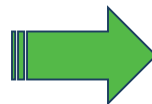


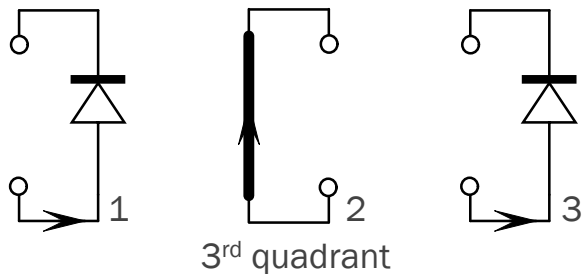- Body diode conduction can hamper efficiency



3rd quadrant

MOSFET + body diode

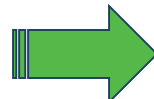

Conduction losses

$$P_Q = I_{Q,rms}^2 r_{DS(on)} = (1 - D_{eff}) \left(I_{out}^2 + \frac{\Delta I_L^2}{12} \right) r_{DS(on)}$$



$$P_{body} = 2 \cdot DT \cdot F_{sw} I_{out} V_f$$

Minimize deadtime without shoot-through



Continuous Conduction in No-Load Conditions

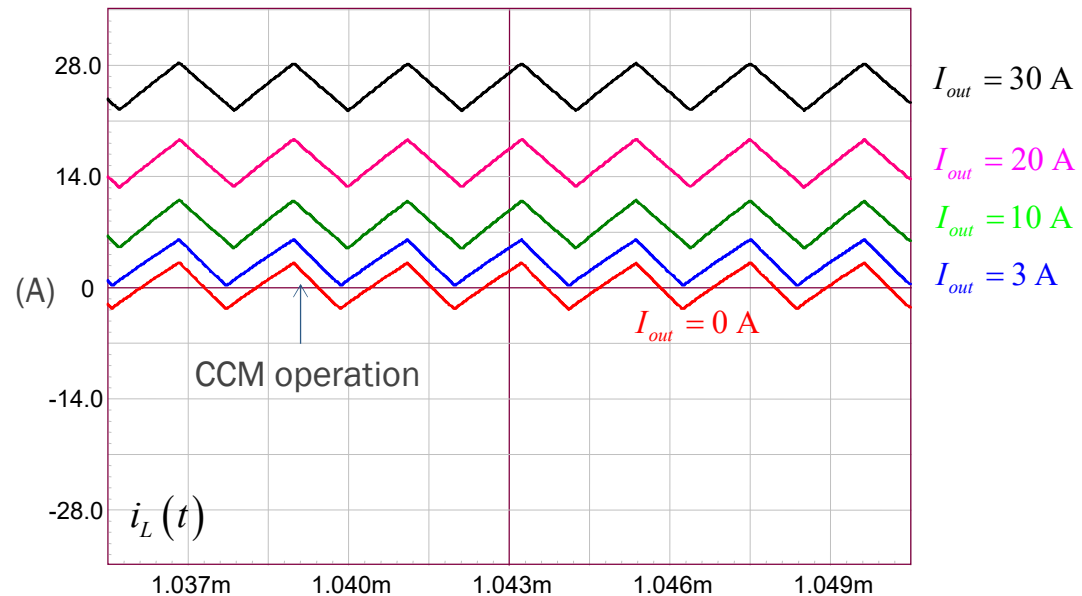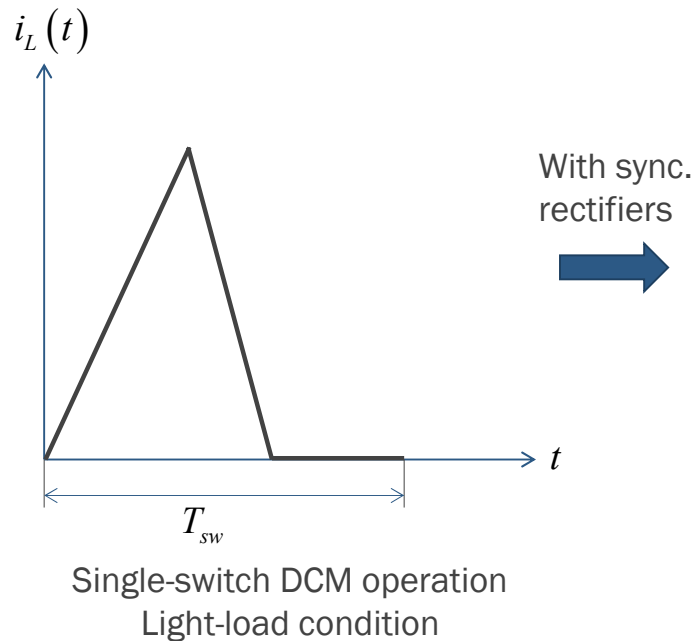- DCM operation is often associated with light- and no-load operation
- Synchronous rectification allows inductor current to swing below 0 A




Course Agenda

- The Buck Converter
- Control Schemes
- Introduction to Modeling
- The PWM Switch in Current-Mode Control
- Introduction to the Fast Analytical Techniques
- The Four Transfer Functions in CCM Current-Mode Control
- Compensation Strategy
- Prototype Measurements



Different Modulation Strategies

Trailing edge

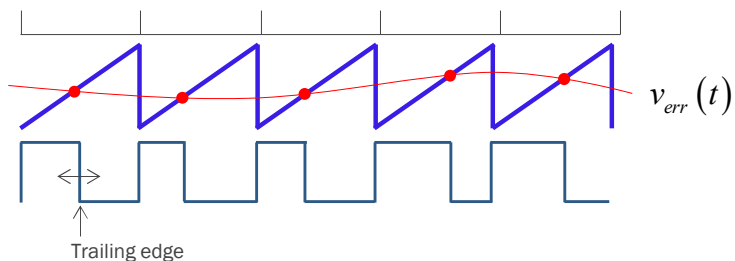


Clocked turn-on
Fast turn-off
Delayed turn-on



Conventional ac-dc, dc-dc

Leading edge

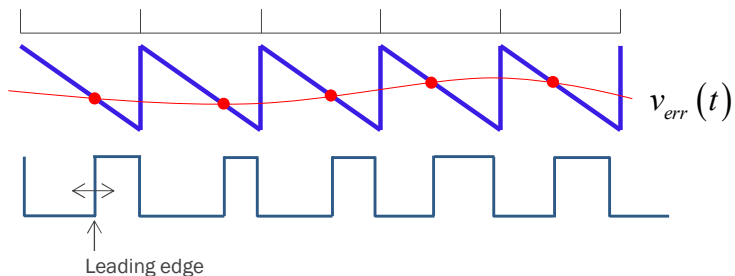


Clocked turn-off
Fast turn-on
Delayed turn-off



Post regulators

Dual edge

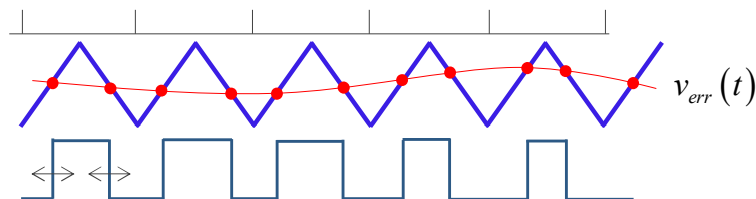


Fast turn-on
Fast turn-off



High-speed dc-dc

Fixed Switching Frequency Operation

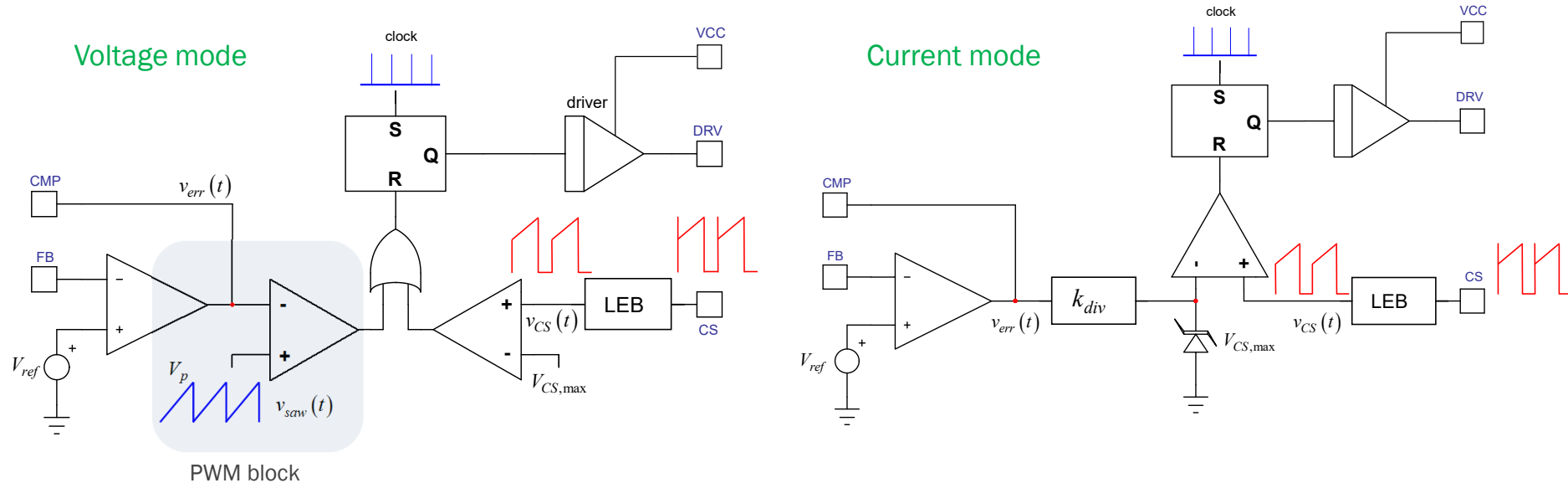- The main switch turns on at the clock occurrence





➤ The duty ratio is directly controlled by V_{err}

- The peak current is controlled by V_{err}
- D is indirectly controlled by V_{err}


Duty Ratio Generation – Pulse Width Modulation

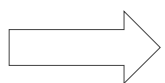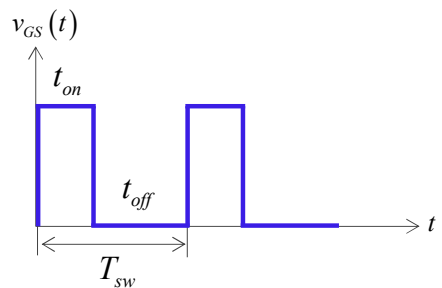□ The power stage is controlled via the duty ratio D



$$D = \frac{t_{on}}{T_{sw}} = \frac{3\mu}{10\mu} = 30\%$$

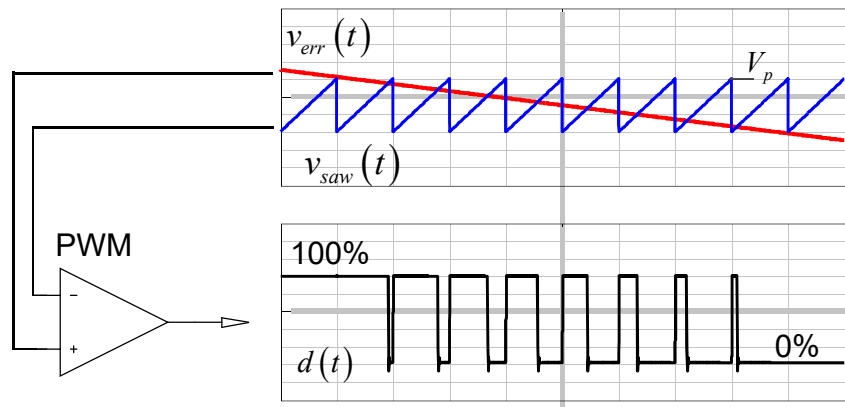□ An artificial ramp is compared to the control voltage



$$\left. \begin{aligned} v_{saw}(t) &= V_p \frac{t}{T_{sw}} \\ v_{err}(t) &= V_p d(t) \end{aligned} \right\} d(t) = \frac{v_{err}(t)}{V_p}$$





Modeling the PWM Block

- Its role is to convert a voltage V_{err} into a duty ratio D

$$d(t) = \frac{v_{err}(t)}{V_p} \xrightarrow{\text{average over } T_{sw}} D(V_{err}) = \frac{V_{err}}{V_p} \longrightarrow G_{PWM} = \frac{dD(V_{err})}{dV_{err}} = \frac{1}{V_p}$$

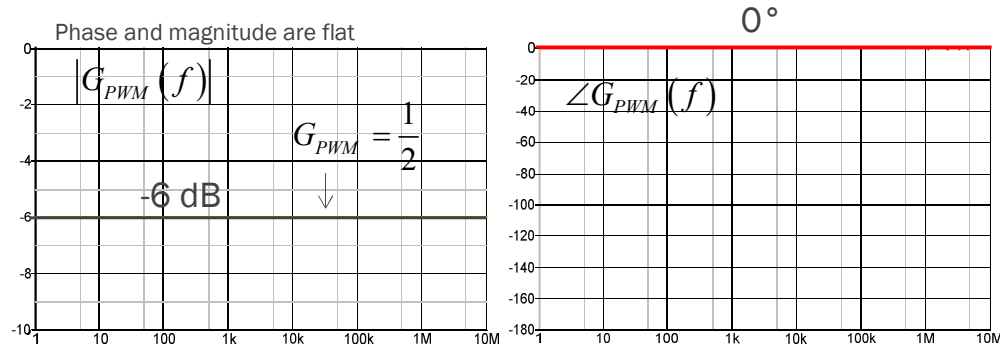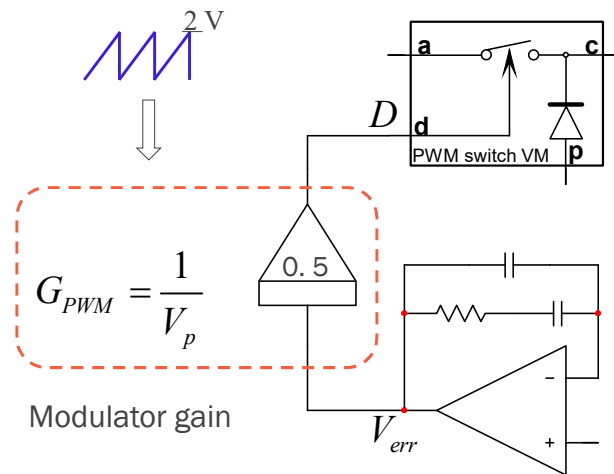- It is a simple block inserted before the D input of the model





Frequency response of the naturally-sampled modulator is flat

→ With a perfect comparator, $t_p = 0$

Current-Mode Operations

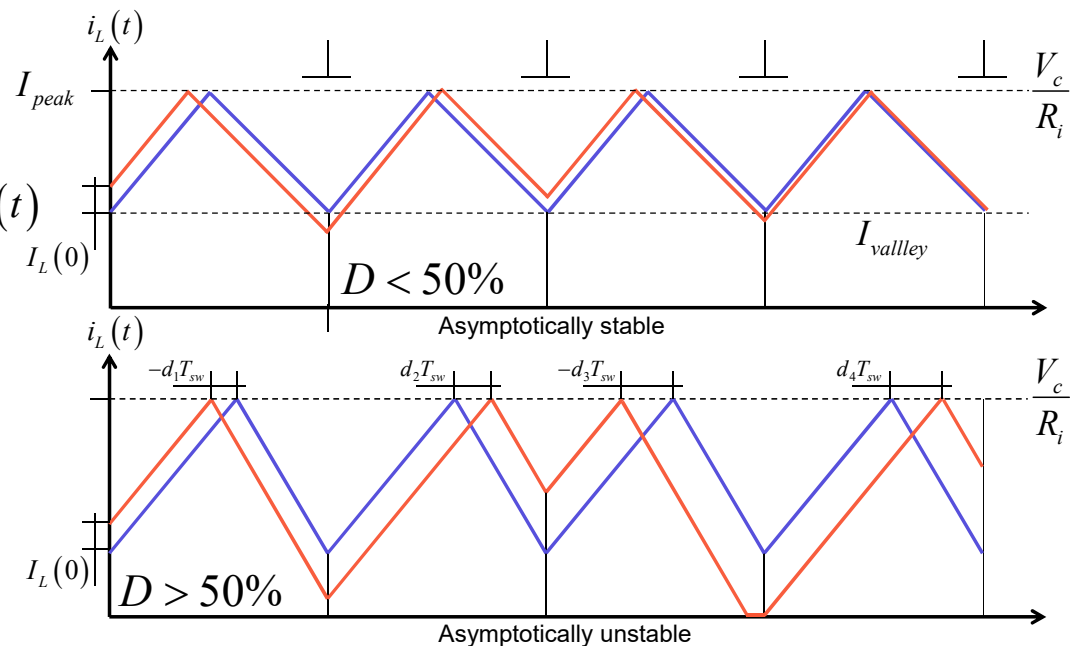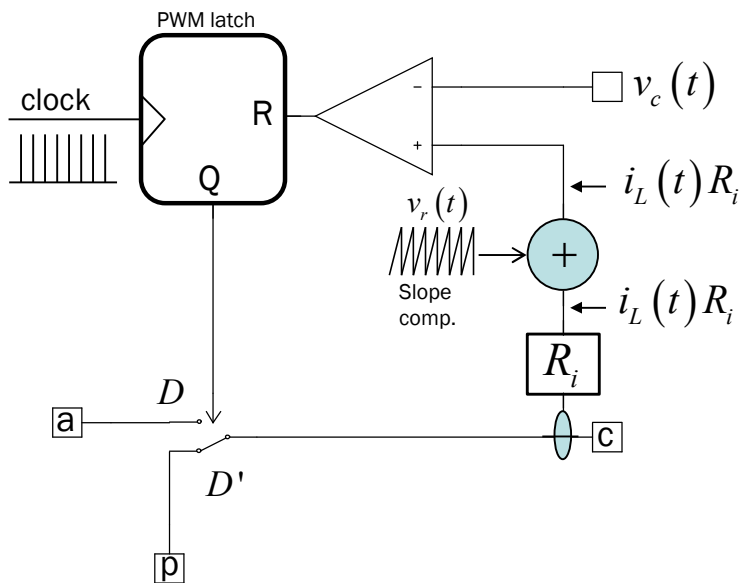
- The artificial ramp is replaced by the inductor current



- In CCM with $D > 50\%$ subharmonic instabilities occur


Slope Compensation Cures Oscillations

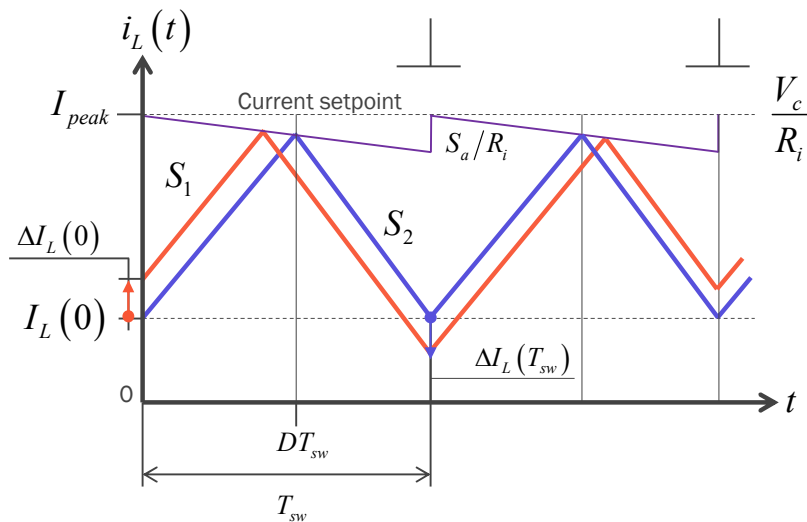□ Injecting an external ramp damps the poles at $F_{sw}/2$




□ Do not overcompensate

❖ Current mode turns into voltage mode

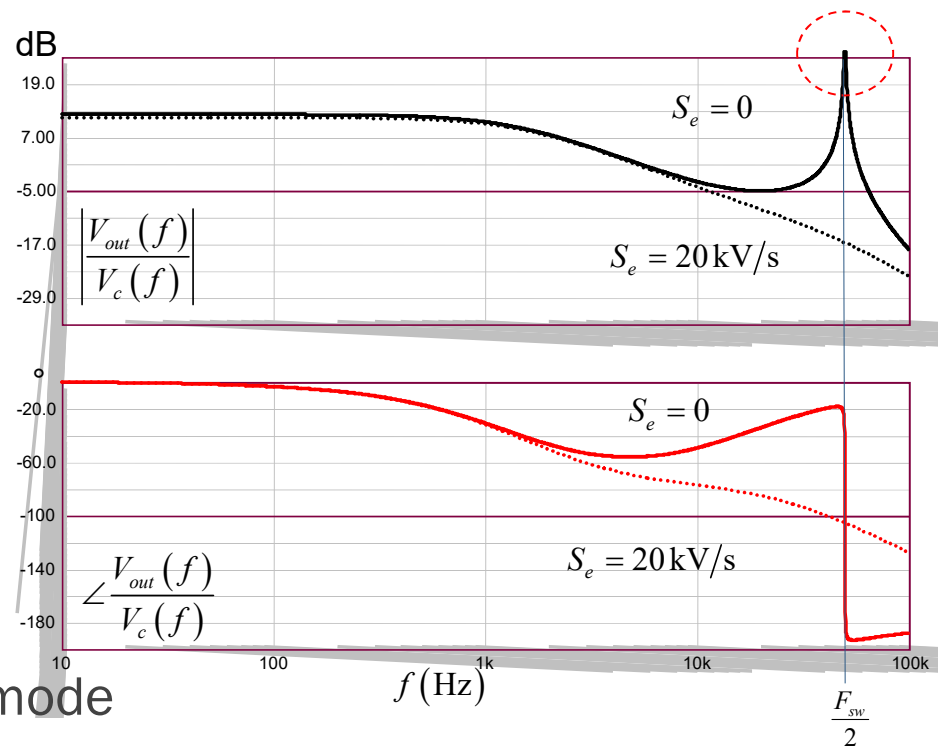


Self-Relaxing Quasi-Resonant Operations

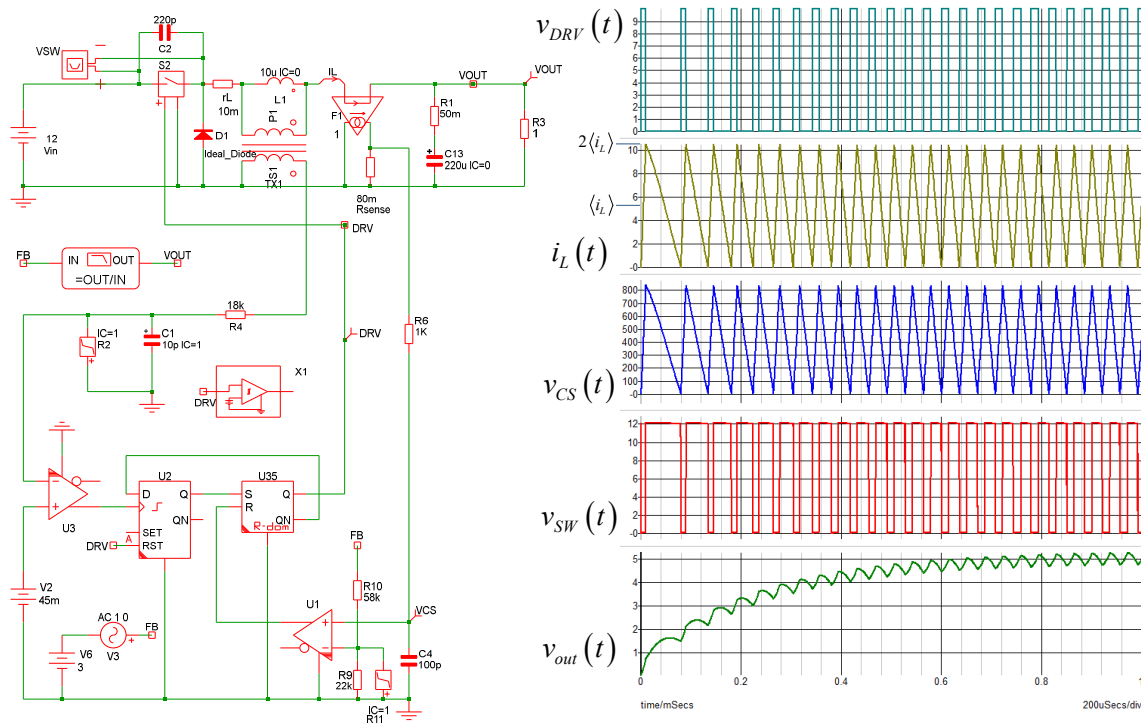□ The converter operates in borderline conduction mode



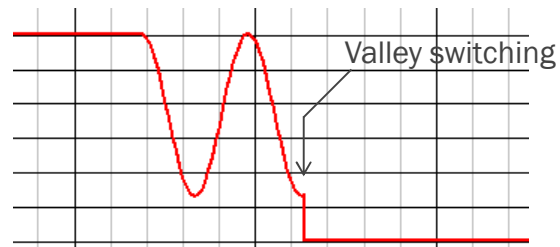- ❖ 200% inductor ripple current
- ❖ load/line-dependent frequency
- ❖ needs an extra winding over L




$v_{SW}(t)$


- ✓ Reduced switching losses

Hysteretic Control – the Basic System

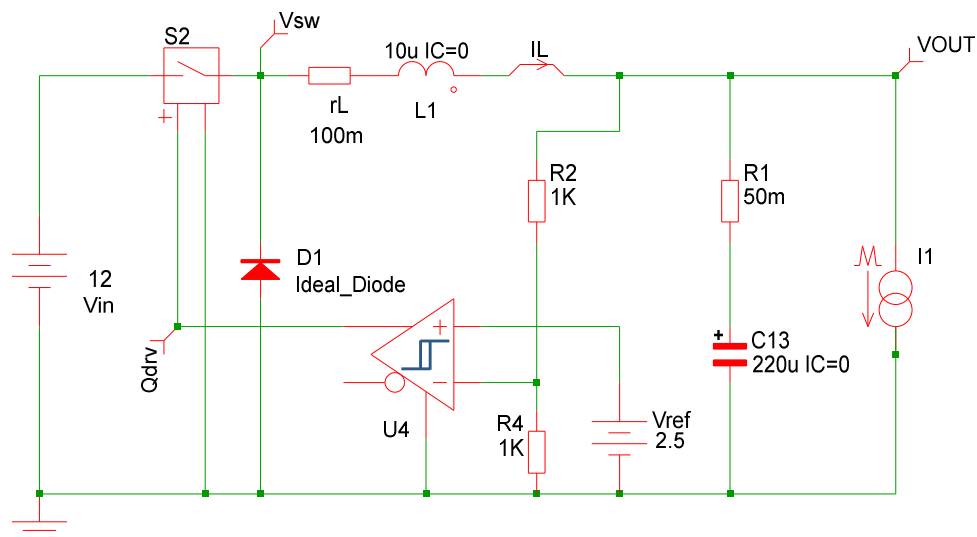□ The simplest and fastest switching converter



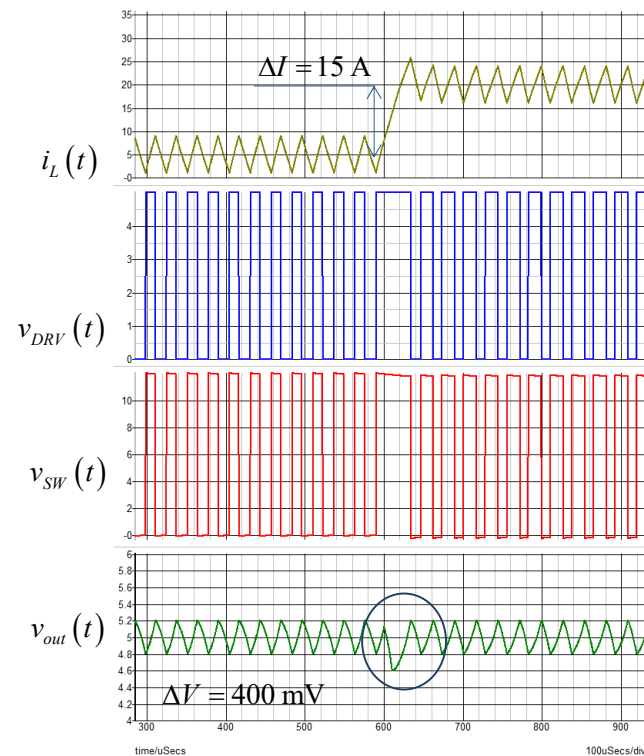
- ❖ Variable frequency operation
- ❖ Capacitor ESL affects stability in DCM



R. Redl and J. Sun, *Ripple-based control of switching regulators—an overview*, IEEE Tr. Power Electronics, Dec. 2009, 4 vol. 24, no. 12, pp. 2669 – 2680.


Hysteretic Control – Adding an Op-Amp

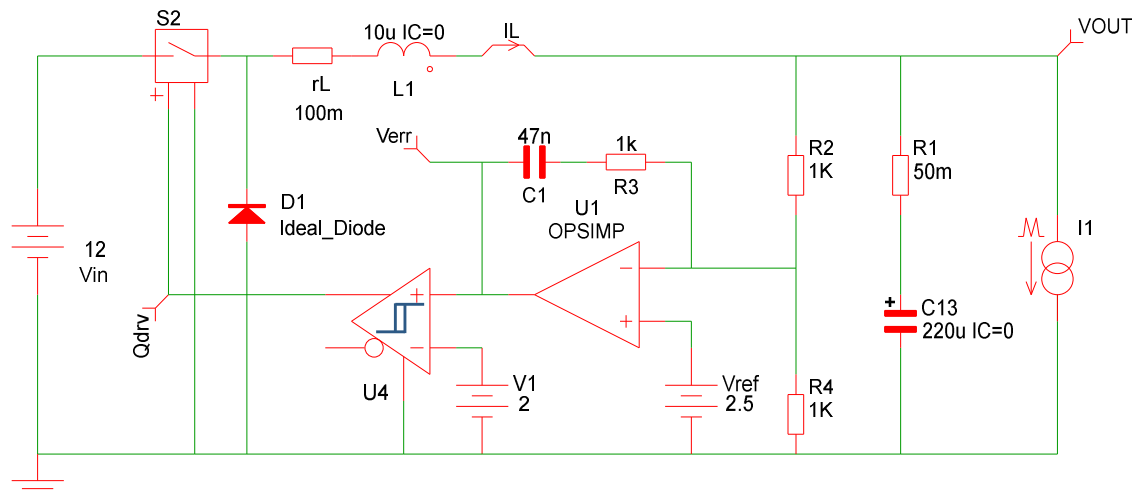❑ You can add an error amplifier to improve dc regulation



❖ A compensation network is needed


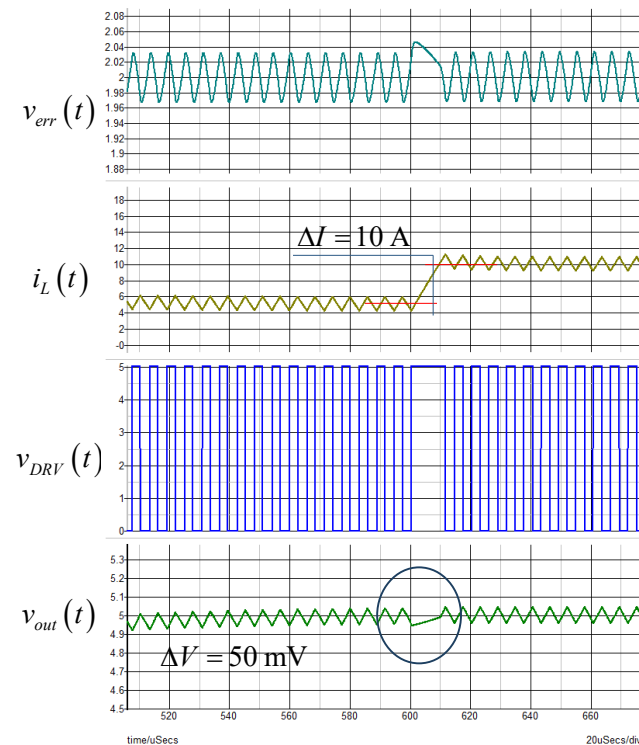
❑ Many techniques to:
stabilize F_{sw} , improve stability, reduce drop...



R. Redl, Ripple-Based Dc-Dc Converters, In-House Seminar, Toulouse 2010.

Extension to Multiphase Conversion

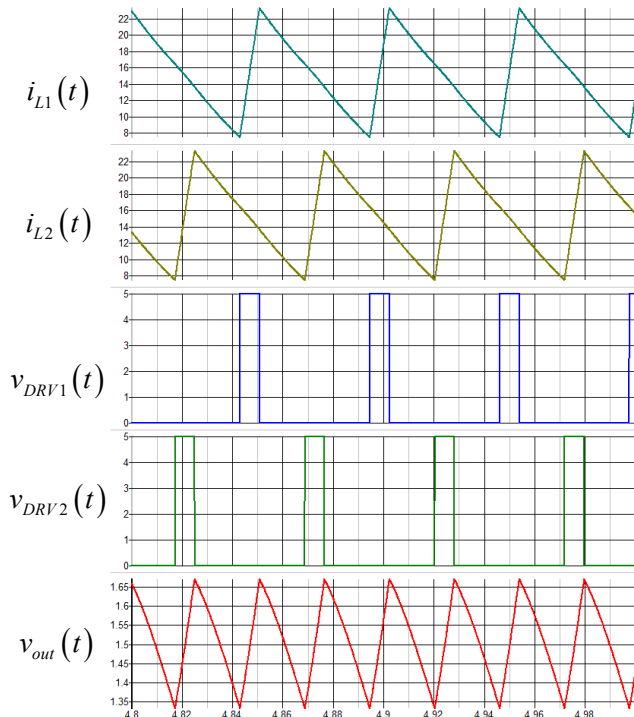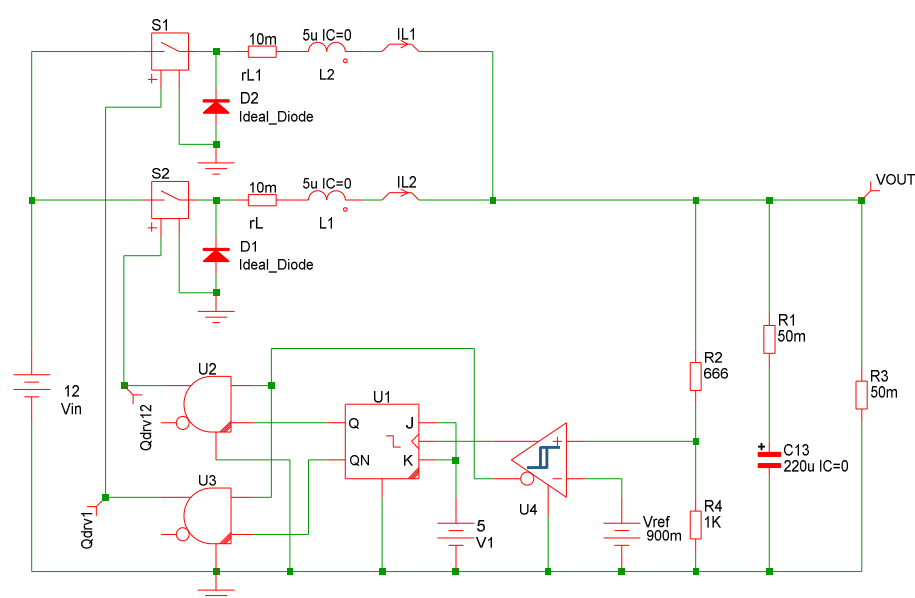❑ The two-phase extension requires a simple logic control



OVP: optimal voltage positioning


- ❖ Bad dynamic current sharing (no sensing)
- ❑ Popular in dc-dc with OVP (motherboards)



Constant-On-Time Valley-Current Control - COT


□ On-time duration is fixed – restart is given by the valley current

On-time generator

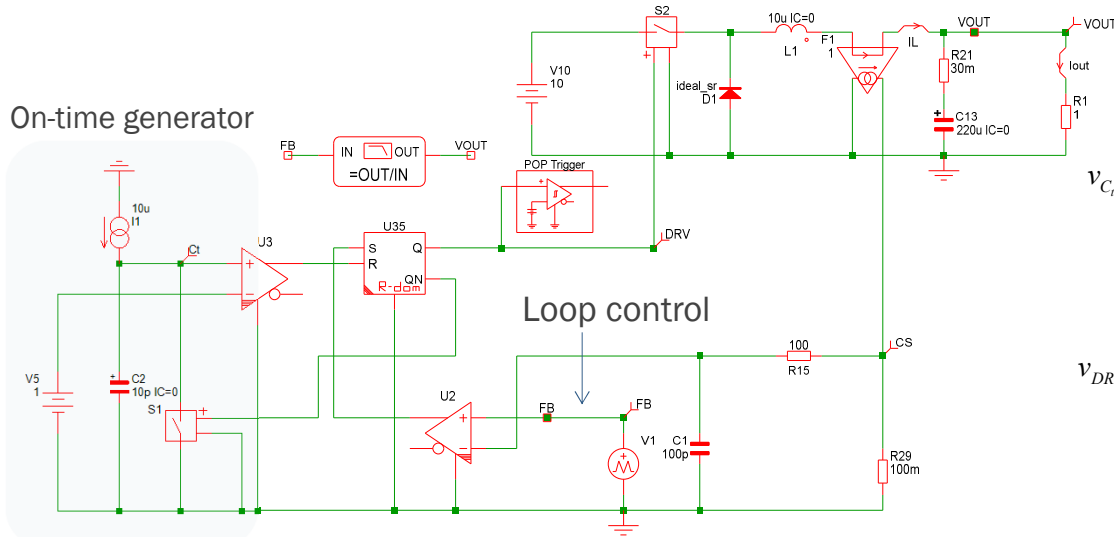

❖ Can be subject to instabilities

$$r_c C > \frac{t_{off}}{2}$$


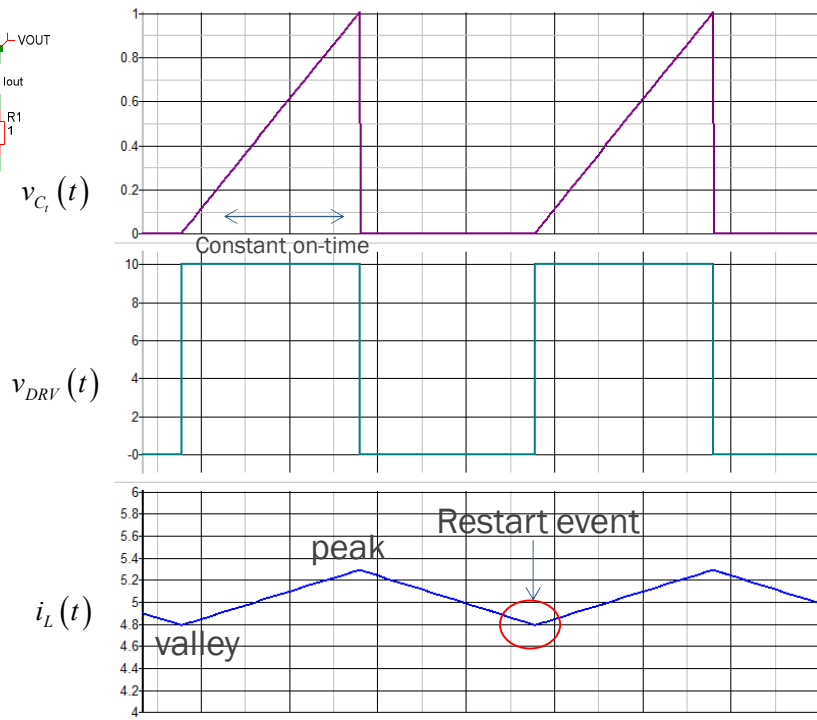


R. Redl, *Ripple Regulator Review*, Professional Education APEC seminar 2008.

Fixed-Off-Time Peak-Current Control - FOT


❑ Off-time duration is fixed – restart is given by the peak current

Off-time generator

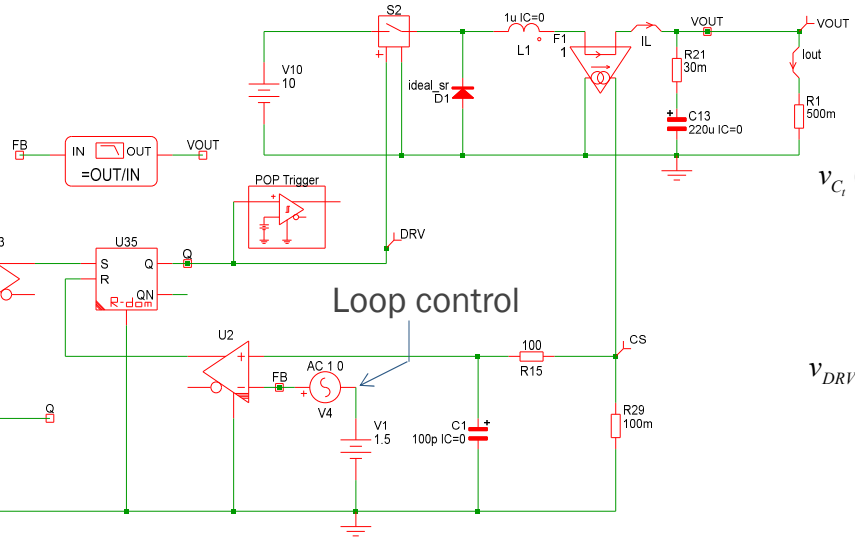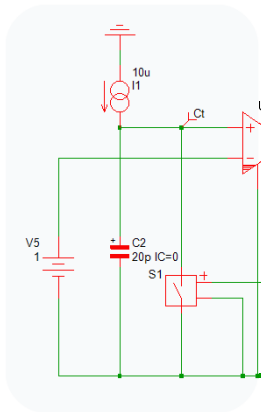

❖ Can be subject to instabilities

$$r_c C > \frac{t_{on}}{2}$$

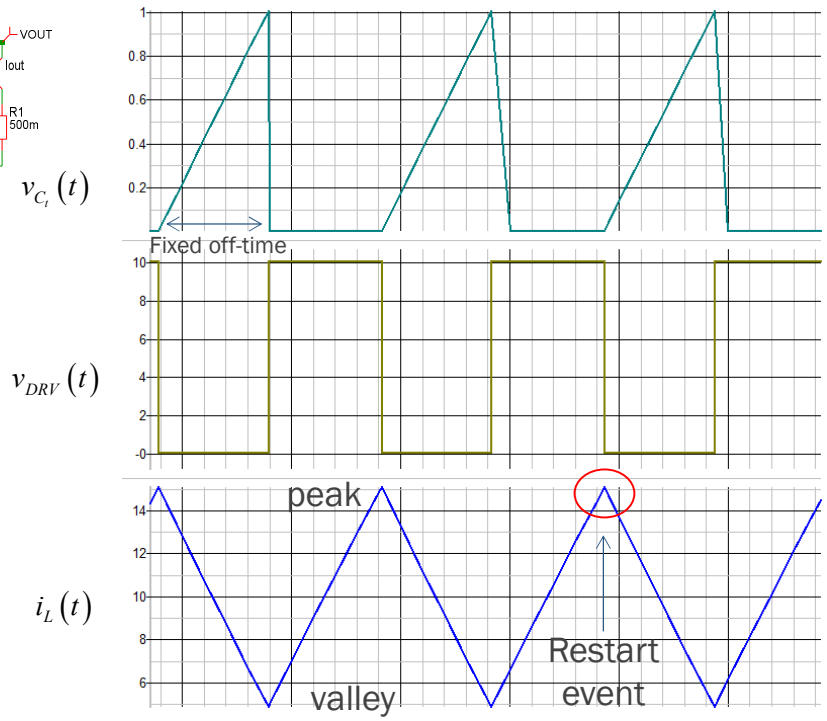

R. Redl, *Ripple Regulator Review*, Professional Education APEC seminar 2008.


Course Agenda

- The Buck Converter
- Control Schemes
- Introduction to Modeling
- The PWM Switch in Current-Mode Control
- Introduction to the Fast Analytical Techniques
- The Four Transfer Functions in CCM Current-Mode Control
- Compensation Strategy
- Prototype Measurements




Time-Discontinuous Switching Waveforms

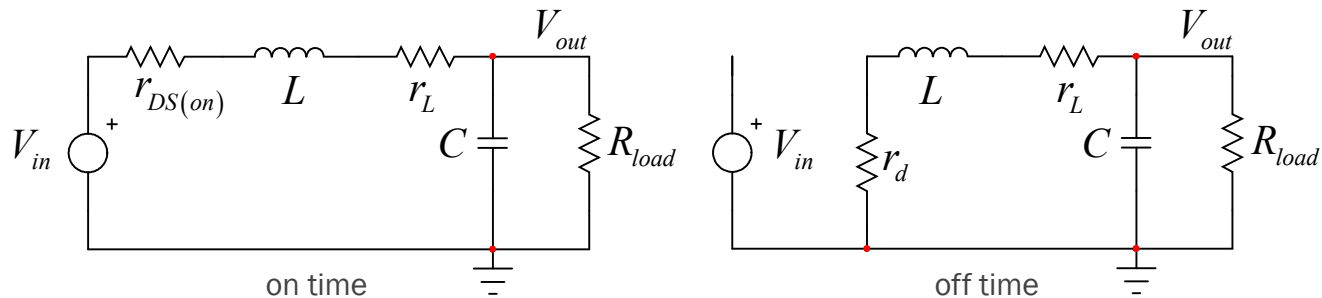
- A switching converter is made of linear elements



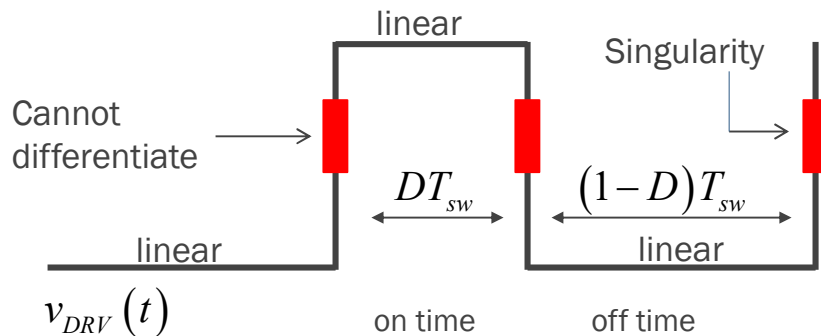- The non-linearity or discontinuity is coming from transitions



How do we get this?

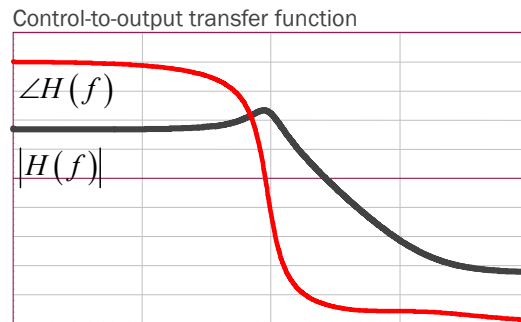

State Space Averaging Technique

- ❑ Despite linear networks, equation is discontinuous in time
- ❑ Introduced in 76, SSA weights on and off expressions


$$\dot{x} = \left[\mathbf{A}_1 D + \mathbf{A}_2 (1-D) \right] x(t) + \left[\mathbf{B}_1 D + \mathbf{B}_2 (1-D) \right] u(t)$$

valid during $(1-D)T_{sw}$
valid during DT_{sw}

\mathbf{A} is the state coefficient matrix
 \mathbf{B} is the source coefficient matrix

- ❑ Singularity is gone (time continuous)
- ❖ Equation is nonlinear now
- ❑ Linearize and feed the canonical model
- ❖ Add a new element: restart from scratch!


Canonical model

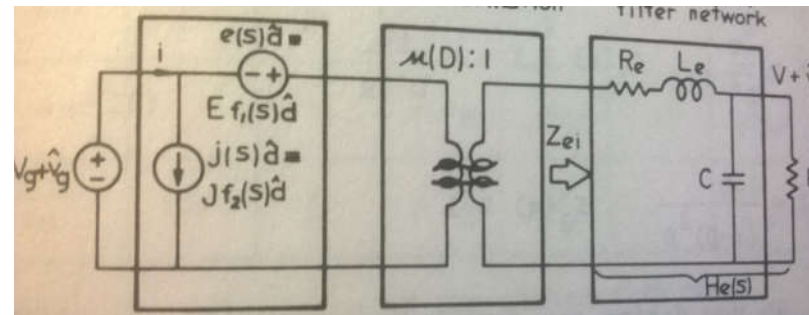

S.Ćuk, Modeling, Analysis and Design of Switching Converters, Ph. D. Thesis, Caltech November 1976

The PWM Switch Model in Voltage Mode

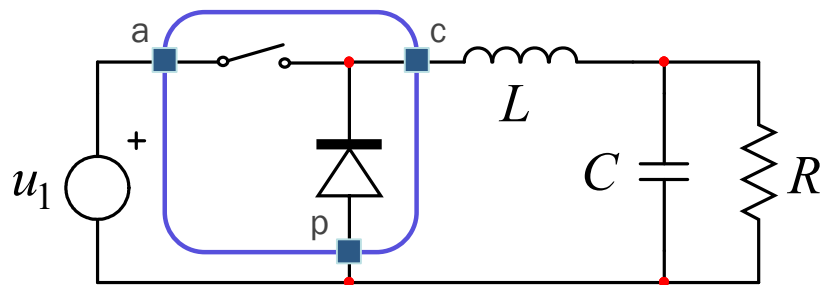- We know that non-linearity is brought by the switching cell




a: active
c: common
p: passive



Add a filter or a resistance



- Why not linearize the cell alone?

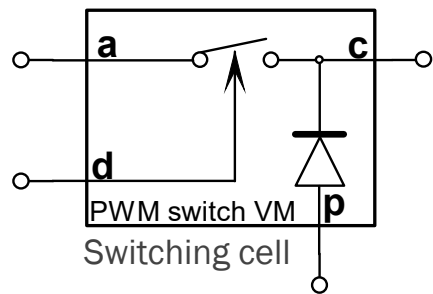

Small-signal model
(CCM voltage-mode)

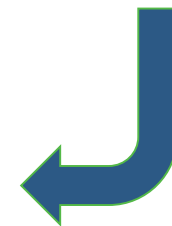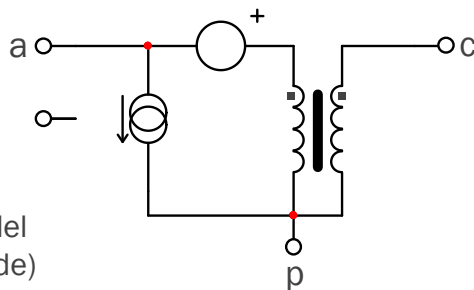


Model is unchanged

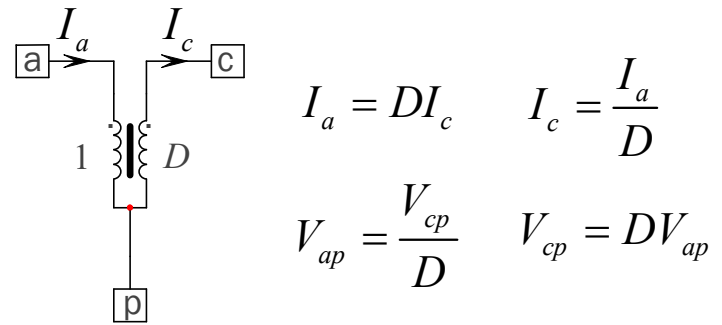V. Vorpérian, *Simplified Analysis of PWM Converters using Model of PWM Switch*, IEEE Transactions on Aerospace and Electronic Systems, Vol. 26, NO. 3, 1990



The VM-PWM Switch Model is a Transformer

❑ The PWM switch large-signal model is a dc "transformer"!




Immediate results

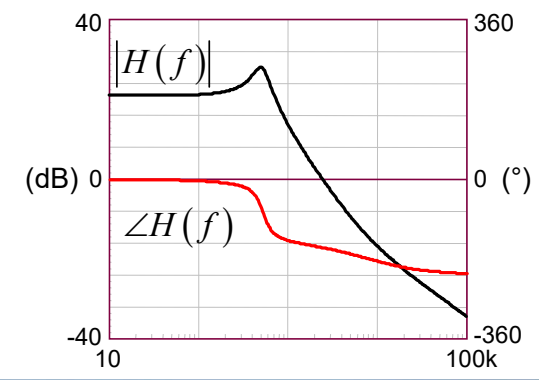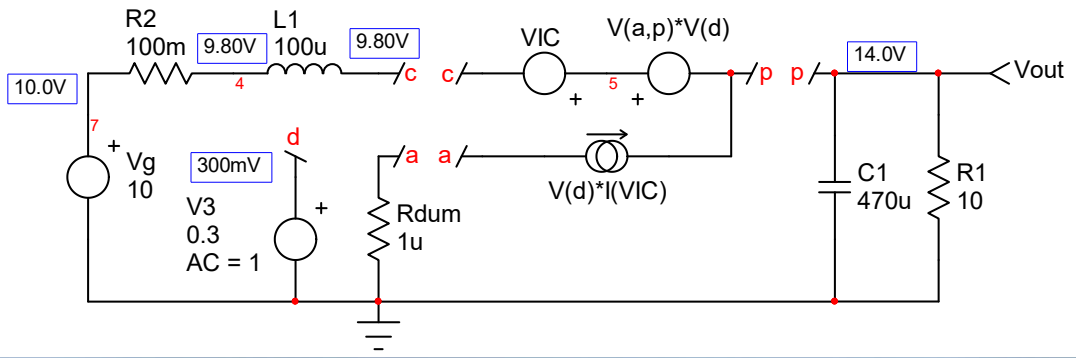❑ It can be plugged into any 2-switch CCM converter




Update the Schematic Diagram with the PWM Switch

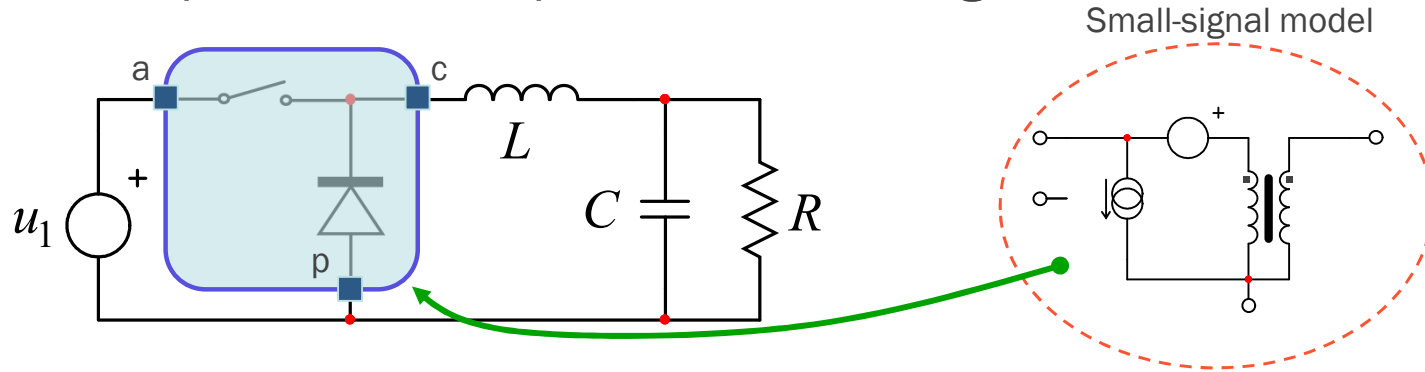- Like in a bipolar circuit, replace the switching cell...




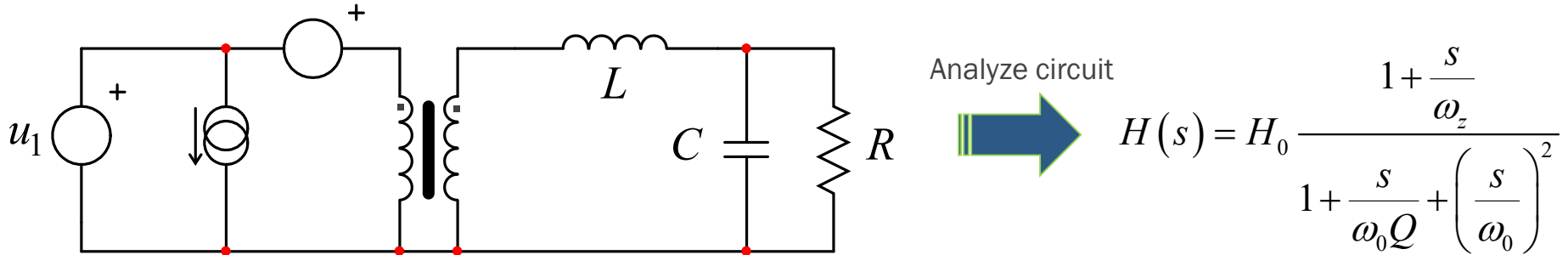- ...and solve a set of linear equations!





The Model fits all Converters Architectures

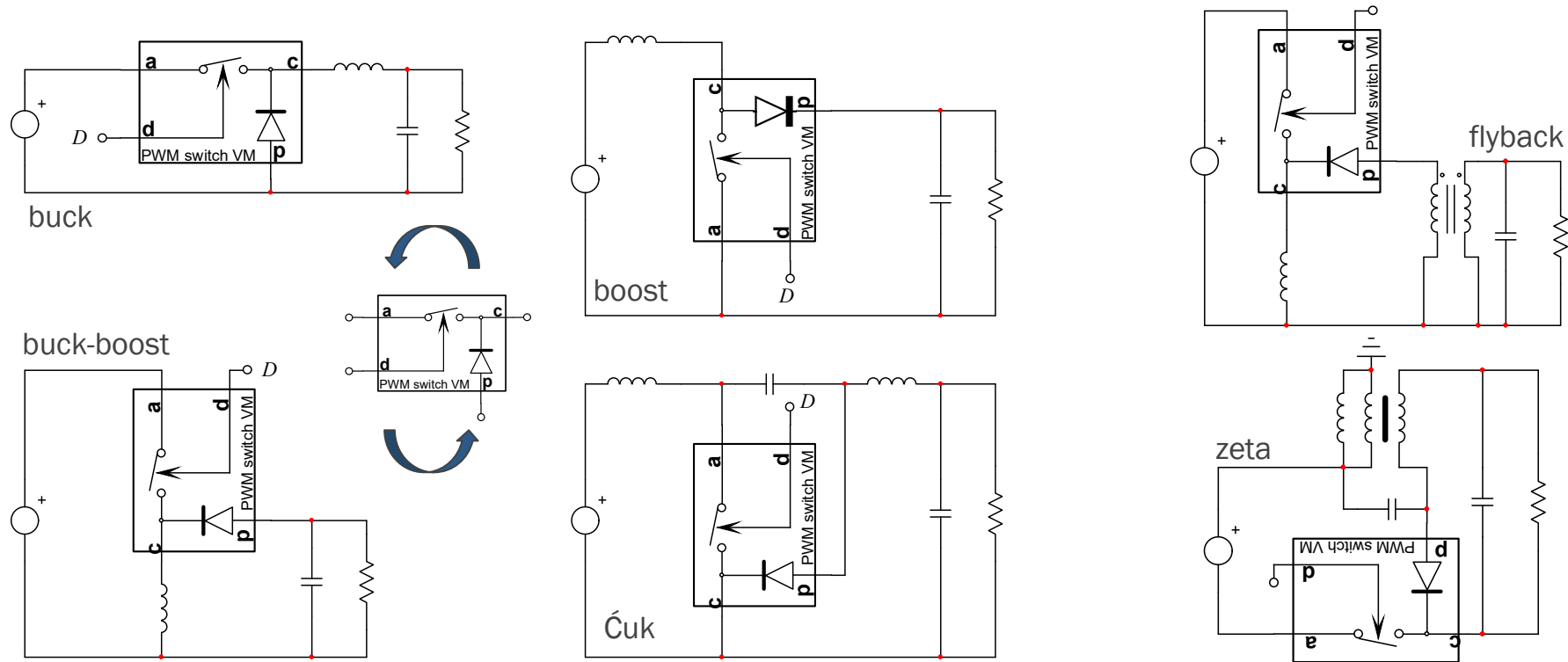□ The switching cell is everywhere: the model is invariant



Independent Switch Modeling: Direct Connections


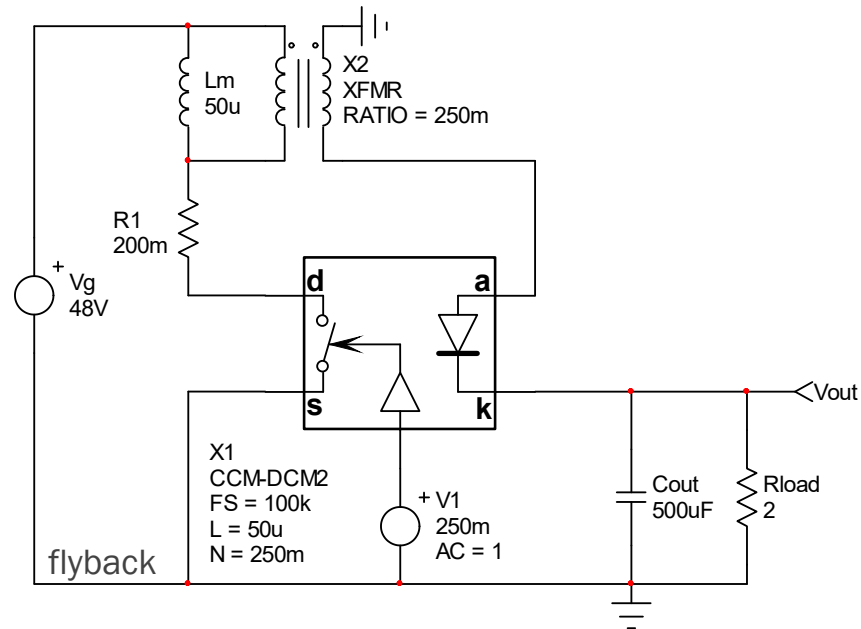
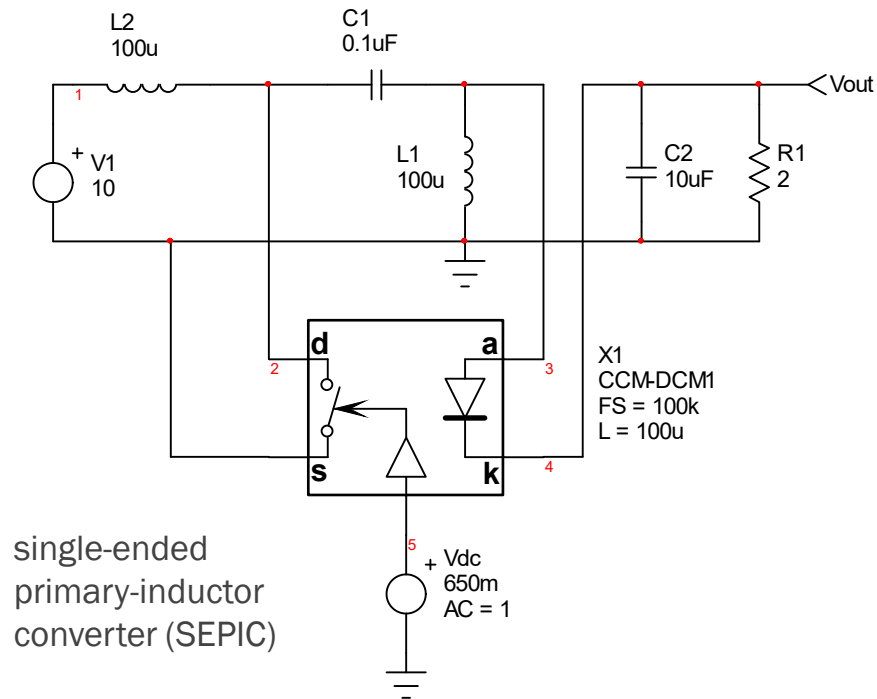
□ The switch and diode are individually modeled: easy substitution



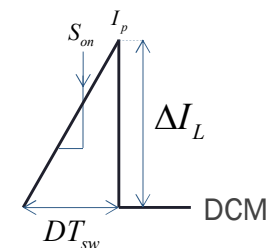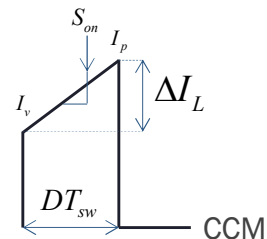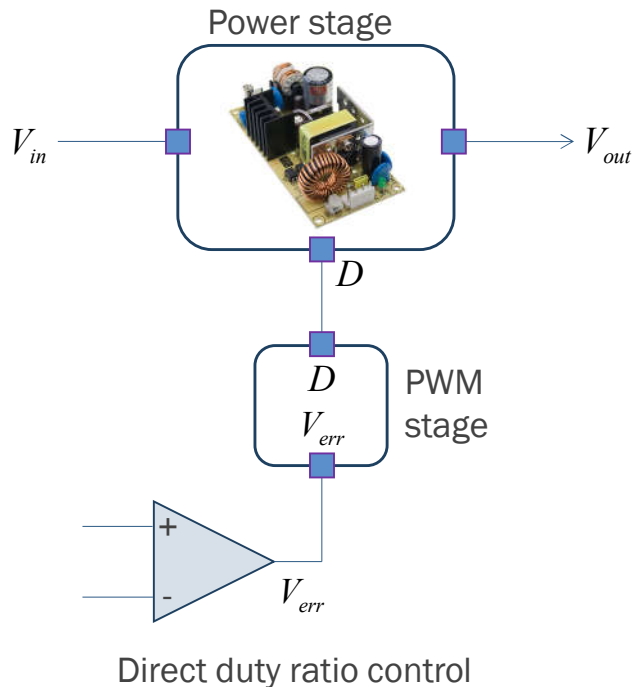
B. Erickson, D. Maksimovic, *Advances in Averaged Switch Modeling and Simulation*, professional seminar, PESC, Charleston, 1999

Peak-Current-Mode Control Models

- The control voltage V_c adjusts the inductor peak current
- ❖ the duty ratio is indirectly controlled by V_c





Same static waveforms in VM and CM

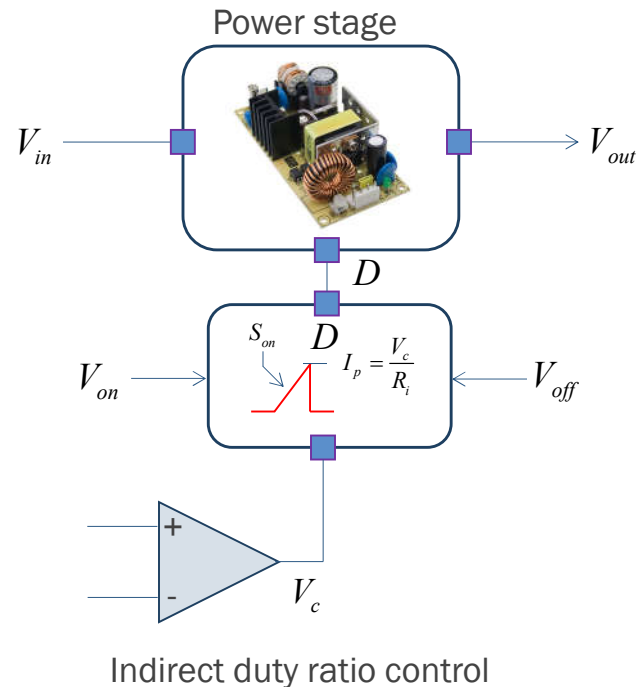


A VM-PWM Switch-Based Small-Signal Model

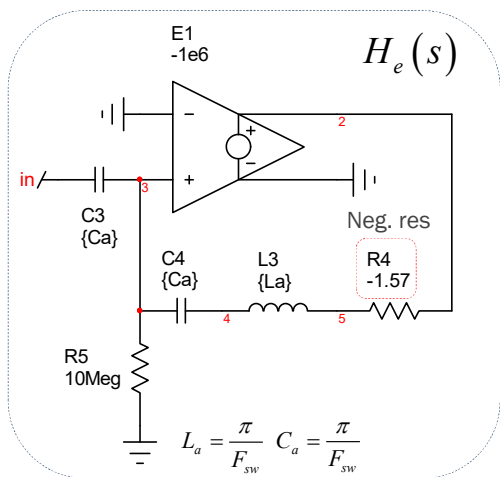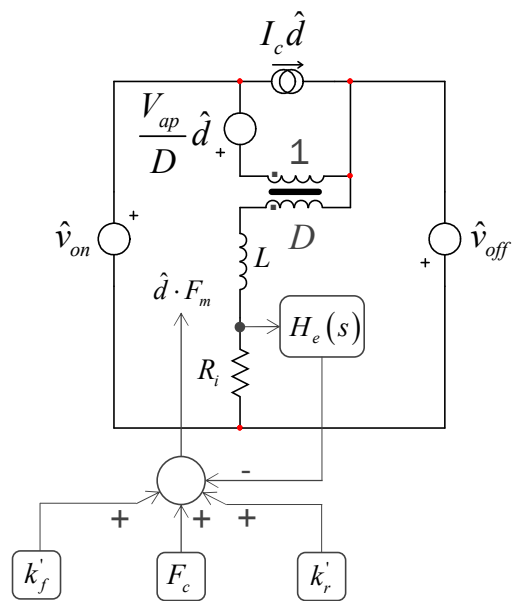□ Small-signal model built after sampled-data analysis



Pair of RHP Zeroes

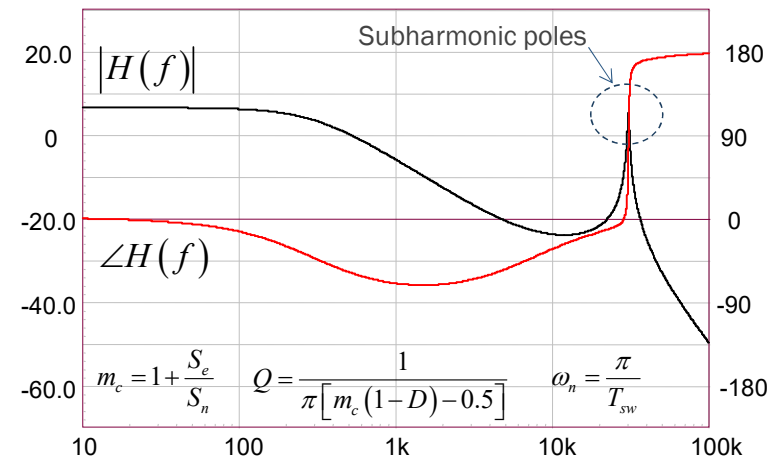

$$m_c = 1 + \frac{S_e}{S_n} \quad Q = \frac{1}{\pi [m_c (1-D) - 0.5]} \quad \omega_n = \frac{\pi}{T_{sw}}$$


□ Model accurately predicts subharmonic oscillations but is ac only

R. Ridley, *A New Small-Signal Model for Current Mode Control*, Ph. D. dissertation, Virginia Polytechnic Institute and State University, 1990



A Current-Mode PWM Switch Model

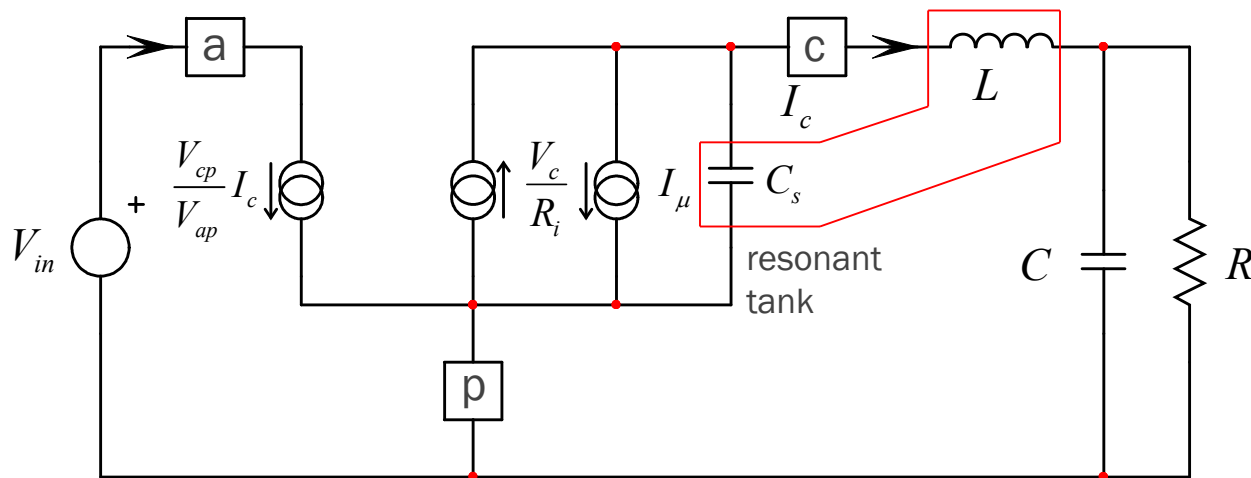- The large-signal model associates three simple current sources



$$H(s) \approx H_0 \frac{1 + \frac{s}{\omega_{z_1}}}{1 + \frac{s}{\omega_{p_1}}} \frac{1}{1 + \frac{s}{\omega_n Q} + \left(\frac{s}{\omega_n}\right)^2}$$


Same result with that obtained with sampled-data analysis.

- It can compute a bias point and accepts transient simulations
- The resonant tank reproduces subharmonic oscillations

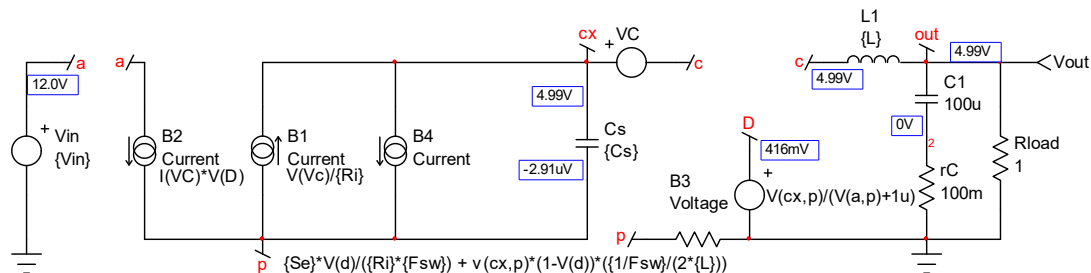V. Vorpérian, *Analysis of Current-Controlled PWM Converters using the Model of the PWM Switch*, PCIM Conference, 1990


Implementing the CM-PWM switch Model

❑ You cannot beat the CM-PWM switch model in terms of simplicity




parameters

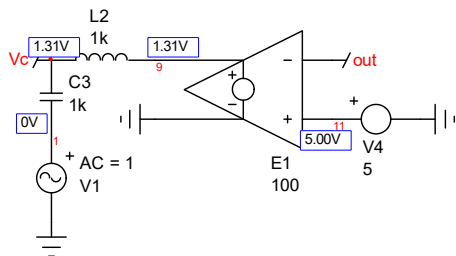$V_{in}=12$
 $V_{out}=5$
 $F_{sw}=100k$
 $T_{sw}=1/F_{sw}$
 $L=100u$
 $\pi=3.14159$
 $C_s=1/(L*(F_{sw}*\pi)^2)$
 $R_i=250m$
 $S_e=7k$



Only these parameters are needed


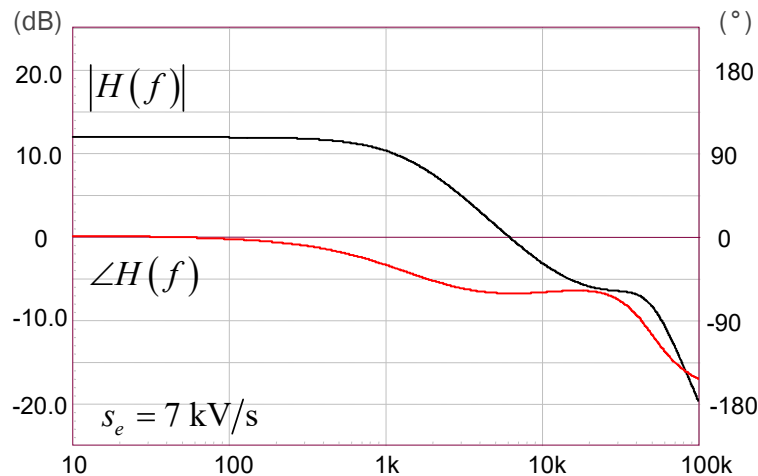


Poles are damped by slope compensation

➤ It is a large-signal model which also predicts transient response

Extended Frequency-Range PWM Model

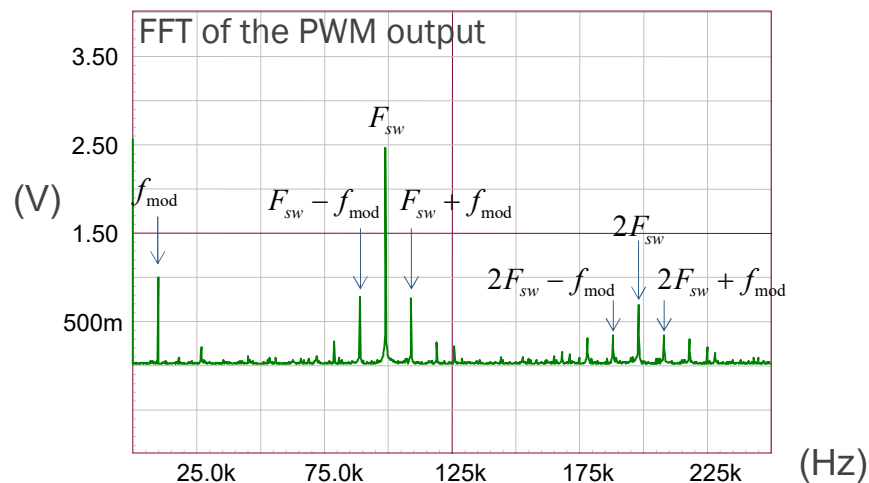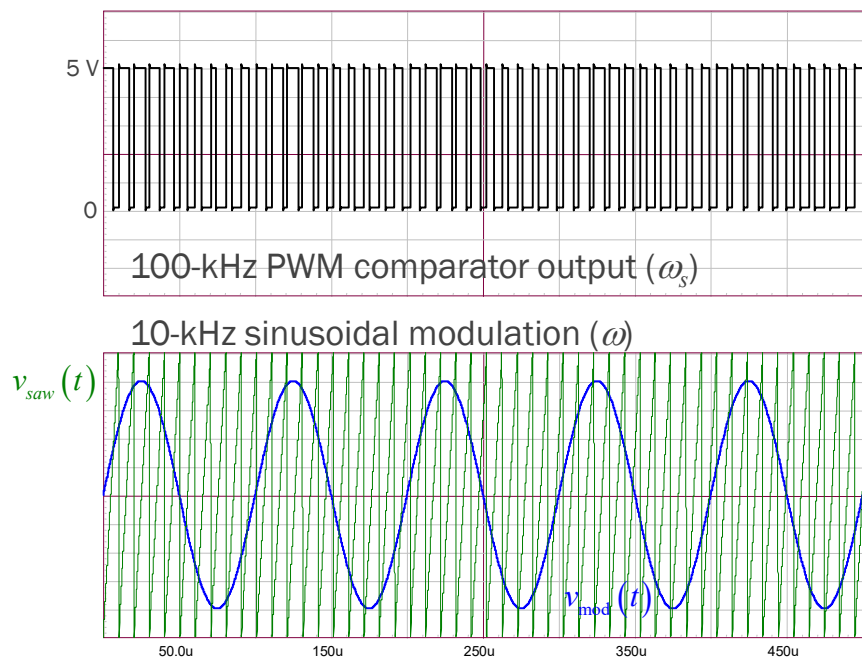- ❑ The pulse width modulator is a highly nonlinear structure









- ❖ Harmonics are fed back through the loop
- ❖ Additional perturbations go through PWM
- Aliasing effects are observed

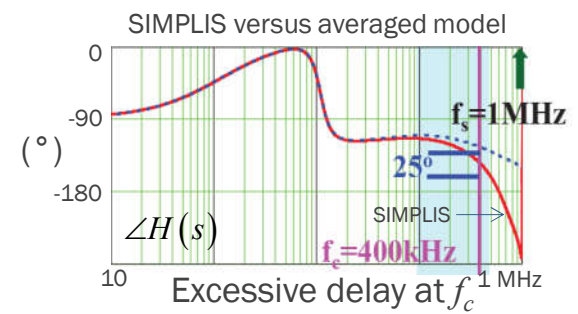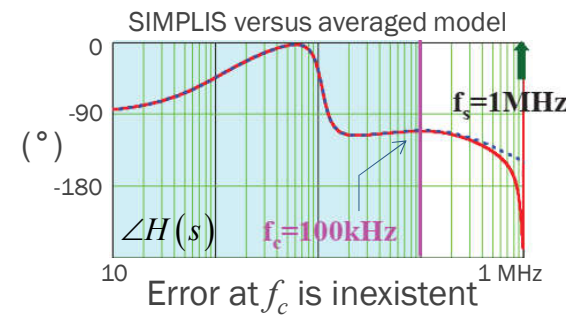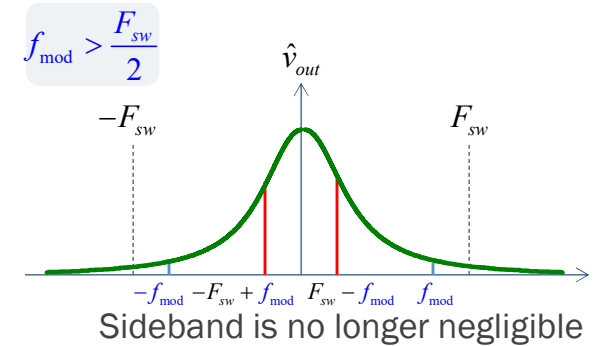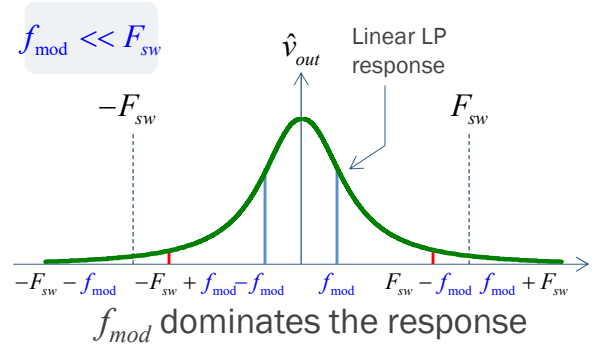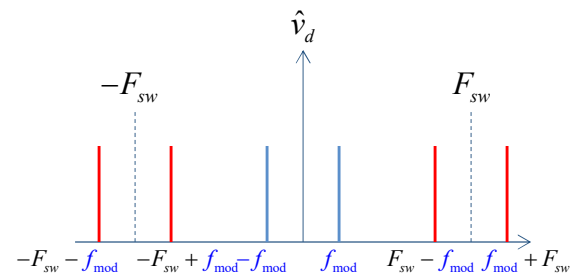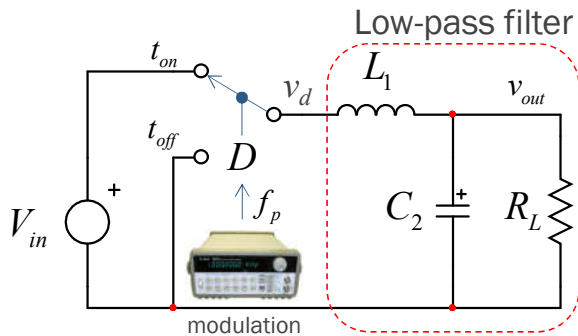X. Lin and al., *Small-Signal Models with Extended Frequency Range for dc-dc Converters with Large Modulation Ripple*, IEEE Transactions on Power Electronics, VOL. 33, NO. 9, September 2018

Predicting Phase Lag Approaching $F_{sw}/2$

□ Modulation and sidebands go through the low-pass filter



F. Lee, Review of Current-Mode-Control Modeling, APEC 2017 Professional Education Seminars, Tampa, FL




Accounting for Sidebands Effects

□ Harmonics are responsible for the phase deviation as f_{mod} approaches $F_{sw}/2$


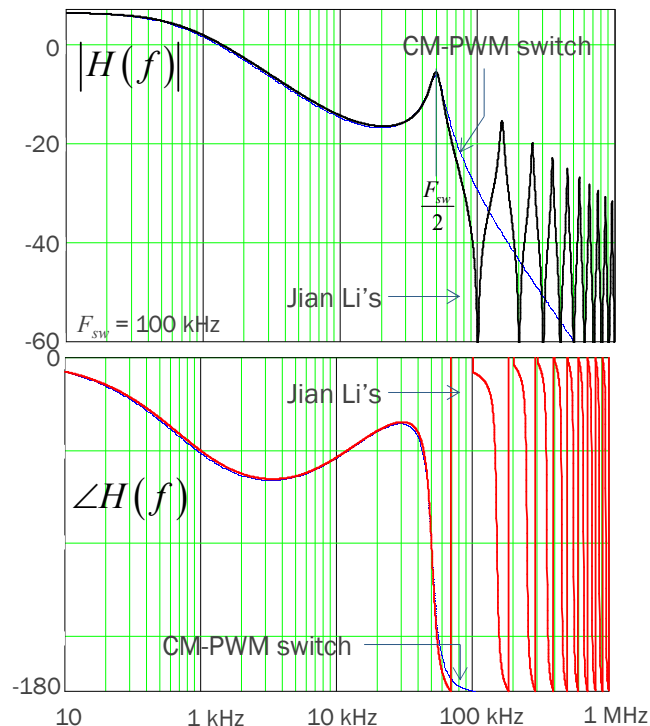
$$\frac{V_{out}(s)}{V_c(s)} = \frac{F_{sw}}{(S_n + S_e) + (S_f - S_e)e^{-sT_{sw}}} \frac{R_{load}V_{in}}{sL} \frac{1 + \frac{s}{\omega_z} (1 - e^{-sT_{sw}})}{1 + \frac{s}{\omega_p}}$$



J. Li, F.C. Lee, New Modeling Approach and Equivalent Circuit Representation for CM Control, Power Electronics IEEE Transactions, VOL. 25, NO. 5, pp. 1218-1230, May 2010




Simplifying The Model towards a Universal Subcircuit

- Yingyi Yan's model is a universal subcircuit covering various operating schemes

parameters

$V_{in}=12$
 $V_{out}=5$
 $F_{sw}=100k$
 $T_{sw}=1/F_{sw}$
 $L=100\mu$
 $\pi=3.14159$
 $C_s=1/(L*(F_{sw}*\pi)^2)$
 $R_i=250m$
 $V_{ac}=V_{in}-V_{out}$
 $V_{ap}=V_{in}$
 $V_{cp}=V_{out}$
 $S_e=0$
 $S_n=(V_{ac}/L)*R_i$
 $S_f=(V_{cp}/L)*R_i$
 $V_c=1.28$
 $R_e=L/(((S_n+S_e)/(S_n+S_f))-0.5)*T_{sw}$
 $C_e=T_{sw}^2/(L*\pi^2)$
 $D=418m$
 $w_2=\pi/T_{sw}$
 $Q_2=1/(\pi*(((S_n+S_e)/(S_n+S_f))-0.5))$
 $k_{in}=(D/L)*(1/(Q_2*w_2)-(1-D)*T_{sw}/2)$

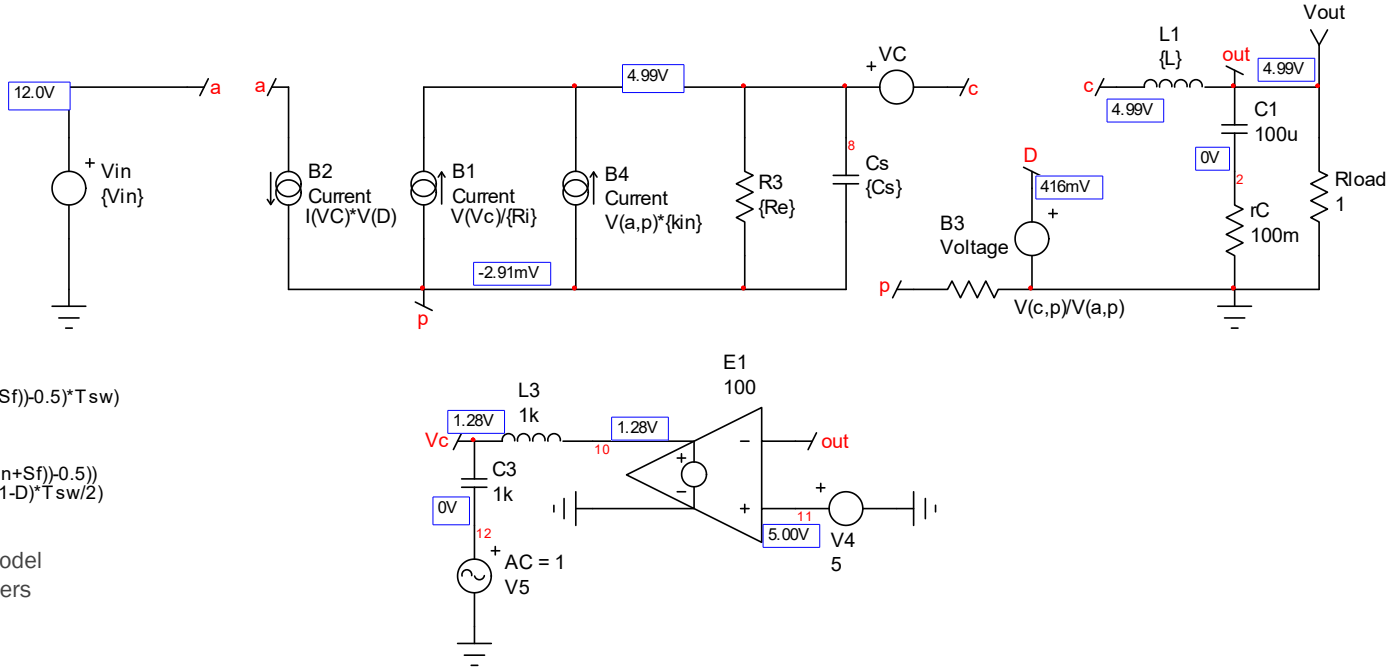Need to feed the model with static parameters



- Same performance as CM-PWM switch but with a more complex implementation

Y. Yan, F. Lee, P. Mattavelli, *Unified 3-Terminal Switch Model for Current Mode Controls*, IEEE Transactions on Power Electronics, VOL. 27, NO. 9, Sept. 2012


Five Different Control Schemes can be Analyzed

□ Replace some parameters with new expressions and simulate

Constant On-Time:

$$C_e = t_{on}^2 / (L\pi^2) \quad R_e = 2L/t_{on}$$

$$K_{ap} = t_{off} / t_{on}$$

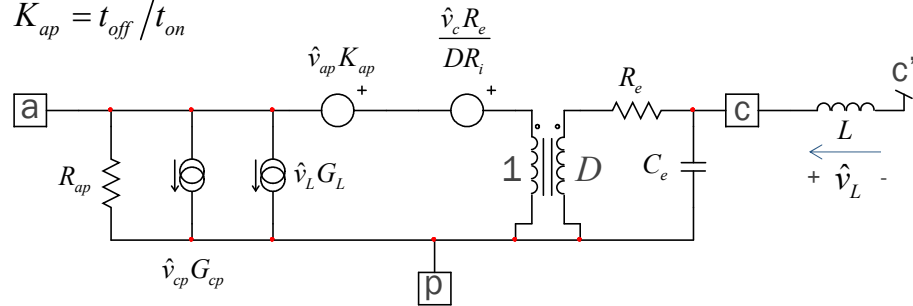

Constant Off-Time:

$$C_e = t_{off}^2 / (L\pi^2) \quad R_e = 2L/t_{off}$$

$$K_{ap} = -1$$

Charge Control:

$$C_e = T_{sw}^2 / (L\pi^2) \quad R_e = L / \left[T_{sw} \left(\frac{LI_c}{V_{cp} T_{sw}} - \frac{D}{2} + \frac{S_e}{S_f} \frac{C_T}{T_{sw}} \right) \right]$$

$$K_{ap} = (t_{off} / 2L) R_e$$

Valley-Current Mode Control:

$$C_e = T_{sw}^2 / (L\pi^2) \quad R_e = L / \left[T_{sw} \left(\frac{S_n + S_e}{S_n + S_f} - 0.5 \right) \right]$$

$$K_{ap} = (t_{on} / 2L) R_e$$

Peak-Current Mode Control:

$$C_e = T_{sw}^2 / (L\pi^2) \quad R_e = L / \left[T_{sw} \left(\frac{S_n + S_e}{S_n + S_f} - 0.5 \right) \right]$$

$$K_{ap} = -(t_{off} / 2L) R_e$$


Course Agenda

- The Buck Converter
- Control Schemes
- Introduction to Modeling
- The PWM Switch in Current-Mode Control
- Introduction to the Fast Analytical Techniques
- The Four Transfer Functions in CCM Current-Mode Control
- Compensation Strategy
- Prototype Measurements



The PWM Switch in Current-Mode Control

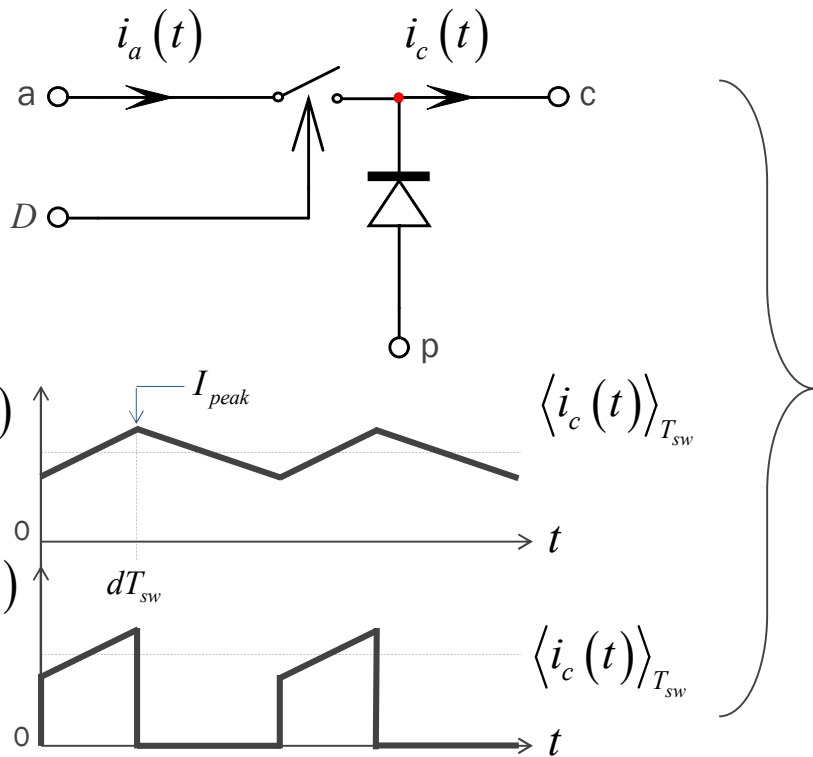
- Determine a time-continuous equation linking variables



$$\langle i_a(t) \rangle_{T_{sw}} = I_a = \frac{1}{T_{sw}} \int_0^{dT_{sw}} i_a(t) dt = D \langle i_c(t) \rangle_{T_{sw}} = DI_c$$

↓

$$I_a = DI_c$$


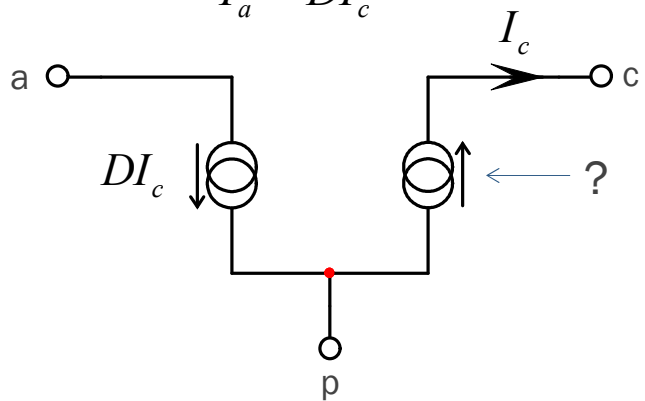


CCM



Accounting for Compensation Ramp Effects

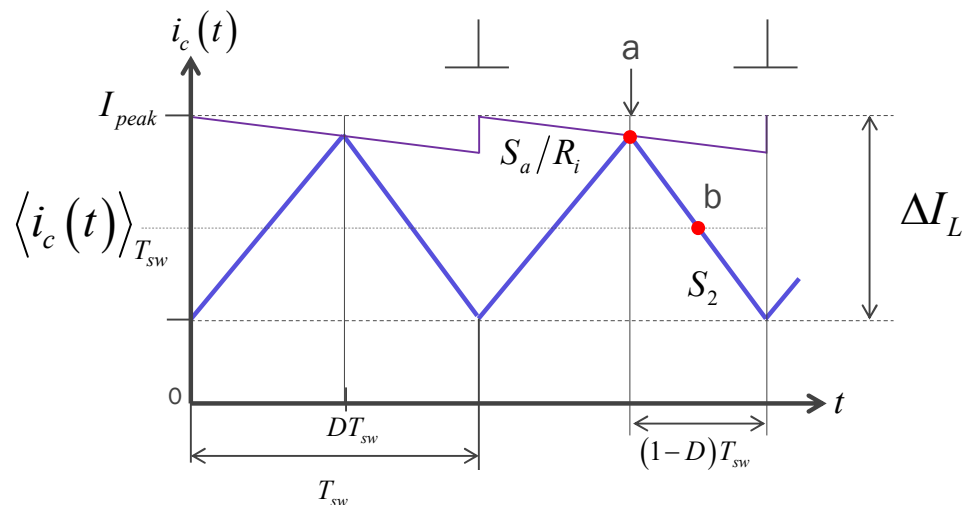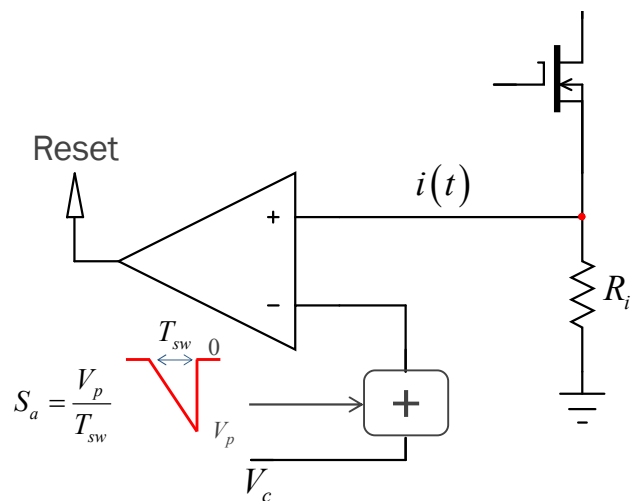- The compensation ramp reduces the effective peak current




- Current at point **b** is that of **a** minus half the inductor ripple

$$\langle i_c(t) \rangle_{T_{sw}} = \left(\frac{V_c}{R_i} - \frac{S_a}{R_i} DT_{sw} \right) - \frac{S_2 D' T_{sw}}{2}$$

Invariant Properties for the PWM Switch Model

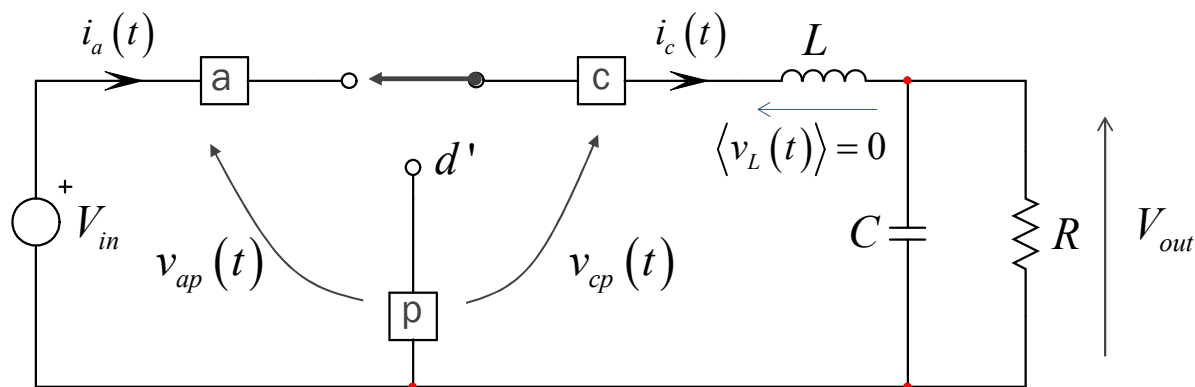- The inductor downslope S_2 in a buck is defined by $S_2 = V_{out} / L$



- The downslope depends on the output voltage V_{out} : $S_2 = \frac{V_{out}}{L}$
- The inductor average voltage is 0 V at steady-state: $V_{cp} = V_{out}$

Topology-dependent

Invariant expression

$$S_2 = \frac{V_{cp}}{L}$$


Associating Current Sources

- Update the previous equation to obtain the final definition

$$I_c = \frac{V_c}{R_i} - V_{cp} (1-D) \frac{T_{sw}}{2L} - \frac{S_a DT_{sw}}{R_i} \quad \xrightarrow{\text{Group 2}^{\text{nd}} \text{ and } 3^{\text{rd}} \text{ terms}} \quad I_\mu = V_{cp} (1-D) \frac{T_{sw}}{2L} + \frac{S_a DT_{sw}}{R_i}$$



Peak current setpoint Half inductor ripple Compensation ramp

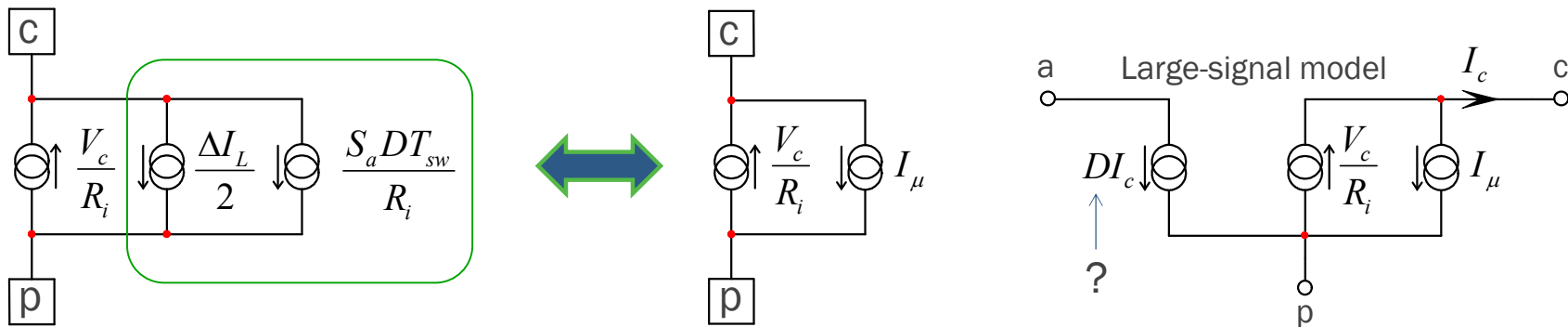- Inductor ripple and compensation ramp alter peak value



Predicting Sub-Harmonic Oscillations

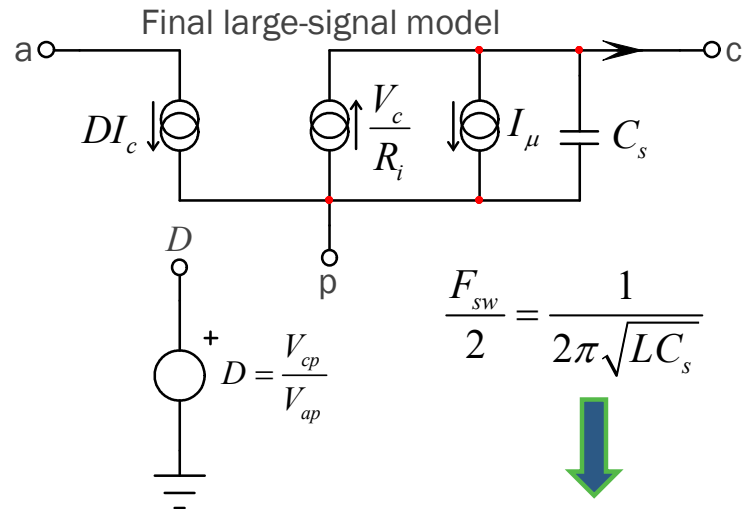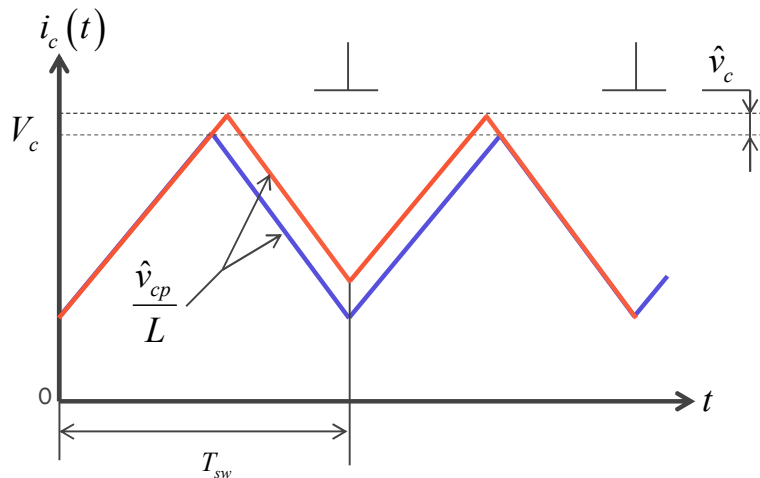- ❑ The model, as it is, cannot predict instabilities
- Let's observe a small-signal perturbation in v_c



$$\frac{F_{sw}}{2} = \frac{1}{2\pi\sqrt{LC_s}}$$



$$C_s = \frac{1}{L(F_{sw}\pi)^2}$$

- ❑ The off-slope does not change as \hat{v}_{cp} keeps constant
- ❑ This "memory" effect is modeled with a capacitor C_s



Small-Signal Model of the CM-PWM Switch

□ You can perturb...

$$I_c + \hat{i}_c \quad V_c + \hat{v}_c \quad V_{cp} + \hat{v}_{cp} \quad V_{ap} + \hat{v}_{ap}$$

$$\downarrow \quad \downarrow \quad \downarrow \quad \downarrow$$


$$I_c = \frac{V_c}{R_i} - V_{cp} (1-D) \frac{T_{sw}}{2L} - \frac{S_a}{R_i} DT_{sw}$$



...or apply partial differentiation

$$\hat{i}_c = \frac{\partial I_c}{\partial V_c} \hat{v}_c + \frac{\partial I_c}{\partial V_{ap}} \hat{v}_{ap} + \frac{\partial I_c}{\partial V_{cp}} \hat{v}_{cp}$$
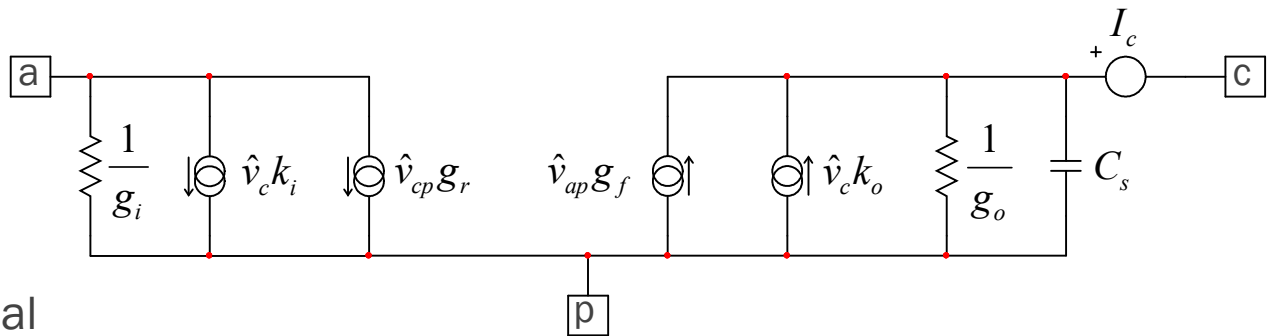
$$\hat{i}_a = \frac{\partial I_a}{\partial V_c} \hat{v}_c + \frac{\partial I_a}{\partial V_{ap}} \hat{v}_{ap} + \frac{\partial I_a}{\partial V_{cp}} \hat{v}_{cp}$$



$$g_o = \frac{T_{sw}}{L} \left(D' \frac{S_a}{S_n} + \frac{1}{2} - D \right) \quad k_o = \frac{1}{R_i} \quad g_f = Dg_o - \frac{DD'T_{sw}}{2L}$$



$$g_i = D \left(g_f - \frac{I_c}{V_{ap}} \right) \quad k_i = \frac{D}{R_i} \quad g_r = \frac{I_c}{V_{ap}} - g_o D$$

□ Laplace Transform now holds on this linear network



The PWM Switch Model in a COT Converter

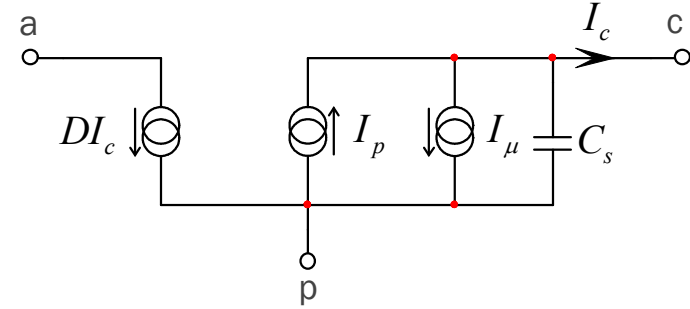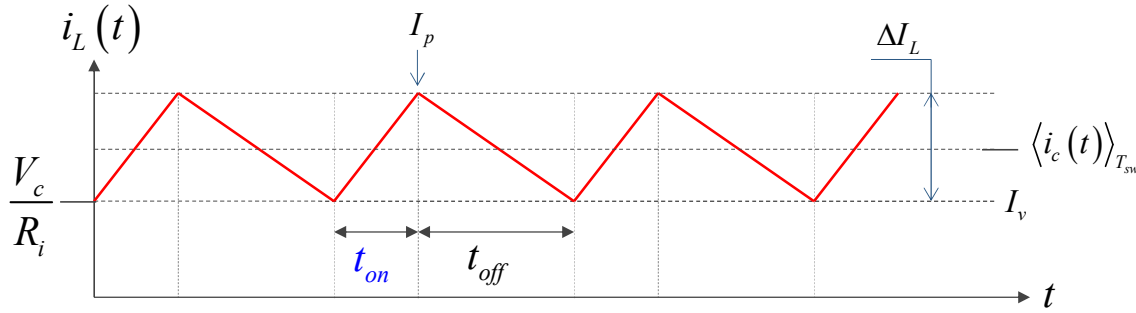□ In a constant on-time circuit, the loop controls the *valley* current



Same structure as CM model

$$I_p = \frac{V_c}{R_i} + \frac{V_{ac}}{L} t_{on} \quad I_c = I_p - \frac{\Delta I_L}{2} = \left(\frac{V_c}{R_i} + \frac{V_{ac}}{L} t_{on} \right) - \frac{V_{cp}}{2L} \left(1 - \frac{t_{on}}{T_{sw}} \right) T_{sw}$$

Valley current

$$\frac{V_c}{R_i} = I_p - S_{off} t_{off} = I_p - \frac{V_{cp}}{L} t_{off} \quad t_{off} = \left(I_p - \frac{V_c}{R_i} \right) \frac{L}{V_{cp}} \rightarrow t_{off} = \left(\frac{V_c}{R_i} + \frac{V_{ac}}{L} t_{on} - \frac{V_c}{R_i} \right) \frac{L}{V_{cp}} = \frac{V_{ac}}{V_{cp}} t_{on}$$

Fixed value


$$I_\mu = \frac{V_{cp}}{2L} \left(1 - \frac{t_{on}}{T_{sw}} \right) T_{sw} \quad T_{sw} = t_{on} + t_{off} \quad D = \frac{t_{on}}{T_{sw}}$$

Testing the COT Model in Transient Analysis

□ We compare the cycle-by-cycle response with that of the averaged model


Parameters

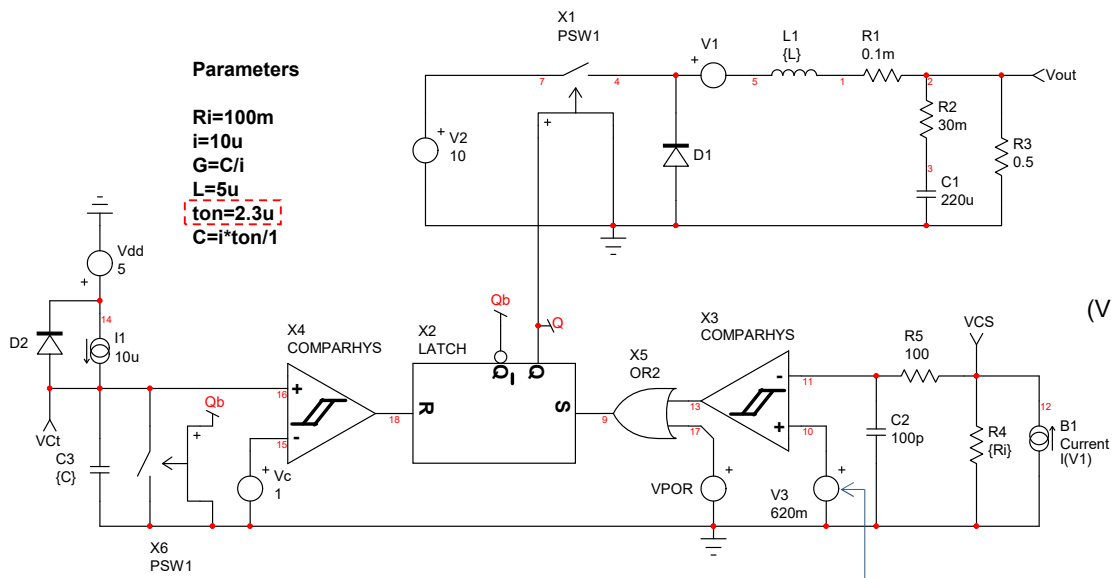$R_i = 100m$
 $i = 10u$
 $G = C/i$
 $L = 5u$
 $t_{on} = 2.3u$
 $C = i * t_{on} / 1$



Keeps the switch closed for a fixed t_{on} .


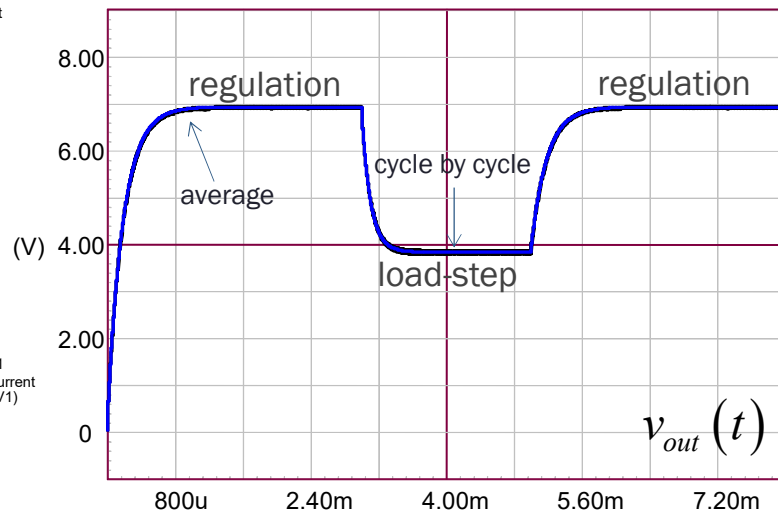
Sets the latch back high when valley current set by V_c is reached.



Transient responses are identical

Small-Signal Response: SPICE versus SIMPLIS®

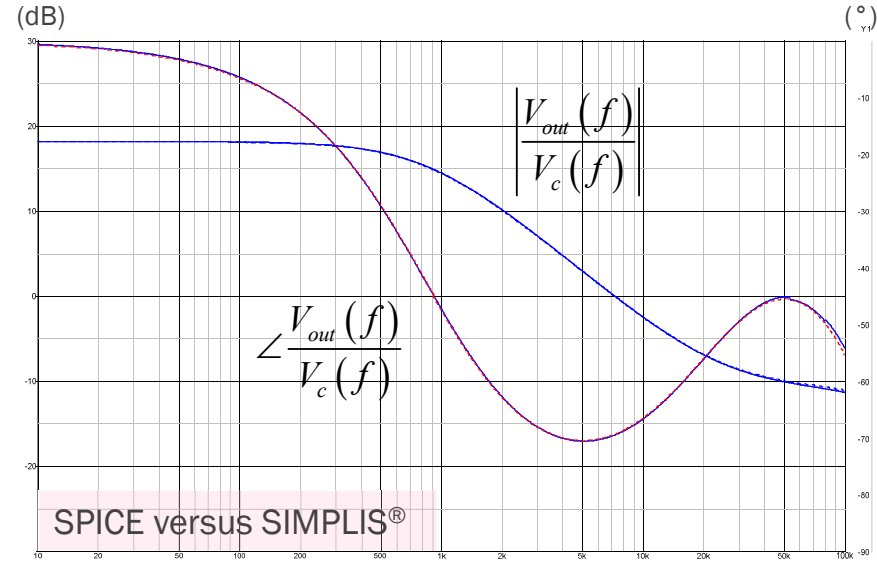
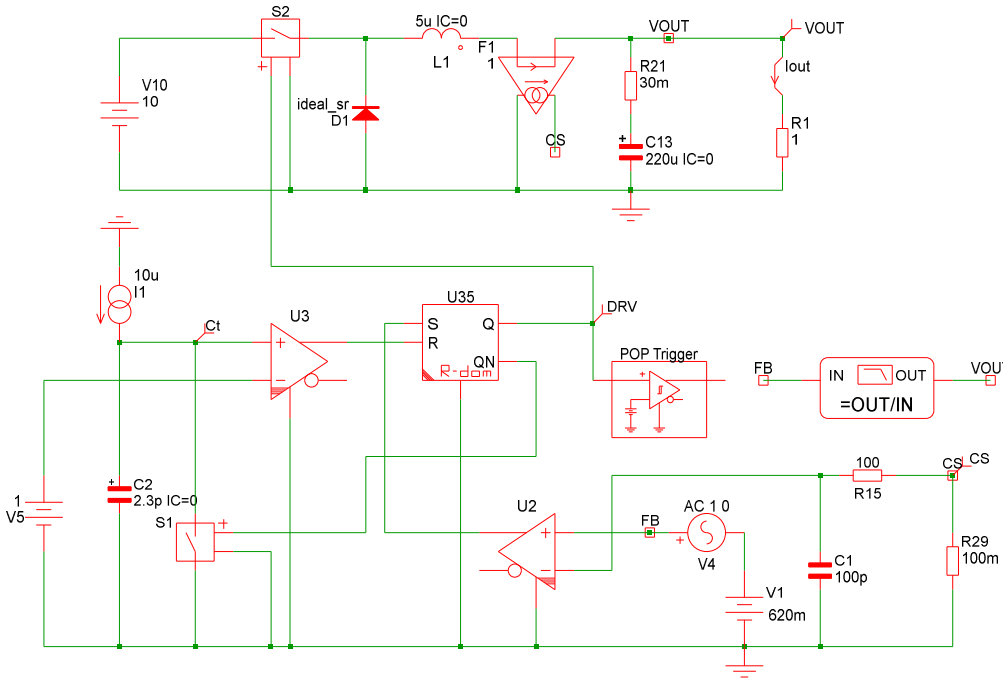
□ SIMPLIS lets us obtain the dynamic response in a few seconds



Dynamic responses are identical

The PWM Switch Model in a FOT Converter

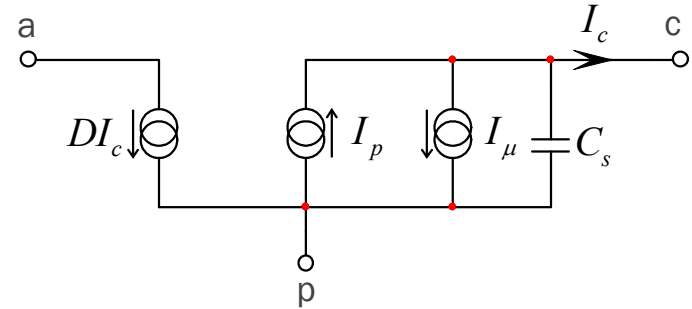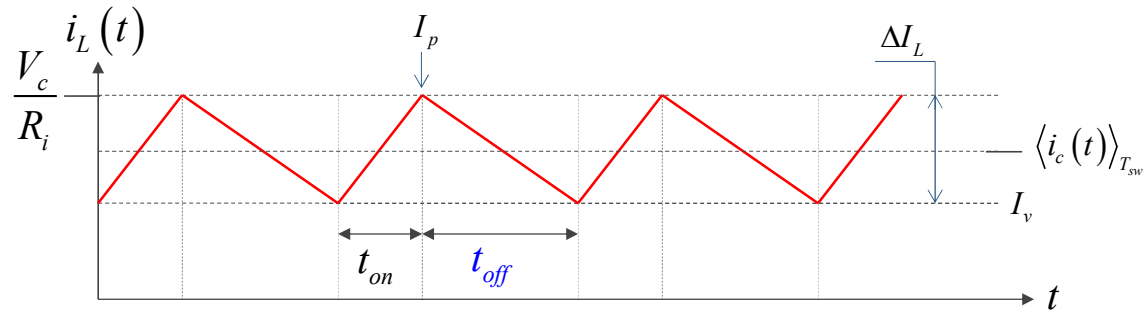
□ In a fixed-off-time circuit, the loop controls the *peak* current



Same structure as CM model

$$I_c = \frac{V_c}{R_i} \frac{\Delta L_L}{2} = \frac{V_c}{R_i} - \frac{V_{ac}}{2L} t_{on} \longrightarrow t_{on} = \frac{\left(\frac{V_c}{R_i} - I_c\right) 2L}{V_{ac}} \quad t_{off} \text{ is fixed}$$
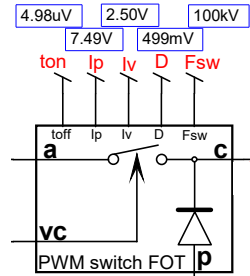
$$I_\mu = \frac{V_{cp}}{2L} t_{off} \quad T_{sw} = t_{on} + t_{off} \quad I_C = \frac{V_c}{R_i} - I_\mu \quad D = \frac{t_{on}}{T_{sw}}$$



Encapsulated version




Comparing the Cycle-by-Cycle Transient Waveforms

□ We compare the cycle-by-cycle response with that of the averaged model


Parameters

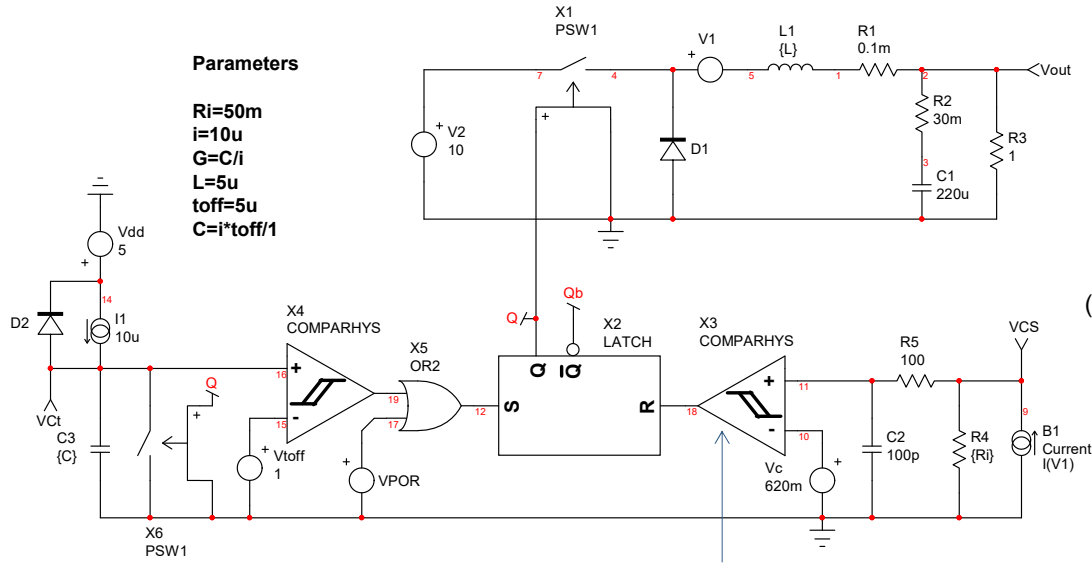$R_i=50m$
 $i=10u$
 $G=C/i$
 $L=5u$
 $t_{off}=5u$
 $C=i*t_{off}/1$



Keeps the switch open for a fixed t_{on} .

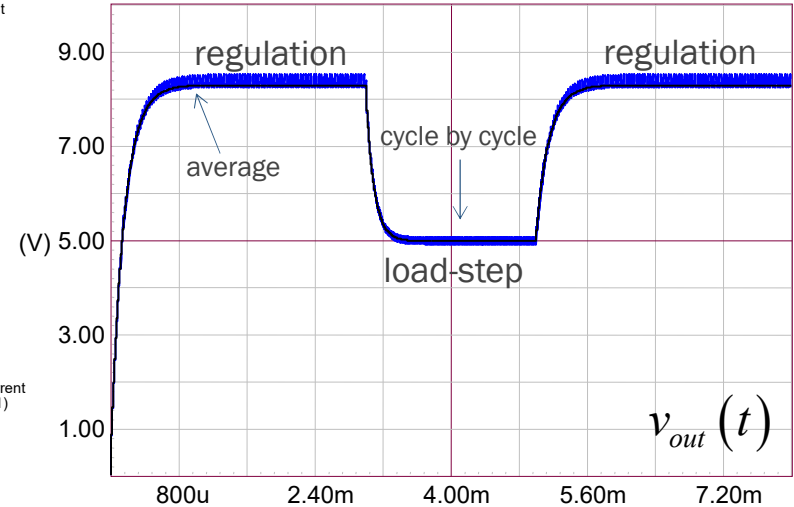
Resets the latch when the peak current set by V_c is reached.



Transient responses are identical


Small-Signal Response: SPICE versus SIMPLIS®

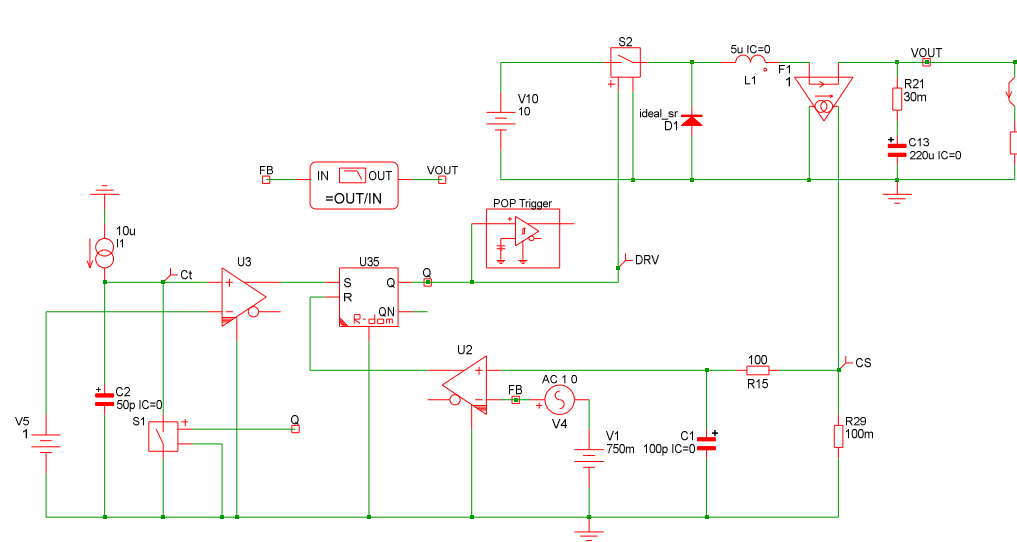□ SIMPLIS® easily simulates the fixed-off-time converter



Fixed-off-time generator

Peak-current control



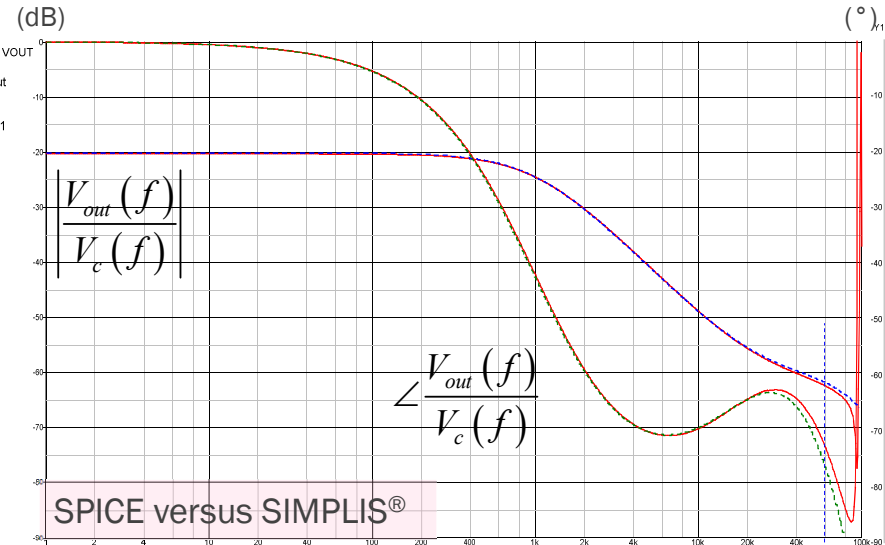


SPICE versus SIMPLIS®

Dynamic responses are very close

Quasi-Square-Wave Converters

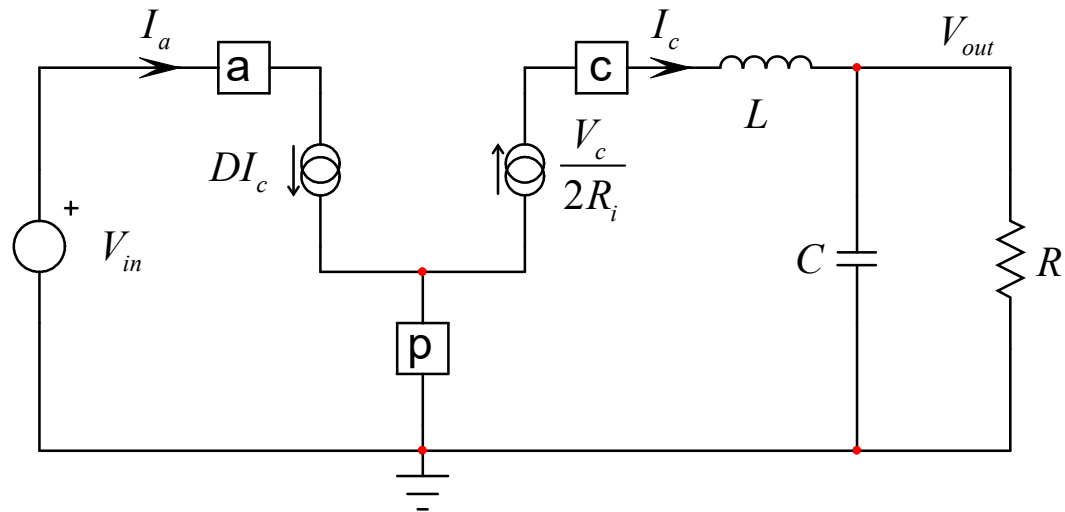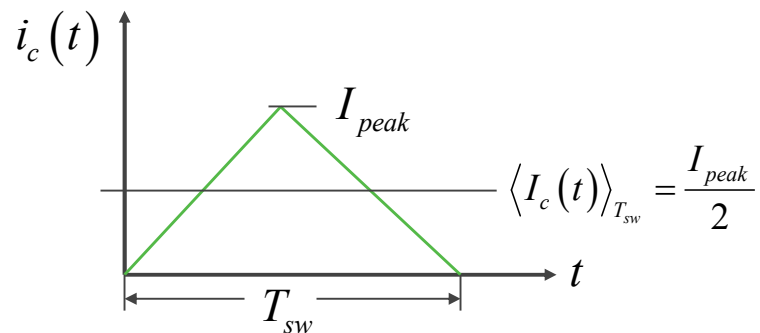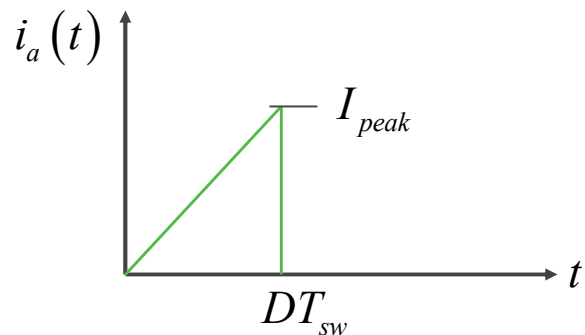□ The waveform average values do not include the deadtime



Derive operating points and dc transfer function


C. Basso, *Small-Signal Modeling of Power Converters*, Professional Education APEC seminar 2013.

From Large- to Small-Signal Models

□ Partial differentiation will give small-signal coefficients

$$I_c = f(V_c) \longrightarrow \hat{i}_c = \frac{\partial I_c(V_c)}{\partial V_c} \hat{v}_c \quad \hat{i}_c = \hat{v}_c \left(\frac{1}{2R_i} \right) = \hat{v}_c k_c \quad k_c = \frac{1}{2R_i}$$

$$\hat{i}_a = \left. \frac{\partial I_a(V_{cp}, V_{ac}, I_c)}{\partial V_{cp}} \right|_{I_c, V_{ac}} \hat{v}_{cp} + \left. \frac{\partial I_a(V_{cp}, V_{ac}, I_c)}{\partial I_c} \right|_{V_{cp}, V_{ac}} \hat{i}_c + \left. \frac{\partial I_a(V_{cp}, V_{ac}, I_c)}{\partial V_{ac}} \right|_{I_c, V_{cp}} \hat{v}_{ac} \longrightarrow \hat{i}_a = \hat{v}_{cp} k_{cp} + k_{ic} \hat{i}_c - \hat{v}_{ac} k_{ac}$$

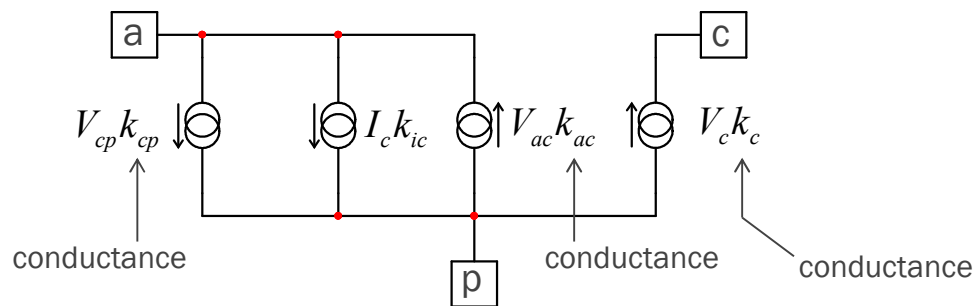

Small-signal model

$$k_{cp} = \frac{I_{c0} V_{ac0}}{(V_{ac0} + V_{cp0})^2}$$


$$k_{ic} = \frac{V_{cp0}}{V_{cp0} + V_{ac0}}$$

$$k_{ac} = \frac{V_{cp0} I_{c0}}{(V_{ac0} + V_{cp0})^2}$$



Static coefficients

Cycle-by-Cycle and Averaged Responses

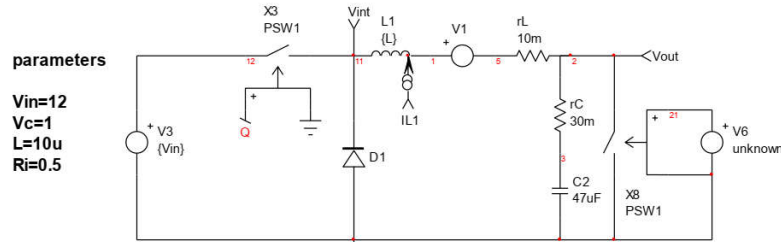- ❑ The cycle-by-cycle circuit requires an extra winding to detect core reset





Demagnetization detection

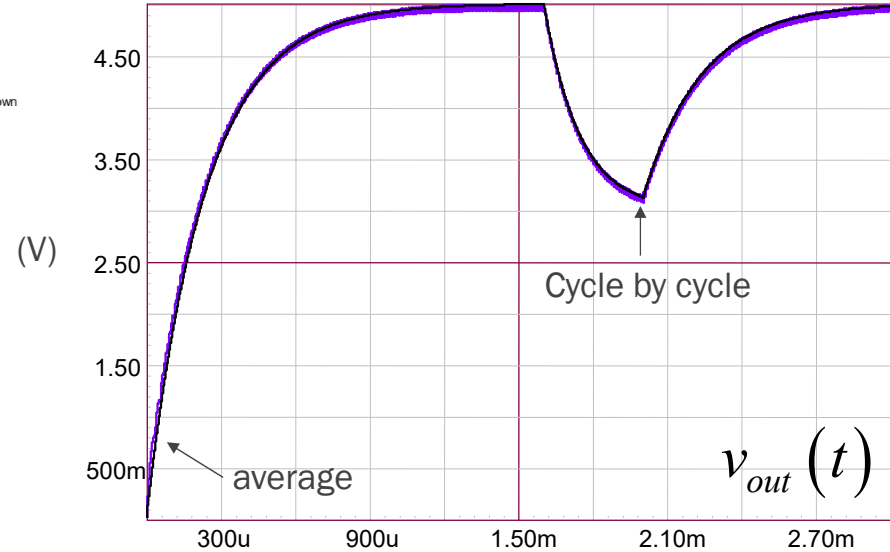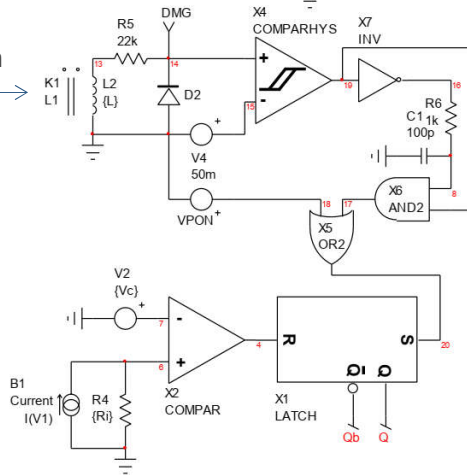


Transient responses are identical

SIMPLIS® Delivers the Full Picture: Transient and Ac

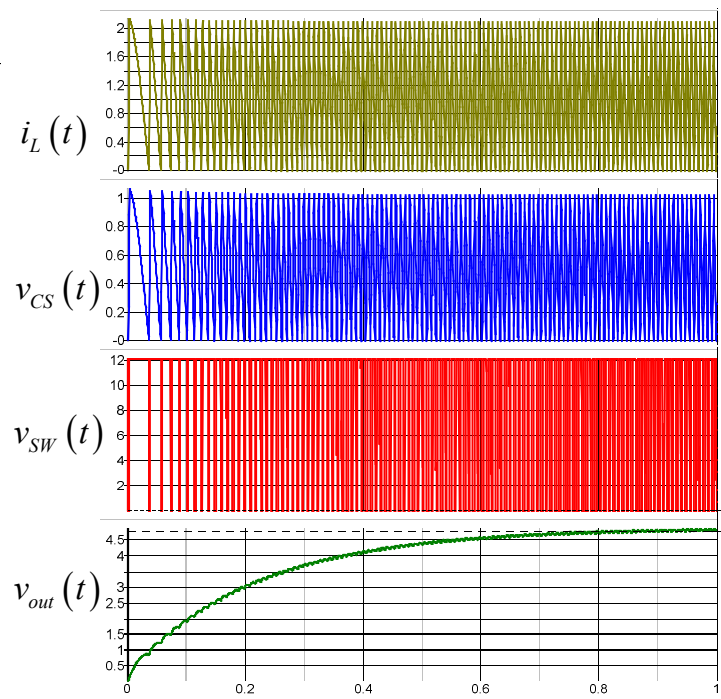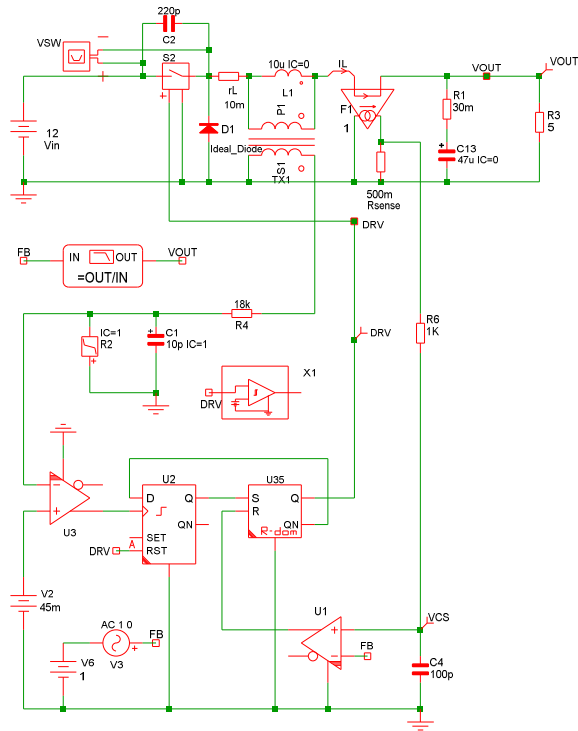□ The switching frequency varies with line and load conditions



Cycle-by-cycle results

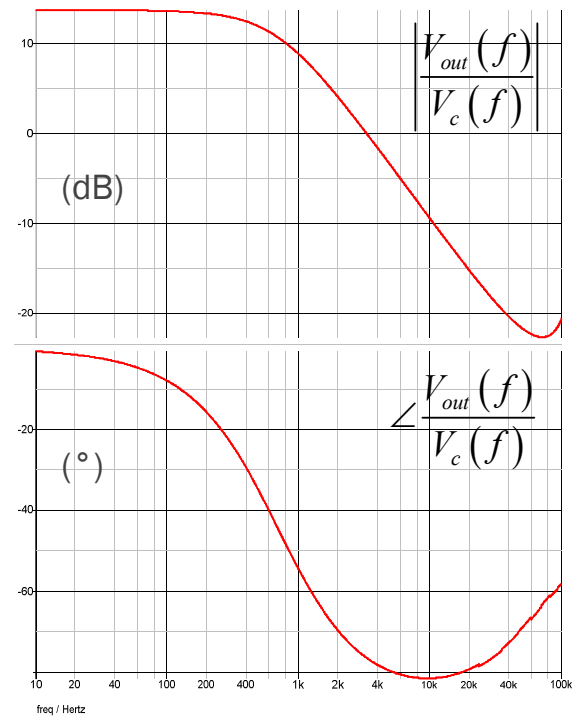

1st-order dynamic response

Course Agenda

- The Buck Converter
- Control Schemes
- Introduction to Modeling
- The PWM Switch in Current-Mode Control
- Introduction to the Fast Analytical Techniques
- The Four Transfer Functions in CCM Current-Mode Control
- Compensation Strategy
- Prototype Measurements



The Fastest Way to Determine a Transfer Function

- We can use the Fast Analytical Circuits Techniques or FACTS


$$\frac{V_{out}(s)}{D(s)} = H_0 \frac{1 + a_1s + a_2s^2}{1 + b_1s + b_2s^2}$$

Same dimension

$$\left. \begin{array}{l} a_1 \text{ and } b_1 \text{ [s]} \\ a_2 \text{ and } b_2 \text{ [s}^2\text{]} \end{array} \right\} \begin{array}{l} a_1 = \tau_{1N} + \tau_{2N} \\ a_2 = \tau_{1N}\tau_{2N} \end{array} \quad \begin{array}{l} b_1 = \tau_1 + \tau_2 \\ b_2 = \tau_1\tau_2 \end{array}$$

Nulled response Zeroed excitation

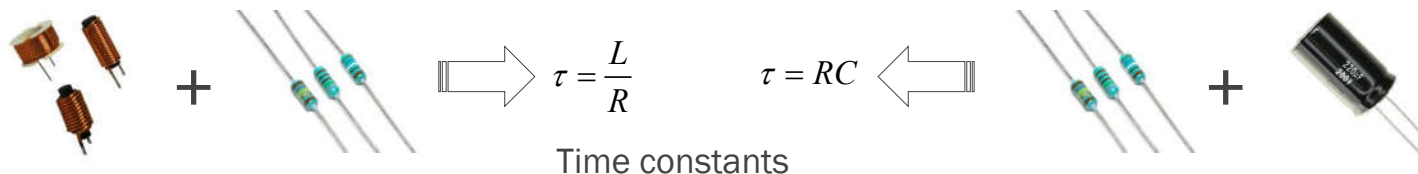- Energy-storing elements are combined with resistances



- Capacitors and inductors behave differently for $s = 0$ and $s \rightarrow \infty$






Determine the Dc Gain

□ Look at the circuit for $s = 0$

- Capacitor are open circuited
- Inductors are short circuited

} SPICE operating point calculation

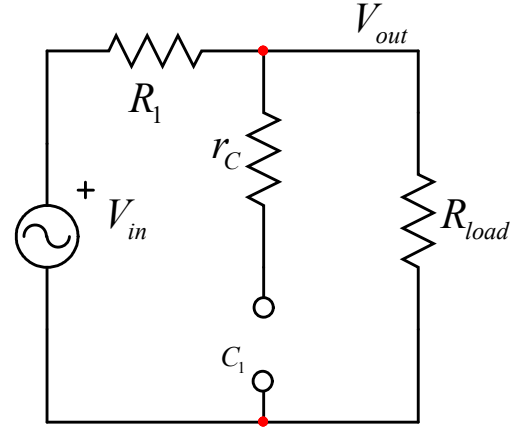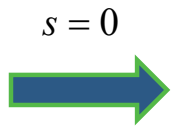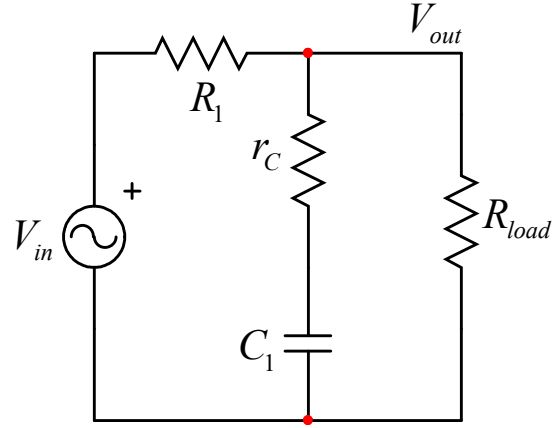


□ Determine the gain in this condition:
$$H_0 = \frac{R_{load}}{R_{load} + R_1}$$

Determine the Time Constant

- Look at the resistance driving the energy-storing element

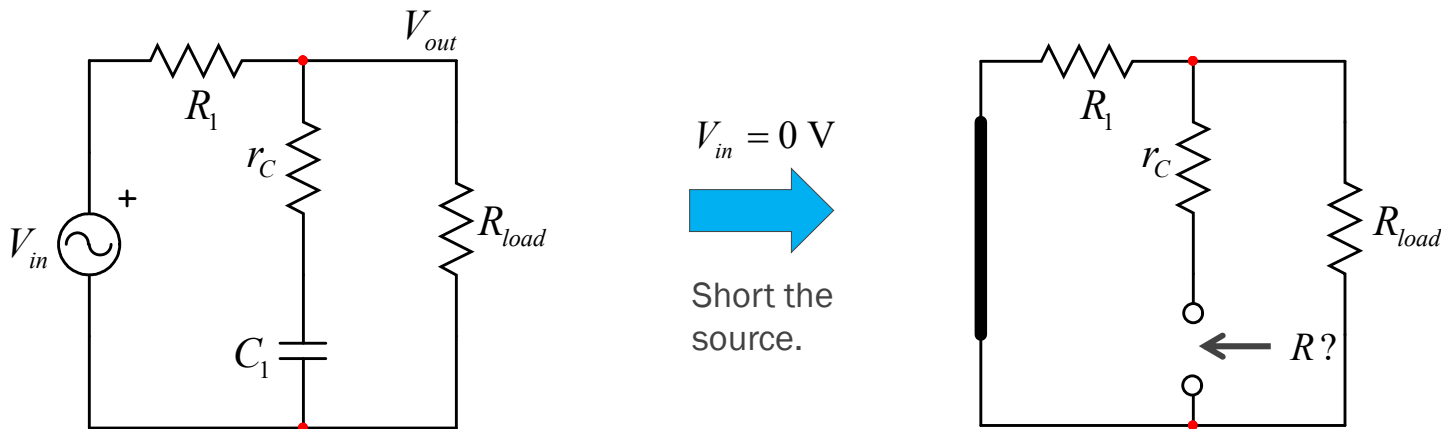1. When the excitation is turned off, $V_{in} = 0 \text{ V}$




- Remove the capacitor and “look” into its terminals

➤ The first time constant is $\tau_1 = (r_c + R_1 \parallel R_{load}) C_1$


Null the Output to Unveil the Zero Location

□ Bring the excitation back

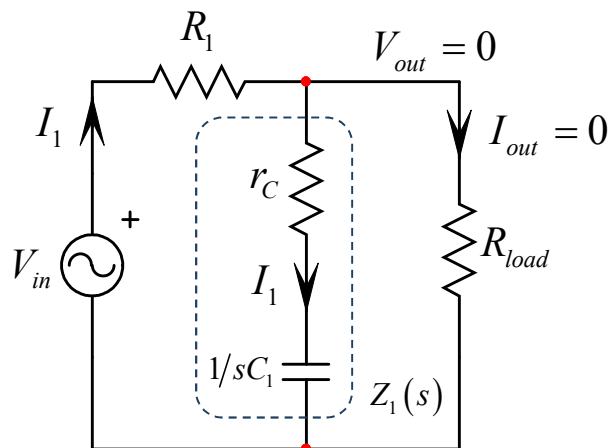
2. Check the condition bringing $V_{out} = 0$ V



$V_{out} = 0$ V

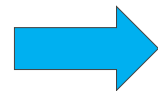

Transformed short circuit

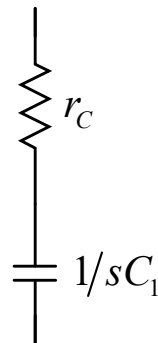

$$Z_1(s) = r_C + \frac{1}{sC_1} = 0$$



$$s_z = -\frac{1}{r_C C_1}$$



$$\omega_z = \frac{1}{r_C C_1}$$

□ You can also remove the capacitor and look into its terminals

➤ The second time constant in the null condition is $\tau_2 = r_C C_1$

Combine the Time Constants in a Low-Entropy Form

- By combining time constants, we have

$$H(s) = H_0 \frac{1 + s\tau_2}{1 + s\tau_1} = \frac{R_{load}}{R_{load} + R_1} \frac{1 + sr_C C_1}{1 + s(r_C + R_1 \parallel R_{load}) C_1}$$



- Rearrange the equation to unveil a pole and a zero

$$H(s) = H_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \left. \begin{array}{l} \omega_z = \frac{1}{r_C C_1} \\ \omega_p = \frac{1}{(r_C + R_1 \parallel R_{load}) C_1} \end{array} \right\} \quad H_0 = \frac{R_{load}}{R_{load} + R_1}$$

- This is a *low-entropy* expression

Second-Order Circuits: New Notation

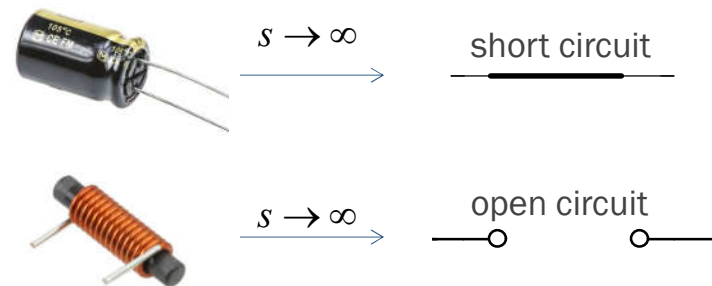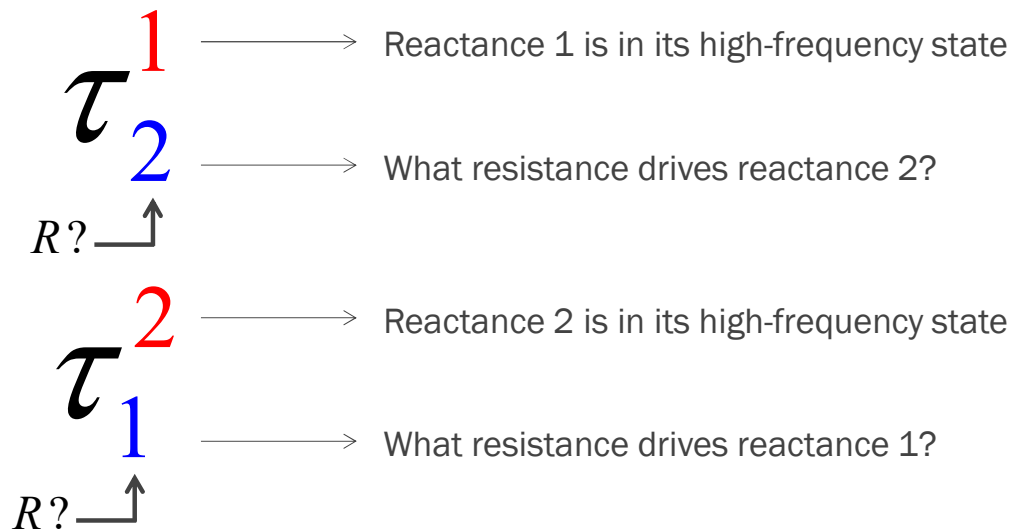- Set one reactance into its high-frequency state




- There is redundancy: pick the simplest result

$$b_2 = \tau_1 \tau_2^1 \iff b_2 = \tau_2 \tau_1^2$$

A Simple Low-Pass LC Filter

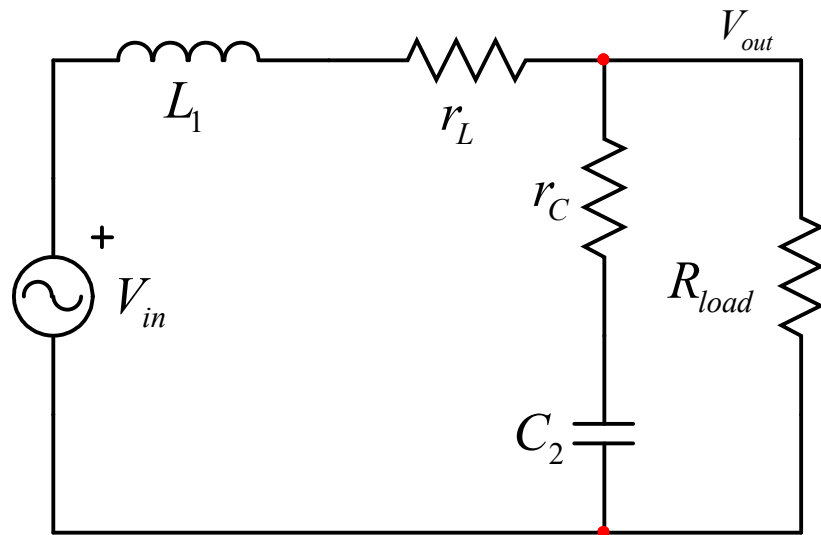- There are two energy-storing elements: 2nd-order filter



- What transfer function links V_{out} to V_{in} ?

Set s to zero: short inductors, open caps.

Determine H_0

Reduce excitation to 0 V: short V_{in}

Find 1st-order time constants with L_1 and C_2

Find 2nd-order time constants with L_1 and C_2


Null the output and find zero(es)

Assemble results in a low-entropy form

$$H(s) = H_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

Start with the Dc Gain

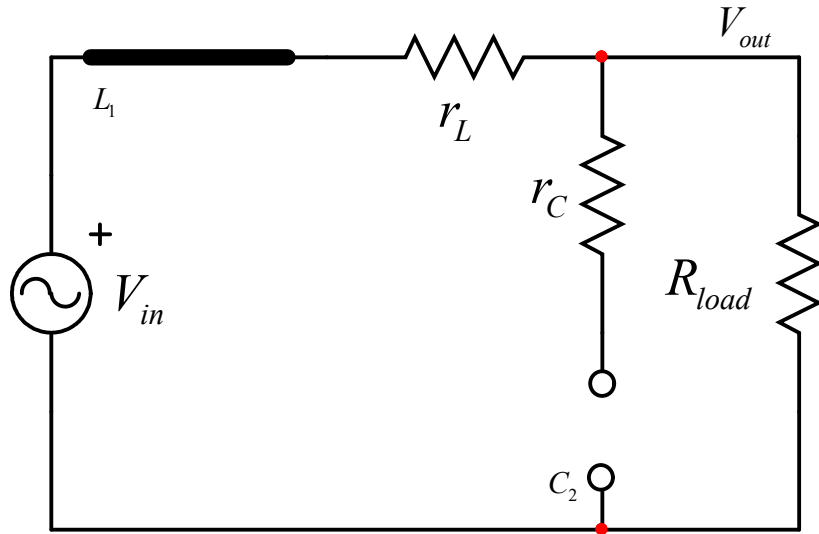- Short the inductor and open the capacitor



$s = 0$



short circuit



$s = 0$



open circuit




$$H_0 = \frac{R_{load}}{R_{load} + r_L}$$


- This expression is obtained by inspecting the circuit: no algebra

Reduce the Excitation to 0 V: Short V_{in}

□ Determine the 1st-order time constants

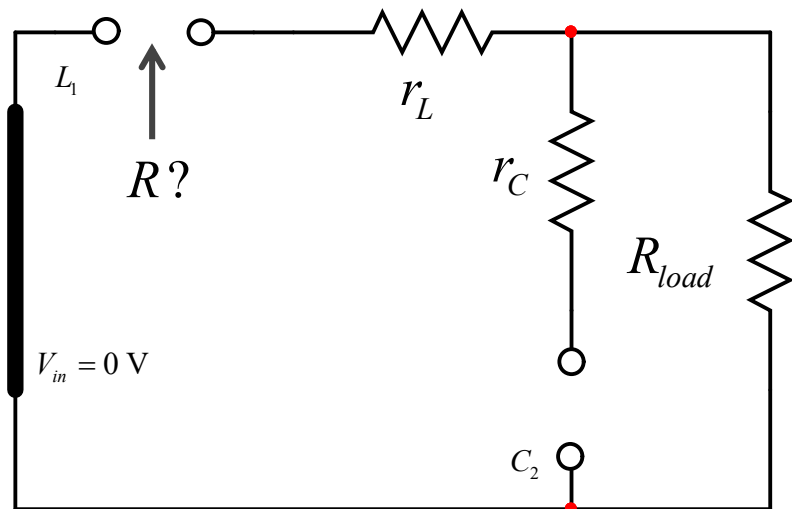

$$\tau_1 = \frac{L_1}{R_{load} + r_L}$$


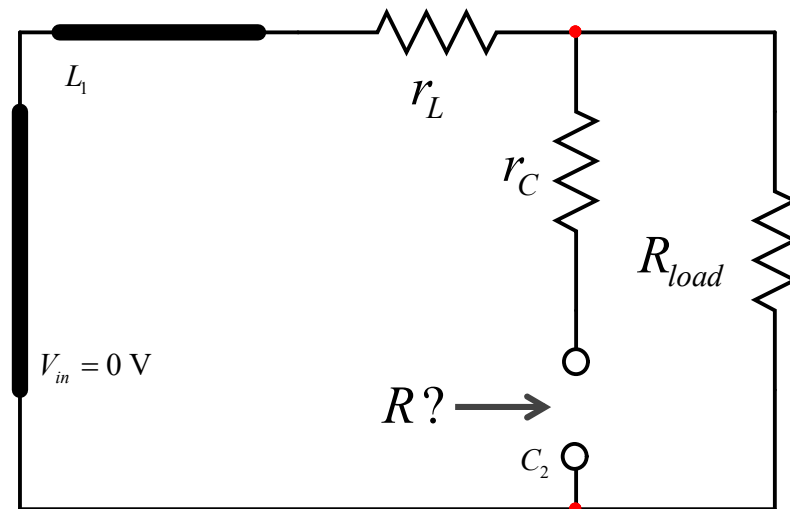


$$\tau_2 = (r_C + r_L \parallel R_{load}) C_2$$

↑
Don't expand!


Pick the Simplest Time Constant Combination

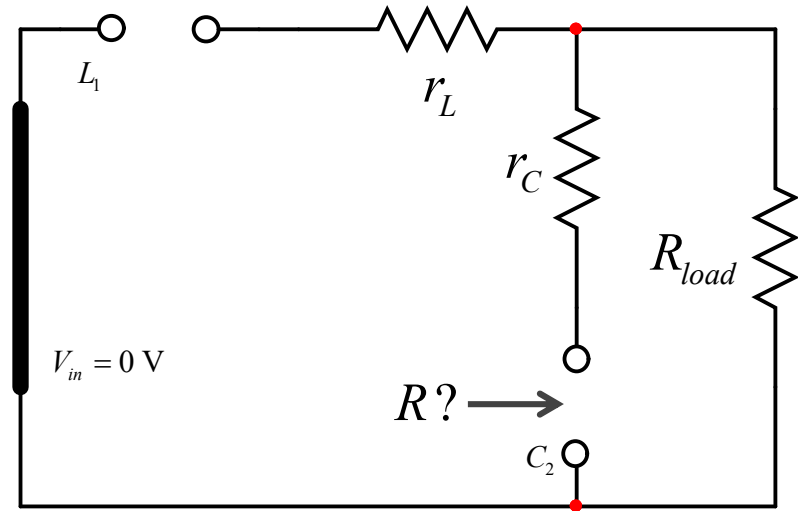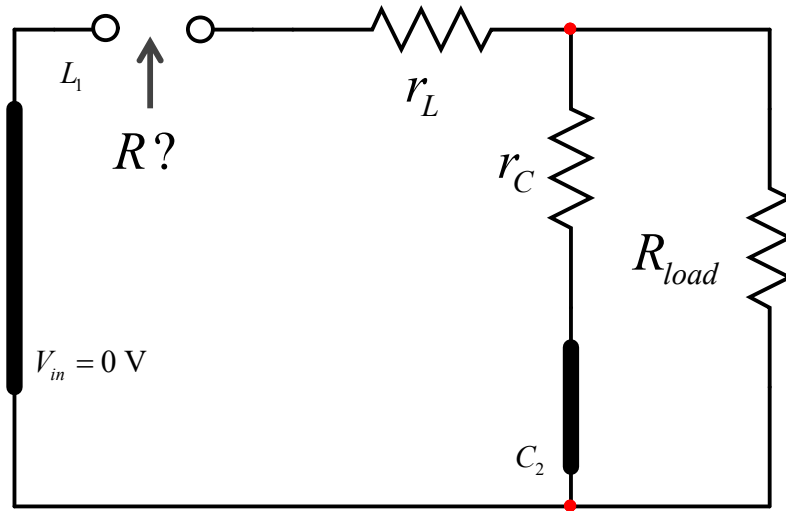- Set one of the energy-storing elements in its high-frequency state



$$\tau_1^2 = \frac{L_1}{r_L + r_C \parallel R_{load}}$$

$$b_2 = \tau_2 \tau_1^2$$

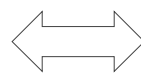

$$b_2 = \tau_1 \tau_2^1$$


$$\tau_2^1 = C_2 (r_C + R_{load})$$

- You have to select the simplest combination between the two options



Determine the Zero Instantaneously

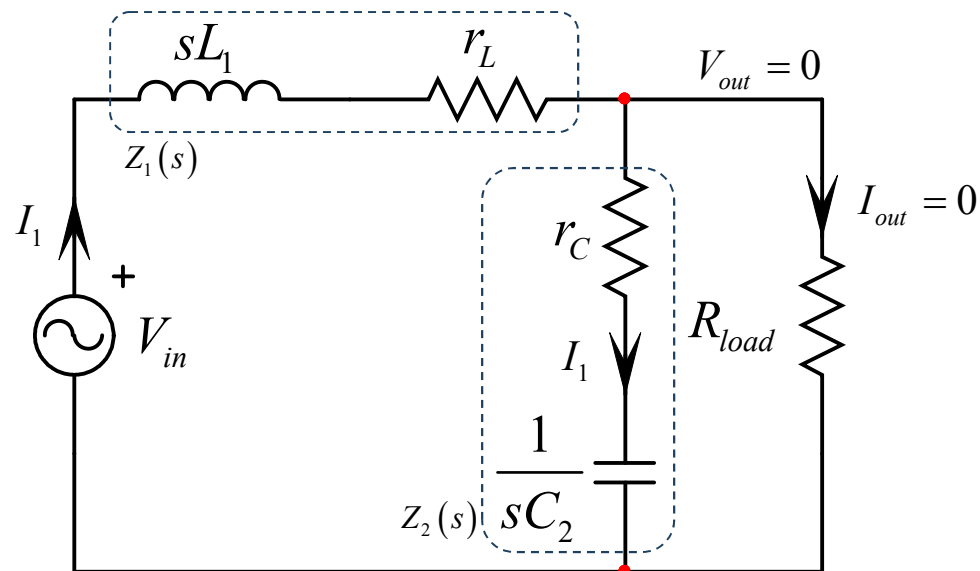- What would prevent the stimulus (V_{in}) from forming a response (V_{out})?



- There is one single zero contributed by C_2

$$Z_1(s) = sL_1 + r_L \rightarrow \infty$$

Only for s approaching infinity

$$Z_2(s) = \frac{1}{sC_2} + r_C = 0$$

$$s_z = -\frac{1}{r_C C_1}$$



$$\omega_z = \frac{1}{r_C C_1}$$

Assemble all Time Constants to form $H(s)$

- The denominator is obtained by combining the time constants

$$D(s) = 1 + b_1s + b_2s^2 = 1 + s \left[\frac{L_1}{R_{load} + r_L} + (r_C + r_L \parallel R_{load}) C_2 \right] + L_1 C_2 \frac{r_C + R_{load}}{R_{load} + r_L} \cdot s^2$$

- The numerator features one zero only

$$N(s) = 1 + sr_C C_2$$

- Read gains, poles and zero with the *low-entropy* format

$$H(s) = H_0 \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2} \left\{ \begin{array}{l} \omega_z = \frac{1}{r_C C_2} \quad \omega_0 = \frac{1}{\sqrt{L_1 C_2}} \sqrt{\frac{r_L + R_{load}}{r_C + R_{load}}} \quad H_0 = \frac{R_{load}}{r_L + R_{load}} \\ Q = \frac{r_L + R_{load}}{L_1 + C_2 [r_C r_L + R_{load} (r_C + r_L)]} \frac{1}{\omega_0} \end{array} \right.$$

R. D. Middlebrook, *Methods of Design-Oriented Analysis: Low Entropy Expressions*, New Approaches to Undergraduate Education, July 1992



Check Results and Easily Run Corrections if needed

□ Verify the expression in a Mathcad® sheet and compare responses

$$r_L := 0.1\Omega \quad r_C := 1\Omega \quad C_2 := 1\mu\text{F} \quad L_1 := 20\mu\text{H} \quad R_{\text{load}} := 5\Omega \quad \|(x,y) := \frac{x \cdot y}{x + y}$$

$$H_0 := \frac{R_{\text{load}}}{r_L + R_{\text{load}}} = 0.98$$

$$\tau_1 := \frac{L_1}{r_L + R_{\text{load}}} = 3.922\mu\text{s} \quad \tau_2 := C_2 \cdot (r_L \parallel R_{\text{load}} + r_C) = 1.098 \times 10^3 \cdot \text{ns} \quad b_1 := \tau_1 + \tau_2 = 5.02\mu\text{s}$$

$$\tau_{12} := C_2 \cdot (r_C + R_{\text{load}}) = 6\mu\text{s} \quad \tau_{21} := \frac{L_1}{r_L + R_{\text{load}} \parallel r_C} = 21.429\mu\text{s} \quad b_2 := \tau_2 \cdot \tau_{21} = 23.529\mu\text{s}^2$$


$$N_1(s) := 1 + s \cdot r_C \cdot C_2 \quad D_1(s) := 1 + b_1 \cdot s + b_2 \cdot s^2 \quad H_1(s) := H_0 \cdot \frac{N_1(s)}{D_1(s)}$$

$$\omega_z := \frac{1}{r_C \cdot C_2} \quad \omega_0 := \frac{1}{\sqrt{L_1 \cdot C_2}} \cdot \sqrt{\frac{r_L + R_{\text{load}}}{r_C + R_{\text{load}}}} \quad Q := \frac{L_1 \cdot C_2 \cdot \omega_0 \cdot (r_C + R_{\text{load}})}{L_1 + C_2 \cdot (r_L \cdot r_C + r_L \cdot R_{\text{load}} + r_C \cdot R_{\text{load}})}$$

$$H_2(s) := H_0 \cdot \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}$$

$$Z_1(s) := s \cdot L_1 + r_L \quad Z_2(s) := \left(\frac{1}{s \cdot C_2} + r_C\right) \parallel R_{\text{load}}$$
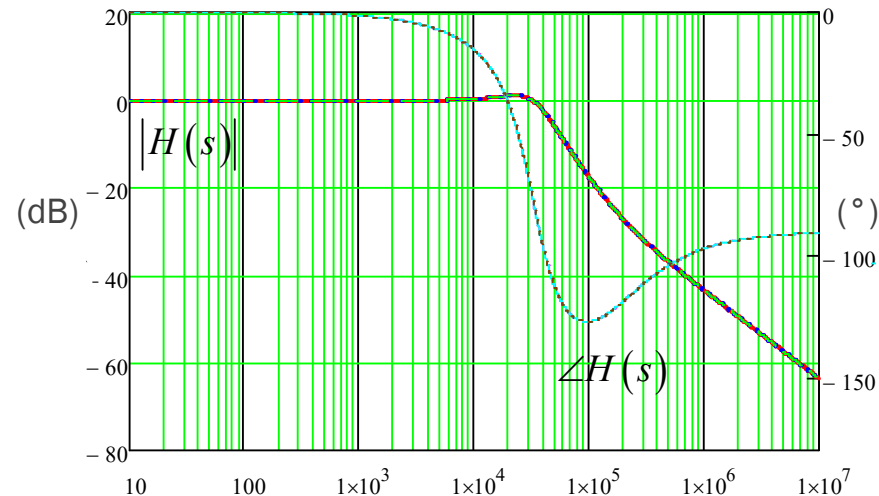
$$H_{\text{ref}}(s) := \frac{Z_2(s)}{Z_2(s) + Z_1(s)} \quad \text{Brute-force expression}$$



□ If a deviation exists, fix the guilty sketch and don't restart from scratch



Third-Order Transfer Function: more Choice!

- Combine the three low-frequency times constants together

τ_{13}

→ Reactance 1 and 3 are set in their high-frequency state

τ_2

→ What resistance drives reactance 2?

$R? \uparrow$

τ_{23}

→ Reactance 2 and 3 are set in their high-frequency state


τ_1

→ What resistance drives reactance 1?

$R? \uparrow$


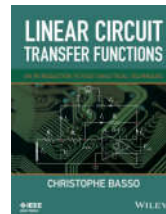
$$D(s) = 1 + s(\tau_1 + \tau_2 + \tau_3) + s^2(\tau_1\tau_2 + \tau_1\tau_3 + \tau_2\tau_3) + s^3\tau_1\tau_2\tau_3$$



C. Basso, *Linear Circuits Transfer Functions: An Introduction to Fast Analytical Techniques*, Wiley 2016



Course Agenda

- The Buck Converter
- Control Schemes
- Introduction to Modeling
- The PWM Switch in Current-Mode Control
- Introduction to the Fast Analytical Techniques
- The Four Transfer Functions in CCM Current-Mode Control
- Compensation Strategy
- Prototype Measurements



The Four Transfer Functions of the CM Buck Converter

- There are four open-loop transfer functions of interest:

$$\left. \frac{V_{out}(s)}{V_c(s)} \right|_{\hat{v}_{in}=0}$$

Control-to-output with ac-silent input source

“How does a voltage perturbation on v_c propagate to v_{out} ?”

$$\left. \frac{V_{out}(s)}{V_{in}(s)} \right|_{\hat{v}_c=0}$$

Input-to-output with static control V_c

“How does a voltage perturbation on v_{in} propagate to v_{out} ?”

$$\left. \frac{V_{out}(s)}{I_{out}(s)} \right|_{\hat{v}_{in}=\hat{v}_c=0}$$





Output impedance with static control V_c

“How does a current perturbation on i_{out} propagate to v_{out} ?”

$$\left. \frac{V_{in}(s)}{I_{in}(s)} \right|_{\hat{v}_c=0}$$


Input impedance with static control V_c

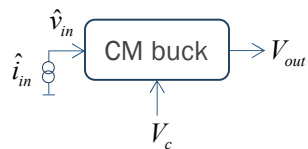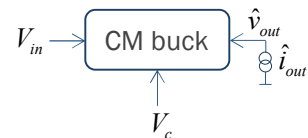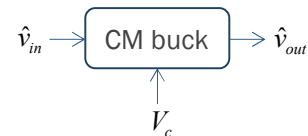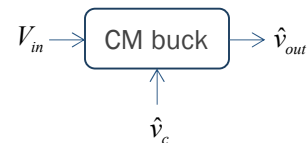“How does a current perturbation on i_{in} propagate to v_{in} ?”



Control-to-Output Transfer Function

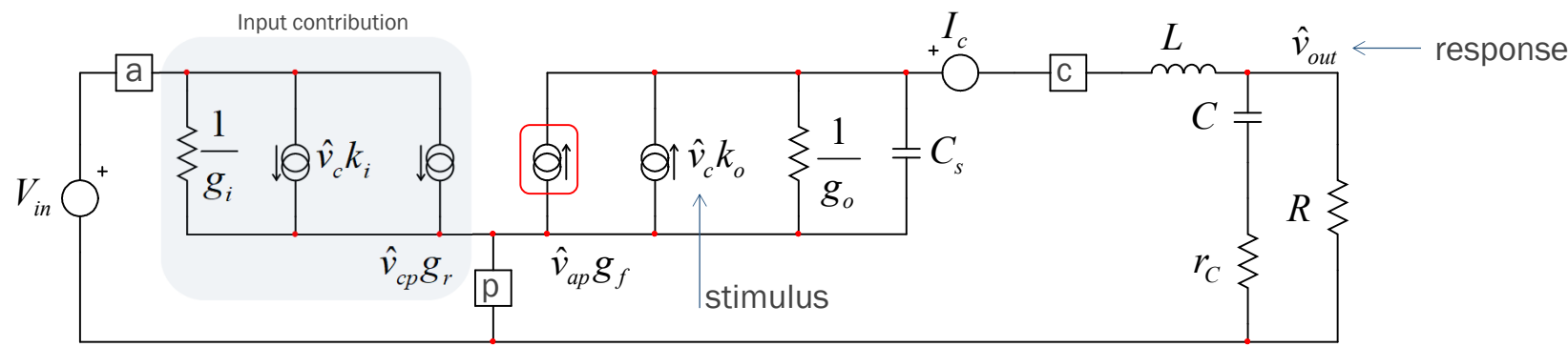- Install the small-signal CM-PWM switch in the buck converter



- We want the control-to-output function, the input source is ac-silent:

$$\hat{v}_{in} = 0 \longrightarrow \hat{v}_{ap} g_f = 0$$


- The input contribution can also disappear, no interest in Z_{in} for now

Control to output



Simplify and Rearrange the Circuit

□ The circuit now looks simpler to study

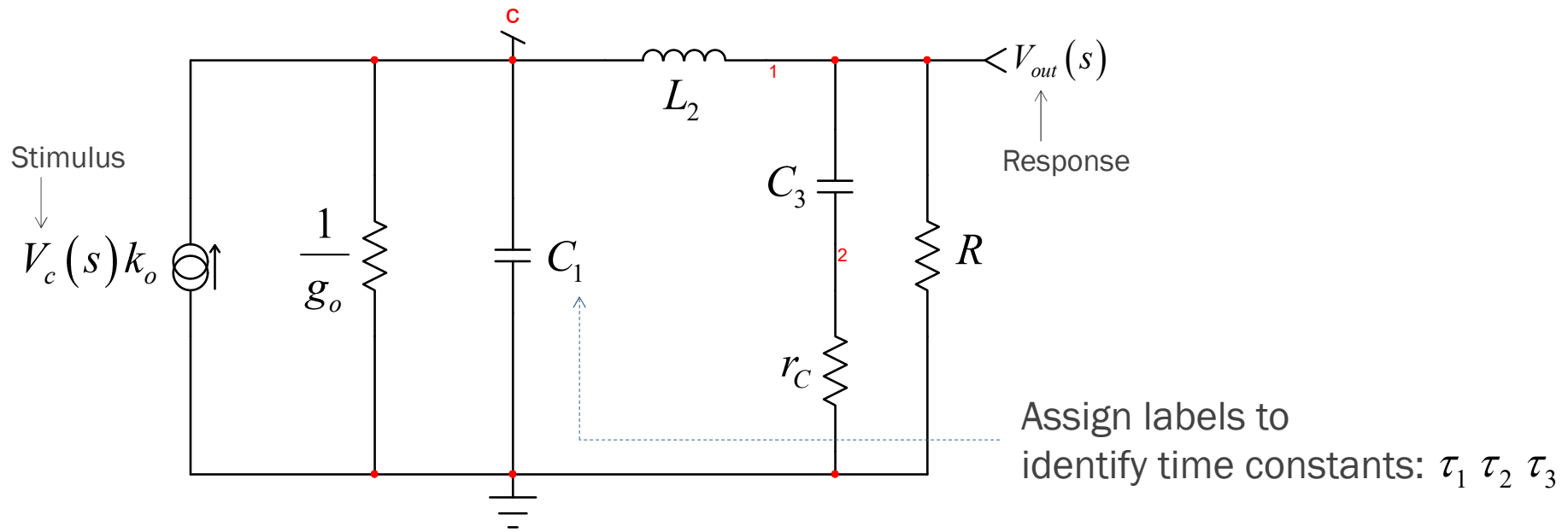


□ There are 3 energy-storing elements: 3rd-order system

Control to output




Look at each Time Constant when Excitation is Off

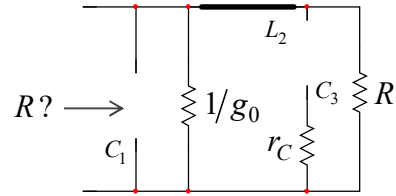
- ❑ The excitation is zero, elements are in their dc states
- ❑ 3 storage elements, 3 time constants, 3 drawings


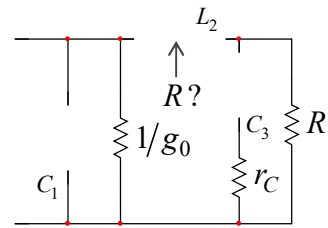
$$\tau_1 = f(C_1) \longrightarrow \tau_1 = C_1 \left(\frac{1}{g_o} \parallel R \right)$$


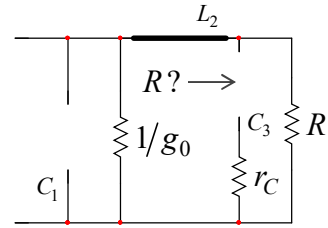
$$\tau_2 = f(L_2) \longrightarrow \tau_2 = \frac{L_2}{\frac{1}{g_o} + R}$$



$$\tau_3 = f(C_3) \longrightarrow \tau_3 = C_3 \left(r_C + \left(\frac{1}{g_o} \parallel R \right) \right)$$

Sum time constants
Dimension is time [s]



$$b_1 = \tau_1 + \tau_2 + \tau_3$$



$$b_1 = C_1 \left(\frac{1}{g_o} \parallel R \right) + \frac{L_2}{\frac{1}{g_o} + R} + C_3 \left(r_C + \left(\frac{1}{g_o} \parallel R \right) \right)$$

Control to output



Determine Second-Order Coefficients

□ One element is now set in its high-frequency state

τ_2^1

C_1 (HF)

L_2 (dc)

C_3 (dc)

$R?$ ↑

$\tau_2^1 = \frac{L_2}{R}$

τ_3^2

L_2 (HF)

C_3 (dc)

C_1 (dc)

$R?$ ↑

$\tau_3^2 = (r_C + R)C_3$

$b_2 = \tau_1\tau_2^1 + \tau_1\tau_3^1 + \tau_2\tau_3^2 \left[s^2 \right]$

↓

$b_2 = C_1 \left(\frac{1}{g_o} \parallel R \right) \frac{L_2}{R} + C_1 \left(\frac{1}{g_o} \parallel R \right) r_C C_3 + \frac{L_2}{\frac{1}{g_o} + R} (r_C + R) C_3$

Control to output

τ_3^1

C_1 (HF)

L_2 (dc)

C_3

$R?$ ↑


$\tau_3^1 = r_C C_3$

Two Elements are now set in High-Frequency State

- For b_3 , we multiply by a third time-constant

$$b_3 = \tau_1 \tau_2^1 \tau_3^{12} \longrightarrow \text{Dimension is time}^3$$

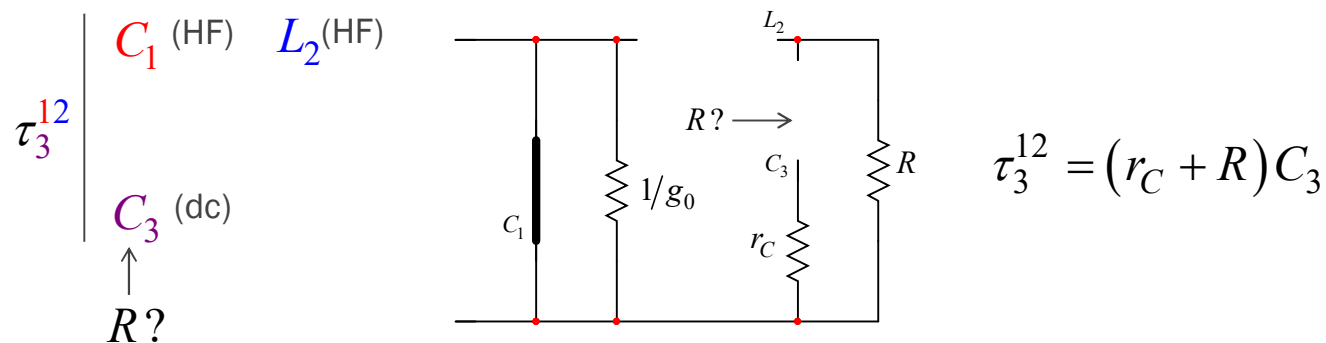- What is this new time constant definition?



- The final coefficient has been identified

$$b_3 = C_1 \left(\frac{1}{g_o} \parallel R \right) \frac{L_2}{R} (r_C + R) C_3$$

Assemble Time Constants to Build the Transfer Function

□ A Mathcad[®] sheet can be built to verify these calculations

$$H(s) = G_0 \frac{1 + \frac{s}{\omega_{z_1}}}{1 + b_1 s + b_2 s^2 + b_3 s^3} \quad G_0 = k_0 \left(R \parallel \frac{1}{g_0} \right)$$

$$\omega_{z_1} = \frac{1}{r_C C}$$

$$b_1 = C_1 \left(\frac{1}{g_o} \parallel R \right) + \frac{L_2}{\frac{1}{1} + R} + C_3 \left(r_C + \left(\frac{1}{g_0} \parallel R \right) \right)$$

$$b_2 = C_1 \left(\frac{1}{g_o} \parallel R \right) \frac{L_2}{R} + C_1 \left(\frac{1}{g_o} \parallel R \right) r_C C_3 + \frac{L_2}{\frac{1}{1} + R} (r_C + R) C_3$$

$$b_3 = C_1 \left(\frac{1}{g_o} \parallel R \right) \frac{L_2}{R} (r_C + R) C_3$$

5 V/1 A buck

$V_{in} = 10 \text{ V}, F_{sw} = 100 \text{ kHz}, R_i = 0.25 \Omega, S_e = 2.5 \text{ kV/s}$
 $C = 100 \mu\text{F}, r_C = 0.1 \Omega, L = 100 \mu\text{H}, C_s = 101 \text{ nF}, V_c = 1.28 \text{ V}$

$I_c = 4.94 \text{ A}$

$k_i = 2 \Omega^{-1} \quad k_0 = 4 \Omega^{-1}$

$g_0 = 0.01 \Omega^{-1}$

$g_f = -7.5 \text{ m}\Omega^{-1} \quad g_r = 0.49 \Omega^{-1}$

$g_i = -250 \text{ m}\Omega^{-1}$

$G_0 = 12 \text{ dB} \quad f_{z_1} = 15.9 \text{ kHz}$



Control to output



Excellent Agreement between SPICE and Equations

□ Superimposed curves means transfer functions are identical

dB

20

10

0

-10

-20

$|H(f)|$

10

100

1×10^3

1×10^4

1×10^5

°

0

-50

-100

-150

$\arg H(f)$

1


10^5

Rearrange the Expression in a *Low-Entropy* Form

- Proper arrangement is necessary to gain insight in the expression

$$D(s) = 1 + b_1s + b_2s^2 + b_3s^3$$

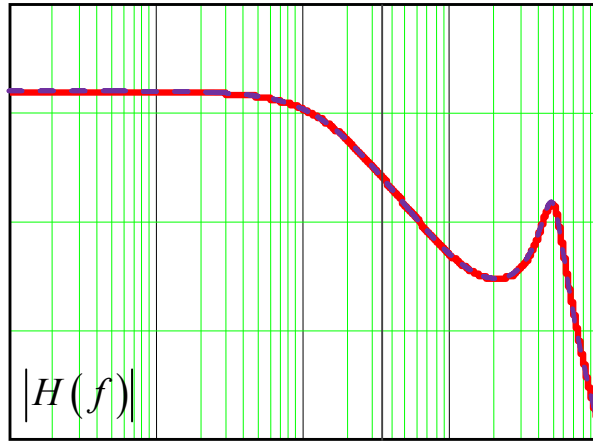- This is a third-order polynomial form that can be factored



$$D(s) \approx 1 + b_1s \quad \leftarrow \text{Low frequency} \quad \text{High frequency} \quad \rightarrow \quad D(s) \approx 1 + \frac{b_2}{b_1}s + \frac{b_3}{b_1}s^2$$



$$H(s) \approx H_0 \frac{1 + \frac{s}{\omega_{z_1}}}{1 + \frac{s}{\omega_{p_1}}} \frac{1}{1 + \frac{s}{\omega_n Q} + \left(\frac{s}{\omega_n}\right)^2}$$

Control to output

Final Expression shows Poles and Zeroes

- The transfer function can now unveil peaking and damping


$$H_0 = \frac{R}{R_i} \frac{1}{1 + \frac{RT_{sw}}{L_2} [m_c(1-D) - 0.5]}$$

$$\omega_{p1} = \frac{1}{RC_3} + \frac{T_{sw}}{L_2 C_3} [m_c(1-D) - 0.5] \quad \omega_{z1} = \frac{1}{r_C C_3}$$

$$\omega_n = \frac{\pi}{T_{sw}} \quad Q = \frac{1}{\pi [m_c(1-D) - 0.5]}$$

$$m_c = 1 + \frac{S_e}{S_n}$$


Artificial ramp
Inductor on-slope

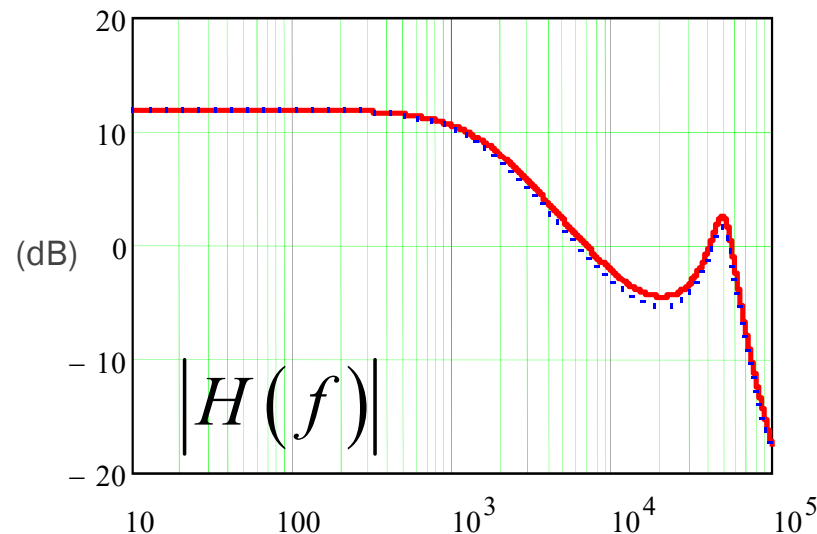

R. B. Ridley, *A new Continuous-Time Model for CM Control*, IEEE Transactions of Power Electronics, Vol. 6, April 1991

Input-to-Output Transfer Function or Audio-Susceptibility

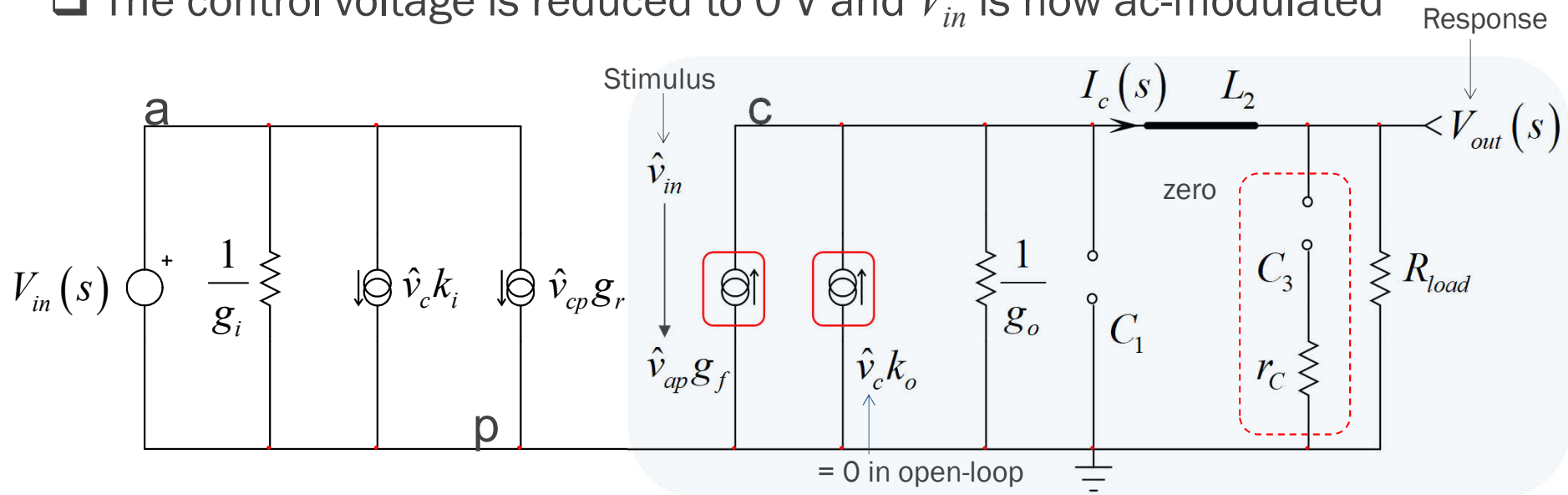- The control voltage is reduced to 0 V and V_{in} is now ac-modulated




- We have no interest in the left-side part now as it affects Z_{in} only
- ❖ In open-loop conditions, $\hat{v}_c(s)$ is 0 V and it simplifies the circuit

Input to output

The Dc Gain is Immediate

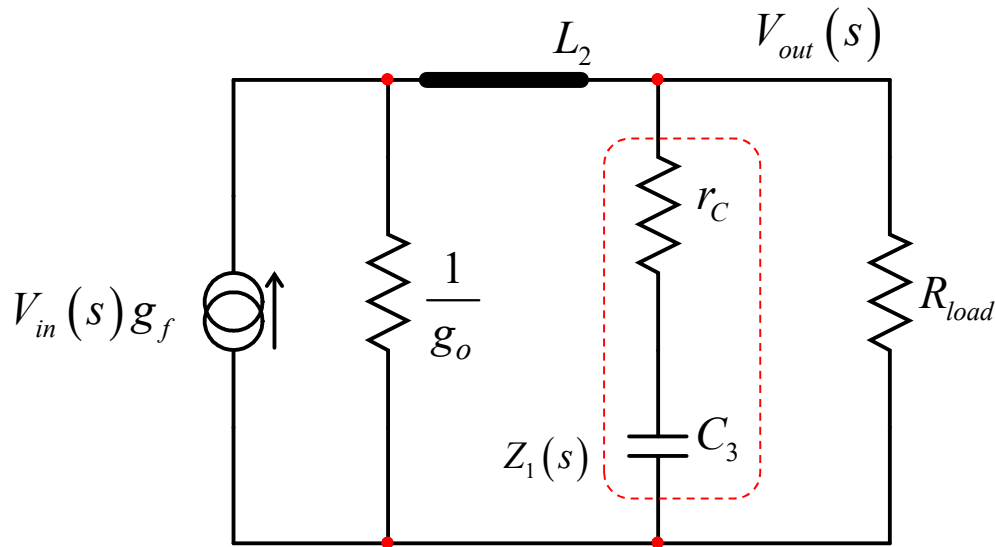- When the excitation is zeroed, the circuit returns to its natural state
- ✓ Reuse the denominator you have already determined



$$H(s) \approx H_0 \frac{1 + \frac{s}{\omega_{z_1}}}{1 + \frac{s}{\omega_{p_1}}} \frac{1}{1 + \frac{s}{\omega_n Q} + \left(\frac{s}{\omega_n}\right)^2}$$

$$H_0 = g_f \left(\frac{1}{g_o} \parallel R_{load} \right) \quad \omega_{z_1} = \frac{1}{r_C C_3}$$

- ✓ Current-mode control naturally rejects the input contribution as H_0 is low

Input to output

Rejecting the Input Voltage Contribution

□ Calculate the amount of external ramp to reject V_{in} perturbations

$$H_0 \approx \frac{D \left[m_c (1-D) - \left(1 - \frac{D}{2} \right) \right]}{\frac{L_2}{R_{load} T_{sw}} + \left[m_c (1-D) - 0.5 \right]}$$


$$D \left[m_c (1-D) - \left(1 - \frac{D}{2} \right) \right] = 0$$



$$m_c = \frac{D-2}{2D-2} \rightarrow \begin{matrix} S_e = 50\% \cdot S_n \\ D = 50\% \end{matrix}$$


✓ Theoretical infinite input rejection!

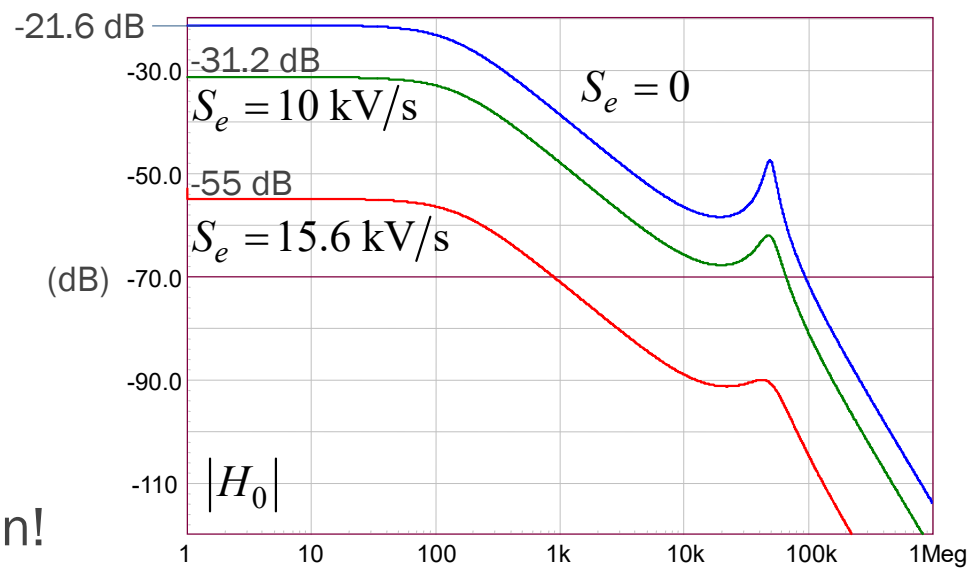$D := 56.6\%$ $V_{in} := 9V$ $V_{out} := 5V$ $L_2 := 100\mu H$ $R_L := 5\Omega$ $F_{sw} := 100kHz$ $R_i := 0.6\Omega$
 $T_{sw} := \frac{1}{100kHz}$ $S_n := \frac{V_{in} - V_{out}}{L_2} \cdot R_i = 24 \frac{kV}{s}$ $S_e := 15.65 \frac{kV}{s}$ $m_c := \frac{S_e}{S_n} + 1 = 1.652$




Output Impedance Determination

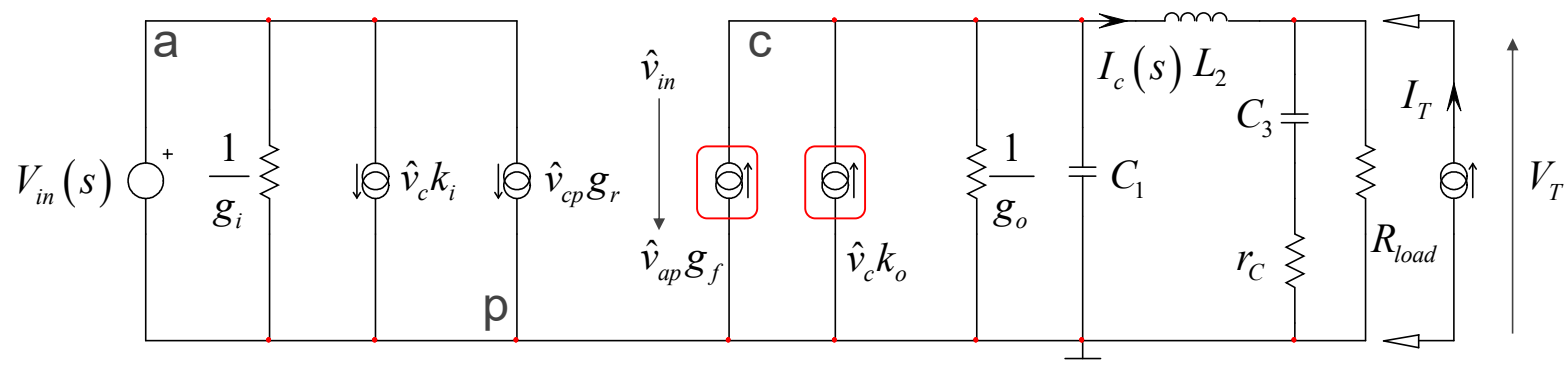- Install a current source across the load resistance



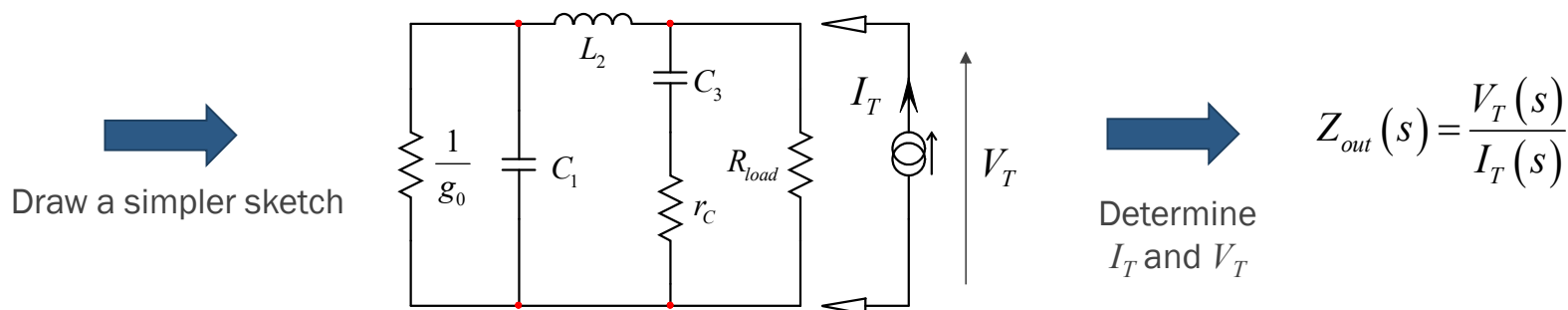
- The two controlled sources are turned off as V_{in} and V_c are 0 V




Output impedance

Determine Time Constants by Inspection

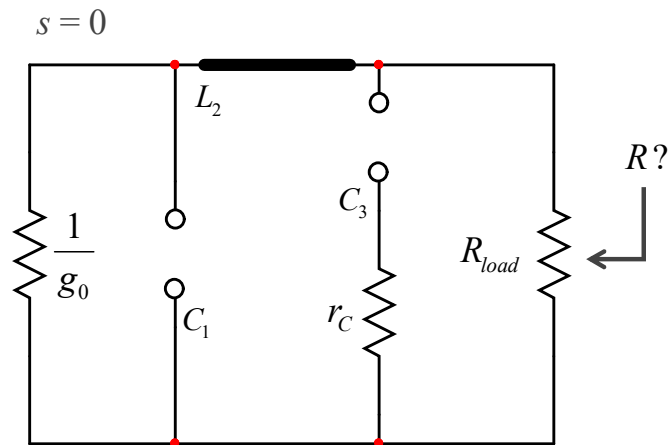- Short the inductor and open the capacitor for R_0


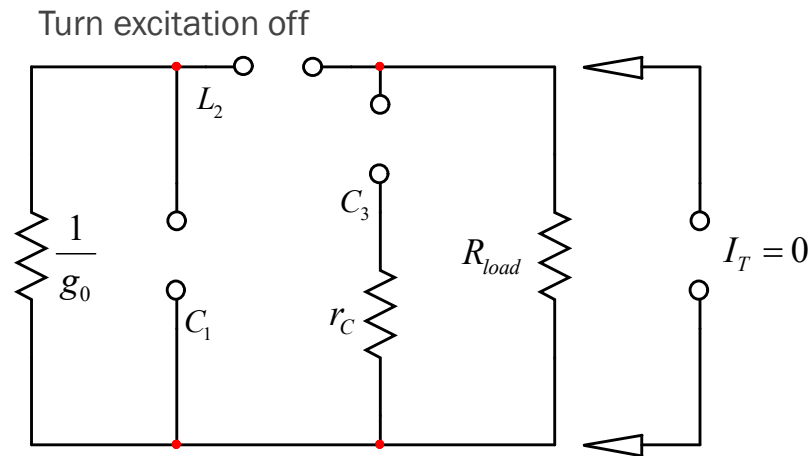
$$R_0 = R_{load} \parallel \frac{1}{g_0}$$




Back to the natural structure
Reuse previous denominator

$$D(s) \approx \left(1 + \frac{s}{\omega_{p1}}\right) \left[1 + \frac{s}{\omega_n Q} + \left(\frac{s}{\omega_n}\right)^2\right]$$

Output impedance

Null the Response for the Zeroes

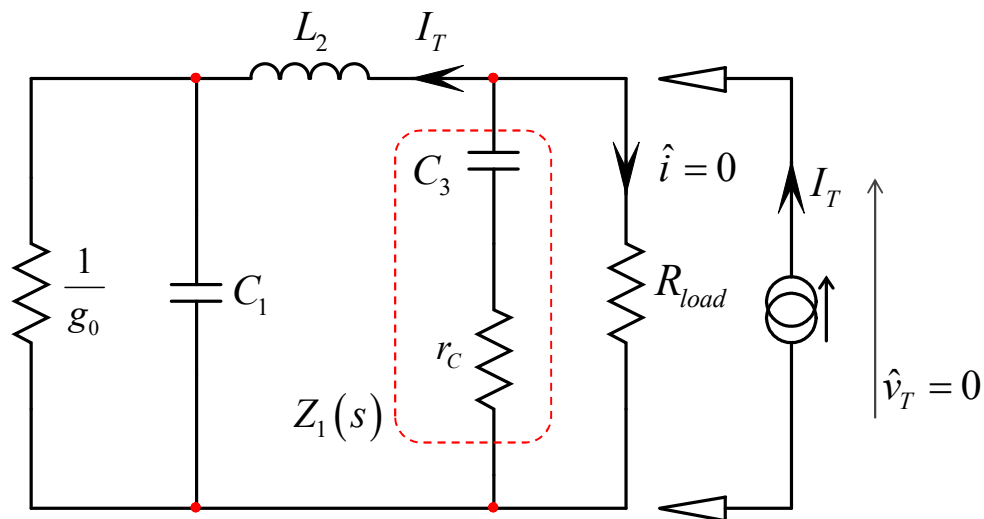- The response is nulled when no current circulates in R_{load}



1st zero

➔ $Z_1(s) = r_c + \frac{1}{sC_3} = 0 \quad \omega_z = \frac{1}{r_c C_3}$

No current flows in R_{load}



All the I_T current circulates in L_2



The impedance involving L_2 , C_1 and the conductance is a transformed short circuit

$$Z_2(s) = sL_2 + \frac{1}{g_0} \parallel \frac{1}{sC_1} = 0$$

$$Z_2(s) = \frac{1 + sg_0L_2 + s^2L_2C_1}{D(s)} = 0$$

$$N(s) = 1 + \frac{s}{\omega_N Q_N} + \left(\frac{s}{\omega_N} \right)^2$$

Simplify and test the Final Expression

□ The second-order polynomial form is affected by Q and ω_0

$$\omega_N = \frac{1}{\sqrt{L_2 C_1}} \quad Q_N = \frac{1}{g_o} \sqrt{\frac{C_1}{L_2}}$$




High-frequency contribution

$$Z_{out}(s) = R_0 \frac{1 + \frac{s}{\omega_z} \left[1 + \frac{s}{\omega_N Q_N} + \left(\frac{s}{\omega_N} \right)^2 \right]}{1 + \frac{s}{\omega_p} \left[1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0} \right)^2 \right]}$$


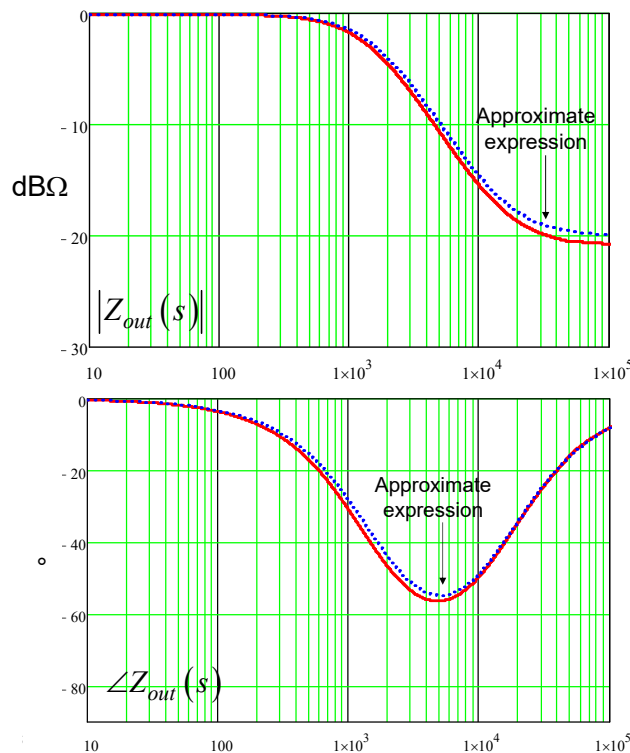
$$Z_{out}(s) \approx \frac{R_{load}}{1 + \frac{R_{load}}{L_2} T_{sw} [m_c (1-D) - 0.5]} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$



The impedance is dominated by R_{load} in low frequency




Need high open-loop gain to lower Z_{out}

Output impedance




Input Impedance Determination

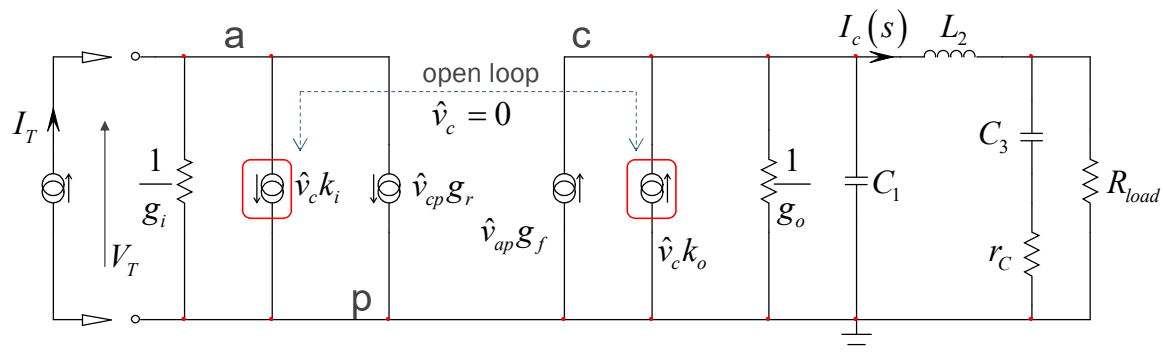□ The excitation source now biases the input port



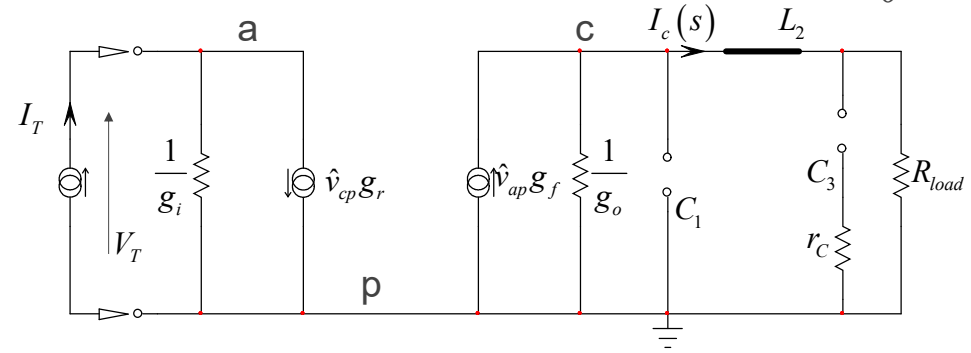□ Determine the incremental resistance R_0 for $s = 0$



Temporarily disconnect $\frac{1}{g_i}$

Intermediate result without $\frac{1}{g_i}$


$$R_0 = R_{int} \parallel \frac{1}{g_i}$$

Input impedance



A Negative Open-Loop Incremental Resistance

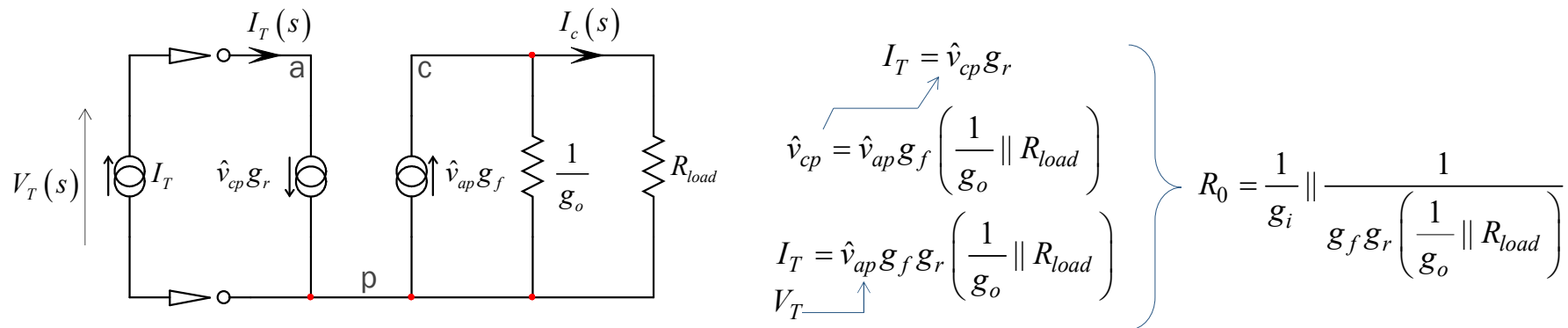- The input current is the test current I_T



- Replace coefficients by their definition and rearrange

$$R_0 = - \frac{R_1 \left[\left(\frac{L_2}{R_{load} T_{sw}} + 0.5 - D \right) S_n + S_e (1 - D) \right]}{\left[\left(S_e + \frac{S_n}{2} \right) D^3 - \left(S_e + \frac{M}{2} S_n \right) D^2 + \frac{M}{2} S_n D \right] + M D S_n \frac{L_2}{R_{load} T_{sw}}}$$




The incremental resistance of the CCM open-loop buck converter is negative


Input impedance

Turn the Excitation off and Determine Time Constants

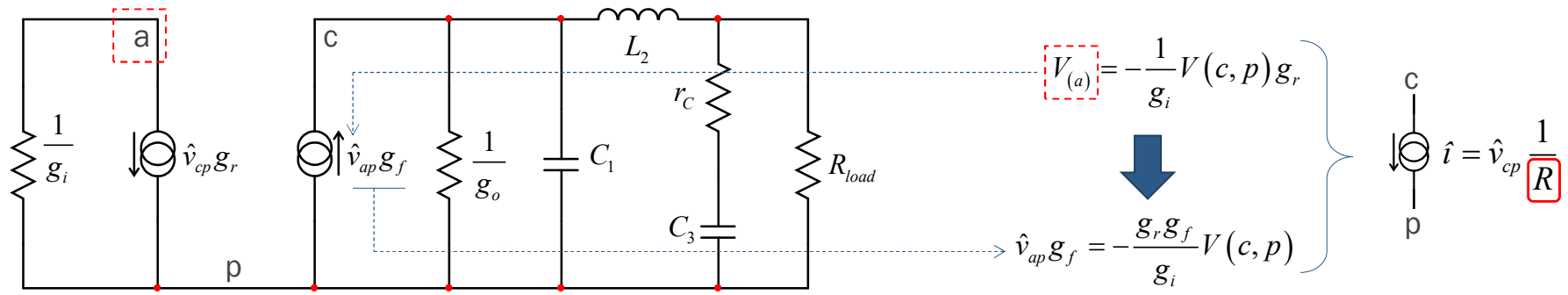
❑ Get rid of the controlled sources for an easy inspection



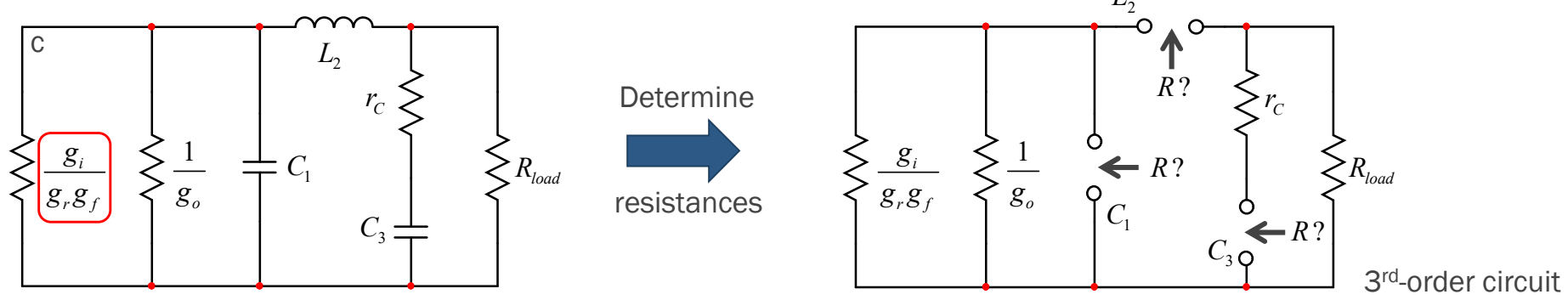
❑ Inspection works to determine the time constants



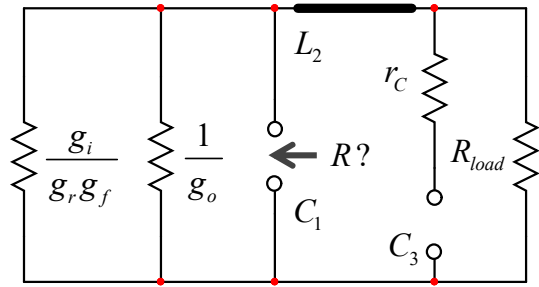
Break the Circuit into Small Individual Sketches



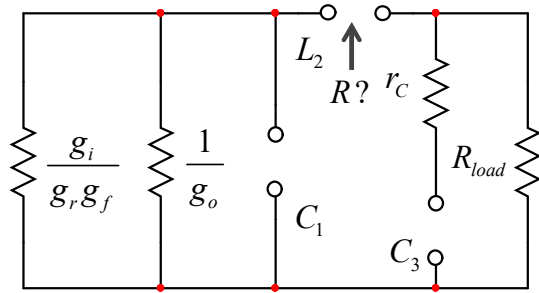
$$\tau_1 = C_1 \left(\frac{1}{g_o} \parallel R_{load} \parallel \frac{g_i}{g_r g_f} \right)$$



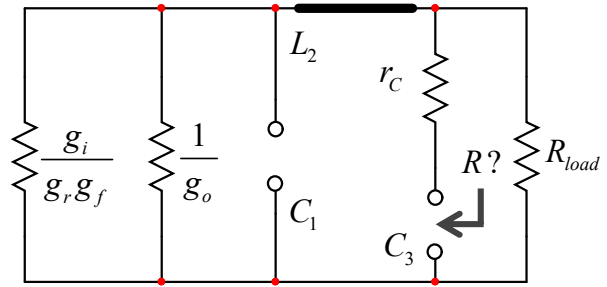
$$\tau_2 = \frac{L_2}{\frac{1}{g_o} \parallel \frac{g_i}{g_r g_f} + R_{load}}$$



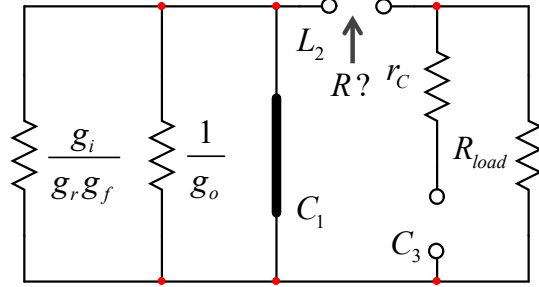
$$\tau_3 = C_3 \left(r_c + \frac{1}{g_o} \parallel R_{load} \parallel \frac{g_i}{g_r g_f} \right)$$



$$\tau_2^1 = \frac{L_2}{R_{load}}$$

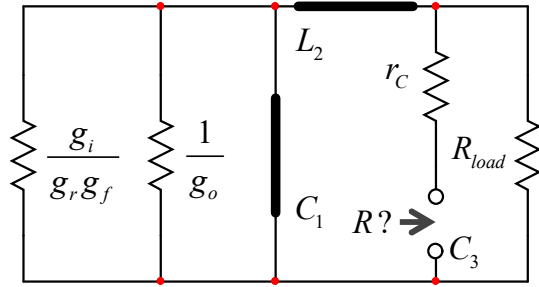

$$\tau_3^1 = C_3 r_c$$

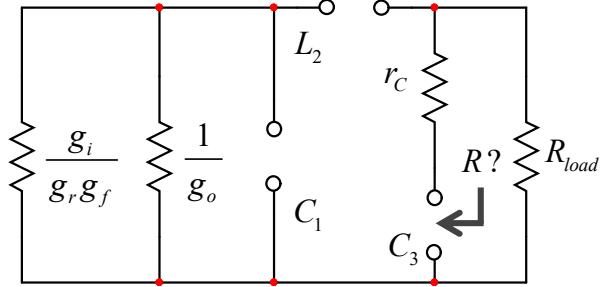


$$\tau_3^2 = C_3 (r_c + R_{load})$$

Input impedance



Combine the Time Constants

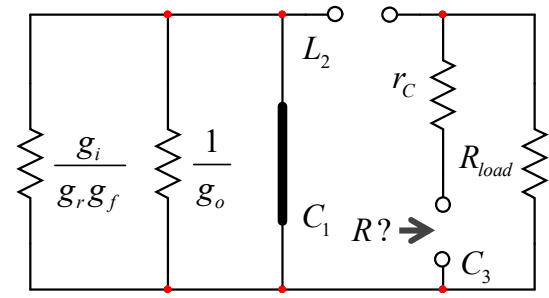□ Assemble the time constants to form the denominator



$$\tau_3^{12} = C_3 (r_c + R_{load})$$

$$D(s) = 1 + sb_1 + s^2 b_2 + s^3 b_3$$

$$b_1 = \tau_1 + \tau_2 + \tau_3$$

$$b_2 = \tau_1 \tau_2^1 + \tau_1 \tau_3^1 + \tau_2 \tau_3^2$$


$$b_3 = \tau_1 \tau_2^1 \tau_3^{12}$$

$$b_1 = C_s \left(\frac{1}{g_o} \parallel R_{load} \parallel \frac{g_i}{g_r g_f} \right) + \frac{L_2}{\frac{1}{g_o} \parallel \frac{g_i}{g_r g_f}} + C_1 \left(r_c + \frac{1}{g_o} \parallel R_{load} \parallel \frac{g_i}{g_r g_f} \right)$$

$$b_2 = C_s \left(\frac{1}{g_o} \parallel R_{load} \parallel \frac{g_i}{g_r g_f} \right) \frac{L_2}{R_{load}} + C_s \left(\frac{1}{g_o} \parallel R_{load} \parallel \frac{g_i}{g_r g_f} \right) C_3 r_c + \frac{L_2}{\frac{1}{g_o} \parallel \frac{g_i}{g_r g_f}} C_3 (r_c + R_{load})$$

$$b_3 = C_s \left(\frac{1}{g_o} \parallel R_{load} \parallel \frac{g_i}{g_r g_f} \right) \frac{L_2}{R_{load}} C_3 (r_c + R_{load})$$

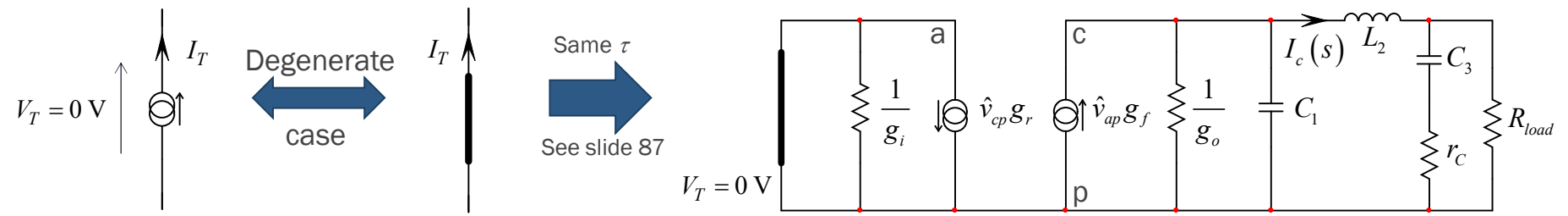□ 0-V V_T brings the circuit back to its structure: reuse former $D(s)$ of slide 87





Plot the Open-Loop Input Impedance

- The input impedance is negative up to high frequencies

$$Z_{in}(s) = R_0 \frac{N(s)}{D(s)} \quad N(s) = 1 + a_1s + a_2s^2 + a_3s^3 \quad D(s) = 1 + b_1s + b_2s^2 + b_3s^3$$



See slide 87

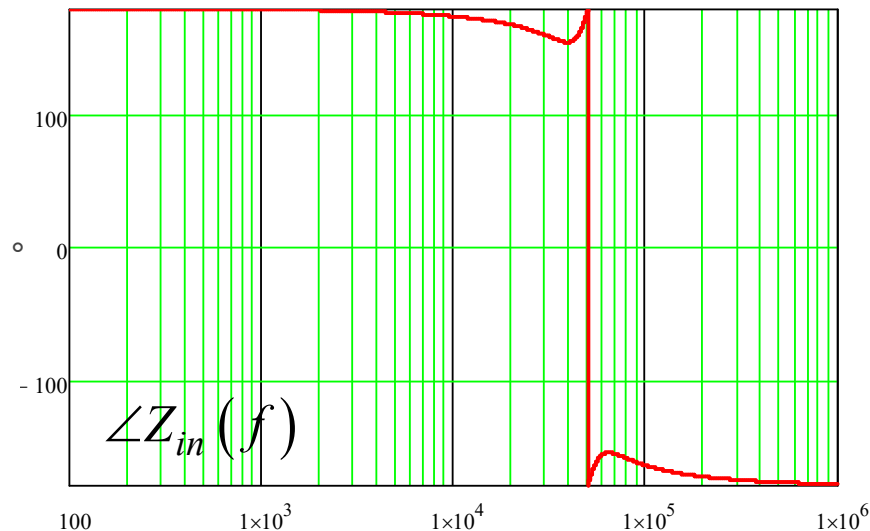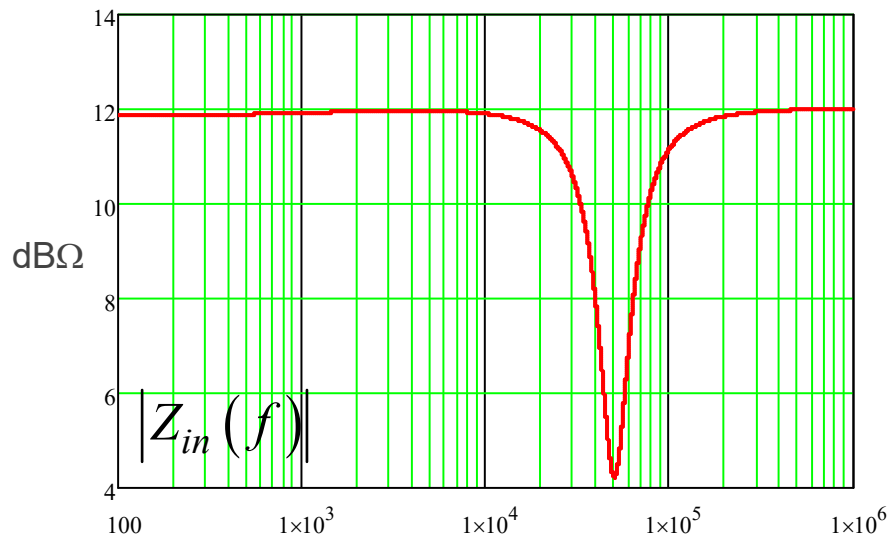

Input impedance

Why is the Incremental Resistance Negative?

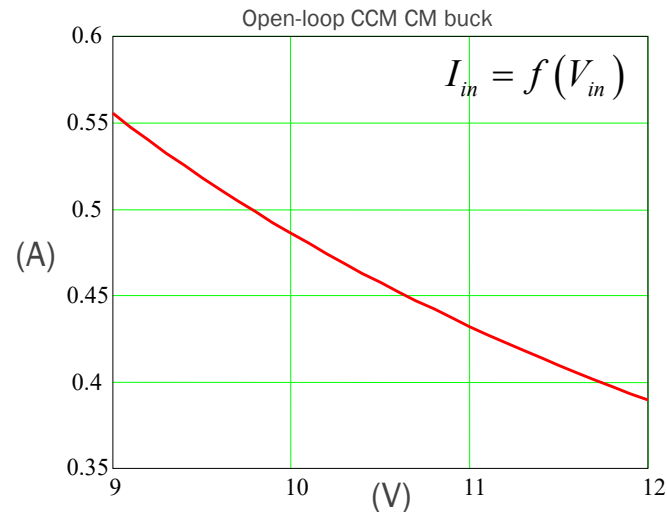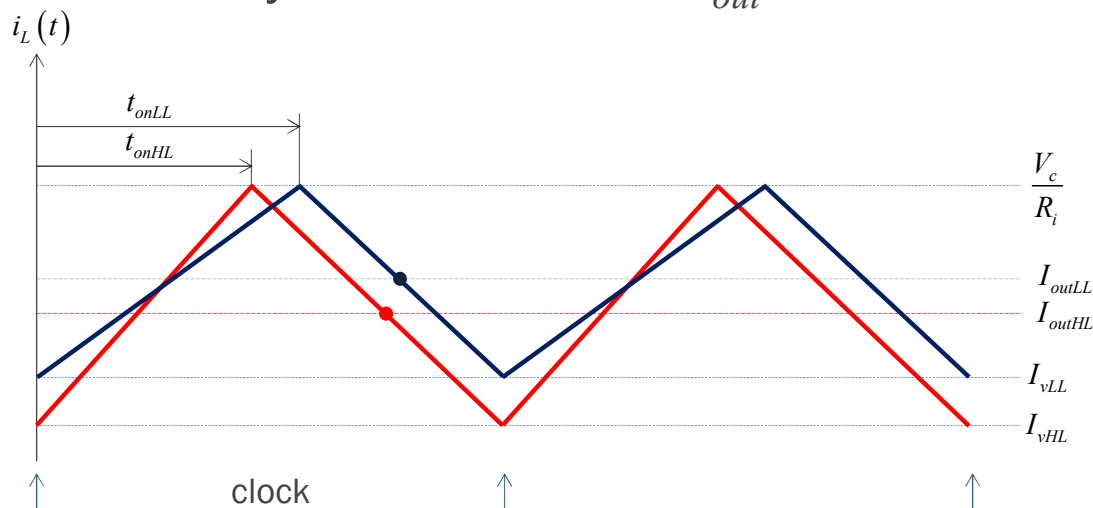- The smaller on-time at high line offers more demagnetization time
- The valley current is lower: I_{out} decreases when V_{in} increases



A voltage increase brings an input current decrease:


$$R_0 := \frac{V_1 + V_{step} - V_1}{I_{in}(V_1 + V_{step}) - I_{in}(V_1)} = -12.61\Omega \quad 5 \text{ V/1 A}$$

$$V_1 = 9 \text{ V} \quad V_{step} = 1 \text{ mV}$$



Unstable in Open-Loop Conditions with an EMI Filter

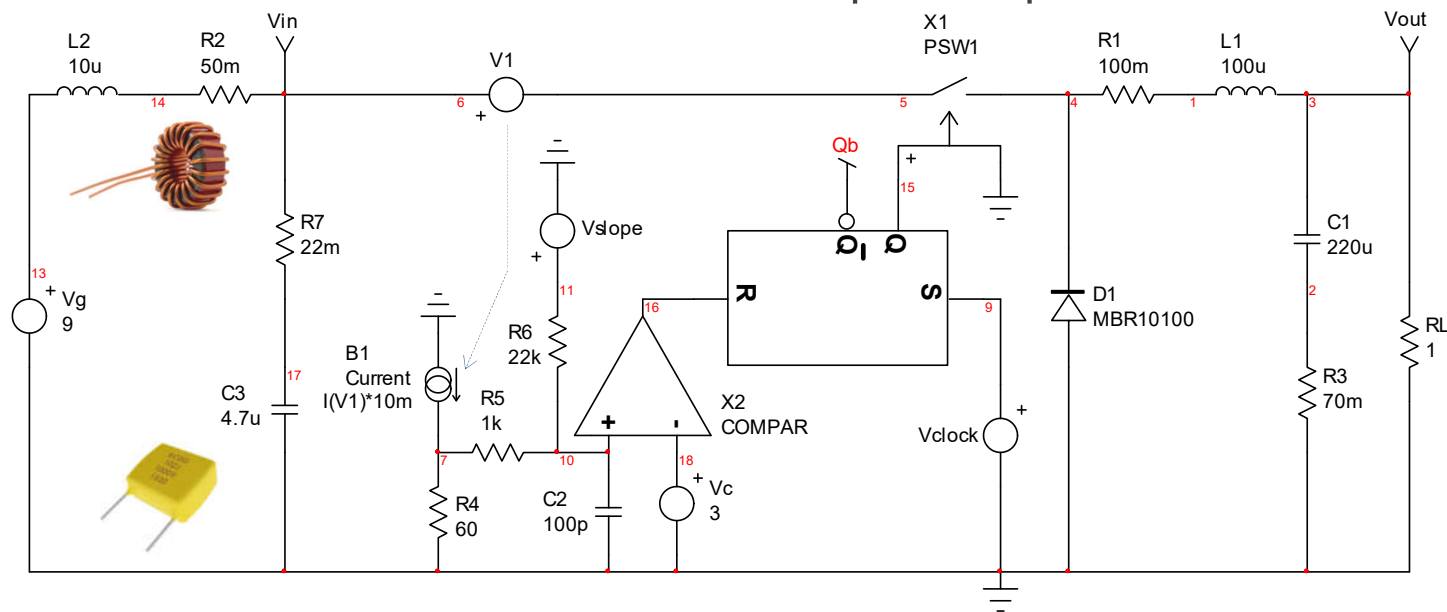- ❑ For many converters, filter-related instabilities occur in closed loop
- The CCM CM buck can be unstable in open-loop conditions




- ❑ It is a simple open-loop configuration, 5 V/5 A.


Input impedance

The Filter Output is Affected by a High Ripple

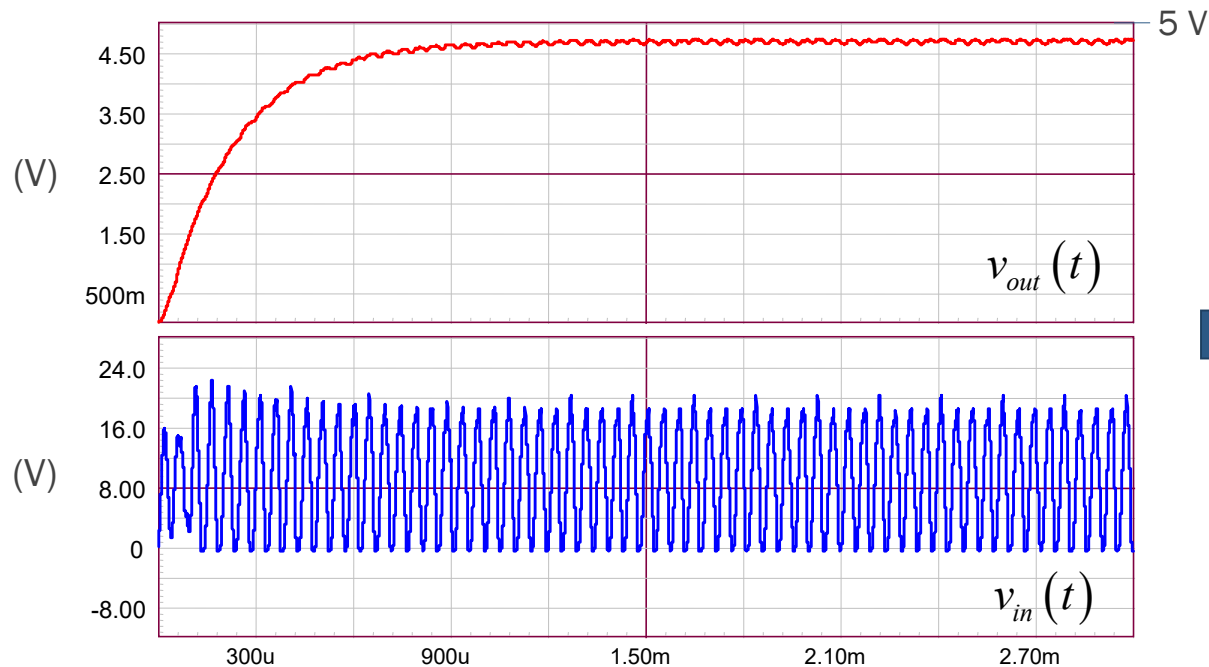- ❑ The converter can barely deliver the voltage but its input is highly unstable



Filter damping is an absolute necessity!

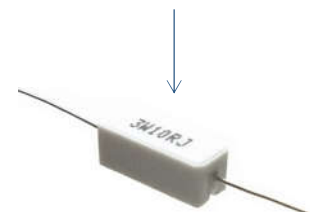


Generate losses



The Filter Output Impedance brings the Problem

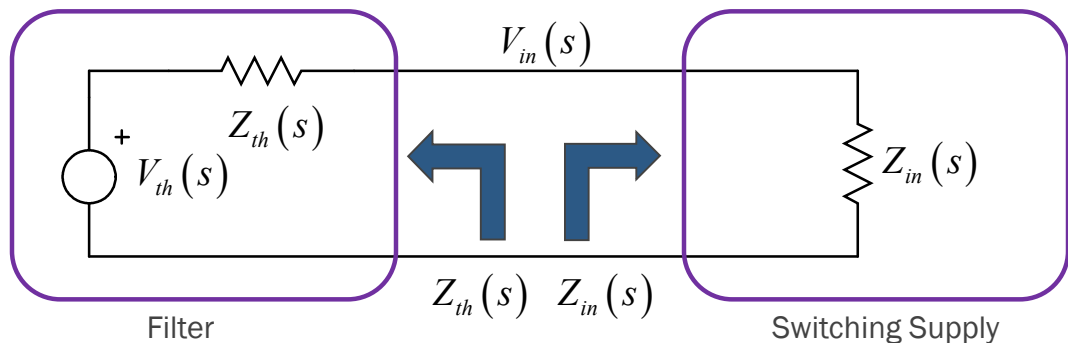- Stability can be at stake when inserting the filter




The Nyquist criterion applies



$$\frac{Z_{th}(s)}{Z_{in}(s)} = -1 \quad \triangle!$$

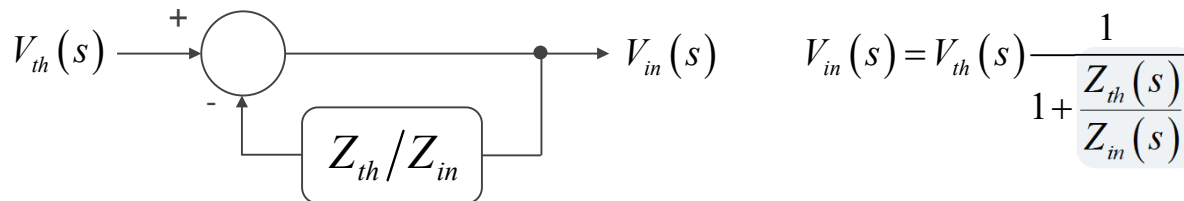- The circuit can be modeled to reveal a minor loop



$$V_{in}(s) = V_{th}(s) \frac{1}{1 + \frac{Z_{th}(s)}{Z_{in}(s)}}$$

$$\left| \frac{Z_{th}(s)}{Z_{in}(s)} \right| = 1 \text{ and } \angle \frac{Z_{th}(s)}{Z_{in}(s)} = -180^\circ$$



Stay away from overlaps

R. D. Middlebrook, *Input Filter Considerations in Design and Application of Switching Regulators*, IEEE Proceedings, 1976



Check EMI Filter Output Impedance Peaking

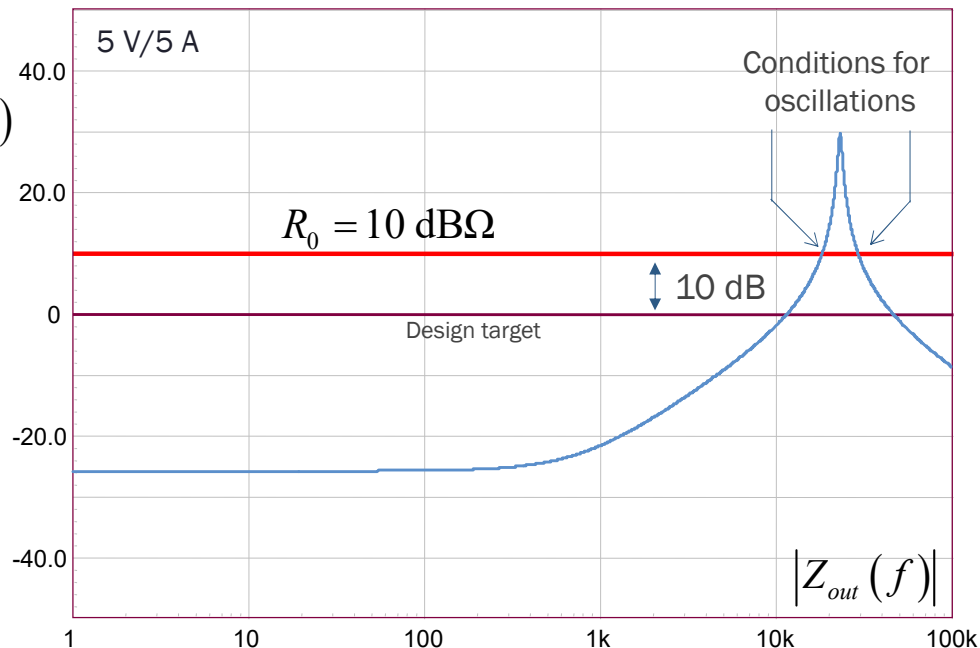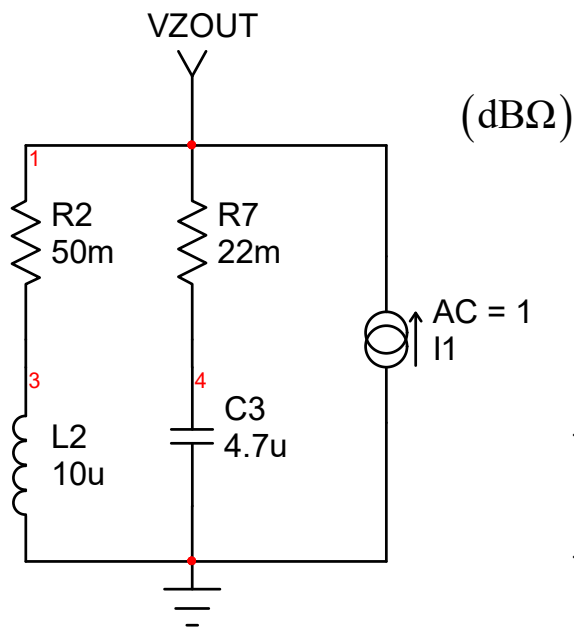- ❑ Does overlap exist with the negative incremental resistance?
- Yes – damp the filter with external components



Input impedance


Optimally Damp the Filter Output Impedance

- The target is to reduce the filter impedance peak to 0 dBΩ or 1 Ω

$$\left. \begin{aligned} R_0 &= \sqrt{\frac{L_f}{C_f}} \\ \frac{|Z_{out}|_{mm}}{R_0} &= \sqrt{\frac{2(2+n)}{n^2}} \end{aligned} \right\} n = \frac{R_0 \left(R_0 + \sqrt{R_0^2 + 4(|Z_{out}|_{mm})^2} \right)}{(|Z_{out}|_{mm})^2} = 5.738$$

1-Ω target ↑
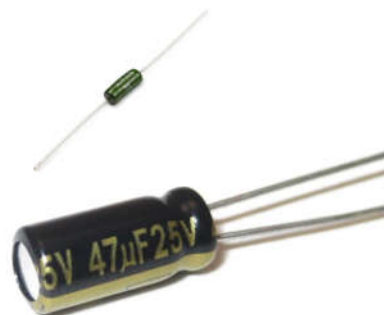
$$Q_{opt} = \sqrt{\frac{(4+3n)(2+n)}{2n^2(4+n)}} = 0.506$$
$$R_{damp} = R_0 Q_{opt} = 0.74 \Omega$$
$$C_{damp} = n C_f = 27 \mu\text{F}$$




- This is a rather large capacitance value for a ceramic device
- A 47-μF electrolytic capacitor and its ESR can do the job
- ❖ Watch for temperature effects as ESR increases at low temp!

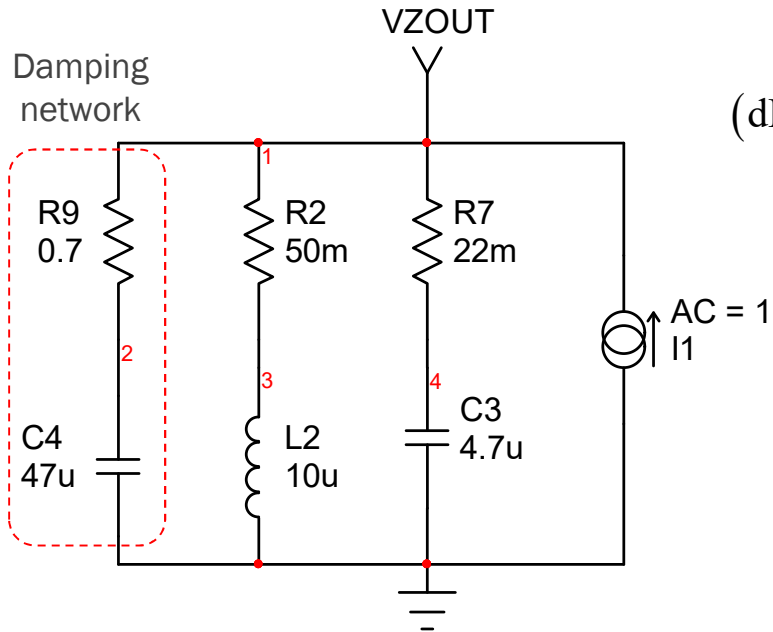
C. Basso, *EMI Input Filter Interaction with Switching Converters*, APEC Professional Seminars, 2017

The Peak is Lowered Owing to Extra Losses

- The added RC network exactly meets the design target





(dBΩ)

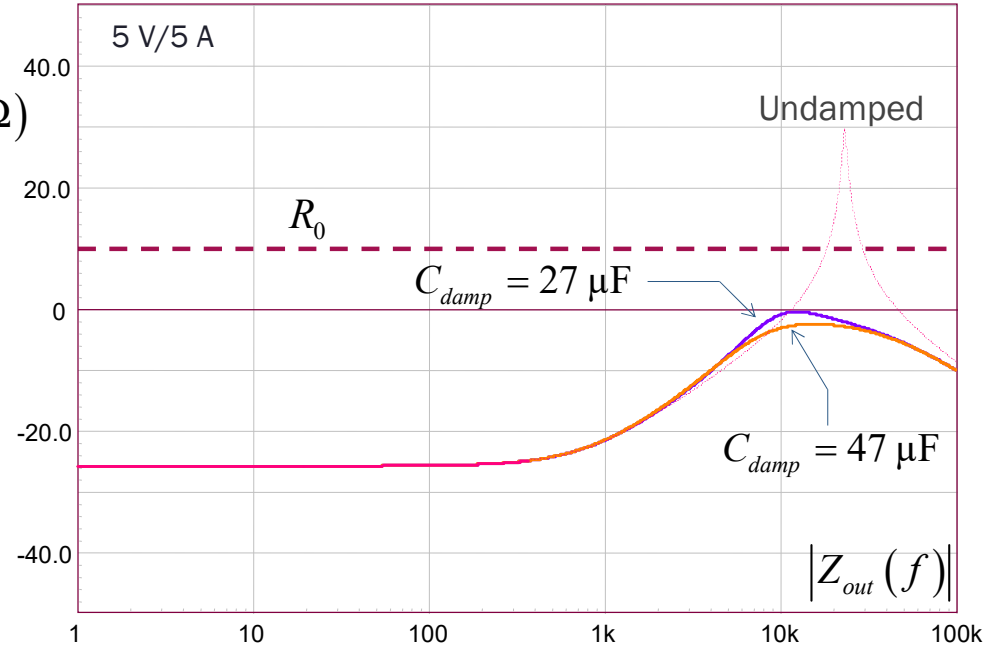

Filter Damping has calmed down Oscillations

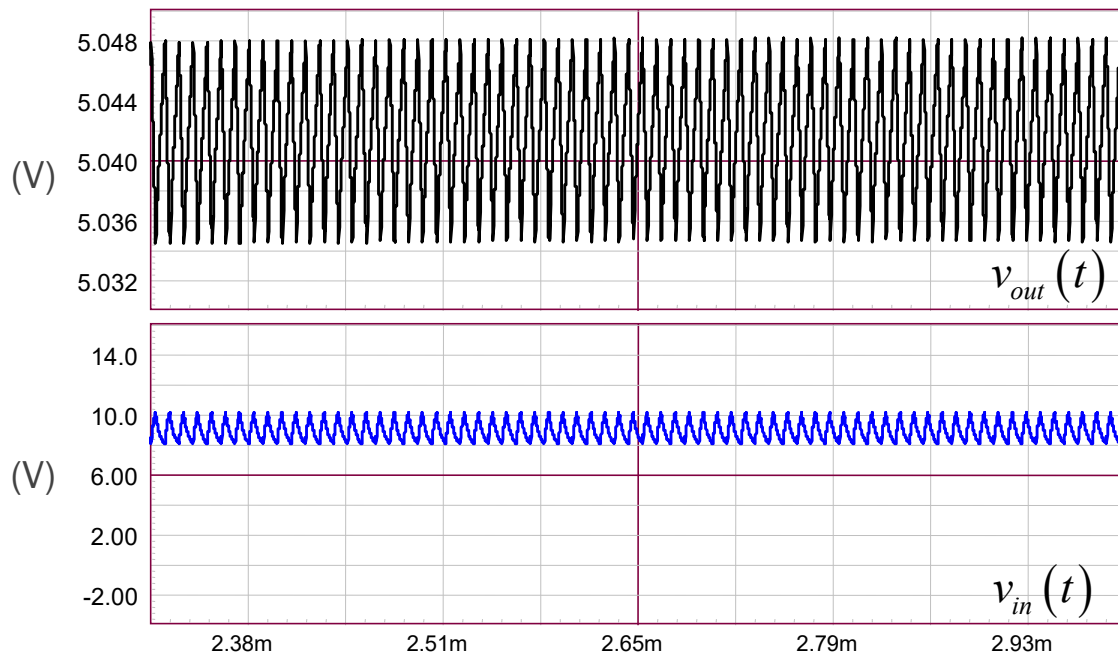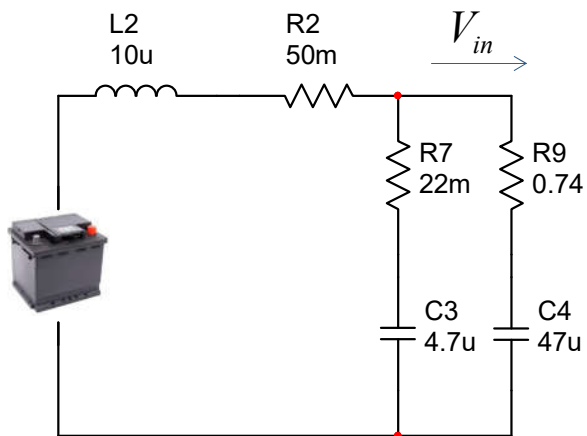- Once the damper is added, high-frequency ripple remains



- ❖ Check margins again once the converter is compensated



Input impedance

Reduce the Load Current to enter DCM

□ The control-to-output transfer function is still of second order!

$$H(s) \approx H_0 \frac{1 + \frac{s}{\omega_z}}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$
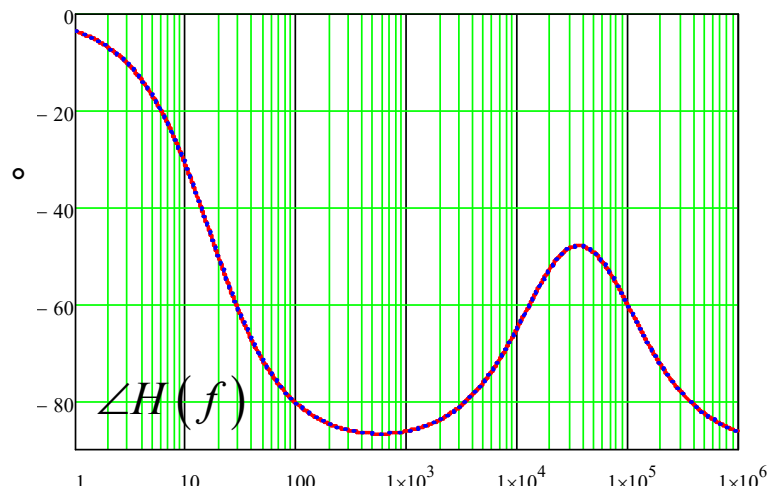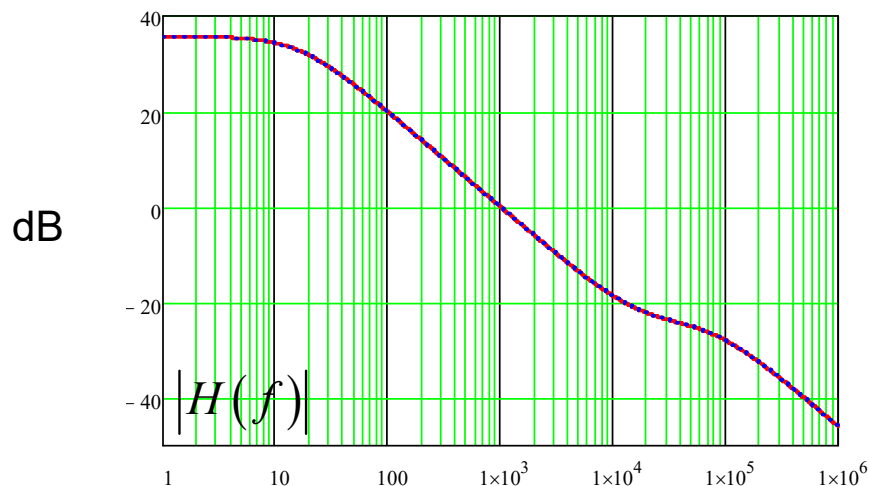
$$\omega_{p1} = \frac{1}{R_{load} C_1} \frac{2m_c - (2 + m_c)M}{m_c(1 - M)} \quad \omega_{p2} = 2F_{sw} \left(\frac{M}{D}\right)^2$$



R. B. Ridley, *A new Continuous-Time Model for CM Control*, IEEE Transactions of Power Electronics, Vol. 6, April 1991




Instability in Absence of Compensation Ramp

- When the ramp reduces to zero, the DCM CM buck can be unstable

$$\omega_{p_1} = \frac{1}{R_{load} C_1} \frac{2m_c - (2 + m_c)M}{m_c(1 - M)} \quad \text{Reduce } m_c \text{ to } 1 \quad \longrightarrow \quad \omega_{p_1} = \frac{1}{R_{load} C_1} \frac{2 - 3M}{1 - M}$$

- Plot the pole position versus M

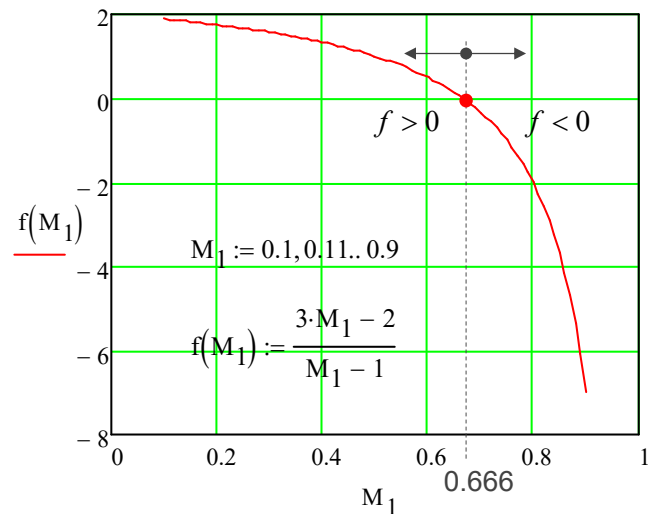

- As M increases (V_{in} is lowered), the pole approaches the origin
- For $M = 0.666$, the pole is at the origin
- For M greater than 0.666, the pole jumps in the right half-plane

➔ Despite DCM, a compensation ramp is needed

$$M = \frac{V_{out}}{V_{in}}$$


Course Agenda

- The Buck Converter
- Control Schemes
- Introduction to Modeling
- The PWM Switch in Current-Mode Control
- Introduction to the Fast Analytical Techniques
- The Four Transfer Functions in CCM Current-Mode Control
- Compensation Strategy
- Prototype Measurements



Transient Response and Compensation Strategy

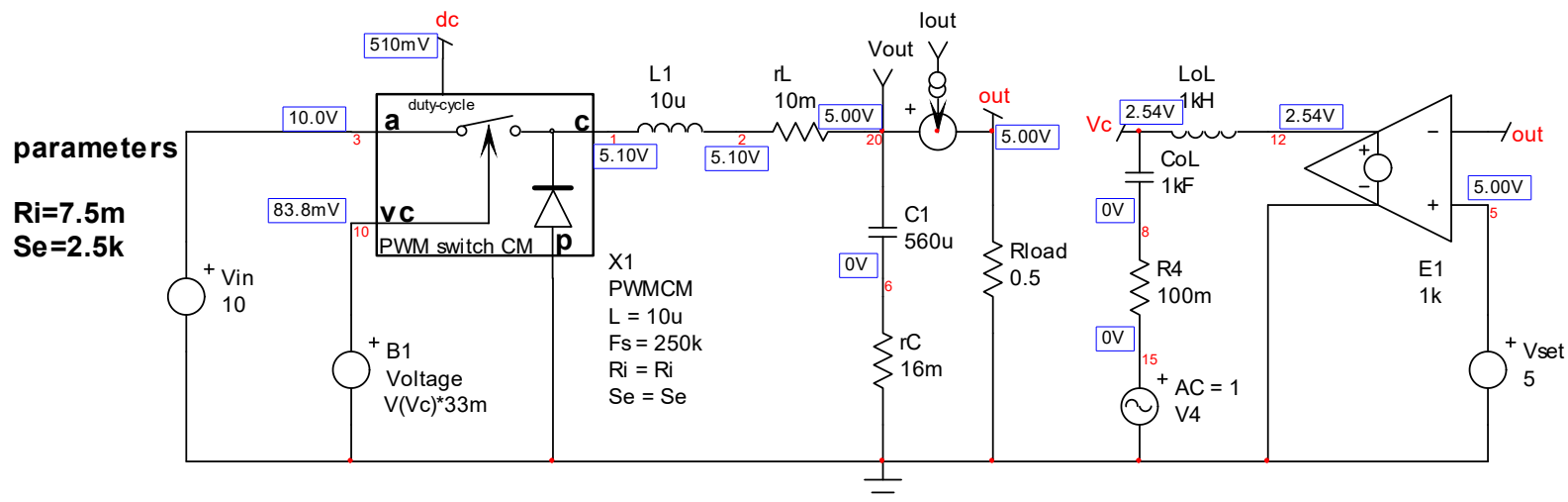
- A nonlinear average model is the ideal tool
- ❖ Auto-bias the output to its operating point, $I_{out} = 10$ A



- Check all operating points are correct ($V_{out} = 5$ V)
- Extract magnitude and phase information from the Bode plot



Stabilizing the Current-Mode Buck Converter

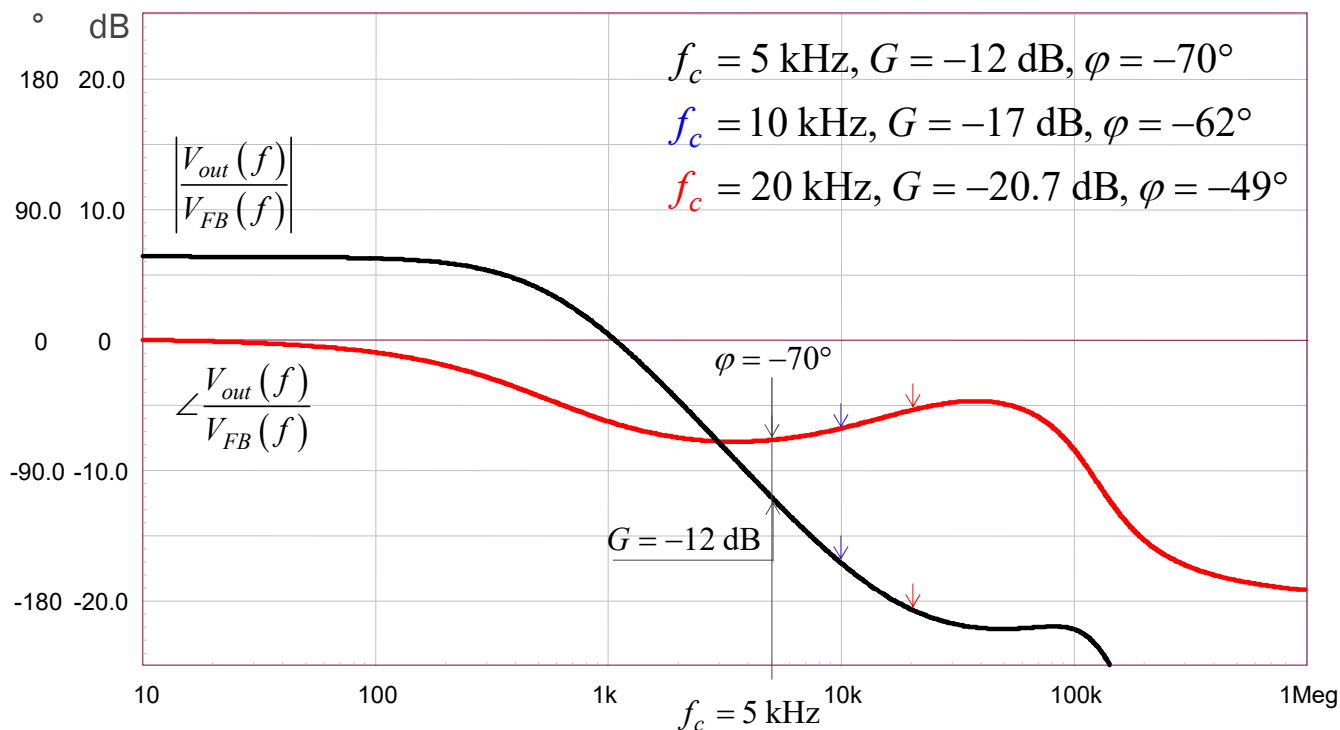- What you need is the control-to-output transfer function of the power stage



Automate the Compensation Process with k-Factor

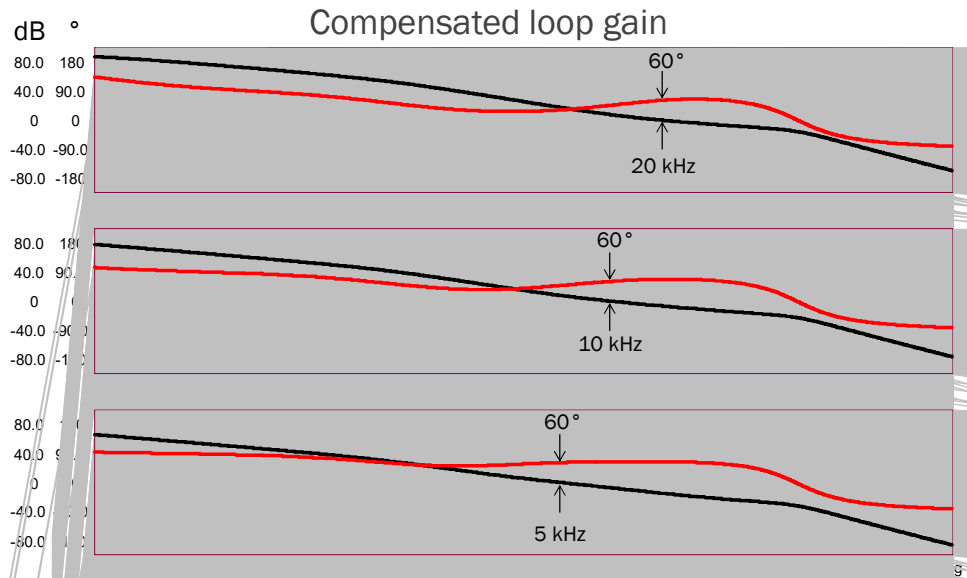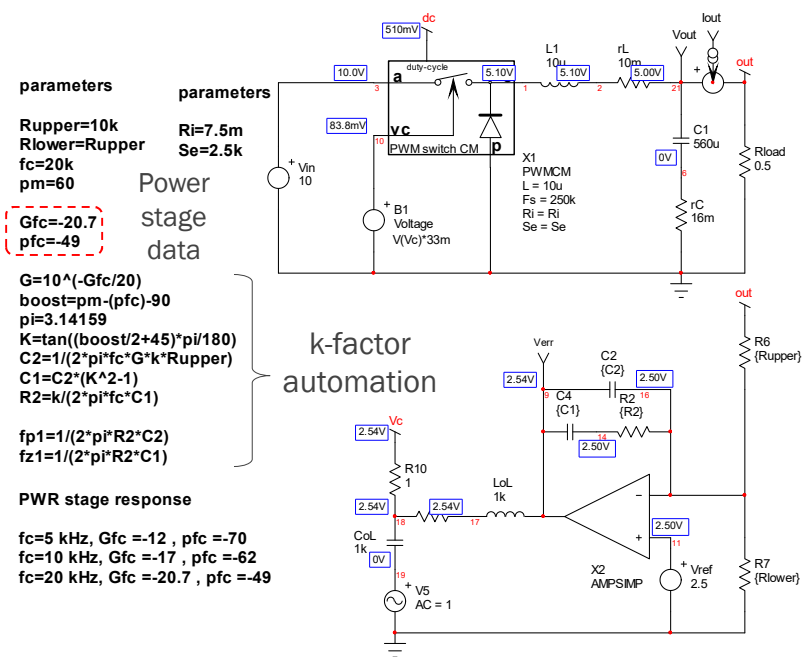
- Use a SPICE simulation to try different compensation scenarios




- Keep phase margin constant and adjust crossover frequency

Step-Load the Output of the Converter in Closed Loop

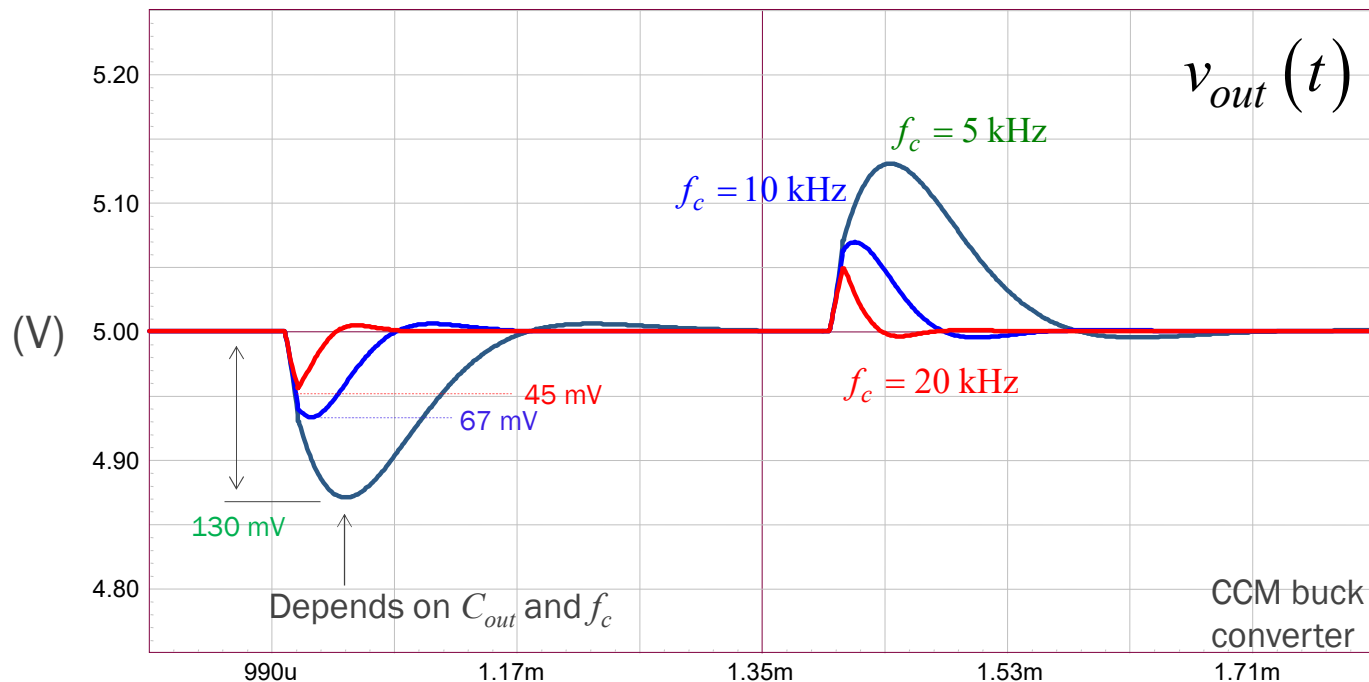- With a constant 60° phase margin, recovery slope is constant



Step load

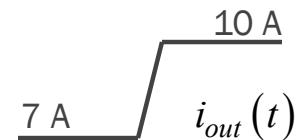


$$\Delta I_{out} = 3 \text{ A in } 3 \mu\text{s}$$




Sweep Phase Margin at Constant Crossover

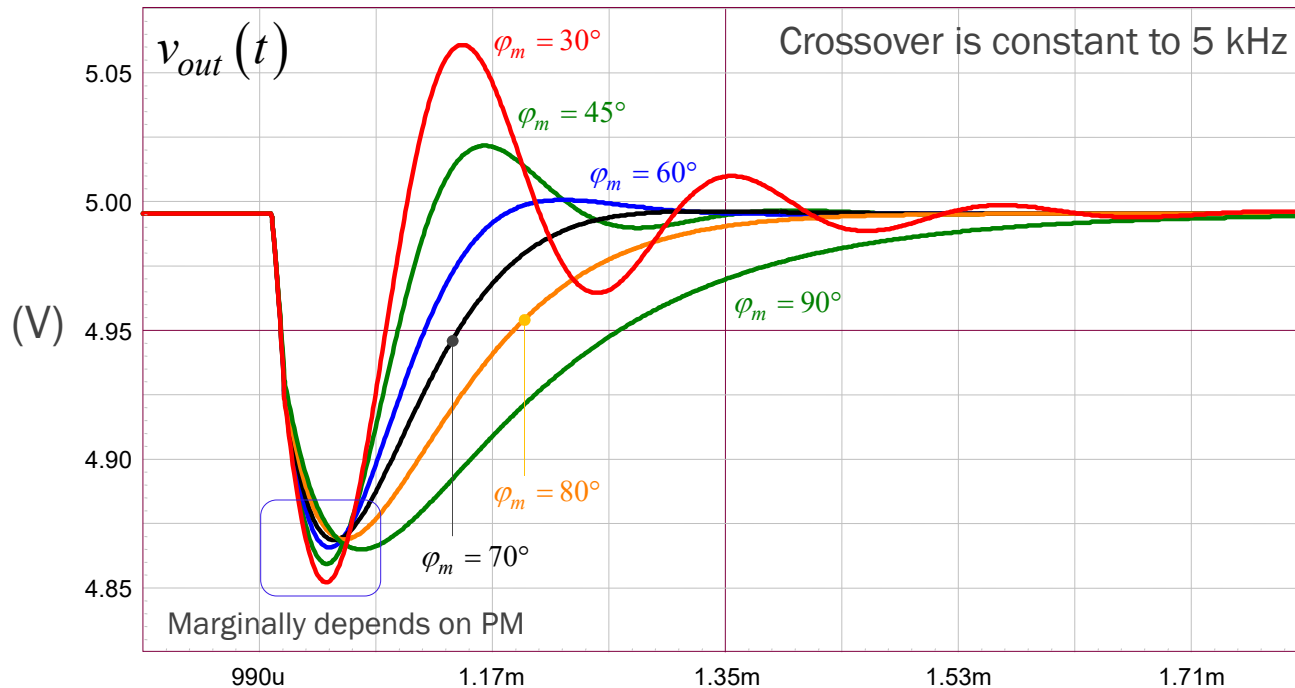- The phase margin affects the overshoot and the recovery time



Step load

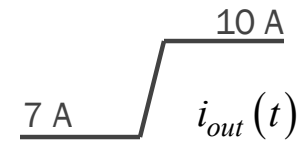


$\Delta I_{out} = 3 \text{ A in } 3 \mu\text{s}$




Phase Margin and Transient Response

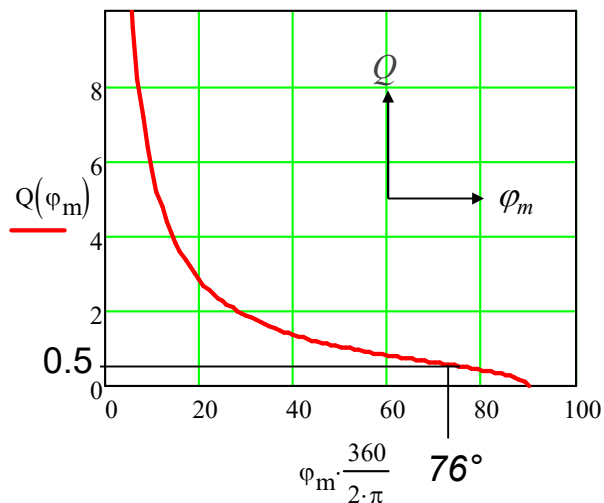- The phase margin selection depends on the transient response you want



$$Q = \frac{\sqrt{\cos(\varphi_m)}}{\sin(\varphi_m)}$$

↑ Closed loop ↑ Open loop

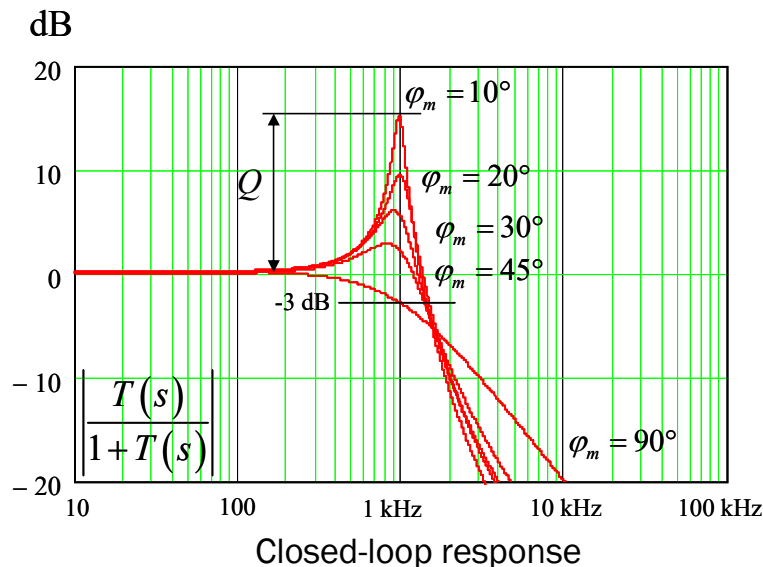


- ✓ The *open-loop* phase margin affects the *closed-loop* quality factor

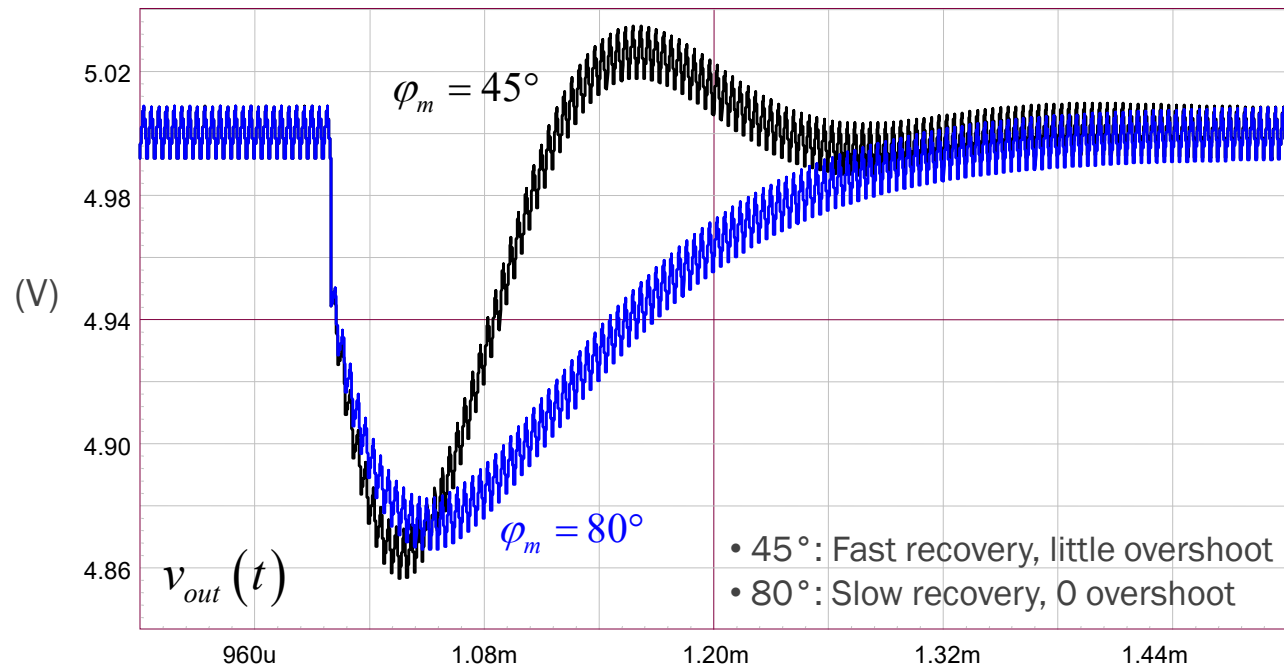
C. Basso, *The Dark Side of Loop Control Theory*, APEC 2012 Professional Seminar

What Transient Response is Needed?

- ☐ Choose phase margin based on the transient response you want



Step
load


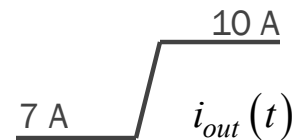


$$\Delta I_{out} = 3 \text{ A in } 3 \mu\text{s}$$



Crossover Selection for the Buck VM Converter

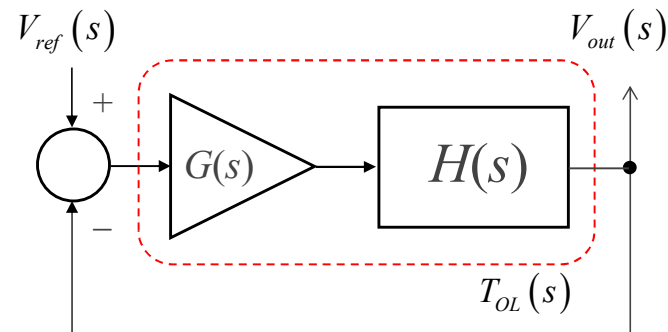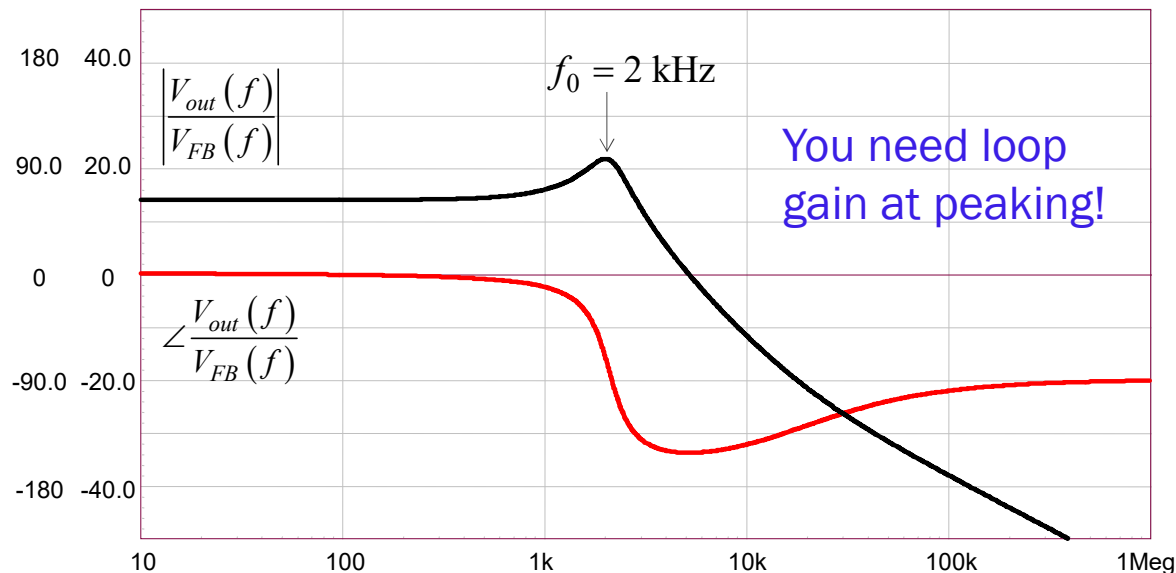- ❑ Before selecting a value, there are limits to respect




- ✓ You must have gain in the system at the perturbation frequency


- ❑ Crossover for a CCM VM buck must be: $3 \cdot f_0 < f_c < \frac{F_{sw}}{2}$
- ❖ In this example: $f_c > 6 \text{ kHz}$

Compensation in Current Mode is Easier

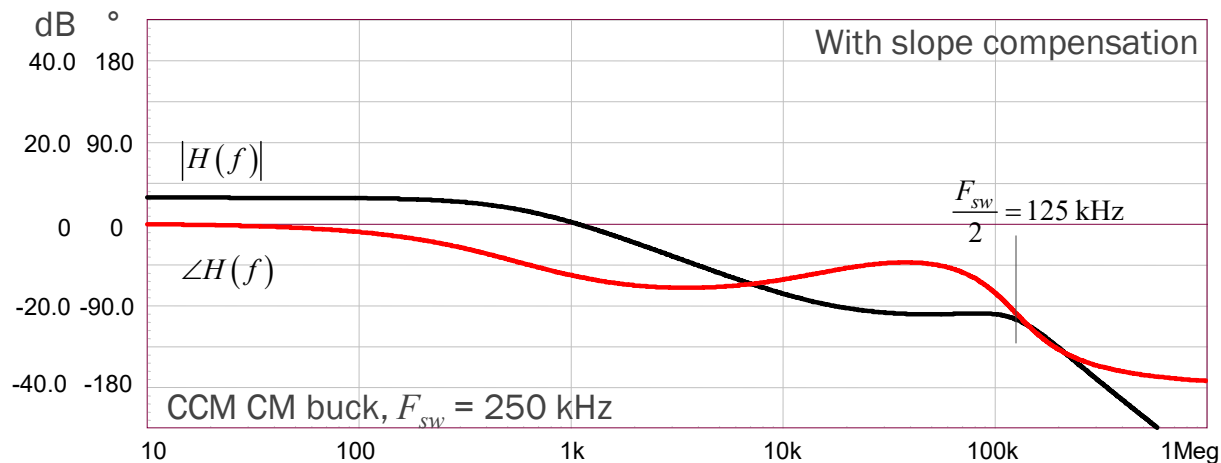- Once the poles are damped, the *theoretical* crossover limit is $F_{sw}/2$




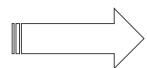
- ❖ Don't push f_c too far as it increases susceptibility to noise 🍷
- ❖ As f_c goes up, beware of various delays (conversion time, prop. del.)



Choose crossover to meet transient response, not more!

Approximating the Transient Response

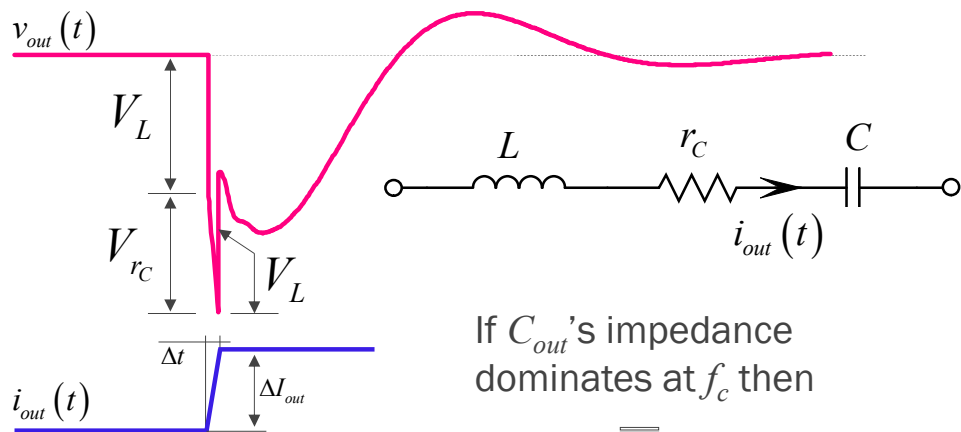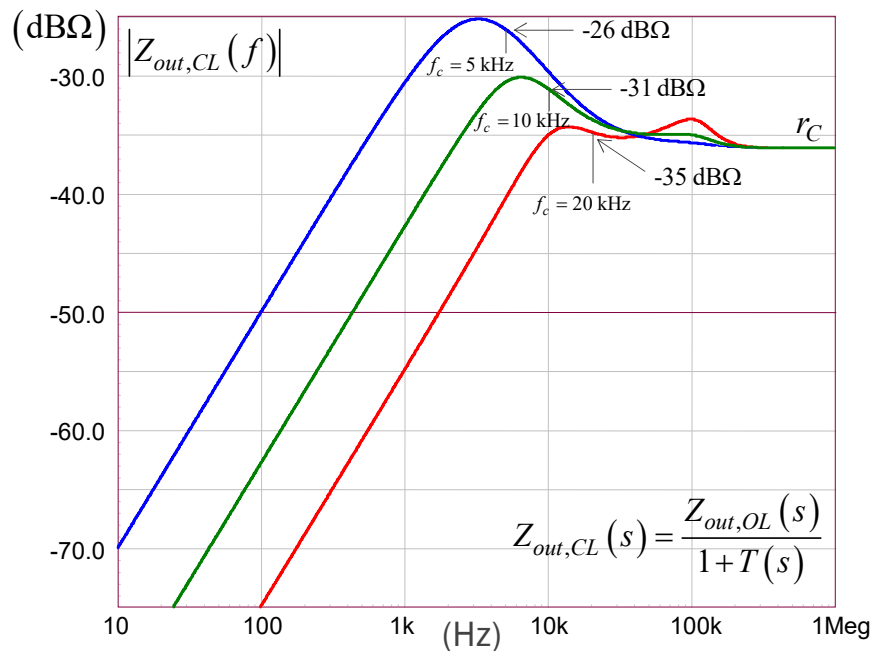□ The capacitor impedance at crossover dominates the output impedance



If C_{out} 's impedance dominates at f_c then


$$\Delta V_{out} \approx \frac{\Delta I_{out}}{2\pi f_c C_{out}}$$

□ As crossover increases, Z_{out} approaches the minimum set by r_C

$$r_C \ll \frac{1}{2\pi f_c C_{out}}$$


A Simple Guide to Crossover Selection

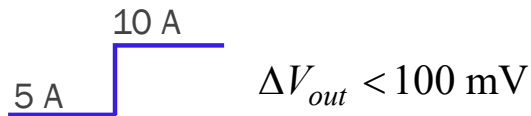- ❑ Select the output capacitor based on ripple current, ESR etc.
- ✓ Choose the crossover frequency to meet undershoot specs



$C_{out} = 560 \mu\text{F}$
 $r_C = 5 \text{ m}\Omega$
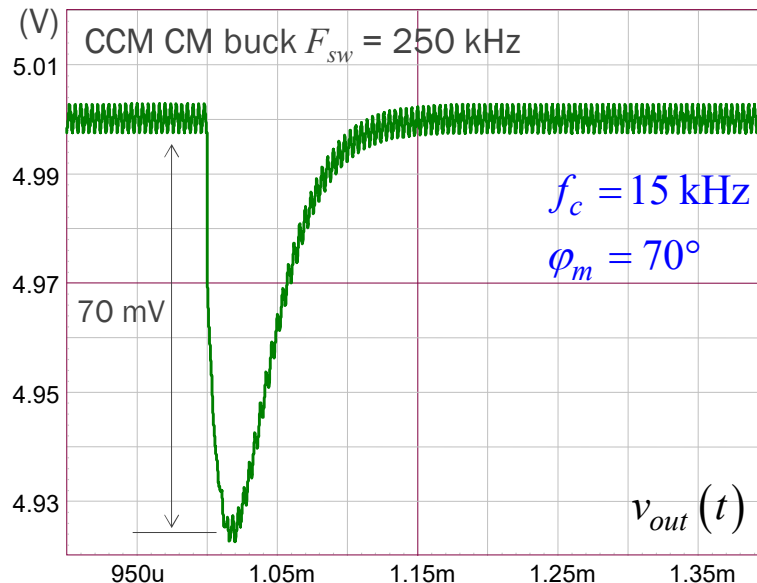
$$f_c \approx \frac{\Delta I_{out}}{2\pi C_{out} \Delta V_{out}} = 15 \text{ kHz}$$




- ❑ It surely is an approximation as the system is nonlinear but it's a guide




Stabilizing the Buck Converter Operated in Voltage Mode

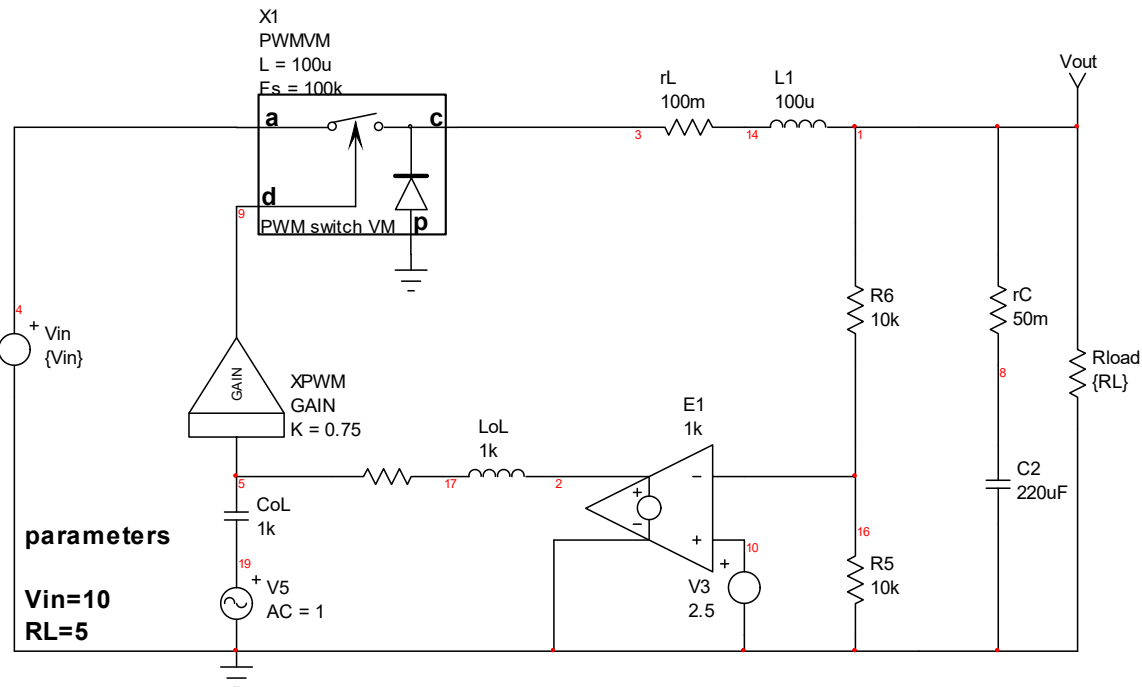□ Display the control-to-output transfer function with SPICE, SIMPLIS® etc...



Control to output – CCM VM

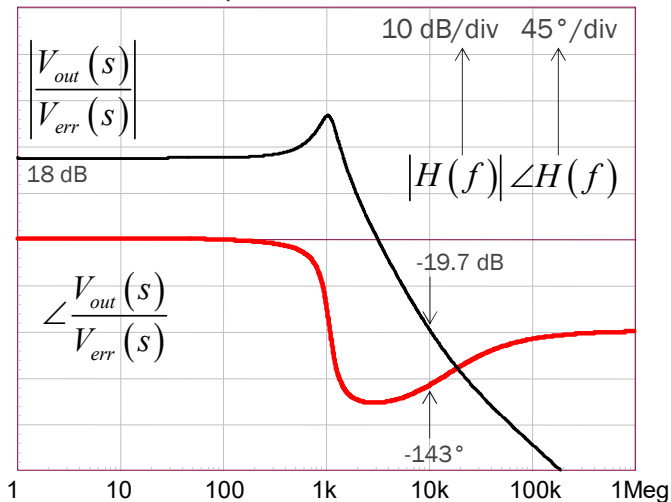

➤ Extract magnitude and phase data at 10 kHz: a type 3 is required

Place Poles and Zeros

- ✓ Place two coincident zeroes at the resonant frequency (1 kHz)
- ✓ Place the first pole to build phase margin
- ✓ Place the second pole at $F_{sw}/2$ to roll-off the gain at high frequency


parameters

Rupper=10k
 fc=10k
 Gfc=-19.6
 pfc=-143
 pm=70
 boost=pm-(pfc)-90
 G=10^{-(-Gfc/20)}
 pi=3.14159

$a = \sqrt{(fc^2/fp1^2)+1}$
 $b = \sqrt{(fc^2/fp2^2)+1}$
 $c = \sqrt{(fz1^2/fc^2)+1}$
 $d = \sqrt{(fc^2/fz2^2)+1}$
 $R2 = ((a*b)/(c*d))/(fp1-fz1) * Rupper * G * fp1$



fz1=1k
 fz2=1k
 $fp1 = fc / \tan((2 * \text{atan}(fc/fz1) - \text{atan}(fc/fp2)) - \text{boost} * \pi / 180)$
 fp2=50k

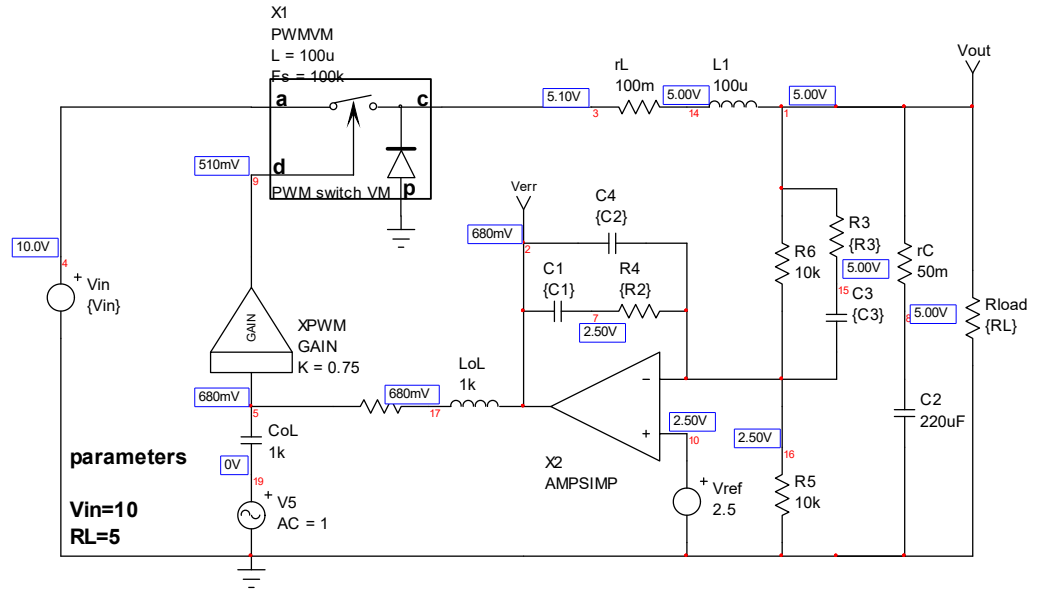$C1 = 1 / (2 * \pi * fz1 * R2)$
 $C2 = C1 / (C1 * R2 * 2 * \pi * fp1 - 1)$
 $C3 = (fp2 - fz2) / (2 * \pi * Rupper * fp2 * fz2)$
 $R3 = Rupper * fz2 / (fp2 - fz2)$



Check the Loop Gain in CCM and DCM

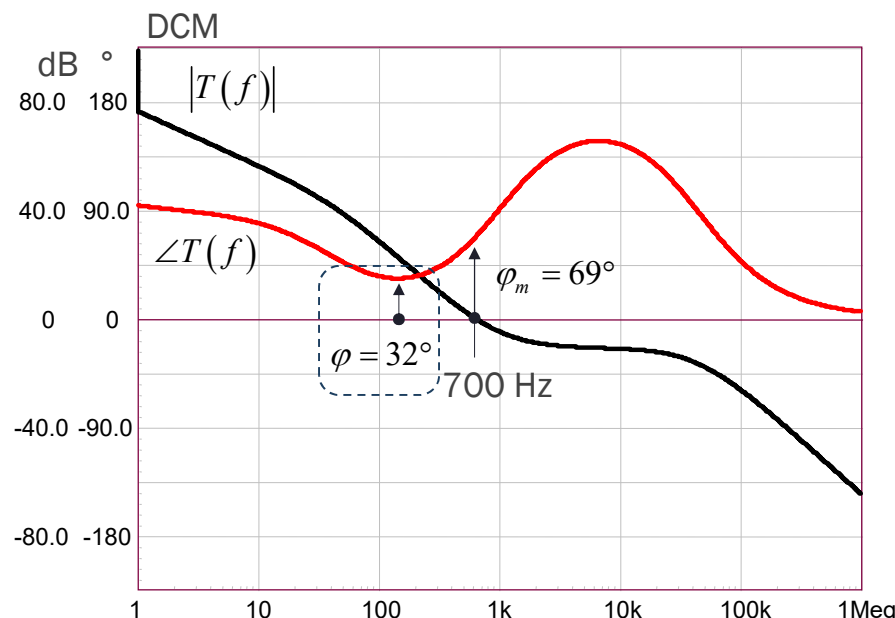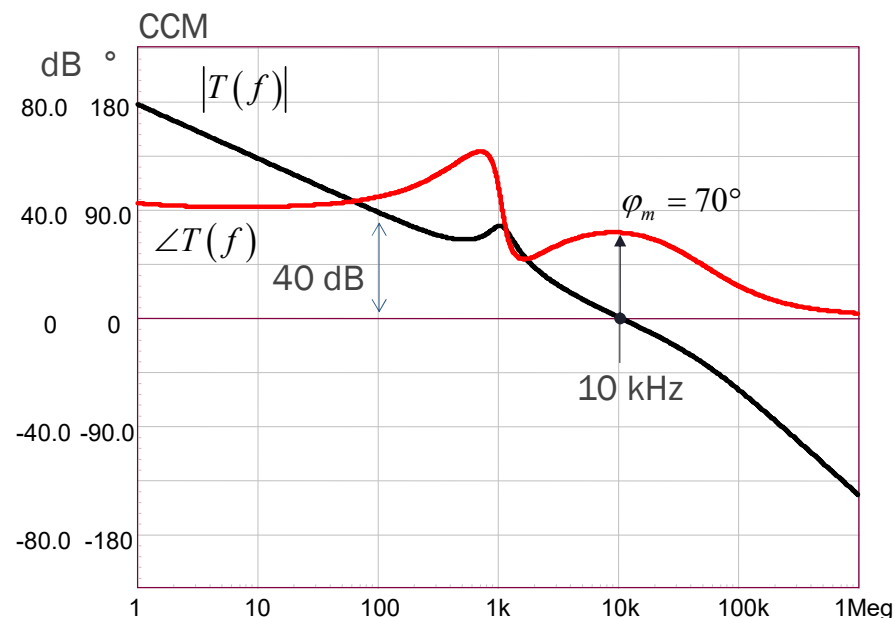❑ Reducing the load to 50 Ω forces discontinuous operation





➤ Loop gain changes in DCM: watch weak phase margin zone



Split the Zeroes to Improve the Phase Response

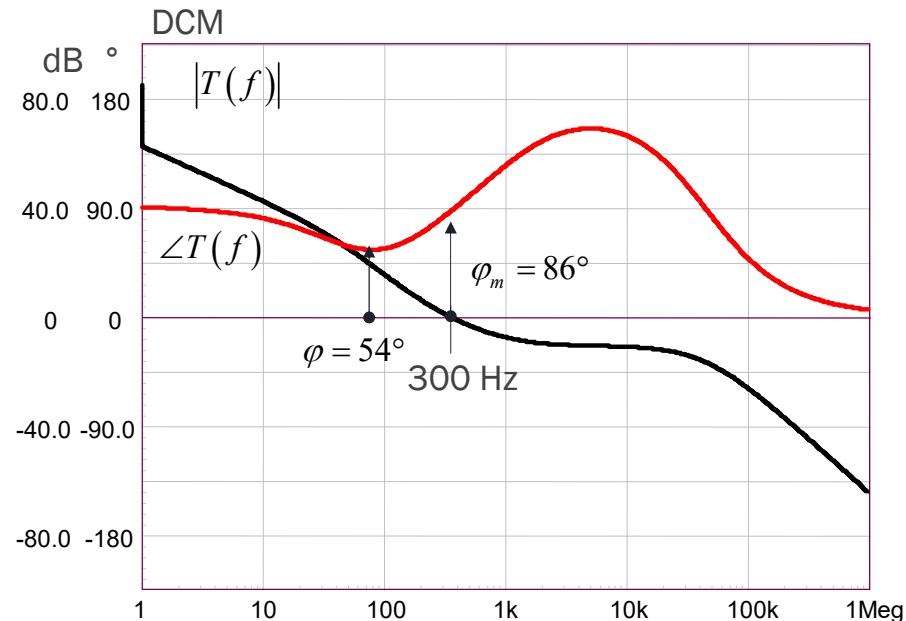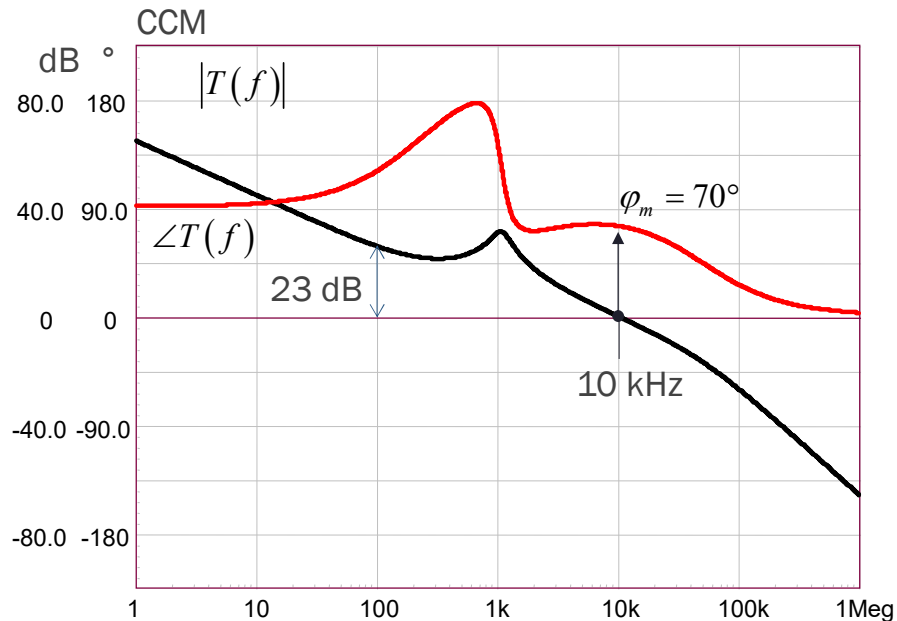
- Rather than two coincident zeroes, place one at f_0 and another at 200 Hz



- Lowering the zero with a constant f_c reduces the gain at low frequency

A Better Phase Margin in DCM Slows the Response

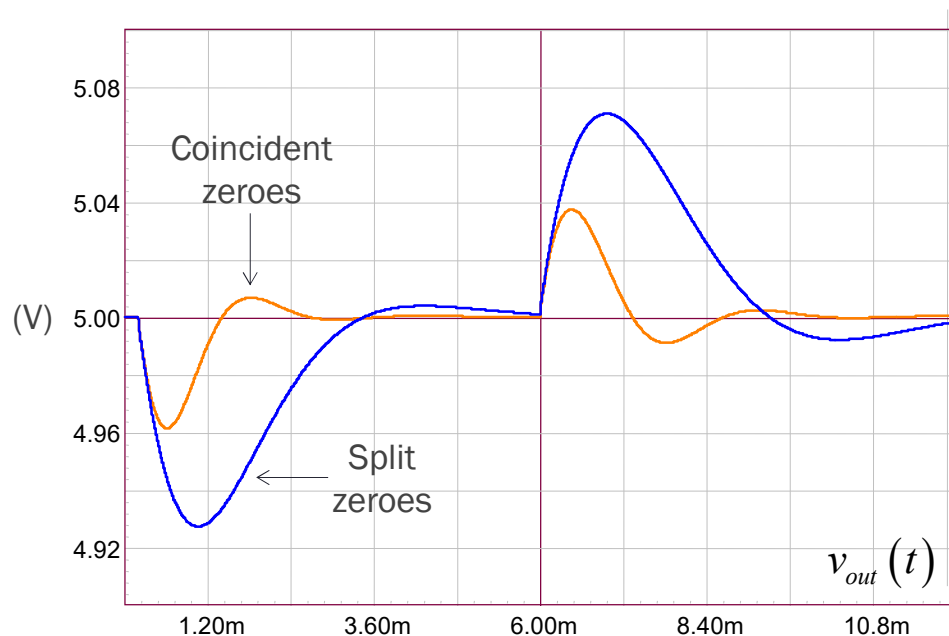- More pronounced undershoot with split zeroes and longer recovery




| | Frequency | Overshoot | Settling time | Phase margin |
|-----------|-----------|-----------|---------------|--------------|
| f_{z_1} | ↗ | ↗ | faster | ↘ |
| | ↘ | ↘ | slower | ↗ |
| f_{z_2} | ↗ | ↗ | faster | ↘ |


- Adjusting the second zero position changes the transient response

Stabilizing the Buck Converter Operated in Current Mode

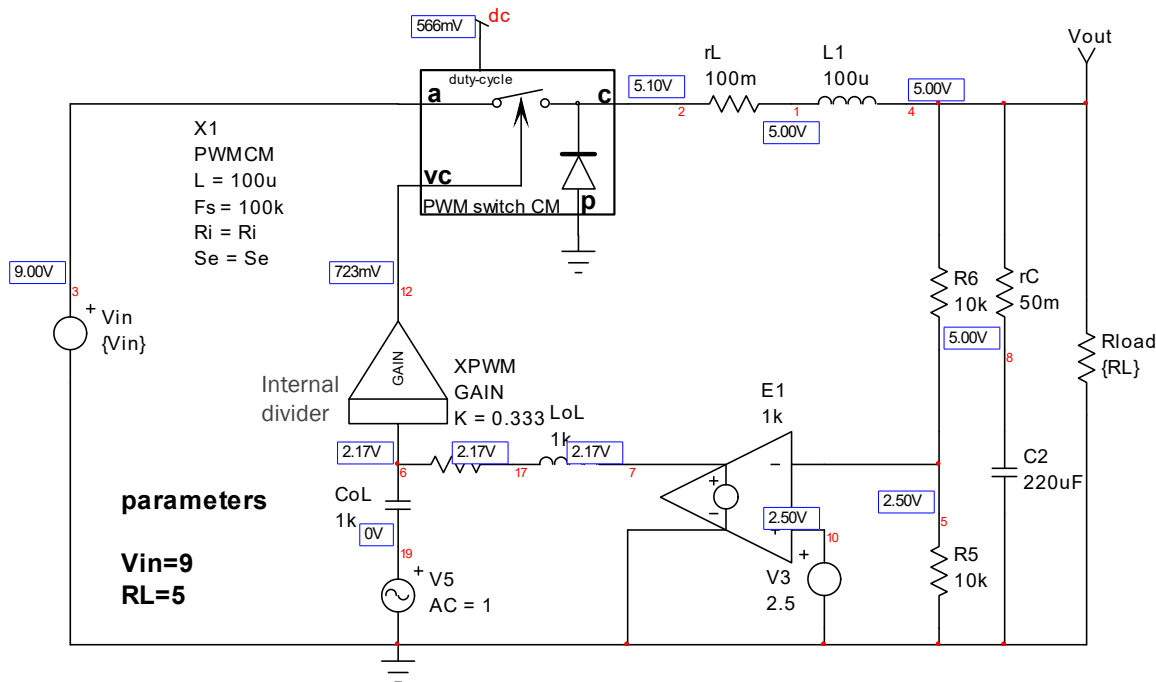□ Use the PWM switch to plot the control-to-output transfer function



Control to output - CCM CM

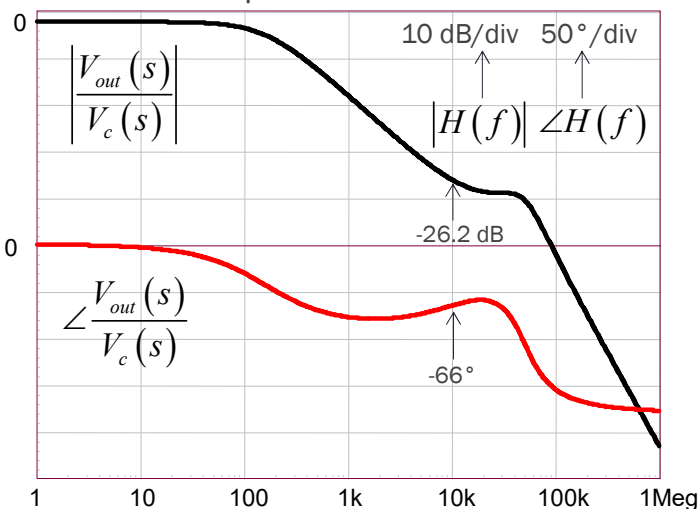

➤ Extract magnitude and phase data at 10 kHz: a type 2 is required

Pole and Zero to Compensate the CM Buck


- ❑ You can use the k-factor method in CM designs
- ✓ Zero and pole are spread to boost the phase at crossover
- ✓ The pole at the origin provides dc gain to minimize the static error

parameters

Rupper=10k
 fc=10k
 Gfc=-26.2
 pfc=66
 pm=70
 Se=20k
 Ri=600m

boost=pm-(pfc)-90


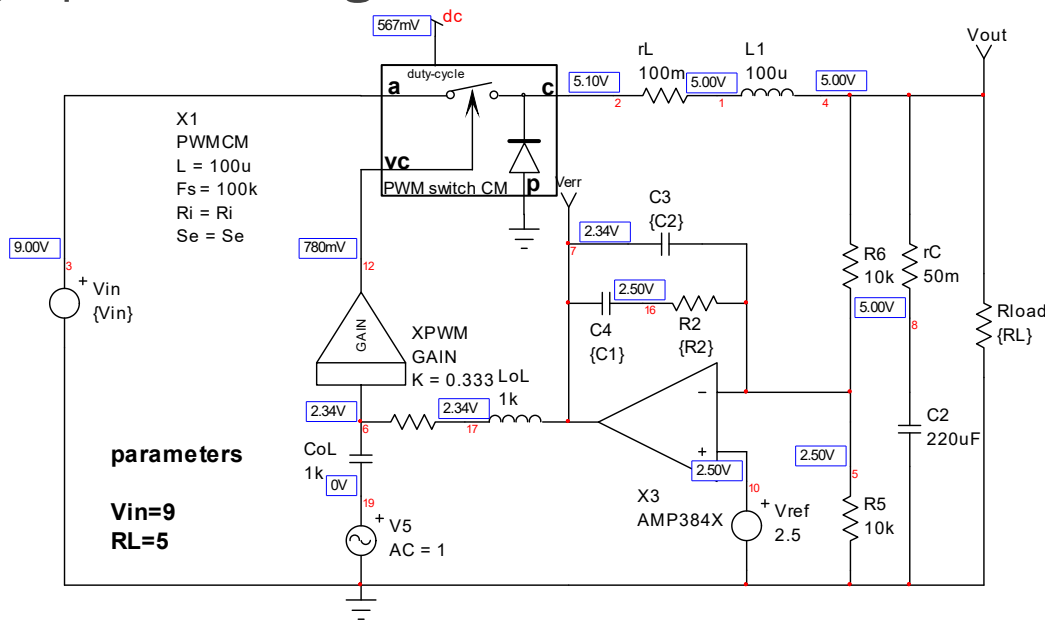
$G=10^{-(Gfc/20)}$
 boost=pm-(pfc)-90
 $\pi=3.14159$
 $K=\tan((\text{boost}/2+45)*\pi/180)$
 $C2=1/(2*\pi*fc*G*k*Rupper)$
 $C1=C2*(K^2-1)$
 $R2=k/(2*\pi*fc*C1)$



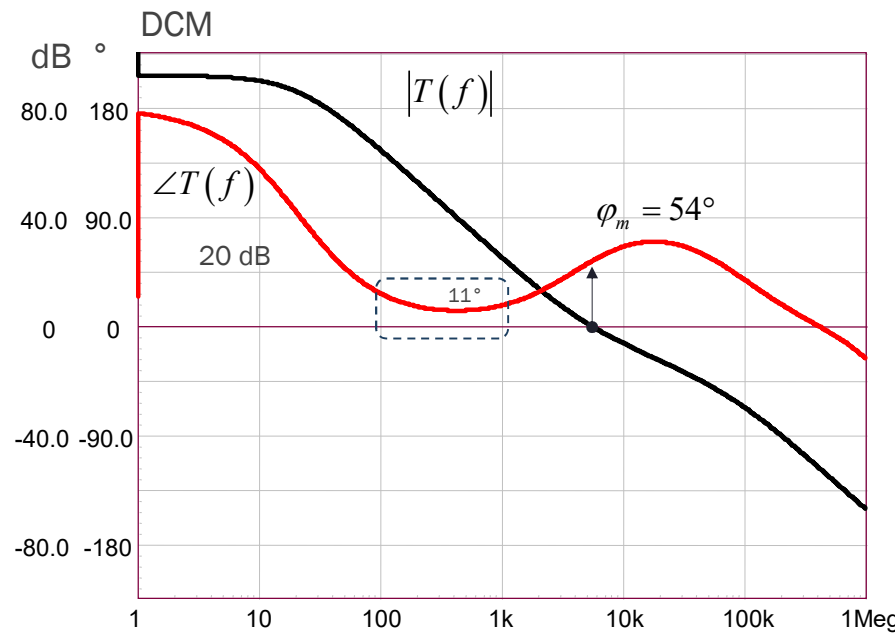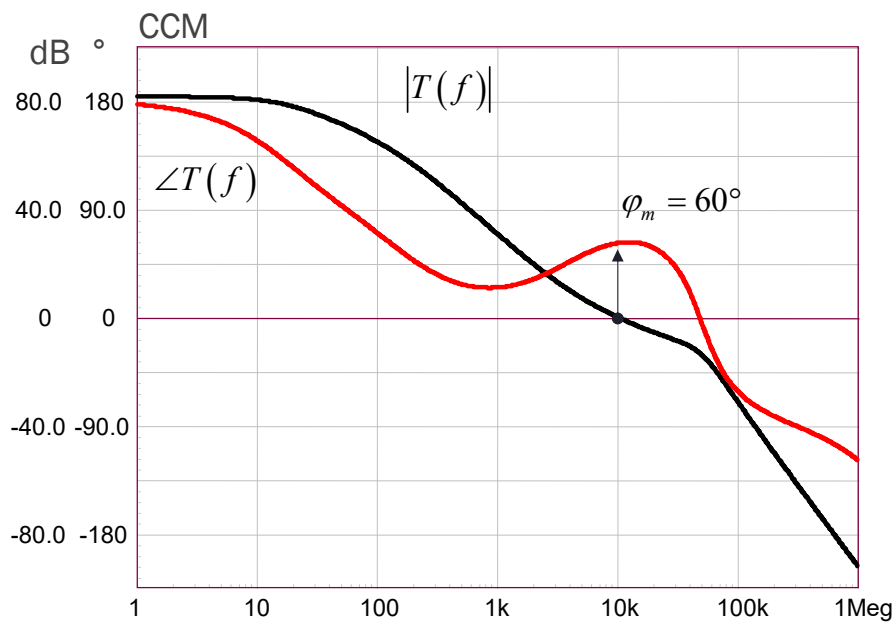D. Venable, *The k factor: A New Mathematical Tool for Stability Analysis and Synthesis*, Proceedings of Powercon 10, 1983, pp. 1-12

Check the Loop Gain in CCM and DCM

□ Crossover frequency does not significantly change in DCM



➤ Less loop gain impact in DCM: 20-dB margin in magnitude curve



Course Agenda


- The Buck Converter
- Control Schemes
- Introduction to Modeling
- The PWM Switch in Current-Mode Control
- Introduction to the Fast Analytical Techniques
- The Four Transfer Functions in CCM Current-Mode Control
- Compensation Strategy
- Prototype Measurements




Characterize your Components on the Bench

- ❑ Bench experiments are a mandatory step
- Are the assumptions adopted for the analytical model confirmed?
- Feed the model back with real measurements, refine simulations
- Check the behavior in temperature, particularly stability


❖ Capacitance change with bias voltage?

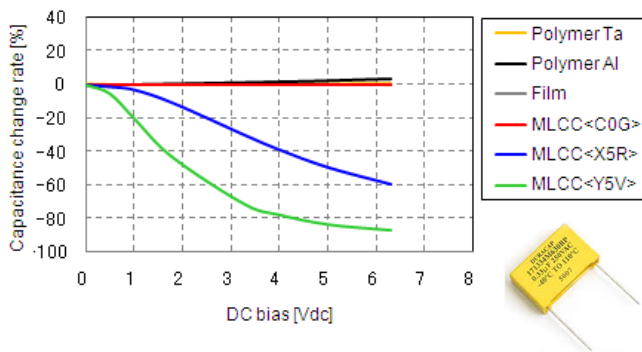

Characterization

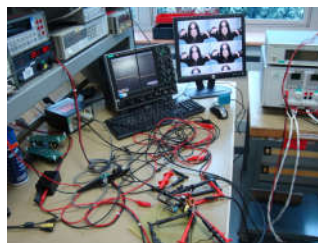


❖ Margin before inductor saturation?

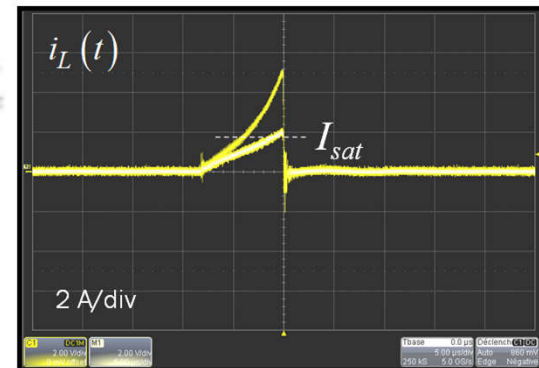

A Buck Converter in Voltage-Mode Control

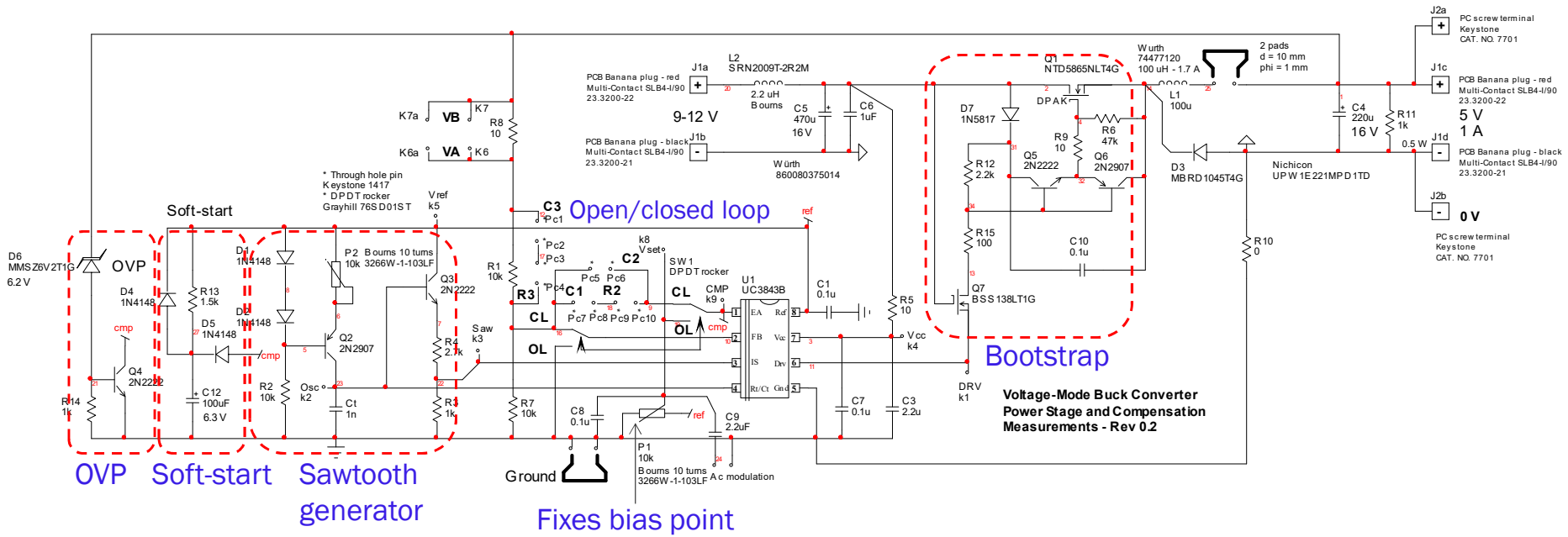☐ Turn the UC3843 into a voltage-mode controller




- ❖ The soft-start provides a smooth start-up sequence
- ❖ The OVP circuit protects the converter in open-loop operations



The Prototype in Voltage-Mode Control

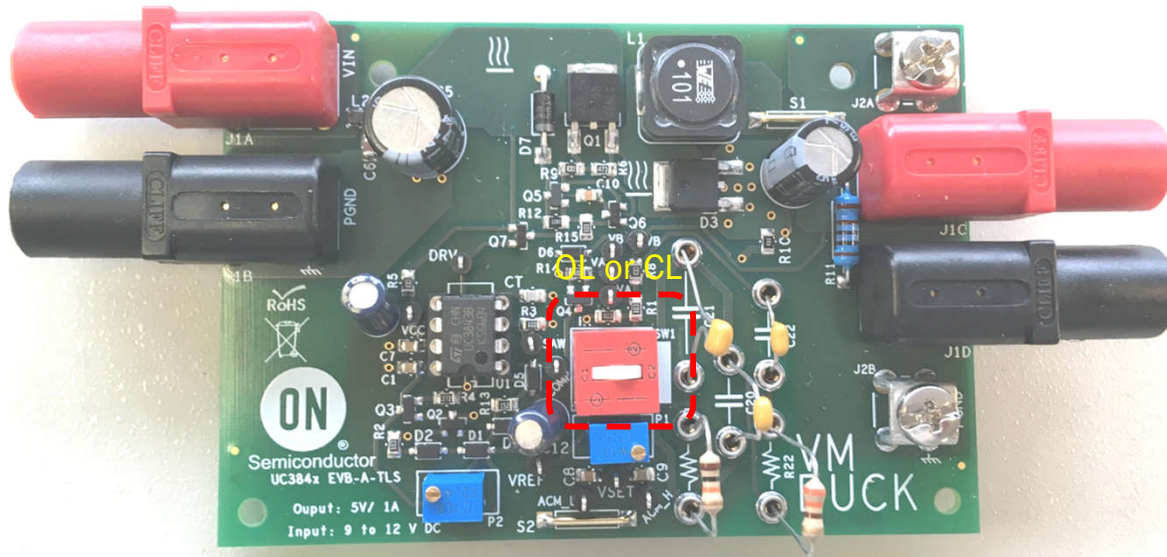
- The board allows the easy testing of various compensation strategies



- You can toggle between open- and closed-loop configurations

Extract the Control-to-Output Transfer Function

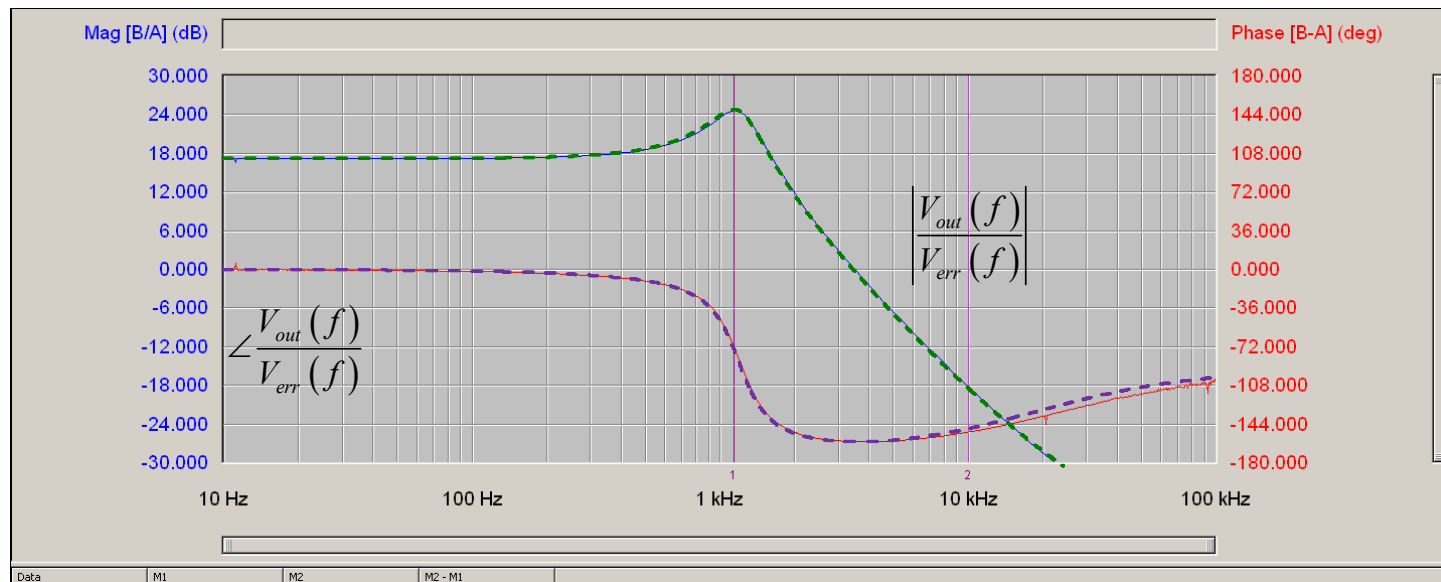- Simulation and bench experiments agree well with each other



I'll tell ya a little secret:
pay attention
to parasitics!




Mr Natural

- Good parasitics extraction is key to validate the model

Loop Gain after Compensation Strategy

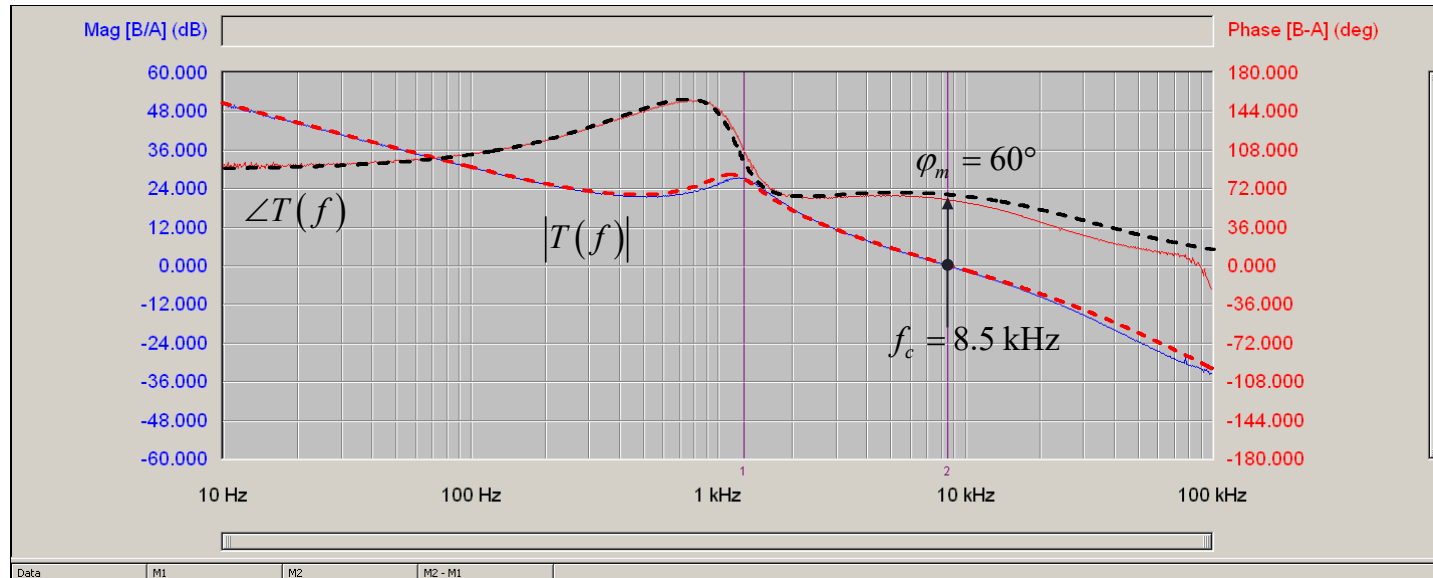
- The crossover frequency is slightly below 10 kHz, good phase margin




- This plot confirms the model is representative of the hardware

Transient Tests in Closed-Loop Conditions

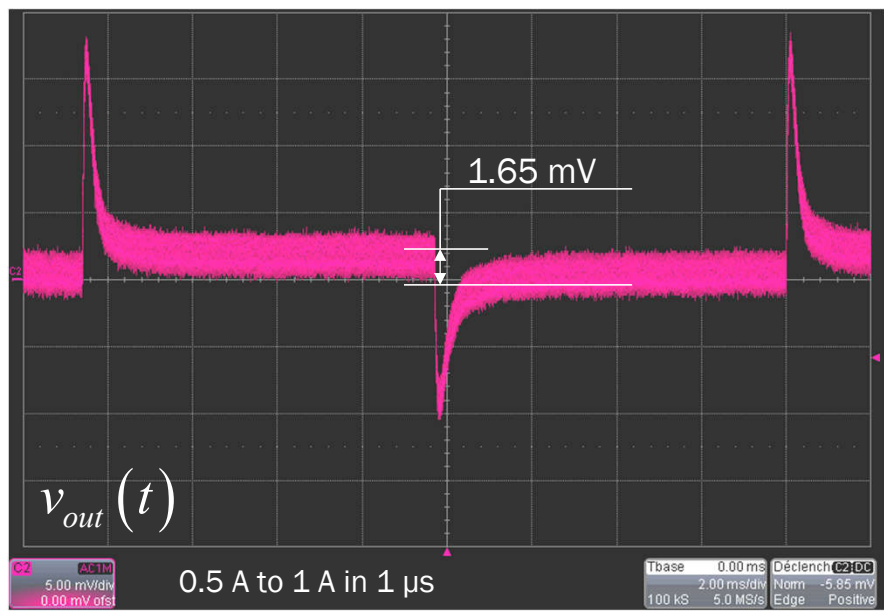□ The transient response is excellent and shows a low dc deviation



8.5-kHz crossover with 60° PM

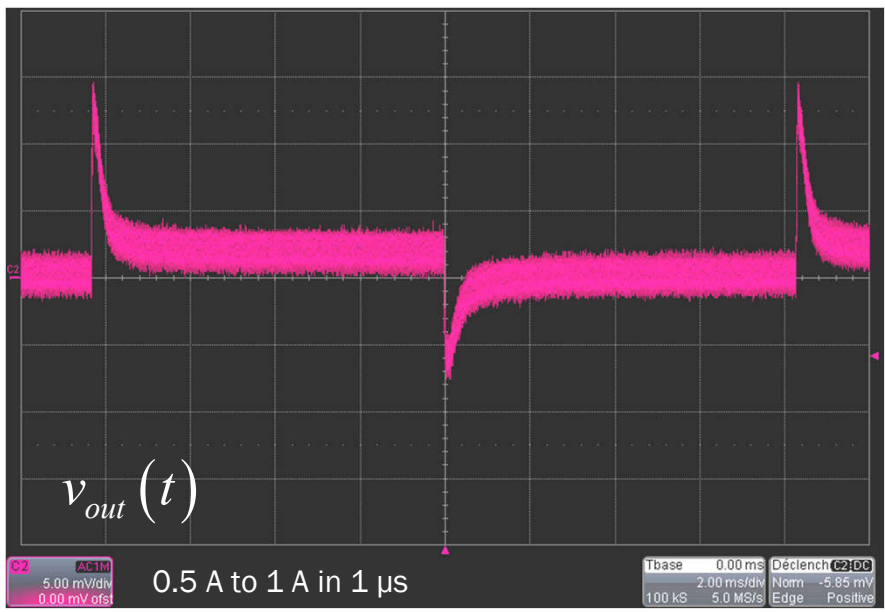



9.5-kHz crossover with 45° PM

➤ It's impossible to infer margins from transient tests: always go for Bode plot




No Gain, No Feedback!

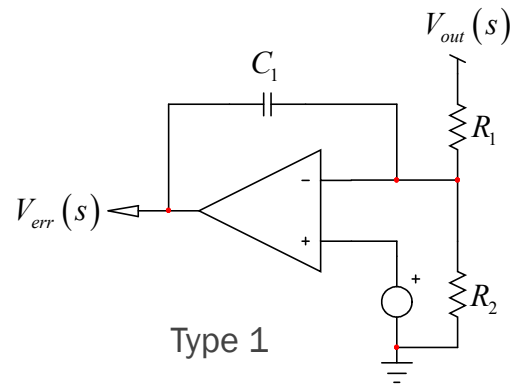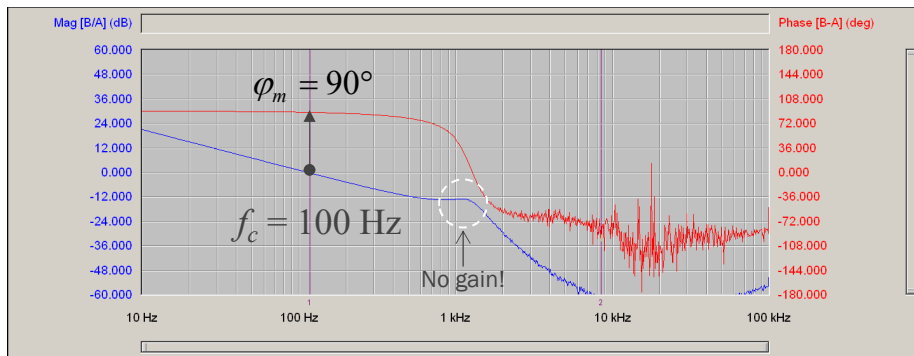- ❑ Wrongly selecting the crossover shows oscillations in the response



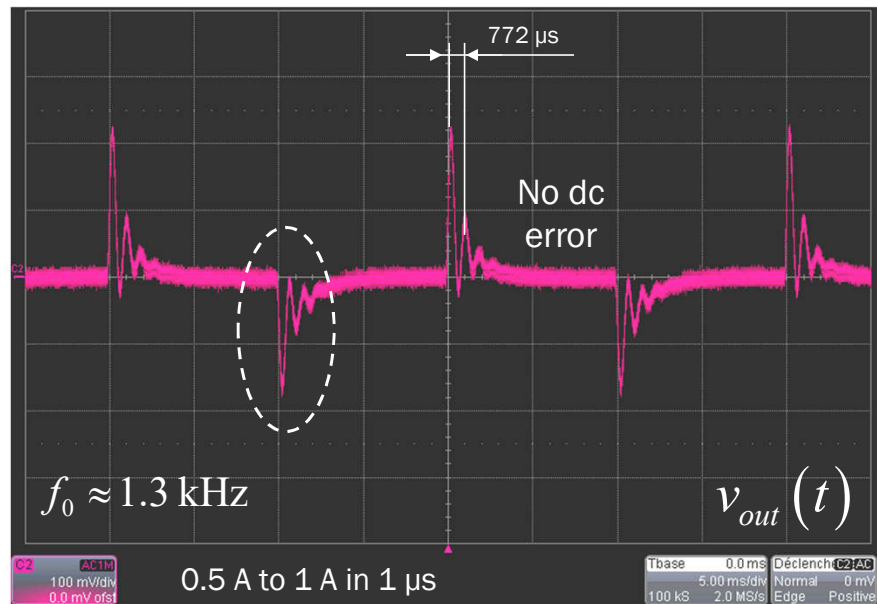
The system regulates well in dc but cannot fight the oscillations brought by the *LC* filter: increase crossover!



An output impedance magnitude plot would show the peaking

A Buck Converter in Current-Mode Control

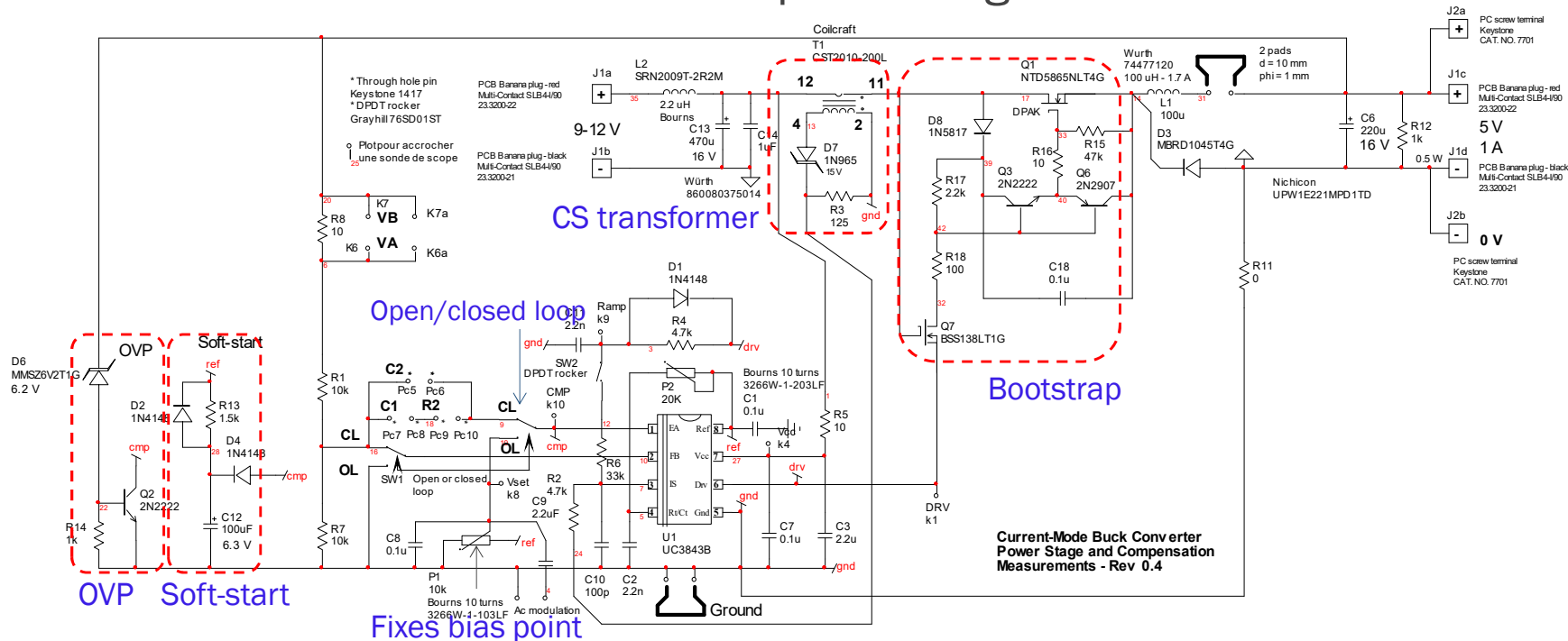□ The current mode architecture requires a high-side sense




➤ A current transformer references the inductor current to ground



The Prototype in Current-Mode Control

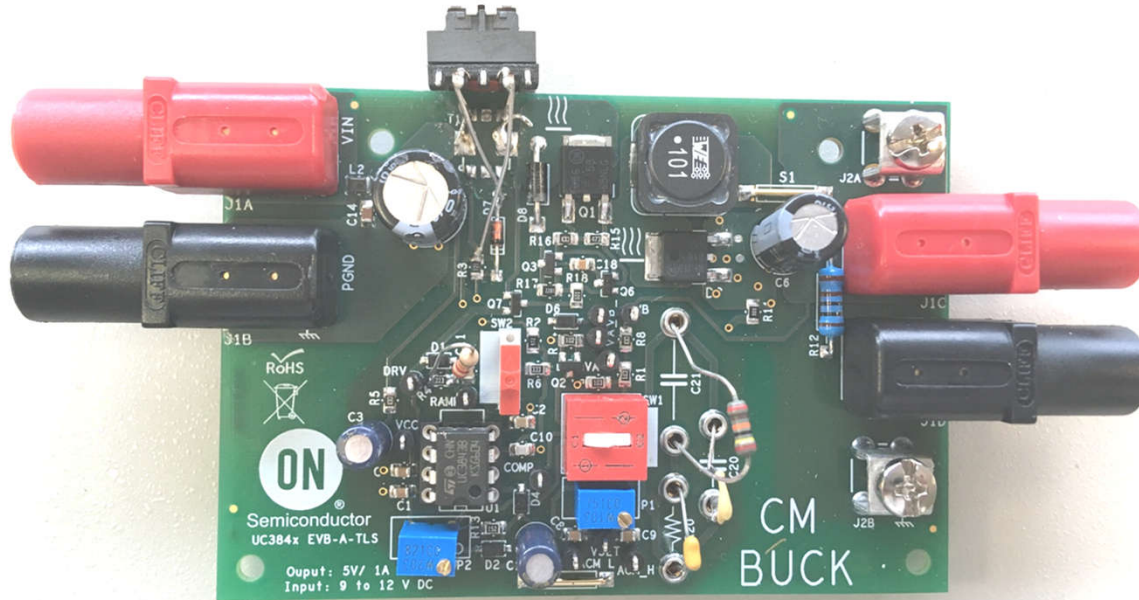
- A current sense transformer is now needed to sense $i_L(t)$



- You can toggle between open- and closed-loop configurations

Current Sense Transformer Operations

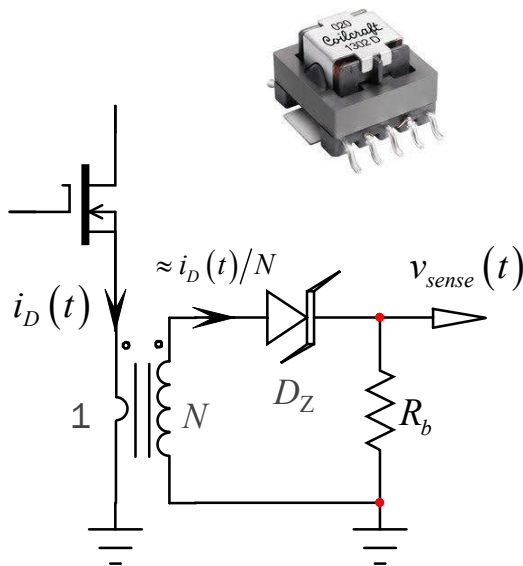- ❑ The current is scaled by the turns ratio and generate a sense voltage




$$V_{sense,max} = 1 \text{ V}$$

$$N = 100$$

$$I_{D,max} = 8 \text{ A}$$
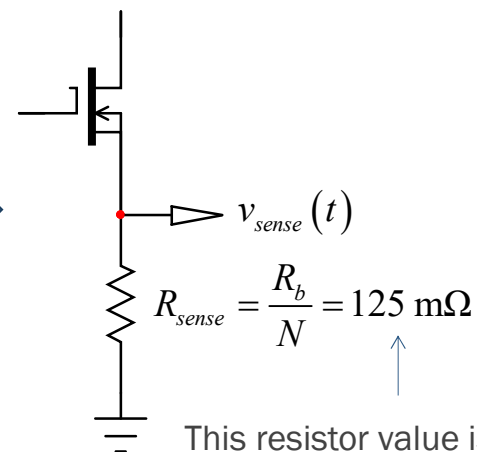
$$R_b = \frac{V_{sense,max}}{I_{D,max}} N = \frac{1}{8} 100 = 12.5 \Omega$$



This resistor value is passed to the model

- ❖ The equivalent resistance value is used for small-signal analysis



Current Sense Reset Scheme

- ❑ The transformer features a magnetization inductance
- Reset is mandatory




| Part No. | Turns Ratio | E-T Product (V·μs) | Ls ¹ (mH, min.) | Rs ² (Ω, max.) | Current Rating ⁵ (A) | Hi-Pot (V _{AC}) |
|----------|-------------|-----------------------|-------------------------------|------------------------------|------------------------------------|------------------------------|
| CT02-050 | 1:50 | 4.0 | 0.44 | 1.25 | 15.0 | 1500 |
| CT02-100 | 1:100 | 8.0 | 1.8 | 4.8 | 18.0 | 1500 |
| CT02-150 | 1:150 | 12.0 | 4.0 | 15.0 | 18.0 | 1500 |
| CT02-200 | 1:200 | 16.0 | 7.1 | 25.0 | 18.0 | 1500 |
| CT02-250 | 1:250 | 20.0 | 11.1 | 37.2 | 18.0 | 1500 |
| CT02-300 | 1:300 | 24.0 | 15.0 | 55.0 | 18.0 | 1500 |

$$V_{mag} D_{max} T_{sw} = V_{reset} (1 - D_{max}) T_{sw} \quad \text{max V.s}$$

$$V_{mag} D_{max} T_{sw} = (V_{sense,max} + V_f) D_{max} T_{sw} \quad [\text{V} \cdot \mu\text{s}]$$



$$\Rightarrow V_{reset} = \frac{V_{mag} D_{max}}{1 - D_{max}}$$

← The Zener diode provides the reset

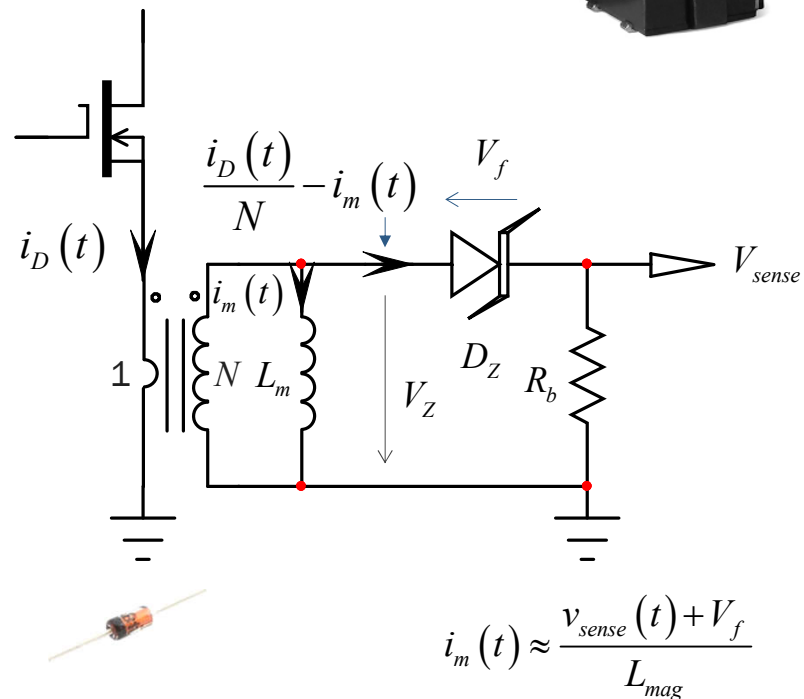

Watch for the Magnetizing Current

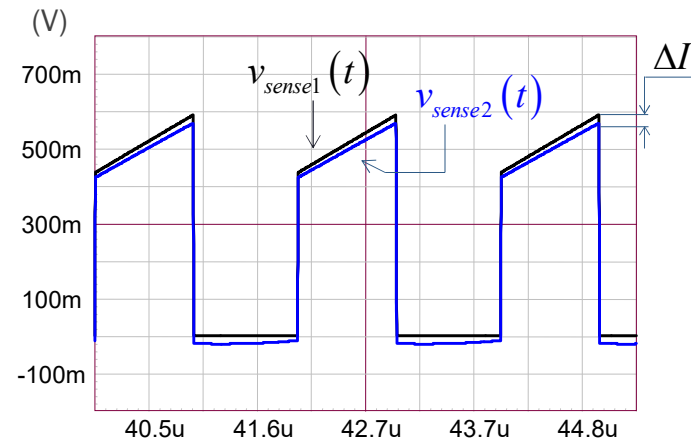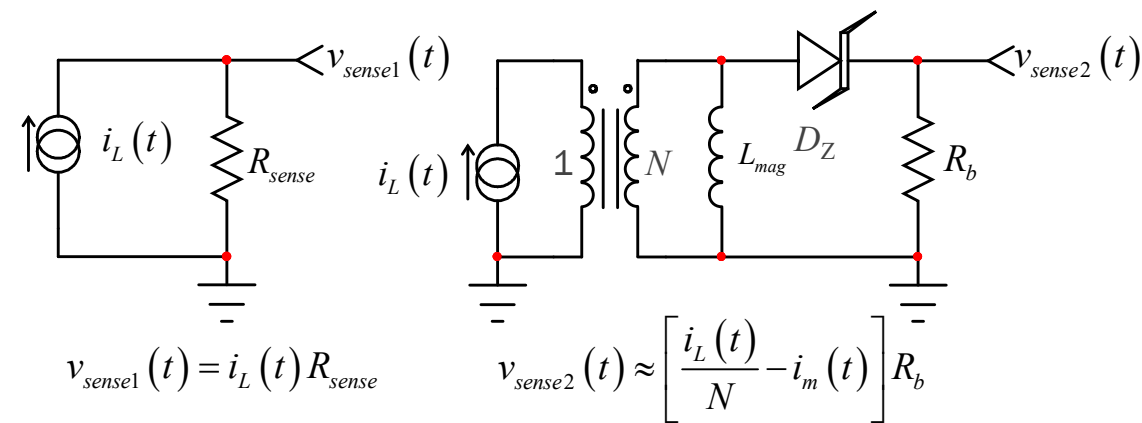□ The magnetizing current can affect the precision



➔

$$\Delta I(\%) = \frac{V_{CS} + V_f}{L_{mag}} DT_{sw} \frac{V_{CS}}{R_b} \times 100$$

Check the magnetizing inductance value to minimize this error

V_{CS} is the maximum voltage sense limit


The Magnetizing Current Affects Compensation

- ❑ The magnetizing current subtracts from the monitored current
- A *wrongly-selected* current transformer can bring instabilities

On-time slope
$$S_n = \frac{V_{in} - V_{out}}{L} \frac{R_b}{N}$$


Compensation slope
$$S_a = [\text{V/s}]$$

Magnetizing slope
$$S_m = \frac{V_f + V_{CS}}{L_m} R_b$$




$$S_{tot} = S_n - S_m + S_a$$

Can affect slope compensation

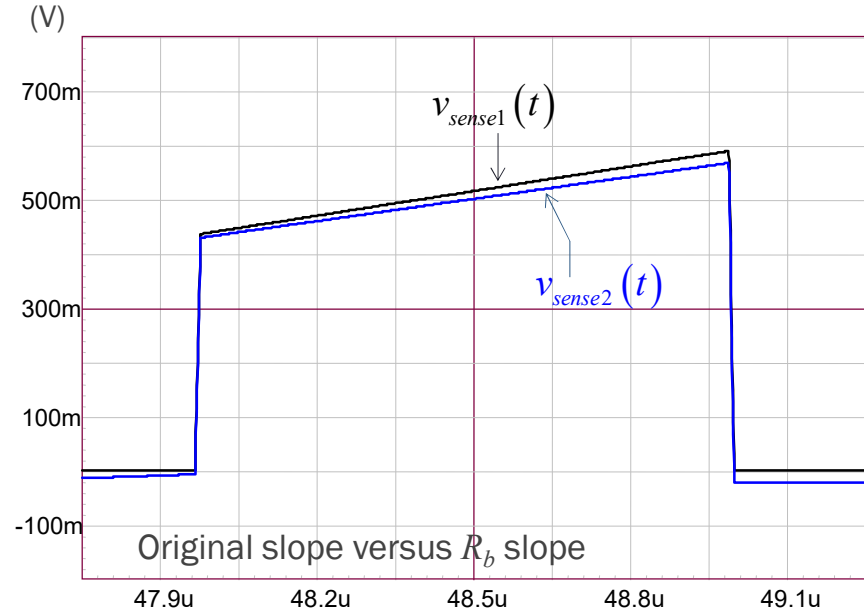

Extract the Plant Control-to-Output Transfer Function

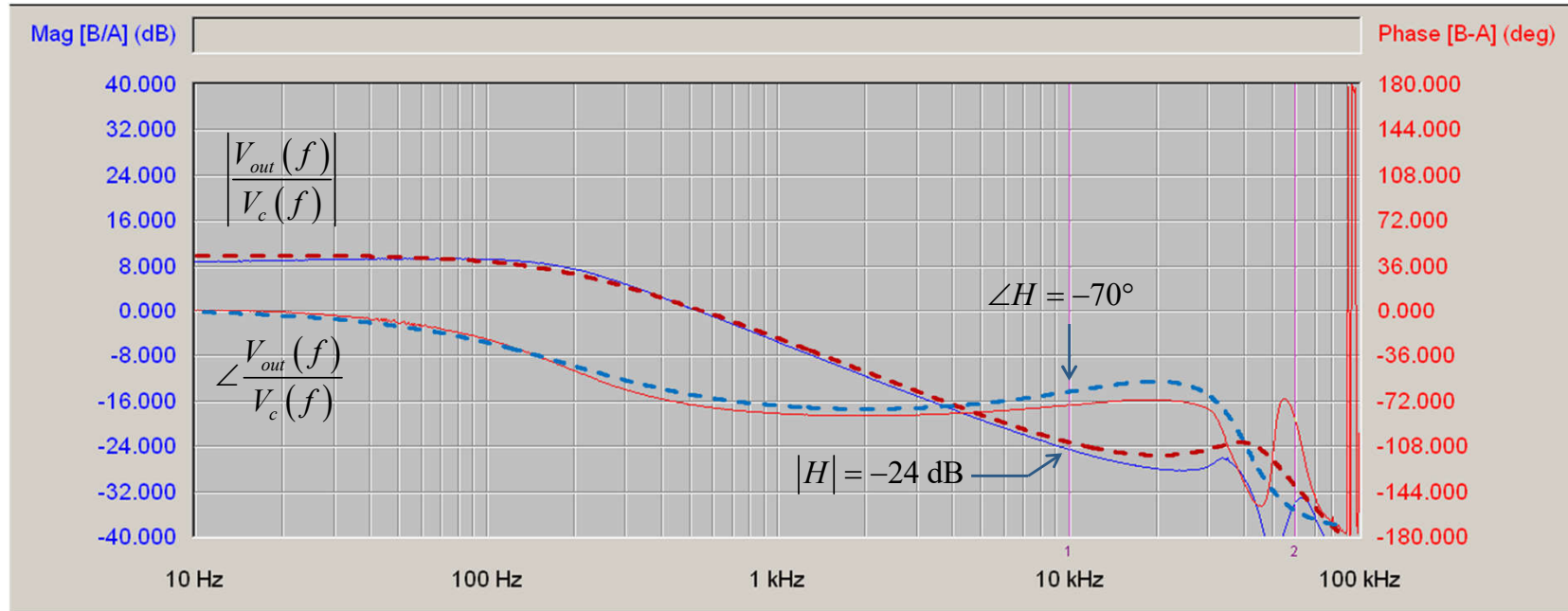
- ❑ Simulation and bench experiments show some discrepancies



- Probably a better parasitic extraction is needed from the components

Loop Gain of the Current-Mode Buck Converter

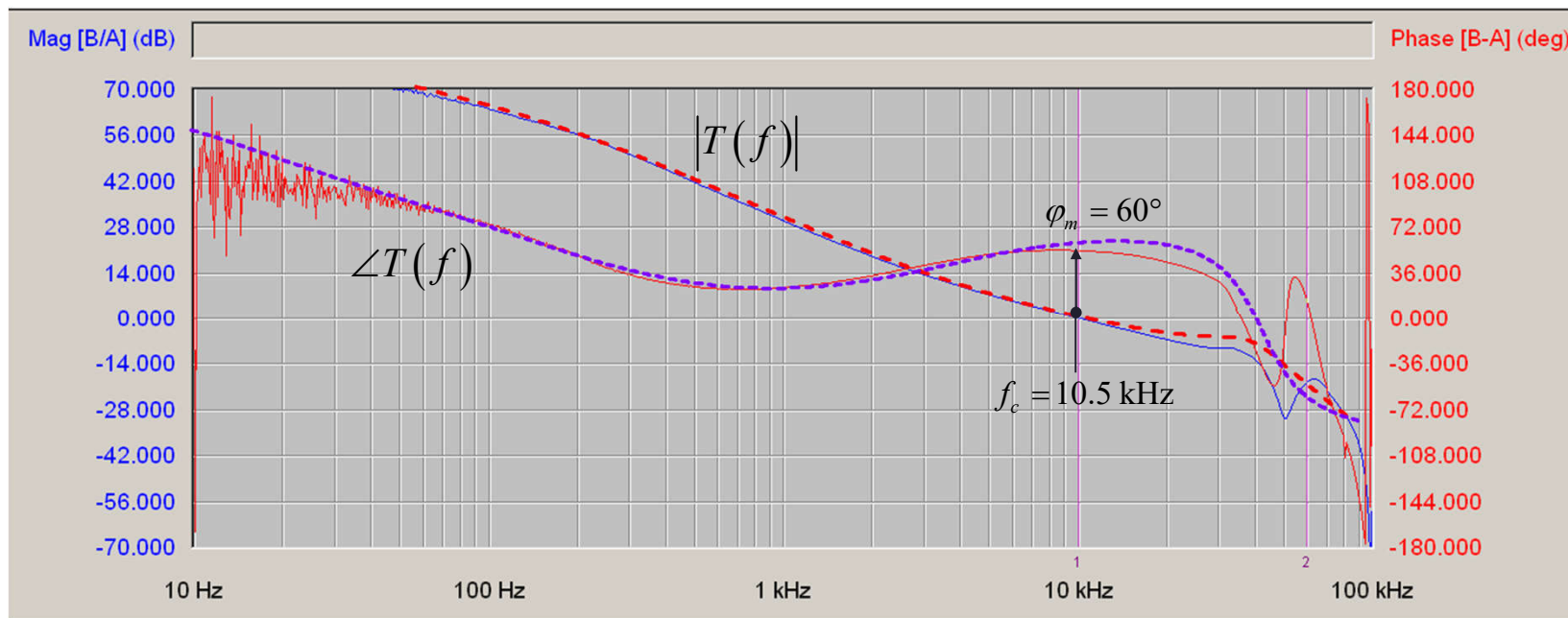
- The crossover frequency is slightly above 10 kHz, good phase margin




- A large dc gain induces a low output static error

Predicting the Transient Response Dropout

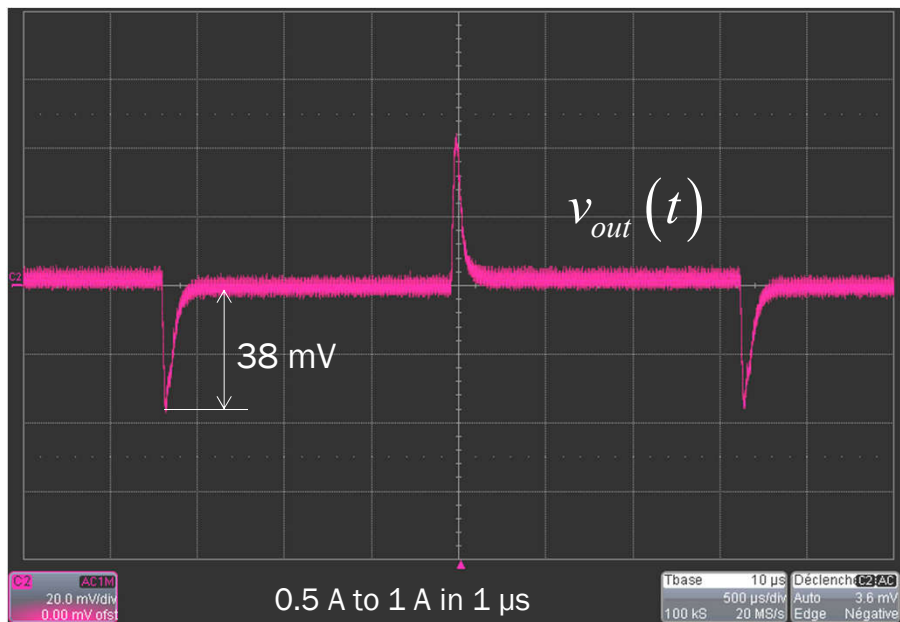
□ The transient tests confirm a stable converter


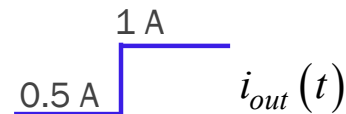
$$V_{in} = 9 \text{ V}, f_c = 10.5 \text{ kHz}, \text{PM} = 60^\circ$$


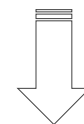
$$C_{out} = 220 \mu\text{F}$$
$$r_C = 50 \text{ m}\Omega$$




Approximate
expression

$$\Delta V_{out} \approx \Delta I_{out} \frac{1}{2\pi f_c C_{out}} = 34 \text{ mV}$$


Instability in Discontinuous Conduction Mode

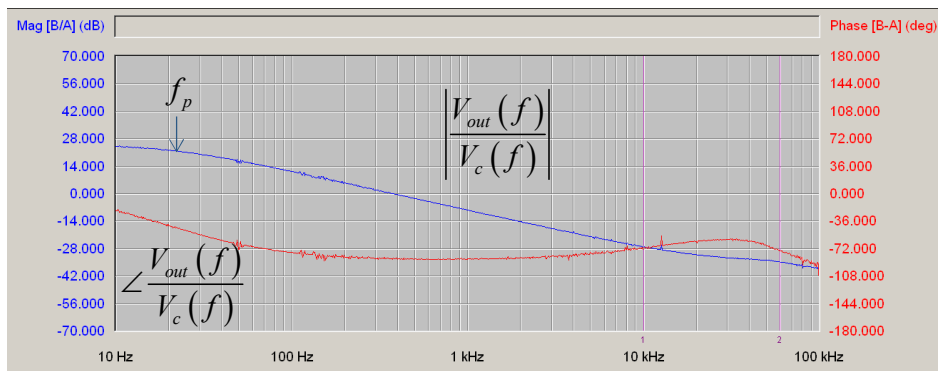□ As M approaches 0.666, the pole goes to lower frequency



Current mode:
 $V_{in} = 14 \text{ V}$
 $V_{out} = 5.8 \text{ V}$
 $R_{load} = 80 \Omega$
 DCM operation

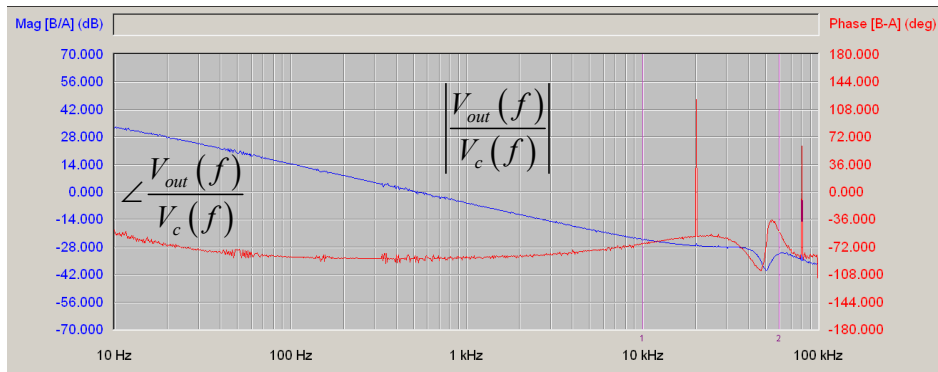Inject slope
 compensation
 to stabilize
 the converter



Current mode:
 $V_{in} = 9.55 \text{ V}$
 $V_{out} = 5.6 \text{ V}$
 $R_{load} = 80 \Omega$
 DCM operation

$$S_a > 0.086 \cdot S_{off}$$

B. Erickson, D. Maksimović, *Fundamentals of Power Electronics*, 2nd edition, Springer



Conclusion

- ❑ The buck converter can be operated with different schemes
- ❖ Current-mode control is the most popular technique
- ❑ Modeling still sees new emerging techniques
- ❖ The PWM switch model is truly the simplest approach
- ❖ You can improve models by accounting for harmonics
- ❑ The FACTs are an efficient tool to determine transfer functions
- ❖ Analytical analysis gets you the insight on who does what?
- ❑ Slope compensation is necessary in current-mode CCM
- but also in DCM for the buck converter to keep stability
- ❑ As usual, analytical analysis + simulation + bench prototype = success!



Merci !
Thank you!
Xiè-xie!