



ON Semiconductor®

Analytical Analysis and Small-Signal Modeling of a QR Power Converter

Christophe Basso

IEEE Senior Member

Course Agenda

- ❑ What is a QR Converter?
- ❑ Deriving Operating Conditions
- ❑ The Over Power Problem
- ❑ Three Operating Modes
- ❑ Small-Signal Analysis – QR
- ❑ Small-Signal Analysis – VCO
- ❑ Compensating with TL431
- ❑ Control Loop Design Example
- ❑ Conclusion





Course Agenda

- ❑ **What is a QR Converter?**
- ❑ Deriving Operating Conditions
- ❑ The Over Power Problem
- ❑ Three Operating Modes
- ❑ Small-Signal Analysis – QR
- ❑ Small-Signal Analysis – VCO
- ❑ Compensating with TL431
- ❑ Control Loop Design Example
- ❑ Conclusion




Why QR Operation?

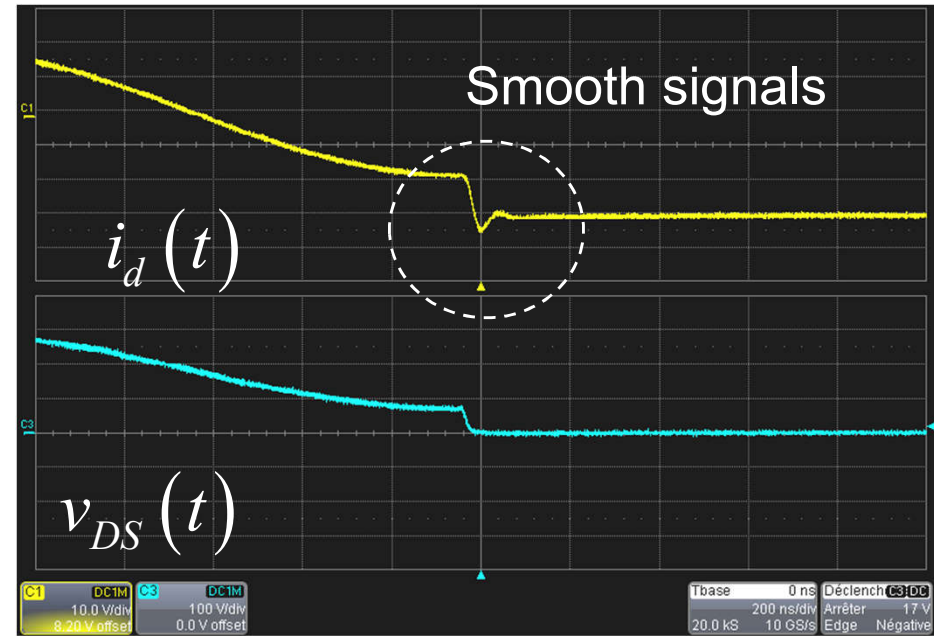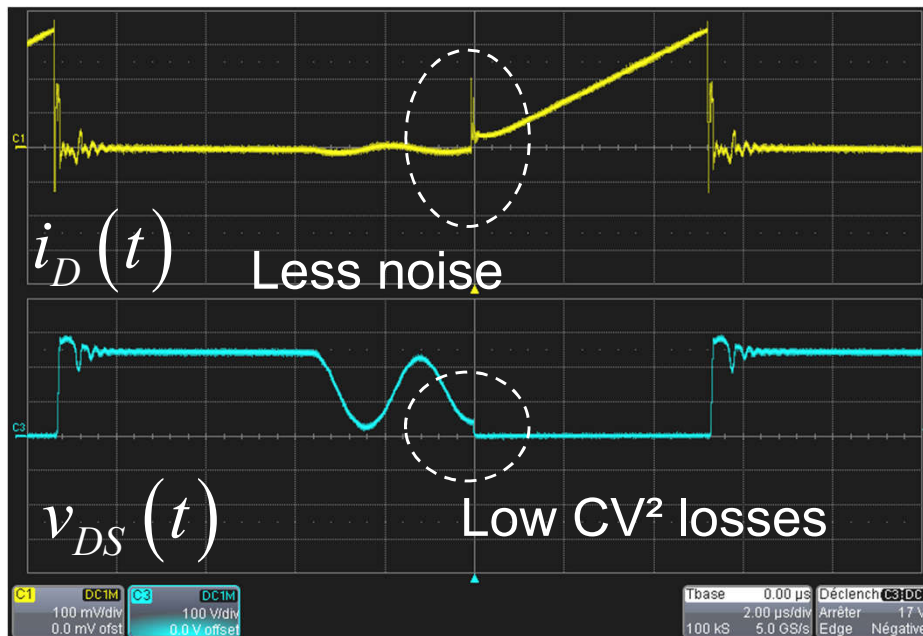- ❑ More converters are using variable-frequency operation
- ❑ This is known as Quasi-Square Wave Resonant mode: QR
 - Valley switching ensures extremely low capacitive losses
 - DCM operation saves losses on the secondary diode
 - Easier synchronous rectification
 - The Right Half-Plane Zero is pushed to high frequencies




What is the Principle of Operation?

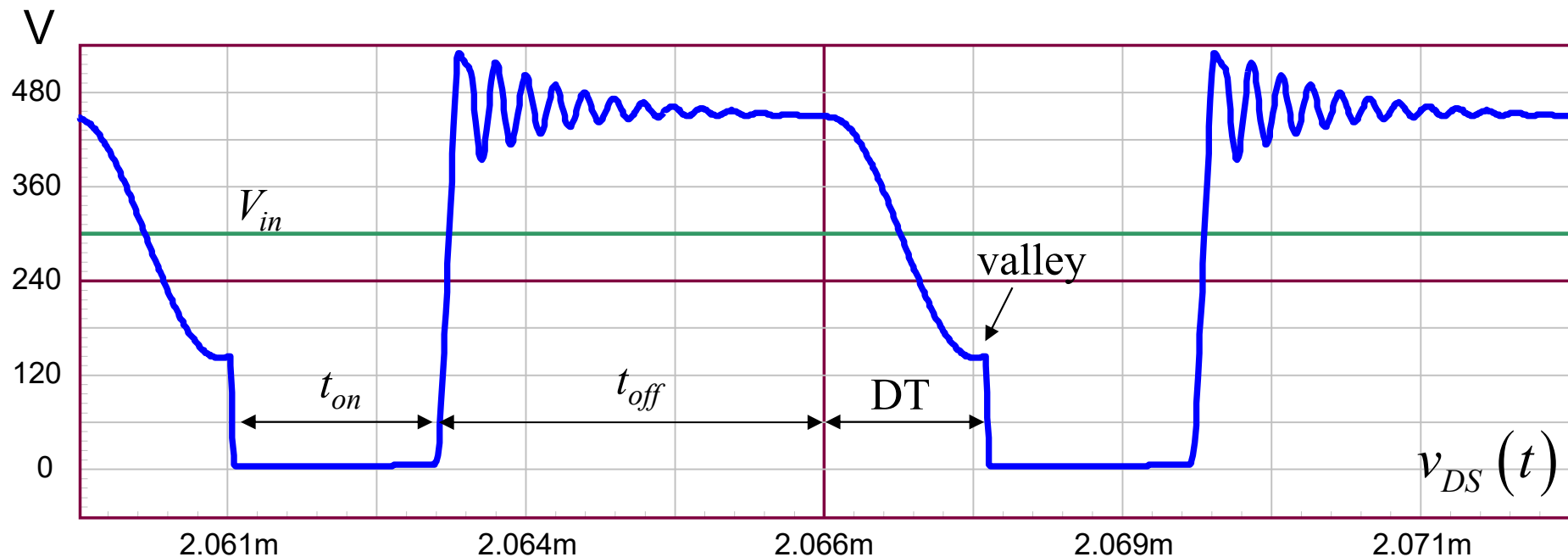- ❑ The drain-source signal is made of peaks and valleys
- ❑ A valley presence means:
 - The drain is at a minimum level, capacitors are naturally discharged
 - The converter is operating in the discontinuous conduction mode





A QR Circuit Does not Need a Clock

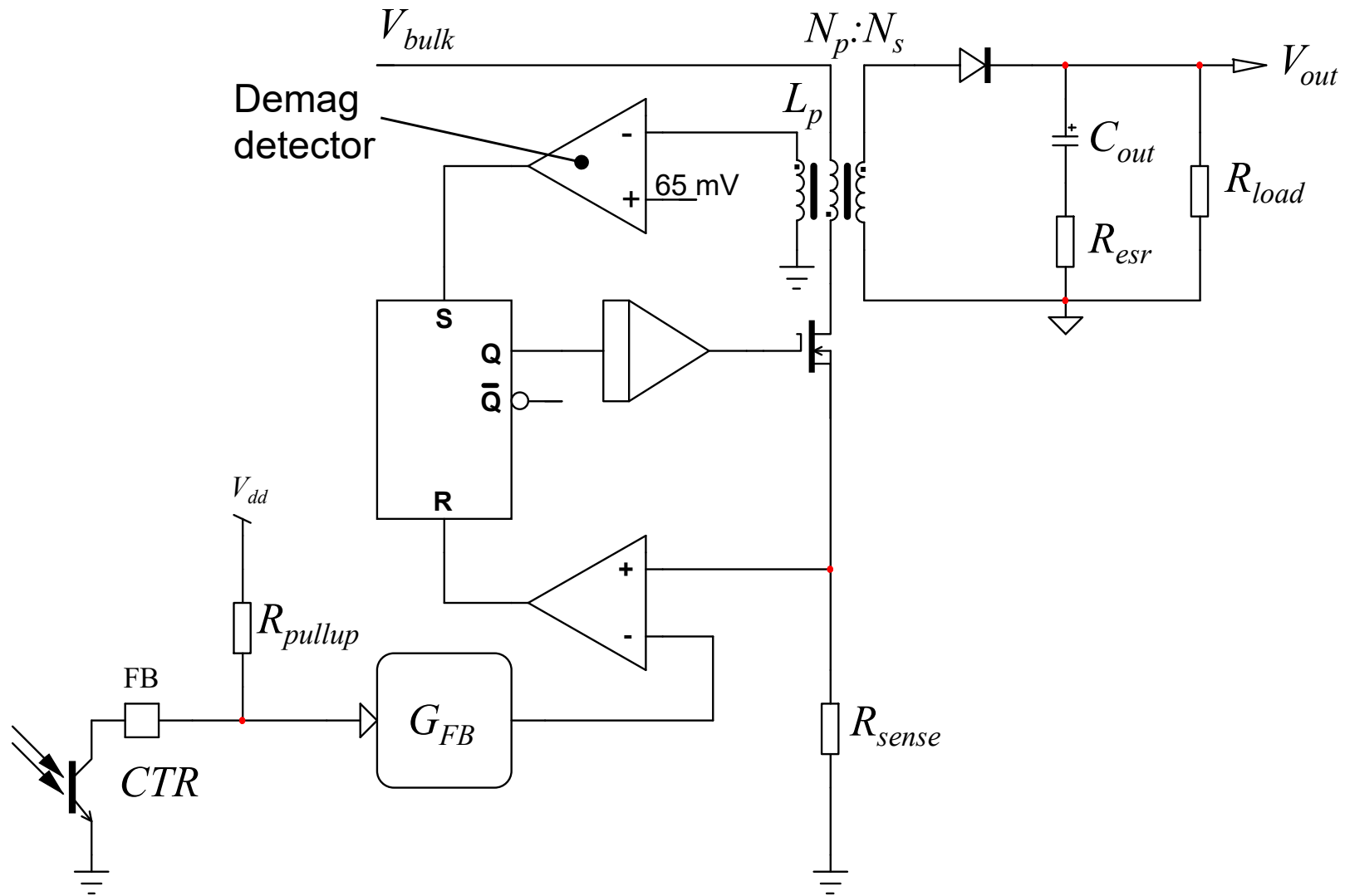- ❑ The system is a self-oscillating current-mode converter




A Winding is Used to Detect Core Reset

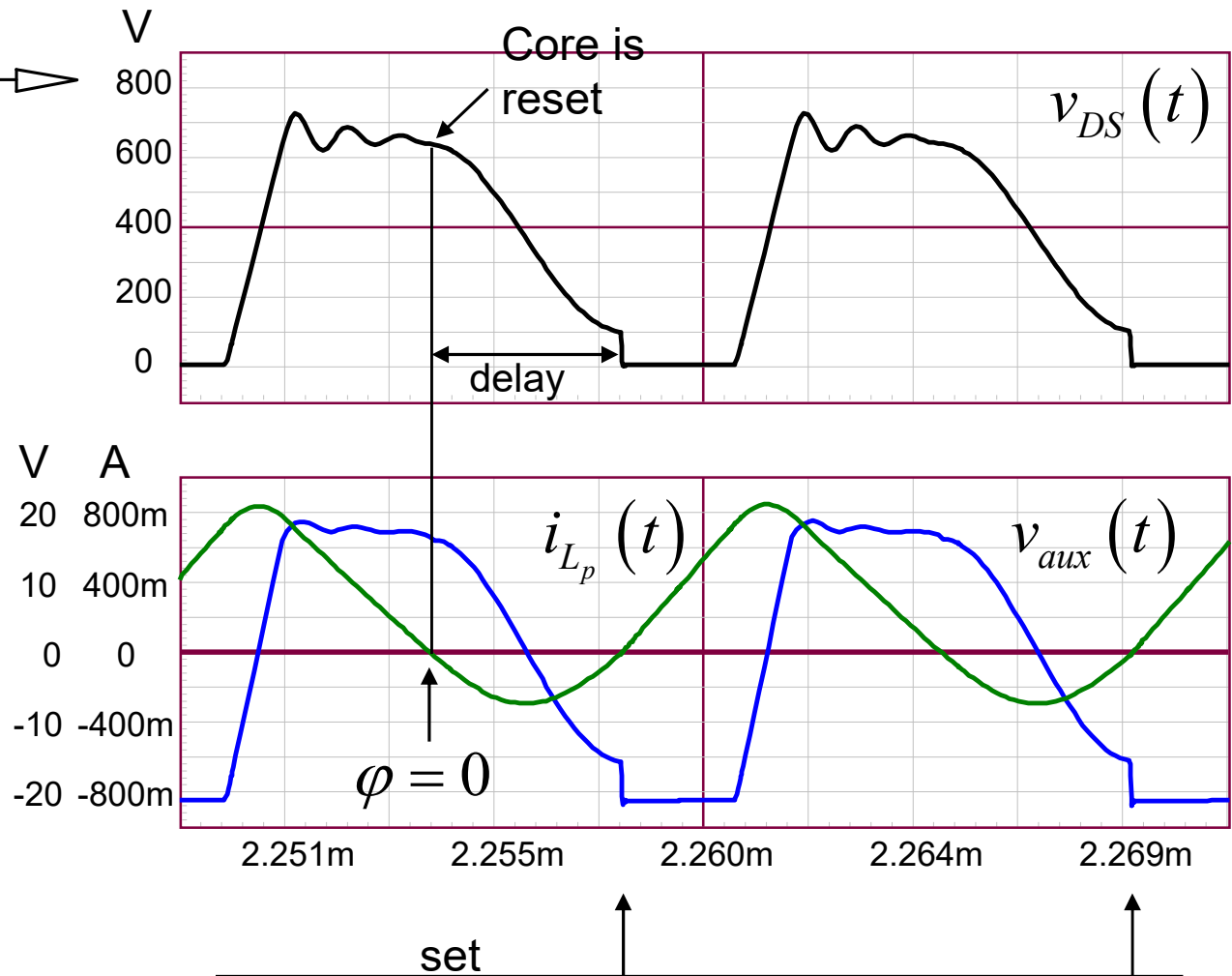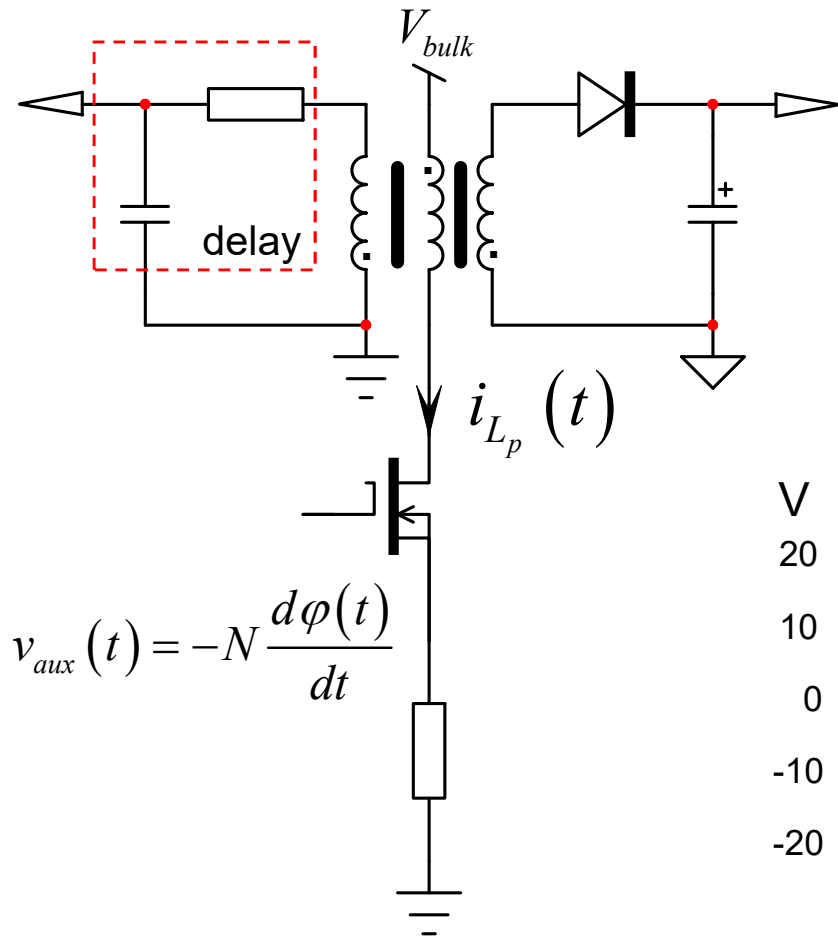- ❑ When the flux returns to zero, the aux. voltage drops
- ❑ Discontinuous Mode is always maintained



What Does Core Reset Mean?

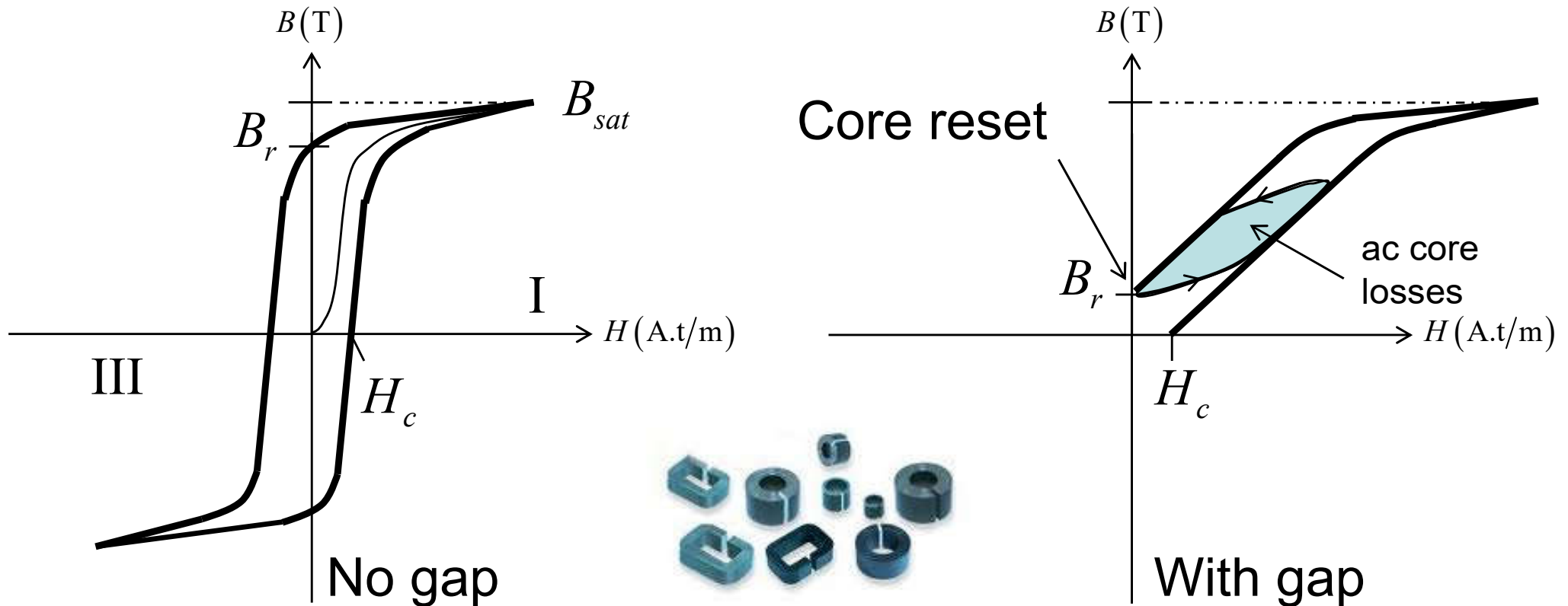
- The core flux density returns to zero in a switching cycle



- There is always a remanent flux in the transformer core

Frequency Changes over Line and Load


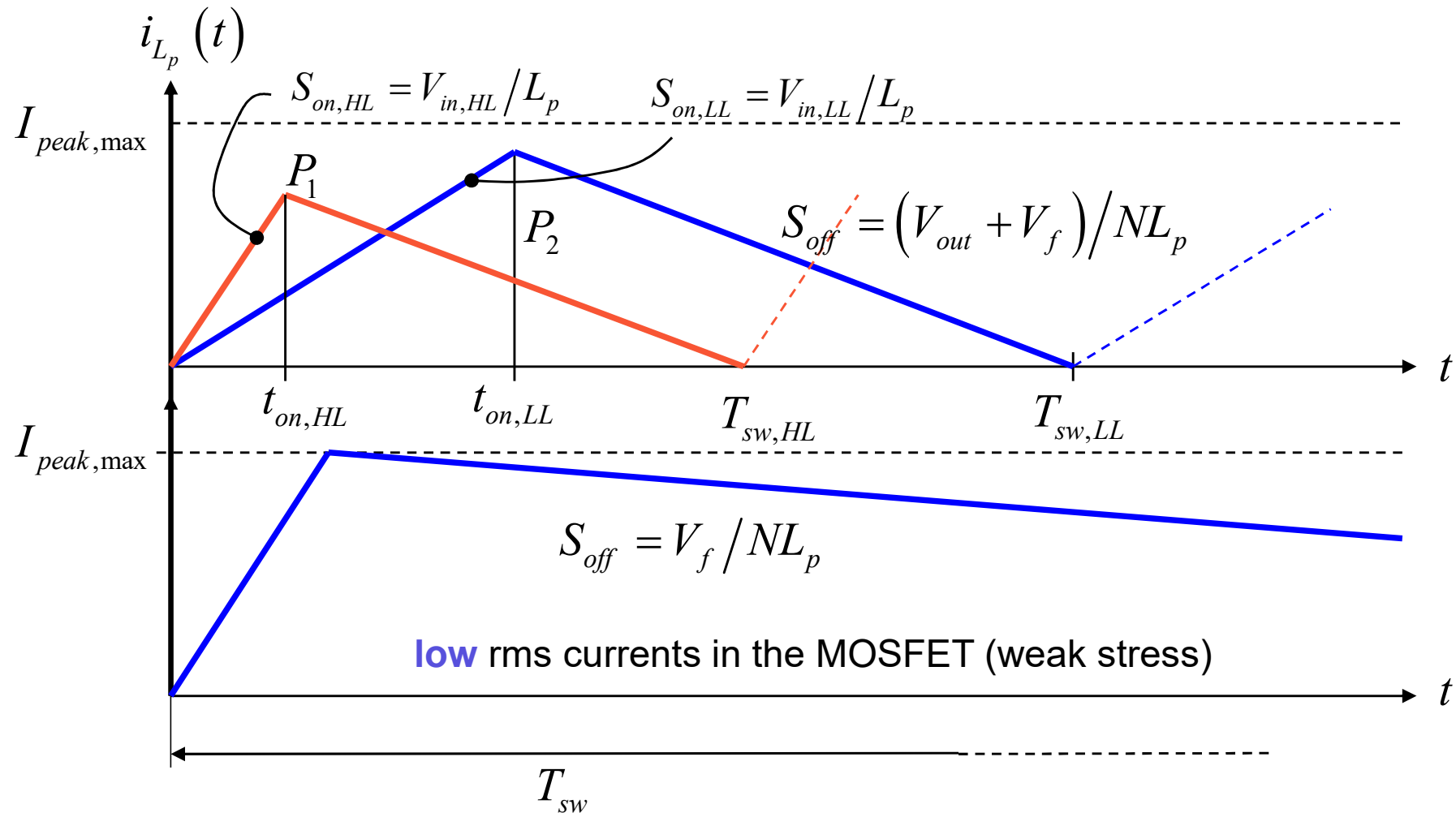
- As the peak current and the on-slope vary, T_{sw} changes



- Excellent behavior in short circuit conditions!

The Excursion Can be Quite Large

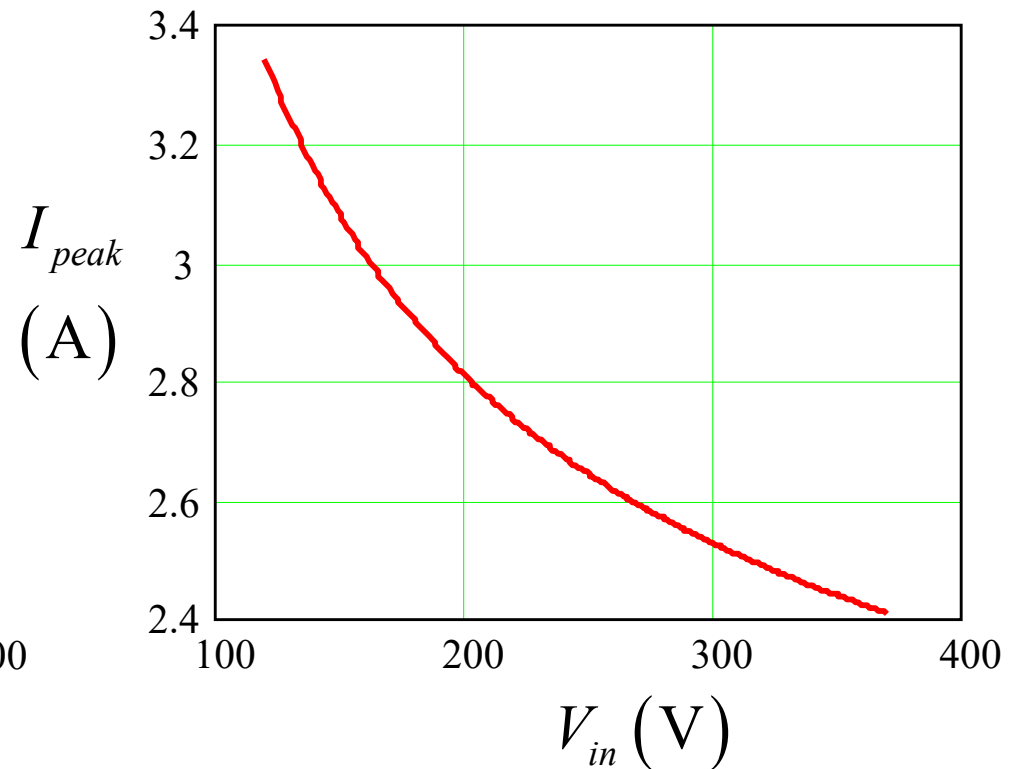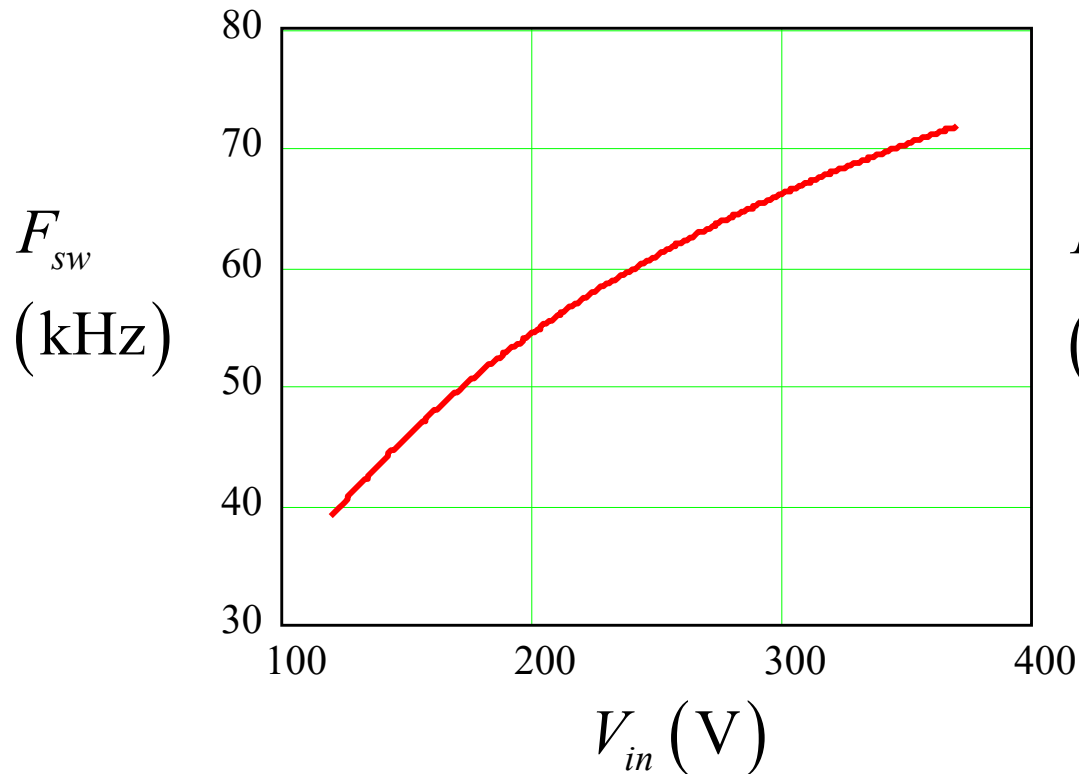- ❑ In heavy load low-line conditions, F_{sw} decreases
- ❑ In light-load and high-line operations, F_{sw} can go very high



- ❑ EMI and switching losses are at stake as F_{sw} goes up
- ❑ Standby power obviously suffers from this condition


Agenda

- ❑ What is a QR Converter?
- ❑ **Deriving Operating Conditions**
- ❑ The Over Power Problem
- ❑ Three Operating Modes
- ❑ Small-Signal Analysis – QR
- ❑ Small-Signal Analysis – VCO
- ❑ Compensating with TL431
- ❑ Control Loop Design Example
- ❑ Conclusion




QR Converter Typical Waveforms

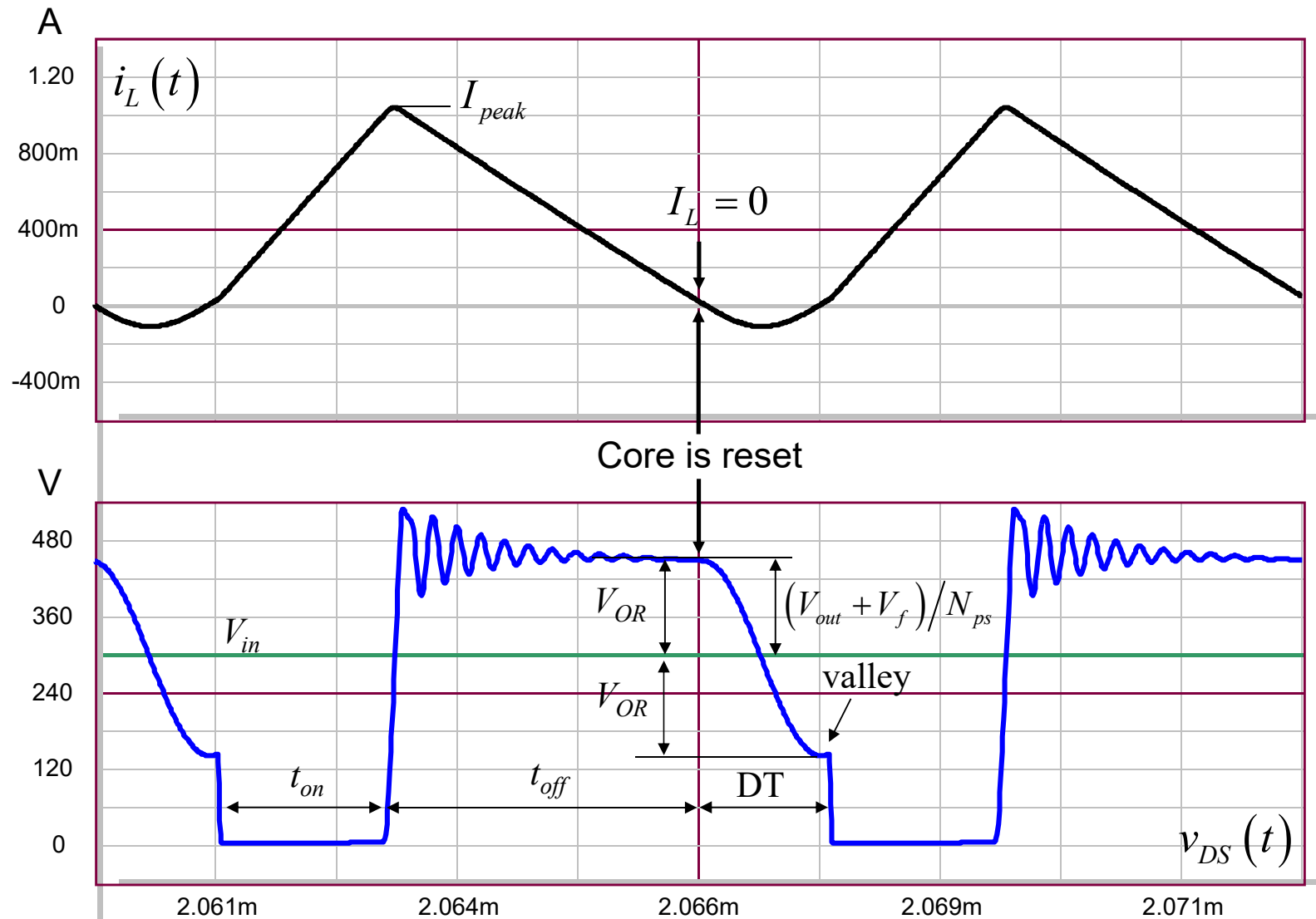- The waveforms at the switch opening are smooth



A Variable Frequency Converter

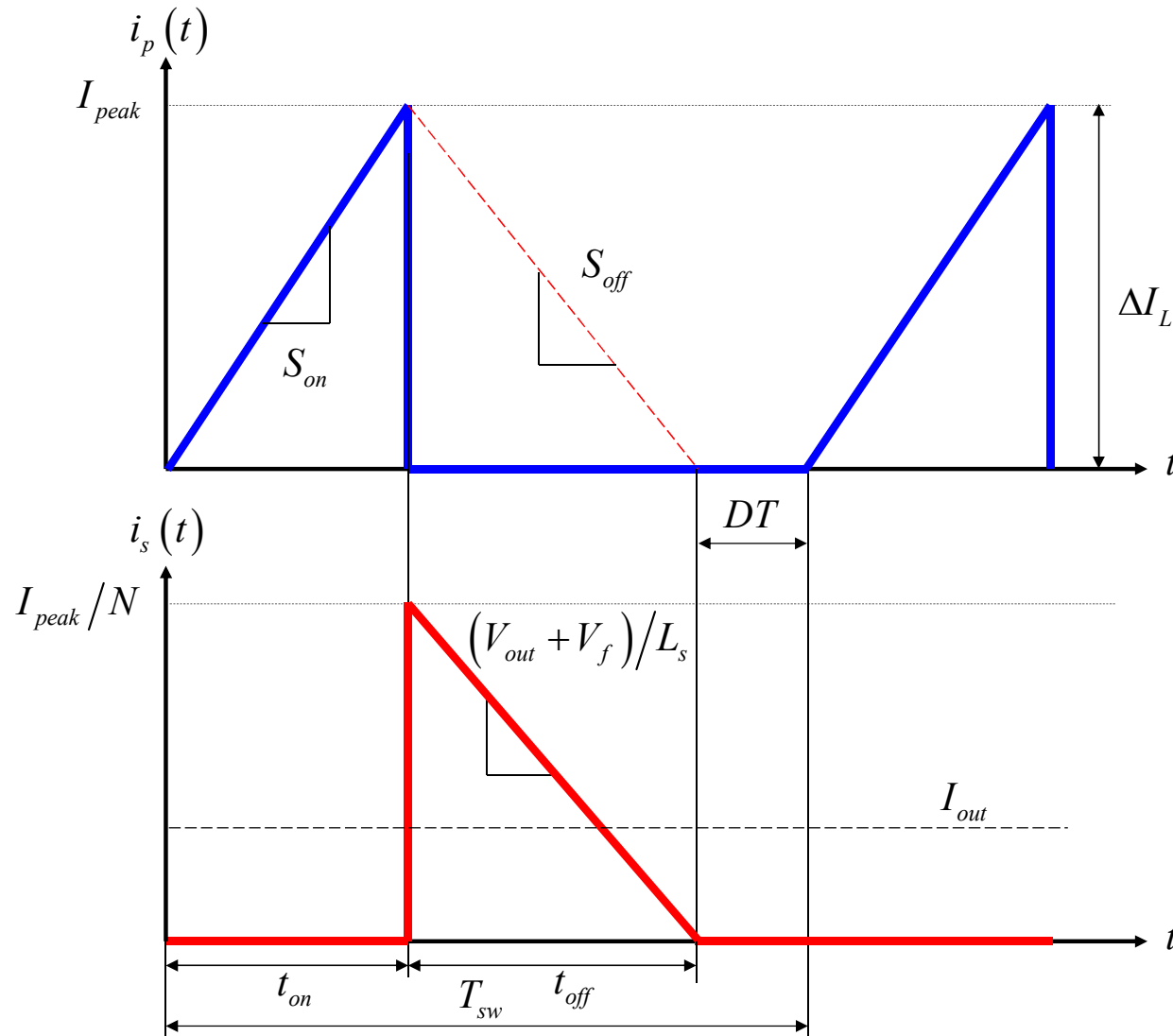- S_{on} and S_{off} are constant parameters at steady state




A Variable Frequency Converter

- Frequency depends on the *on* and *off* slopes

$$S_{on} = \frac{V_{in}}{L_p} \quad S_{off} = -\frac{V_{out} + V_f}{NL_p}$$

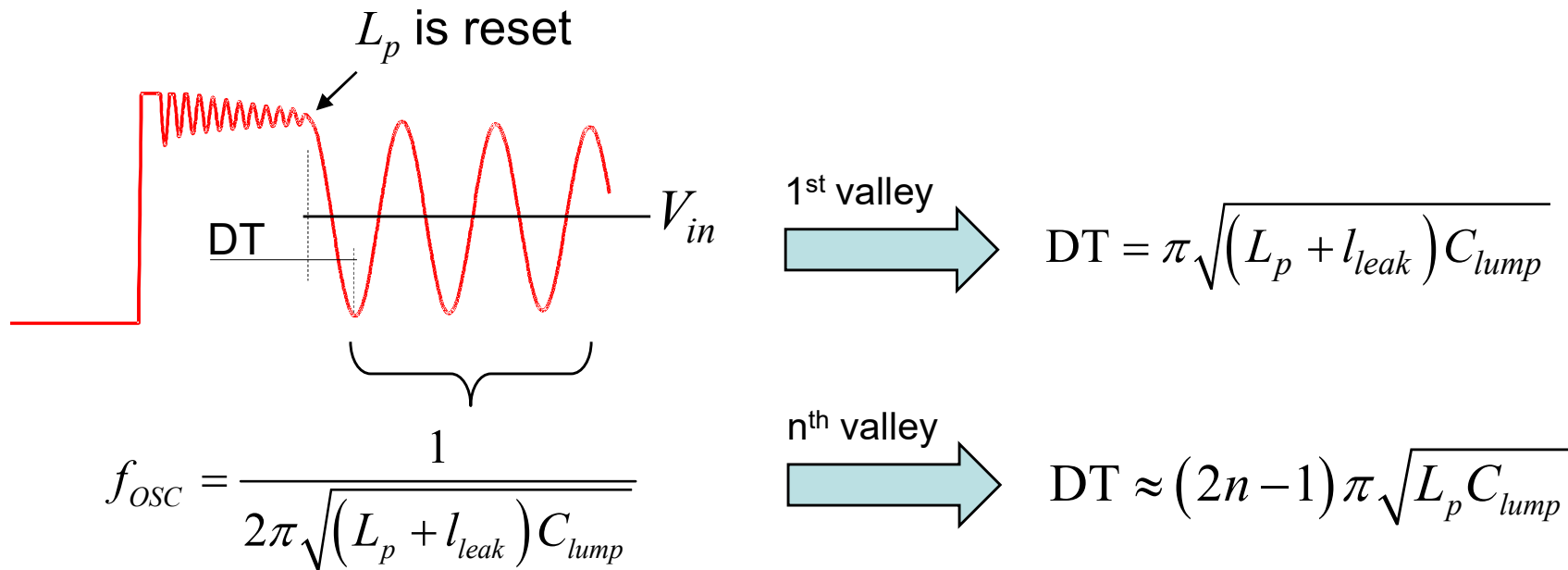- ...but also on the valley-switching deadtime



What is the Switching Period?

- The total period depends on t_{on} and t_{off} plus DT

$$T_{sw} = t_{on} + t_{off} + DT$$

- From slope definitions, we have:

$$I_{L,peak} = S_{on} t_{on} \quad I_{L,peak} = \frac{V_{in}}{L_p} t_{on} \quad \longrightarrow \quad t_{on} = \frac{L_p I_{L,peak}}{V_{in}}$$

$$I_{L,peak} = S_{off} t_{off} \quad I_{L,peak} = \frac{V_{out} + V_f}{NL_p} t_{off} \quad \longrightarrow \quad t_{off} = I_{L,peak} \frac{NL_p}{V_{out} + V_f}$$

- A flyback operated in the Discontinuous Mode delivers

$$P_{out} = \frac{1}{2} F_{sw} L_p I_{L,peak}^2 \eta \quad \longrightarrow \quad I_{L,peak} = \sqrt{\frac{2T_{sw} P_{out}}{L_p \eta}}$$



What is the Switching Period?

- Update t_{on} and t_{off} definitions with $I_{L,peak}$

$$t_{on} = \frac{L_p}{V_{in}} \sqrt{\frac{2T_{sw}P_{out}}{L_p\eta}} \quad t_{off} = \sqrt{\frac{2T_{sw}P_{out}}{L_p\eta}} \frac{NL_p}{V_{out} + V_f}$$

- Include the dead-time contribution

$$T_{sw} = \sqrt{\frac{2T_{sw}P_{out}}{L_p\eta}} \left(\frac{L_p}{V_{in}} + \frac{NL_p}{V_{out} + V_f} \right) + DT$$

- Rearrange and rewrite

$$-T_{sw} + \sqrt{T_{sw}} \sqrt{\frac{2P_{out}}{L_p\eta}} \left(\frac{L_p}{V_{in}} + \frac{NL_p}{V_{out} + V_f} \right) + DT = 0 \quad \left| \begin{array}{l} x = \sqrt{T_{sw}} \\ B = \sqrt{\frac{2P_{out}}{L_p\eta}} \left(\frac{L_p}{V_{in}} + \frac{NL_p}{V_{out} + V_f} \right) \end{array} \right.$$



The Switching Frequency Definition

- Solve the equation to extract the final definition

$$-x^2 + Bx + DT = 0 \longrightarrow x = \frac{\left(B + \sqrt{B^2 + 4DT}\right)^2}{4}$$



- Replace and trust Mathcad®!

$$F_{sw} = \frac{4}{\left(\sqrt{4DT + \frac{2L_p P_{out} (V_f + V_{out} + NV_{in})^2}{\eta V_{in}^2 (V_{out} + V_f)^2}} + \frac{\sqrt{2}L_p (V_f + V_{out} + NV_{in}) \sqrt{\frac{P_{out}}{\eta L_p}}}{V_{in} (V_{out} + V_f)} \right)^2}$$



Frequency and Peak Current Change

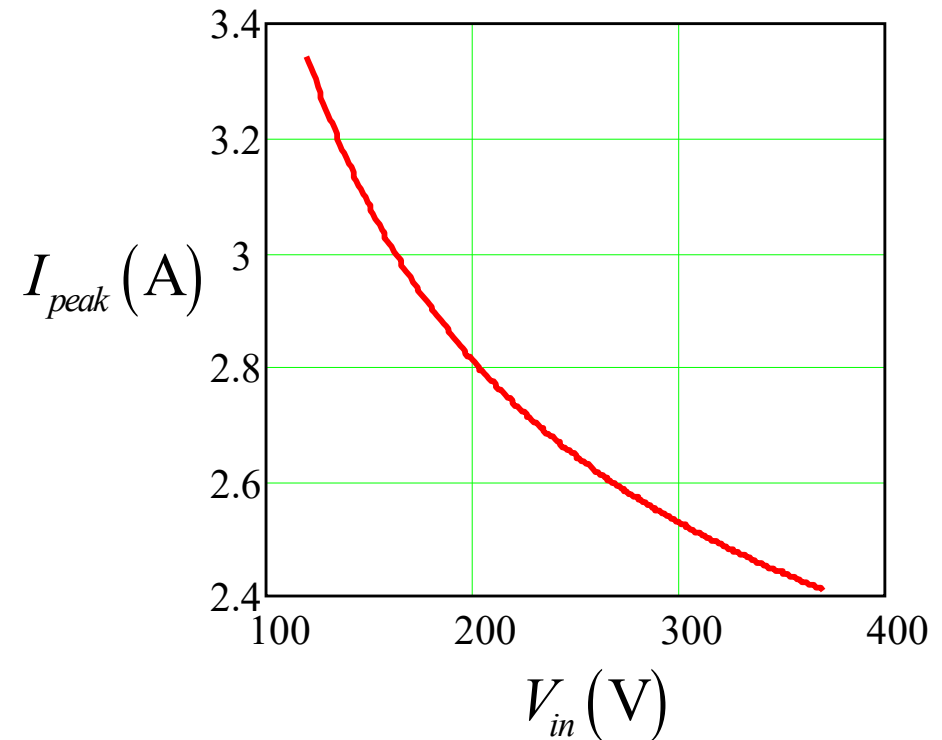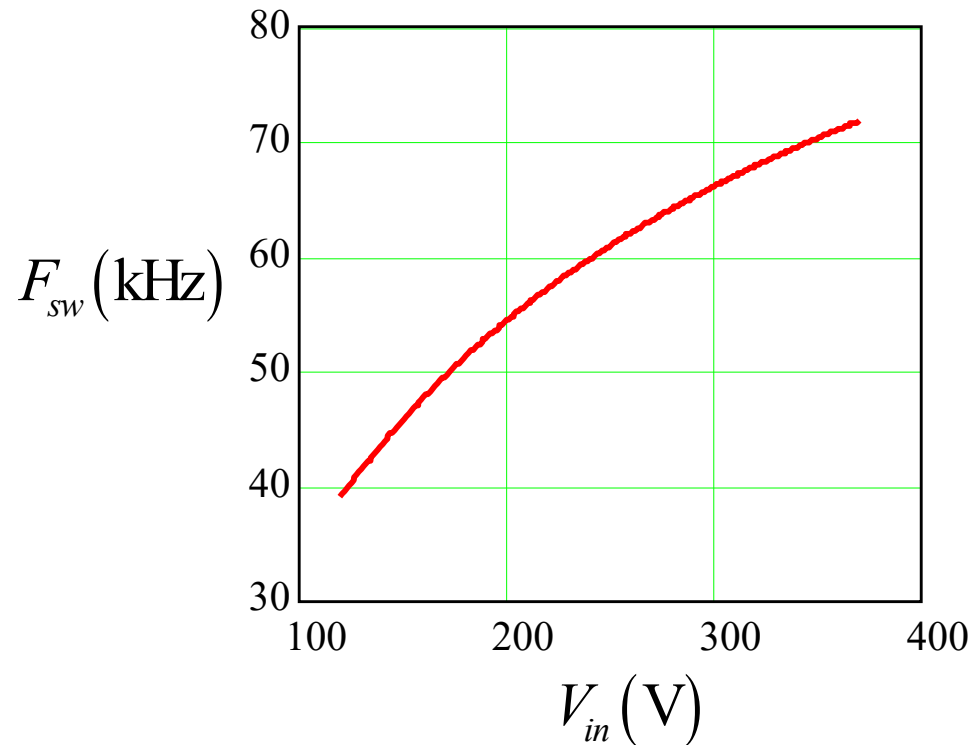- Frequency increases in light-load conditions



- Peak current demand is larger at low line than high line...
- More power capability at high line brings OPP problems!


Agenda

- ❑ What is a QR Converter?
- ❑ Deriving Operating Conditions
- ❑ **The Over Power Problem**
- ❑ Three Operating Modes
- ❑ Small-Signal Analysis – QR
- ❑ Small-Signal Analysis – VCO
- ❑ Compensating with TL431
- ❑ Control Loop Design Example
- ❑ Conclusion




Over Power in a DCM Converter

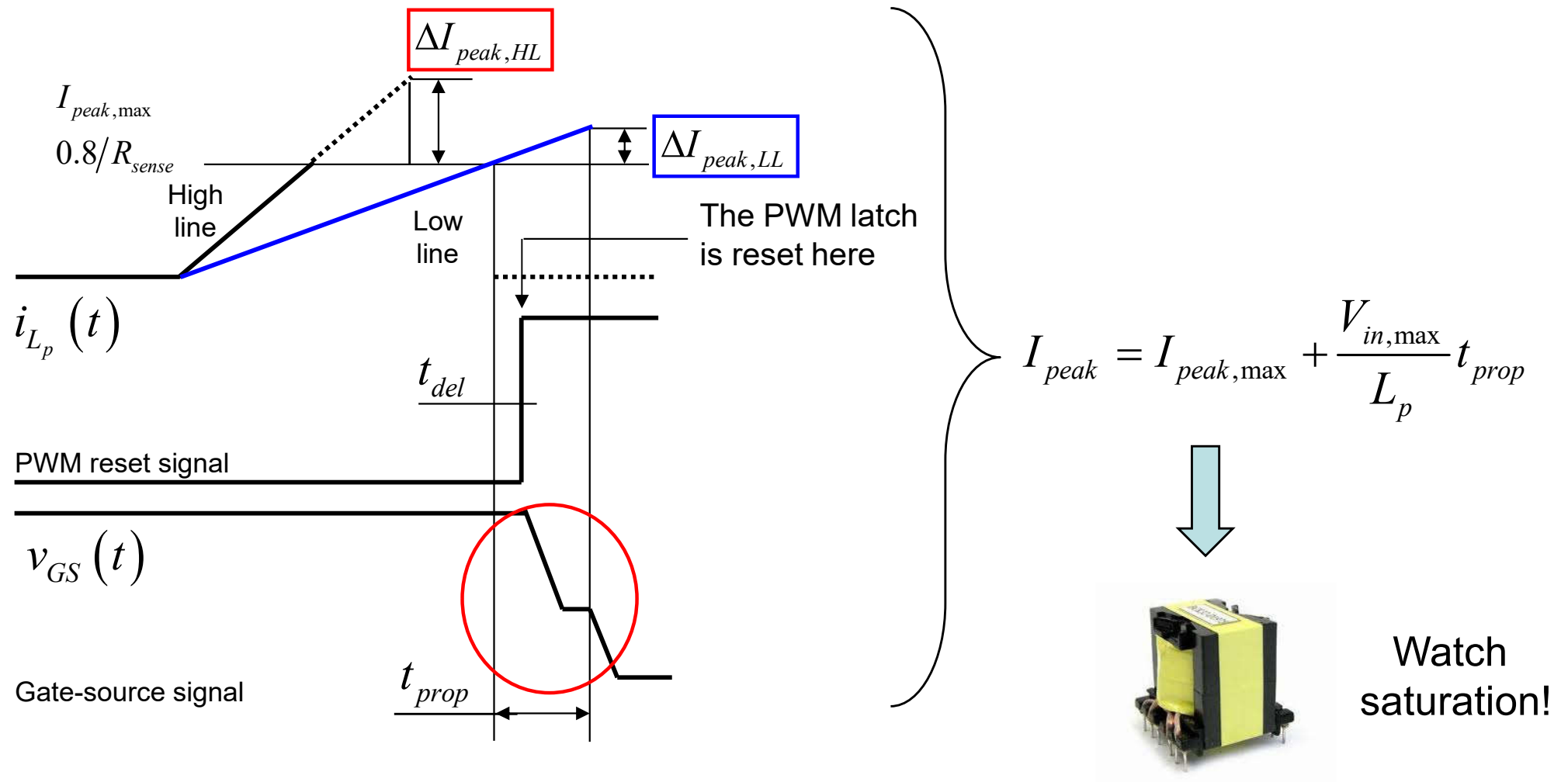- ❑ What maximum peak current at different input voltages?




Power Runaway is Worse in QR

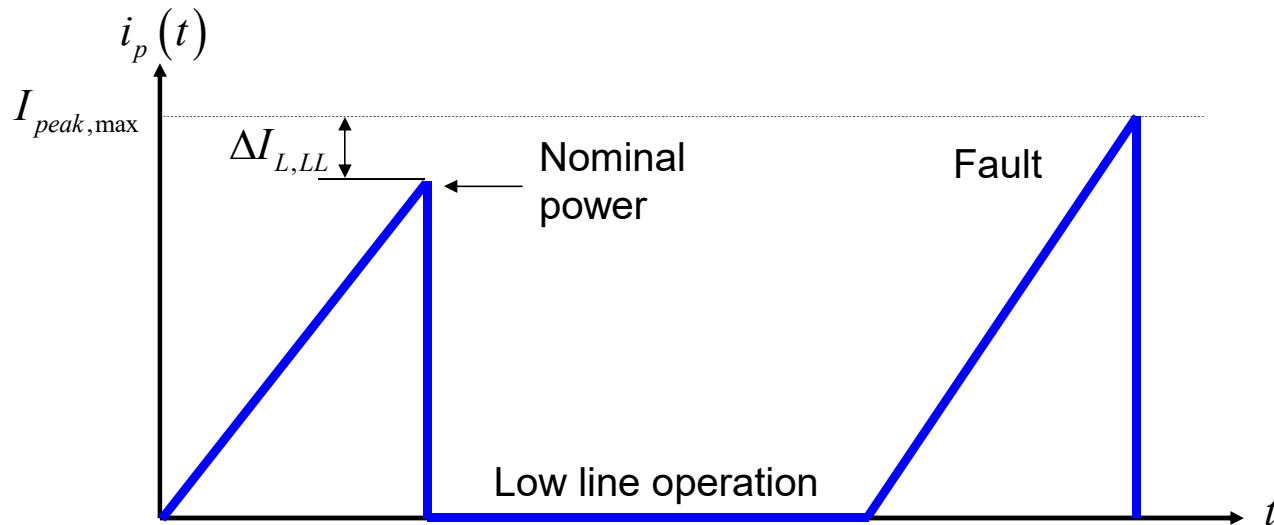- As frequency is high, nominal peak at low line is small



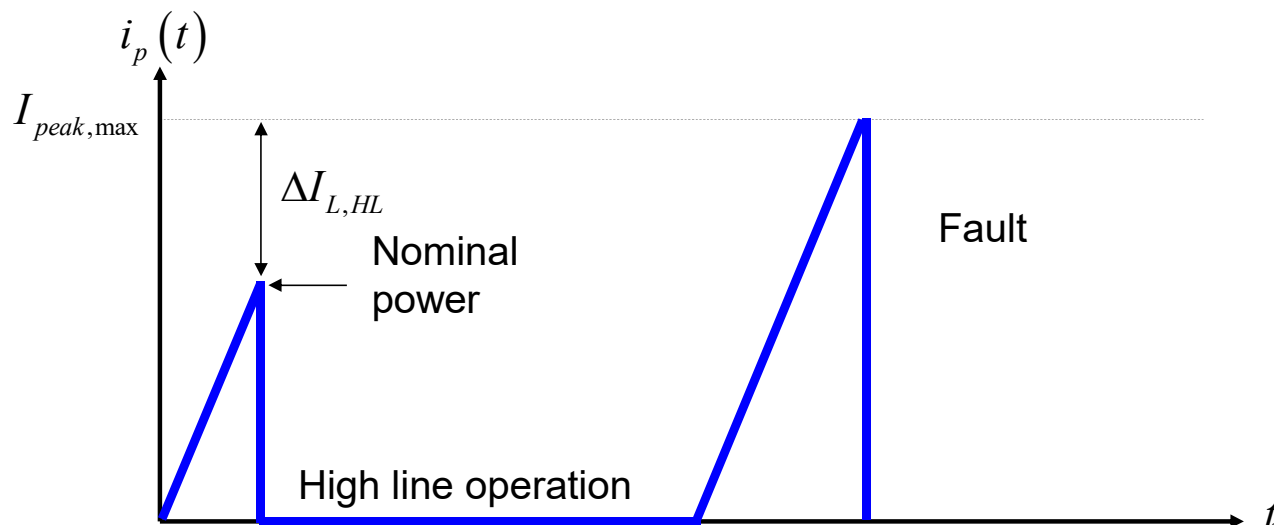Low line: small headroom before protection trips



High line: large Headroom, current can grow further

Quantifying Power Excursion

- Let us assume the following components values

$$R_{sense} = 0.2 \Omega \quad \longrightarrow \quad I_{p,max} = 0.8/0.2 = 4 \text{ A}$$

$$L_p = 350 \mu\text{H} \quad N = 0.25 \quad t_{prop} = 350 \text{ ns} \quad \text{DT} = 831 \text{ ns}$$

- The operating frequency with these elements is

$$F_{sw} = \frac{1}{I_{L,max} L_p \left(\frac{1}{V_{in}} + \frac{N}{V_{out} + V_f} \right) + \text{DT}}$$

$F_{sw} = 32 \text{ kHz low line}$
 $F_{sw} = 40.7 \text{ kHz high line}$

- Applying the DCM output power formula, we calculate


$$P_{out} = \frac{1}{2} F_{sw} L_p I_{L,peak}^2 \eta \quad \longrightarrow$$

$P_{out} = 80.6 \text{ W low line}$
 $P_{out} = 121 \text{ W high line}$



Harnessing the Maximum Output Power

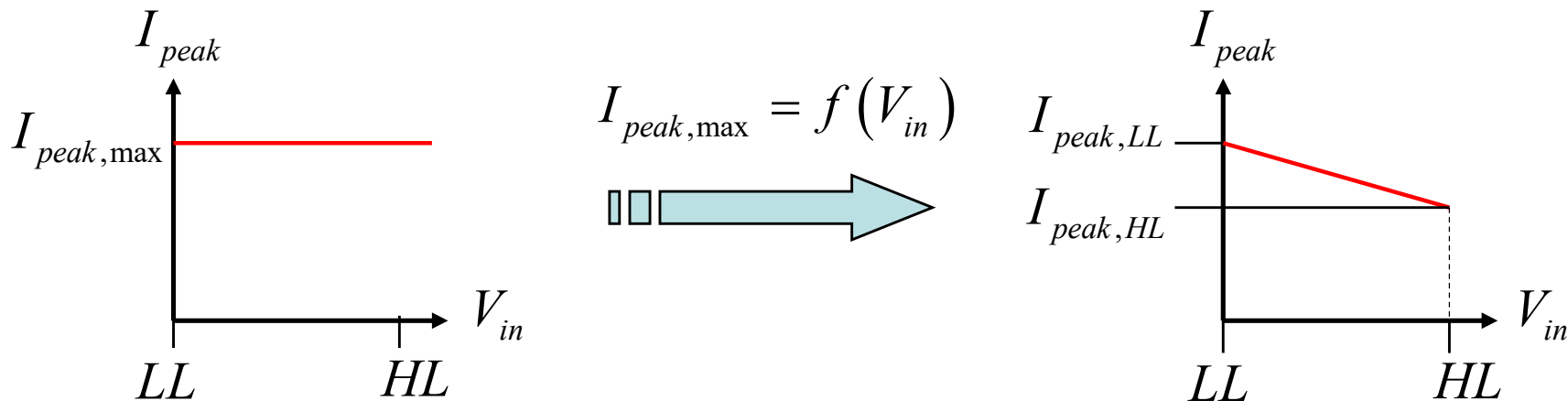- ❑ There are easy options to pursue:
 - we reduce the maximum peak current at high line



- ❑ How to calculate the compensated hi-line current?
 - ❖ Equate lo-line power with hi-line power and solve for I_{peak}

$$P_{out,max,LL} = \frac{1}{2} L_p I_{peak,max,HL}^2 F_{sw} \eta_{HL}$$

→ Solve for I_{peak}

With a QR Converter Frequency Varies

- ❑ Fix the power level you can accept at high line: 80 W
- ❑ Calculate the switching frequency for 80 W high line

$$F_{sw,HL} = \frac{4}{\left(\sqrt{4 \times 831n + \frac{2 \times 350u \times 80 \times (0.5 + 19 + 0.25 \times 370)^2}{0.89 \times 370^2 (19 + 0.5)^2}} + \frac{\sqrt{2} \times 350u \times (0.5 + 19 + 0.25 \times 370) \sqrt{\frac{80}{0.89 \times 350u}}}{370 \times (19 + 0.5)} \right)^2} = 59.2 \text{ kHz}$$

- ❑ Calculate the corresponding peak current at this frequency


$$I_{L,max,CMP} = \sqrt{\frac{2P_{out}}{\eta L_p F_{sw}}} = \sqrt{\frac{2 \times 80}{0.89 \times 350u \times 59.2k}} = 2.95 \text{ A}$$

- ❑ Question, how to reduce the peak setpoint versus line?



Offsetting the Current Sense

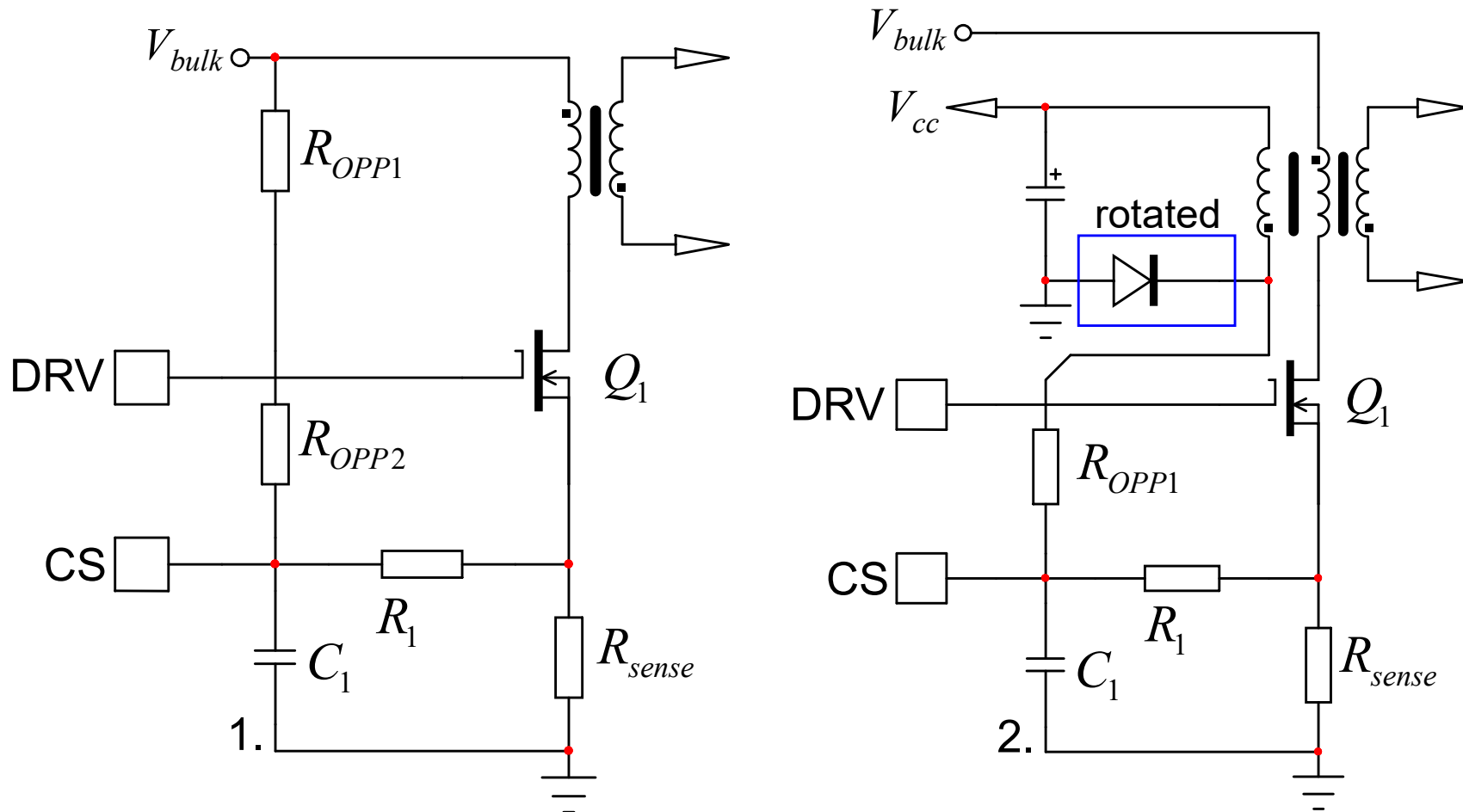
- ❑ This offset must be proportional to the input voltage



- ❑ Offset degrades light-load operation
- ❑ Radiated EMI can be affected in solution 2

ON Semiconductor Proprietary OPP Scheme

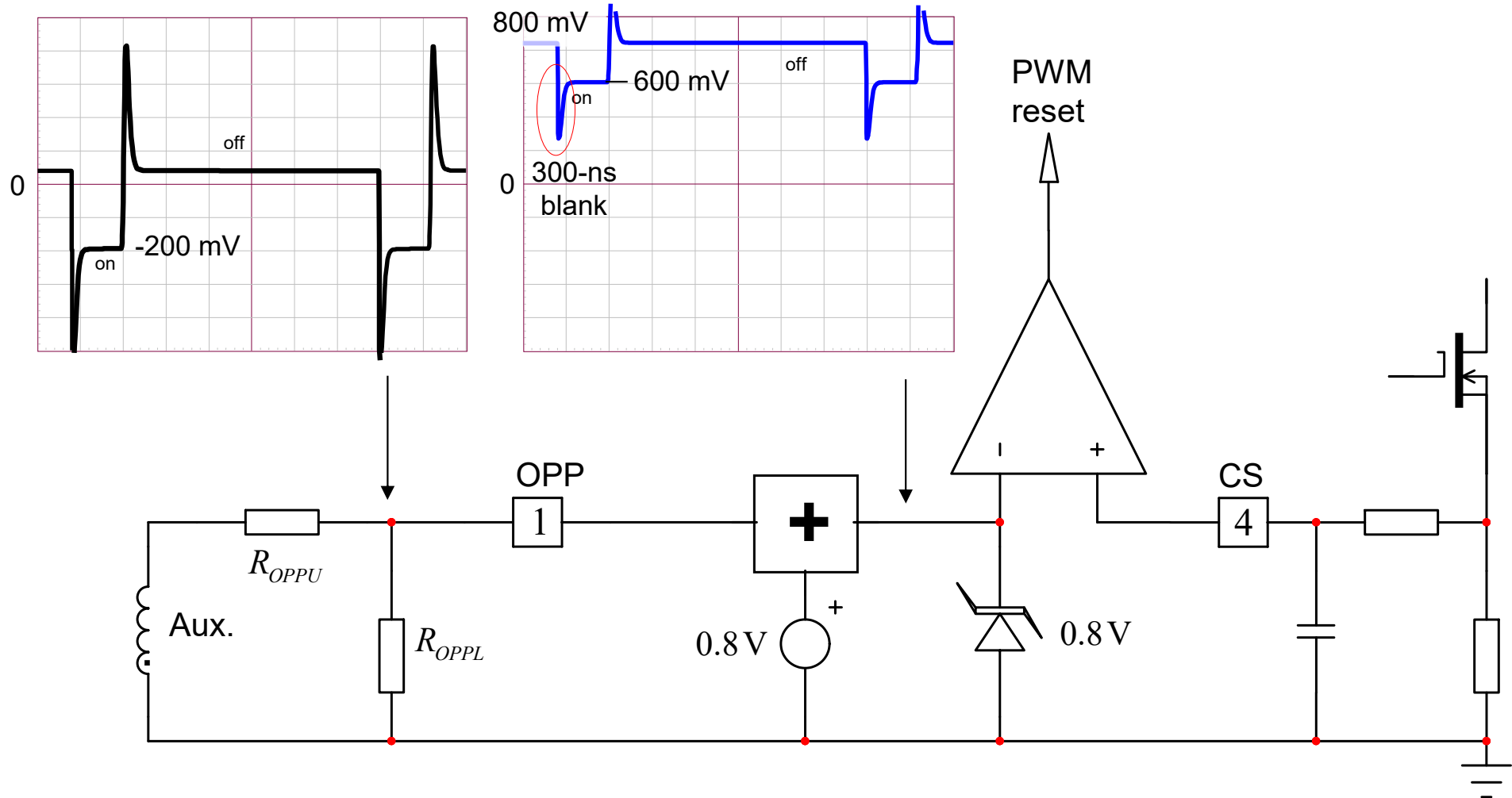□ This is a non-dissipative OPP circuitry



□ The aux. swings to $-V_{in}$ and reduces setpoint \rightarrow OPP


Peak Current Reduction is Easy Then

- We need 2.95 A from previous calculation

$$V_{sense,max,CMP} = R_{sense} \left(I_{L,max,CMP} - \frac{V_{in,HL}}{L_p} t_{prop} \right) = 0.2 \times \left(2.95 - \frac{370}{350u} \times 350n \right) = 516 \text{ mV}$$

Accounts for prop. delay \swarrow

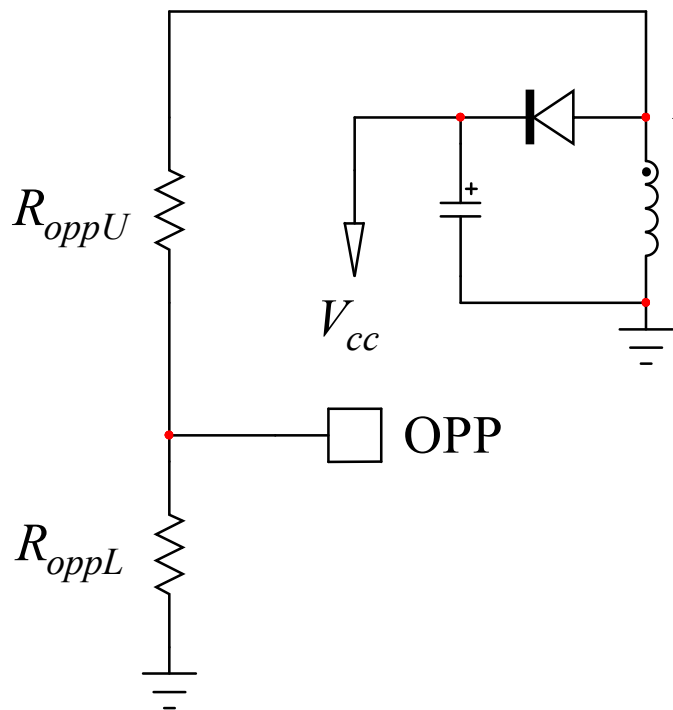- The negative contribution must simply be 284 mV



Swings to -60 V during on-time hi line

1. Fix R_{oppL} to 1 k Ω

2. Calculate current: $I_{R_{oppL}} = \frac{284m}{1k} = 284 \mu\text{A}$

3. Calculate R_{oppU} : $R_{oppU} = \frac{60 - 284m}{284u} = 210 \text{ k}\Omega$

4. You are done!

Agenda


- ❑ What is a QR Converter?
- ❑ Deriving Operating Conditions
- ❑ The Over Power Problem
- ❑ **Three Operating Modes**
- ❑ Small-Signal Analysis – QR
- ❑ Small-Signal Analysis – VCO
- ❑ Compensating with TL431
- ❑ Control Loop Design Example
- ❑ Conclusion




A Controller With 3 Operating Modes

- ❑ Modern controllers need to cope with specifications on
 - ✓ acoustic noise: vibrations in audible range must be avoided
 - ✓ efficiency: full-load efficiency but also light-load efficiency
 - ✓ standby power: in no-load conditions, absorbed power is close to 0 W

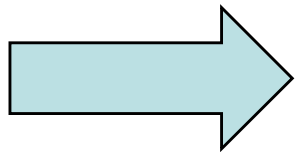- ❑ Need to find solutions to fulfill all these requirements
 1. Valley lockout elegantly solves this issue by going down the valleys
 2. Voltage-Controlled Oscillator folds the frequency back in light load
 3. Skip cycle helps reduce consumption in no-load standby





NCP1336/39 operate this way

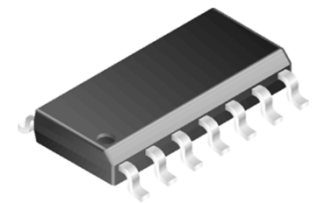


Valley Jumping and Lockout

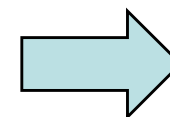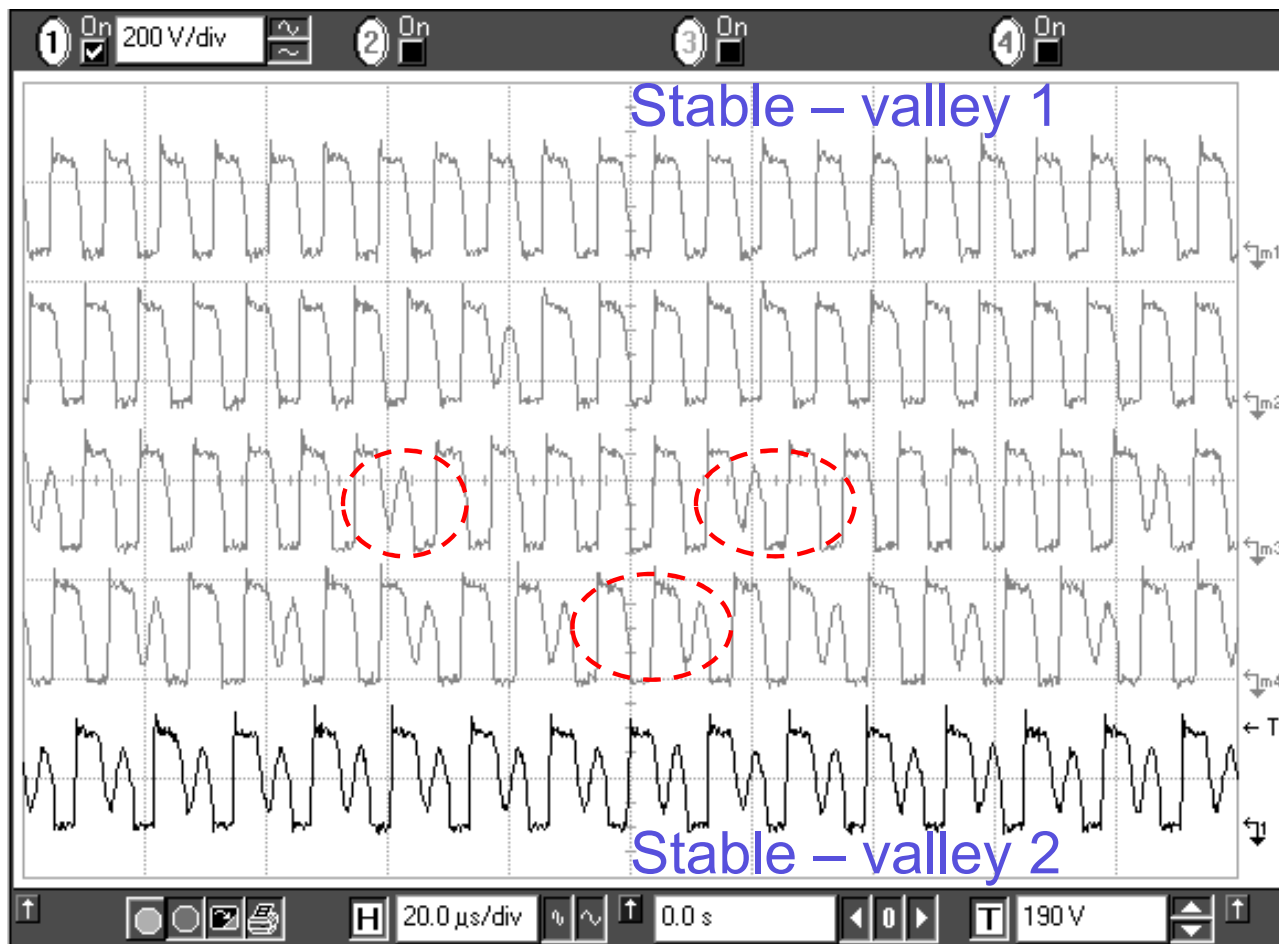- ❑ Jumps between valleys generate instability and potential noise



New Controllers Lock in the Valleys

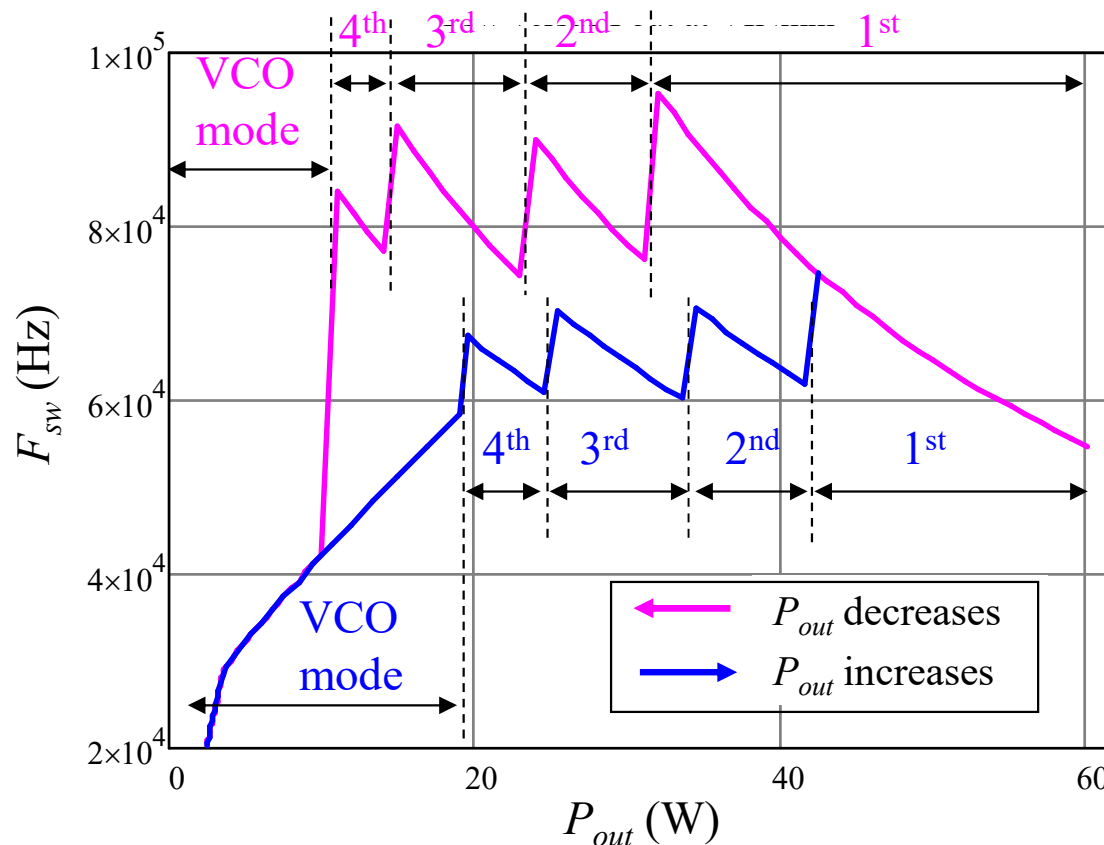
- ❑ To prevent the noise, the NCP1336/39 lock the valley
- ❑ The current is allowed to move within a certain limit
- ❑ When it exceeds this limit, the controller selects a new valley
- ❑ As the load gets lighter, a VCO takes over and reduce F_{sw}



NCP1336/1339

Three Operating Modes

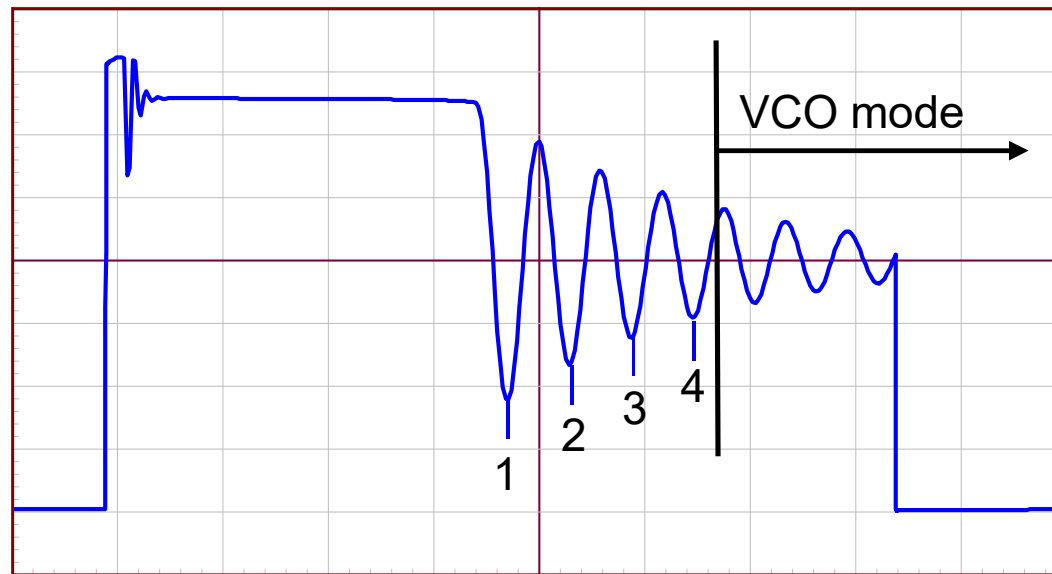1. In Quasi-Resonant mode, controlled variable is I_{peak}
 - ❖ Switching frequency changes with valley position
 - ❖ Transfer function can be affected by different operating points



2. In VCO mode, the controlled variable is F_{sw} , I_{peak} is frozen
3. In skip cycle, frequency and peak current are frozen: hysteretic


Agenda

- ❑ What is a QR Converter?
- ❑ Deriving Operating Conditions
- ❑ The Over Power Problem
- ❑ Three Operating Modes
- ❑ **Small-Signal Analysis – QR**
- ❑ Small-Signal Analysis – VCO
- ❑ Compensating with TL431
- ❑ Control Loop Design Example
- ❑ Conclusion



Small-Signal Analysis

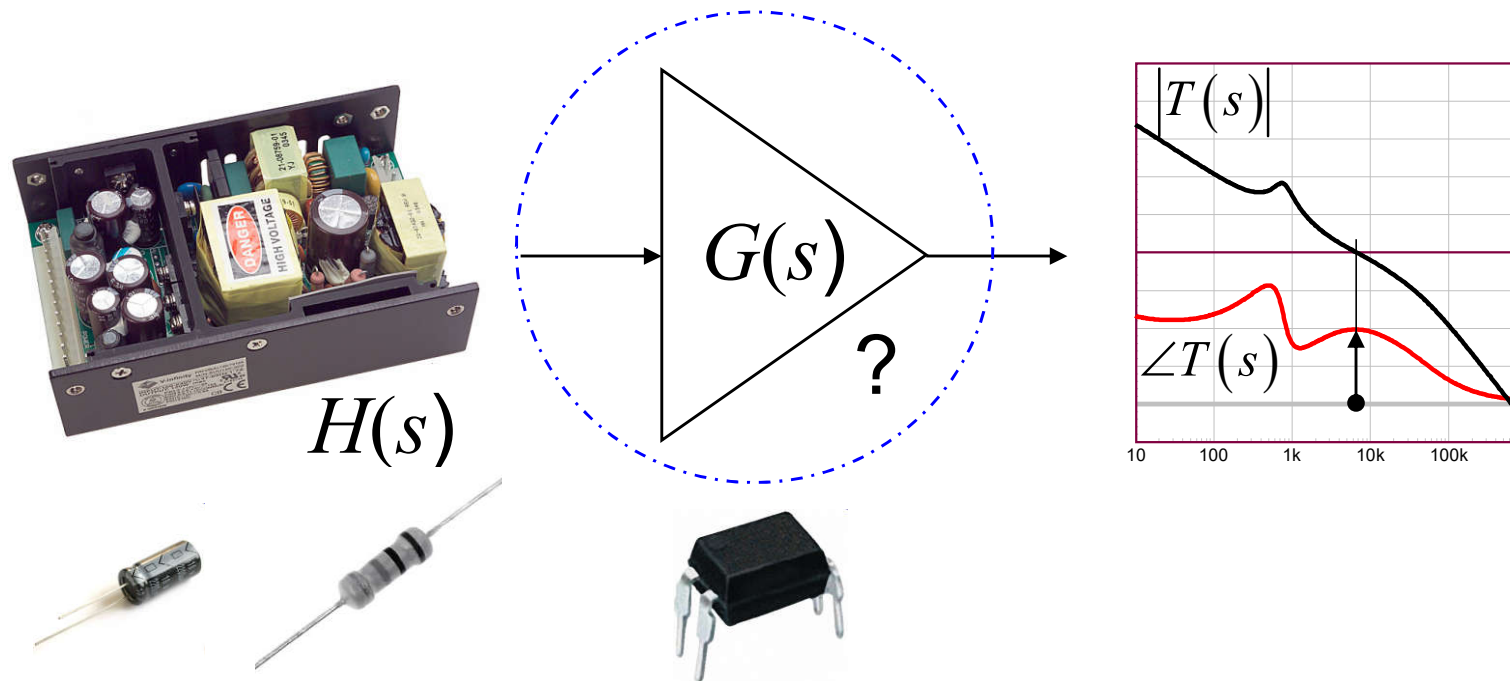- ❑ Loop instability is a common issue in production
- ❑ Due to time pressure, designers often use trial and error
 - no indication on design margins
 - offenders are ignored, robustness is at stake



- ❖ Understand and counteract their variations when building $G(s)$

There are Two Options

- ❑ Analytical analysis of the power stage:
 - ✓ best to see where the offenders are hidden (ESR, opto pole etc.)
 - ✓ equations are complex but literature abounds
 - ❖ transfer function are for DCM or CCM
 - ❖ difficult to predict transient response


- ❑ SPICE models:
 - ✓ easy-to-implement averaged models
 - ✓ can work in ac or transient mode
 - ✓ easily transition between CCM and DCM
 - ❖ do not explicitly disclose the position of poles and zeros



A measurement on the bench is mandatory, whatever you choose!

Analytical Analysis

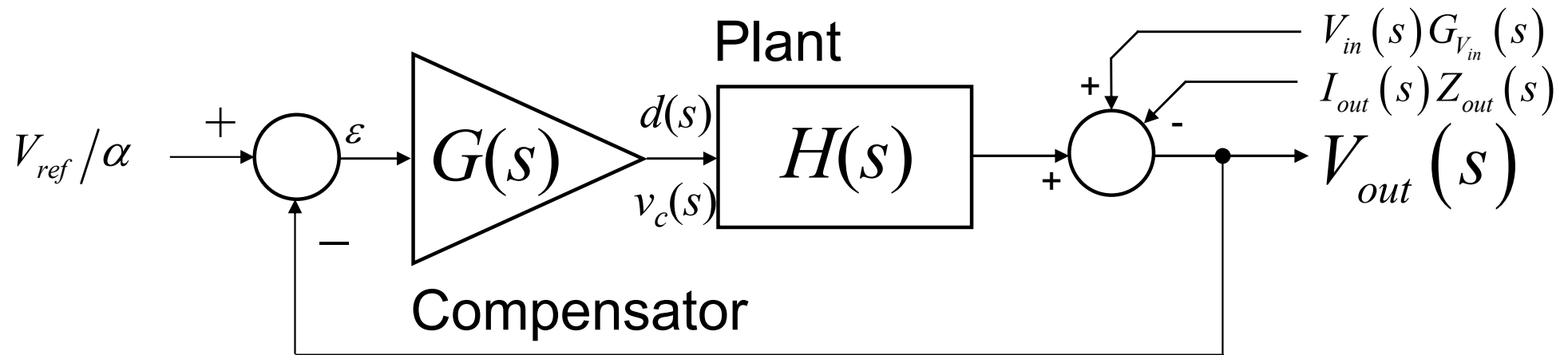- ❑ You must first characterize the "plant" transfer function
 - what are your power stage ac characteristics?



$$H(s) = \frac{V_{out}(s)}{v_c(s)}$$


Current-mode control

$$H(s) = \frac{V_{out}(s)}{d(s)}$$

Voltage-mode control



How do we Stabilize a Converter?

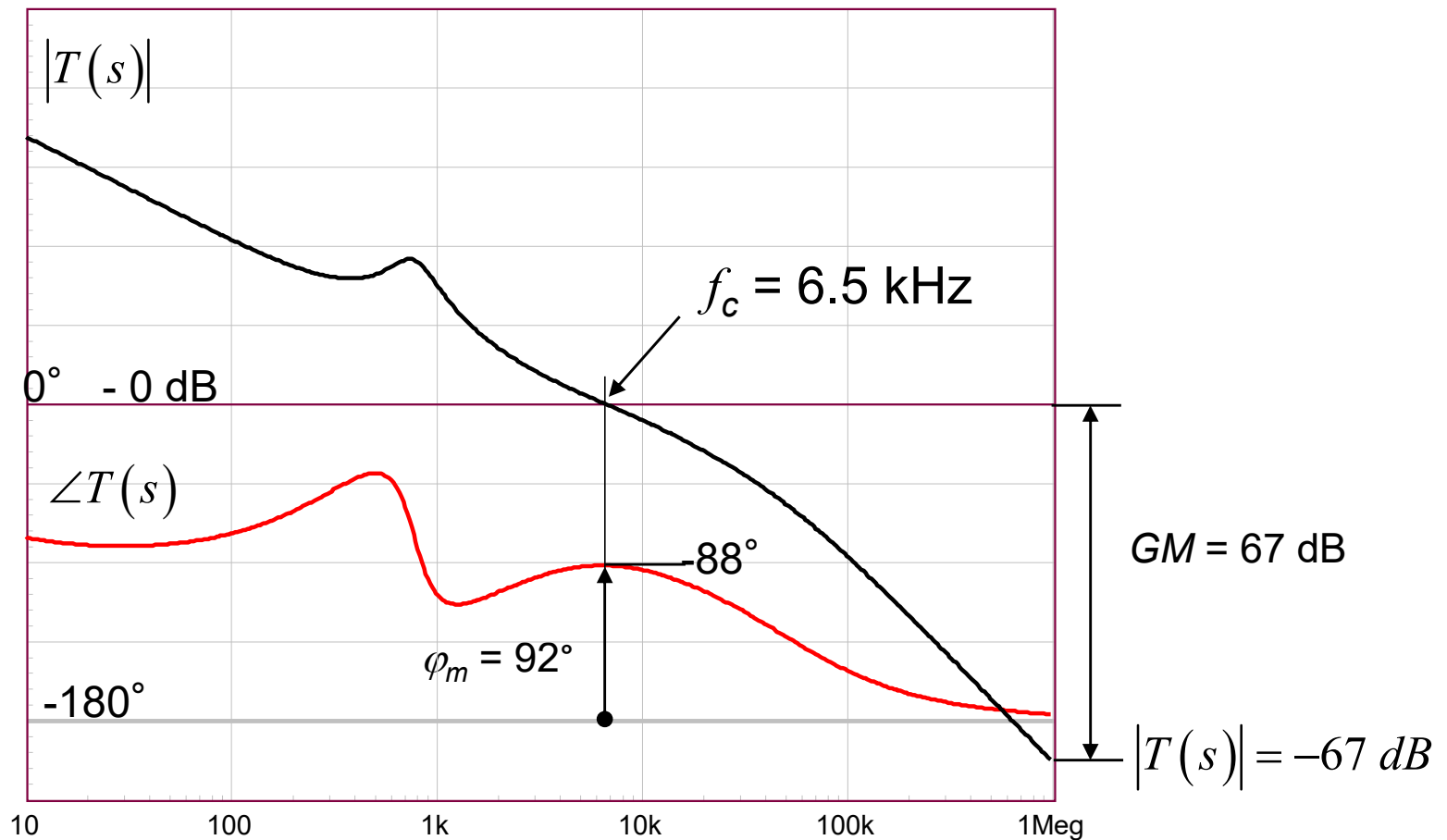- ❑ We need a high gain at dc for a low static error
- ❑ We want a sufficiently high crossover frequency for response speed
- Shape the compensator $G(s)$ to build phase and gain margins!



How much phase margin to chose?

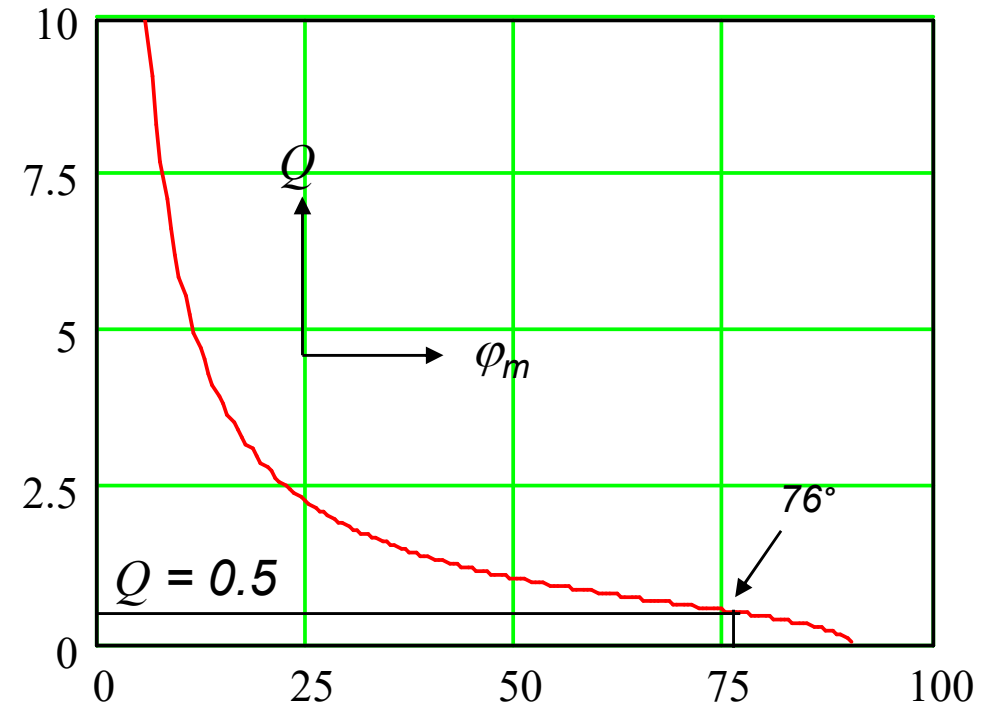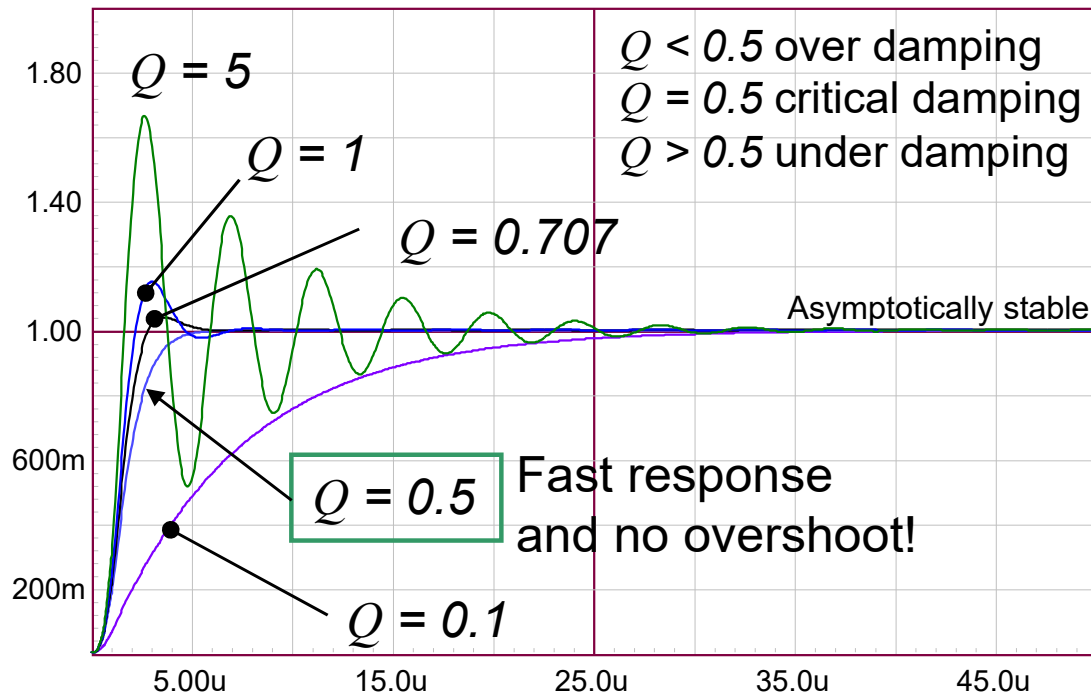
- ❑ a Q factor of 0.5 (critical response) implies a φ_m of 76°
- ❑ a 45° φ_m corresponds to a Q of 1.2: oscillatory response!




- ❑ phase margin depends on the needed response: fast, no overshoot...
- ❑ good practice is to shoot for 60° and make sure φ_m always $> 45^\circ$

What Compensator Types do we Need?


- There are basically 3 compensator types:
 - type 1, 1 pole at the origin, no phase boost
 - type 2, 1 pole at the origin, 1 zero, 1 pole. Phase boost up to 90°
 - type 3, 1 pole at the origin, 1 zero pair, 1 pole pair. Boost up to 180°

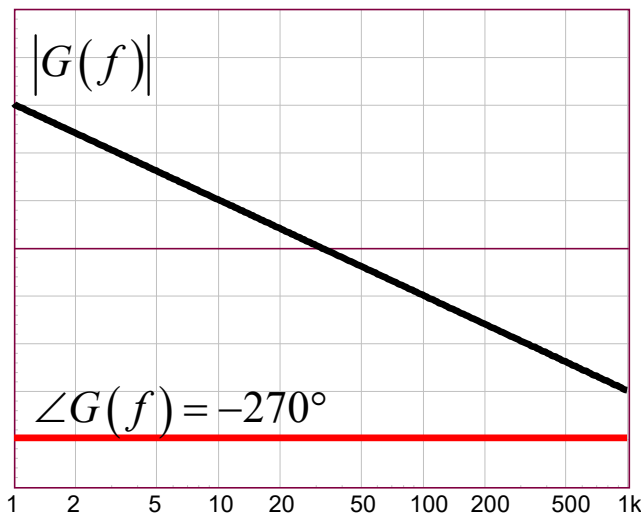

Type 1

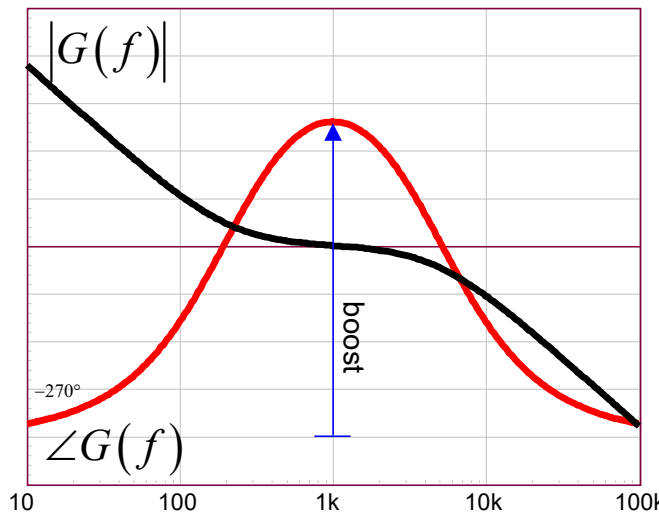



Type 2

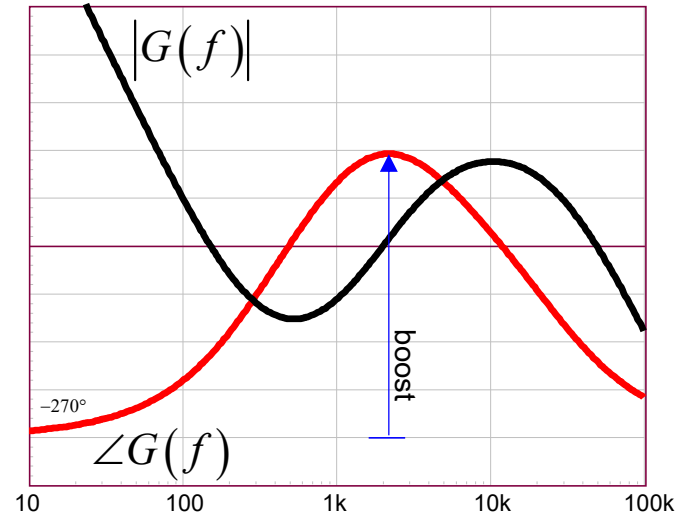


Type 3

Variable-Frequency Current-Mode

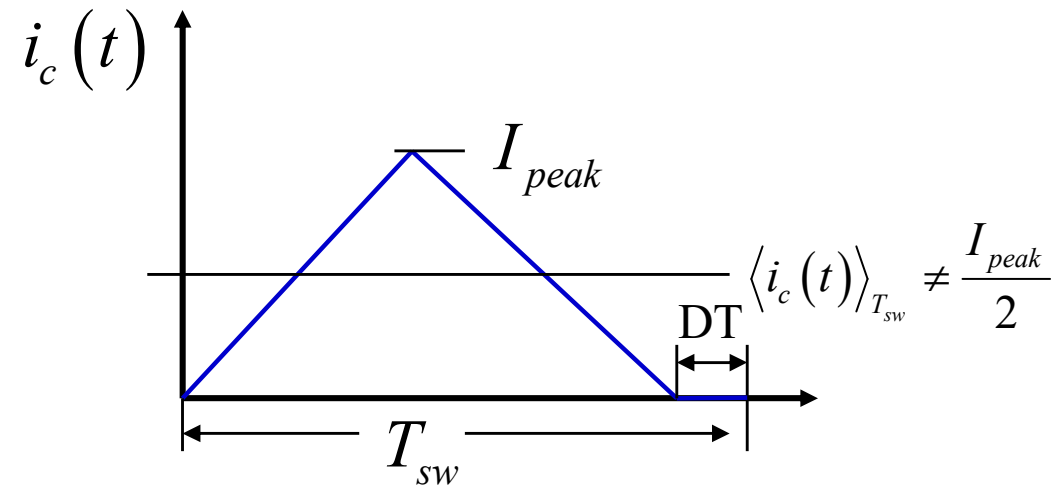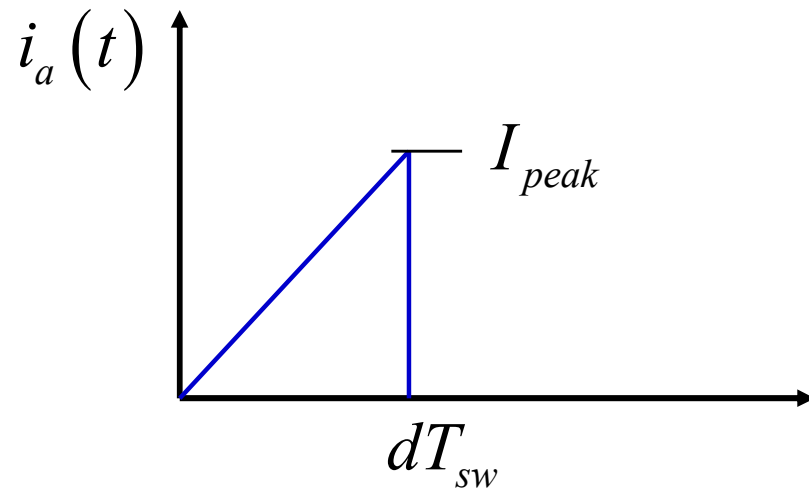- Observing the waveforms helps us to derive an average model



- It leads to a large-signal model

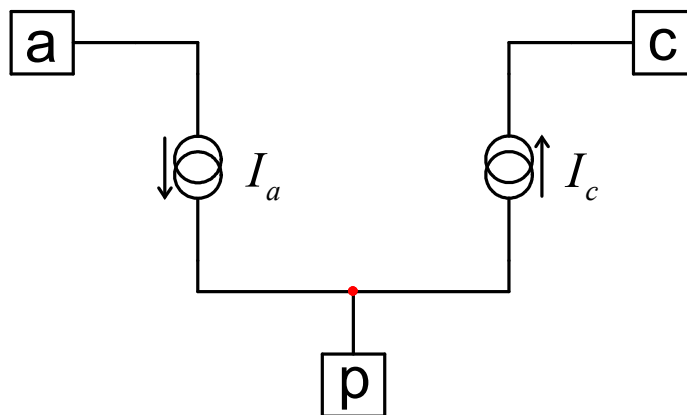


Equations Account for the DeadTime

- Former equations no longer work and need to include DT

$$\left. \begin{aligned} d_1 &= \frac{V_c}{R_i} \frac{L}{V_{ac} T_{sw}} \\ &\quad \uparrow \\ &\quad V_{in} \\ d_2 &= \frac{V_c}{R_i} \frac{L}{V_{cp} T_{sw}} \\ &\quad \uparrow \\ &\quad V_{out}/N \end{aligned} \right\} \begin{aligned} t_{on} &= \frac{V_c}{R_i} \frac{L}{V_{ac}} \\ t_{off} &= \frac{V_c}{R_i} \frac{L}{V_{cp}} \end{aligned} \rightarrow T_{sw} = \frac{V_c L}{R_i} \left(\frac{1}{V_{ac}} + \frac{1}{V_{cp}} \right) + \text{DT}$$

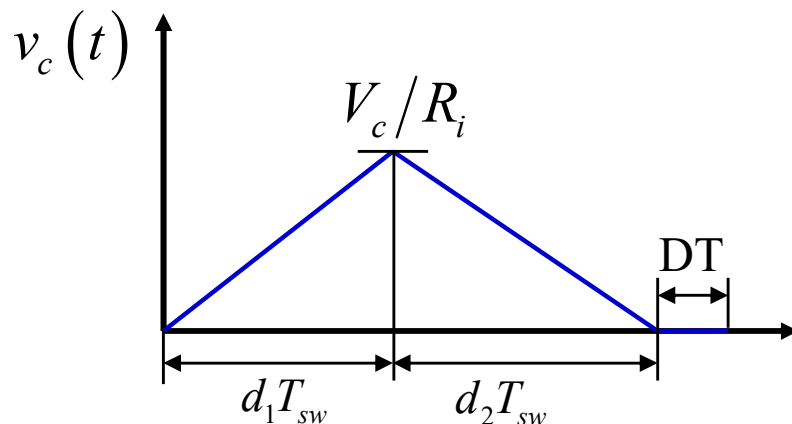- The average current in terminal c now depends on d_1 and d_2



$$I_c = \frac{V_c}{R_i} \left(\frac{d_1 + d_2}{2} \right) = \left(\frac{V_c}{R_i} \right)^2 \frac{L(V_{ac} + V_{cp})}{2T_{sw} V_{ac} V_{cp}}$$

Define Terminals a and c Currents

- Substitute d_1 and d_2 in I_c definition and rearrange

$$I_c = \frac{V_c}{2R_i} \frac{V_{ac} + V_{cp}}{V_{ac} + V_{cp} + \frac{DT \cdot R_i V_{ac} V_{cp}}{LV_c}}$$

- Same method for I_a , express I_{peak} , substitute, rearrange

$$I_a = \frac{I_{peak}}{2} d_1 = I_c \frac{d_1}{d_1 + d_2} = I_a = I_c \frac{V_{cp}}{V_{ac} + V_{cp}}$$

$$\Rightarrow I_a = \frac{V_c}{2R_i \left(\frac{V_{ac}}{V_{cp}} + 1 + DT \frac{R_i V_{ac}}{L V_c} \right)}$$

Large-Signal to Small-Signal

- We have large-signal equations that we must linearize

$$I_c = f(V_c, V_{ac}, V_{cp}) \quad I_a = f(V_c, V_{ac}, V_{cp})$$

- Apply partial differentiation to I_a and I_c

$$\hat{i}_c = \frac{\partial I_c(V_c, V_{ac}, V_{cp})}{\partial V_c} \hat{v}_c + \frac{\partial I_c(V_c, V_{ac}, V_{cp})}{\partial V_{ac}} \hat{v}_{ac} + \frac{\partial I_c(V_c, V_{ac}, V_{cp})}{\partial V_{cp}} \hat{v}_{cp}$$

$$\hat{i}_c = k_1 \hat{v}_c + k_2 \hat{v}_{ac} + k_3 \hat{v}_{cp}$$

$$\hat{i}_a = \frac{\partial I_a(V_c, V_{ac}, V_{cp})}{\partial V_c} \hat{v}_c + \frac{\partial I_a(V_c, V_{ac}, V_{cp})}{\partial V_{ac}} \hat{v}_{ac} + \frac{\partial I_a(V_c, V_{ac}, V_{cp})}{\partial V_{cp}} \hat{v}_{cp}$$

$$\hat{i}_a = k_4 \hat{v}_c + k_5 \hat{v}_{ac} + k_6 \hat{v}_{cp}$$

Small-Signal Expressions

□ Calculate and collect all individual coefficients

$$k_1 = \frac{L_p V_c (V_{ac} + V_{cp}) (L_p V_c V_{ac} + L_p V_c V_{cp} + 2 \cdot DT \cdot R_i V_{ac} V_{cp})}{2R_i (L_p V_c V_{ac} + L_p V_c V_{cp} + DT \cdot R_i V_{ac} V_{cp})^2} \quad k_2 = -\frac{DT \cdot L_p V_c^2 V_{cp}^2}{2(L_p V_c V_{ac} + L_p V_c V_{cp} + DT \cdot R_i V_{ac} V_{cp})^2}$$

$$k_3 = -\frac{DT \cdot L_p V_c^2 V_{ac}^2}{2(L_p V_c V_{ac} + L_p V_c V_{cp} + DT \cdot R_i V_{ac} V_{cp})^2} \quad \text{Terms for } I_c$$

$$k_4 = \frac{L_p V_c V_{cp} (L_p V_c V_{ac} + L_p V_c V_{cp} + 2 \cdot DT \cdot R_i V_{ac} V_{cp})}{2R_i (L_p V_c V_{ac} + L_p V_c V_{cp} + DT \cdot R_i V_{ac} V_{cp})^2} \quad k_5 = -\frac{V_c \left(\frac{1}{V_{cp}} + \frac{DT \cdot R_i}{L_p V_c} \right)}{2R_i \left(\frac{V_{ac}}{V_{cp}} + \frac{DT \cdot R_i V_{ac}}{L_p V_c} + 1 \right)^2}$$

$$k_6 = \frac{V_c V_{ac}}{2R_i V_{cp}^2 \left(\frac{V_{ac}}{V_{cp}} + \frac{DT \cdot R_i V_{ac}}{L_p V_c} + 1 \right)^2} \quad \text{Terms for } I_a$$



A Small-Signal PWM Switch Model in QR

- Associate current sources together to form the small-signal model

parameters


Vout=12
 Vin=100
 Pout=70
 Lp=450u
 Ri=0.25
 N=1/7.5
 Cout=1500u
 ESR=50m
 Rload=Vout^2/Pout
 Vc=947m

Clump=200p
 nv=6
 DT=(2*nv-1)*3.14159*sqrt(Lp*Clump)

Vac=Vin
 Vcp=Vout/N

A=(Lp*Vc*Vac+Lp*Vc*Vcp+DT*Ri*Vac*Vcp)^2
 B=(Lp*Vc*Vac+Lp*Vc*Vcp+2*DT*Ri*Vac*Vcp)
 C=2*Ri*((Vac/Vcp)+DT*Ri*Vac/(Lp*Vc)+1)^2
 k1=Lp*Vc*(Vac+Vcp)*B/(2*Ri*A)
 k2=-DT*Lp*Vc^2*Vcp^2/(2*A)
 k3=-DT*Lp*Vc^2*Vac^2/(2*A)
 k4=Lp*Vc*Vcp*B/(2*Ri*A)
 k5=-Vc*((1/Vcp)+DT*Ri/(Lp*Vc))/C
 k6=Vc*Vac/(Vcp^2*C)

Deadtime calculations

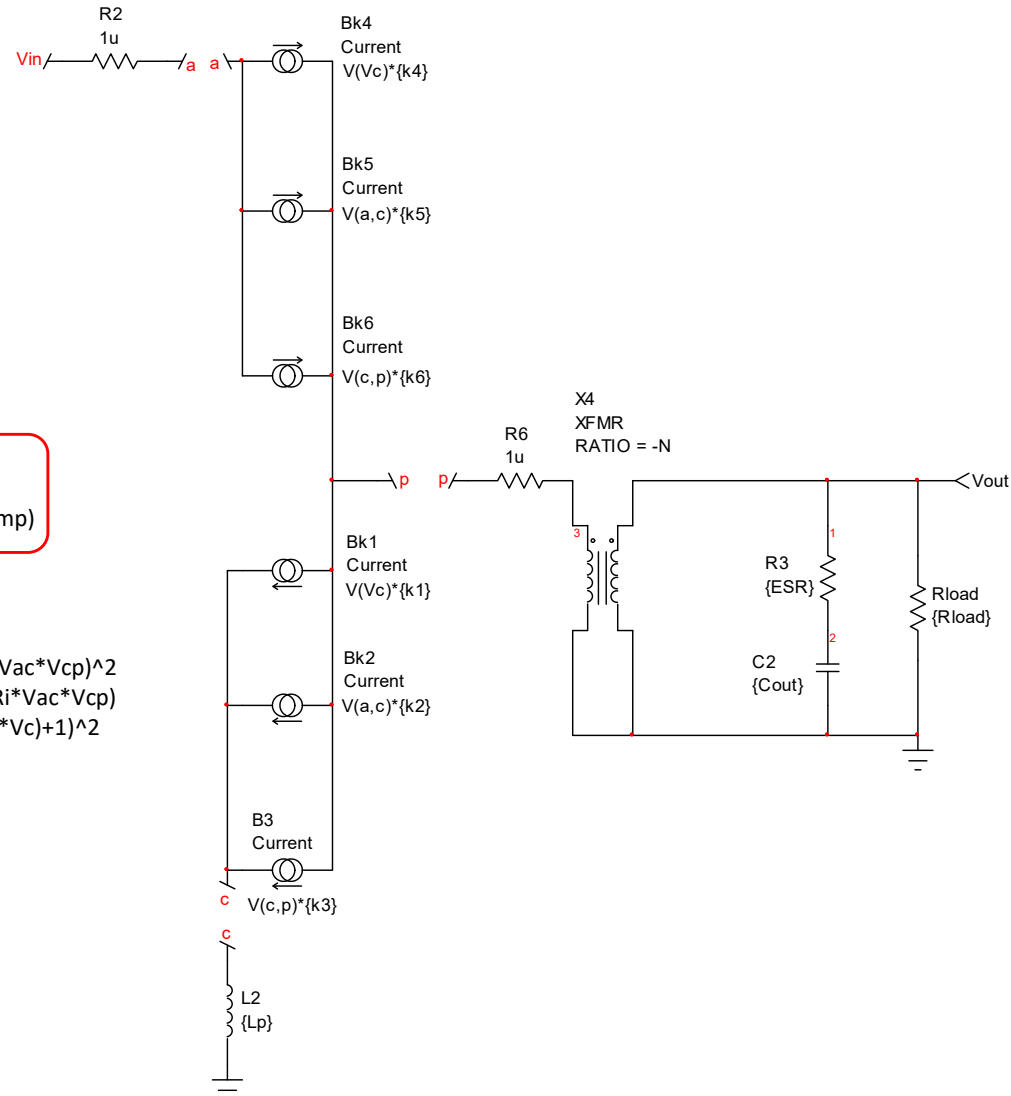

Build a SPICE Model

□ Modify the original QR model to account for valley switching

```
.subckt PWMQR a c p vc ton fsw params : L=1.2m Ri=0.5 DT=1
```

```
*
```

```
* This subckt is a current-mode BCM model, version 1
```

```
*
```

```
.subckt limit d dc params: clampH=0.99 clampL=16m
```

```
*
```

```
Gd 0 dcx d 0 100u
```

```
Rdc dcx 0 10k
```

```
V1 clpn 0 {clampL}
```

```
V2 clpp 0 {clampH}
```

```
D1 clpn dcx dclamp
```

```
D2 dcx clpp dclamp
```

```
Bdc dc 0 V=V(dcx)
```

```
.model dclamp d n=0.01 rs=100m
```

```
.ENDS
```

```
*
```

```
Btsw tsw 0 V= ( V(vc)*{L}/{Ri} ) * ( 1/v(a,cx) + 1/v(cx,p) )+{DT} ) *1Meg
```

```
Bdc dcx 0 V=V(vc)*{L}/{Ri}*V(a,cx)*(V(tsw)/1Meg)
```

```
Xdc dcx dc limit params: clampH=0.99 clampL=7m
```

```
Blap a p I=I(VM)*V(dc)/(V(dc)+V(d2))
```

```
Bd2 d2 0 V=V(vc)*{L}/{Ri}*V(c,p)*(V(tsw)/1Meg)
```

```
Blpc p cx I=V(vc)/{Ri}
```

```
Blmju cx p I=(v(cx,p)/{L})*V(d2)*(V(tsw)/1Meg)*(1-(V(dc)+V(d2))/2)
```

```
Bton ton 0 V = V(dc)*v(tsw)
```

```
Bfsw fsw 0 V = (1/((V(tsw)/1Meg)))/1k
```

```
Rdum1 vc 0 1Meg
```

```
VM cx c
```


```
*
```

```
.ENDS
```

DT changes in relationship
to valley selection


Compare Analytic to Simulated Curves

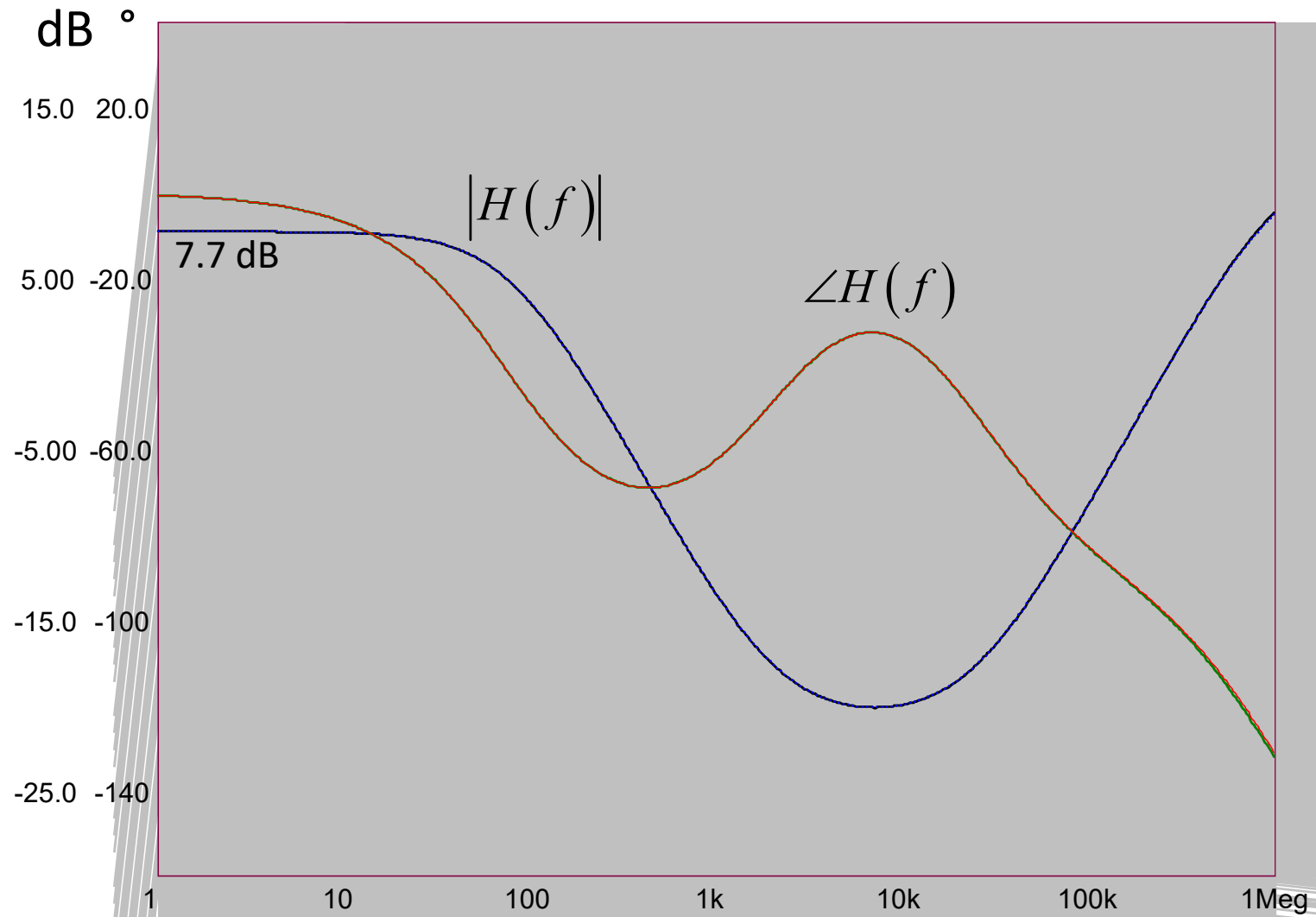- Curves have to be identical before proceeding



Simplify, Simplify and Simplify!

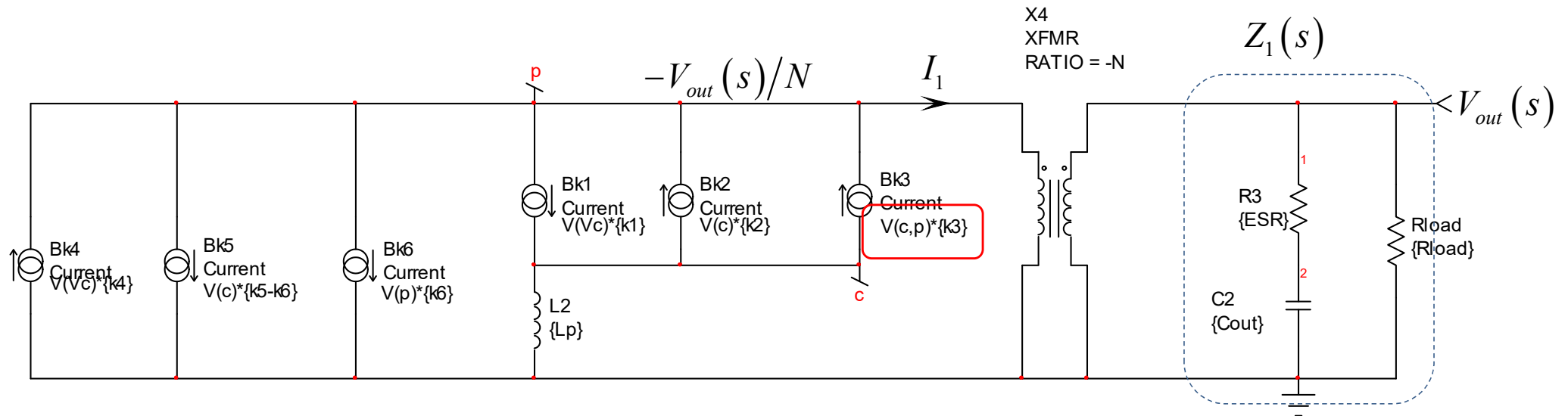- ❑ The key to solving transfer functions is to simplify networks
- ❑ Here, the input voltage is not modulated, hence $V_{(a)}(s) = 0$



$$V_{(c)}(s) = I_c(s) s L_p B_{k_3} = V(c, p) k_3 = V_{(c)} k_3 - V_{(p)} k_3 = k_3 \left(V_{(c)} + \frac{V_{out}}{N} \right)$$

$$V_{(c)}(s) = I_c(s) s L_p$$

$$I_c(s) = V_c(s) k_1 - V_{(c)} k_2 + \left(V_{(c)} + \frac{V_{out}(s)}{N} \right) k_3$$

Solving the Transfer Function

- Substitute $V_{(c)}$ into I_c and solve for I_c

$$I_c(s) = \frac{V_{out}(s)k_3 + NV_c(s)k_1}{N(1 + sL_p k_2 - sL_p k_3)}$$

- The current I_1 entering the transformer is given by:

$$I_1(s) = V_c(s)k_4 - I_c(s)sL_p(k_5 - k_6) + \frac{V_{out}}{N}k_6 - I_c(s)$$

- A nice equation comes out:

$$I_1(s) = -\frac{V_{out}(s)(k_3 - k_6) + NV_c(s)(k_1 - k_4) + sL_p V_{out}(s)(k_3 k_5 - k_2 k_6) + sV_c(s)NL_p(k_5 k_1 - k_2 k_4 - k_1 k_6 + k_3 k_4)}{N[1 + sL_p(k_2 - k_3)]}$$

- This current enters a complex impedance $Z_1(s)$

$$Z_1(s) = \frac{\left(\frac{r_c}{N^2} + \frac{1}{sC_{out}N^2}\right)\frac{R_{load}}{N^2}}{\left(\frac{r_c}{N^2} + \frac{1}{sC_{out}N^2}\right) + \frac{R_{load}}{N^2}} = \frac{R_{load}}{N^2} \frac{1 + sr_c C_{out}}{1 + sC_{out}(R_{load} + r_c)}$$

Rearranging the Raw Expression

□ Collecting $V_{out}(s)$ and $V_c(s)$, we have our transfer function

$$H(s) = \frac{V_{out}(s)}{V_c(s)} = \frac{NR_{load}}{\text{Div} \cdot [N^2 + R_{load}(k_6 - k_3)]} \frac{(1 + sr_C C_{out})(k_1 - k_4 + sL_p(k_1k_5 - k_2k_4 - k_1k_6 + k_3k_4))}{1 + a_1s + a_2s^2}$$

In which we have

$$a_1 = \frac{C_{out}N^2R_{load} + C_{out}N^2r_C + L_pN^2k_2 - L_pN^2k_3 - C_{out}R_{load}k_3r_C + C_{out}R_{load}k_6r_C - L_pR_{load}k_2k_6 - L_pR_{load}k_3k_5}{N^2 + R_{load}(k_6 - k_3)}$$


$$a_2 = \frac{\text{Div} \cdot C_{out}L_p(N^2R_{load}k_3 - N^2R_{load}k_2 - N^2k_2r_C + N^2k_3r_C + R_{load}r_Ck_2k_6 + R_{load}r_Ck_3k_5)}{\text{Div} \cdot [R_{load}(k_3 - k_6) - N^2]}$$

□ Rearranging the formula, we have

$$H(s) = \frac{NR_{load}(k_1 - k_4)}{\text{Div} \cdot [N^2 + R_{load}(k_6 - k_3)]} \frac{(1 + sr_C C_{out}) \left(1 + sL_p \frac{k_1k_5 - k_2k_4 - k_1k_6 + k_3k_4}{k_1 - k_4} \right)}{1 + a_1s + a_2s^2}$$

The Low- Q Approximation

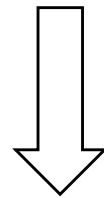- In this expression, we have a quality factor Q : $Q = \frac{\sqrt{a_2}}{a_1}$
- The resonant angular frequency Q is: $\omega_0 = \frac{1}{\sqrt{a_2}}$



With a low Q
2nd order form simplifies

$$1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2 \approx \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \longrightarrow \begin{aligned} \omega_{p1} &= \omega_0 Q \\ \omega_{p2} &= \frac{\omega_0}{Q} \end{aligned}$$

$$\omega_{p1} = \frac{N^2 + R_{load} (k_6 - k_3)}{C_{out} N^2 (R_{load} + r_C) + L_p N^2 (k_2 - k_3) - C_{out} R_{load} r_C (k_6 - k_3) - L_p R_{load} (k_2 k_6 + k_3 k_5)}$$

$$L_p \text{ and } r_C \ll 1 \longrightarrow \omega_{p1} \approx \frac{1}{C_{out} \frac{R_{load} + r_C}{1 + \frac{R_{load} (k_6 - k_3)}{N^2}}}$$



The Complete Expression

- ❑ The second pole is at high frequencies and can be neglected
- ❑ There is a RHP Zero defined as:

$$\omega_{z_2} = \frac{k_1 - k_4}{L_p (k_1 k_5 - k_2 k_4 - k_1 k_6 + k_3 k_4)}$$

- ❑ The dc gain depends on the load and other coefficients


$$H_0 = \frac{NR_{load} (k_1 - k_4)}{\text{Div} \cdot [N^2 + R_{load} (k_6 - k_3)]}$$

- ❑ Finally, the complete transfer function looks like

$$H(s) \approx H_0 \frac{\left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 + \frac{s}{\omega_{z_2}}\right)}{1 + \frac{s}{\omega_{p_1}}}$$

Simulation versus Equations

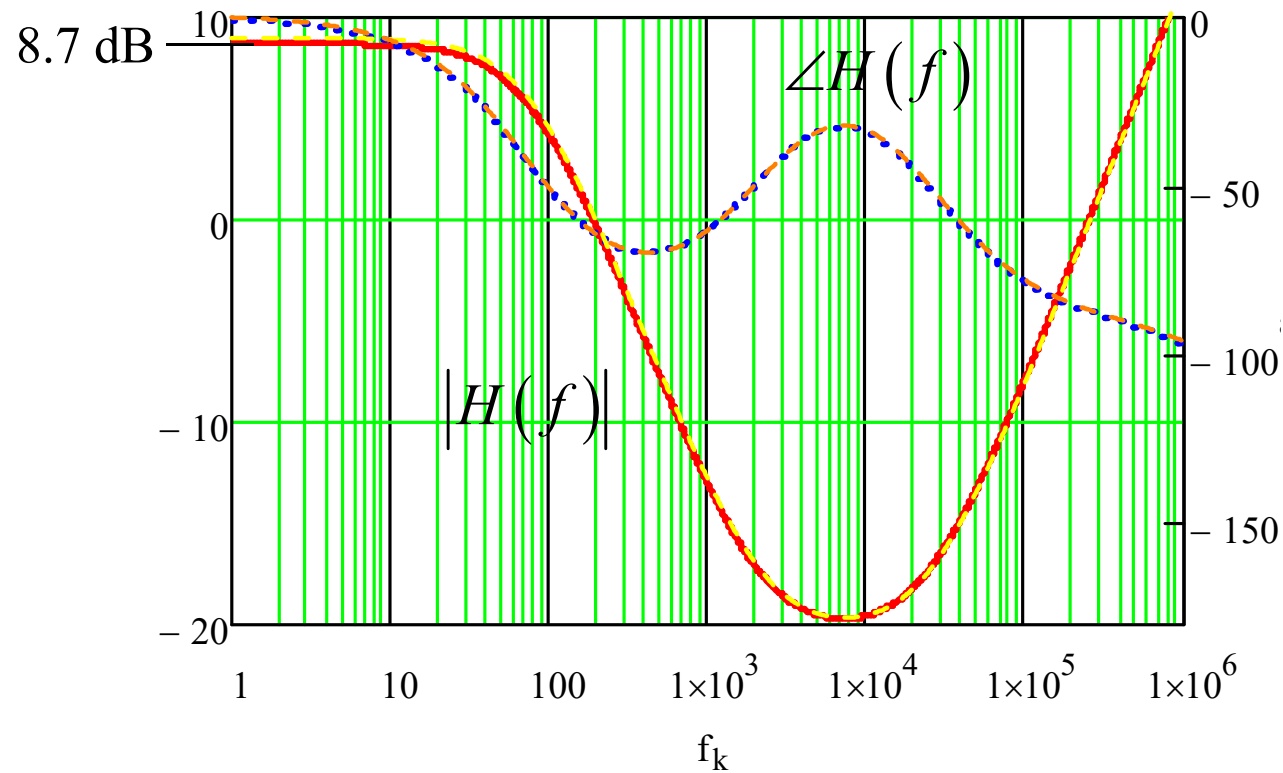
- It is important to test matching between model and equations




1st valley operation

Simulation and Calculations

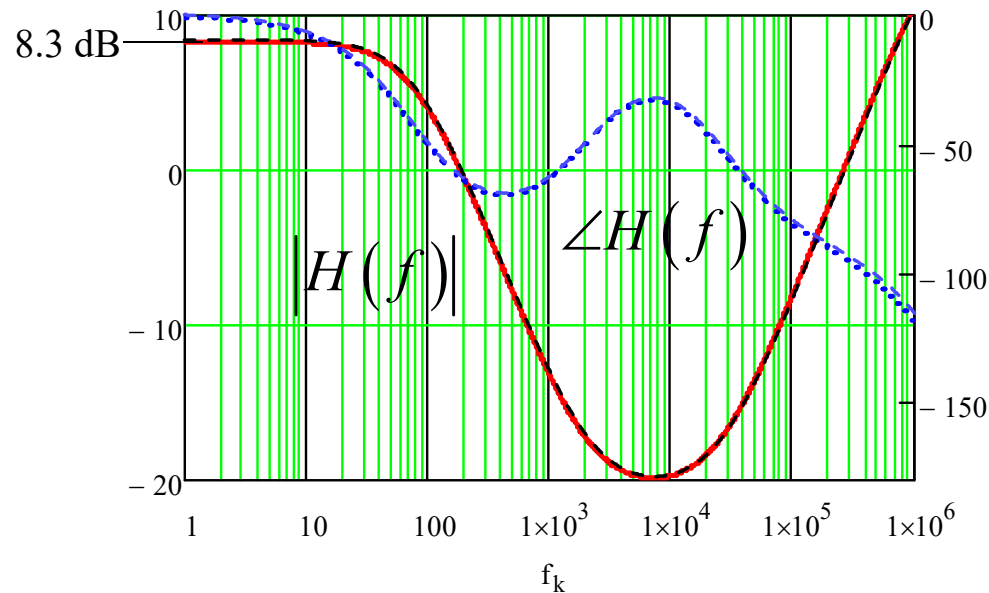- The dc gain slightly changes as valley number is modified



3rd valley operation

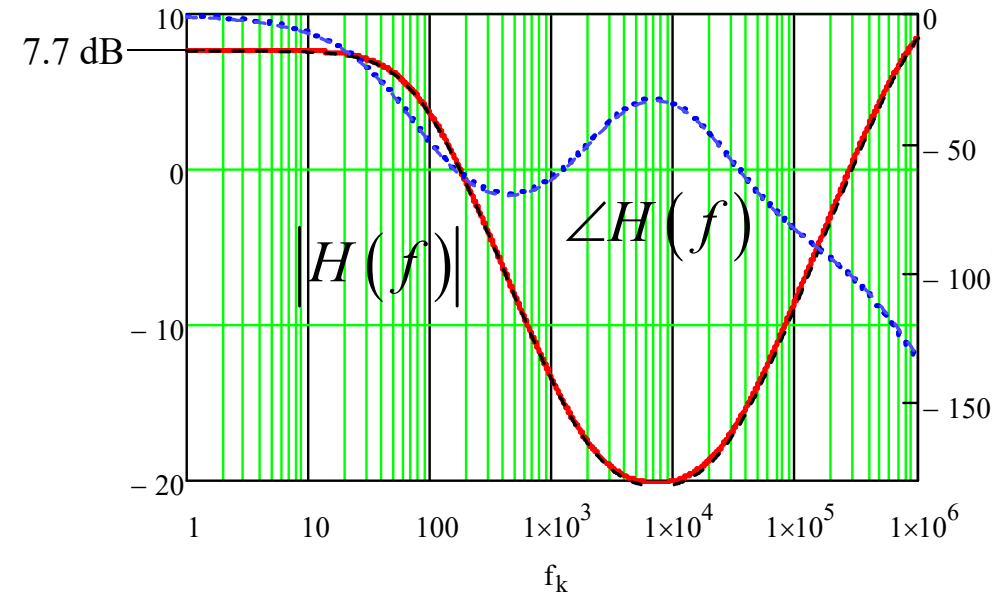


6th valley operation

- The dc gain slightly changes as valley number is modified

Laboratory Tests (1)

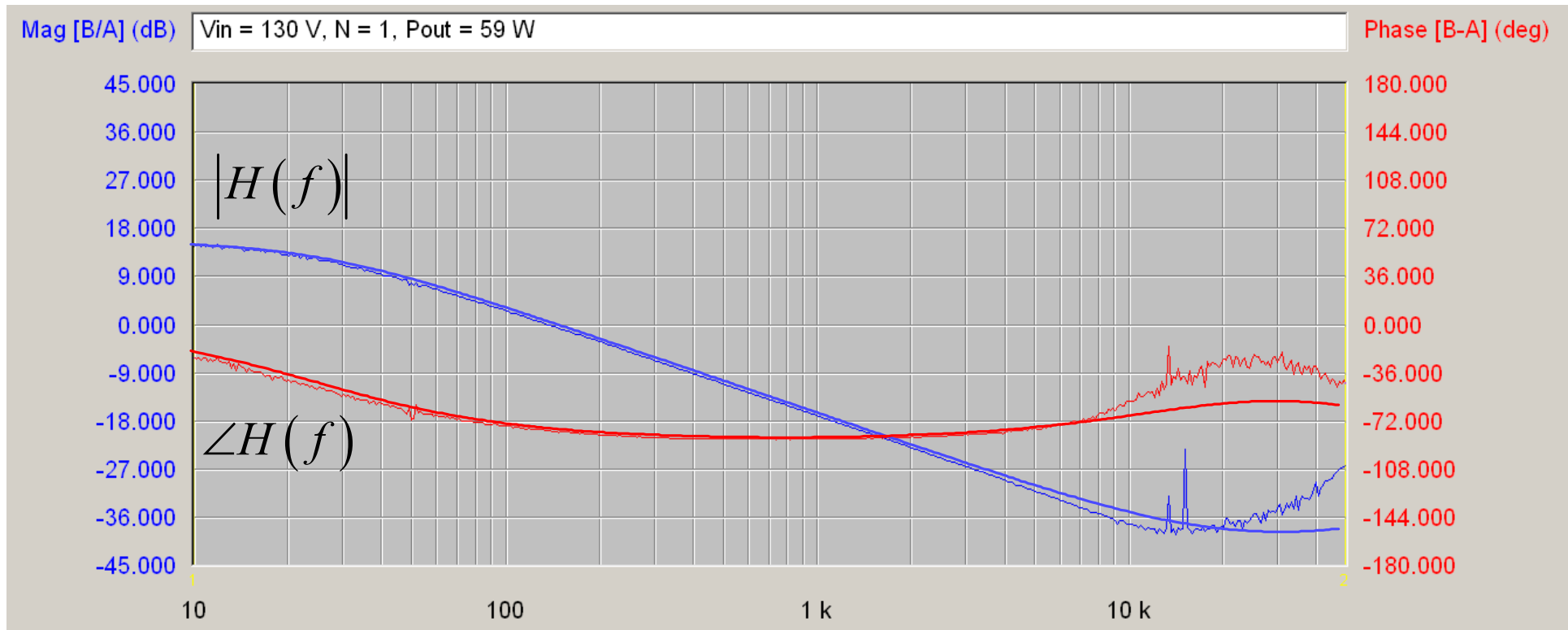
- The low to middle freq. agreement is good, deviation beyond



$$V_{in} = 130 \text{ V, valley} = 1$$

Laboratory Tests (2)

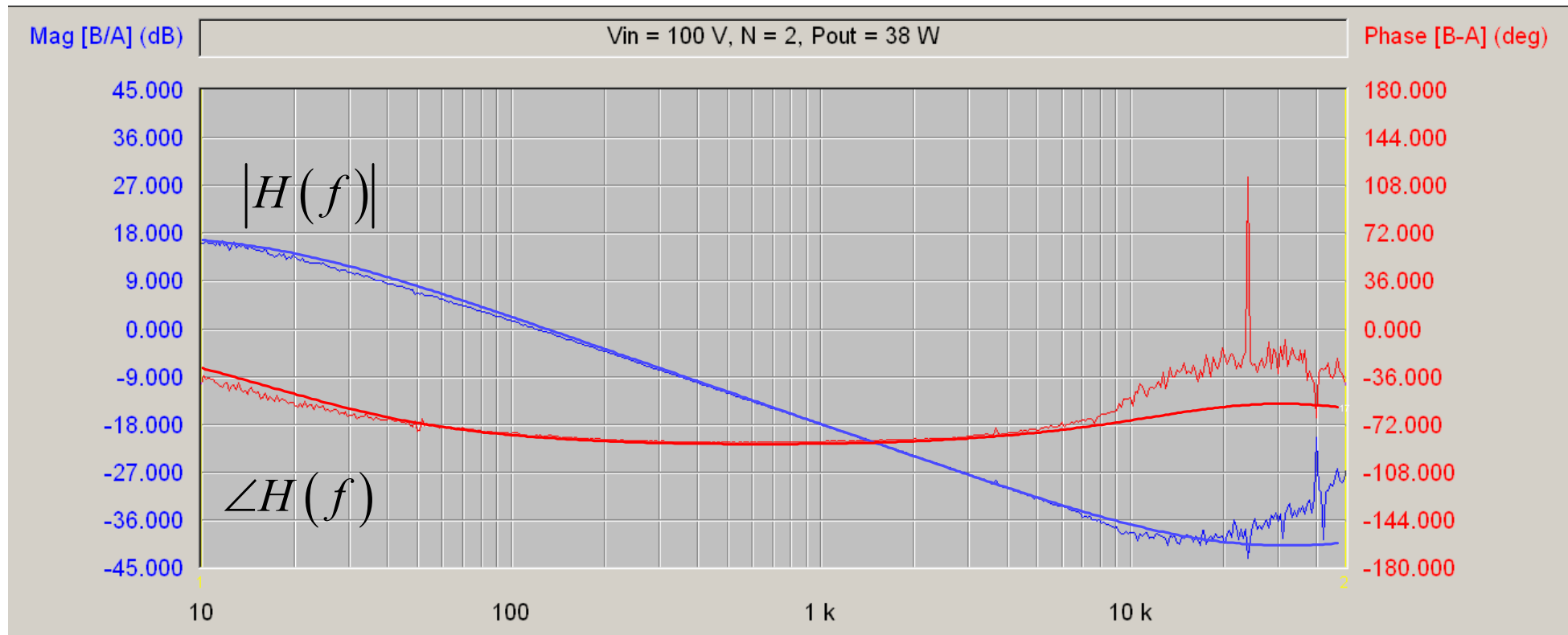
- The output power is changed and valley number 2 is engaged



$$V_{in} = 100 \text{ V, valley} = 2$$

Laboratory Tests (3)

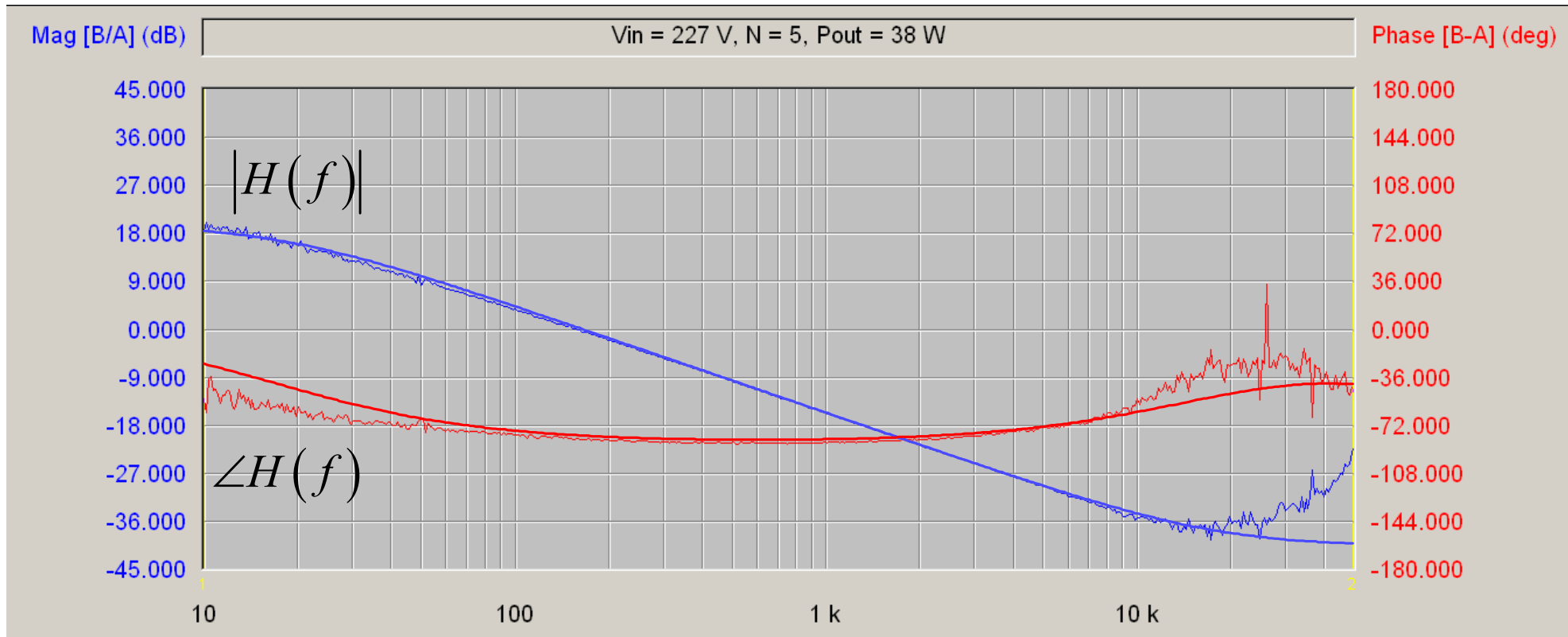- The input voltage is increased and valley changes to 5



$$V_{in} = 227 \text{ V, valley} = 5$$


Course Agenda

- What is a QR Converter?
- Deriving Operating Conditions
- The Over Power Problem
- Three Operating Modes
- Small-Signal Analysis – QR
- Small-Signal Analysis – VCO**
- Compensating with TL431
- Control Loop Design Example
- Conclusion



Where do We Start From?

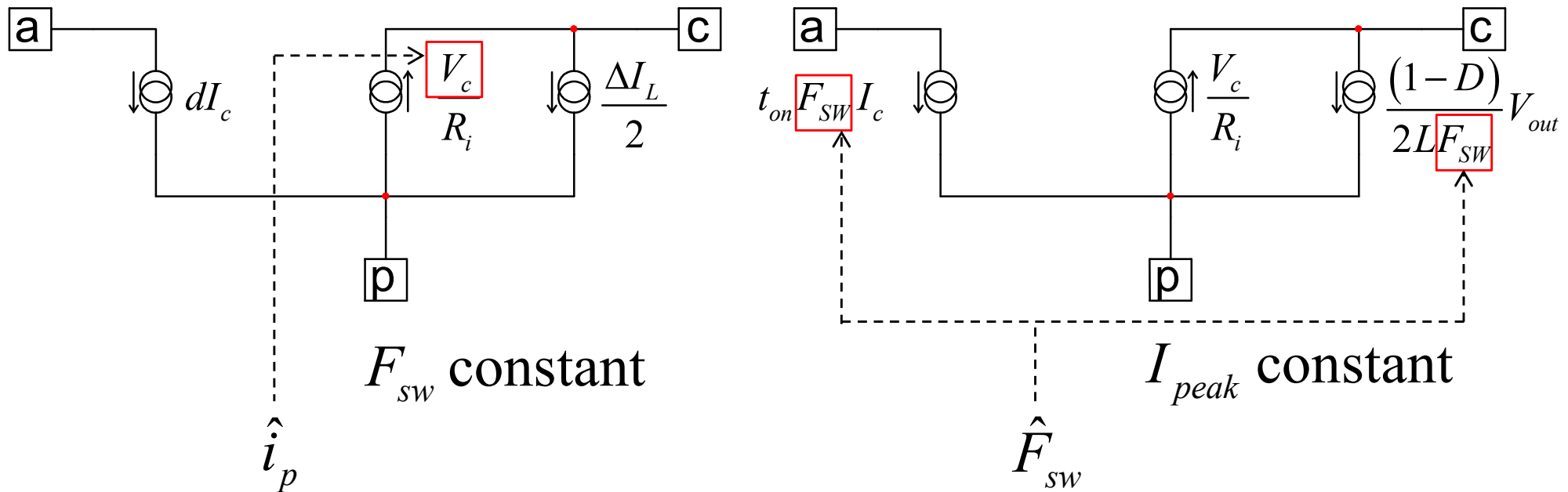
- ❑ We have a DCM peak-current mode control large-signal model
- ❑ The PWM switch controls the peak current at a fixed F_{sw}
- ❑ Why not fixing the peak current and controlling F_{sw} ?



- ❑ The peak current is frozen and the frequency is controlled

A Transient Load Step Response First

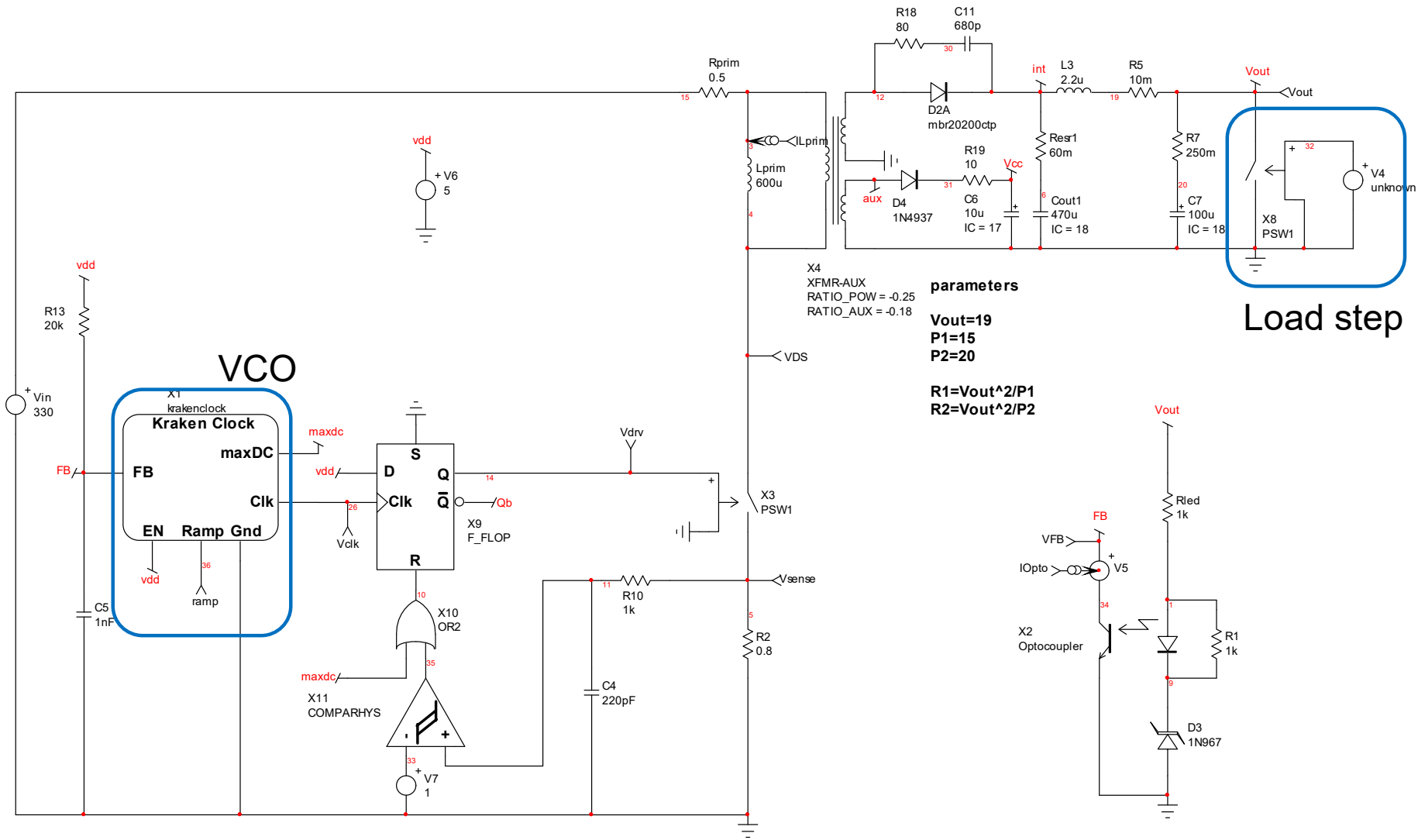□ We can check the cycle-by-cycle response to a load step




Cycle by cycle model

$F_{sw} = 51 \text{ kHz}$



A Transient Load Step Response First

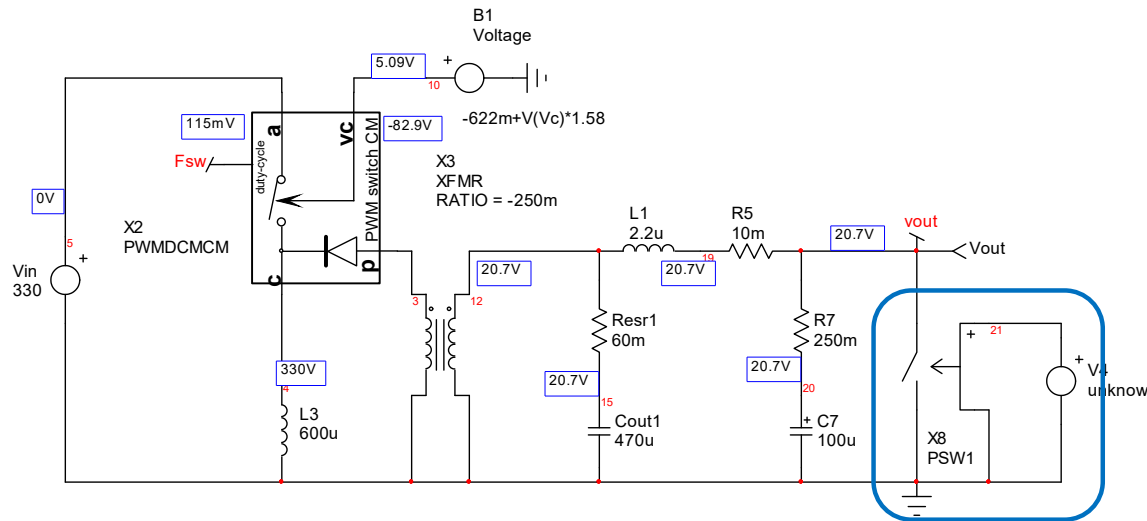
□ And compare it to that of a modified PWM switch model



parameters

Vout=19
P1=15
P2=20

R1=Vout^2/P1
R2=Vout^2/P2

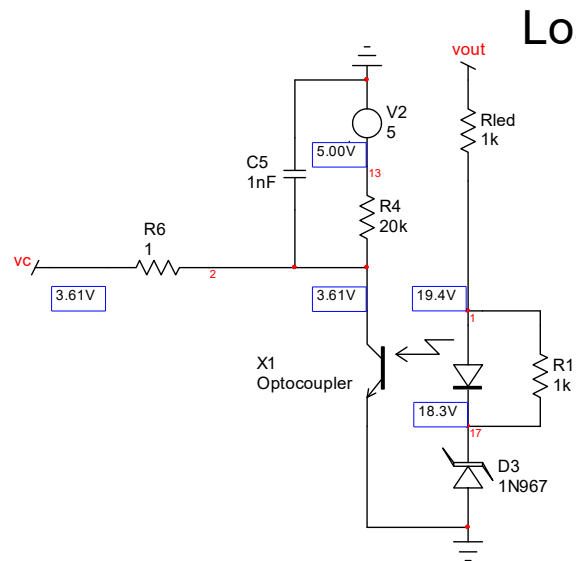

Load step

*
.param {Vc}=1 Current frozen to $1/R_{sense}$
*

```

Bdc dcx 0 V =
{Vc}*V(Fsw)*10k/({Se}+(abs(v(a,c))*{Ri})){L}+1u)
Xdc dcx dc limit params: clampH=0.99
clampL=7m
BVcp 6 p V=(V(dc)/(V(dc)+V(d2)))*V(a,p)
Blap a p I=(V(dc)/(V(dc)+V(d2)))*I(VM)
Bd2 d2X 0 V=(2*I(VM)*{L}-
v(a,c)*V(dc)^2*1/(V(Fsw)*10k)) / (
+v(a,c)*V(dc)*1/(V(Fsw)*10k)+1u )
Xd2 d2X dc d2 limit2
Rdum1 dc 0 1Meg
Rdum2 vc 0 1Meg
RS 7 c 1u
VM 6 7
*
.ENDS
    
```

1 V = 10 kHz

Modified netlist of the PWM switch


Averaged model

$F_{sw} = 50.9 \text{ kHz}$



You Need to Adjust the VCO Modulator

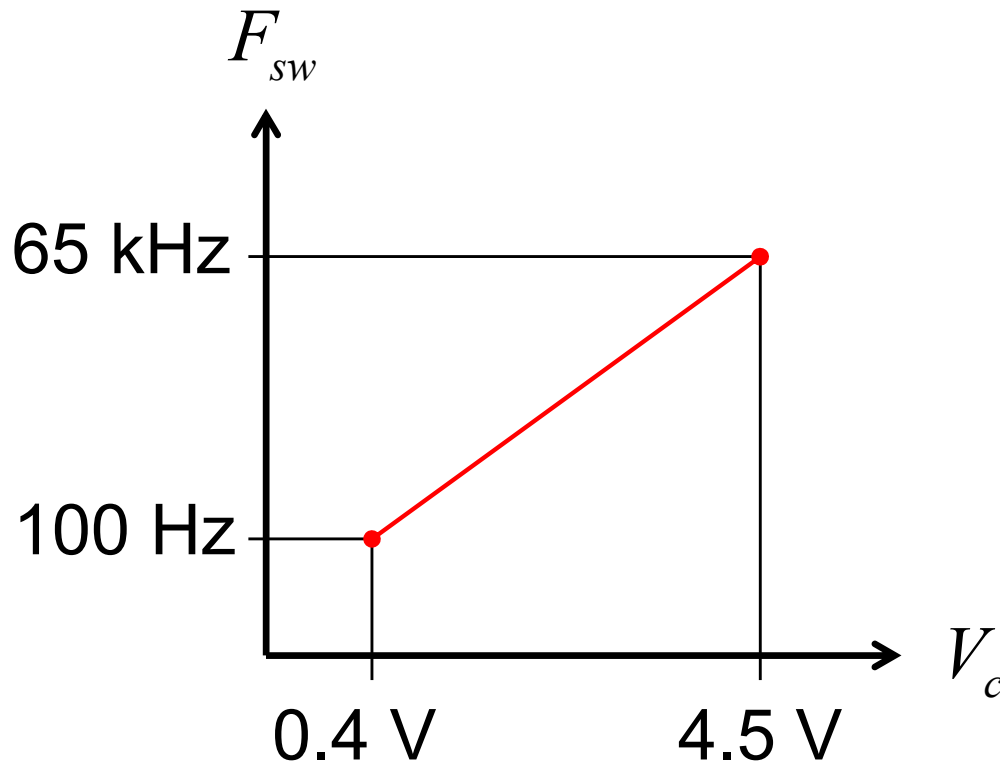- The control voltage to the switching frequency is the VCO gain




$$y = ax + b$$

$$y = \frac{\Delta F_{sw}}{\Delta V_c} = \frac{64.9k}{4.1} = 15.8 \text{ kHz/V}$$

$$100 = ax + b = 0.4 \times 15.8k + b$$

↓ 1/10000 Scaling factor

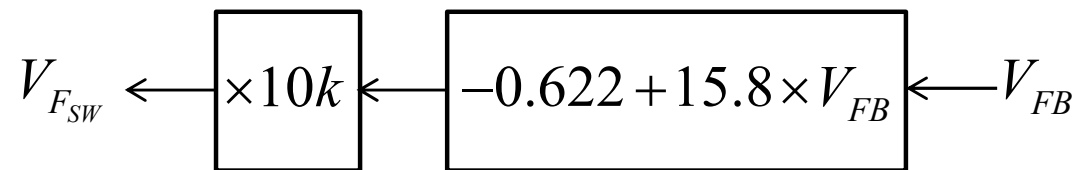
$$b = 0.10 - 0.4 \times 15.8 = -622 \text{ mV}$$



VCO gain G_{VCO} is 15.8 kHz/V


Compare the Transient Responses

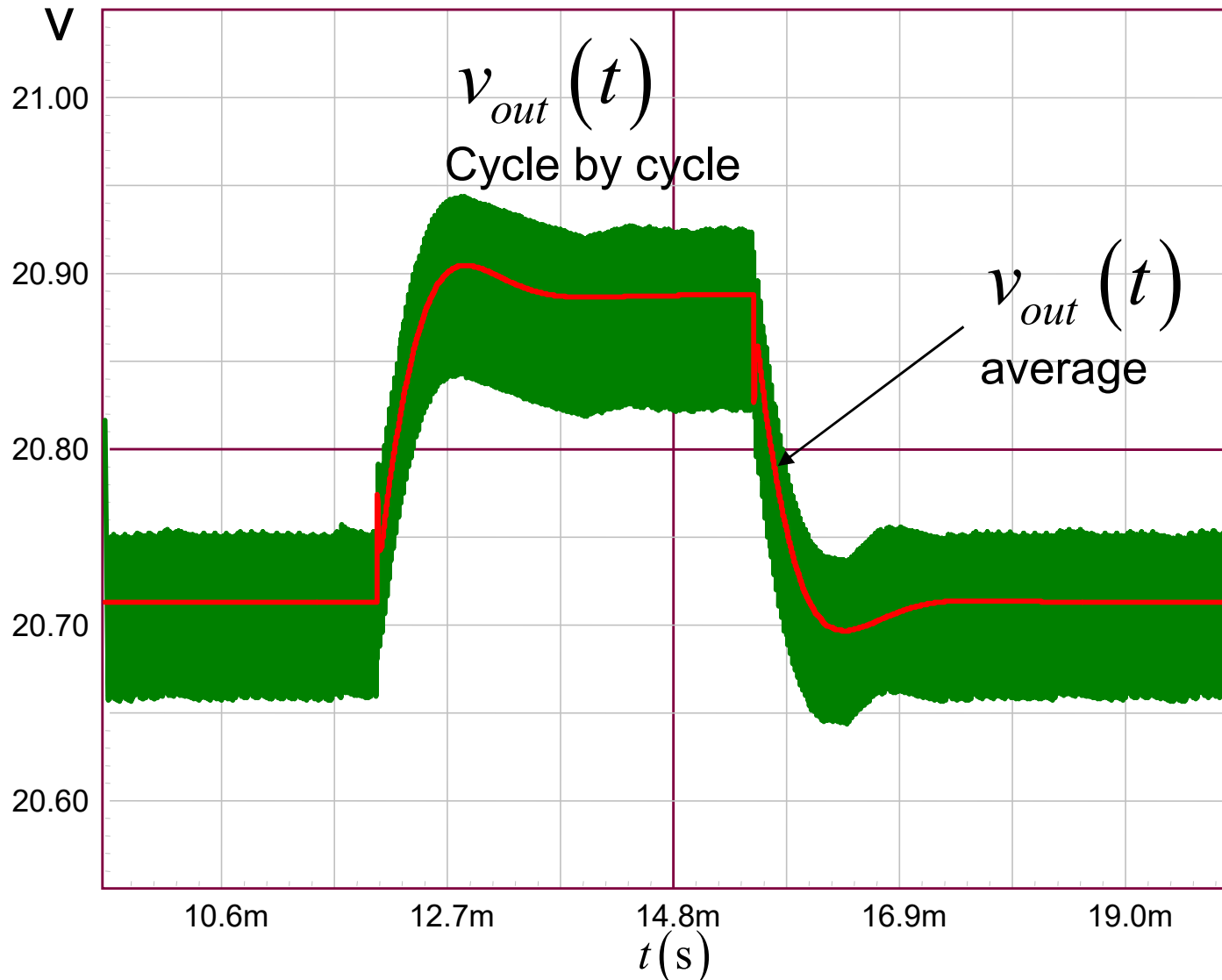- Responses are identical, the averaged version looks correct



Keys of Small-Signal Analysis

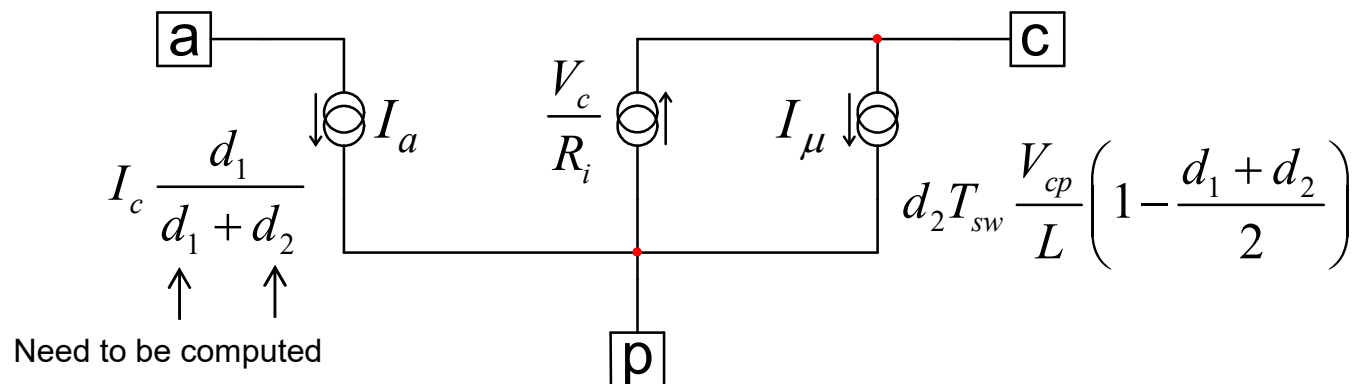- ❑ Rather than going full speed into small-signal analysis:
 - break down the system into smaller parts
 - run simplifications whenever you can
 - go step by step and verify the answer always fits the original



Start from here, DCM model


"Switch-mode Power Supplies: SPICE Simulations and Practical Designs", C. Basso, McGraw-Hill 2008, page 161

Simplifying and Compacting the Model

- Compact the DCM model to suppress variables calculation

$$I_a = I_c \frac{d_1}{d_1 + d_2} \quad I_\mu = \frac{d_2 V_{cp}}{F_{sw} L_p} \left(1 - \frac{d_1 + d_2}{2} \right) \quad \boxed{d_1} = \frac{L_p V_c F_{sw}}{V_{ac} R_i} \quad d_2 = \frac{2 I_c F_{sw} L_p}{d_1 V_{ac}} - \boxed{d_1}$$

substitute

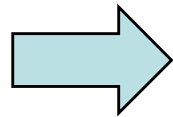

"Let the craziness begin"

$$I_a = I_c \frac{d_1}{d_1 + d_2}$$


$$I_a = \frac{F_{sw} L_p V_c^2}{2 R_i^2 V_{ac}}$$

$$I_\mu = - \frac{V_{cp} (V_c - I_c R_i) (F_{sw} L_p V_c^2 - 2 I_c R_i^2 V_{ac})}{F_{sw} L_p R_i V_c^2 V_{ac}}$$




The New Model Looks Simpler

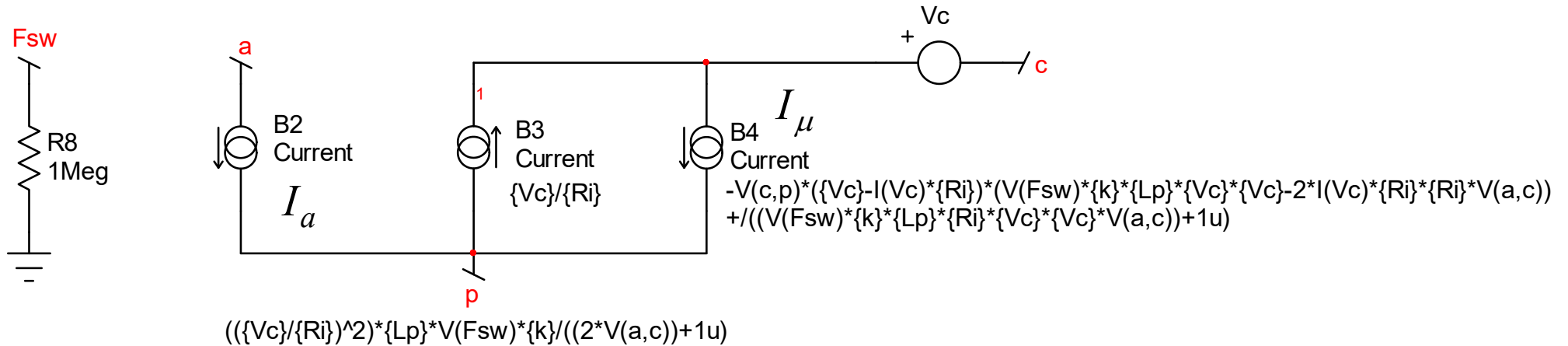- The equations no longer include a computed variable




Check against the complete model

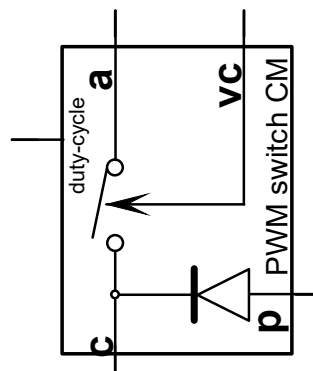

X2
PWMDCMCM

Ac Responses are Similar

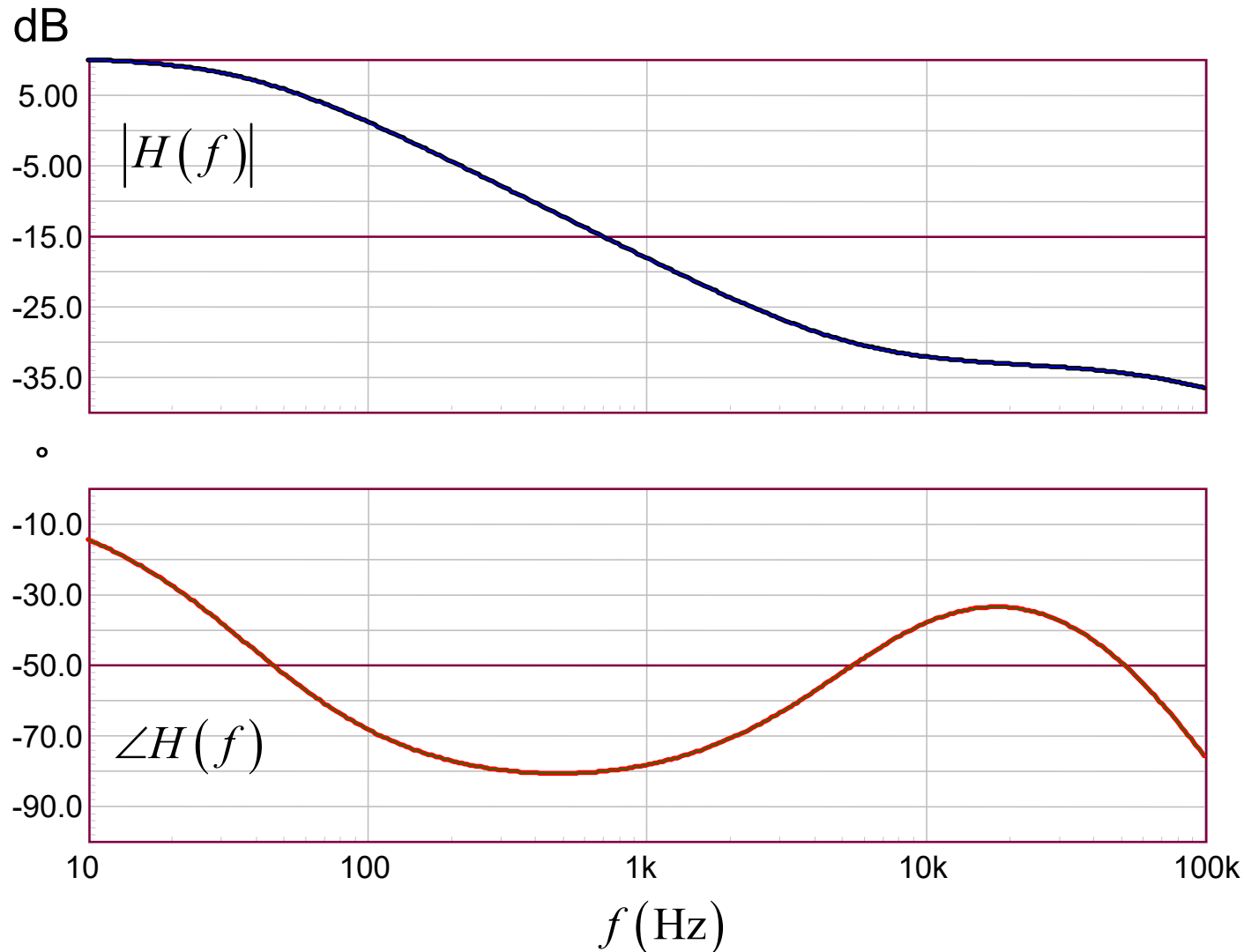- The curves perfectly superimpose, 1st step is ok



Second Step, Linearize the Sources

- ❑ To apply Laplace equations, we need linear elements
- ❑ Linearization can be done in different ways:
 - ✓ perturb all equations with a small quantity (the "hat" notation)
 - ✓ re-arrange the terms and collect dc and ac contributors
 - ❖ can be tedious to re-arrange, you neglect cross products

$$V_1 = R_1 I_1 + D V_3$$

$$V_1 + \hat{v}_1 = R_1 (I_1 + \hat{i}_1) + (\hat{d} + D)(V_3 + \hat{v}_3)$$

$$V_1 = R_1 I_1 + D V_3 \quad \text{dc equation (bias point)}$$

$$\hat{v}_1 = R_1 \hat{i}_1 + \hat{d} V_3 + \underbrace{\hat{d} \hat{v}_3}_{\approx 0} + D \hat{v}_3 \quad \text{ac equation}$$

Second Step, Linearize the Sources

- A second option is to calculate partial derivative coefficients
- ✓ the process can be automated by Mathcad®
- ✓ you only have ac terms, no sort needed

$$V_1(I_1, D, V_3) = R_1 I_1 + D V_3$$

$$dV_1 = \left(\frac{\partial V_1(I_1, D, V)}{\partial I_1} \right) \Big|_{D, V_3} dI_1 + \frac{\partial V_1(I_1, D, V)}{\partial D} \Big|_{I_1, V_3} dD + \frac{\partial V_1(I_1, D, V)}{\partial V_3} \Big|_{D, I_1} dV_3$$

$$\hat{v}_1 = \frac{\partial V_1(I_1, D, V)}{\partial I_1} \Big|_{D, V_3} \hat{i}_1 + \frac{\partial V_1(I_1, D, V)}{\partial D} \Big|_{I_1, V_3} \hat{d} + \frac{\partial V_1(I_1, D, V)}{\partial V_3} \Big|_{D, I_1} \hat{v}_3$$

$$\hat{v}_1 = R_1 \hat{i}_1 + D \hat{v}_3 + \hat{d} V_3$$

ac equation, no cross products



Second Step, Linearize the Sources

- Now, identify the variables in each source

$$I_a = \frac{F_{sw} L_p V_c^2}{2R_i^2 V_{ac}} \longrightarrow \frac{F_{sw}}{V_{ac}}$$

$$I_\mu = -\frac{V_{cp} (V_c - I_c R_i) (F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw} L_p R_i V_c^2 V_{ac}} \longrightarrow \begin{matrix} V_{cp} \\ V_{ac} \\ F_{sw} \\ I_c \end{matrix}$$

- 6 variables imply six partial derivatives, 6 coefficients


- You must identify these static variables first

- Look at the PWM switch configuration



Identify the Variables in the Schematic

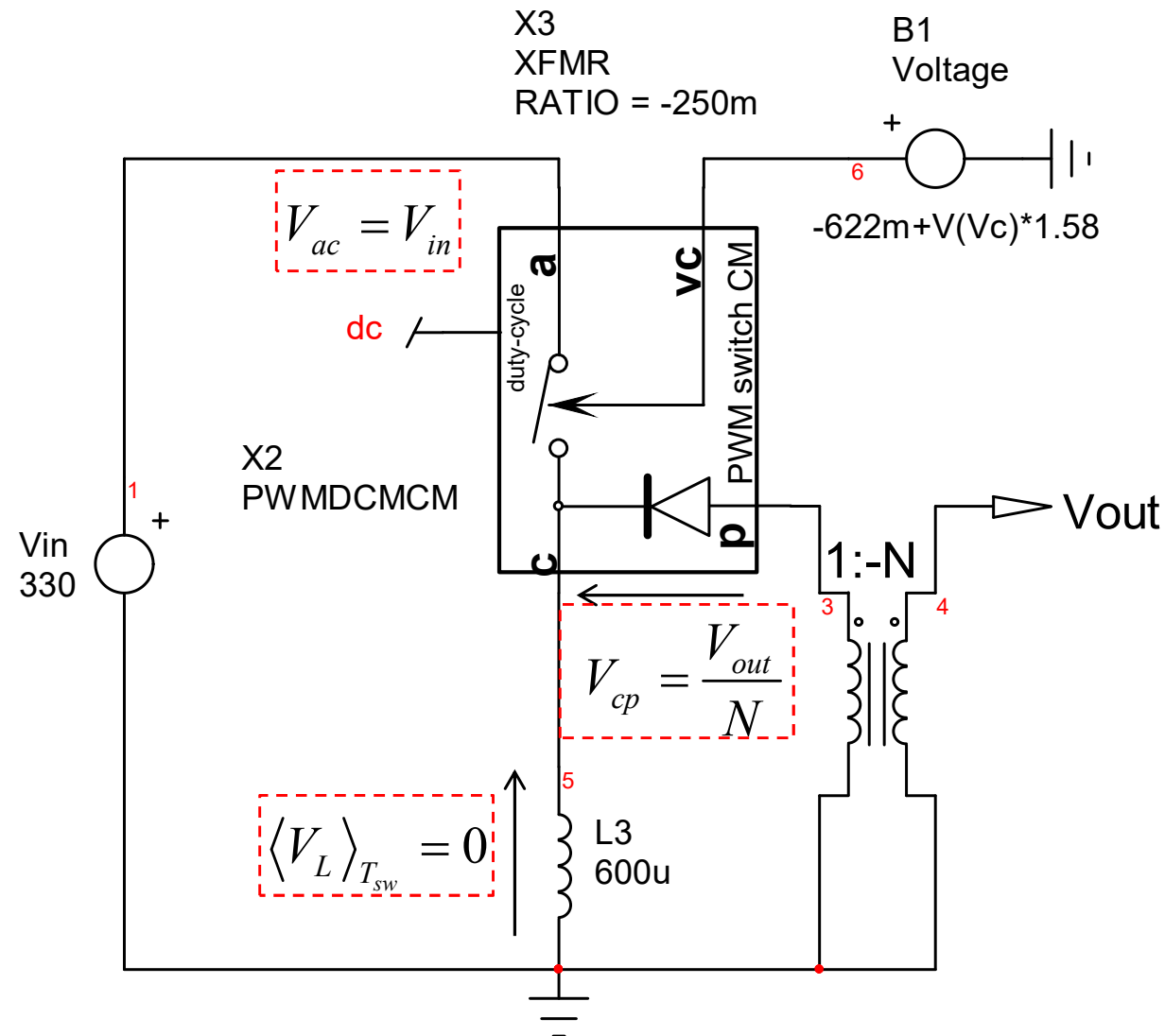- the average voltage across L_3 is 0: point c is grounded.



Sources Derivation

□ We can now individually derive all these sources

$$I_a = \frac{F_{sw} L_p V_c^2}{2R_i^2 V_{ac}}$$

$$\hat{i}_a = \left(\frac{\partial I_a}{\partial F_{sw}} \right)_{V_{ac}} \hat{F}_{sw} + \left(\frac{\partial I_a}{\partial V_{ac}} \right)_{F_{sw}} \hat{v}_{ac}$$

$$k_1 = \frac{L_p V_c^2}{2R_i^2 V_{ac}}$$

$$k_2 = -\frac{F_{sw} L_p V_c^2}{2R_i^2 V_{ac}^2}$$

$$I_\mu = -\frac{V_{cp} (V_c - I_c R_i) (F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw} L_p R_i V_c^2 V_{ac}}$$

$$\hat{i}_\mu = \left(\frac{\partial I_\mu}{\partial V_{cp}} \right)_{I_c, F_{sw}, V_{ac}} \hat{v}_{cp} + \left(\frac{\partial I_\mu}{\partial I_c} \right)_{F_{sw}, V_{cp}, V_{ac}} \hat{i}_c + \left(\frac{\partial I_\mu}{\partial F_{sw}} \right)_{I_c, V_{cp}, V_{ac}} \hat{F}_{sw} + \left(\frac{\partial I_\mu}{\partial V_{ac}} \right)_{V_{cp}, I_c, F_{sw}} \hat{v}_{ac}$$

k_3

k_4

k_5

k_6



Sources Derivation

□ Yes, Mathcad[®] or an equivalent software is of great help...

$$k_3 = -\frac{(V_c - I_c R_i)(F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw} L_p R_i V_c^2 V_{ac}}$$

$$k_4 = \frac{V_{cp} (F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw} L_p V_c^2 V_{ac}} + \frac{2R_i V_{cp} (V_c - I_c R_i)}{F_{sw} L_p V_c^2}$$

$$k_5 = \frac{V_{cp} (V_c - I_c R_i)(F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw}^2 L_p R_i V_c^2 V_{ac}} - \frac{V_{cp} (V_c - I_c R_i)}{F_{sw} R_i V_{ac}}$$

$$k_6 = \frac{V_{cp} (V_c - I_c R_i)(F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw} L_p R_i V_c^2 V_{ac}^2} + \frac{2I_c R_i V_{cp} (V_c - I_c R_i)}{F_{sw} L_p V_c^2 V_{ac}}$$



Evaluate all These Coefficients

- Select a converter at a certain operating point

$$V_{out} = 21.1 \text{ V}$$

$$R_{load} = 18 \ \Omega$$

$$R_i = 0.8 \ \Omega$$

$$V_c = 1 \text{ V}$$

$$V_{ac} = 330 \text{ V}$$

$$r_C = 0.06 \ \Omega$$

$$C_{out} = 470 \ \mu\text{F}$$

$$N_1 = 0.25$$

$$V_{cp} = \frac{V_{out}}{N_1} = 84.4 \text{ V}$$

$$L_p = 600 \ \mu\text{H}$$

$$k_F = 10000$$

$$F_{sw} = \frac{2I_{out}R_i^2V_{out}}{L_pV_c^2} = 52.8 \text{ kHz}$$


$$I_c = \frac{F_{sw}L_pV_c^2(V_{ac} + V_{cp})}{2R_i^2V_{ac}V_{cp}} = 0.368 \text{ A}$$

$$I_a = \frac{F_{sw}L_pV_c^2}{2R_i^2V_{ac}} = 0.075 \text{ A}$$

$$I_\mu = 0.882 \text{ A}$$



Test the Coefficient Values with the Sources

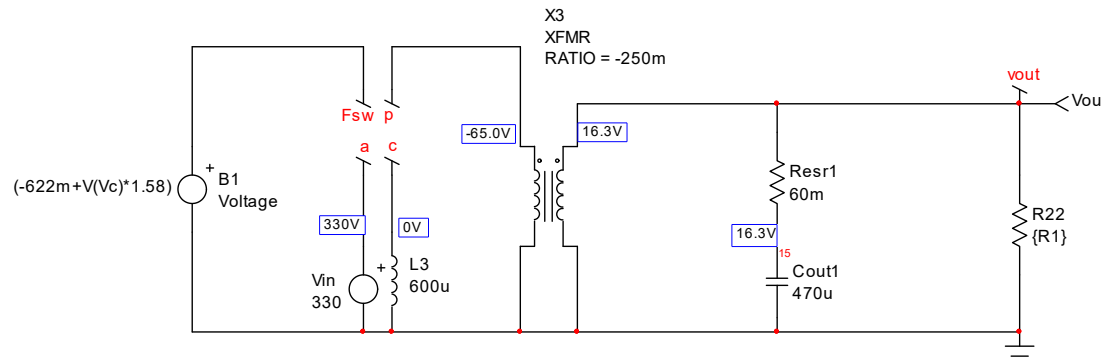□ Capture a new schematic with the linearized sources




parameters

Vout=21.1
P1=24.73
R1=Vout^2/P1

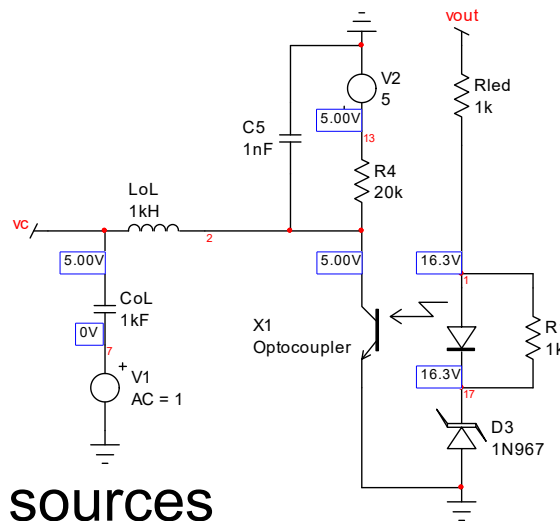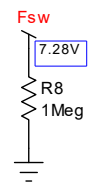

Linearized sources

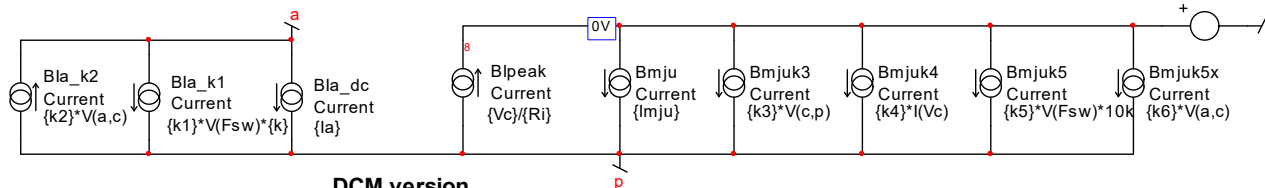

DCM version

parameters


Vc=1
Lp=600u
Ri=0.8
Lp=600u
k=10k
N=250m
Fsw=52.766k
Iout=P1/Vout
Vac=330
Vcp=Vout/N
Ia=Fsw*Lp*Vc^2/(2*Ri^2*Vac)
k1=(Lp*Vc^2)/(2*Ri^2*Vac)
k2=(Fsw*Lp*Vc^2)/(2*Ri^2*Vac^2)
AA=Fsw*Lp*Vc^2*Vac+Fsw*Lp*Vc^2*Vcp
BB=2*Ri^2*Vac*Vcp
Ic=AA/BB
A=-Vcp*(Vc-Ic*Ri)*(Fsw*Lp*Vc^2-2*Ic*Ri^2*Vac)
B=Fsw*Lp*Ri*Vc^2*Vac
Imju=A/B
AAA=-(Vc-Ic*Ri)*(Fsw*Lp*Vc^2-2*Ic*Ri^2*Vac)
BBB=Fsw*Lp*Ri*Vc^2*Vac
k3=AAA/BBB
k4A=Vcp*(Fsw*Lp*Vc^2-2*Ic*Ri^2*Vac)
k4B=Fsw*Lp*Vc^2*Vac
k4C=2*Ri*Vcp*(Vc-Ic*Ri)/(Fsw*Lp*Vc^2)
k4=(k4A/k4B)+k4C
k5A=Vcp*(Vc-Ic*Ri)*(Fsw*Lp*Vc^2-2*Ic*Ri^2*Vac)
k5B=Fsw^2*Lp*Ri*Vc^2*Vac
k5C=Vcp*(Vc-Ic*Ri)/(Fsw*Ri*Vac)
k5=(k5A/k5B)-k5C
k6A=Vcp*(Vc-Ic*Ri)*(Fsw*Lp*Vc^2-2*Ic*Ri^2*Vac)
k6B=Fsw*Lp*Ri*Vc^2*Vac^2
k6C=2*Ic*Ri*Vcp*(Vc-Ic*Ri)/(Fsw*Lp*Vc^2*Vac)
k6=(k6A/k6B)+k6C

Mathcad[®] coefficients



Responses with Previous Models are Similar

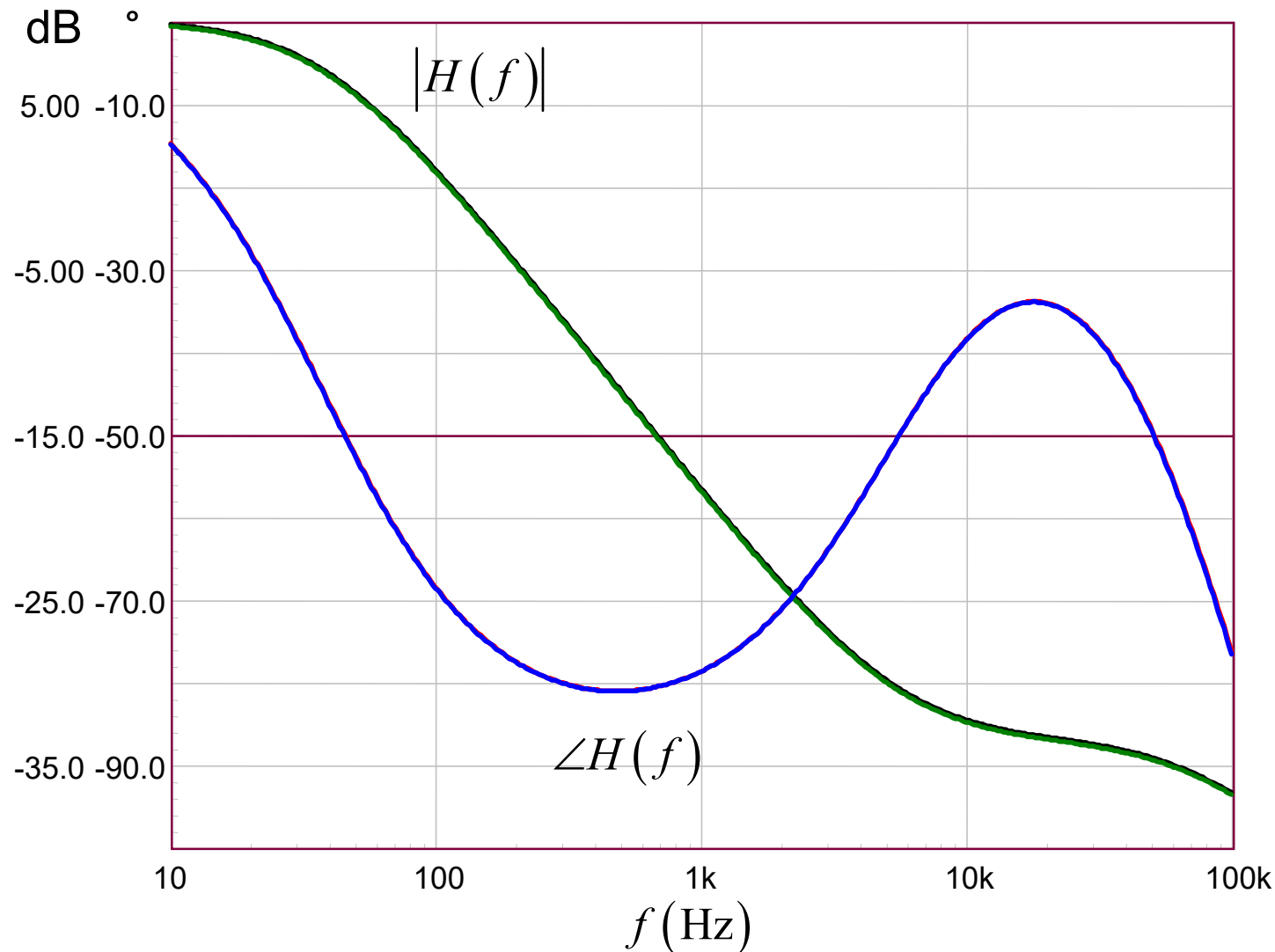
- The curves perfectly superimpose, 2nd step is ok



Combine and Arrange the Sources

Now, re-arrange the sources in a more convenient way

Ac response is ok!

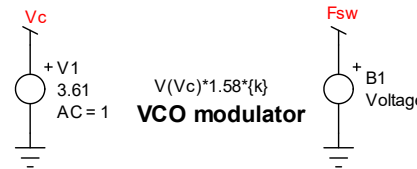

X3
XFMR
RATIO = -N


DCM version
small-signal model
ac only

parameters

Vout=21.1
P1=24.73
R1=Vout^2/P1

parameters

Vc=1
Lp=600u
Ri=0.8
Lp=600u
k=10k
N=250m
Fsw=52.766k
Iout=P1/Vout
Vac=330
Vcp=Vout/N
Ia=Fsw*Lp*Vc^2/(2*Ri^2*Vac)
k1=(Lp*Vc^2)/(2*Ri^2*Vac)
k2=(Fsw*Lp*Vc^2)/(2*Ri^2*Vac^2)
AA=Fsw*Lp*Vc^2*Vac+Fsw*Lp*Vc^2*Vcp
BB=2*Ri^2*Vac*Vcp
Ic=AA/BB
A=-Vcp*(Vc-Ic*Ri)*(Fsw*Lp*Vc^2-2*Ic*Ri^2*Vac)
B=Fsw*Lp*Ri*Vc^2*Vac
Imju=A/B
AAA=-(Vc-Ic*Ri)*(Fsw*Lp*Vc^2-2*Ic*Ri^2*Vac)
BBB=Fsw*Lp*Ri*Vc^2*Vac
k3=AAA/BBB
Rk3=1/k3
k4A=Vcp*(Fsw*Lp*Vc^2-2*Ic*Ri^2*Vac)
k4B=Fsw*Lp*Vc^2*Vac
k4C=2*Ri*Vcp*(Vc-Ic*Ri)/(Fsw*Lp*Vc^2)
k4=(k4A/k4B)+k4C
k5A=Vcp*(Vc-Ic*Ri)*(Fsw*Lp*Vc^2-2*Ic*Ri^2*Vac)
k5B=Fsw^2*Lp*Ri*Vc^2*Vac
k5C=Vcp*(Vc-Ic*Ri)/(Fsw*Ri*Vac)
k5=(k5A/k5B)-k5C
k6A=Vcp*(Vc-Ic*Ri)*(Fsw*Lp*Vc^2-2*Ic*Ri^2*Vac)
k6B=Fsw*Lp*Ri*Vc^2*Vac^2
k6C=2*Ic*Ri*Vcp*(Vc-Ic*Ri)/(Fsw*Lp*Vc^2*Vac)
k6=(k6A/k6B)+k6C

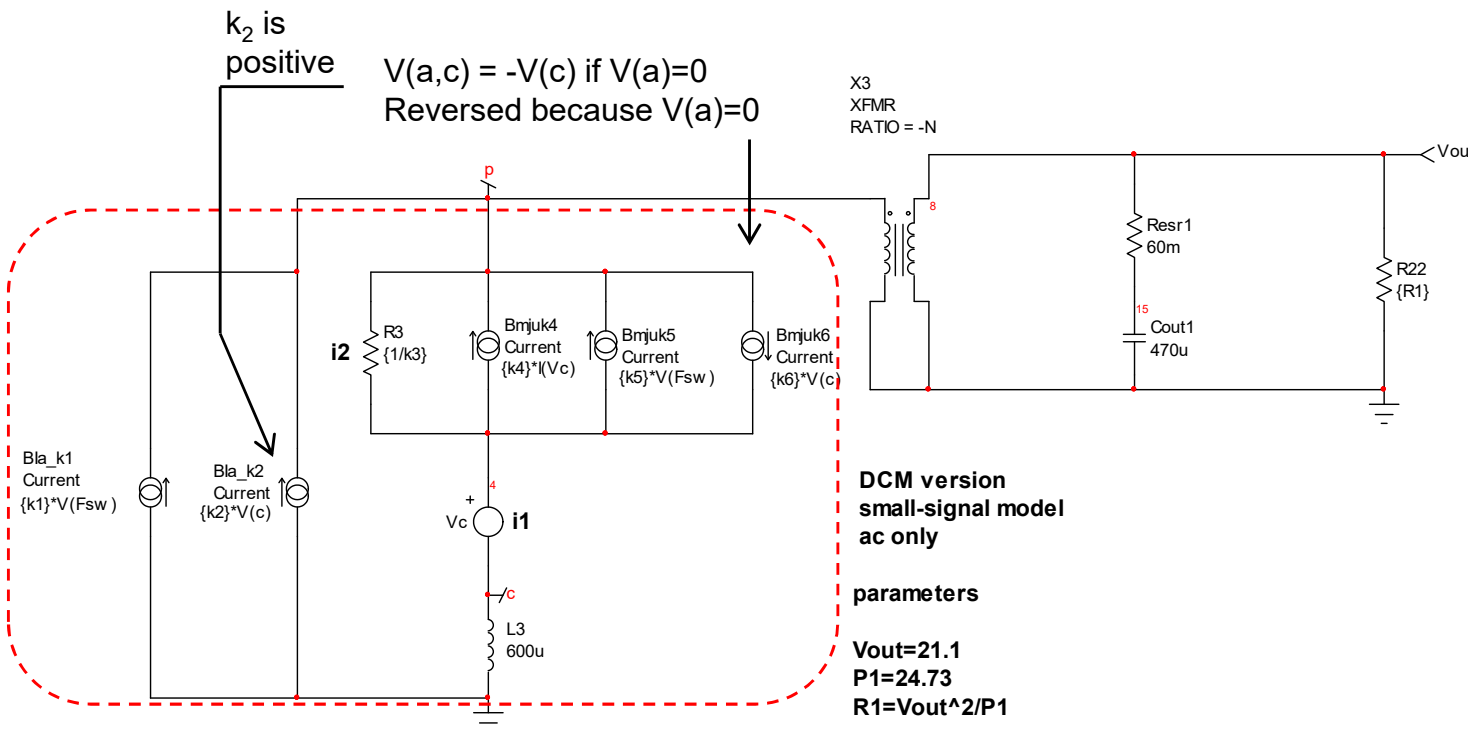


Linearized PWM switch



Go for Mesh and Node Analysis

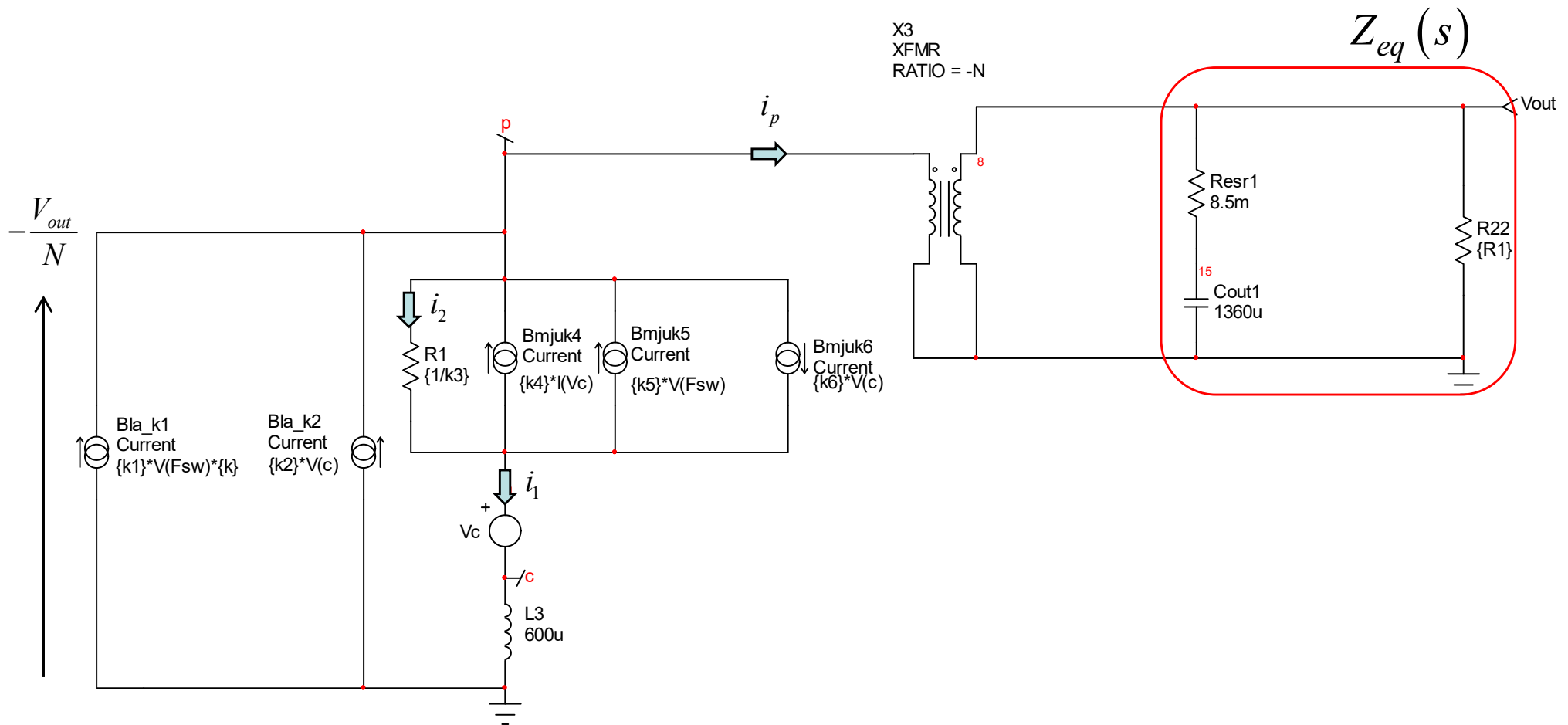- Express the current and voltage in the primary side



Mesh and Node Analysis

□ KCL: the sum of currents arriving at a node equals the sum of currents leaving the node:

$$k_4 i_1 + k_5 V(F_{sw}) + i_1 = i_2 + s k_6 L_p i_1 \quad \boxed{i_2} = i_1 + i_1 k_4 + k_5 V(F_{sw}) - s L_p i_1 k_6$$

$$i_1 = \frac{-\frac{V_{out}}{N_1} - R_1 i_2}{s L_p}$$

$$i_1(s) = -\frac{V_{out}(s) + N_1 R_1 i_1(s) + N_1 R_1 i_1(s) k_4 + N_1 R_1 k_5 V(F_{sw}) - s L_p R_1 i_1(s) k_6 N_1}{L_p N_1 s}$$

□ solve for i_1 :

$$i_1(s) = -\frac{V_{out}(s) + N_1 R_1 k_5 V(F_{sw})}{N_1 R_1 (1 + k_4) + s L_p N_1 (1 - k_6 R_1)}$$

Mesh and Node Analysis

□ Apply similar technique to get the primary current:

$$i_p(s) = k_1 V(F_{sw}) + k_2 i_1(s) s L_p - i_1(s)$$

$$i_p(s) = \frac{V_{out}(s) - L_p V_{out}(s) k_2 s + N_1 R_1 V(F_{sw})(k_1 + k_5 + k_1 k_4) + s L_p N_1 V(F_{sw})(k_1 - R_1 k_1 k_6 - R_1 k_2 k_5)}{N_1 (R_1 + R_1 k_4 + s L_p - s L_p R_1 k_6)}$$

$$i_{out} = -\frac{i_p}{N_1} \quad V_{out} = i_{out} Z_{eq}$$


$$V_{out}(s) = \frac{V_{out}(s) - L_p V_{out}(s) k_2 s + N_1 R_1 V(F_{sw})(k_1 + k_5 + k_1 k_4) + s L_p N_1 V(F_{sw})(k_1 - R_1 k_1 k_6 - R_1 k_2 k_5)}{N_1^2 (R_1 + R_1 k_4 + s L_p - s L_p R_1 k_6)} Z_{eq}(s)$$

$$\frac{V_{out}(s)}{V(F_{sw})} = \frac{(N_1 R_1 (k_1 + k_5 + k_1 k_4) + s L_p N_1 (k_1 - R_1 k_1 k_6 - R_1 k_2 k_5))}{N_1^2 (s R_1 L_p k_6 - s L_p - R_1 k_4 - R_1) - Z_{eq}(s) + s L_p k_2 Z_{eq}(s)} Z_{eq}(s)$$



Fast Analytical Techniques

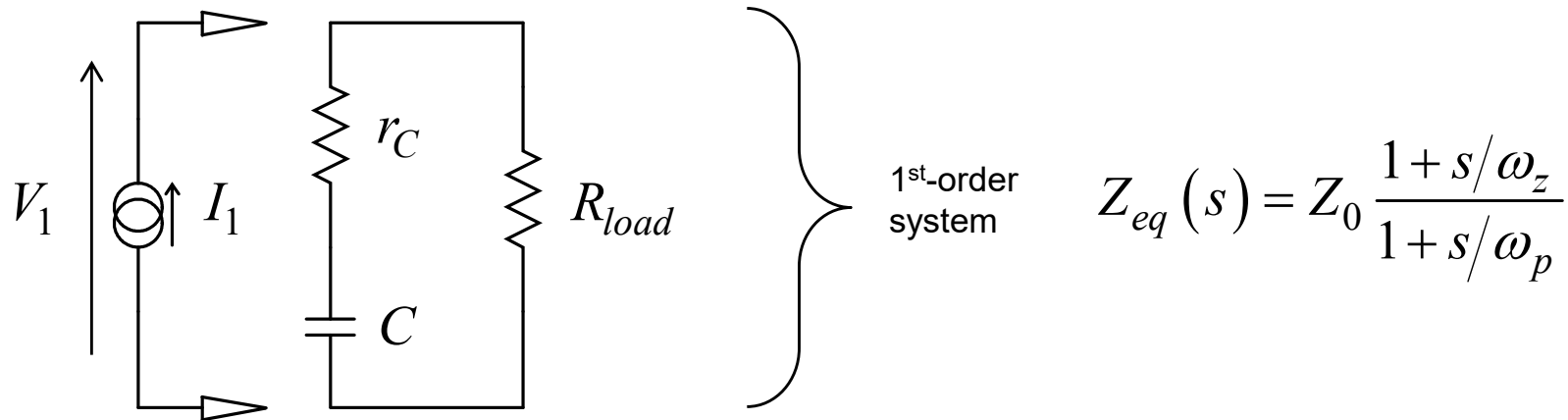□ Fast analytical techniques unveil Z_{eq} in a second!




1. In dc, open the capacitor: $Z_0 = R_{load}$
2. What prevents the excitation I_1 from reaching the output V_1 ?
 - A short-circuit between r_C and C :

$$r_C + \frac{1}{sC} = \frac{sr_C C + 1}{sC} = 0 \quad \Rightarrow \quad \omega_z = \frac{1}{r_C C}$$

Fast Analytical Techniques

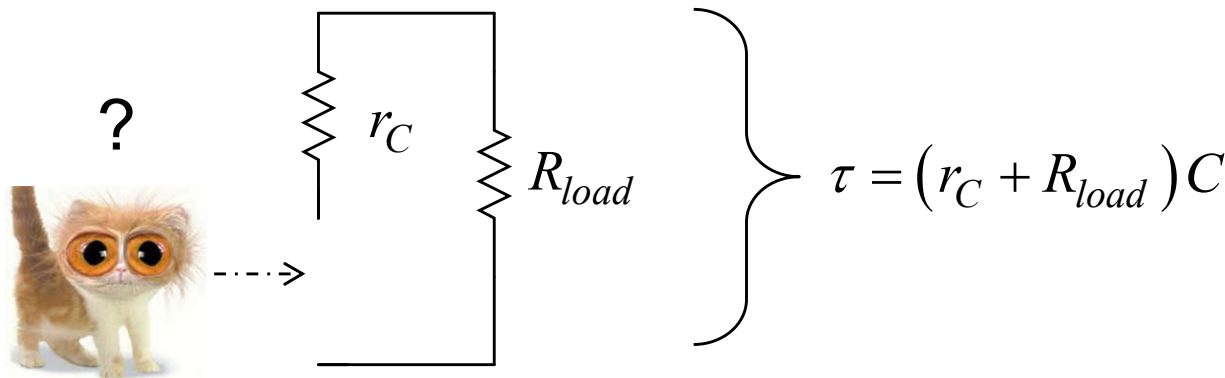- Get the time constant by putting the excitation to zero:
 - open the current source and look at the cap. driving R



- The equivalent impedance is therefore:

$$Z_{eq}(s) = R_{load} \frac{1 + sr_C C}{1 + sC(r_C + R_{load})}$$

You cannot beat equation-solving by inspection!

Almost There...

□ Develop the expression with $Z_{eq}(s)$, cry and re-arrange:

$$H(s) = H_0 \frac{N(s)}{D(s)} \quad H_0 = -G_{VCO} \frac{N_1 R_{load} R_1 (k_1 + k_5 + k_1 k_4)}{R_{load} + N_1^2 R_1 (1 + k_4)} = \frac{V_{out}}{2F_{sw}} G_{VCO}$$

$$N(s) = \left(1 + sL_p \left(\frac{k_1 - R_1 k_1 k_6 - R_1 k_2 k_5}{R_1 (k_1 + k_5 + k_1 k_4)} \right) \right) (1 + sr_C C) \quad D(s) = 1 + as + bs^2$$

$$a = C_{out} \left(R_{load} + r_C - \frac{R_{load}^2}{R_{load} + N_1^2 R_1 (1 + k_4)} \right) + L_p \left(\frac{N_1^2 - R_{load} k_2 - N_1^2 R_1 k_6}{R_{load} + N_1^2 R_1 (1 + k_4)} \right)$$

$$b = L_p N_1^2 C_{out} \left(\frac{R_{load} + r_C - \frac{R_{load}}{N_1^2} k_2 r_C - R_1 R_{load} k_6 - R_1 k_6 r_C}{R_{load} + N_1^2 R_1 (1 + k_4)} \right)$$

A Few More Minutes, Keep the Faith...

- Put the denominator under a second-order form and identify

$$D(s) = 1 + as + bs^2 = 1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2$$

$$f_0 = \frac{1}{2\pi\sqrt{L_p C_{out}}} \sqrt{\frac{\frac{R_{load}}{N_1^2} + R_1(1+k_4)}{R_{load} + r_C - \frac{R_{load}}{N_1^2}k_2r_C - R_1k_6(R_{load} + r_C)}}} = 1.75 \text{ kHz}$$

$$Q = \frac{1}{\omega_0 \left(C_{out} \left(R_{load} + r_C - \frac{R_{load}^2}{R_{load} + N_1^2 R_1 (1+k_4)} \right) + L_p \left(\frac{N_1^2 - R_{load}k_2 - N_1^2 R_1 k_6}{R_{load} + N_1^2 R_1 (1+k_4)} \right) \right)} = 0.021$$



A Few More Minutes, Keep the Faith...

□ Extract the zeros:

$$f_{z_1} = \frac{1}{2\pi L_p \left(\frac{k_1 - R_1(k_1 k_6 - k_2 k_5)}{R_1(k_1 + k_5 + k_1 k_4)} \right)} = \underset{\substack{\uparrow \\ \text{RHPZ}}}{487 \text{ kHz}} \quad f_{z_2} = \frac{1}{2\pi r_C C_{out}} = 5.6 \text{ kHz}$$

□ Extract the low-frequency poles:

$$f_{p_1} = \frac{1}{2\pi C_{out} \left(R_{load} + r_C - \frac{R_{load}^2}{R_{load} + N_1^2 R_1 (1 + k_4)} \right)} = \frac{1}{2\pi C_{out} \left(R_{load} + r_C - \frac{R_{load}}{2} \right)} \approx \frac{1}{\pi R_{load} C_{out}}$$

$$f_{p_1} = \frac{1}{\pi C_{out} (R_{load} + r_C)} = 37.73 \text{ Hz}$$


$$\downarrow \\ r_C \ll R_{load}$$

$$f_{p_2} = \frac{1}{2\pi L_p \left(\frac{N_1^2 - R_{load} k_2 - N_1^2 R_1 k_6}{R_{load} + N_1^2 R_1 (1 + k_4)} \right)} = 152 \text{ kHz}$$



Final Lap, Compare the ac Plots

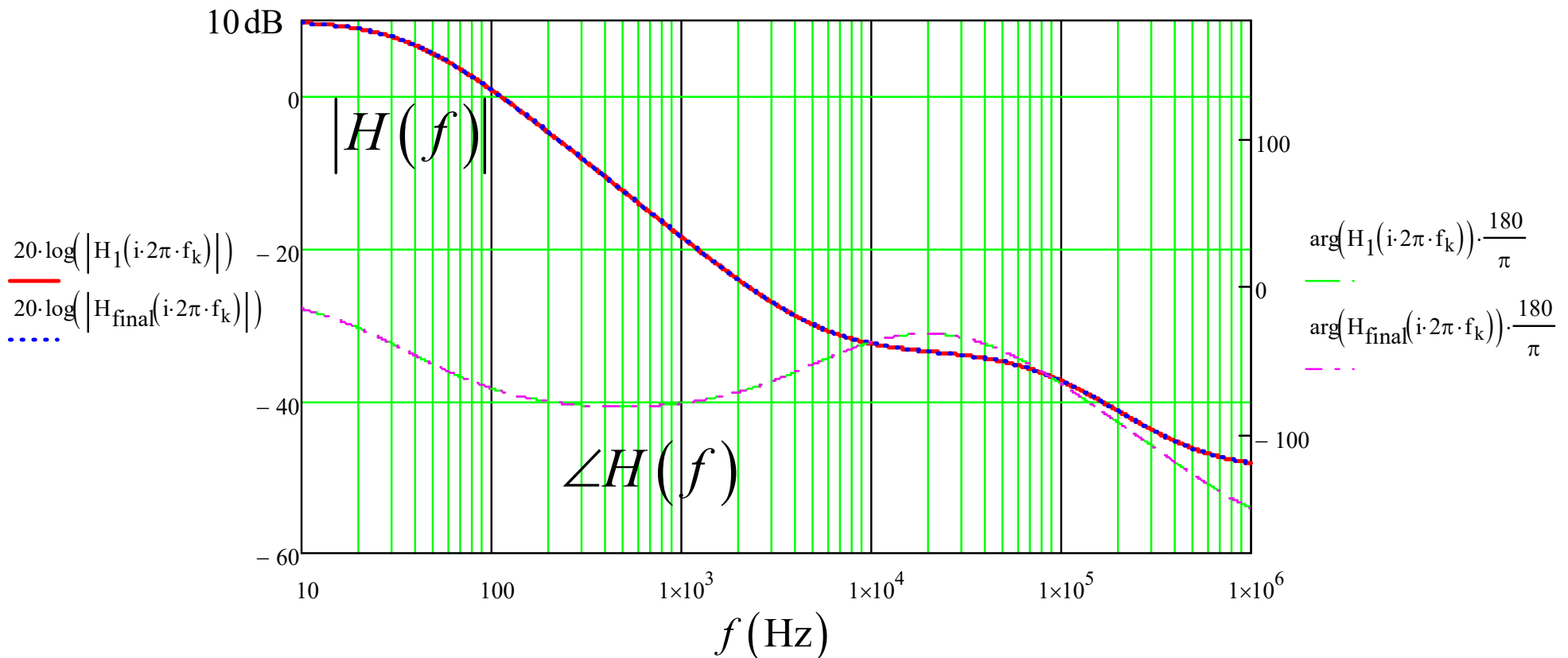- ❑ Compare the original equation and its re-arranged form:




- ❑ It confirms the derivation is correct!


The Final Test: SPICE vs Mathcad

□ If all is well, the curves must perfectly superimpose

dB °

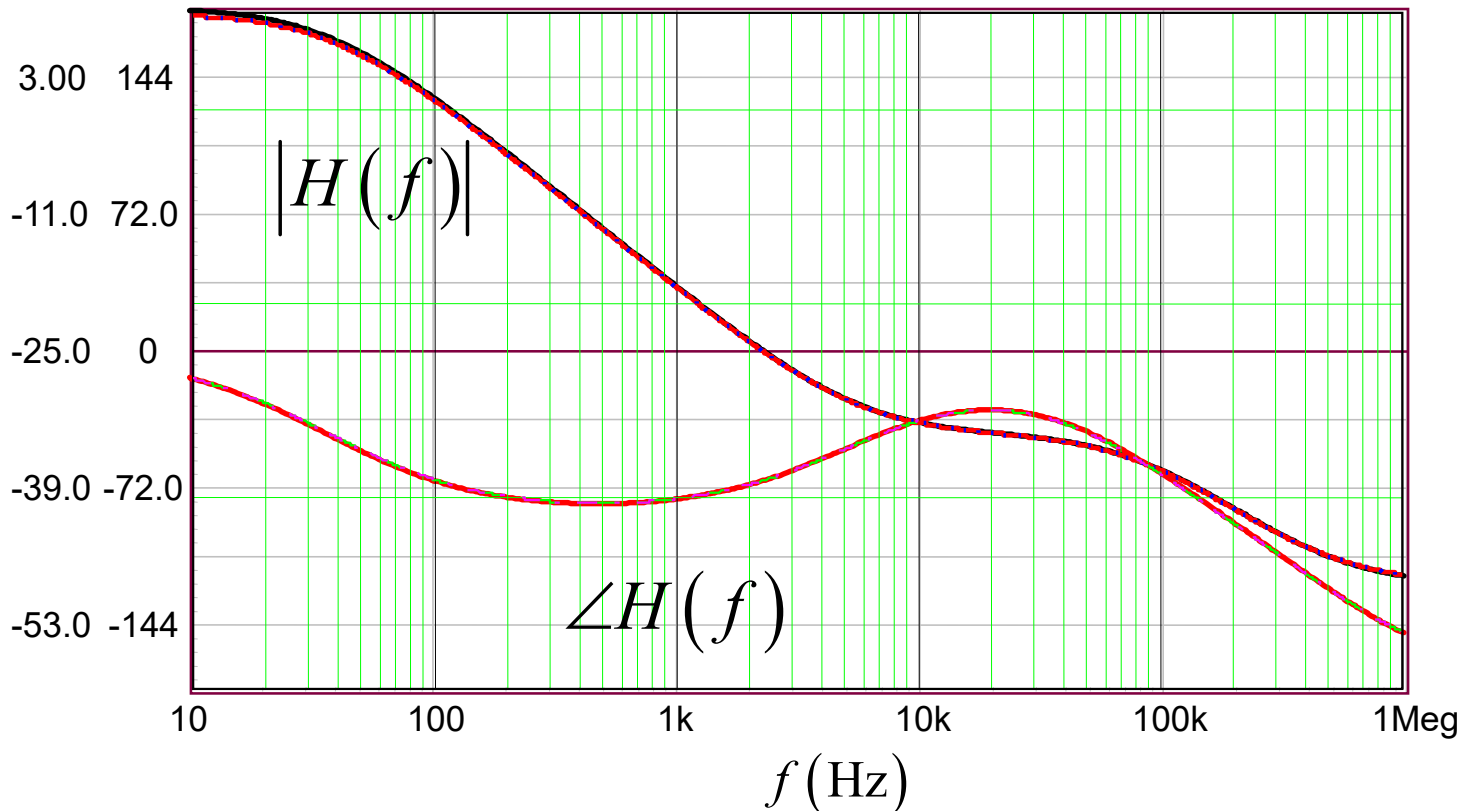


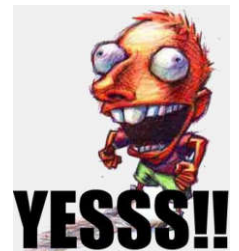➤ If not, there is a hidden mistake: chase it (good luck)



The Final Transfer Function

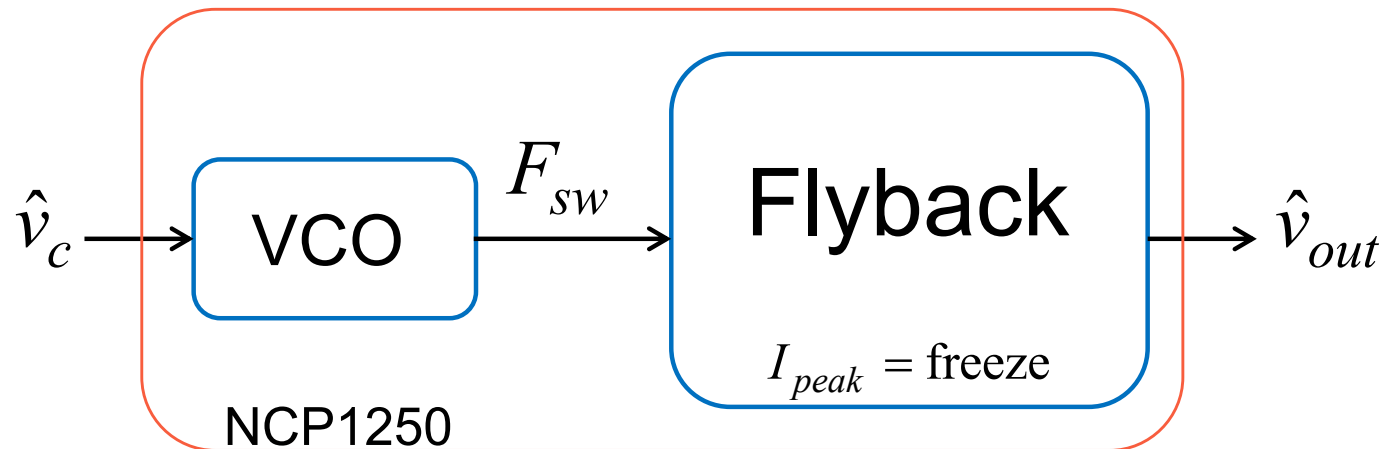
- ❑ The current-mode flyback converter is operated in DCM
- ❑ The peak current is fixed and F_{sw} is controlled
- ❑ What is the simplified transfer function?




$$H(s) = \frac{\hat{v}_{out}}{\hat{v}_c} = H_0 \frac{1 + s/\omega_z}{1 + s/\omega_p} = \frac{V_{out}}{2F_{sw}} G_{VCO} \frac{1 + sr_C C_{out}}{1 + s \frac{R_{load}}{2} C_{out}}$$

A Faster Way?

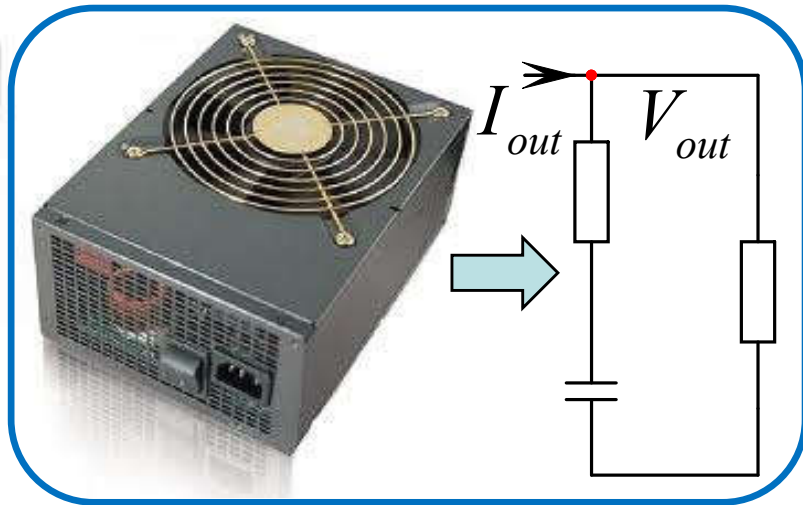- ❑ If you are in a hurry and looking for a faster way:
 - Formulate the output current expression
 - Differentiate the expression to its variables
 - Draw an equivalent schematic and solve the equations



A DCM/CCM
current-mode converter

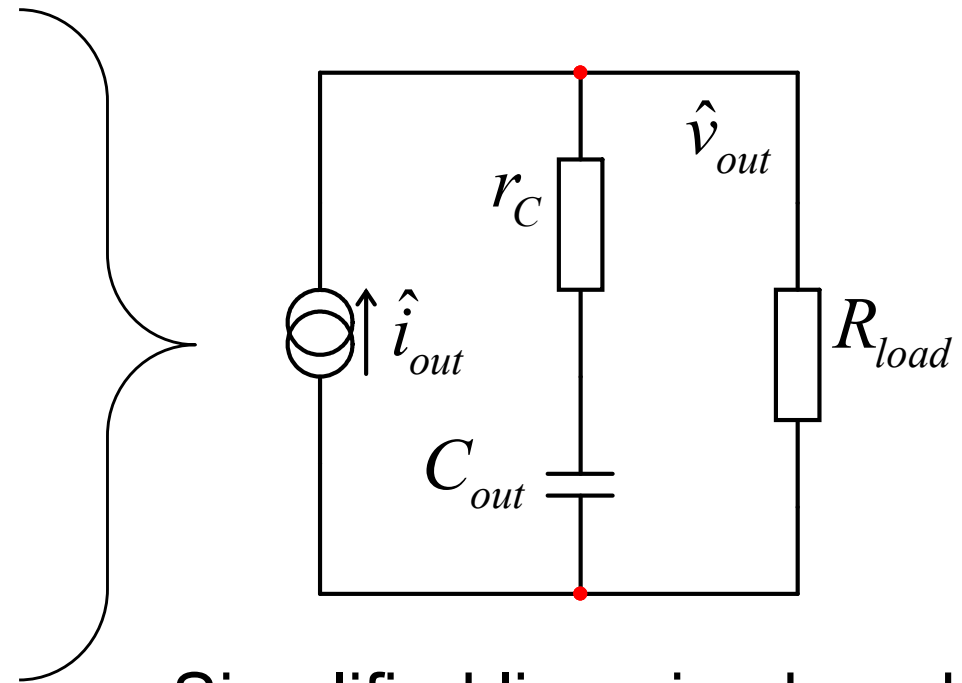

Simplified linearized model


The Founding Equation is Well Known

□ A flyback converter running in DCM obeys:

$$P_{out} = I_{out} V_{out} = \frac{1}{2} L_p I_{peak}^2 F_{sw} \rightarrow I_{peak} = \frac{V_c}{R_i} \rightarrow I_{out} V_{out} = \frac{1}{2} L_p \left(\frac{V_c}{R_i} \right)^2 F_{sw}$$

$$I_{out} = \frac{L_p \left(\frac{V_c}{R_i} \right)^2 F_{sw}}{2V_{out}}$$

Two variables

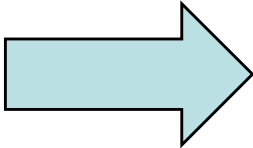

$$\hat{i}_{out} = \left(\frac{\partial I_{out} (F_{sw}, V_{out})}{\partial V_{out}} \right)_{F_{sw}} \hat{v}_{out} + \left(\frac{\partial I_{out} (F_{sw}, V_{out})}{\partial F_{sw}} \right)_{V_{out}} \hat{F}_{sw}$$

First Expression Comes Easily


- Rework the individual coefficients to a simpler form

$$\left(\frac{\partial I_{out}(F_{sw}, V_{out})}{\partial V_{out}} \right)_{F_{sw}} \hat{v}_{out} = - \frac{F_{sw} L_p}{2 V_{out}^2} \left(\frac{V_c}{R_i} \right)^2 \hat{v}_{out} \Rightarrow g_m \cdot \hat{v}_{out} = \frac{1}{R} \hat{v}_{out}$$

\downarrow
 $[\Omega^{-1}]$

$$-\frac{F_{sw} L_p}{2 V_{out}^2} \left(\frac{V_c}{R_i} \right)^2 = -\frac{\frac{1}{2} I_{peak}^2 F_{sw} L_p}{V_{out}^2}$$
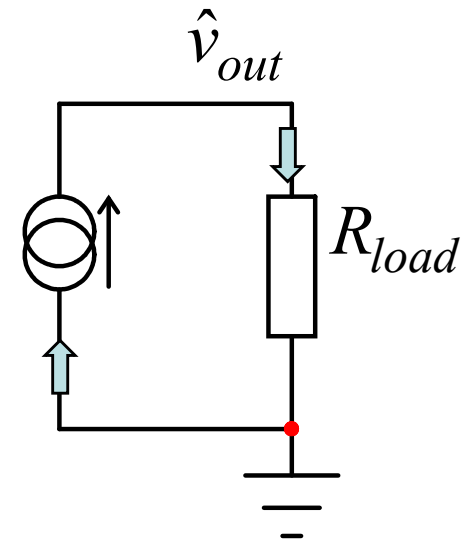
$$-\frac{P_{out}}{V_{out}^2} = -\frac{V_{out} I_{out}}{V_{out} V_{out}} = -\frac{1}{R_{load}}$$




Second Expression is Also Simple

- Identify the power in the equation, simplify...

$$\left(\frac{\partial I_{out}(F_{sw}, V_{out})}{\partial F_{sw}} \right)_{V_{out}} \hat{F}_{sw} = \frac{L_p}{2V_{out}} \left(\frac{V_c}{R_i} \right)^2 \hat{F}_{sw}$$
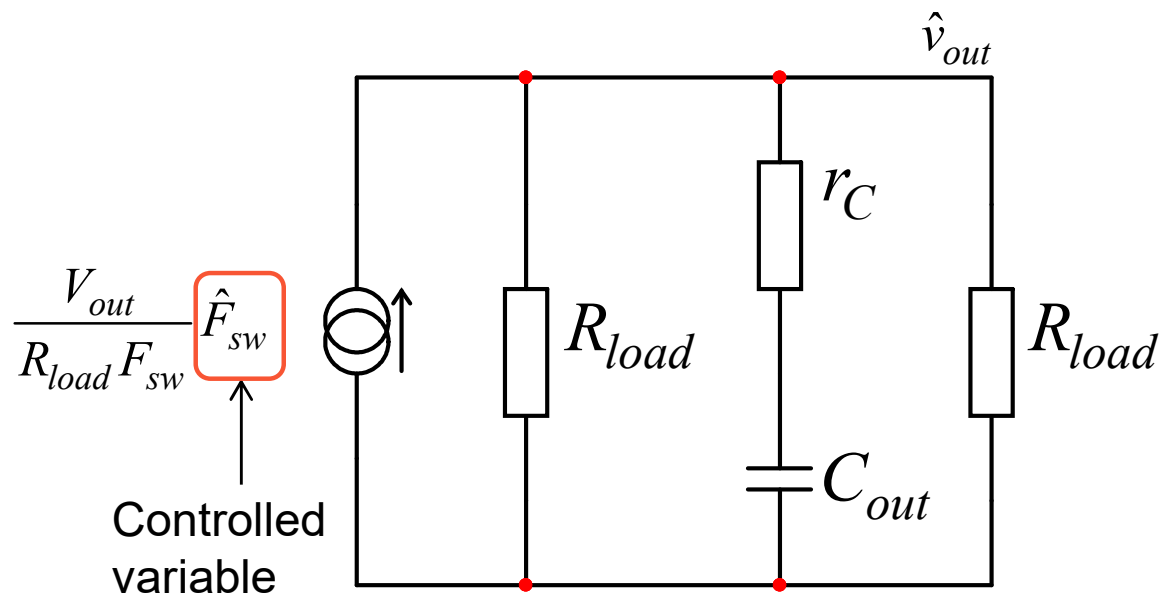
$$\frac{L_p}{2V_{out}} \left(\frac{V_c}{R_i} \right)^2 \hat{F}_{sw} = \frac{P_{out}}{F_{sw} V_{out}} \hat{F}_{sw} = \frac{V_{out}}{R_{load}} \frac{V_{out}}{F_{sw} V_{out}} \hat{F}_{sw} = \frac{V_{out}}{R_{load} F_{sw}} \hat{F}_{sw}$$



Can't beat such a simple schematic!

The Transfer Function is Immediate

- The transfer function is now straightforward

$$\hat{v}_{out}(s) = \hat{F}_{sw}(s) \frac{V_{out}}{R_{load} F_{sw}} \boxed{R_{load} \parallel Z_{eq}(s)} \longrightarrow \approx \frac{R_{load}}{2} \frac{1 + sr_C C}{1 + sC \left(\frac{R_{load}}{2} \right)}$$

$$\hat{v}_{out}(s) = \hat{v}_c(s) k_F G_{VCO} \frac{V_{out}}{2F_{sw}} \frac{1 + sr_C C}{1 + sC \left(\frac{R_{load}}{2} \right)}$$

- Put it under the normalized form

$$H(s) = \frac{\hat{v}_{out}}{\hat{v}_c} = H_0 \frac{1 + s/\omega_z}{1 + s/\omega_p} = \frac{V_{out}}{2F_{sw}} k_F G_{VCO} \frac{1 + sr_C C_{out}}{1 + s \frac{R_{load}}{2} C_{out}}$$



- No RHPZ and no high-frequency pole prediction
- Good for low-frequency analysis only, but good enough for us!



Simulation Shows the Differences

- ❑ SPICE only manipulates linear equations

Large-signal equation

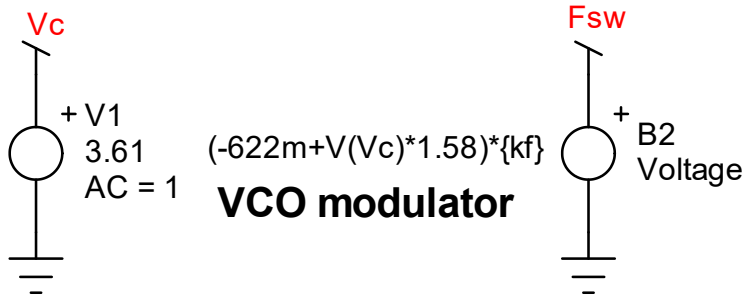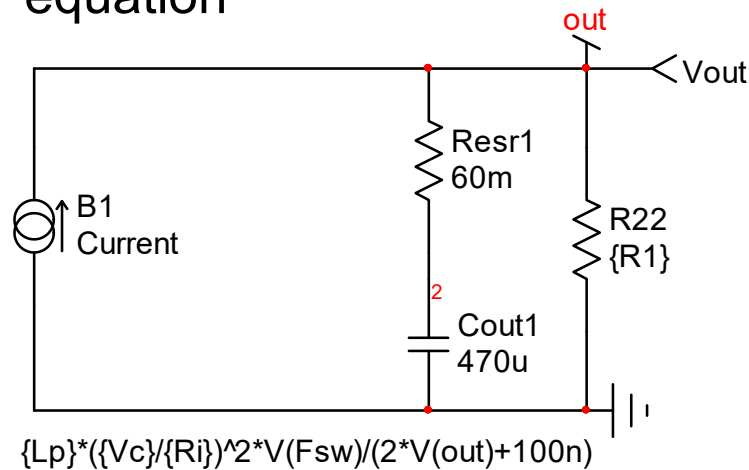


parameters

Vc=1
Lp=600u
Ri=0.8
Lp=600u
kf=10k

Vout=21.1
P1=24.73
R1=Vout^2/P1
Fsw=50.8k


Small-signal equation

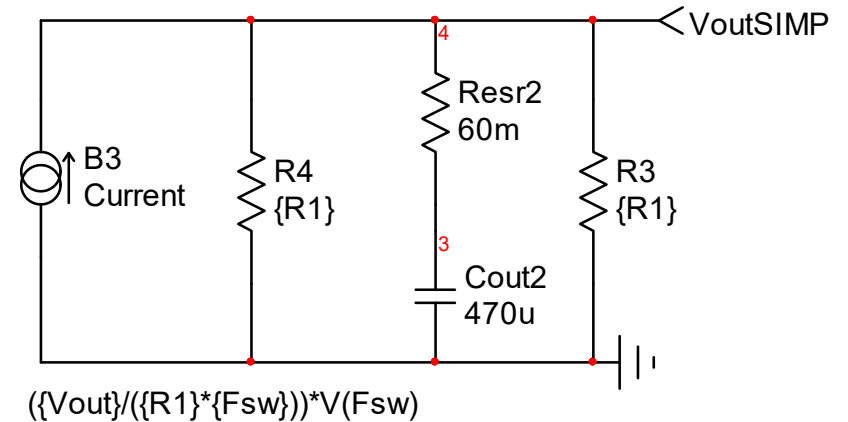

$$20 \log_{10} |H_0| = 20 \log_{10} \left(\frac{V_{out}}{2F_{sw}} k_F G_{VCO} \right) = 20 \log_{10} \left(\frac{21.1}{2 \times 50.8k} 10k \cdot 1.58 \right) = 10.3 \text{ dB}$$


Simulation Shows the Differences

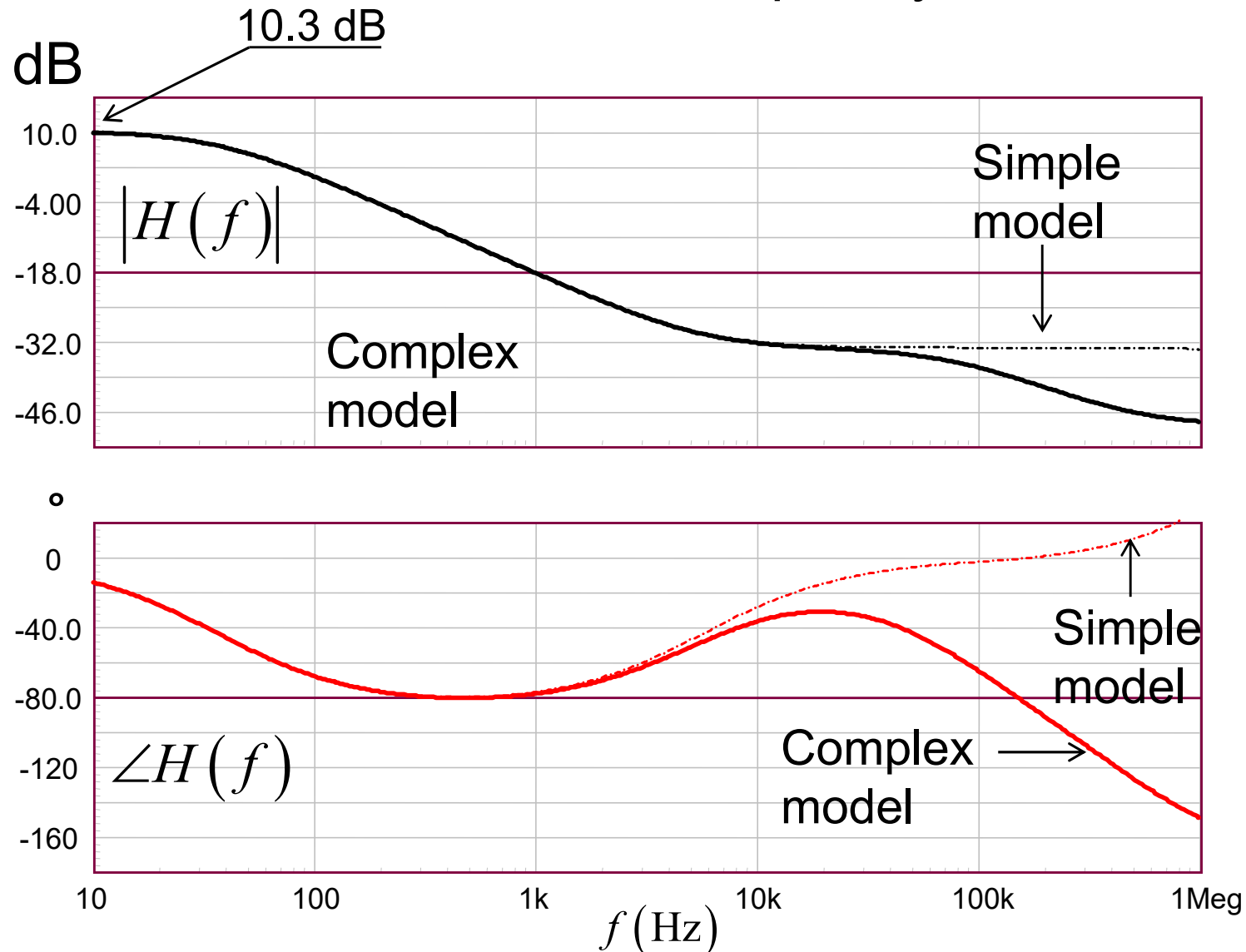- Ac results are identical at low frequency



Test Fixture

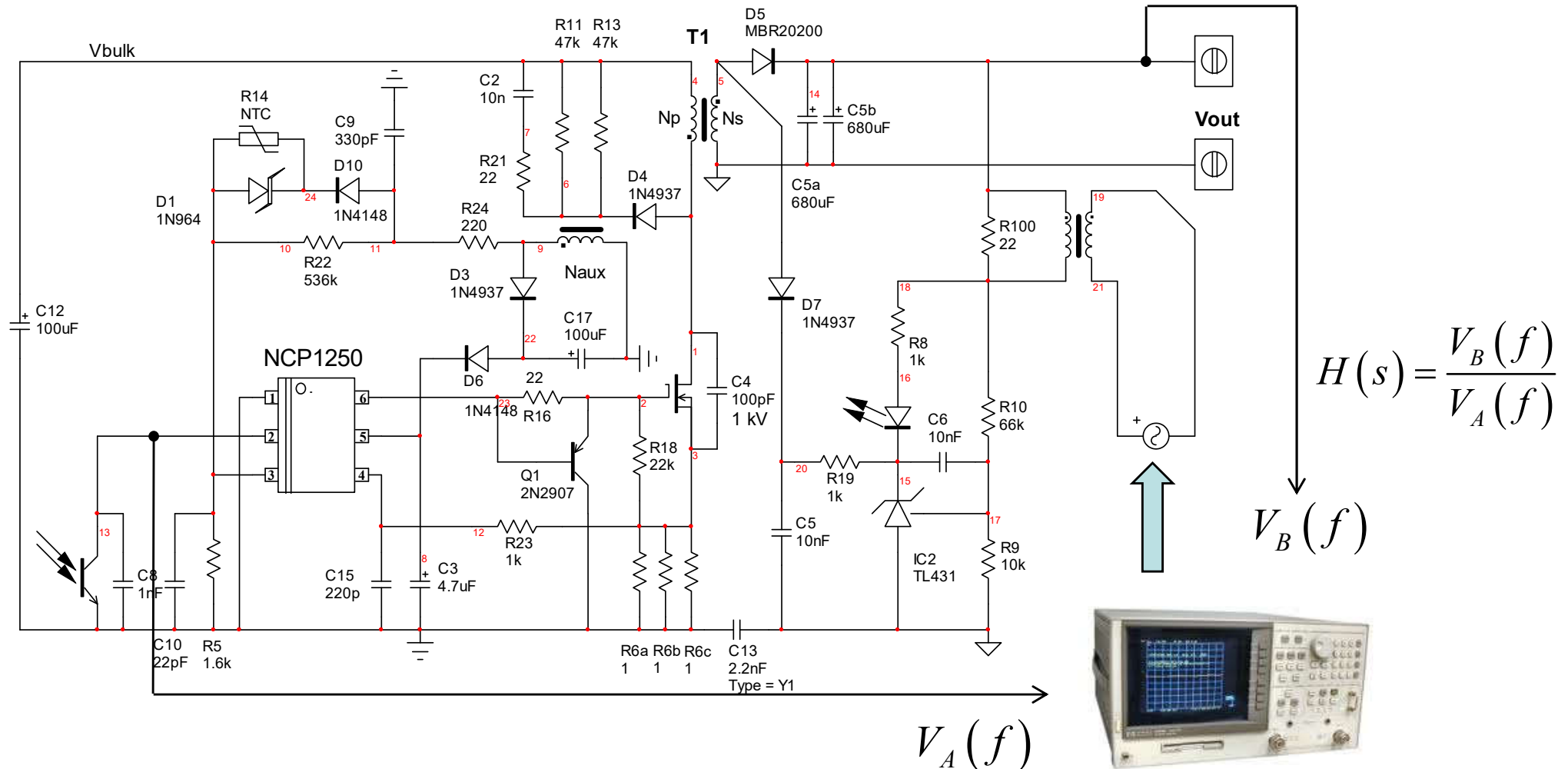- ❑ Plant frequency response with a NCP1250
- ❑ Load is reduced to force DCM where I_{peak} is frozen




Connections

- ❑ Connect probe grounds to a quiet point: opto emitter is ok
- ❑ Use an isolated current-limited dc-supply
- ❑ Short primary and secondary grounds




→
100 V dc

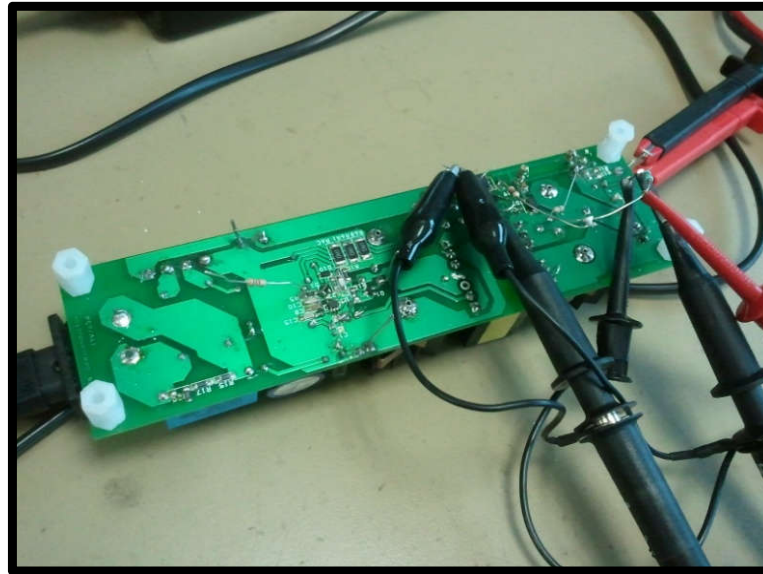

Power supply under test


$H(f)$

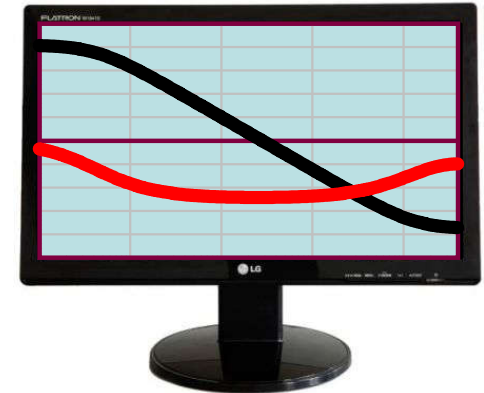

Injection
transformer



Run the SPICE Simulation

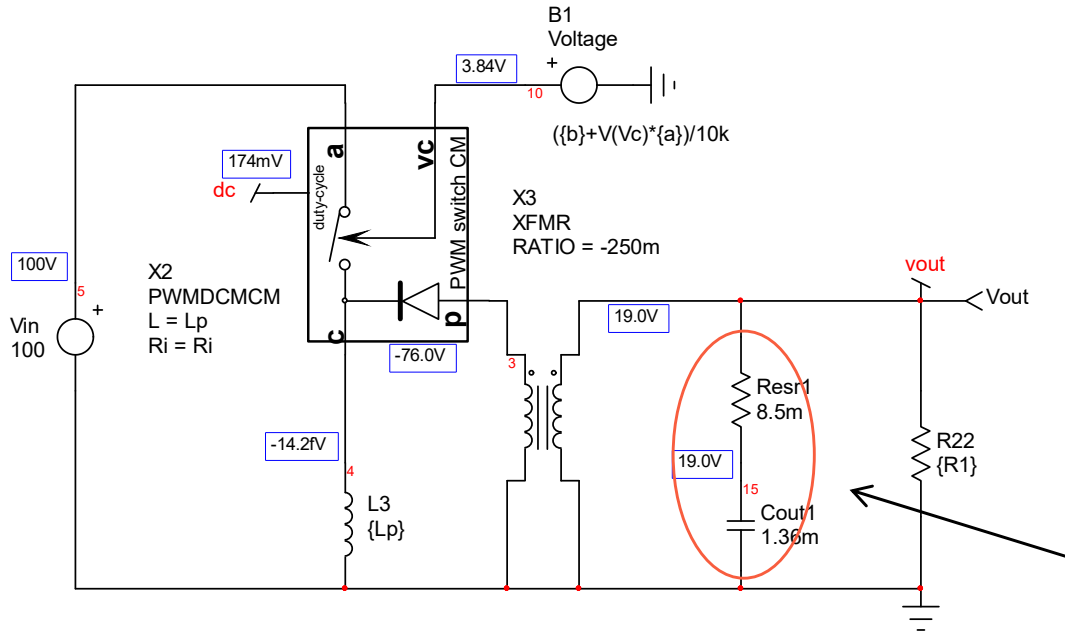

□ Check operating points:

$$F_{sw} = 38.6 \text{ kHz (bench) } 38.4 \text{ kHz (SPICE)}$$

$$V_{FB} = 0.71 \text{ V (bench) } 0.79 \text{ V (SPICE)}$$

Main contributor to errors is the capacitor ESR



parameters

Vout=19
P1=6.6
 $R1=Vout^2/P1$

Lp=600u
Ri=0.33

Fmax=65k
Fmin=26k
Vfold=1.5
Vmin=0.35
 $a2=(Fmax-Fmin)/(Vfold-Vmin)$
a=27.75k
b=Fmin-Vmin*a

VCO slope measured to 27.8 kHz/V

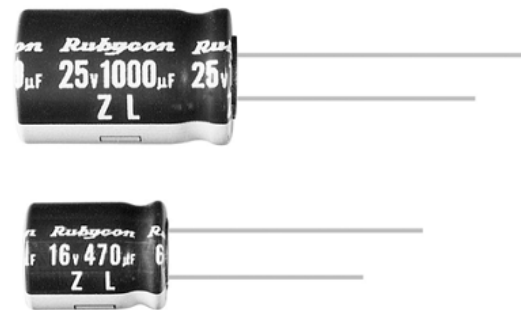
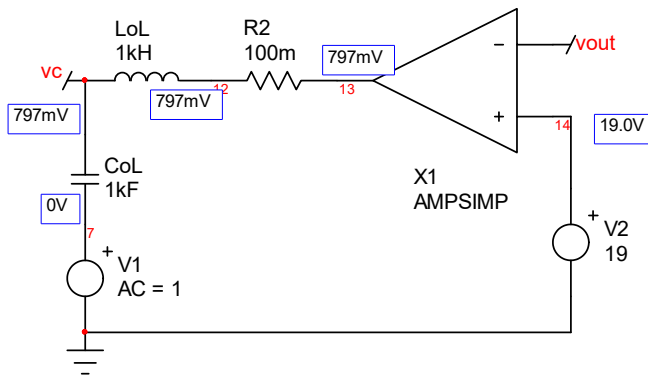


ZL series Rubycon



Approximate ESR Extraction

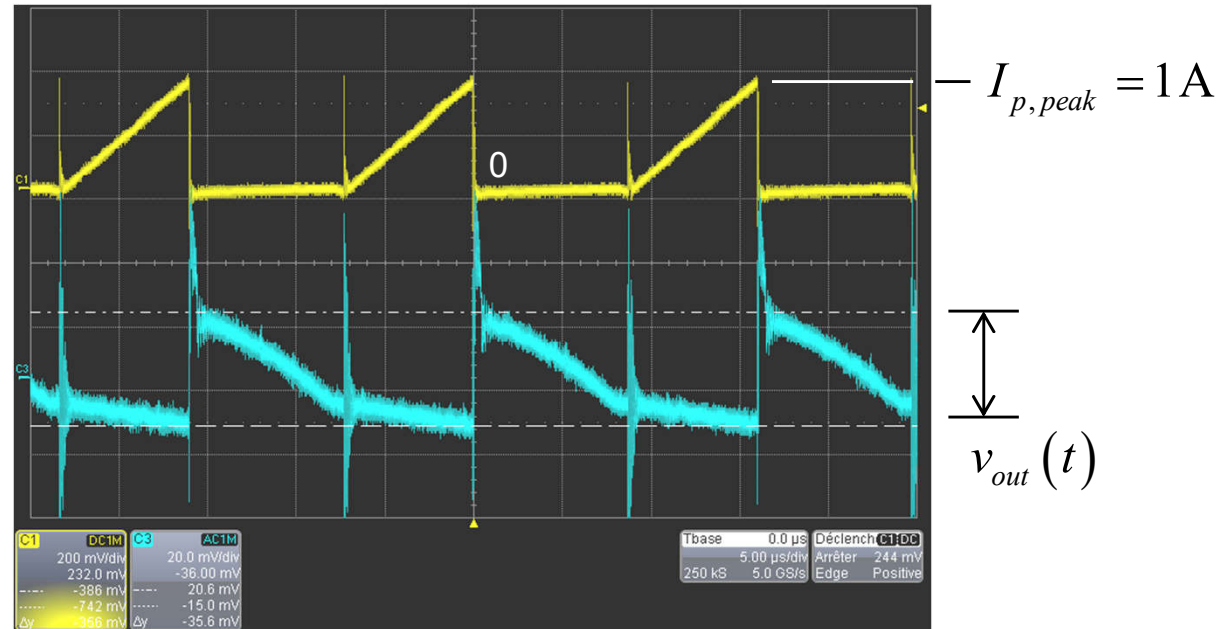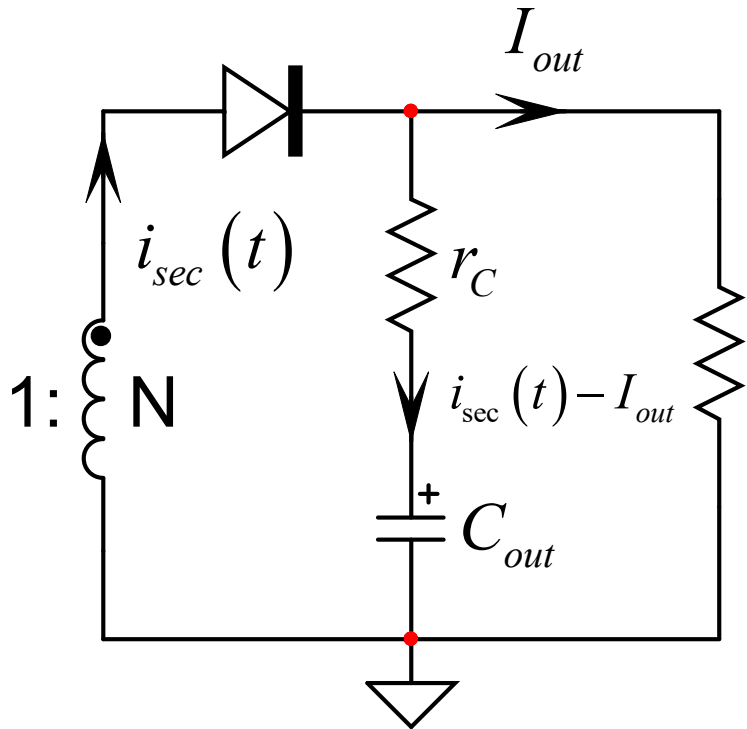- A triangular output shows that ESR is the main contributor




$$I_{sec,peak} = \frac{I_{p,peak}}{N} = \frac{1}{0.25} = 4 \text{ A}$$

$$V_{out,peak} \approx I_{sec,peak} r_C$$

$$r_C \approx \frac{V_{out,pp}}{I_{sec,peak}} = \frac{35m}{4} = 8.75 \text{ m}\Omega$$

DS says
11.5 mΩ

Plant Frequency Response

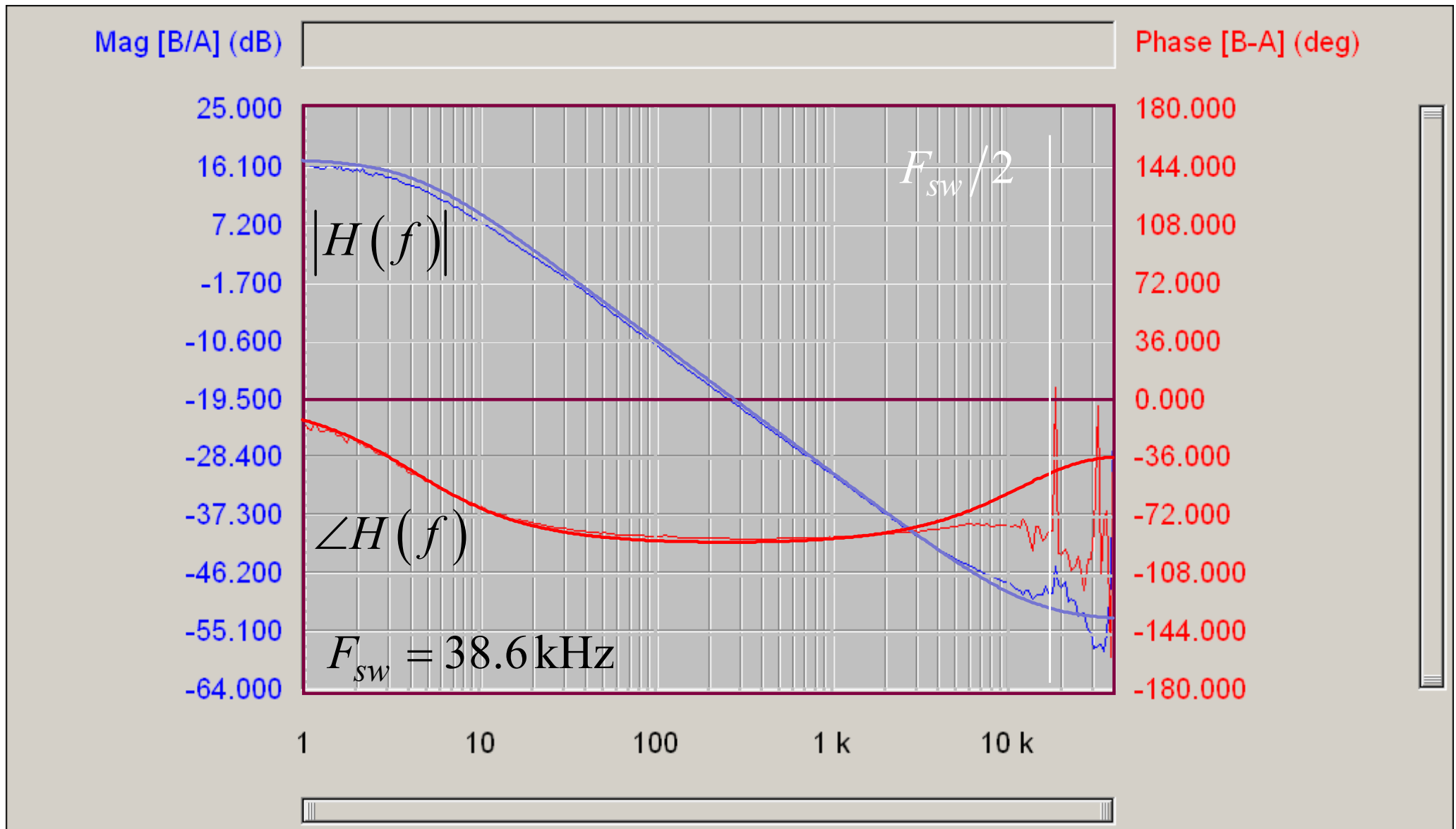




Agenda

- ❑ What is a QR Converter?
- ❑ Deriving Operating Conditions
- ❑ The Over Power Problem
- ❑ Three Operating Modes
- ❑ Small-Signal Analysis – QR
- ❑ Small-Signal Analysis – VCO
- ❑ **Compensating with TL431**
- ❑ Control Loop Design Example
- ❑ Conclusion



How is regulation performed?

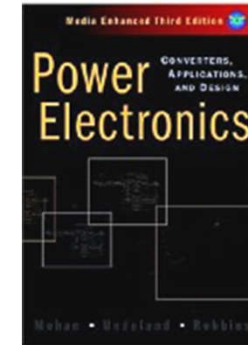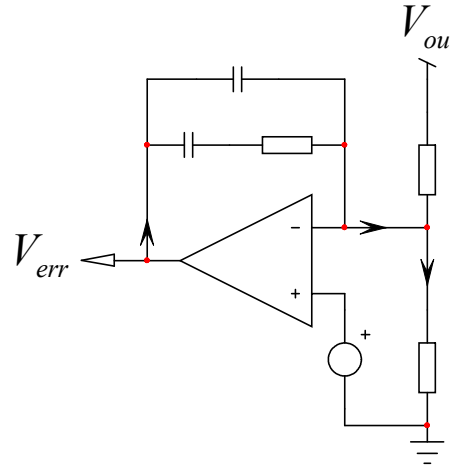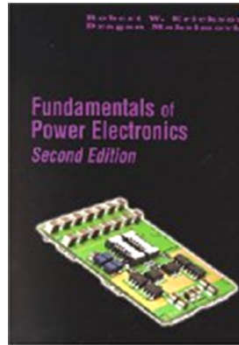- ❑ Text books only describe op amps in compensators...



- ❑ The market reality is different: the TL431 rules!



I'm the law!



TL431






optocoupler

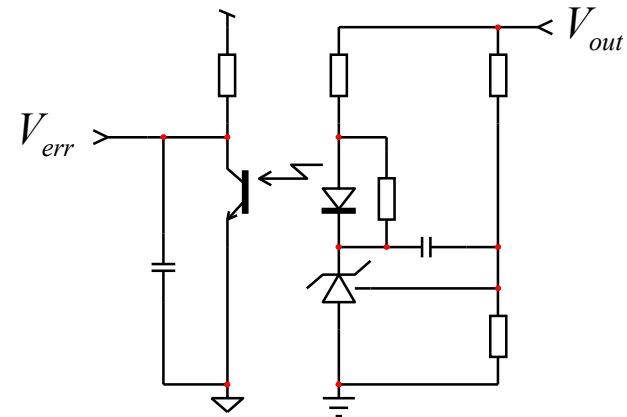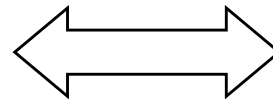

The TL431 Programmable Zener

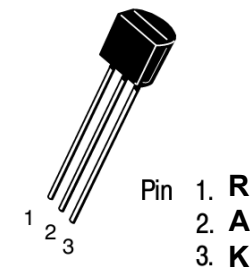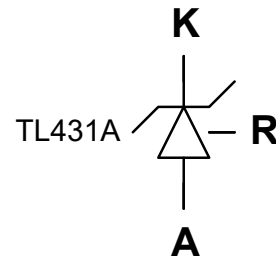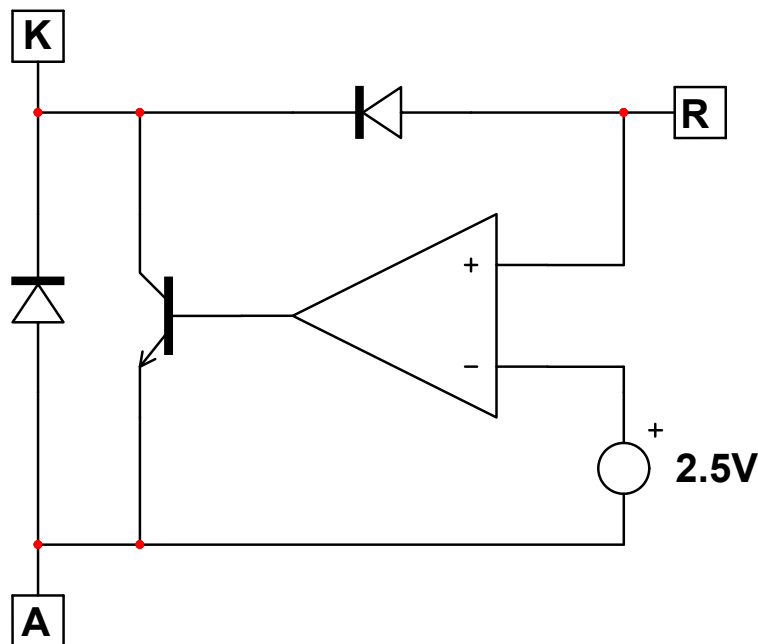
- ❑ The TL431 is the most popular choice in nowadays designs
- ❑ It associates an open-collector op amp and a reference voltage
- ❑ The internal circuitry is self-supplied from the cathode current
- ❑ When the R node exceeds 2.5 V, it sinks current from its cathode



- ❑ The TL431 is a shunt regulator

A Rabbit and a (French) Snail...

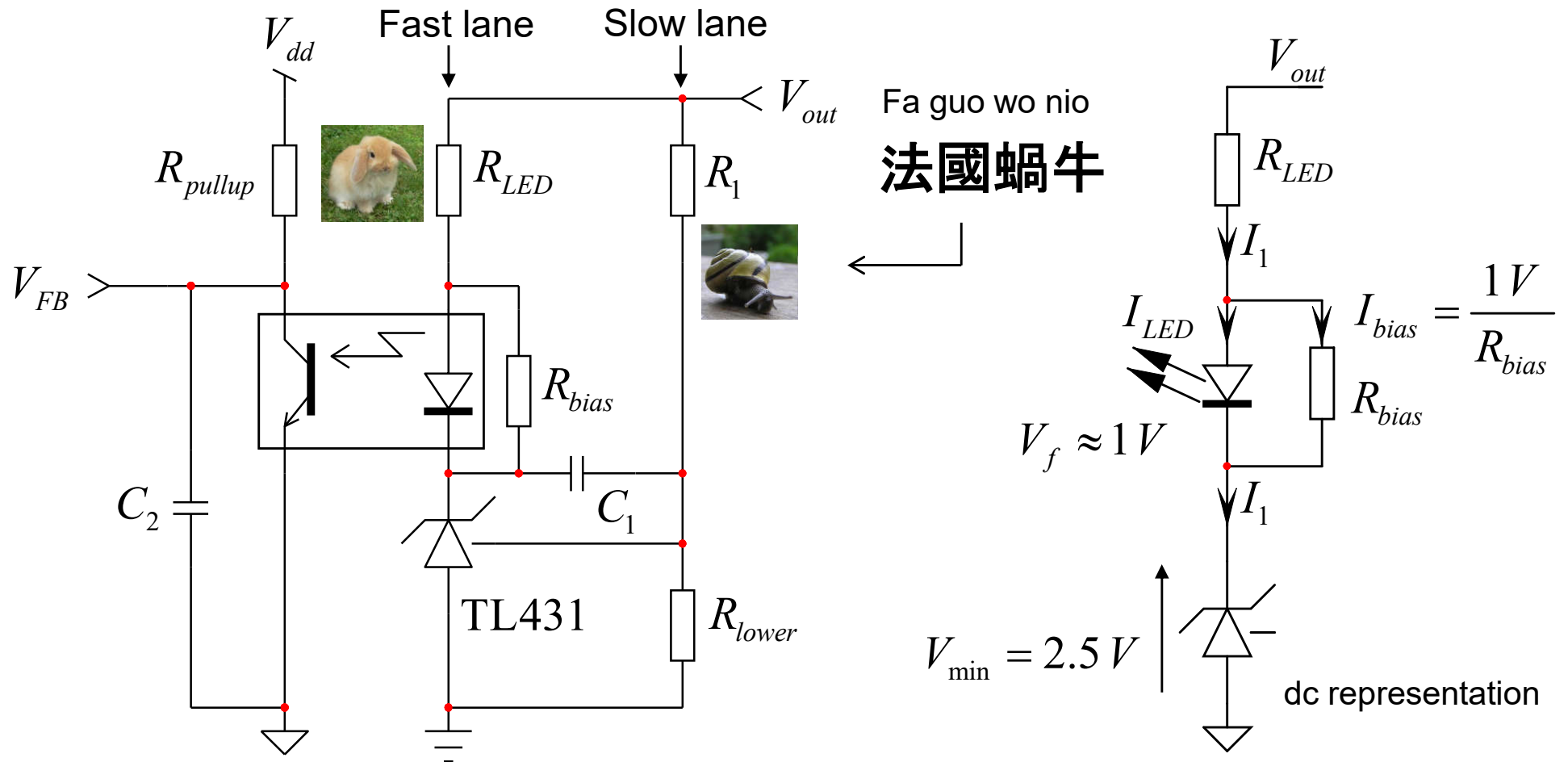- The TL431 lends itself very well to optocoupler control




- R_{LED} must leave enough headroom over the TL431: upper limit!

Understanding the Fast Lane Drawback

□ This LED resistor is a design limiting factor in low output voltages:

$$R_{LED,max} \leq \frac{V_{out} - V_f - V_{TL431,min}}{V_{dd} - V_{CE,sat} + I_{bias} CTR_{min} R_{pullup}} R_{pullup} CTR_{min}$$

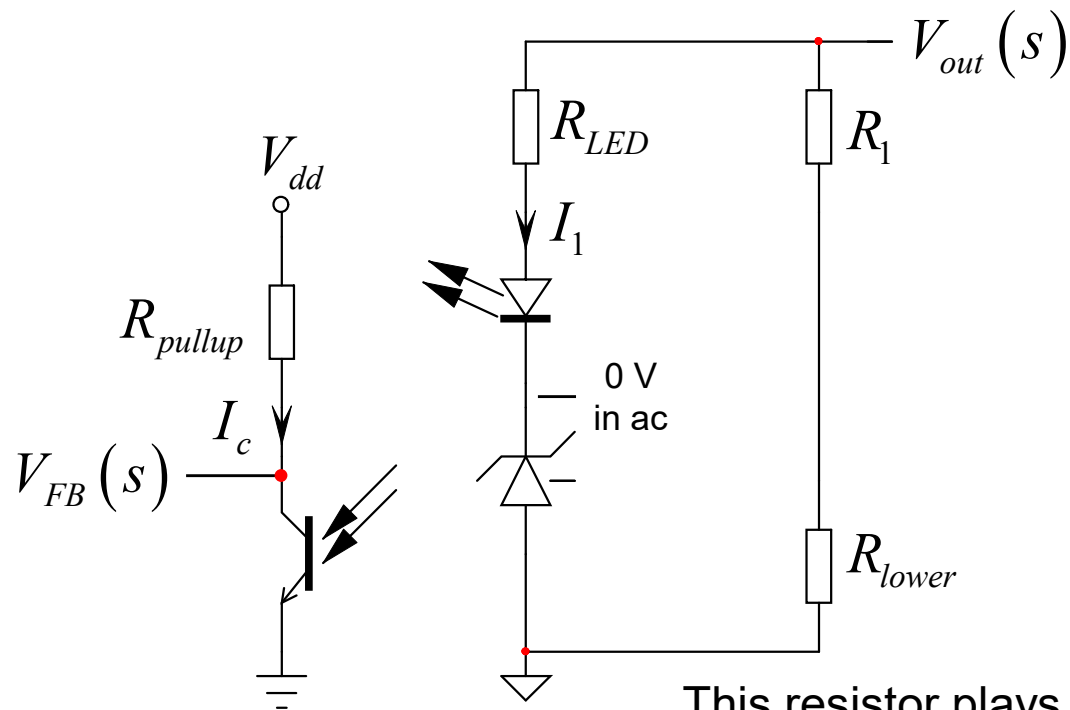□ When the capacitor C_1 is a short-circuit, R_{LED} fixes the fast lane gain



$$V_{FB}(s) = -CTR \cdot R_{pullup} \cdot I_1$$

$$I_1 = \frac{V_{out}(s)}{R_{LED}}$$

$$\frac{V_{FB}(s)}{V_{out}(s)} = -CTR \frac{R_{pullup}}{R_{LED}}$$

This resistor plays a role in dc too!

The Static Gain Limit

□ Let us assume the following design:

$$V_{out} = 5 \text{ V}$$

$$V_f = 1 \text{ V}$$

$$V_{TL431,min} = 2.5 \text{ V}$$

$$V_{dd} = 4.8 \text{ V}$$

$$V_{CE,sat} = 300 \text{ mV}$$

$$I_{bias} = 1 \text{ mA}$$

$$CTR_{min} = 0.3$$

$$R_{pullup} = 20 \text{ k}\Omega$$

$$R_{LED,max} \leq \frac{5 - 1 - 2.5}{4.8 - 0.3 + 1m \times 0.3 \times 20k} \times 20k \times 0.3$$



$$R_{LED,max} \leq 857 \Omega$$




$$G_0 > CTR \frac{R_{pullup}}{R_{LED}} > 0.3 \frac{20}{0.857} > 7 \text{ or } \approx 17 \text{ dB}$$

□ In designs where R_{LED} fixes the gain, G_0 cannot be below 17 dB

⇒ You cannot “amplify” by less than 17 dB



Forbidden Compensation Areas

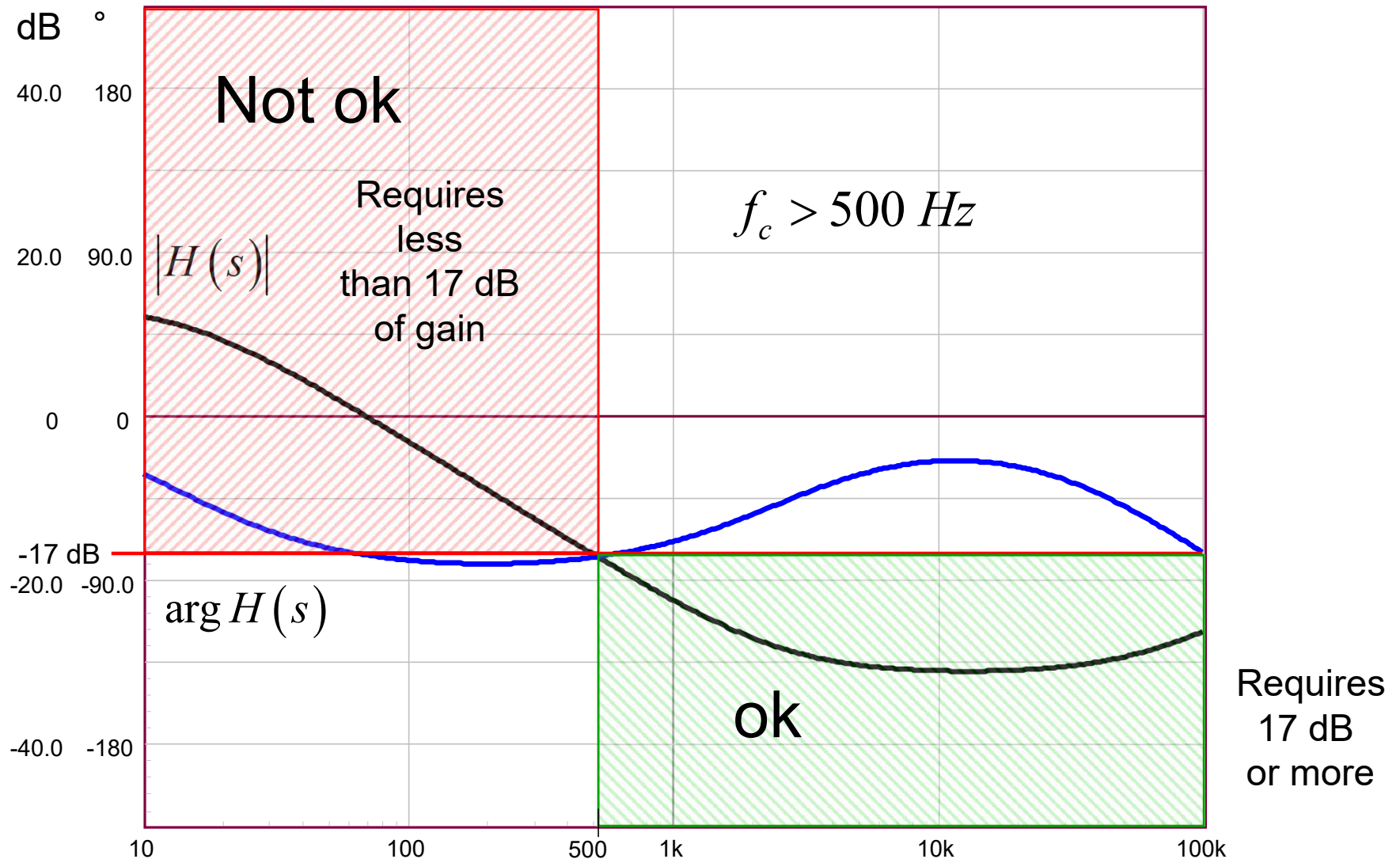- ❑ You must identify the areas where compensation is possible



Injecting Bias Current

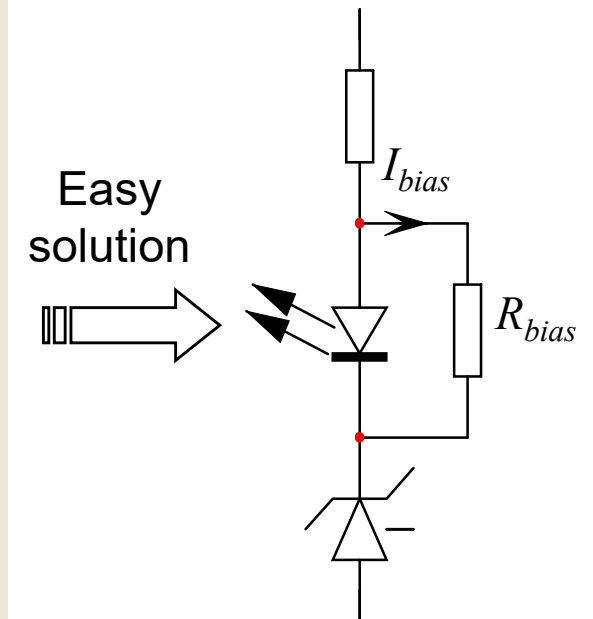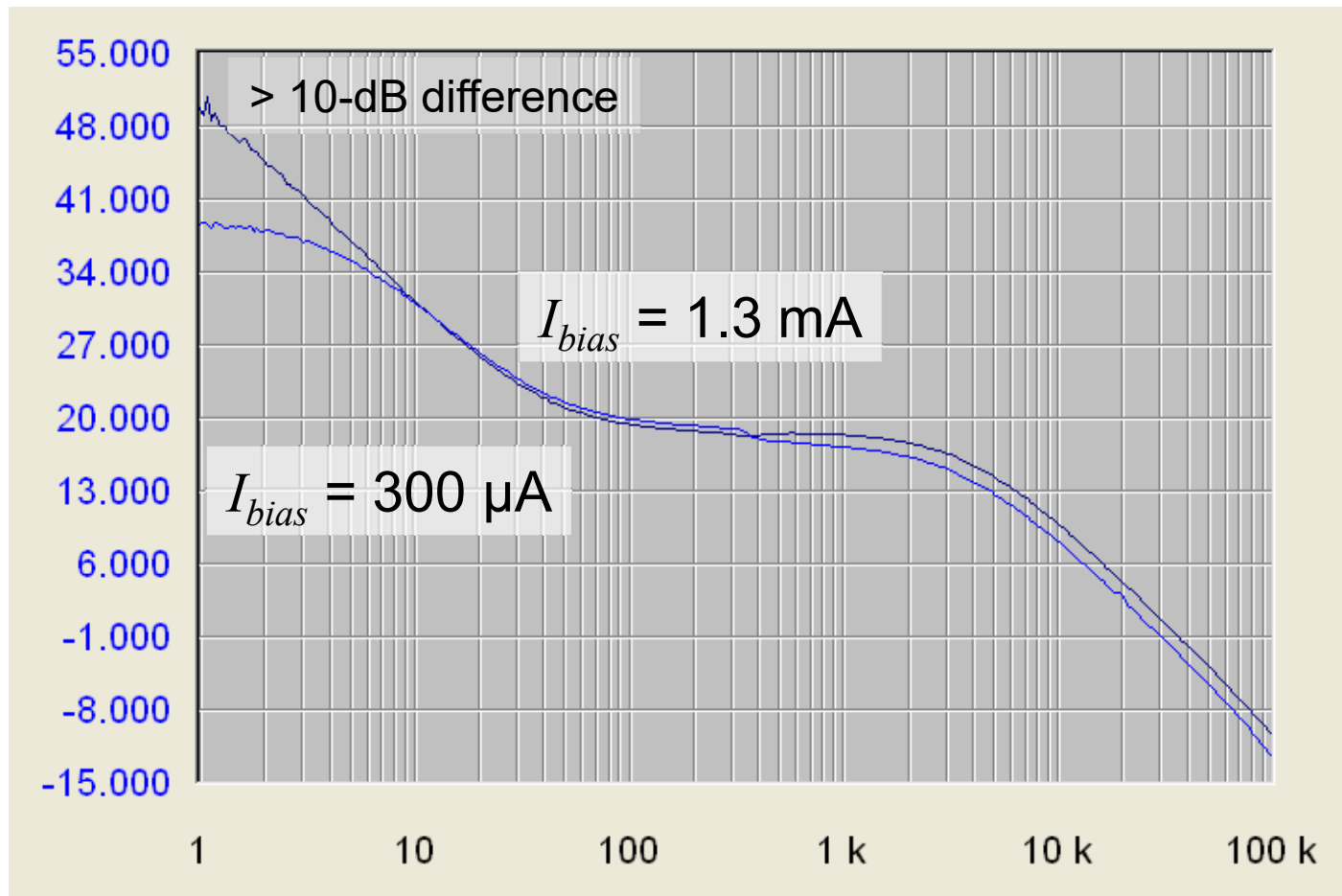
- ❑ Make sure enough current always biases the TL431
- ❑ If not, its open-loop suffers – a 10-dB difference can be observed!



$$R_{bias} = \frac{1}{1m} = 1 \text{ k}\Omega$$

Small-Signal Analysis

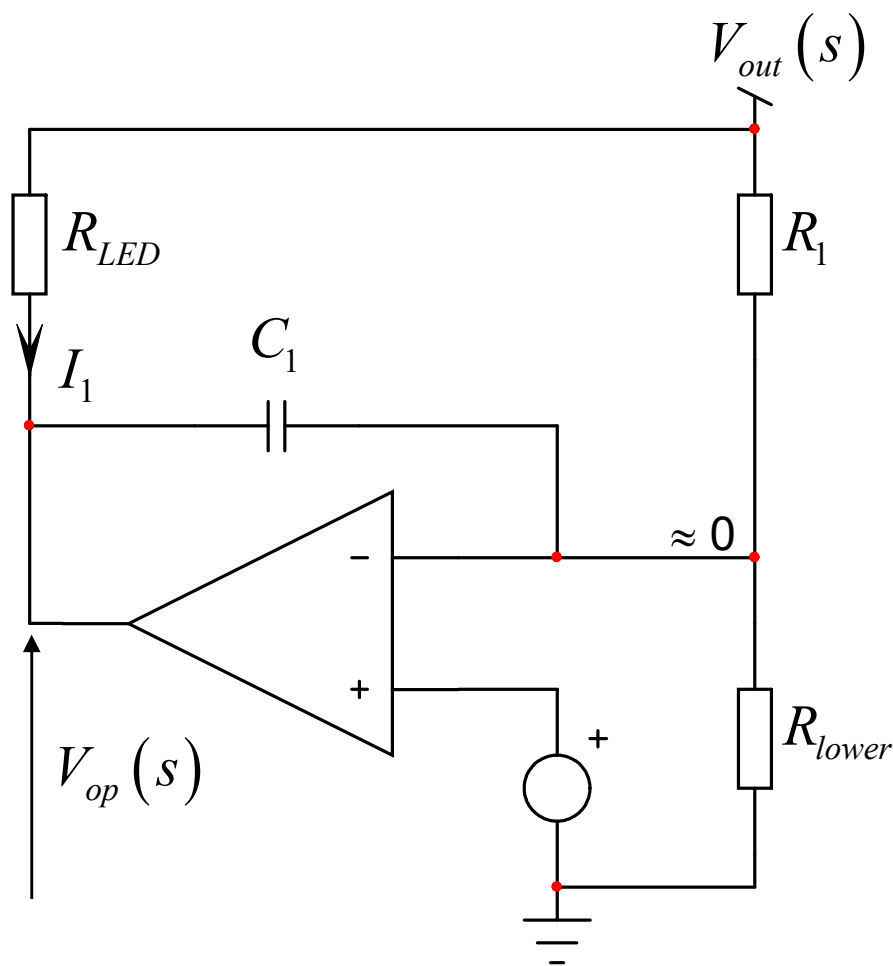- ❑ The TL431 is an open-collector op amp with a reference voltage
- ❑ Neglecting the LED dynamic resistance, we have:



$$I_1(s) = \frac{V_{out}(s) - V_{op}(s)}{R_{LED}} \cdot 1$$

$$V_{op}(s) = -V_{out}(s) \frac{sC_1}{R_{upper}} = -V_{out}(s) \frac{1}{sR_{upper}C_1}$$

$$I_1(s) = V_{out}(s) \frac{1}{R_{LED}} \left[1 + \frac{1}{sR_{upper}C_1} \right]$$

We know that: $V_{FB}(s) = -CTR \cdot R_{pullup} \cdot I_1$

$$\frac{V_{FB}(s)}{V_{out}(s)} = -\frac{R_{pullup} CTR}{R_{LED}} \left[\frac{1 + sR_{upper}C_1}{sR_{upper}C_1} \right]$$

Creating a High-Frequency Pole


□ In the previous equation we have:

✓ a static gain $G_0 = \text{CTR} \frac{R_{pullup}}{R_{LED}}$

✓ a 0-dB origin pole frequency $\omega_{po} = \frac{1}{C_1 R_{upper}}$


✓ a zero $\omega_{z_1} = \frac{1}{R_{upper} C_1}$

□ We are missing a pole for the type 2!

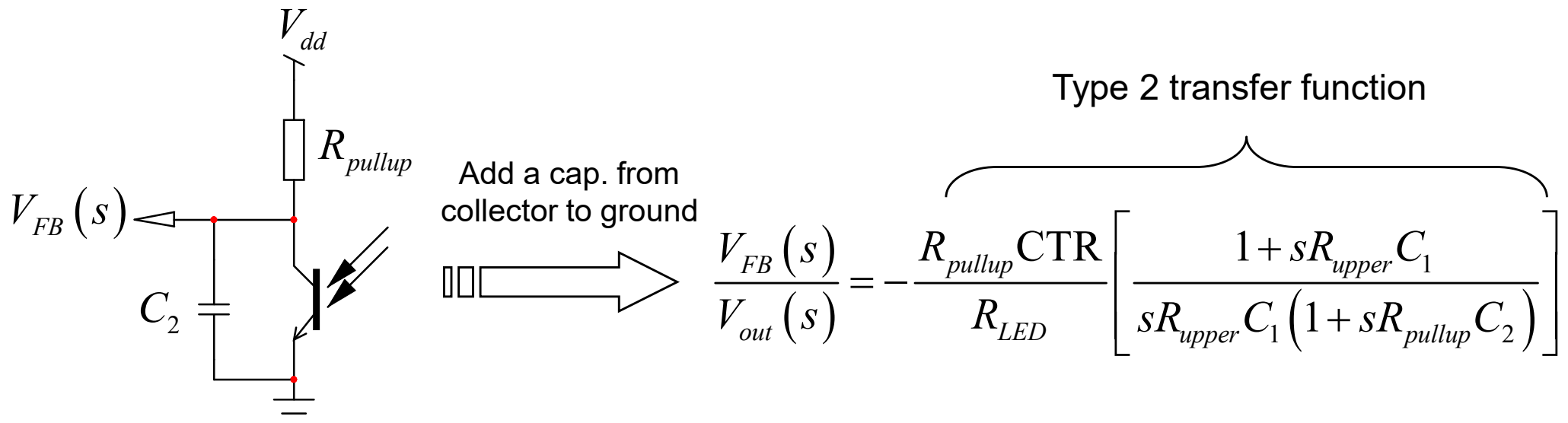



Understanding the Optocoupler Pole

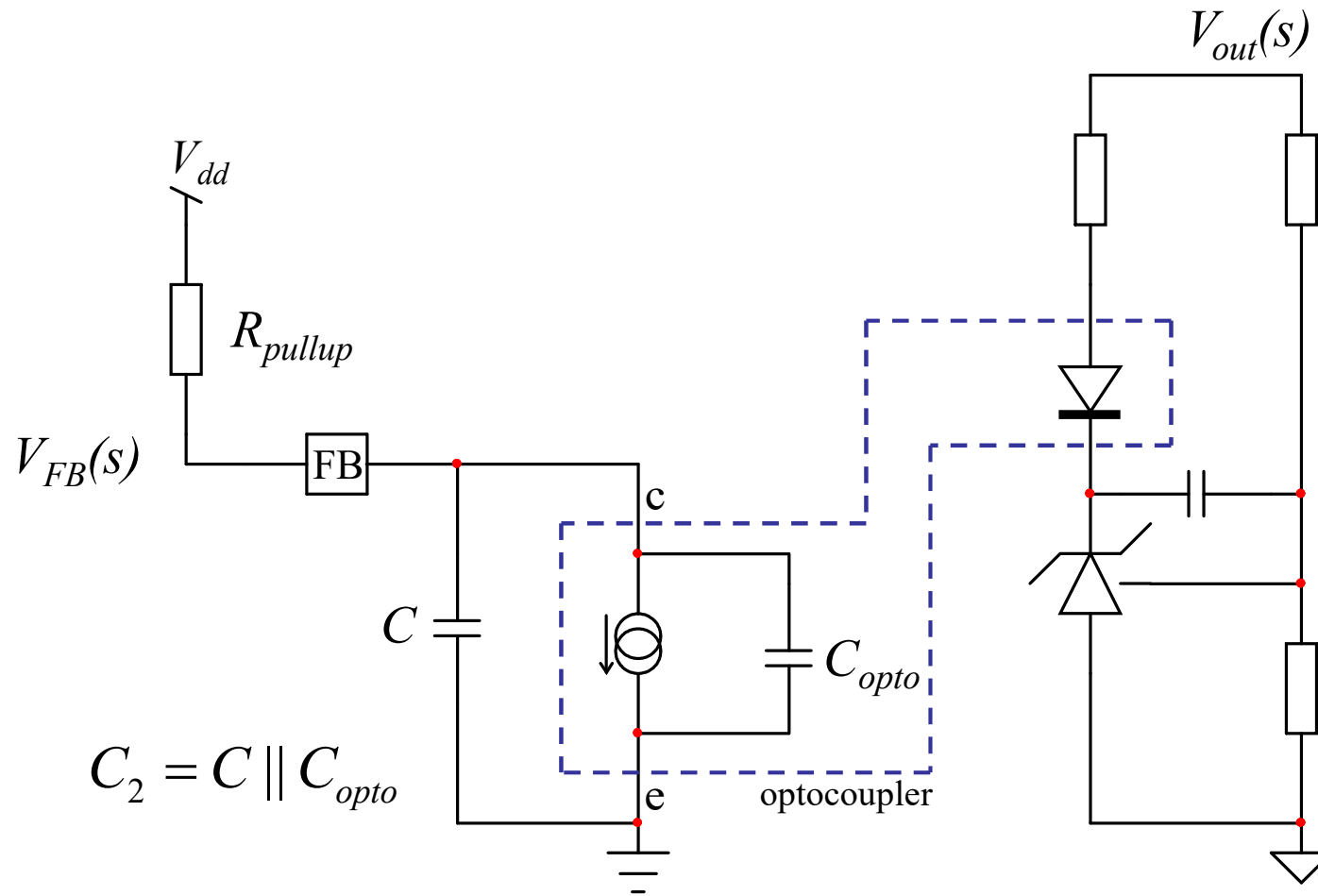- The optocoupler also features a parasitic capacitor
- it comes in parallel with C_2 and must be accounted for



Extracting the Pole

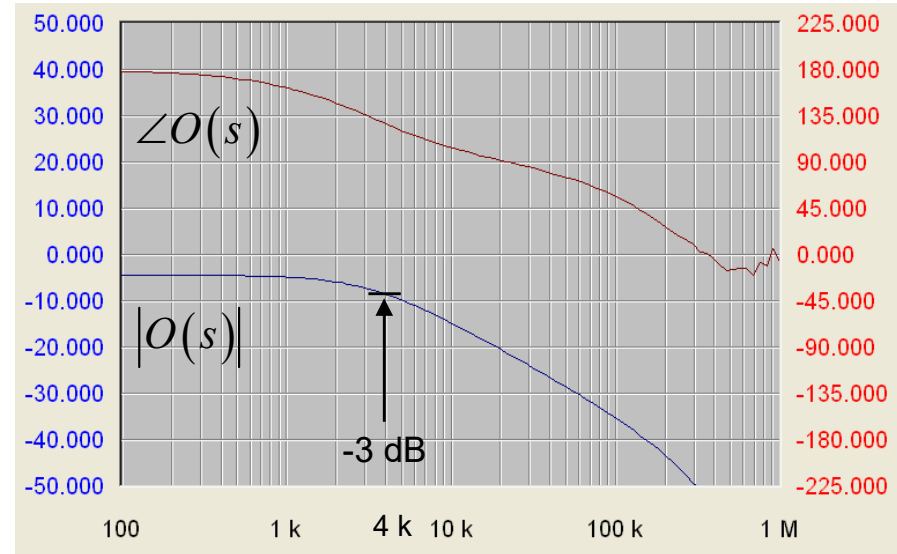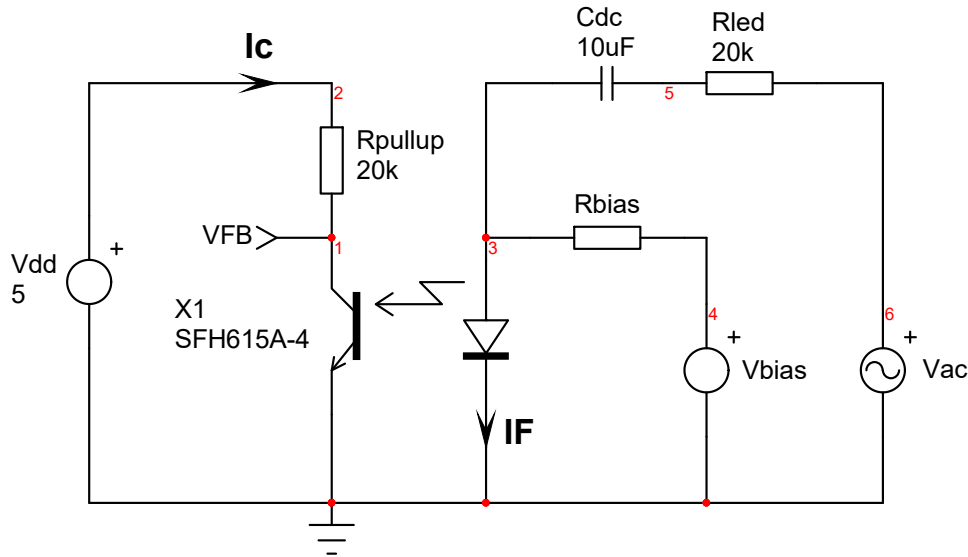
□ The optocoupler must be characterized to know where its pole is



□ Adjust V_{bias} to have V_{FB} at 2-3 V to be in linear region, then ac sweep

□ The pole in this example is found at 4 kHz

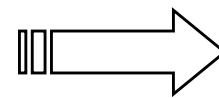
$$C_{opto} = \frac{1}{2\pi R_{pullup} f_{pole}} = \frac{1}{6.28 \times 20k \times 4k} \approx 2 \text{ nF}$$



Another design constraint!

Most Popular Compensator is Type 2

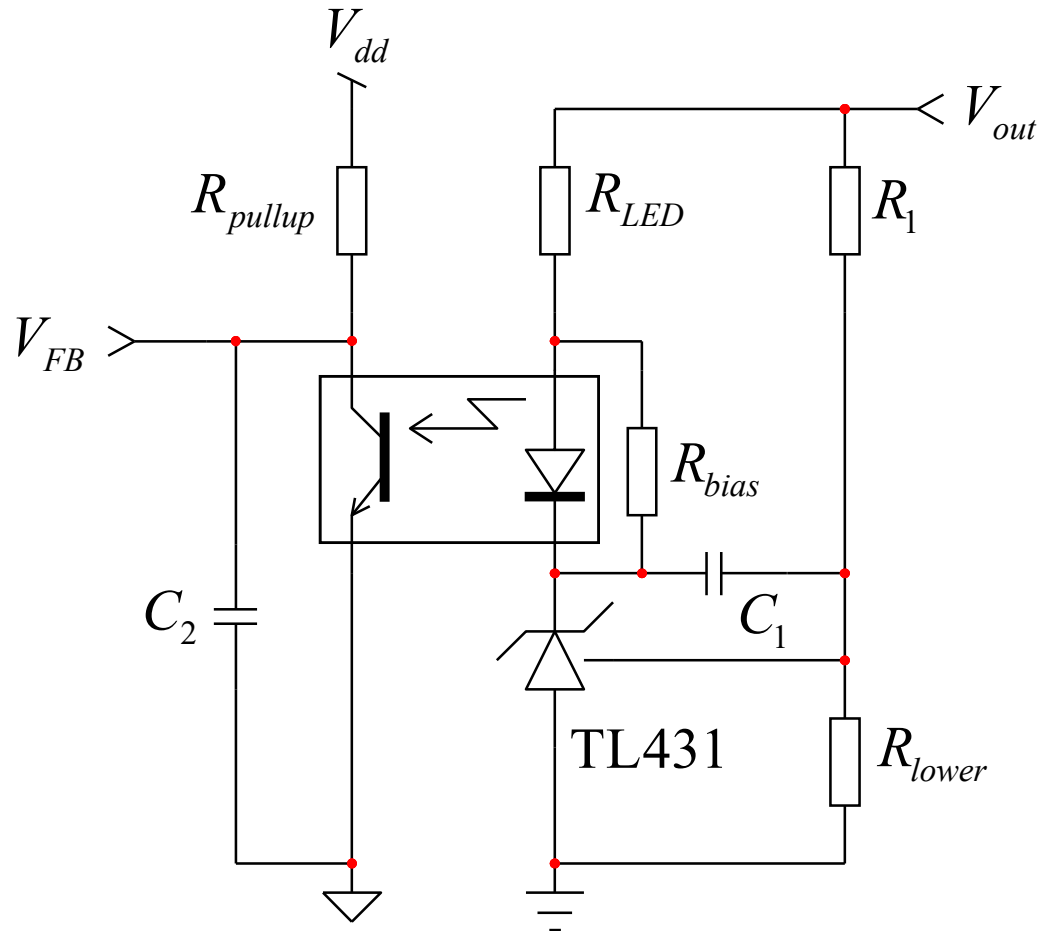- Our first equation was already a type 2 definition, we are all set!



$$G_0 = \text{CTR} \frac{R_{\text{pullup}}}{R_{\text{LED}}}$$

$$\omega_{z_1} = \frac{1}{R_1 C_1}$$

$$\omega_{p_1} = \frac{1}{R_{\text{pullup}} C_2}$$

- Just make sure the optocoupler contribution is involved...

Agenda

- ❑ What is a QR Converter?
- ❑ Deriving Operating Conditions
- ❑ The Over Power Problem
- ❑ Three Operating Modes
- ❑ Small-Signal Analysis – QR
- ❑ Small-Signal Analysis – VCO
- ❑ Compensating with TL431
- ❑ **Control Loop Design Example**
- ❑ Conclusion



Stabilizing a QR Converter

□ Assume a 60-W QR converter with the following values

$$V_{in,min} = 120 \text{ V} \quad N = 0.25 \quad R_{sense} = 0.3 \Omega \quad C_{out} = 1.2 \text{ mF}$$


$$V_{out} = 19 \text{ V} \quad L_p = 600 \mu\text{H} \quad R_{esr} = 20 \text{ m}\Omega \quad P_{out} = 60 \text{ W}$$

□ Plot the ac transfer function, select crossover (1 kHz)

$$f_z = 6.631 \text{ kHz}$$

$$f_{RHPZLL} = 25.001 \text{ kHz}$$

$$20 \cdot \log(|H_{QRLL}(i \cdot 2\pi \cdot f_k)|, 10)$$

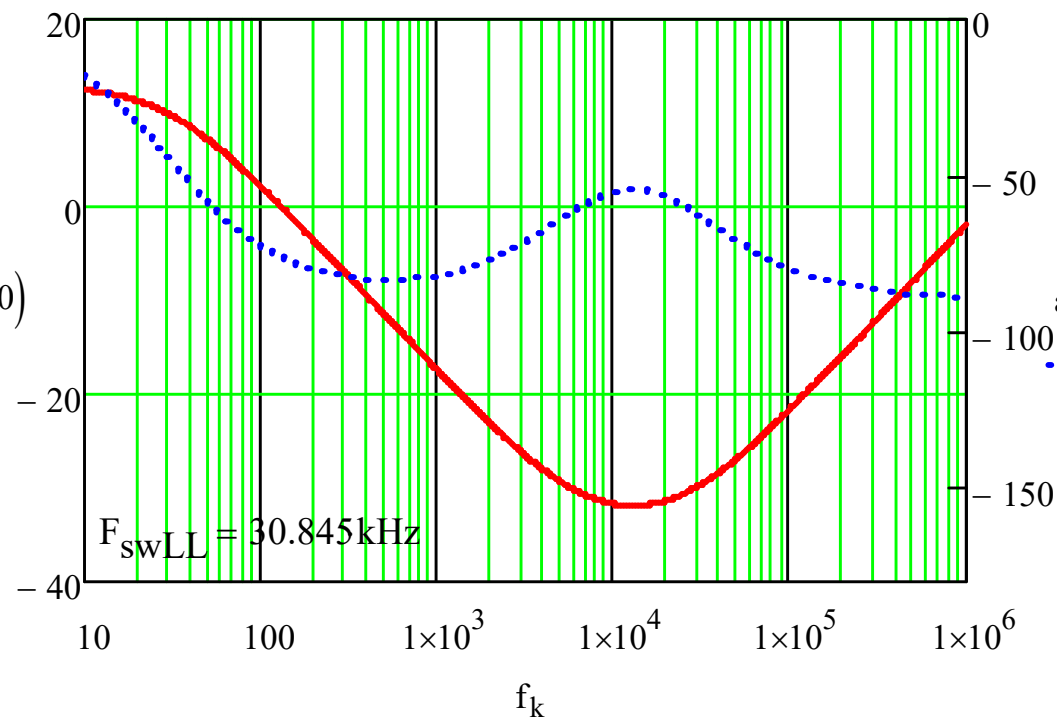

Low line, max power

Tailor the Compensator

- Extract attenuation and phase lag at 1 kHz from the graph

$$|H(1\text{kHz})| = -17.4\text{ dB} \quad \arg H(1\text{kHz}) = -82^\circ$$

- Shoot for a phase margin of 70°

- Lift the gain curve by 17.4 dB at 1 kHz, provide a boost of

$$\text{Boost} = \text{PM} - \arg H(f_c) - 90 = 70 + 82 - 90 = 62^\circ$$

- Position the pole and the zero to boost the phase by 62° at 1 kHz



$$k = \tan\left(\frac{\text{boost}}{2} + 45^\circ\right) = 4 \quad \longrightarrow \quad f_z = \frac{f_c}{k} = 249\text{ Hz} \quad f_p = k \cdot f_c = 4\text{ kHz}$$

- Apply this compensation parameters to the plant transfer function



Check Final Bode Plot

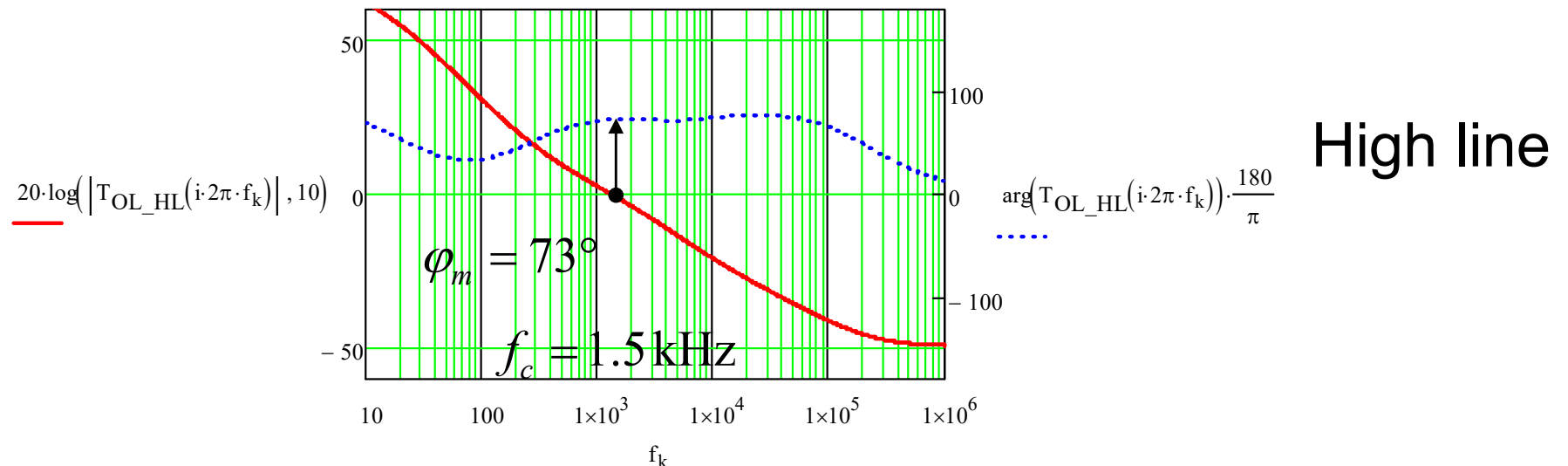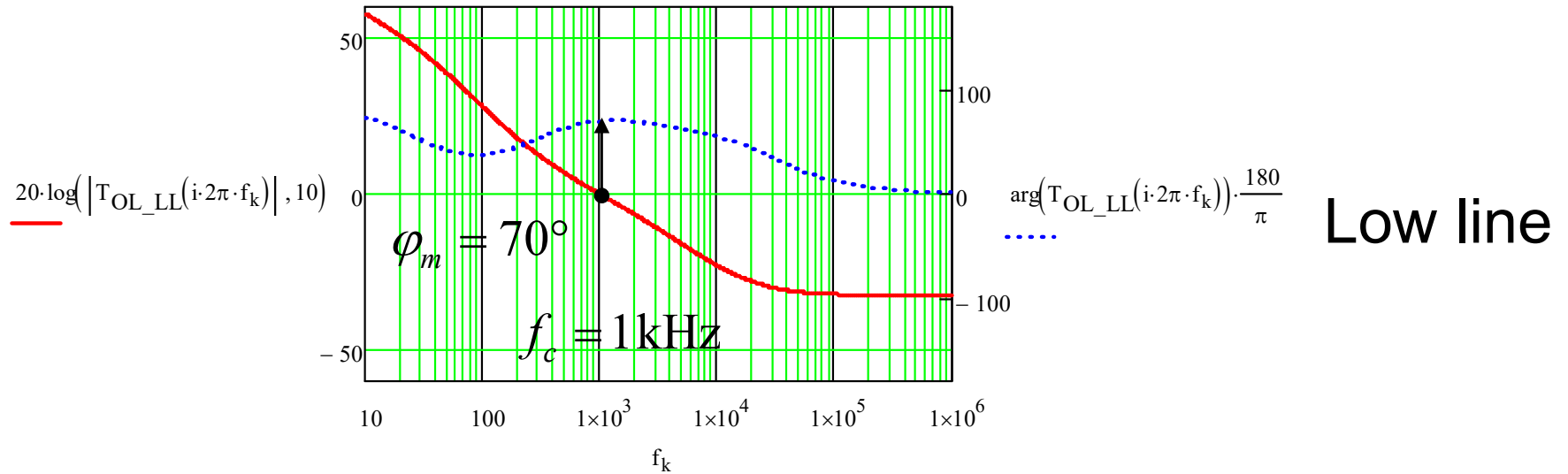- Plot the loop gain and check margins $T(s) = H(s)G(s)$



Test the Computed Values with SPICE

- This fixture gives the type 2 response with a TL431

parameters

$V_{out}=19$
 $R_{upper}=(V_{out}-2.5)/250u$
 $f_c=1k$
 $pm=70$
 $G_{fc}=-17.4$
 $pfc=-82$


 $G=10^{(-G_{fc}/20)}$
 $boost=pm-(pfc)-90$
 $pi=3.14159$
 $K=\tan((boost/2+45)*pi/180)$
 $C2=1/(2*pi*f_c*G*k*R_{upper})$
 $C1=C2*(K^2-1)$
 $R2=k/(2*pi*f_c*C1)$

 $F_{zero}=f_c/k$
 $F_{pole}=k*f_c$

 $R_{pullup}=20k$
 $R_{LED}=CTR*R_{pullup}/G$
 $C_{zero}=1/(2*pi*F_{zero}*R_{upper})$
 $C_{pole1}=1/(2*pi*F_{pole}*R_{pullup})$

 $C_{pole}=C_{pole1}-C_{opto}$

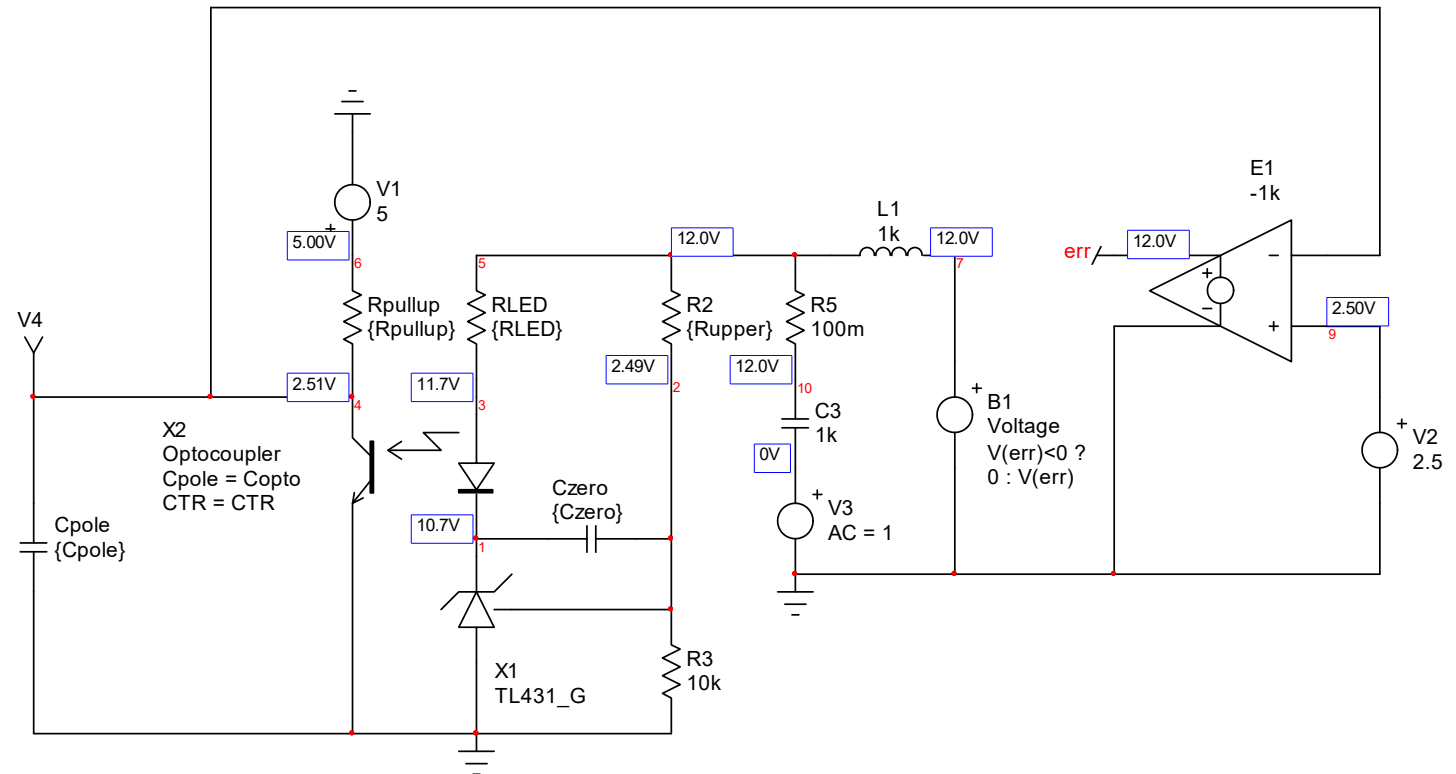
 $F_{opto}=4k$
 $C_{opto}=1/(2*pi*F_{opto}*R_{pullup})$
 $CTR = 0.3$



Automated type 2 compensator using a TL431

TL431 type 2 Design Example

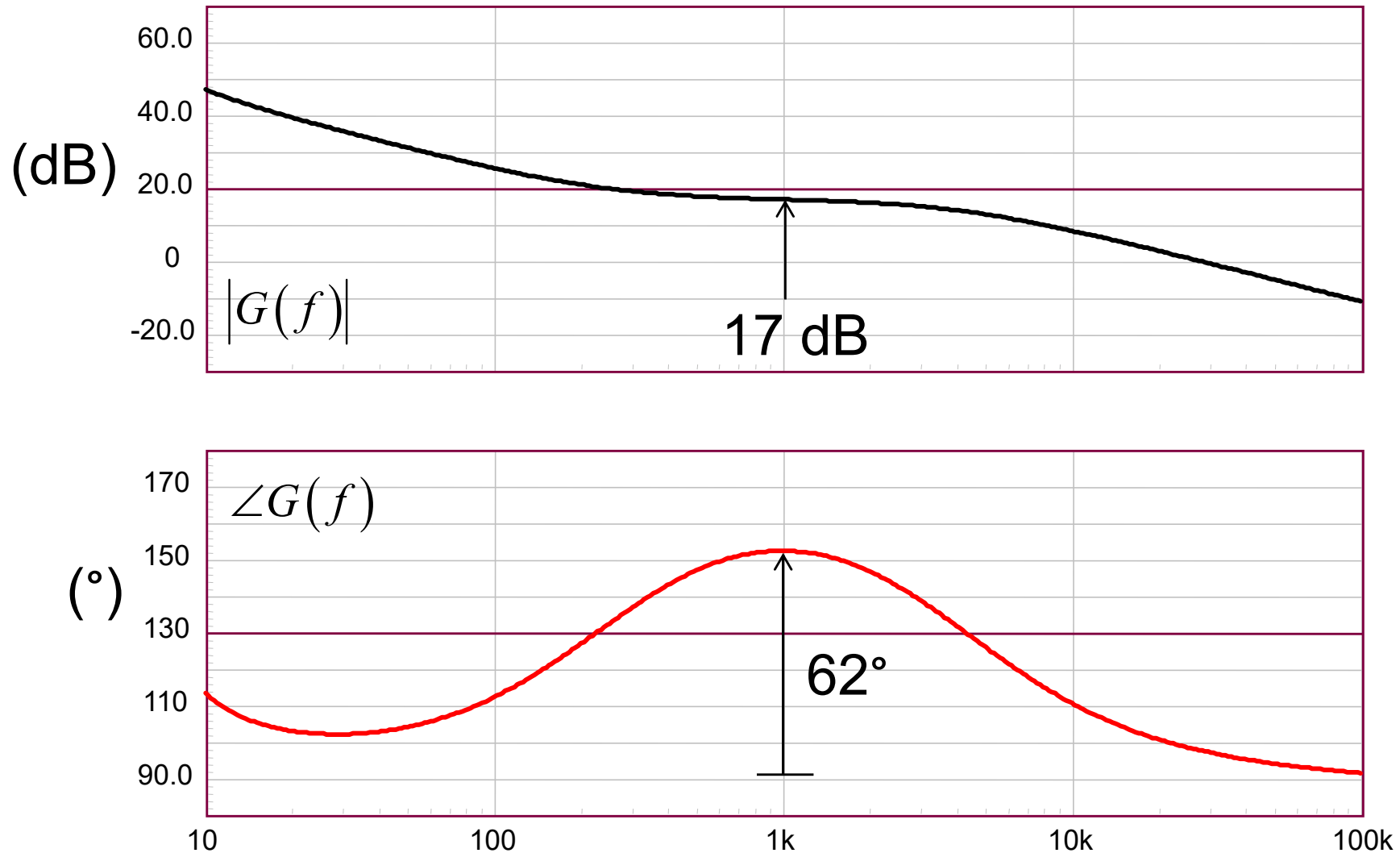- The 1-dB gain difference is linked to R_d and the bias current



ON Semiconductor Offer in QR

Product	Data Sheet	Compliance	Status	Description	Topology	Control Mode	f _{sw} Typ (kHz)	Stand-by Mode	UVLO (V)	Short Circuit Protection	Latch	Soft Start	V _{CC} Max (V)	Drive Cap. (mA)	Package Type
		Y	NEW Y			Y	Variable	Y	Y	Y	Y	Y	Y	Y	Y
NCP1336		Pb-free Halide free	Active NEW	Quasi-Resonant Current Mode Controller w/ HV Start-up	Flyback	Current Mode	Variable	Yes	9 - 15	Yes	Yes	Yes	28	500 / 800	SOIC-14 NB, Less Pin 13
NCL30051		Pb-free Halide free	Active	PFC and Resonant Half Bridge Combo Controller for LED Lighting		Voltage Mode	Variable				No				SOIC-16
NCP1308		Pb-free Halide free	Active	Current Mode Controller for Free Running Quasi-Resonant Operation	Flyback	Current Mode	Variable	Yes ⓘ	Yes ⓘ	Yes	Yes ⓘ	Yes	16	500 / 500	SOIC-8
NCP1337		Pb-free Halide free	Active	Quasi-Resonant Current Mode Controller Featuring Overpower Compensation	Flyback	Current Mode	Variable	Yes ⓘ	Yes ⓘ	Yes	Yes ⓘ	Yes	20	500 / 500	PDIP-8 SOIC-8
NCP1338		Pb-free Halide free	Active	PWM Current Mode Controller for Free Running Quasi-Resonant Operation	Flyback	Current Mode	Variable ⓘ	Yes ⓘ	Yes ⓘ	Yes	Yes	Yes	20	500 / 500	SOIC-8
NCP1351		Pb-free Halide free	Active	Variable Off-Time Current Mode Controller Featuring Short Circuit Protection	Flyback	Current Mode	Variable	No ⓘ	Yes ⓘ	Yes	Yes	No	28	400 / 400 ⓘ	PDIP-8 SOIC-8
NCP1377		Pb-free Halide free	Active	Current-Mode Controller for Free Running Quasi-Resonant Operation	Flyback	Current Mode	Variable	Yes ⓘ	Yes ⓘ	No	Yes ⓘ	Yes	16	500 / 500	PDIP-8 SOIC-8
NCP1379		Pb-free Halide free	Active	Quasi-Resonant Current Mode Controller	Flyback	Current Mode	Variable	Yes	9	Yes	Yes	Yes	28	500 / 800	SOIC-8
NCP1380		Pb-free Halide free	Active	Quasi-Resonant Current Mode Controller	Flyback	Current Mode	Variable	Yes	9	Yes	No Yes	Yes	28	500 / 800	SOIC-8



New Book on Loop Control

DESIGNING CONTROL LOOPS for LINEAR and SWITCHING POWER SUPPLIES

A TUTORIAL GUIDE

CHRISTOPHE BASSO

DESIGNING CONTROL LOOPS for LINEAR and SWITCHING POWER SUPPLIES

A TUTORIAL GUIDE

DESIGNING CONTROL LOOPS for LINEAR and SWITCHING POWER SUPPLIES A TUTORIAL GUIDE

Loop control is an essential area of electronics engineering that today's professionals need to master. Rather than delving into extensive theory, this practical book focuses on what engineers really need to know for compensating or stabilizing a given control system. Readers can turn instantly to practical sections with numerous design examples and ready-made formulas to help them with their projects in the field. Supported with over 450 illustrations and more than 1,500 equations, this authoritative volume:

- Demonstrates how to conduct analysis of control systems and provides extensive details on practical compensators;
- Helps engineers measure their system, showing how to verify whether or not a prototype is stable and features enough design margin;
- Explains how to secure high-volume production by bench-verified safety margins;
- Covers the underpinnings and principles of control loops, so readers can gain a more complete understanding of the material.

Christophe Basso is a product engineering director at ON Semiconductor in Toulouse, France. He received his B.S.E.E. in electronics from Montpellier University and his M.S.E.E. in power electronics from the National Polytechnic Institute of Toulouse. A senior member of the IEEE, Mr. Basso is recognized expert, patent holder, and author in the field.

Include bar code

ISBN 13: 978-1-60807-557-7
ISBN 10: 1-60807-557-5

ARTECH HOUSE
BOSTON | LONDON
www.artechhouse.com

CHRISTOPHE BASSO



Conclusion on QR Converters

- ❑ Quasi Square-Wave Resonant Converters feature:
 - minimal or zero turn-on losses, Zero Voltage Switching, ZVS
 - limited amount of radiated EMI
 - natural frequency dithering at low line
 - safe operation in short circuit
 - easy synchronous rectification implementation
 - 1st order system in small signal, easy to compensate

- ❑ Despite these bullets, QR converters suffer from:
 - variable operating frequency, line and load dependency
 - discontinuous operation leads to high conduction losses
 - large output power delivery discrepancy between line levels
 - higher losses in transformer core compared to CCM

