

Introduction to Space Vector Modulation Terminology and Illustrations

Christophe Basso

Business Development Manager


IEEE Senior Member

Agenda

- Symmetrical Components
- Clarke Transform
- Park Transform
- Power Processing
- Power Factor Correction

Three-Phase Generators

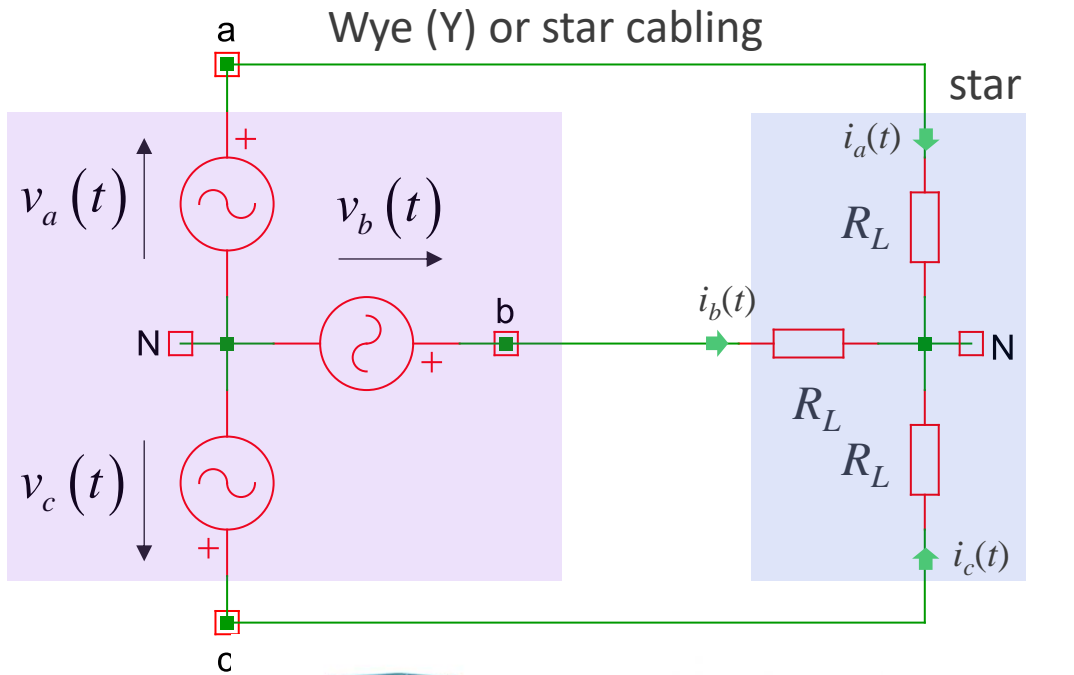- A power plant delivers 3 voltages out of phase by 120° and referenced to a neutral point
- For a given wire gauge, more power is conveyed in a 3-phase than in a 1-phase network
- ✓ In a balanced system, there is no current flowing in the neutral wire



Power plant




Mathworks [video](#)




3-phase load

Phase-neutral voltage

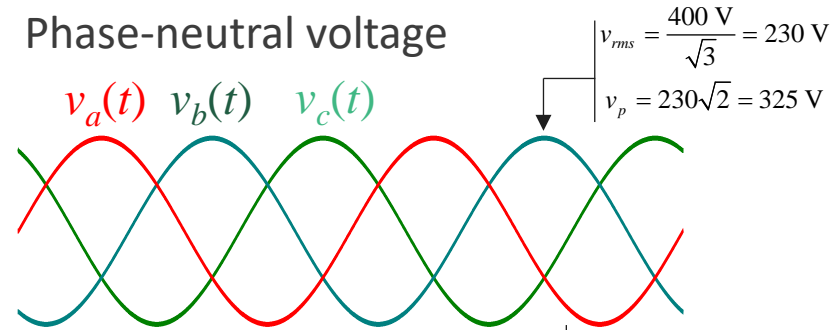

Inter-phase voltage

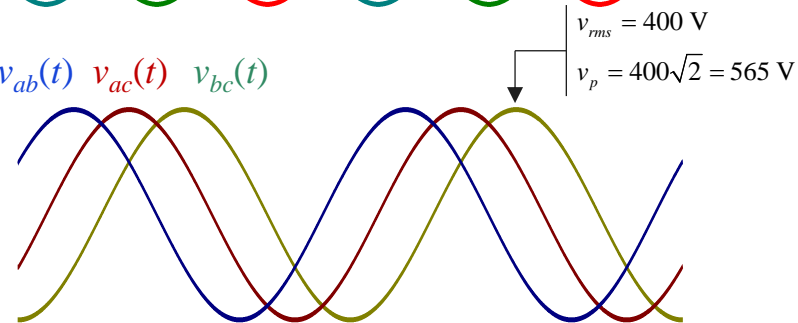

$$v_a(t) = V_{AC}\sqrt{2}\sin(\omega t + \varphi_1) \quad \varphi_1 = 0^\circ$$

$$v_b(t) = V_{AC}\sqrt{2}\sin(\omega t + \varphi_2) \quad \varphi_2 = -120^\circ$$

$$v_c(t) = V_{AC}\sqrt{2}\sin(\omega t + \varphi_3) \quad \varphi_3 = -240^\circ$$

Balanced system



$$\sum_{k \in \{a,b,c\}} v_k(t) = 0 \quad \text{and} \quad \sum_{k \in \{a,b,c\}} i_k(t) = 0$$

$$R_L := 50\Omega$$

$$P_L := \frac{V_{AC}^2}{R_L} = 1.058\text{kW}$$






Total power is 3 times the power per phase

$$P_{3\text{tot}}(t) := \frac{v_a(t)^2}{R_L} + \frac{v_b(t)^2}{R_L} + \frac{v_c(t)^2}{R_L}$$

$$P_{\text{avg}} := F_{\text{line}} \int_0^{T_{\text{line}}} P_{3\text{tot}}(t) dt = 3.174\text{kW}$$


A Balanced System

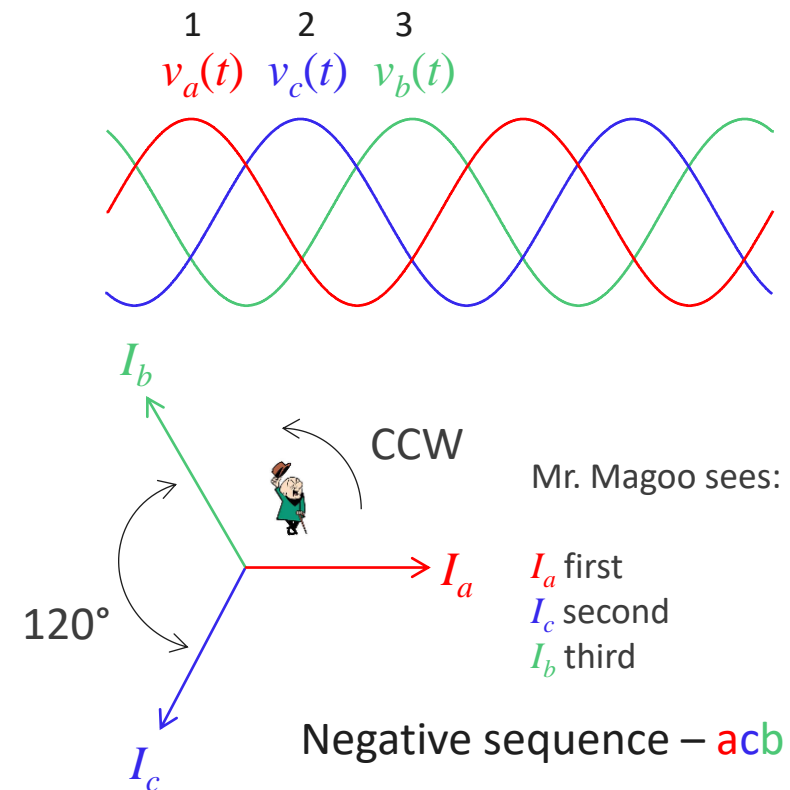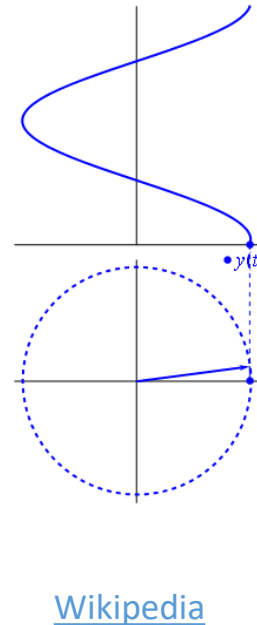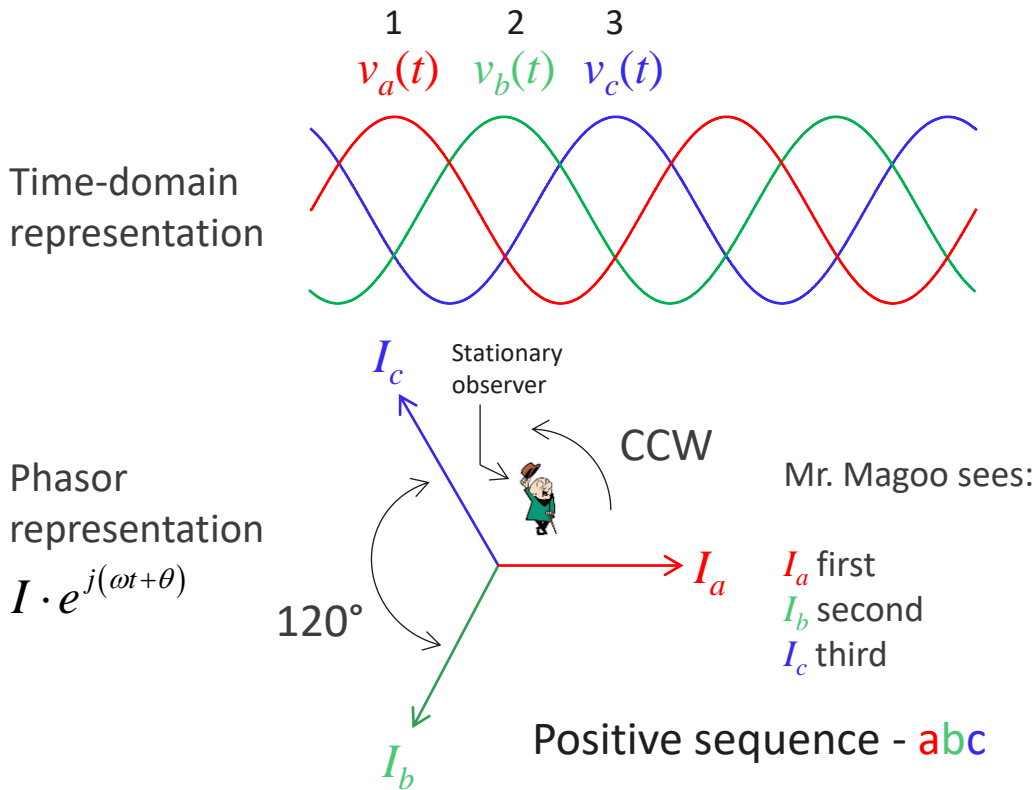- A tri-phase system is balanced when the three conditions below are respected:
 - ✓ Angle: there is a constant 120° angle between each of the sinusoidal waveforms
 - ✓ All phase currents are of equal magnitude: $\bar{I}_a = \bar{I}_b = \bar{I}_c$
 - ✓ The phase sequence is positive with A, B and C or negative with A, C and B




An Unbalanced System

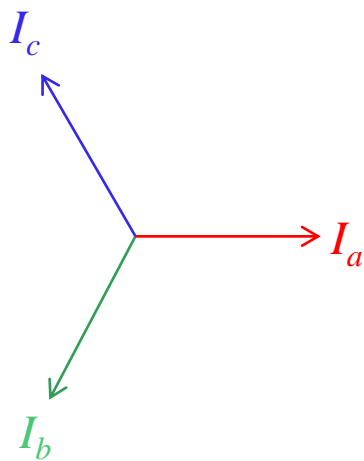
- A system becomes unbalanced or unsymmetrical if:
 - ✓ The output impedances of the distribution networks are unbalanced
 - ✓ A single- or a two-phase loads exhibit unequal consumptions
 - ✓ Highly nonlinear loads are powered from the network: distorted currents
 - ✓ Single phasing occurs in a motor: one of the supply lines opens



Balanced
Symmetrical

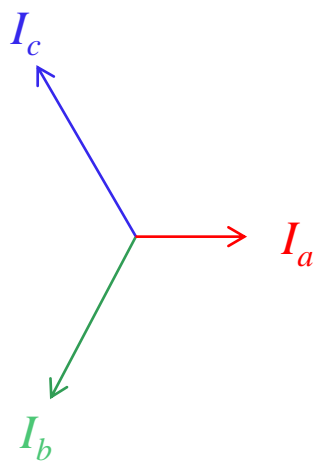

Unbalanced
Unsymmetrical

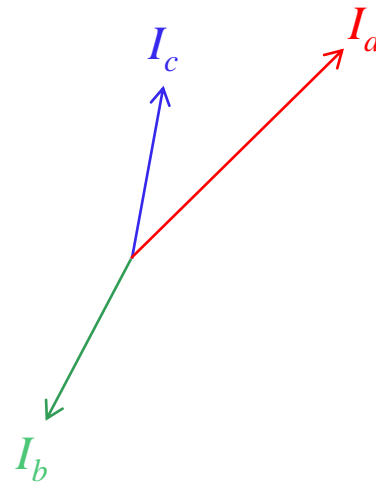




Unbalanced
Unsymmetrical

- ❖ Unbalanced operation leads to negative sequence in 3-phase motors



Faults in a Three-Phase System

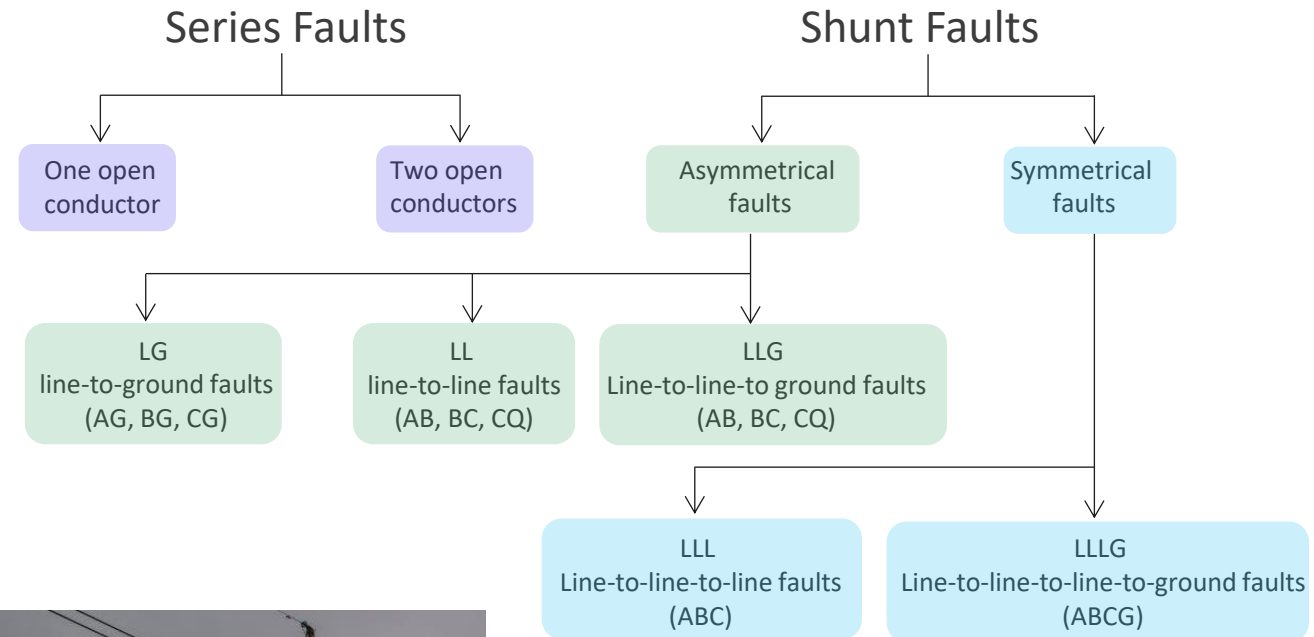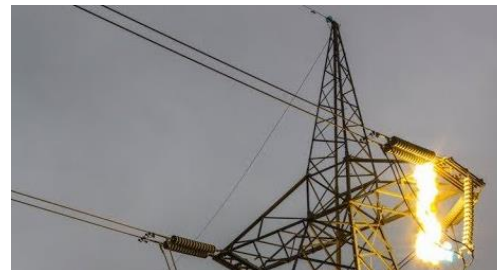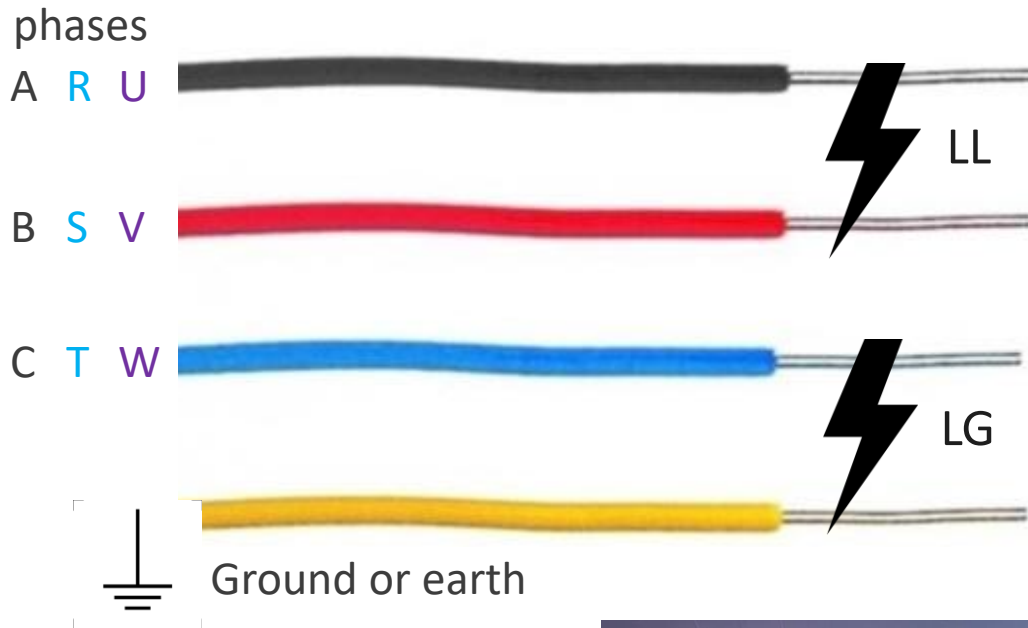
- During operations, short circuits can occur on distribution lines
- It is important for utility companies to understand what the type of short circuits:
 - Line-to-line, line-to-ground, line-to-line-to-ground and so on



How to determine circulating currents in a faulty 3-phase system?


Symmetrical Components

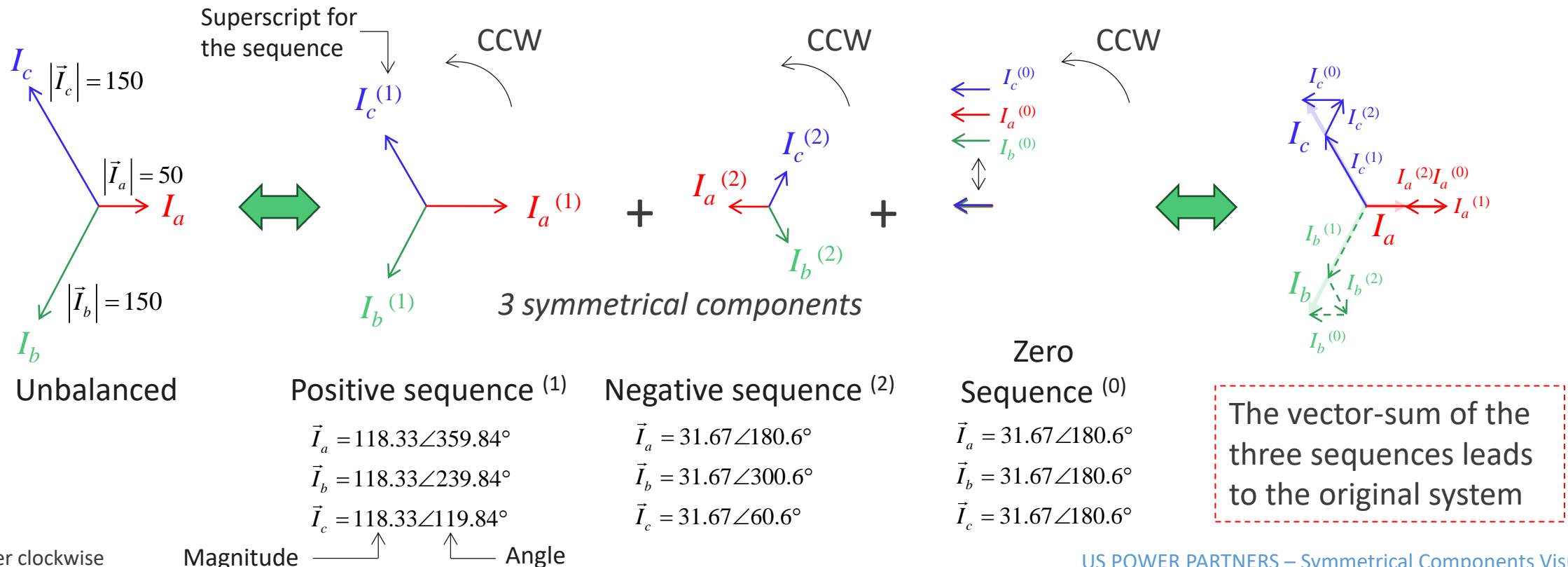- It is possible to show that a set of 3 unbalanced phasors can be expressed as the sum of:
 - ✓ A set of three *positive-sequence* vectors
 - ✓ A set of three *negative-sequence* vectors
 - ✓ A set of three *zero-sequence* vectors
- } **Symmetrical** components: same magnitude, constant 120° angle
 → Same magnitude, all colinear






Symmetrical Components in Absence of Fault

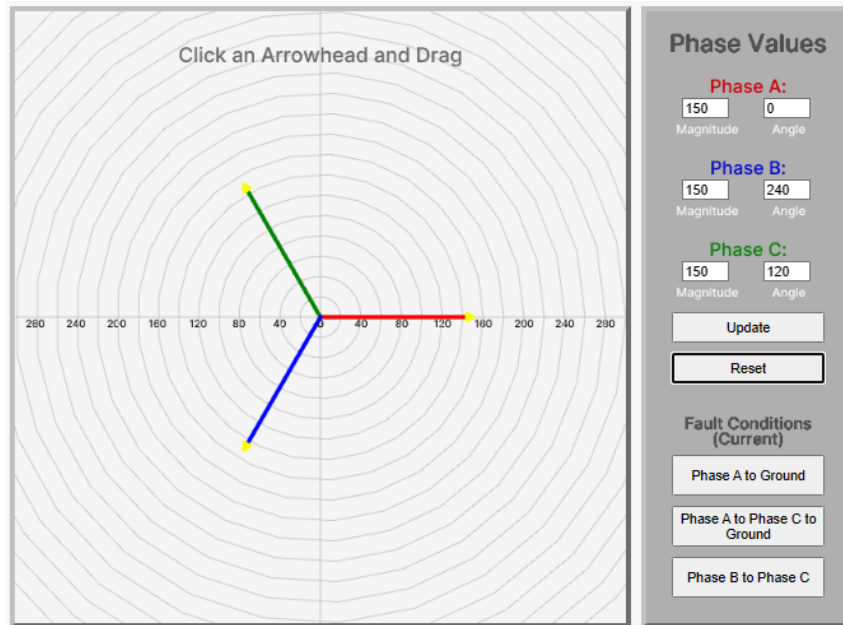- In normal operation, when the system is balanced:
 - ✓ The positive-sequence is the same as the original set of phasors
 - ✓ The negative-sequence component is zero
 - ✓ The zero-sequence component is also zero: $I^{(0)} = I_a + I_b + I_c = 0$





Balanced system

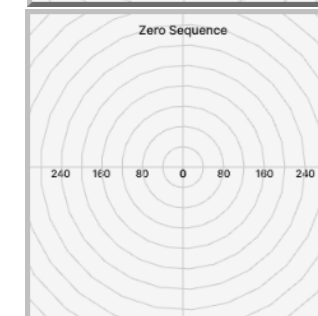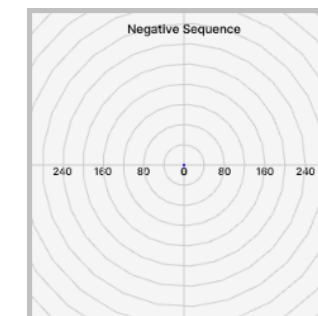
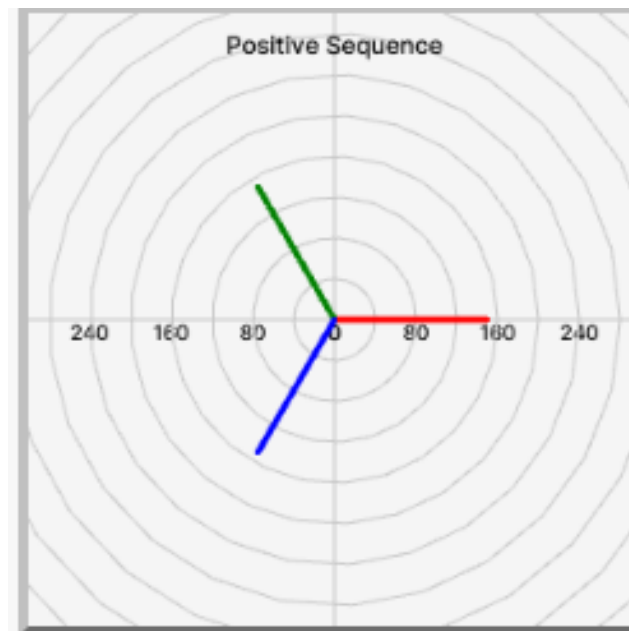


Analyzing Fault Signatures

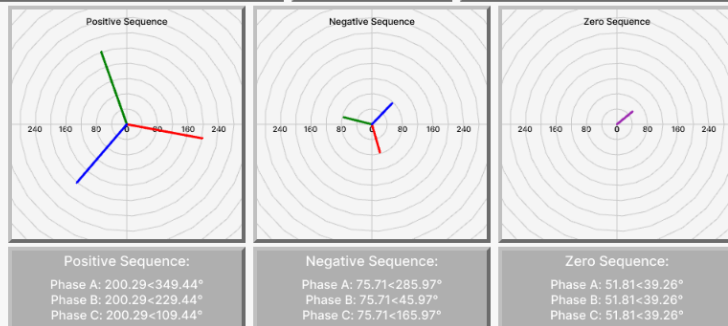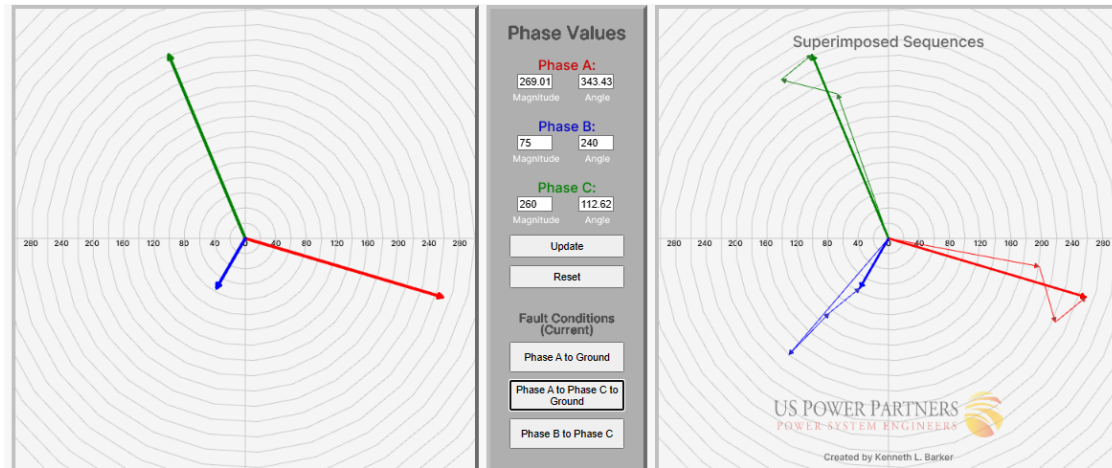- With fault signature analysis, you can identify the issue and react accordingly





Phase A to phase C shorted to ground

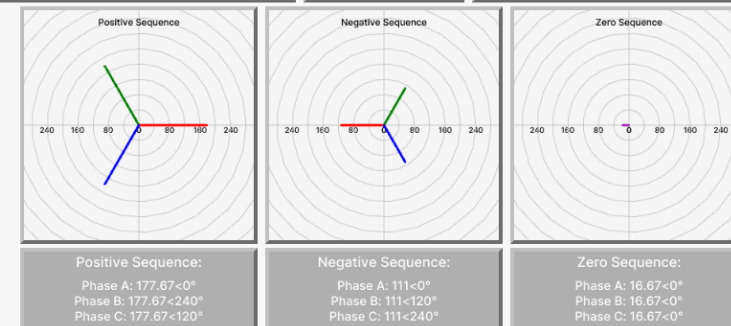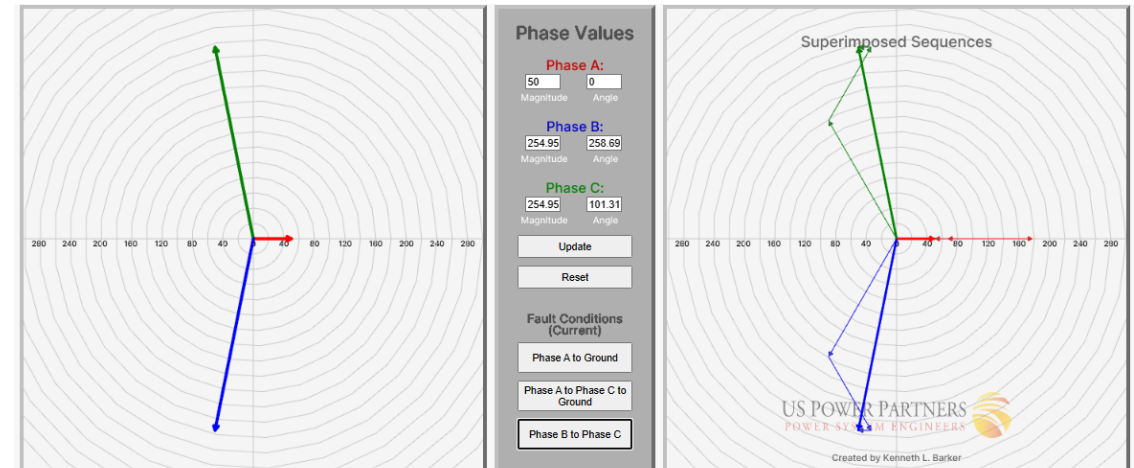

Phase B to phase C short circuit

Magnetic Field

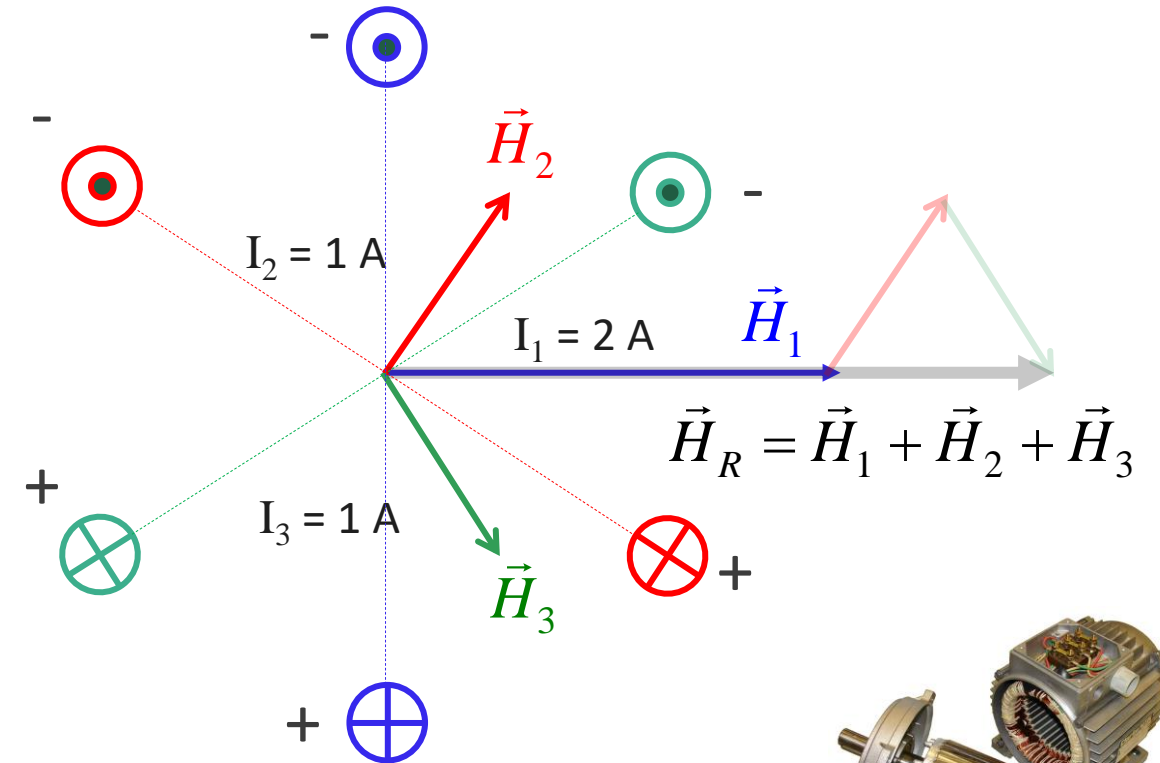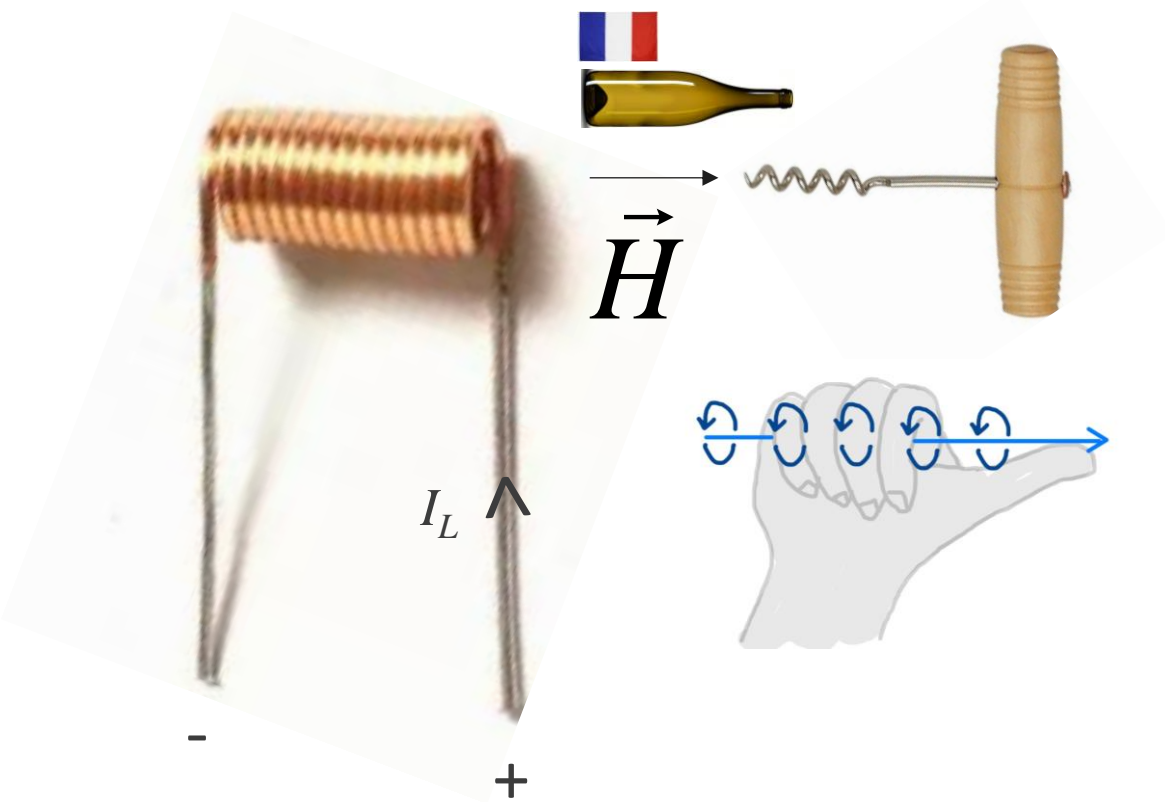- When a coil is subject to a current, it produces a magnetic field
- The direction of the field is determined by the right-hand rule





- Consider three individual coils biased by a current
- ✓ The total magnetic field is the vector sum of the fields

Agenda

- Symmetrical Components
- Clarke Transform
- Park Transform
- Power Processing
- Power Factor Correction

A Rotating Field Vector

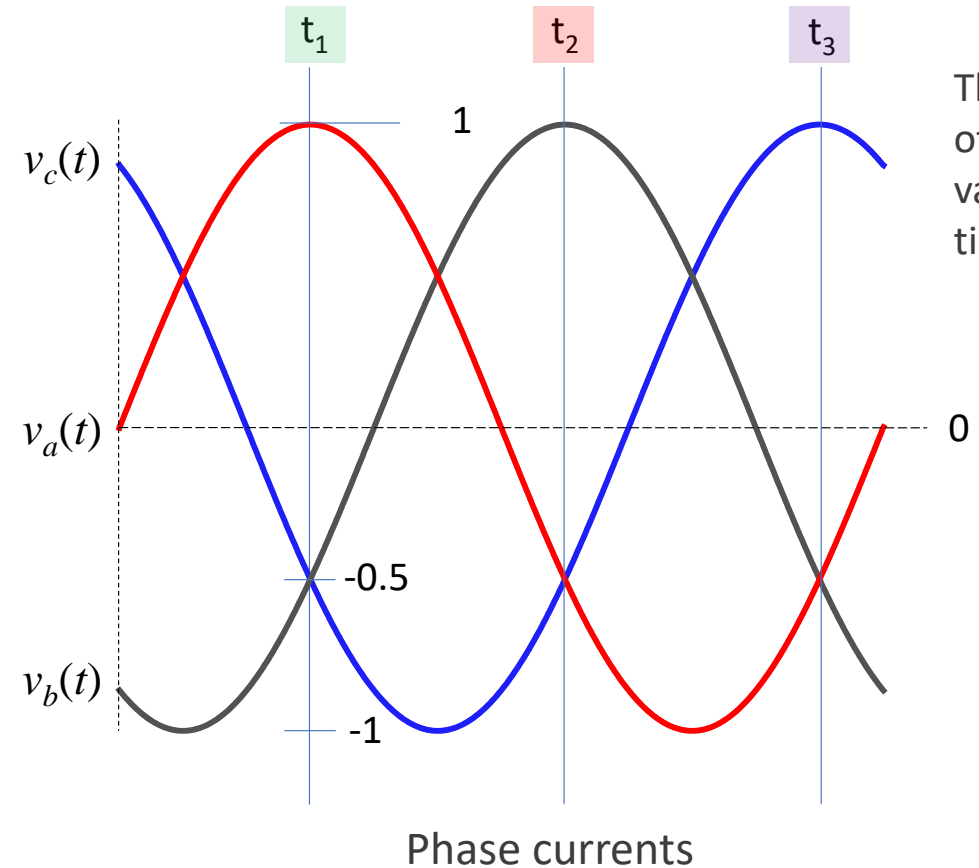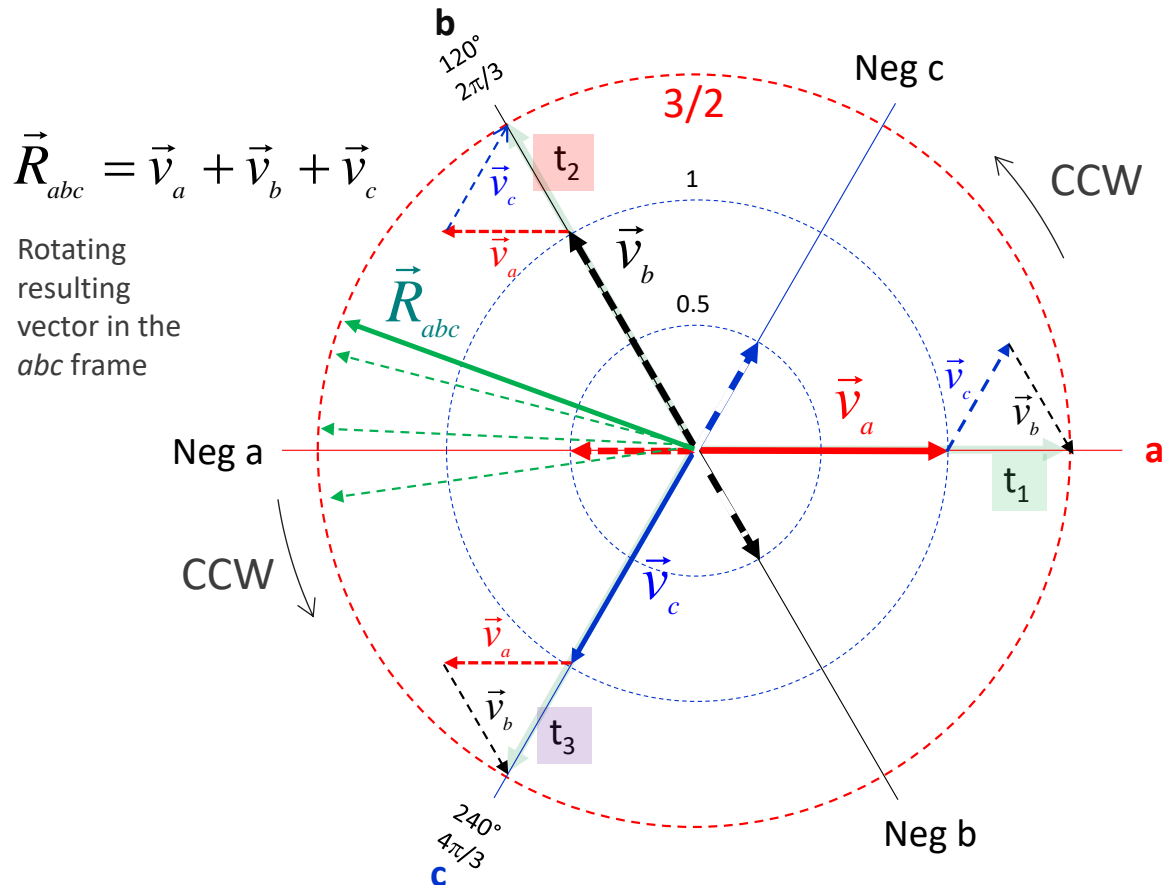
- As each phase current changes amplitude and angle, a rotating *space* vector appears
- The magnitude of this vector is 1.5 times the peak amplitude of the phases



- The resulting vector is made of three components, represented in the *abc* frame


Animated Field

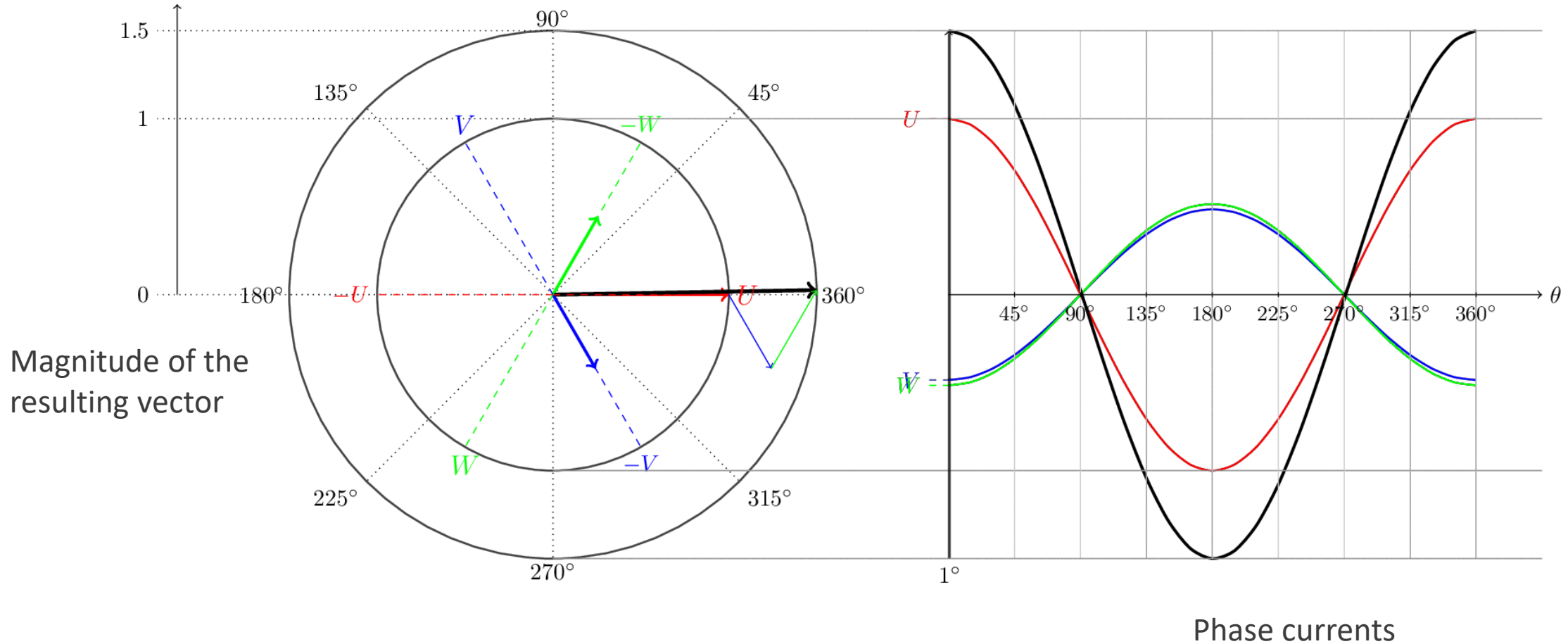- The equivalent *space* vector rotates along the sinusoidal waveforms



Changing the Frame – abc to $\alpha\beta$

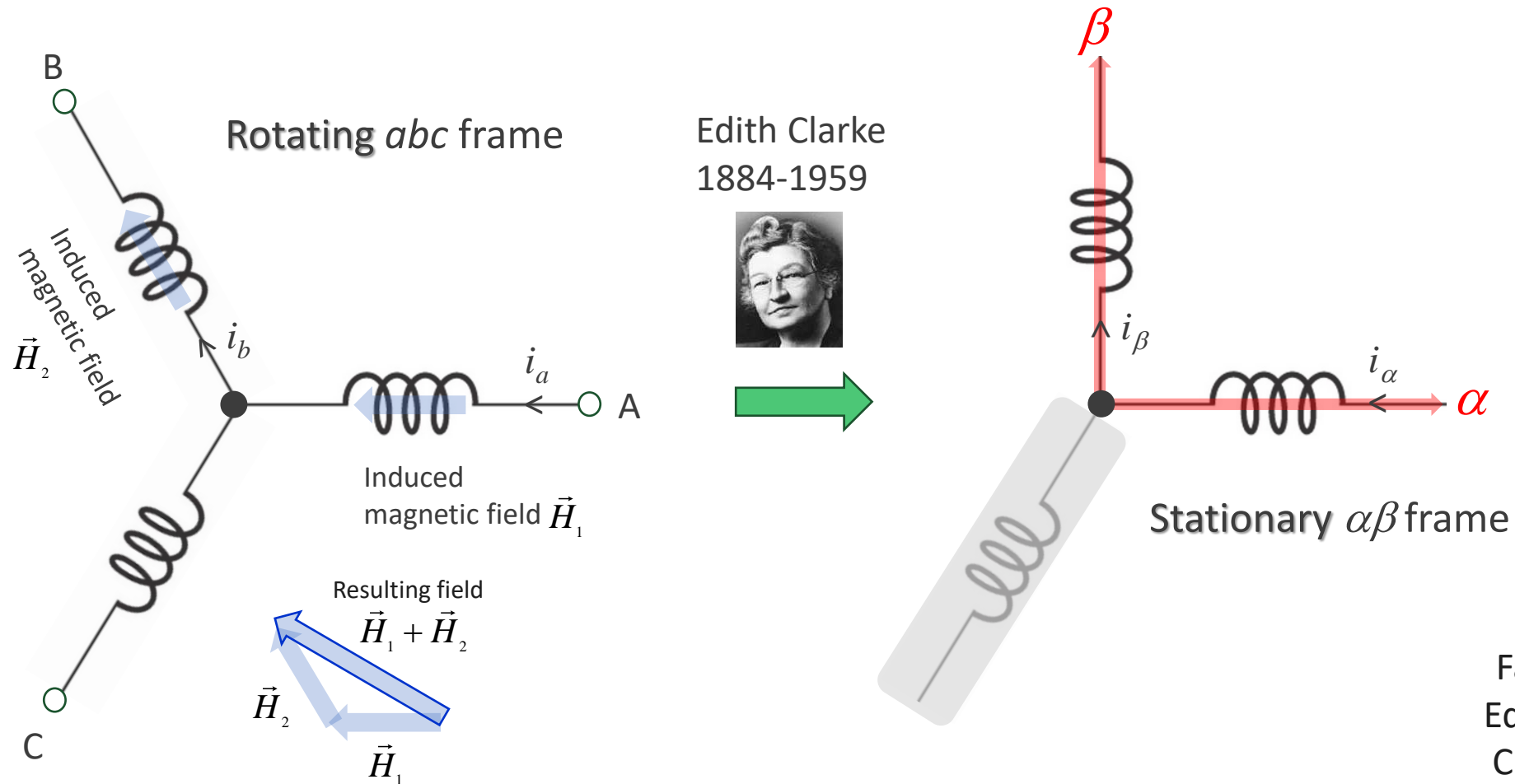- The magnetic field is synthesized by three varying components: 3-dimension frame
- The idea is to go from a **three**-dimension (abc) to a **two**-dimension system ($\alpha\beta$)




Fast Eddie Clark



Understanding the Transform

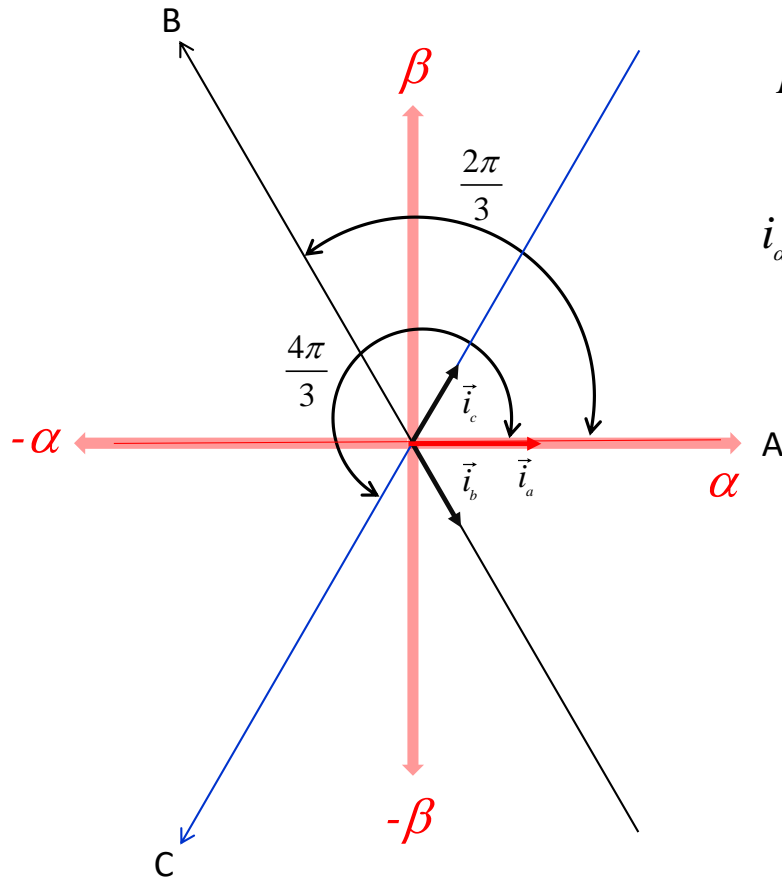- You are projecting three vectors onto two axes, α and β
- Use Euler's notation to write the sum in phasor notation and rearrange



$$\vec{R} = \vec{i}_a + \vec{i}_b + \vec{i}_c = i_a e^{j0} + i_b e^{j\frac{2\pi}{3}} + i_c e^{j\frac{4\pi}{3}} \longrightarrow Ae^{j\theta} = A(\cos\theta + j\sin\theta)$$

$$\vec{R}_{\alpha\beta} = \left[i_a \cdot 1 + i_b \cos\left(\frac{2\pi}{3}\right) + i_c \cos\left(\frac{4\pi}{3}\right) \right] + j \left[i_a \cdot \sin(0) + i_b \sin\left(\frac{2\pi}{3}\right) + i_c \sin\left(\frac{4\pi}{3}\right) \right]$$

$$i_\alpha + j \cdot i_\beta = \left[i_a - 0.5i_b - 0.5i_c \right] + j \left[0 + \frac{\sqrt{3}}{2}i_b - \frac{\sqrt{3}}{2}i_c \right]$$

Real

Imaginary

$$\begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix} = \frac{2}{3} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} \xrightarrow{\text{direct}} \begin{aligned} i_\alpha(t) &= \frac{2}{3}i_a(t) - \frac{1}{3}[i_b(t) + i_c(t)] \\ i_\beta &= \frac{1}{\sqrt{3}}[i_b(t) - i_c(t)] \end{aligned}$$

$$\begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ -\frac{1}{2} & \frac{\sqrt{3}}{2} \\ -\frac{1}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix} \xrightarrow{\text{inverse}} \begin{aligned} i_a(t) &= i_\alpha(t) \\ i_b(t) &= -\frac{1}{2}i_\alpha(t) + \frac{\sqrt{3}}{2}i_\beta(t) \\ i_c(t) &= -\frac{1}{2}i_\alpha(t) - \frac{\sqrt{3}}{2}i_\beta(t) \end{aligned}$$

Power-Invariant Transform

- Clarke's transform preserves current and voltage values but not power
- Concordia's transform is similar to Clarke's but is now power-invariant

$$\text{Direct} \quad \begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix} = \sqrt{\frac{2}{3}} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix}$$

$$\text{Inverse} \quad \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix} = \sqrt{\frac{2}{3}} \begin{bmatrix} 1 & 0 \\ -\frac{1}{2} & \frac{\sqrt{3}}{2} \\ -\frac{1}{2} & -\frac{\sqrt{3}}{2} \end{bmatrix} \begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix}$$

Assume the following instantaneous values at $t = 0$

$$\begin{aligned} v_a &= V_p & i_a &= I_p \\ v_b &= -0.5V_p & i_b &= -0.5I_p \\ v_c &= -0.5V_p & i_c &= -0.5I_p \end{aligned}$$



$$P = v_a i_a + v_b i_b + v_c i_c = \frac{3}{2} V_p I_p$$

Using Clarke's transform:

$$\begin{aligned} v_\alpha &= V_p & i_\alpha &= I_p \\ v_\beta &= 0 & i_\beta &= 0 \end{aligned}$$



$$P = v_\alpha i_\alpha + v_\beta i_\beta = V_p I_p \quad \text{wrong}$$

Using Concordia's transform:

$$\begin{aligned} v_\alpha &= \sqrt{\frac{3}{2}} V_p & i_\alpha &= \sqrt{\frac{3}{2}} I_p \\ v_\beta &= 0 & i_\beta &= 0 \end{aligned}$$



$$P = v_\alpha i_\alpha + v_\beta i_\beta = \frac{3}{2} V_p I_p$$

Simulation Waveforms

$V_{in} := 100V$ $F_{line} := 50Hz$

$t := 10\mu s, 20\mu s .. 100ms$ $T_{line} := \frac{1}{F_{line}}$


$\omega := 2 \cdot \pi \cdot F_{line}$ $R_L := 10\Omega$

$v_a(t) := V_{in} \cdot \sqrt{2} \cdot \sin(\omega \cdot t)$

$v_b(t) := V_{in} \cdot \sqrt{2} \cdot \sin(\omega \cdot t - 120^\circ)$

$v_c(t) := V_{in} \cdot \sqrt{2} \cdot \sin(\omega \cdot t - 240^\circ)$

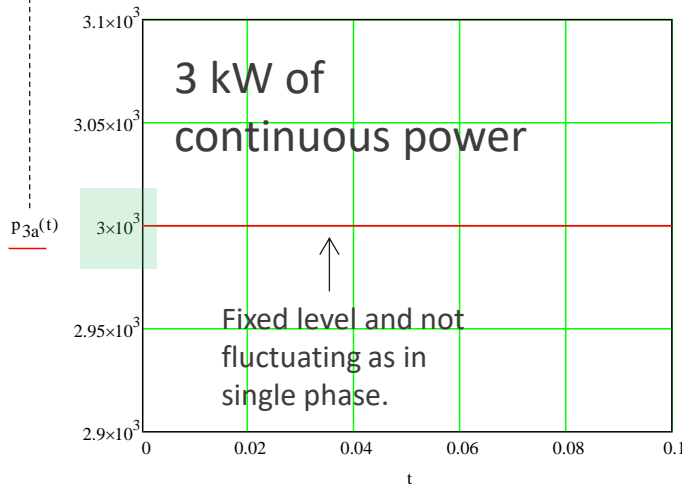$P_{3a}(t) := \frac{v_a(t)^2}{R_L} + \frac{v_b(t)^2}{R_L} + \frac{v_c(t)^2}{R_L}$ Instantaneous power



$V_\alpha(t) := \sqrt{\frac{2}{3}} \cdot \left(v_a(t) - \frac{1}{2} \cdot v_b(t) - \frac{1}{2} \cdot v_c(t) \right)$

$V_\beta(t) := \sqrt{\frac{2}{3}} \cdot \left(0 \cdot v_a(t) + \frac{\sqrt{3}}{2} \cdot v_b(t) - \frac{\sqrt{3}}{2} \cdot v_c(t) \right)$

$V_0(t) := \sqrt{\frac{2}{3}} \cdot \left(\sqrt{\frac{1}{2}} \cdot v_a(t) + \sqrt{\frac{1}{2}} \cdot v_b(t) + \sqrt{\frac{1}{2}} \cdot v_c(t) \right)$

$MagV := \sqrt{(V_\alpha(5ms))^2 + (V_\beta(5ms))^2} = 173.205 V$

$I_\alpha(t) := \sqrt{\frac{2}{3}} \cdot \left(i_a(t) - \frac{1}{2} \cdot i_b(t) - \frac{1}{2} \cdot i_c(t) \right)$


$I_\beta(t) := \sqrt{\frac{2}{3}} \cdot \left(0 \cdot i_a(t) + \frac{\sqrt{3}}{2} \cdot i_b(t) - \frac{\sqrt{3}}{2} \cdot i_c(t) \right)$

$I_0(t) := \sqrt{\frac{2}{3}} \cdot \left(\sqrt{\frac{1}{2}} \cdot i_a(t) + \sqrt{\frac{1}{2}} \cdot i_b(t) + \sqrt{\frac{1}{2}} \cdot i_c(t) \right)$


$MagI := \sqrt{(I_\alpha(5ms))^2 + (I_\beta(5ms))^2} = 17.321 A$

$P_{INV} := MagI \cdot MagV = 3kW$ The computed averaged power is correct

Instantaneous $\alpha\beta$ currents

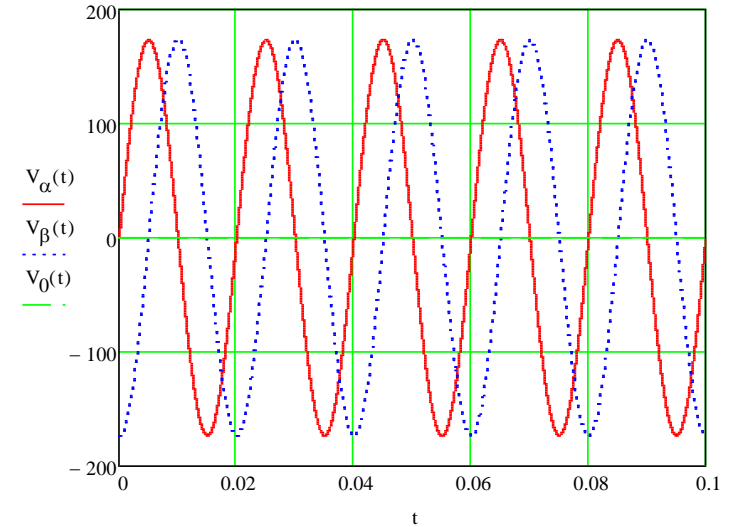

Instantaneous $\alpha\beta$ voltages

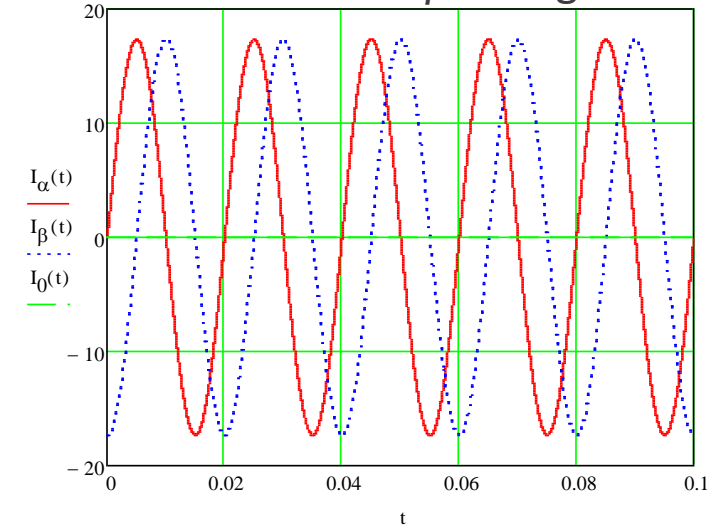


Agenda

- Symmetrical Components
- Clarke Transform
- **Park Transform**
- Power Processing
- Power Factor Correction


The Park Transformation

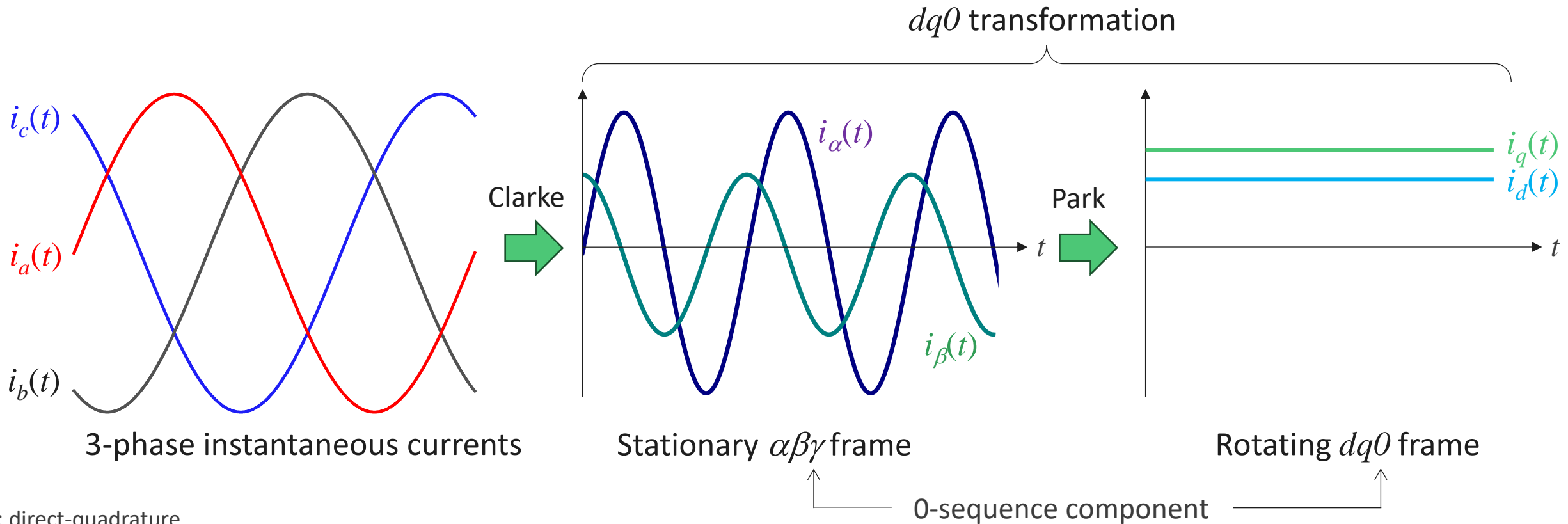- Clarke's transform turns a three-phase system into a two-phase reference frame
- ❖ The variables α and β are still fluctuating: building a control system is difficult
- ✓ Park's transform turns these two waveforms into two dc components, d and q
- Implementing a control system with dc references now becomes easier





Changing the Frame – $\alpha\beta$ to dq

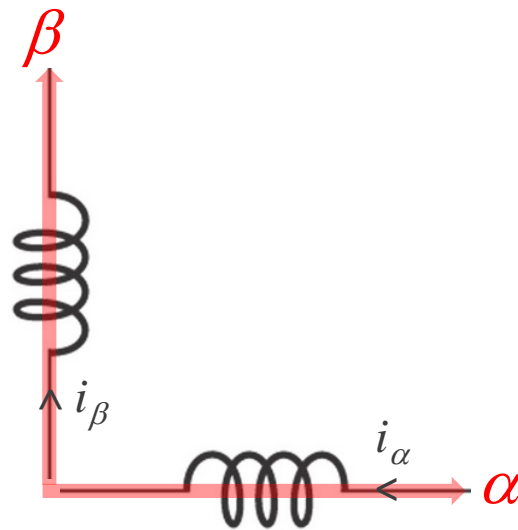- The $\alpha\beta$ frame is *stationary* and impractical for a control system
- Park's transform converts this *stationary* frame into a *rotating* frame
- ✓ The resulting dq values are dc signals representing active and reactive components



Stationary $\alpha\beta$ frame

Robert H. Park
1902-1994

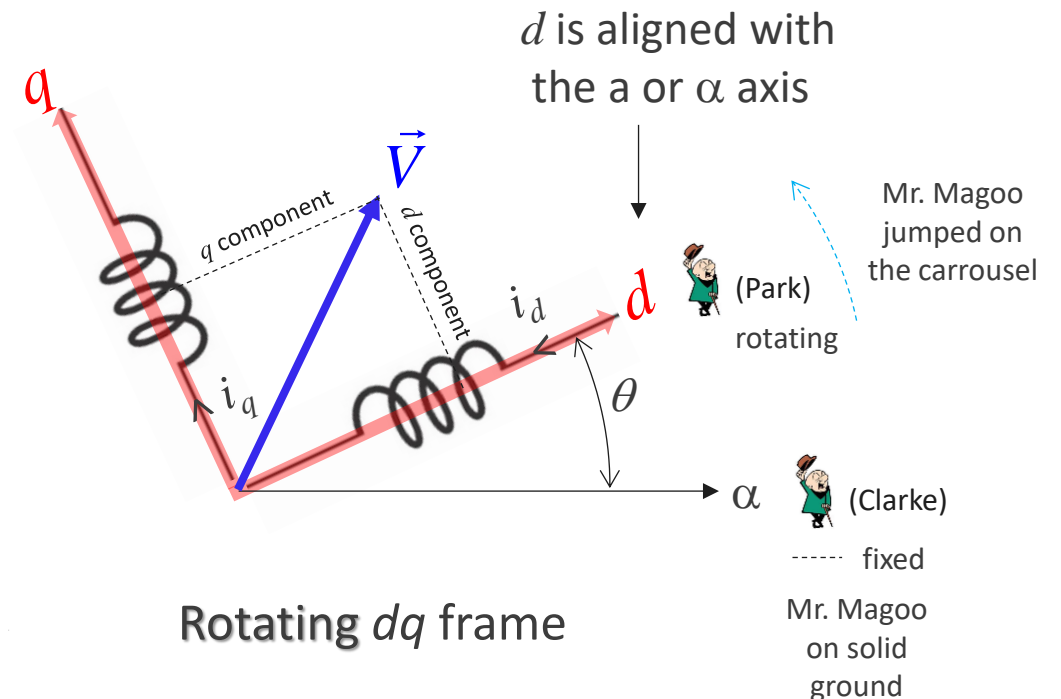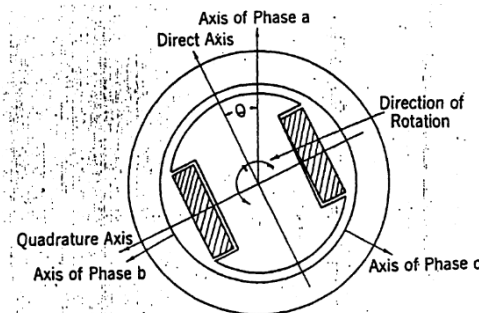


Rotating dq frame

Park's Transformation – a Simple Explanation

- Stationary reference frame phasor projected into a rotating reference frame
- Vector \mathbf{V} has the same magnitude but two different angles in $\alpha\beta$ and dq frames

$$\begin{aligned} \vec{V}_{\alpha\beta} &= |\vec{V}| \angle \varphi \\ \vec{V}_{dq} &= |\vec{V}| \angle \delta \end{aligned} \quad \Rightarrow \quad \begin{aligned} \vec{V}_{dq} &= |\vec{V}| \angle (\varphi - \theta) = |\vec{V}| \angle \varphi \cdot 1 \angle -\theta \\ \vec{V}_{dq} &= \vec{V}_{\alpha\beta} \cdot 1 \angle -\theta \rightarrow \vec{V}_{dq} = \vec{V}_{\alpha\beta} \cdot e^{-j\theta} \end{aligned} \quad e^{-j\theta} = \cos(-\theta) + j \sin(-\theta) = \cos(\theta) - j \sin(\theta)$$

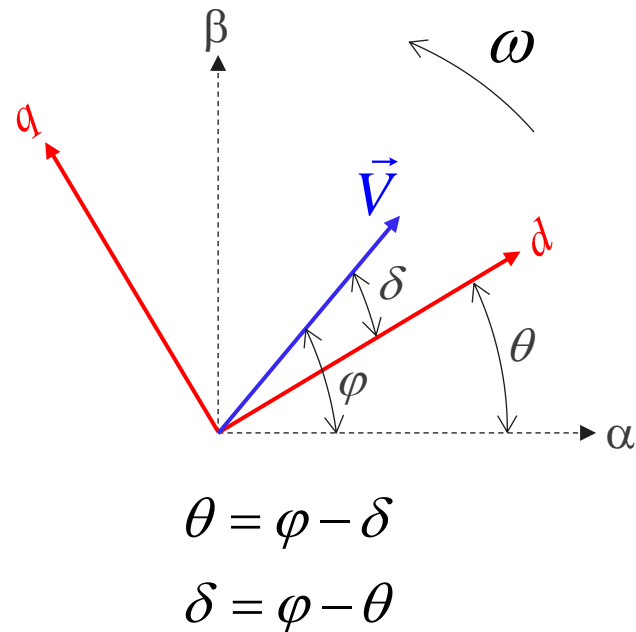

- d and q axes are linked by a 90° angle:

$$\begin{aligned} \cos\left(\theta + \frac{\pi}{2}\right) &= -\sin \theta \\ \sin\left(\theta + \frac{\pi}{2}\right) &= \cos \theta \end{aligned} \quad \Rightarrow \quad \begin{aligned} i_d &= i_\alpha \cos \theta + i_\beta \sin \theta \\ i_q &= -i_\alpha \sin \theta + i_\beta \cos \theta \end{aligned}$$

Park's transform

$$\begin{bmatrix} i_d \\ i_q \end{bmatrix} = \begin{bmatrix} \cos(\theta) & \sin(\theta) \\ -\sin(\theta) & \cos(\theta) \end{bmatrix} \begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix}$$

Inverse Park's transform


$$\begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix} = \begin{bmatrix} \cos(\theta) & -\sin(\theta) \\ \sin(\theta) & \cos(\theta) \end{bmatrix} \begin{bmatrix} i_d \\ i_q \end{bmatrix}$$

$$\theta = \omega t = 2\pi \cdot F_{line} \cdot t$$


↑
You need this instantaneous angle

dq0 Transformation

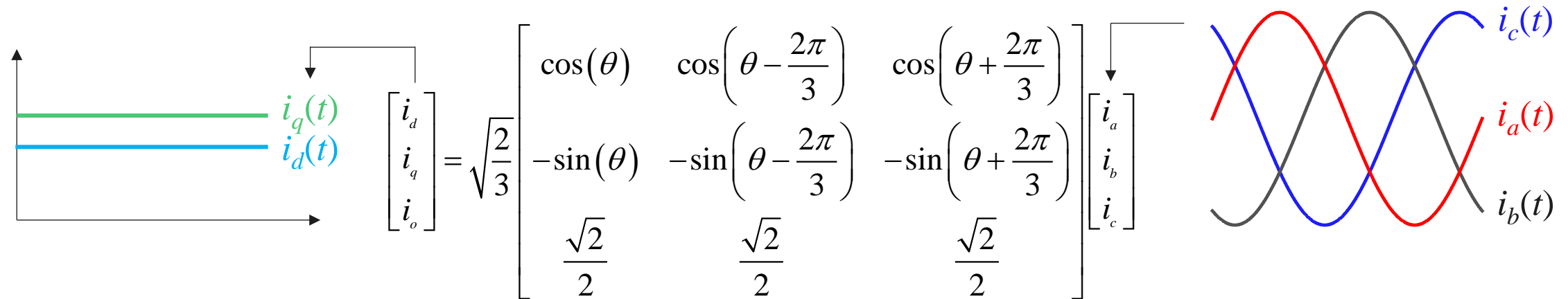- This *power invariant* transformation combines Clarke and Park transforms
- It directly converts the 3-phase signals into dc *d* and *q* variables




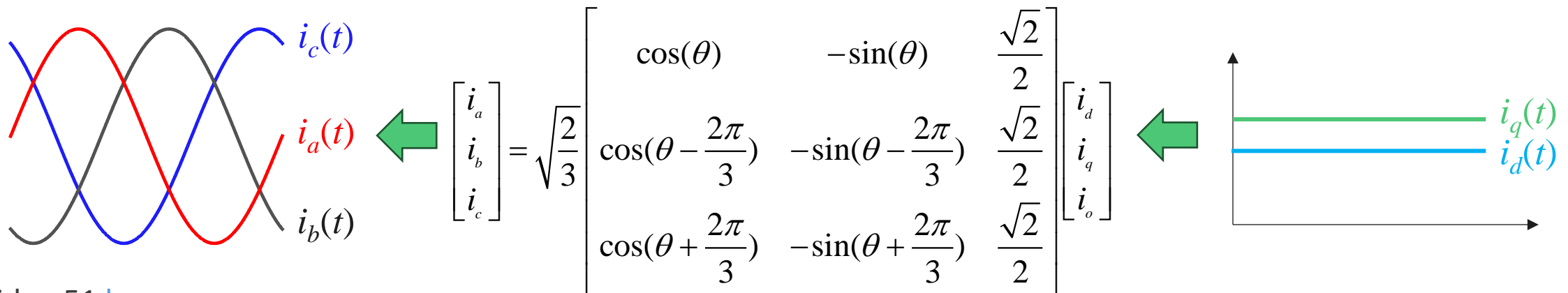✓ The inverse *dq0* reconstructs the corrected waveforms after corrected *d* and *q* variables




Stator and Rotor Fields

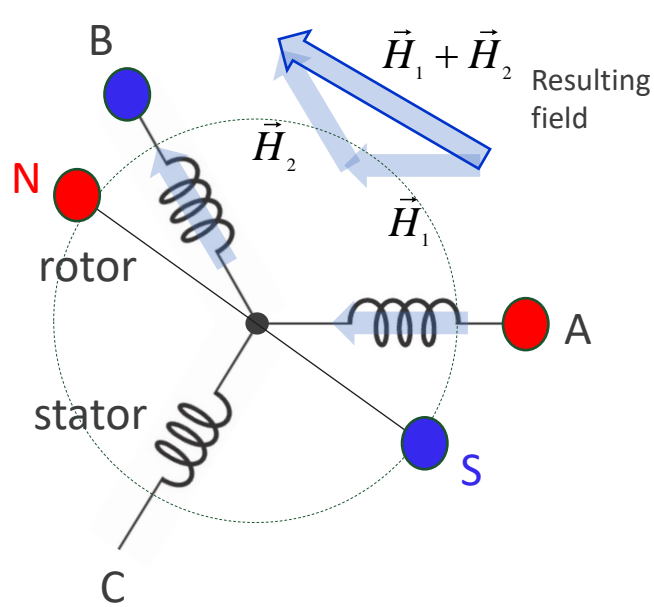- In a brushless dc motor (BLDC), you have stator and rotor fields
- The rotor field is imposed by magnets in a one pole-pair configuration
- The stator field will be controlled by biasing the three windings



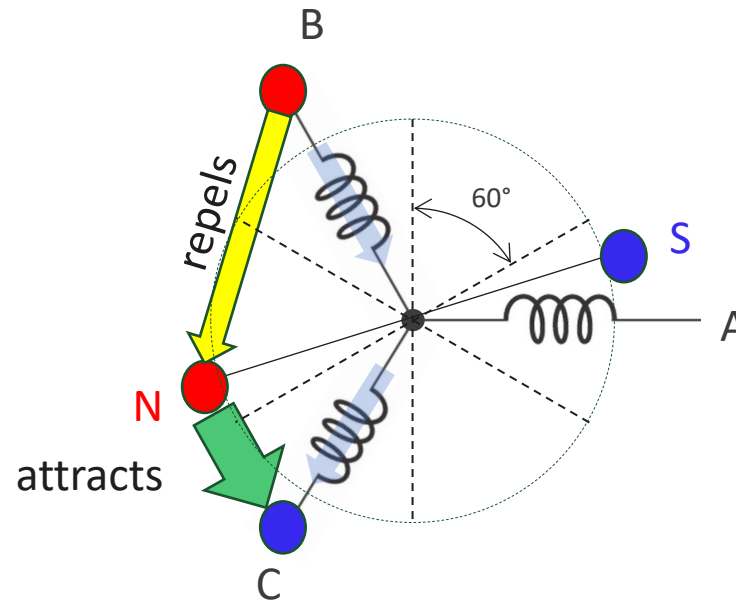
The rotor aligns with the stator field
The torque in this mode is equal to 0



You can energize a stator coil pair in 6 ways
6 possible rotor alignments – 60° apart

➔ 6-step commutation
or **trapezoidal control**

Picture from this [article](#)

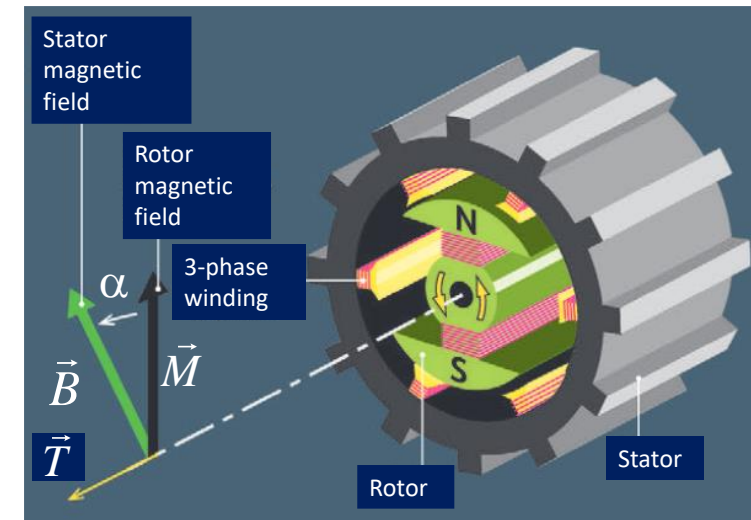


Torque is maximum when $\alpha = 90^\circ$

$$\vec{T} = \vec{M} \wedge \vec{B}$$


$$\|\vec{T}\| = \|\vec{M}\| \cdot \|\vec{B}\| \cdot \sin(\alpha)$$

The Need for Orthogonal Quantities

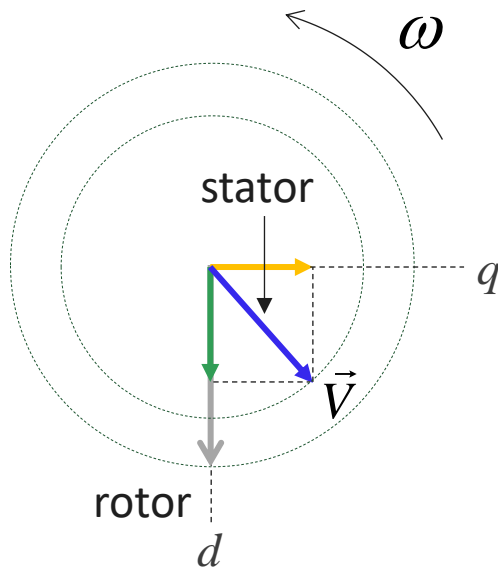
- We want to impose an orthogonal field between the stator and rotor fields
- The stator field is expressed in d and q components via Clarke's and Park's transforms
- ✓ Set d to zero and maximize the q component for orthogonal fields



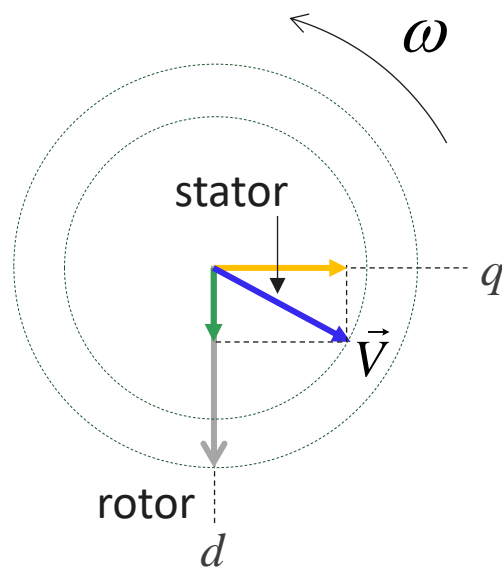The rotor field and the stator field are not orthogonal



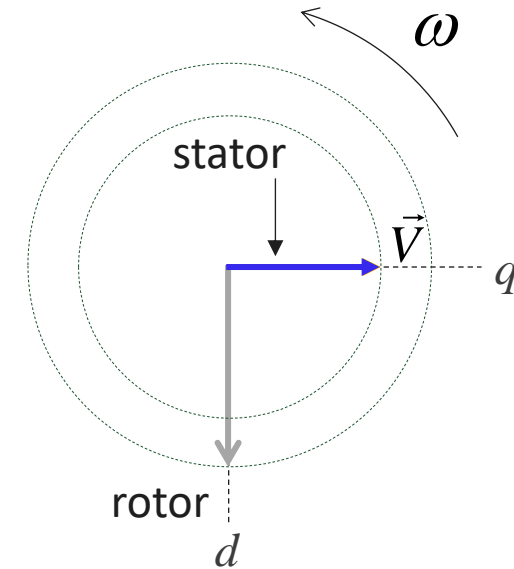
By reducing the d component, the q component grows



When the d component is zeroed, the stator field is orthogonal to the rotor field.

A Practical Implementation

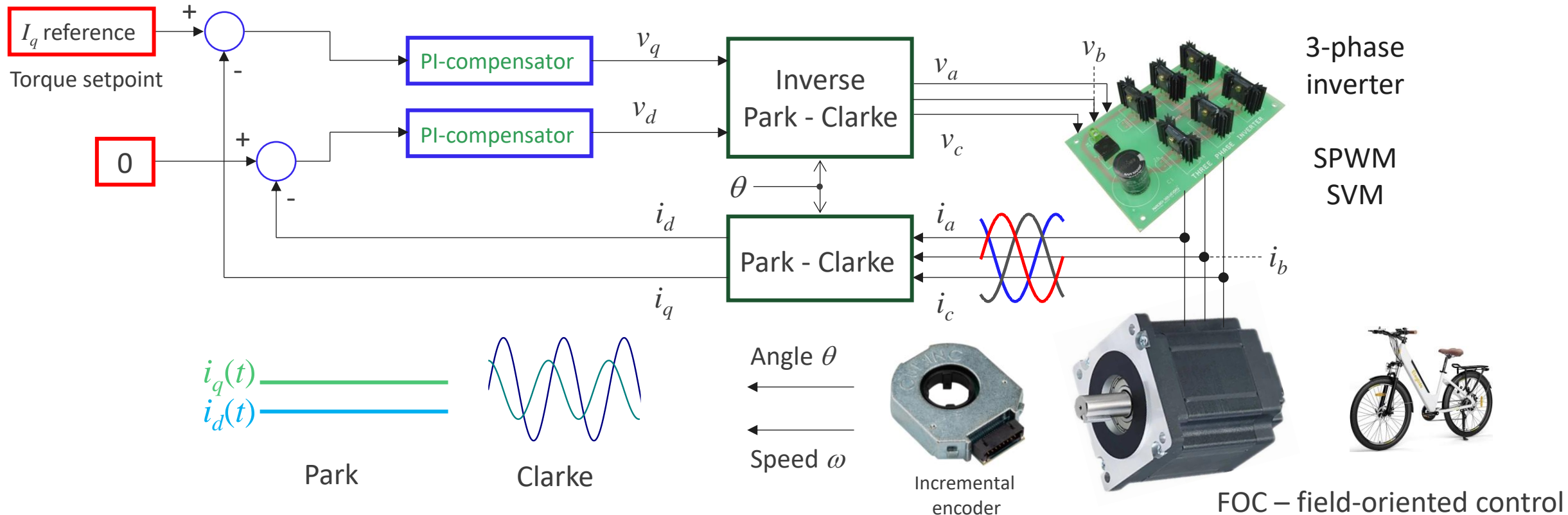- A permanent magnet synchronous motor (PMSM) can be controlled by FOC
- Currents in phases are adjusted by the inverter to control the motor torque
- ✓ A control system zeroes the d components while the q input sets a reference value



Agenda

- Symmetrical Components
- Clarke Transform
- Park Transform
- **Power Processing**
- Power Factor Correction

Power Processing

- We have seen how the Clarke/Park's transforms are used in motor control
- The $dq0$ transform directly leads to d and q components


$$\begin{aligned}
 v_d &= \sqrt{\frac{2}{3}} \left[v_a \cos(\theta) + v_b \cos\left(\theta - \frac{2\pi}{3}\right) + v_c \cos\left(\theta + \frac{2\pi}{3}\right) \right] & i_d &= \sqrt{\frac{2}{3}} \left[i_a \cos(\theta) + i_b \cos\left(\theta - \frac{2\pi}{3}\right) + i_c \cos\left(\theta + \frac{2\pi}{3}\right) \right] \\
 v_q &= \sqrt{\frac{2}{3}} \left[-v_a \sin(\theta) - v_b \sin\left(\theta - \frac{2\pi}{3}\right) - v_c \sin\left(\theta + \frac{2\pi}{3}\right) \right] & i_q &= \sqrt{\frac{2}{3}} \left[-i_a \sin(\theta) - i_b \sin\left(\theta - \frac{2\pi}{3}\right) - i_c \sin\left(\theta + \frac{2\pi}{3}\right) \right] \\
 v_0 &= \sqrt{\frac{1}{6}} [v_a + v_b + v_c] & i_0 &= \sqrt{\frac{1}{6}} [i_a + i_b + i_c]
 \end{aligned}$$

- Average [W] and reactive [VAR] powers can be computed:

$$P = v_d i_d + v_q i_q + v_0 i_0 \quad [\text{W}]$$

$$Q = v_q i_d - v_d i_q \quad [\text{VAR}]$$

$$S = P + jQ \quad [\text{VA}]$$

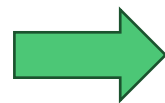

In a PFC system:

- ✓ The loop sets i_d to keep V_{out} constant
- ✓ i_q is set to 0

Computing the Angle

- For processing the d and q parameters, you need the θ angle
- It can be obtained by processing the individual phase voltages

Phase expressions

$$v_a(t) = V_{in} \sqrt{2} \sin(\omega t) \quad v_c(t) - v_b(t) = V_{in} \sqrt{2} \left[\sin\left(\omega t - \frac{4\pi}{3}\right) - \sin\left(\omega t - \frac{2\pi}{3}\right) \right]$$

$$v_b(t) = V_{in} \sqrt{2} \left(\omega t - \frac{2\pi}{3} \right) \quad v_c(t) - v_b(t) = V_{in} \sqrt{6} \cos(\omega t)$$

$$v_c(t) = V_{in} \sqrt{2} \left(\omega t - \frac{4\pi}{3} \right) \quad v_c(t) + v_b(t) = V_{in} \sqrt{2} \left[\sin\left(\omega t - \frac{4\pi}{3}\right) + \sin\left(\omega t - \frac{2\pi}{3}\right) \right]$$


$$v_c(t) + v_b(t) = -V_{in} \sqrt{2} \sin(\omega t)$$

$$\theta(t) = -\tan^{-1} \left(\frac{\sqrt{3} [v_c(t) + v_b(t)]}{v_c(t) - v_b(t)} \right)$$


- The practical implementation can be done this way, involving $v_a(t)$:

$$\theta(t) = -\tan^{-1} \left(-\frac{1}{\sqrt{3}} \frac{v_a(t) - 2v_b(t) - 2v_c(t)}{[v_b(t) - v_c(t)]} \right)$$
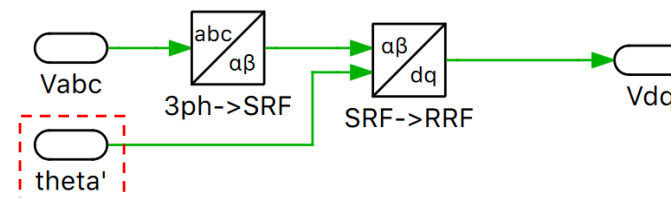
$$\frac{-\operatorname{atan2}[(v_c(t) - v_b(t)), \sqrt{3} \cdot (v_c(t) + v_b(t))]}{\operatorname{atan2}\left[-\frac{\sqrt{3}}{3} \cdot (v_b(t) - v_c(t)), \frac{(v_a(t) - 2 \cdot v_b(t) - 2 \cdot v_c(t))}{3}\right]}$$




PLECS $dq0$ block needs θ

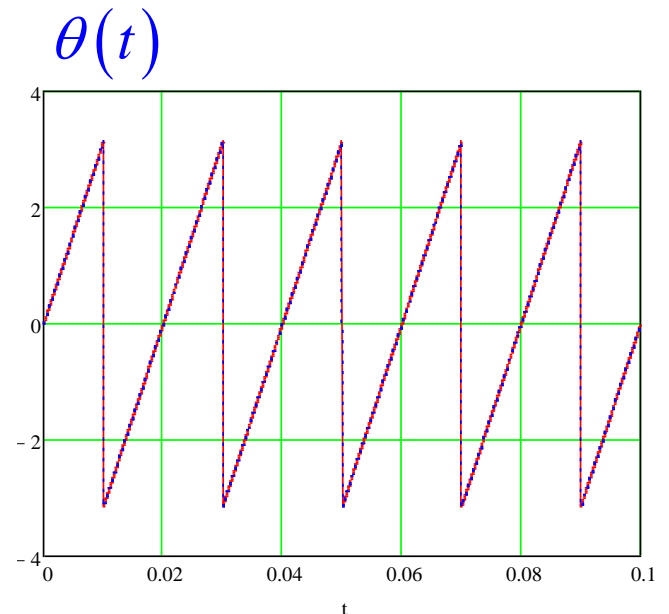


Balanced System – no Reactive Power

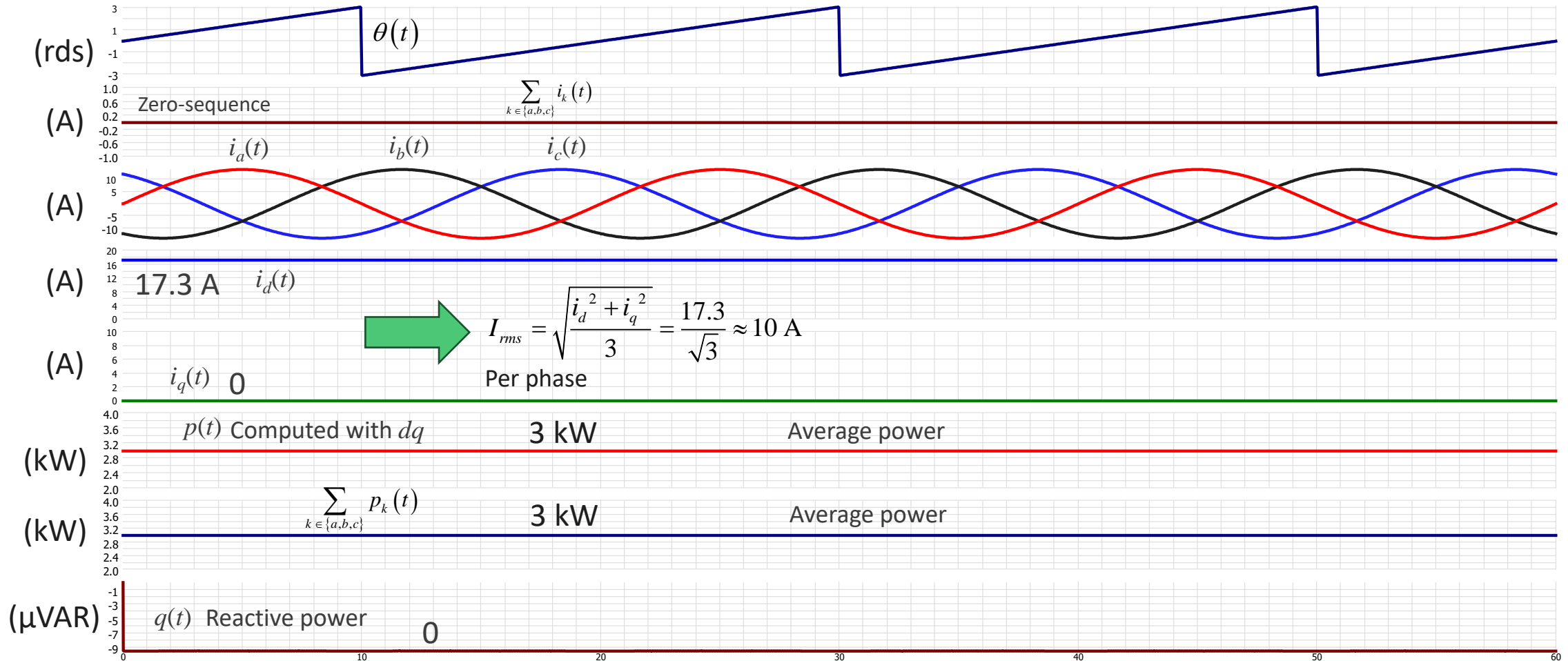- 3-phase 100-V rms feeds 10-ohm loads, no capacitive component $I_{rms} = \sqrt{\frac{P_{tot}}{3R_L}} = 10 \text{ A}$



Balanced System – Reactive Power

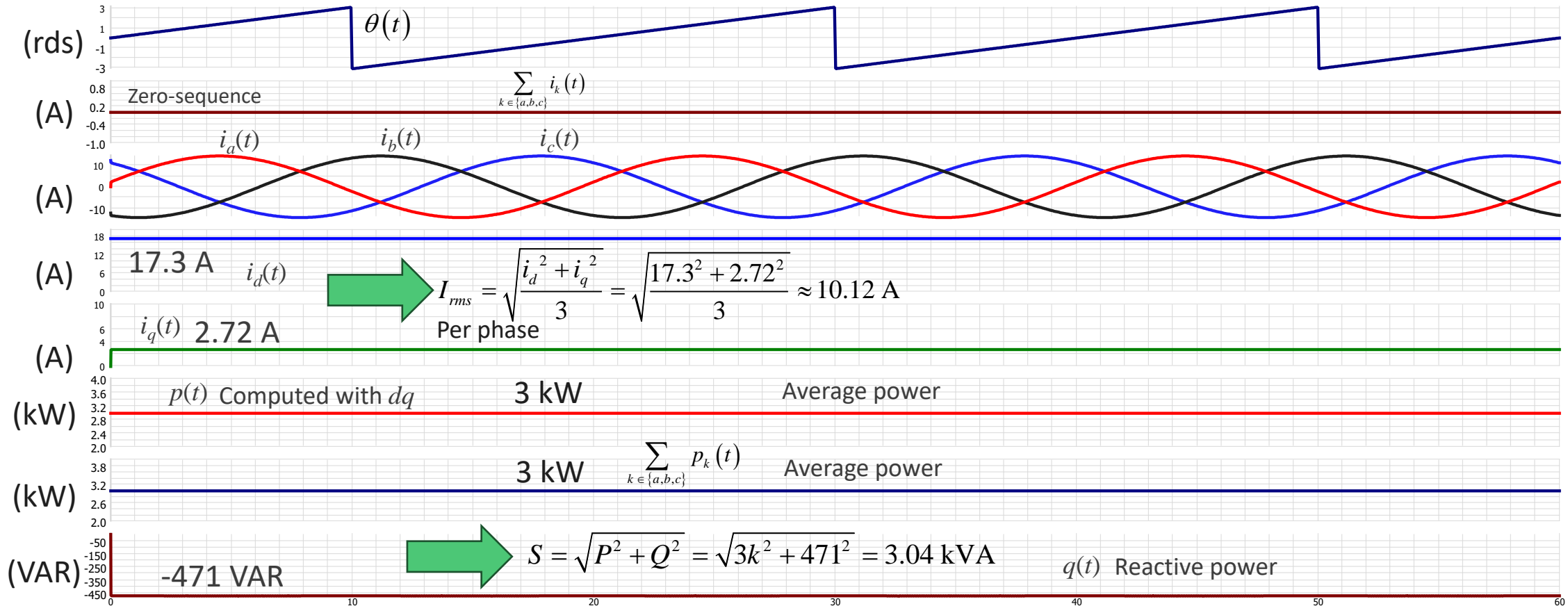- 3-phase 100-V rms feeds 10-ohm loads with 50-μF capacitors in parallel




Agenda

- Symmetrical Components
- Clarke Transform
- Park Transform
- Power Processing
- Power Factor Correction


3-Phase Boost Rectifier with SPWM

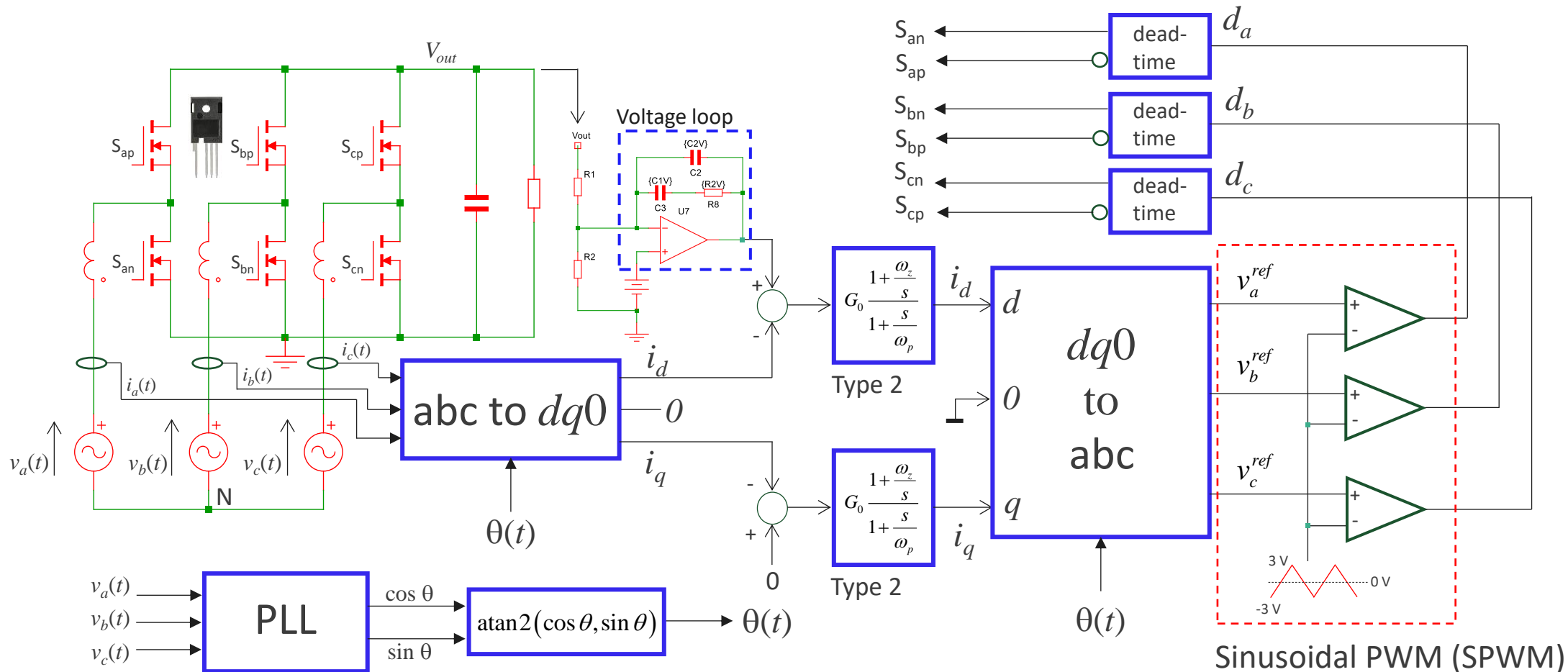- A phase-locked loop (PLL) is used for extracting the angle θ
- Each input current is sensed and used to compute $dq0$ variables with θ





Building Subcircuits Blocks

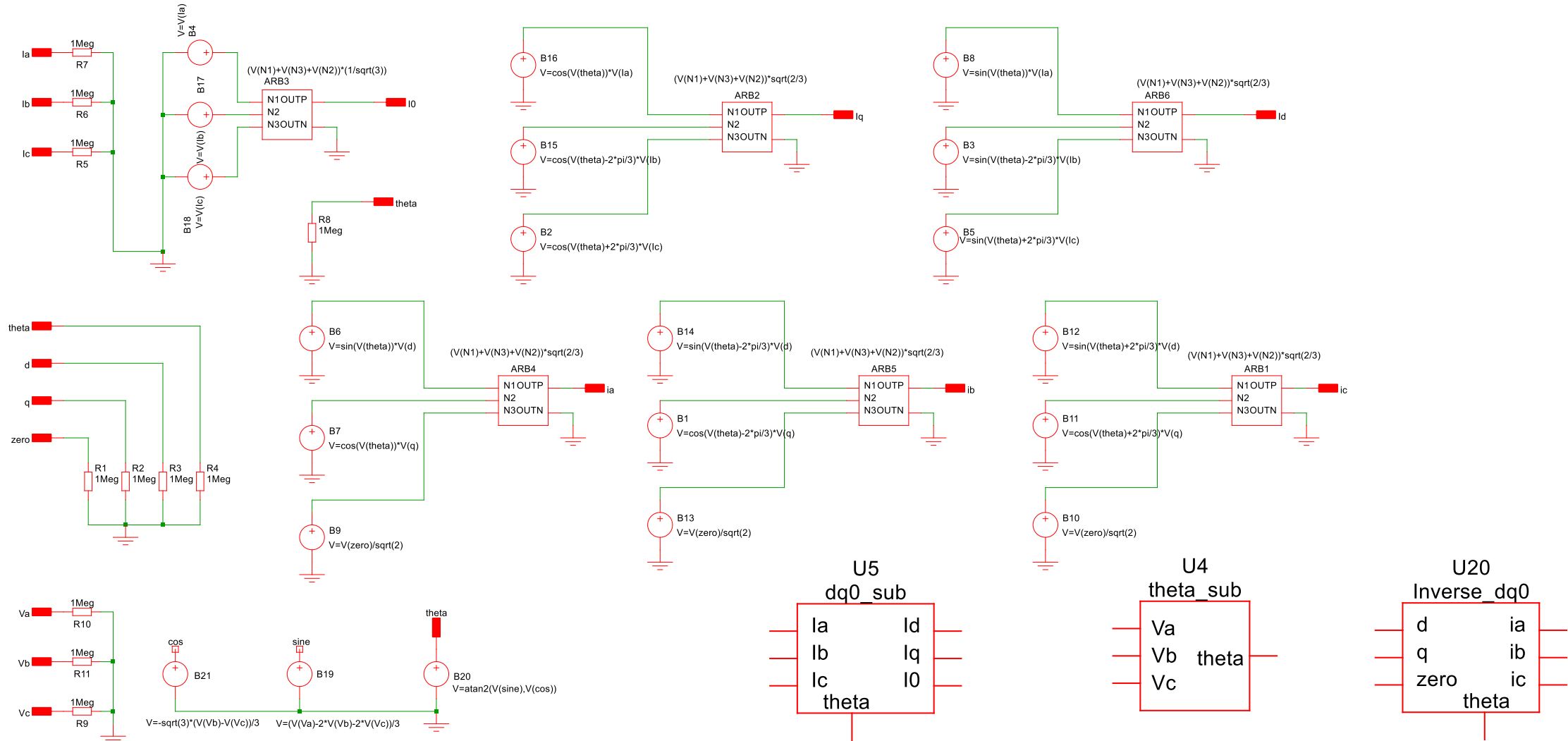- Computing blocks are created in SIMetrix® and encapsulated




Testing Subcircuits

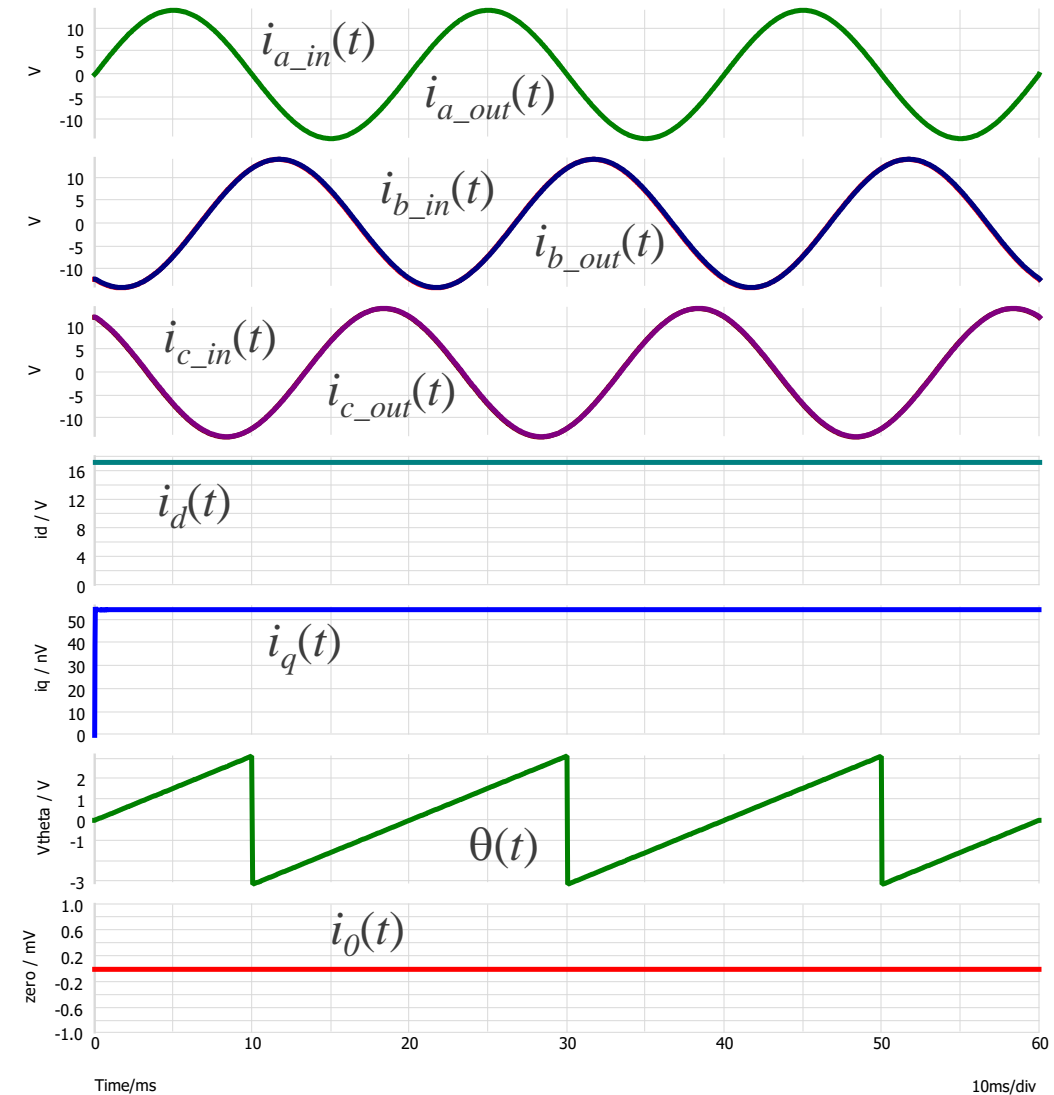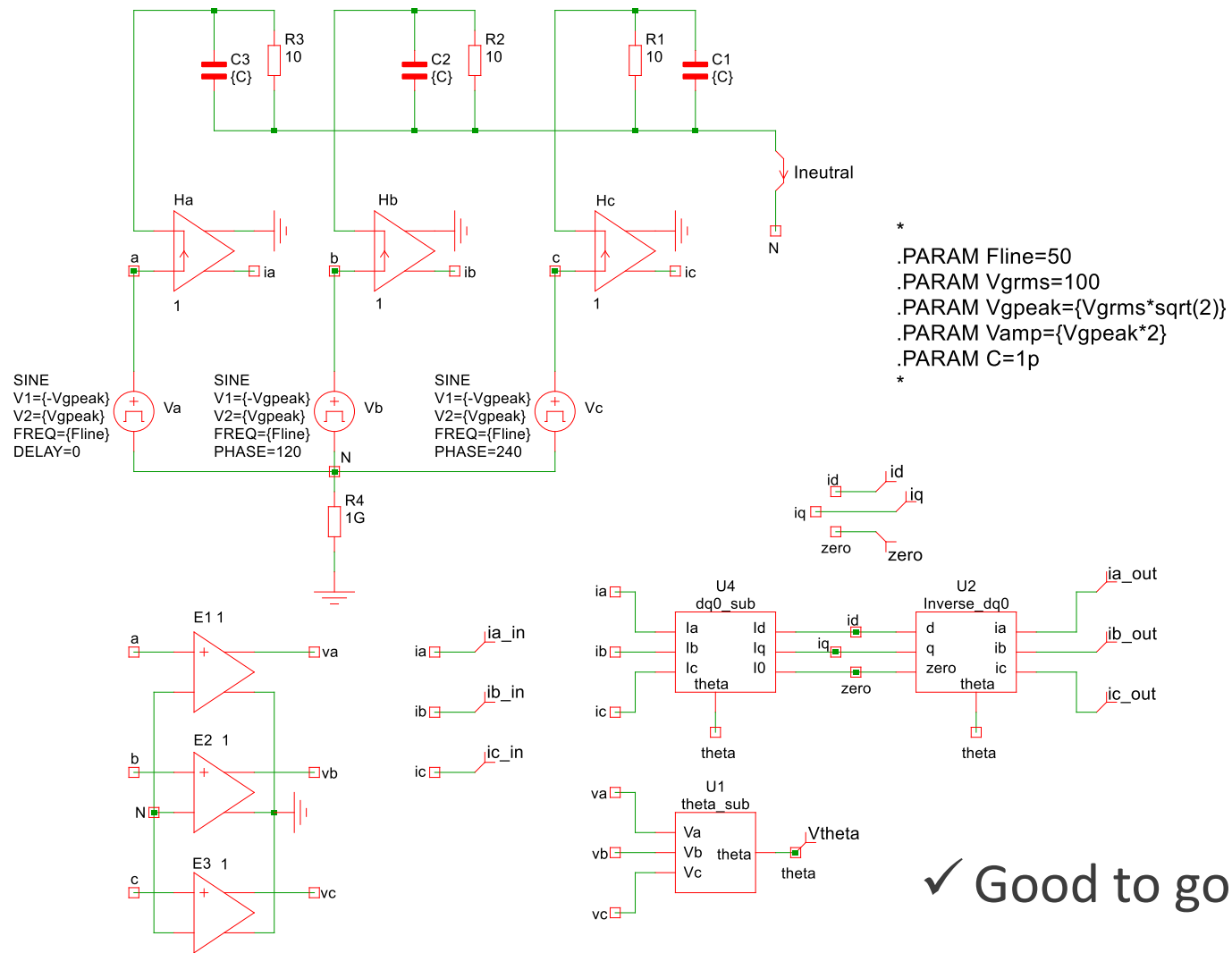- Before operating the blocks in a 3-phase circuit, verify the computed results




✓ Good to go!

The Complete Simulation

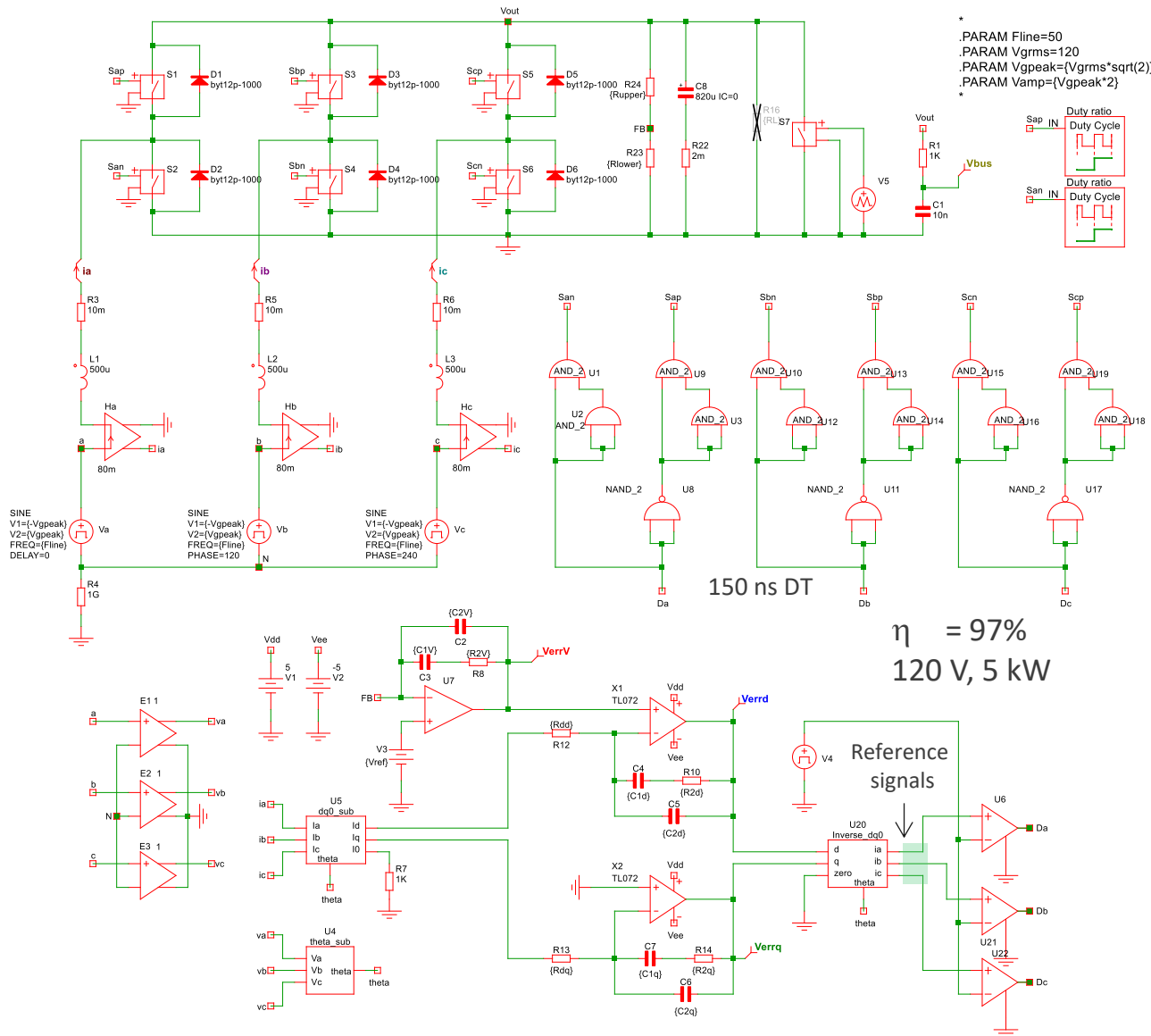

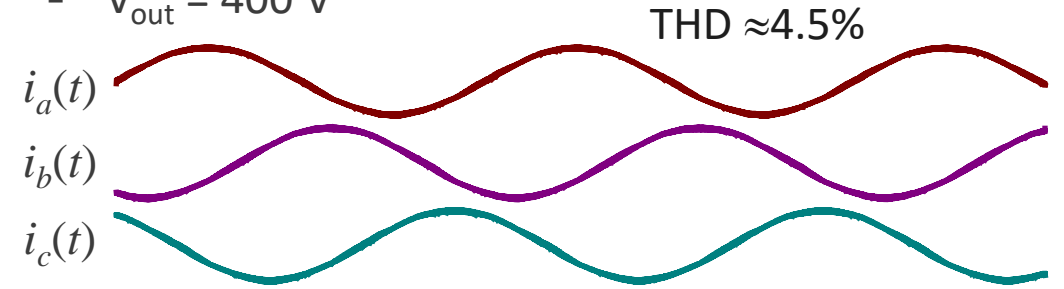- There are three compensators in this circuit
- The voltage loop is compensated for a low crossover
- The inner current loops are faster $\approx 1-2$ kHz
- The converter delivers 5 kW from a 120-V ac input
- $V_{out} = 400$ V



150 ns DT
 $\eta = 97\%$
120 V, 5 kW

```
.param GfcV=20 ; magnitude at crossover *
.param PSV=-90 ; phase lag at crossover *
*
* Enter Design Goals Information Here *
*
.param fcV=20 ; targeted crossover *
.param PMV=60 ; choose phase margin at crossover *
*
* Enter the Values for Vout and Bridge Bias Current *
*
.param Vout=400
.param Pout=5k
.param RL={(Vout)^2/(Pout)}
.param Ibias=100u
.param Vref=2.5
.param Rlower={Vref/Ibias}
.param Rupper={(Vout-Vref)/Ibias}
```




```
*
* Do not edit the below lines *
.param boostV={PMd-PSd-90}
.param GV={10^(-GfcV/20)}
.param kV={tan((boostV/2+45)*pi/180)}
.param fpV={fcV*kV}
.param fzV={fcV/kV}
.param
C2V={1/(2*pi*fcV*GV*kV*Rupper)}
.param C1V={C2V*(kV^2-1)}
.param R2V={kV/(C1V*2*pi*fcV)}
```

Type 2 voltage loop compensation

Simulation time for 200 ms: 5 mn

Switching Pattern at Steady State

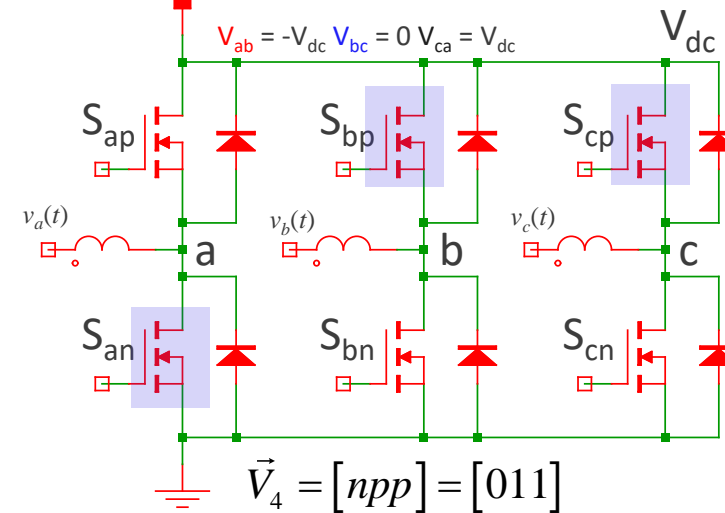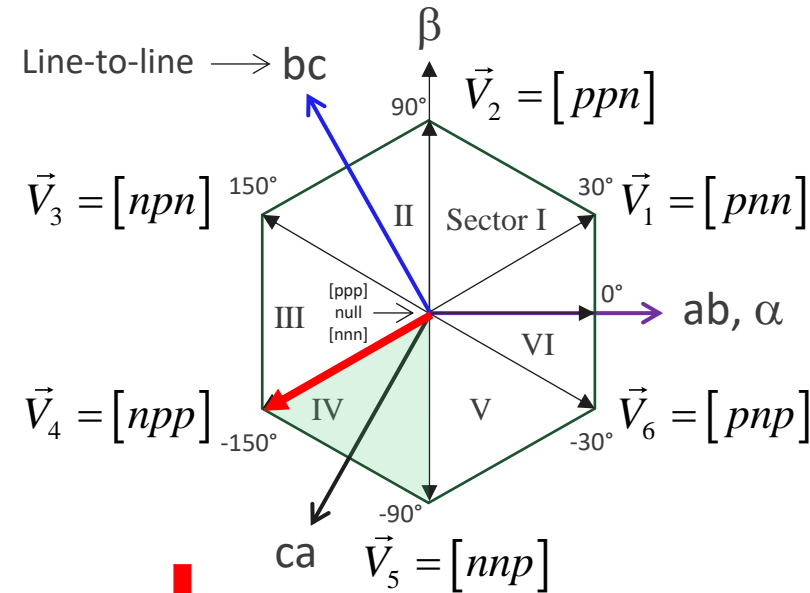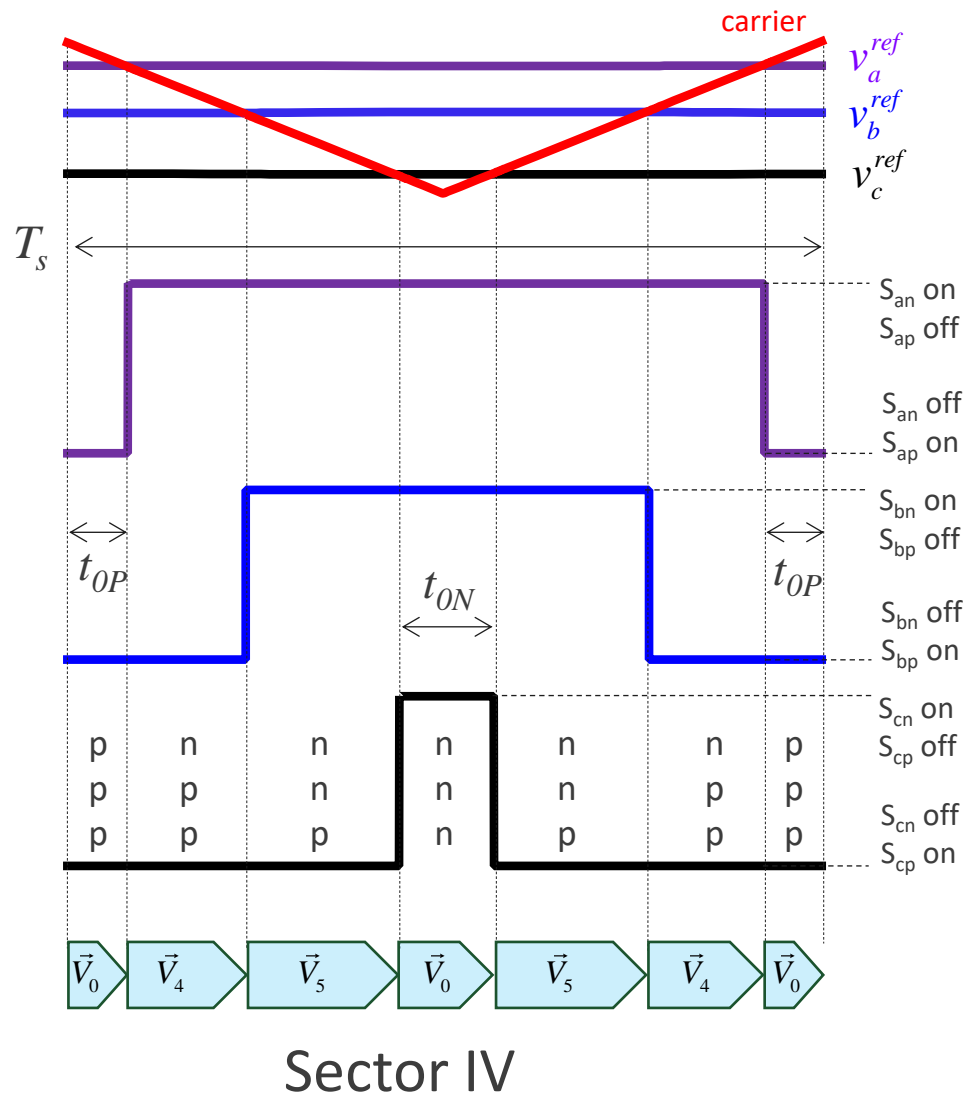- This is a symmetrical center-based three-phase modulation like SVM2



- The idea is to generate a vector \vec{V}_{ref} whose position and magnitude depends on adjacent vectors.
- Here, \vec{V}_{ref} is generated by weighting the time during which vectors \vec{V}_4 and \vec{V}_5 are active.
- The switch pattern in example shows the realization of vector \vec{V}_4 .


$$\vec{V}_{ref} = \rho \cdot e^{j\theta}$$

Space vector in $\alpha\beta$

$$\vec{V}_0 = [ppp] = [nnn]$$

Vectors Hexagon for Star or Delta Configuration

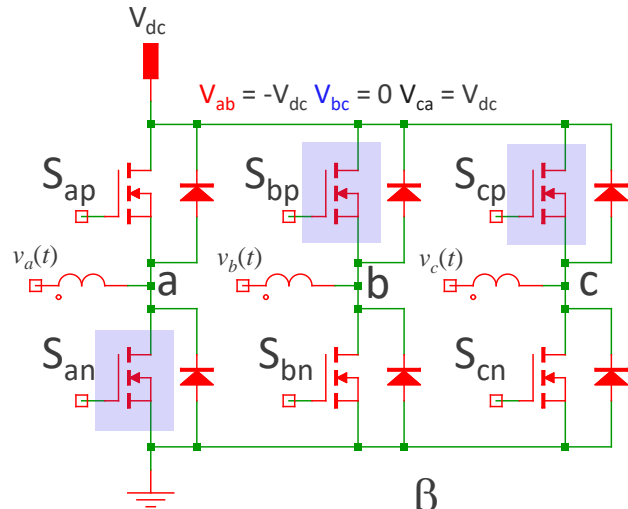- The hexagon represents the six possible vectors for a star or a delta configuration



$$V_{ab} = -V_{dc} \quad V_{bc} = 0 \quad V_{ca} = V_{dc}$$


$$\begin{aligned} V_{ab} &= -V_{dc} \\ V_{bc} &= 0 \\ V_{ca} &= V_{dc} \end{aligned}$$

Vector V_4 is synthesized in $\alpha\beta$




$$\sqrt{\frac{2}{3}} \begin{pmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \frac{\sqrt{3}}{2} & -\frac{\sqrt{3}}{2} \end{pmatrix} \begin{pmatrix} -V_{dc} \\ 0 \\ V_{dc} \end{pmatrix} \rightarrow \begin{pmatrix} \frac{\sqrt{2} \cdot \sqrt{3} \cdot V_{dc}}{2} \\ -\frac{\sqrt{2} \cdot V_{dc}}{2} \end{pmatrix} \rightarrow \begin{matrix} \alpha \\ \beta \end{matrix} \begin{pmatrix} -\frac{\sqrt{3}}{2} \cdot V_{dc} \\ -\frac{1}{\sqrt{2}} \cdot V_{dc} \end{pmatrix}$$
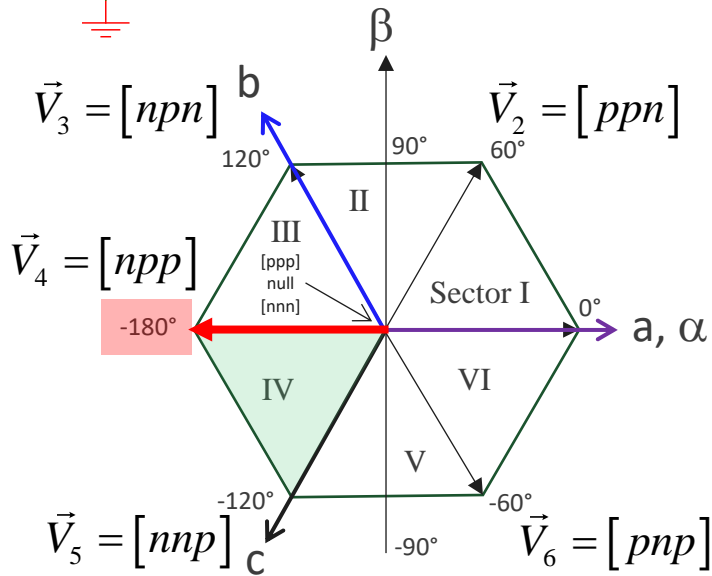
$$\rho = V_{dc} \cdot \sqrt{\left[-\left(\frac{\sqrt{3}}{2}\right)\right]^2 + \left[-\left(\frac{1}{\sqrt{2}}\right)\right]^2} = \sqrt{2} \cdot V_{dc} \quad \theta := \text{atan2}\left[-\frac{\sqrt{3}}{2}, -\left(\frac{1}{\sqrt{2}}\right)\right] = -150^\circ$$




Star configuration

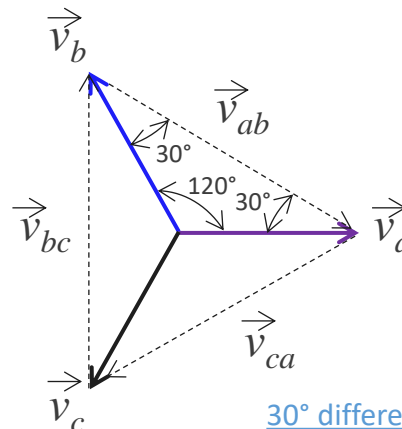- Accounting for the 30° phase difference between delta and star:



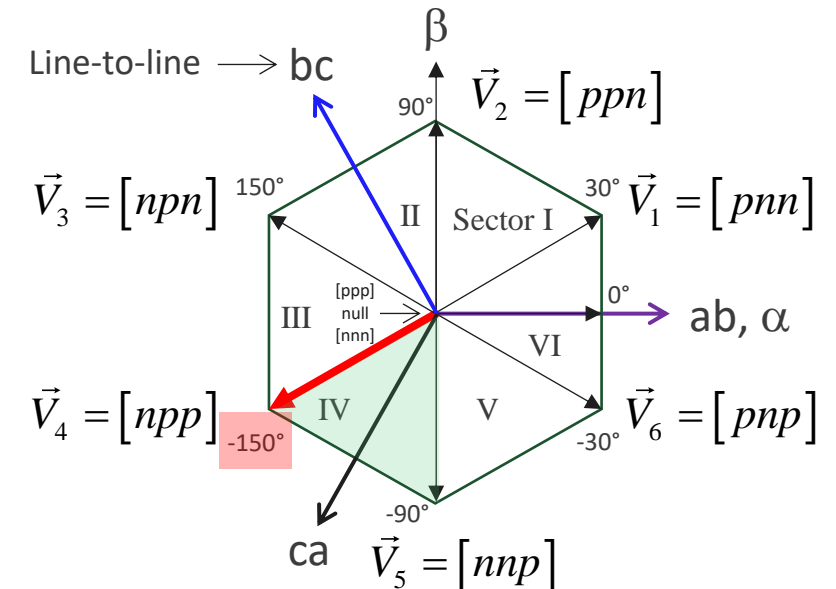
[30° difference in star delta systems](#)



Delta configuration

Synthetizing the Six Vectors

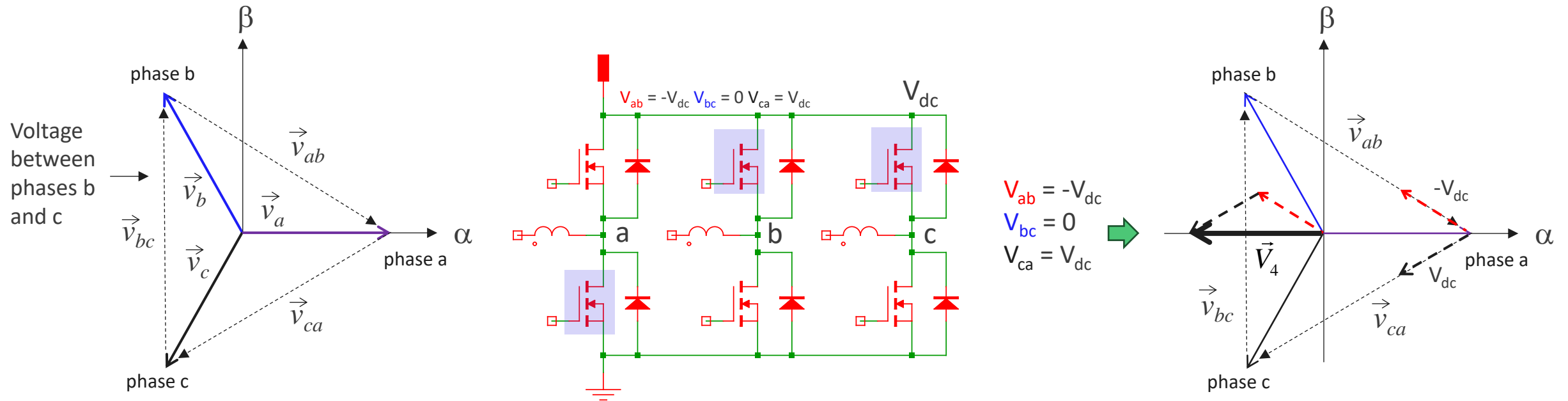
- We want to impose voltages between points a, b and c with the six switches
- \vec{v}_{ab} , \vec{v}_{bc} and \vec{v}_{ca} can take on one of the three values: $-V_{dc}$, 0 or V_{dc}
- ✓ you add or subtract these vectors to obtain the vector imposed by the switches



- Vector V_4 is created by summing the two vectors of $-V_{dc}$ and V_{dc} magnitudes

Averaging the Position



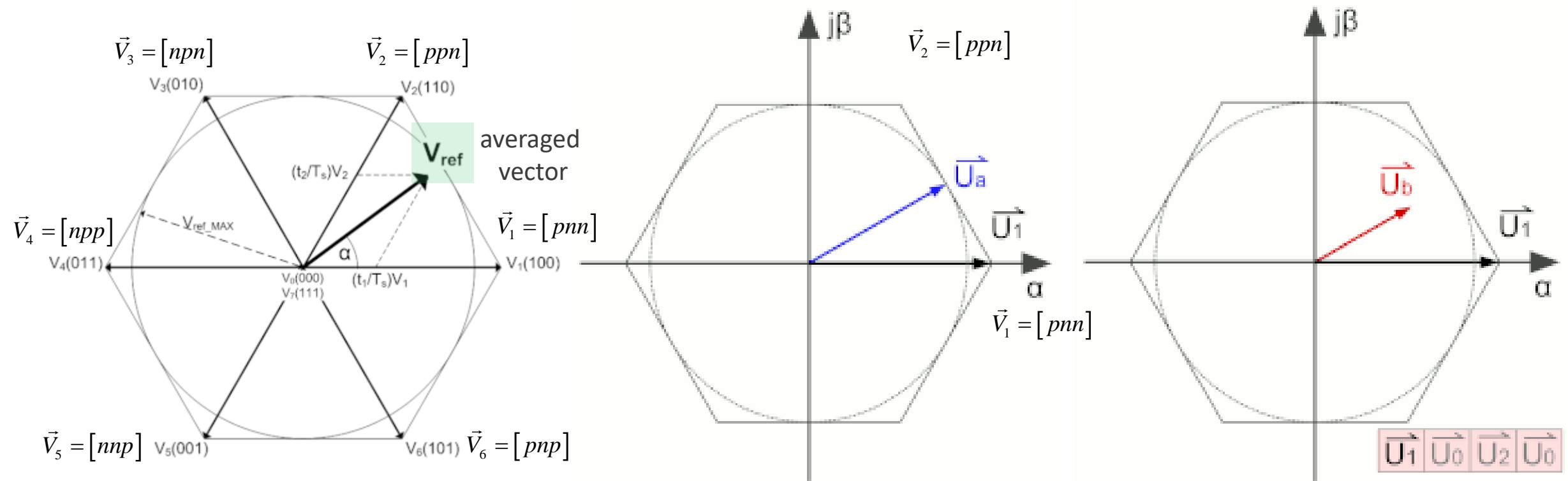
- The reference vector is created by alternating between the two adjacent vectors
- The magnitude is adjusted by inserting a deadtime with vectors 0: [000] or [111]



- Vector \vec{V}_{ref} is synthesized by selecting the adjacent vectors in the considered sector
- The angle is determined by the time duration of each vector in the sector
- The magnitude is adjusted by the insertion of a deadtime via \vec{V}_0


Dwell Times Calculations

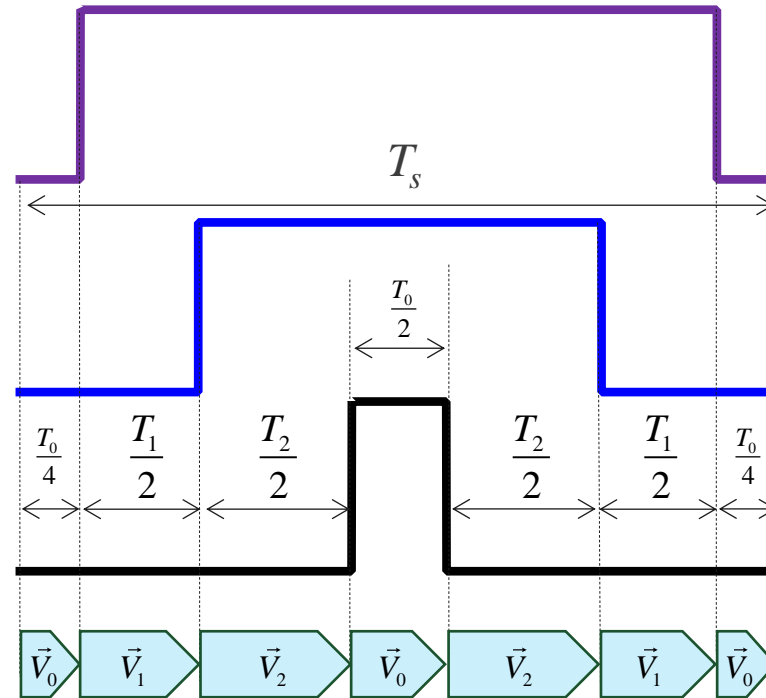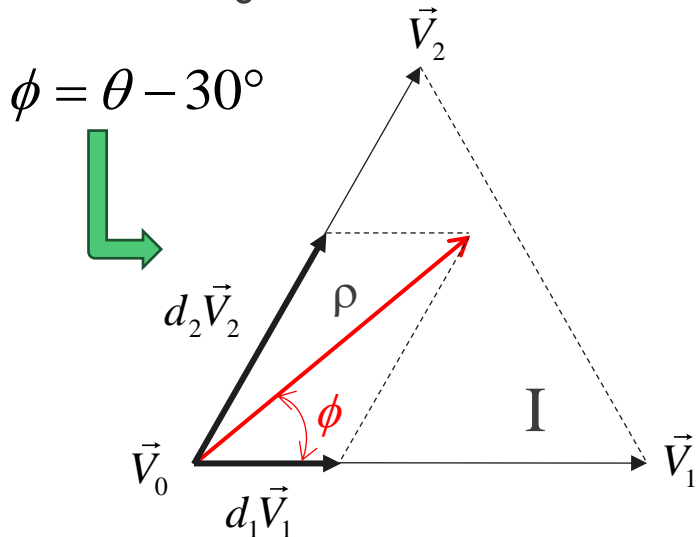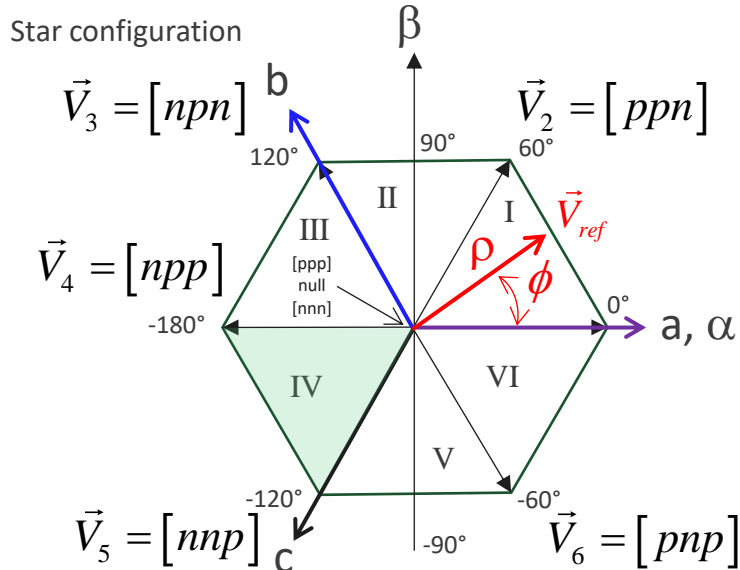- Determine switching pattern time duration for generating the reference vector



$$d_1 = \frac{T_1}{T_s} = \frac{\sqrt{3}}{V_{dc}} \|\vec{V}_{ref}\| \sin(60^\circ - \phi)$$

$$d_2 = \frac{T_2}{T_s} = \frac{\sqrt{3}}{V_{dc}} \|\vec{V}_{ref}\| \sin(\phi)$$

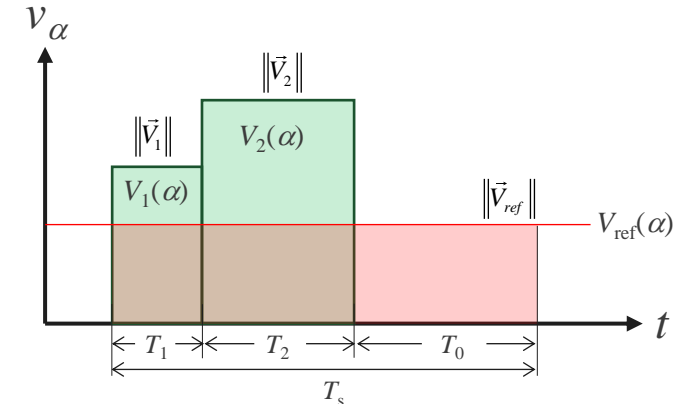

$$\int_0^{T_s} \vec{V}_{ref} dt = \int_0^{T_1} \vec{V}_1 dt + \int_{T_1}^{T_1+T_2} \vec{V}_2 dt + \int_{T_1+T_2}^{T_s} \vec{V}_0 dt$$


$$\|\vec{V}_{ref}\| T_s = \|\vec{V}_1\| T_1 + \|\vec{V}_2\| T_2 + \|\vec{V}_0\| T_0$$

$$T_s = T_1 + T_2 + T_0 \rightarrow 1 = d_1 + d_2 + d_0$$


- \vec{V}_{ref} is synthesized in the $\alpha\beta$ frame and will then be converted in variable setpoints v_a , v_b and v_c

3-Phase Boost Rectifier with SVM

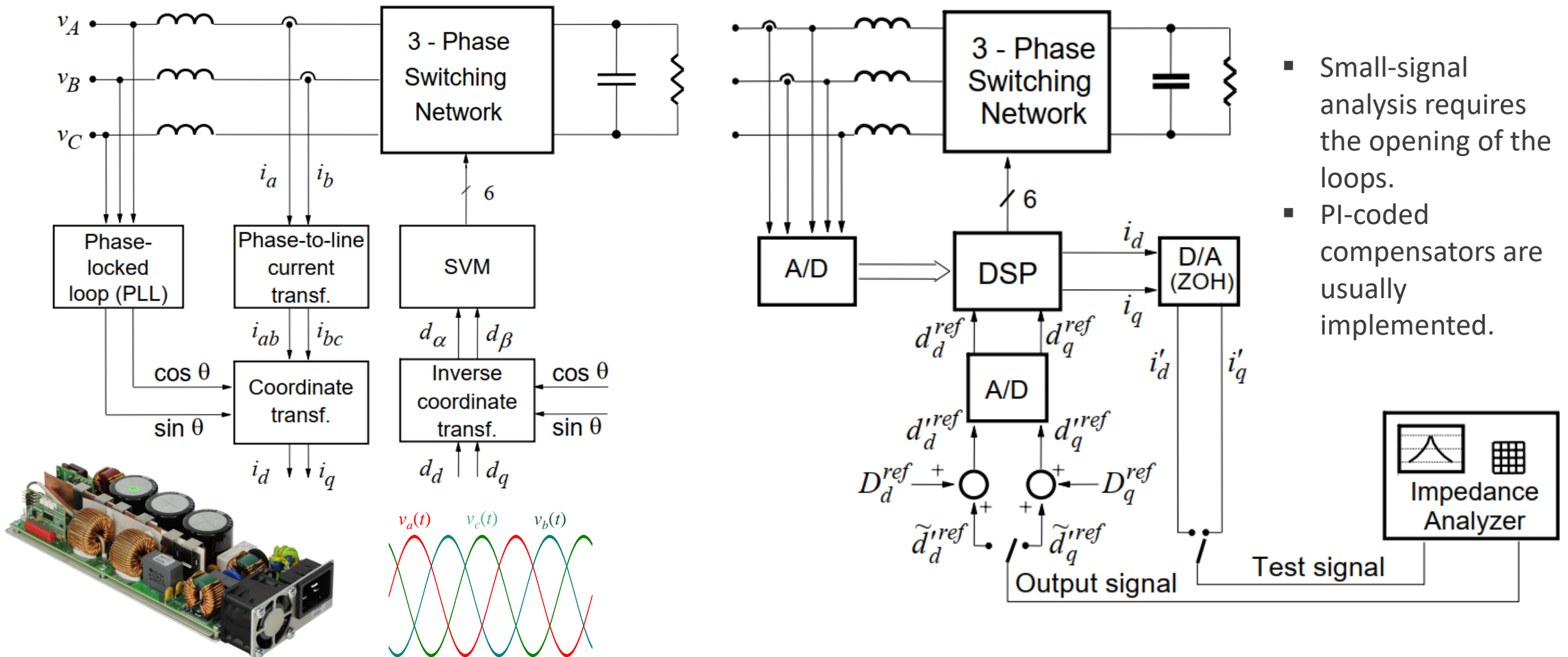- In this example, dq references are transformed into $\alpha\beta$ coordinates before SVM





Transient Response of the SPWM Rectifier

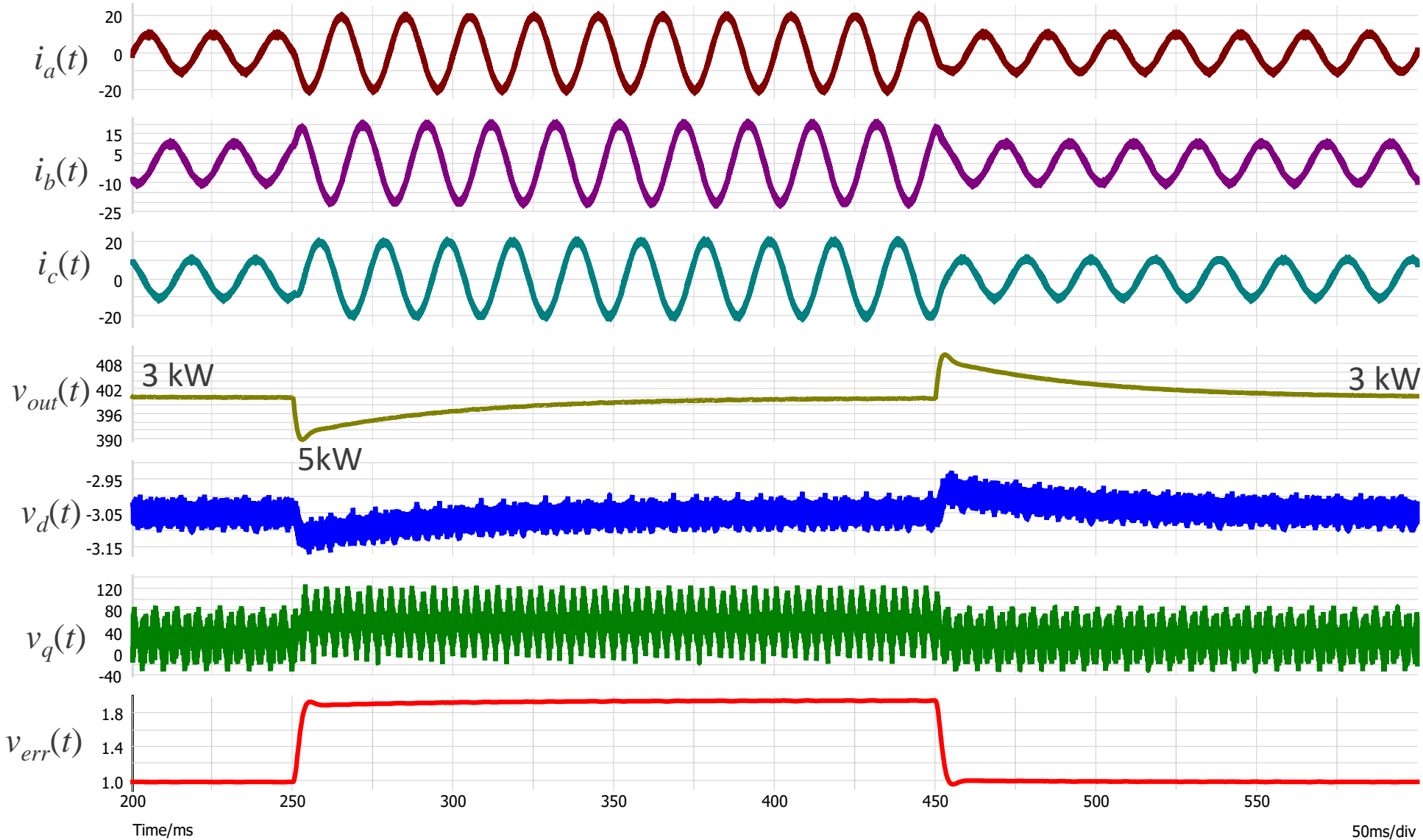

- The power is stepped from 3 kW to 5 kW in a few μ s
- The response is good and does not show oscillations
- The d and q compensated signals react quickly

Average Model of the 3-Phase PFC

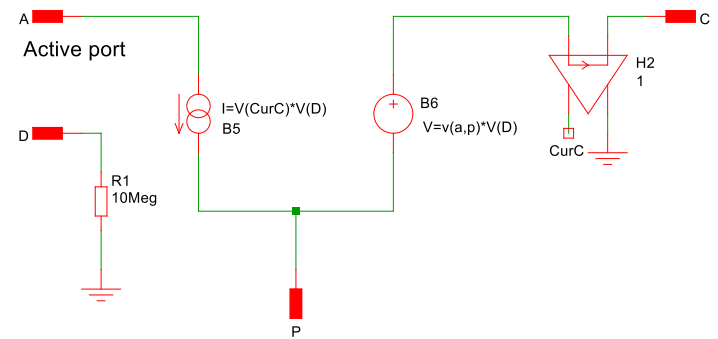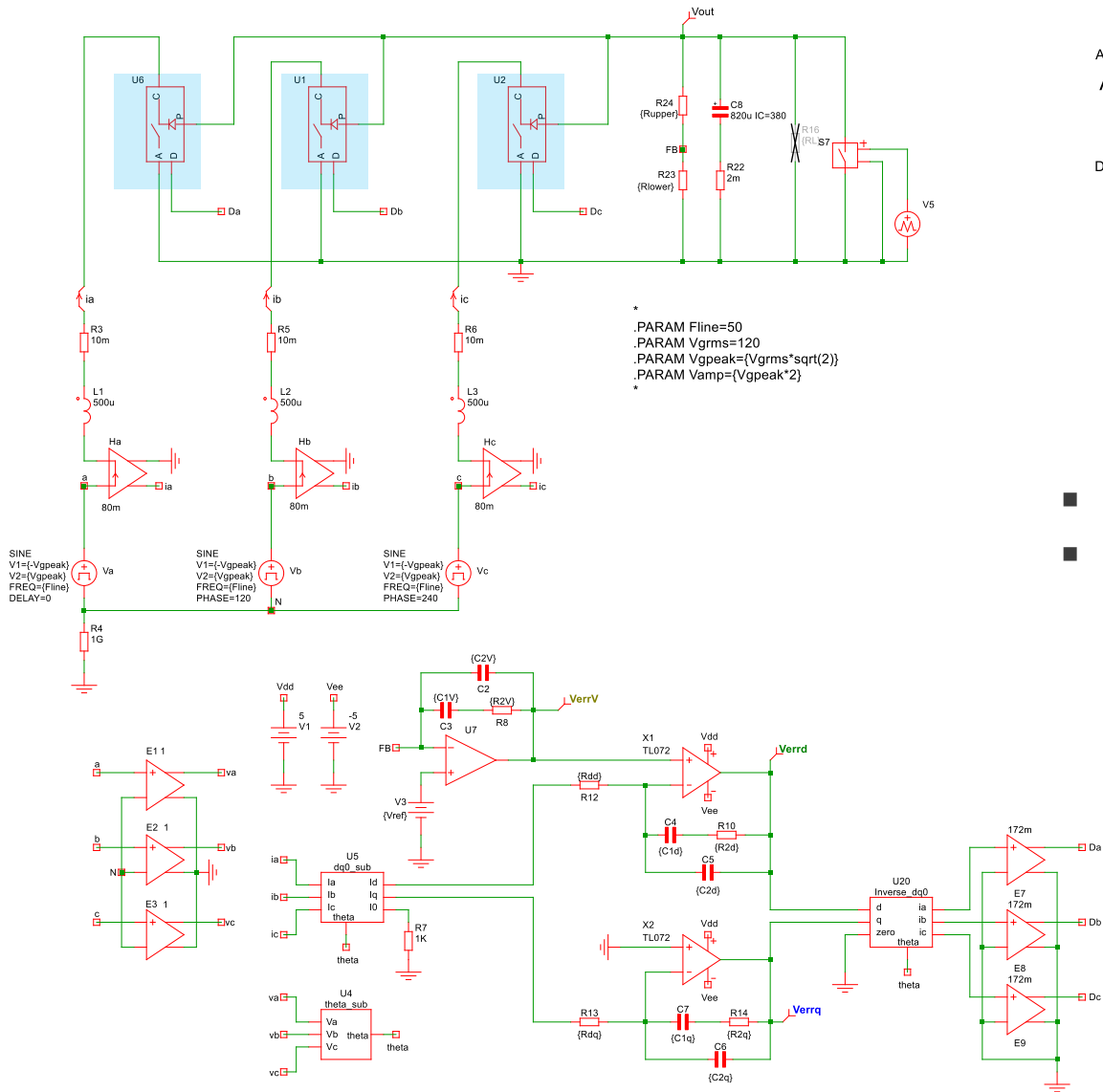


Simplified Analysis of PWM Converters Using Model of PWM Switch
Part I: Continuous Conduction Mode

VATCHÉ VORPÉRIAN
Virginia Polytechnic Institute and State University

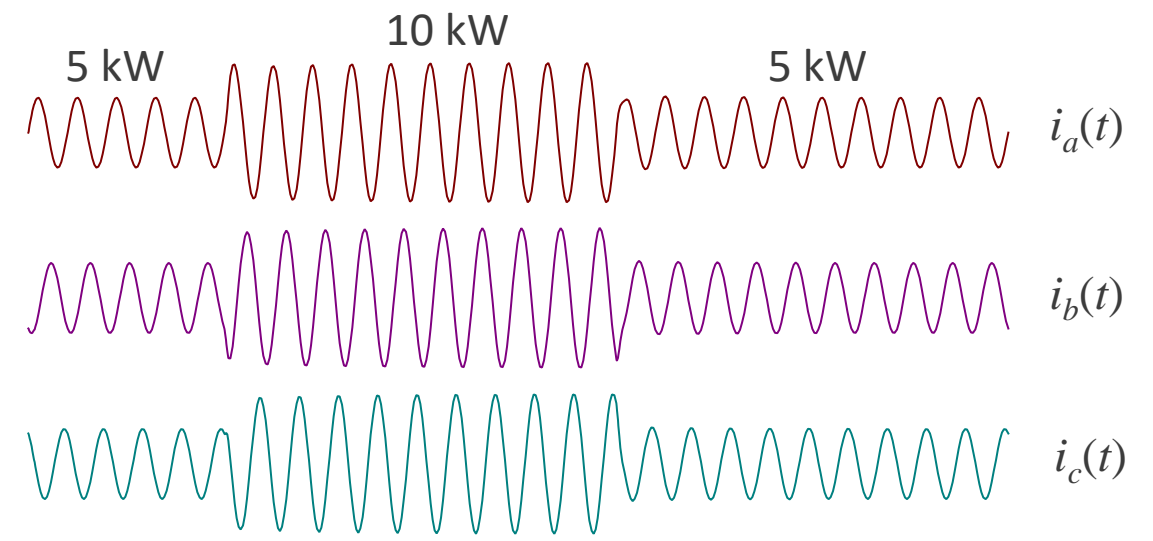
V. Vorpérian, *Simplified analysis of PWM converters using model of PWM switch. Continuous conduction mode*, in *IEEE Transactions on Aerospace and Electronic Systems*, vol. 26, no. 3,, May 1990

- I have replaced the switching cell by the VM PWM switch model
- Pulse-width modulators are replaced by small-signal gains




Control-to-Output Transfer Functions

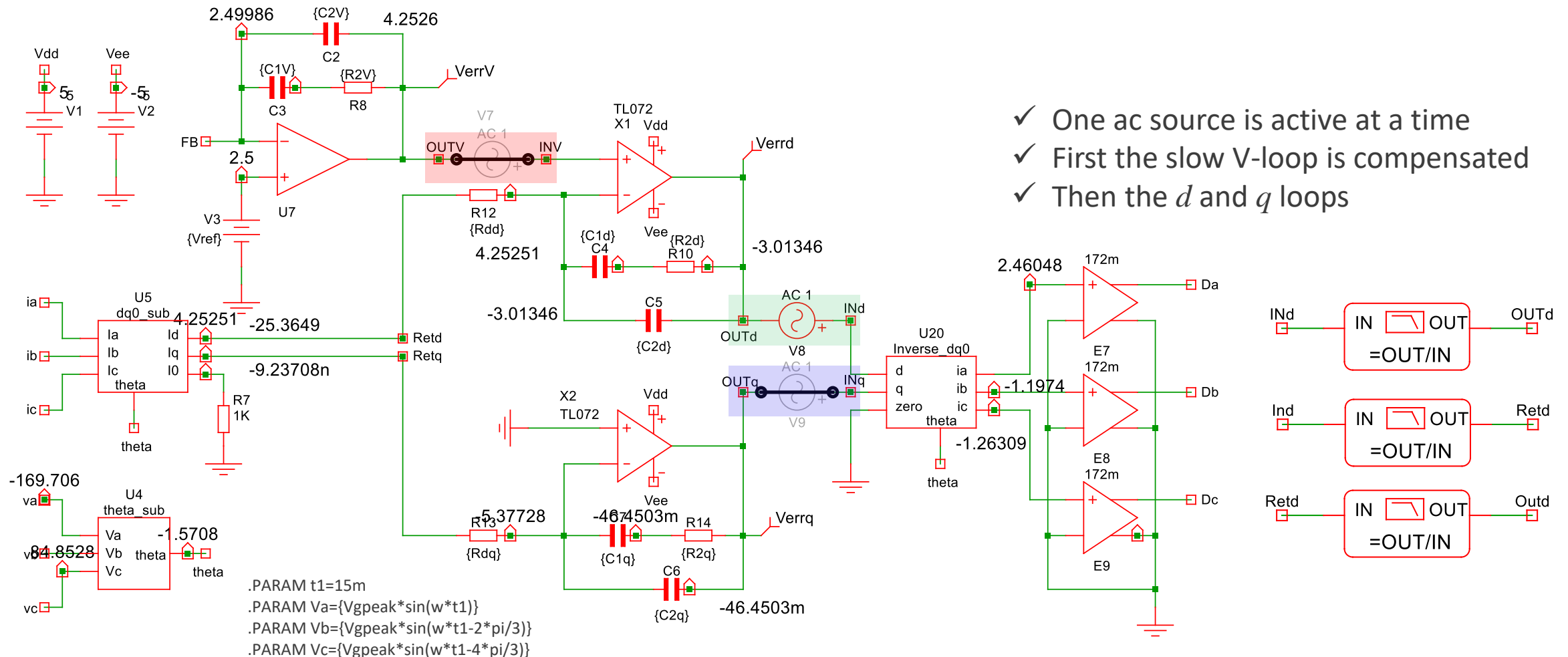- Three loops: V_{out} to be regulated at 400 V and the d and q paths
- The voltage loop will be closed with a 20-Hz crossover while f_c for d and q will be 2 kHz




Compensation Strategies

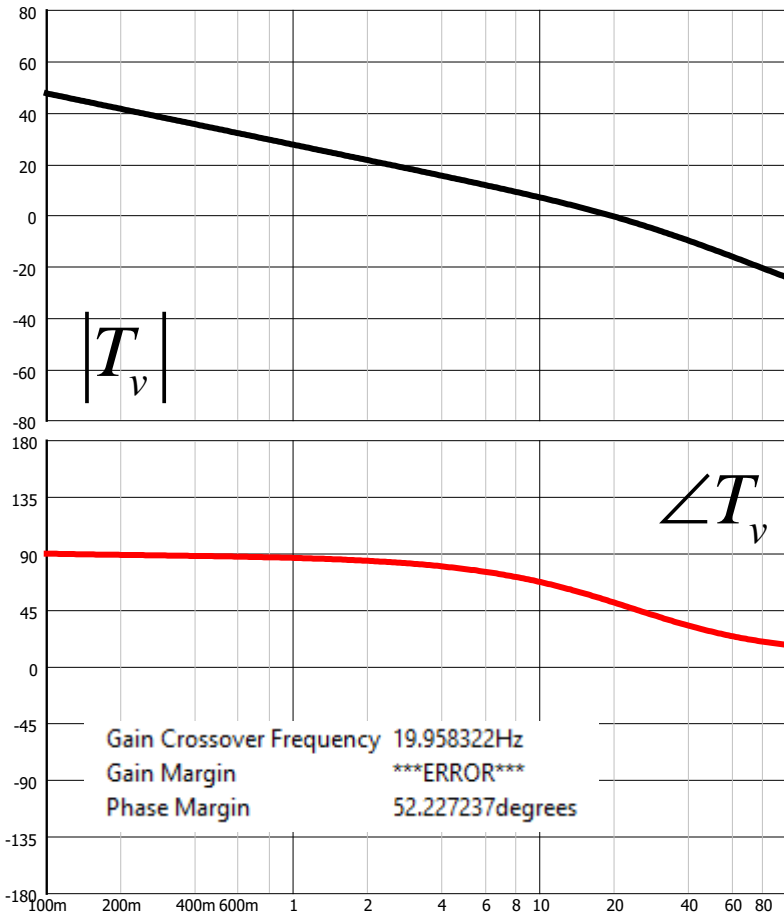
- The three loops are individually compensated with adequate phase and gain margins



Voltage loop – $f_c = 20$ Hz

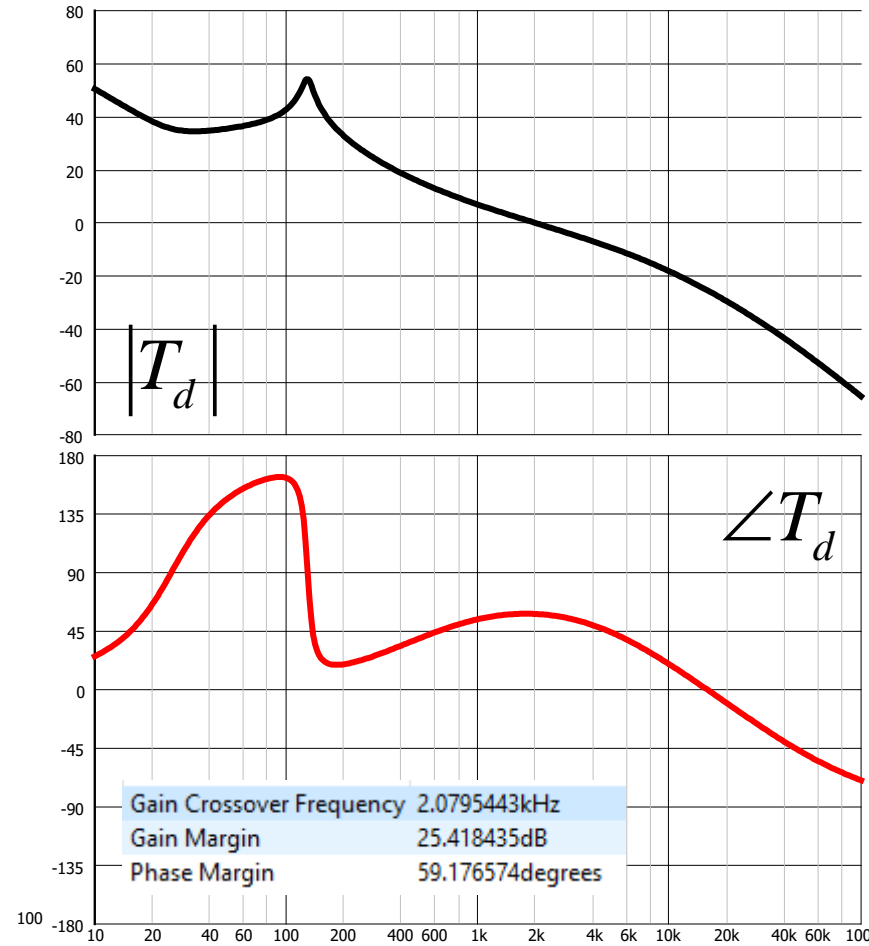


d loop – $f_c = 2$ kHz

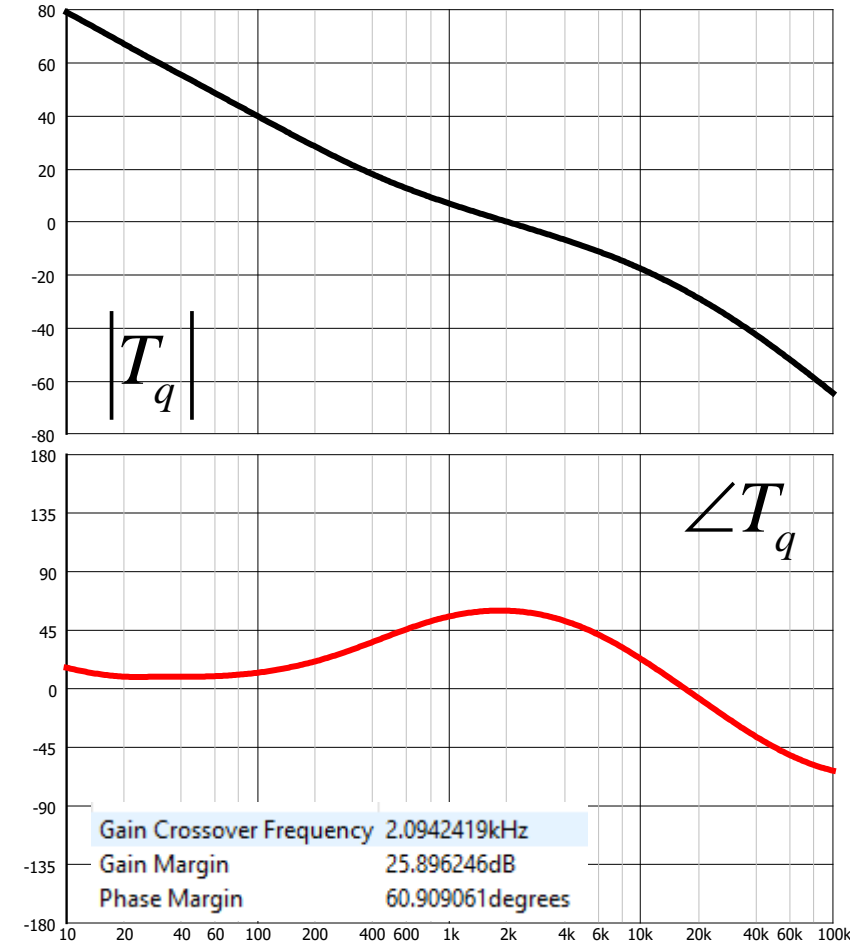

q loop – $f_c = 2$ kHz

Comparison between Models

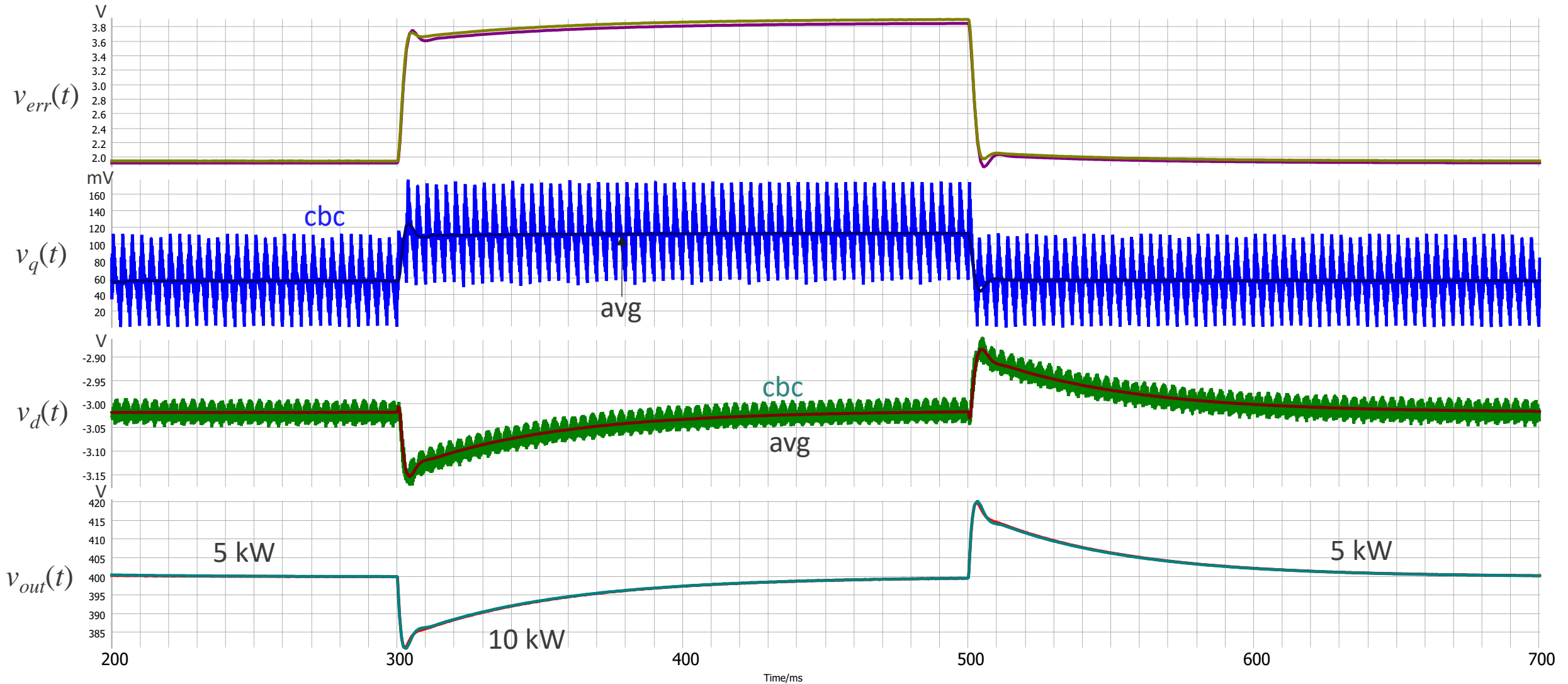- Excellent correlation between cycle-by-cycle and average model waveforms



Conclusion

- Tri-phase electrical networks are generated from spinning machines
- Modeling and controlling a three-variable system is complicated
- ✓ Clarke's equations transform a 3-phase network into a 2-component frame
- ✓ Park's equations transform the 2 ac components into dc variables, d and q
- Regulation on static variables is simpler and various techniques apply
- Numerous modulation schemes exist such as SPWM and SVM
- Average modeling helps extracting ac responses for loop control
- Implementation is rarely analogue but done via DSPs or micro-controllers