

GaN-Based 250-kHz LLC Converter with Hybrid Analogue-Digital Control

Christophe Basso¹, Josef Burger², David Woodcock², Zhi Zhang²

¹ Future Electronics, Colomiers, France


² Future Electronics, Centre of Excellence, Egham, UK

Agenda

- The LLC Converter
- Controlling the Power Flow
- A Closed-Loop Control System
- Bringing a Microcontroller on Board
- Combining Analogue and Digital
- Practical Implementation
- Conclusion


What is an LLC Converter?

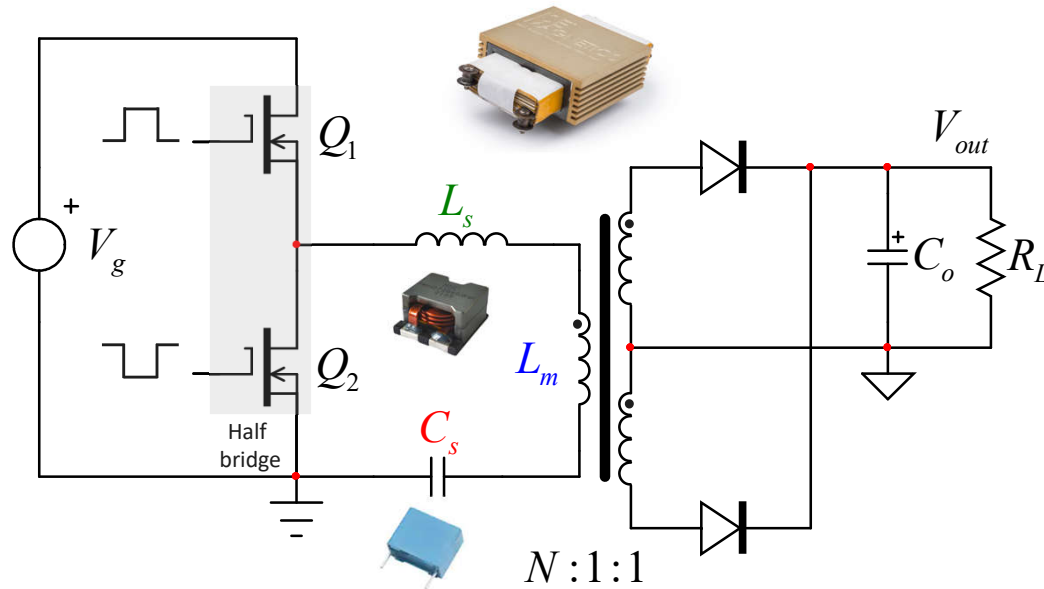- The LLC converter is a member of the series-resonant converters family
- The magnetizing inductance L_m is part of the resonating elements (L)
- The transformer leakage inductance or an extra inductor forms the term L_s (L)
- A series capacitor C_s is inserted to form the complete resonant converter (C)



The Benefits of the LLC Converter

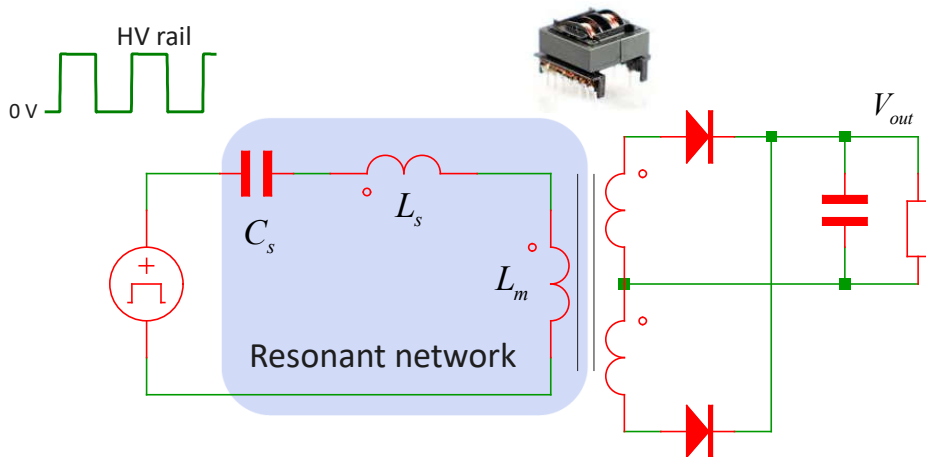
- The LLC converter offers soft-switching conditions in normal-load conditions
- ✓ Zero-voltage switching (ZVS) for the switches in the primary side
- ✓ Zero-current switching (ZCS) for the secondary-side diodes
- It can operate at high switching frequency to build compact converters
- ✓ Perfect for flat-panel displays like LCD TVs, game stations, servers power supplies




- ✓ Three energy-storing elements, C_s , L_s and the transformer magnetizing inductance L_m
- ✓ Components count is limited especially if integrated magnetics is adopted

Different Configurations for the LLC - Primary

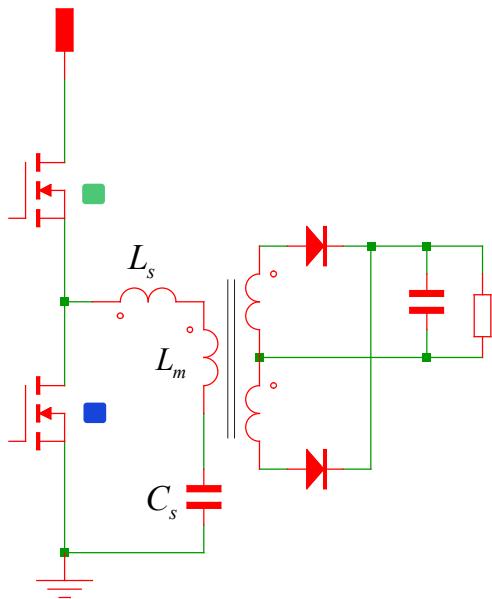
- The LLC converter can be operated in half- or full-bridge configuration



- Power up to 600 W

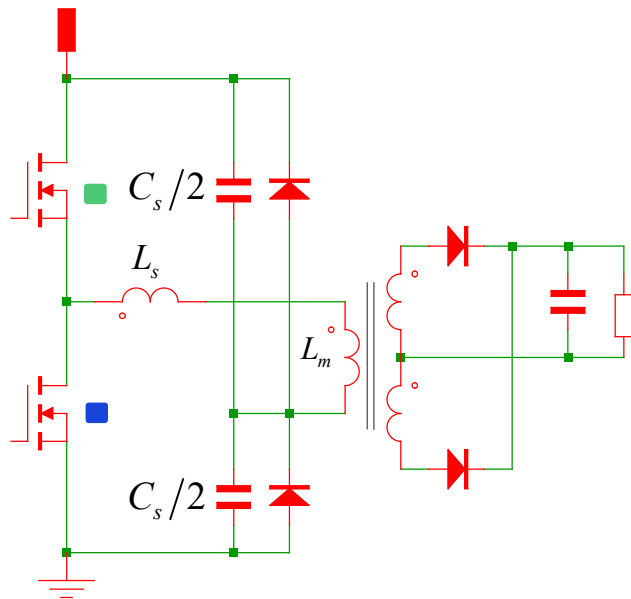

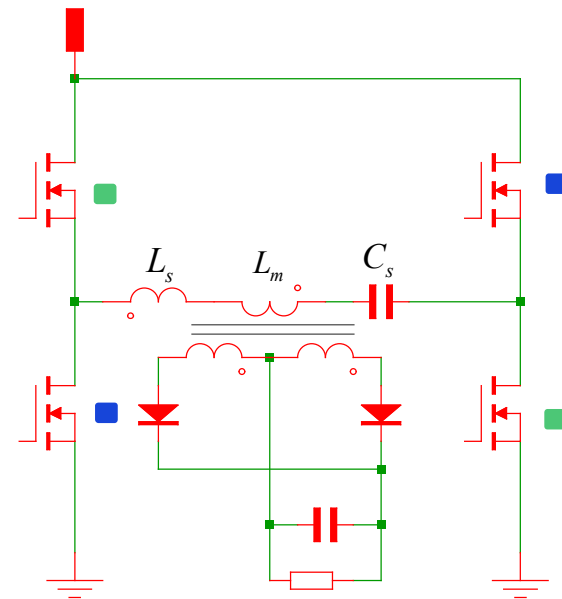
- Robust version with clamp diodes
- ✓ Lower input ripple current
- ✓ Half rms current in a capacitor




- Power beyond 1 kW
- ✓ Diagonal conduction

Different Configurations for the LLC - Secondary

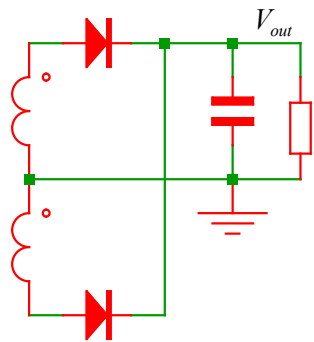
- A full-bridge rectifier requires diodes with a lower breakdown voltage



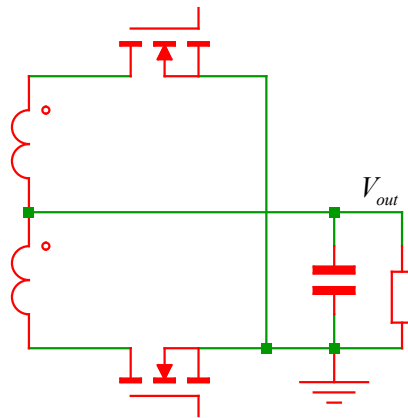- Two separate windings
- $BV > 2V_{out}$
- Secondary leakage brings current imbalance



- Synchronous rectification

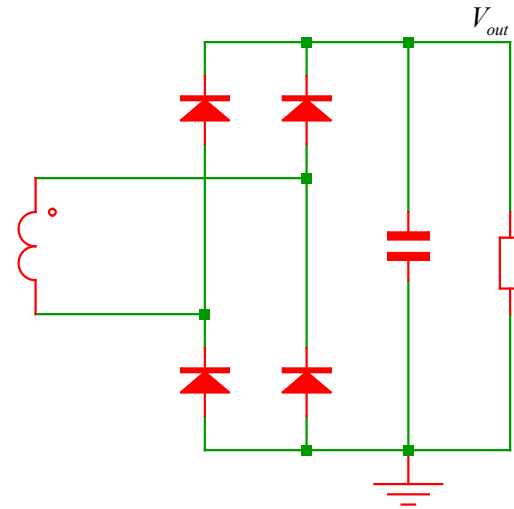


- One single winding
- $BV > V_{out}$
- No current imbalance

Agenda

- The LLC Converter
- Controlling the Power Flow
- A Closed-Loop Control System
- Bringing a Microcontroller on Board
- Combining Analogue and Digital
- Practical Implementation
- Conclusion

Direct Frequency Control

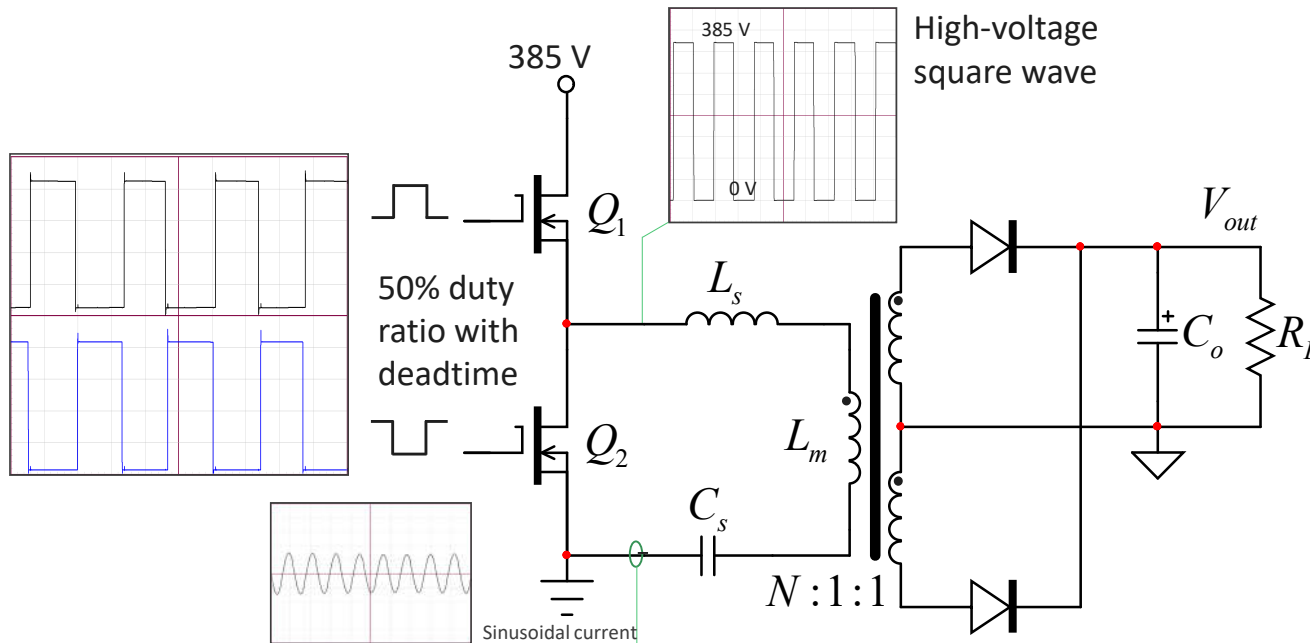- An LLC converter is typically operated from a 50% high-voltage square waveform
- The power flow is then adjusted by varying the switching frequency
- Soft-switching on MOSFETs and diodes depends on frequency with respect to f_s



High power

$$f_s = \frac{1}{2\pi\sqrt{L_s C_s}}$$




A multi-resonance system

$$f_m = \frac{1}{2\pi\sqrt{(L_s + L_m)C_s}}$$

Low power

The Resonance varies with the Output Power

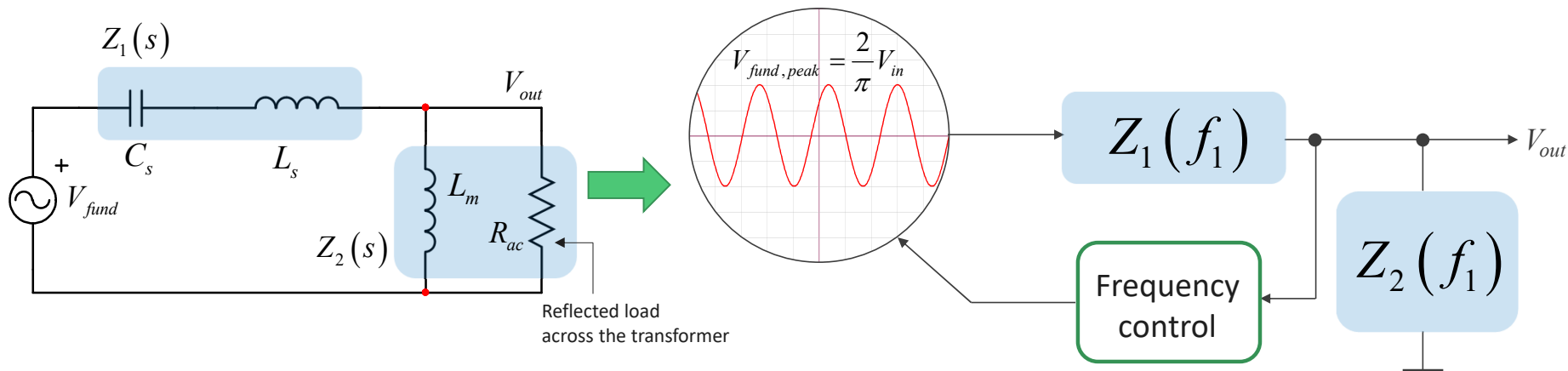
- The LLC converter is a multi-resonance converter depending on operating conditions
- In heavy-load condition, L_s dominates the resonant tank as L_m is shunted by R_{ac}
- In lighter-load operations, L_m and L_s together set the resonant frequency



- The converter is modeled using the first harmonic approximation or FHA

Where to Operate the Converter?

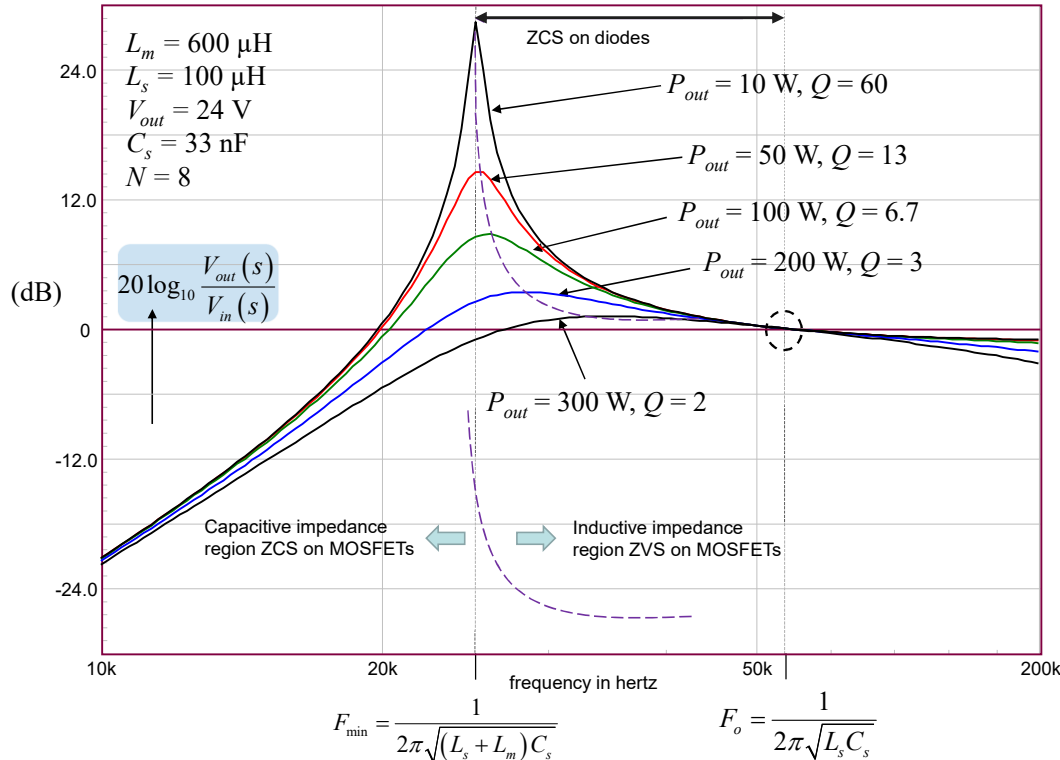- Plotting the dc transfer characteristic of the LLC network reveals several points



- ✓ As load current decreases, L_m enters the picture and brings a second peak
- ✓ An impedance plot shows so-called **capacitive** and **inductive** regions
- ✓ The inductive region brings ZVS on power MOSFETs and ZCS on output diodes
- ✓ ZCS on MOSFETs is occurring in the capacitive region but the control law changes!



Output Voltage of an LLC Converter

- The equivalent network is fed by the square-wave fundamental value according to FHA
- ✓ Determine the output voltage with the transfer function of the 3rd-order network

$$H_{m1}(s) := \frac{1}{N_{ps}} \cdot \frac{\frac{L_3}{L_2} \cdot \left(\frac{s}{\omega_s}\right)^2}{1 + s \cdot \frac{L_3}{R_1} + \left(\frac{s}{\omega_m}\right)^2 + s^3 \cdot \frac{L_3}{L_2 \cdot Q_1 \cdot \omega_s^3}}$$

$$V_{out} := V_{fund} \cdot \left| H_{ref}(i \cdot 2\pi \cdot F_{sw}) \right| = 45.19774V$$
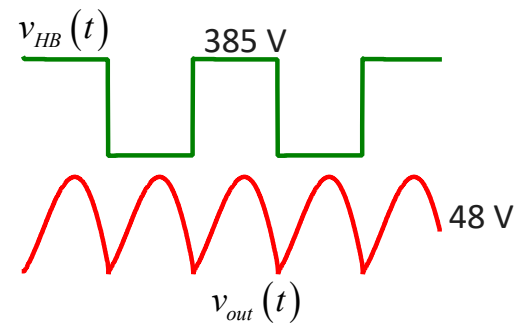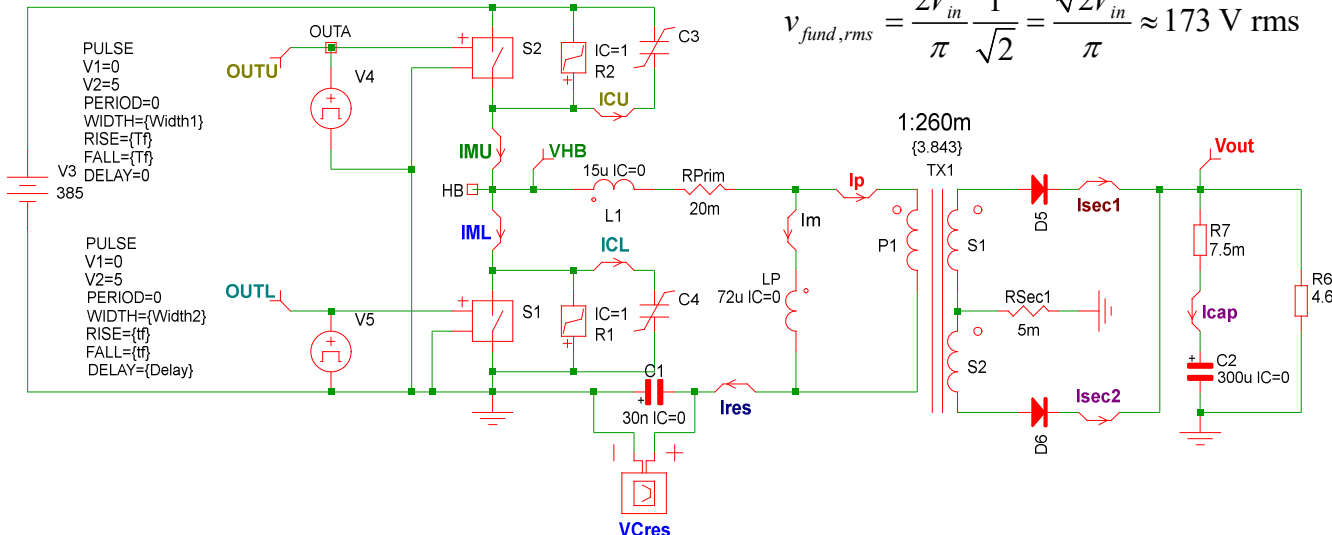
$$v_{fund,rms} = \frac{2V_{in}}{\pi} \cdot \frac{1}{\sqrt{2}} = \frac{\sqrt{2}V_{in}}{\pi} \approx 173 \text{ V rms}$$





Agenda

- The LLC Converter
- Controlling the Power Flow
- A Closed-Loop Control System
- Bringing a Microcontroller on Board
- Combining Analogue and Digital
- Practical Implementation
- Conclusion

Shaping the Loop with the Compensator

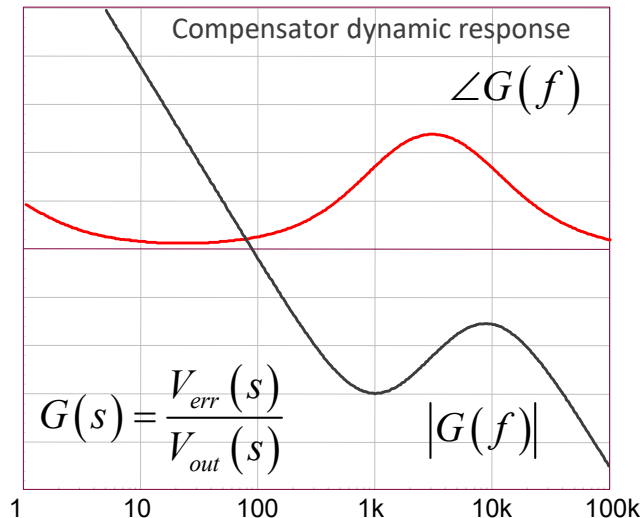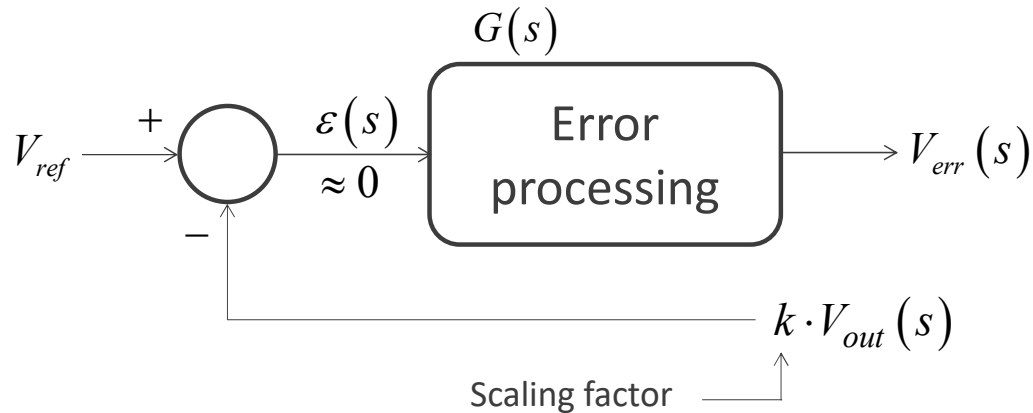
- The compensator builds the error variable and ensures stability
- Insert poles and zeros to create the compensation strategy
- Choose how to cross over at f_c with phase and gain margins




- The block amplifies and shapes the error ε between V_{ref} and V_{out}
- ✓ Minimize the error between the setpoint and the output



Building the Compensator – the Analogue Way

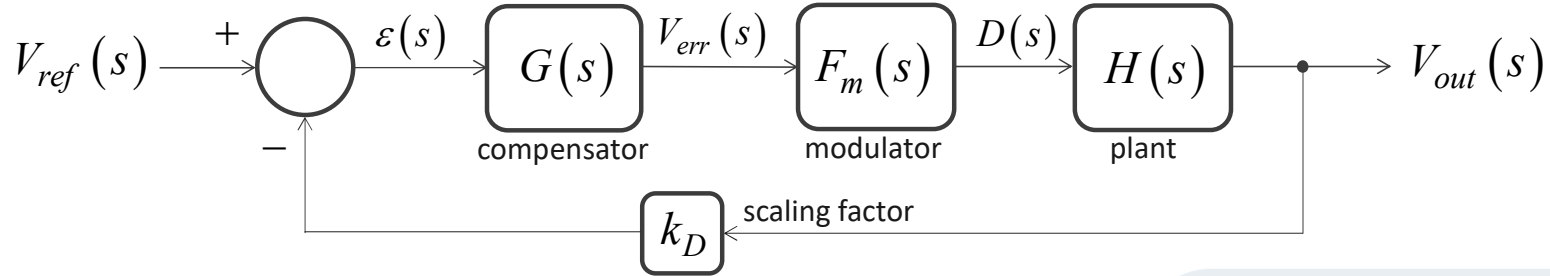- Associate active and passive components to form the compensation chain




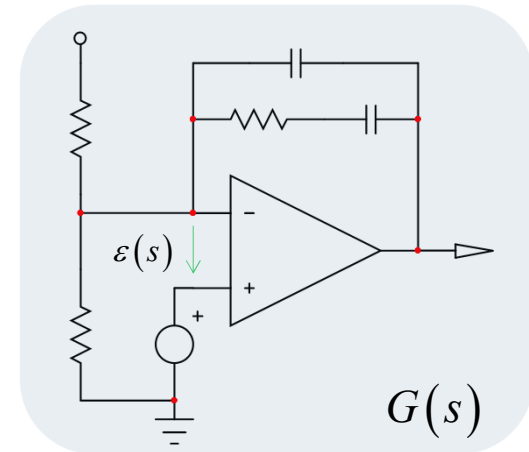
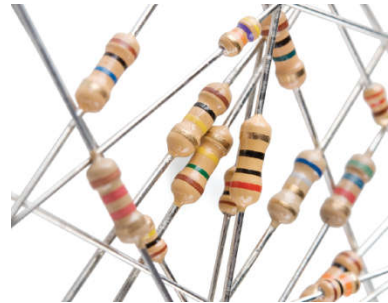
1. Select poles/zeros placement
2. Calculate components values
3. Solder resistors and capacitors

 Change in strategy requires new components values



How do you Build an Analogue Compensator?

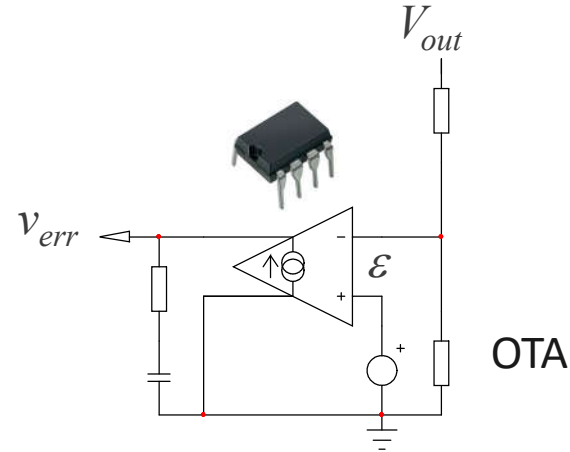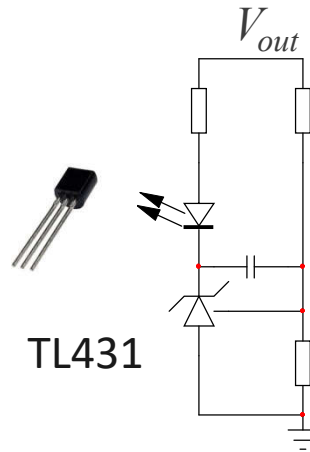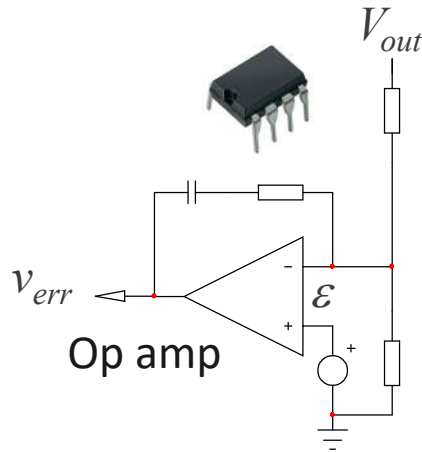
- A compensator can be a passive or active filter shaped for a specific response



- ✓ Passive components suffer drawbacks:
 1. Tolerance, aging
 2. Sensitivity to temperature, humidity



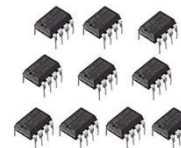
- ✓ Active components are not perfect!
 1. Open-loop gain, bias requirements
 2. Limited in bandwidth, slew-rate
 3. Temperature drift



OTA: operational transconductance amplifier

Building the Compensator – the Digital Way

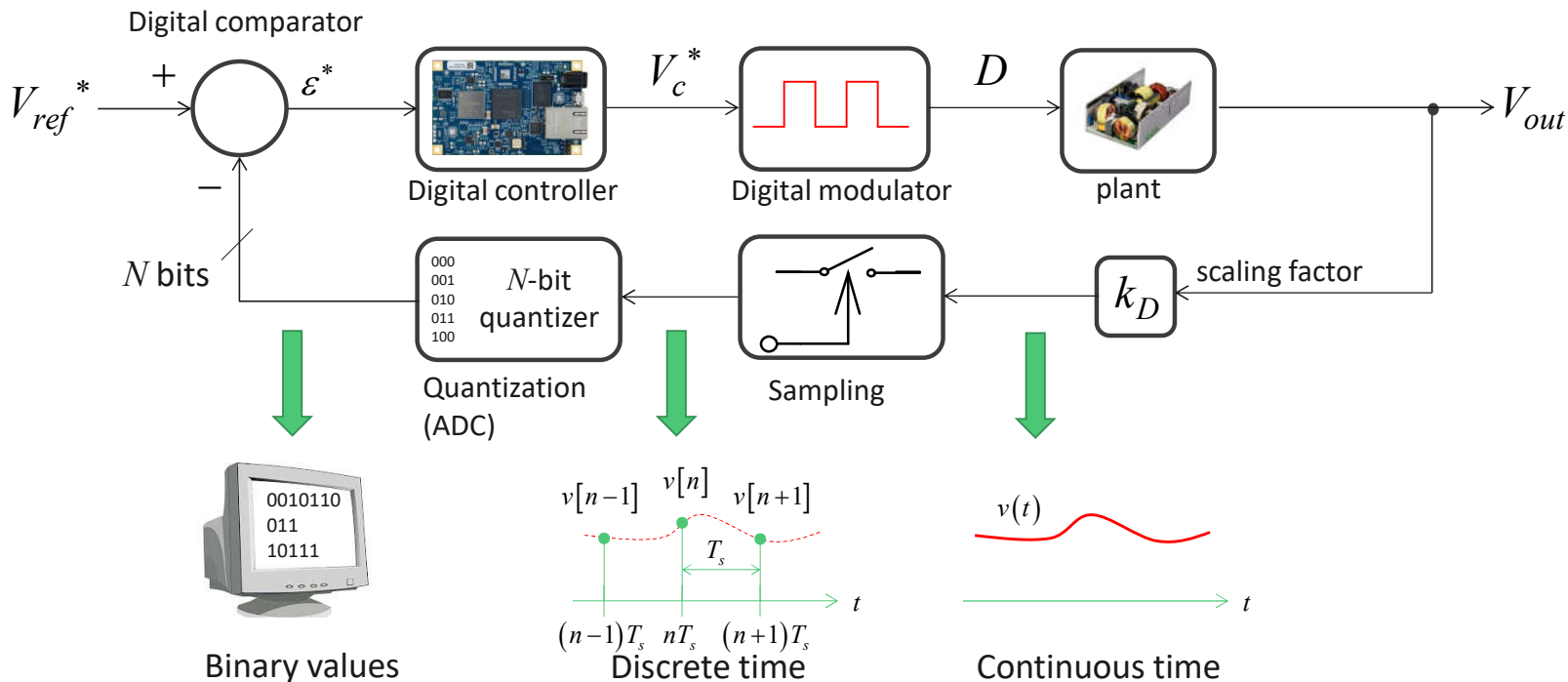
- A digitally-controlled system mixes sampled and continuous-time data



* designates a discrete variable


How do you Implement a Digital Compensator?

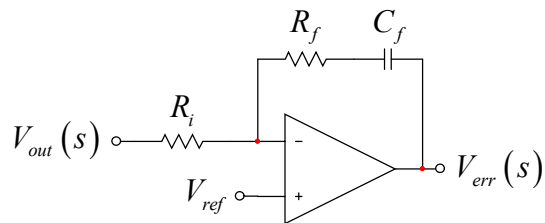- You can start from a continuous-time transfer function expressed in s



$$sV_{err}(s) = -s \frac{R_f}{R_i} V_{out}(s) - \frac{1}{R_i C_f} V_{out}(s)$$


Map into the z-domain

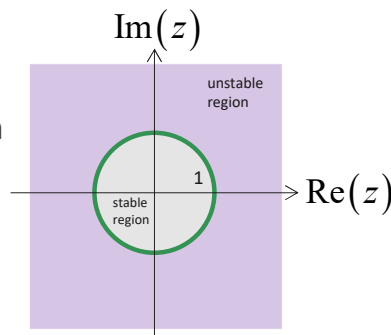

Difference equation

$$b_0 V_{err}(z) + b_1 z^{-1} V_{err}(z) = a_0 V_{out}(z) + a_1 z^{-1} V_{err}(z)$$

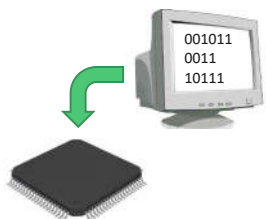- Code the filter equation with a micro-controller or hard-wire it in a FPGA



Digital control

```

1 import PID
2 import time
3 import os.path
4
5 from OmegaExpansion import AdcExp
6 from OmegaExpansion import pwmExp
7
8 pwmExp.setVerbosity(-1)
9 pwmExp.driverInit()
10 adc = AdcExp.AdcExp()
11
12 targetT = 35
13 P = 10
14 I = 1
15 D = 1
    
```

- ✓ No tolerance or age issues
- ✓ Flexibility and optimization
- ✓ On-the-fly poles-zeroes changes
- ❖ More complex to analyze
- ❖ Warping occurs during mapping
- ❖ Lower crossover systems

Learning curve





Agenda

- The LLC Converter
- Controlling the Power Flow
- A Closed-Loop Control System
- **Bringing a Microcontroller on Board**
- Combining Analogue and Digital
- Practical Implementation
- Conclusion

Where to install the Microcontroller?

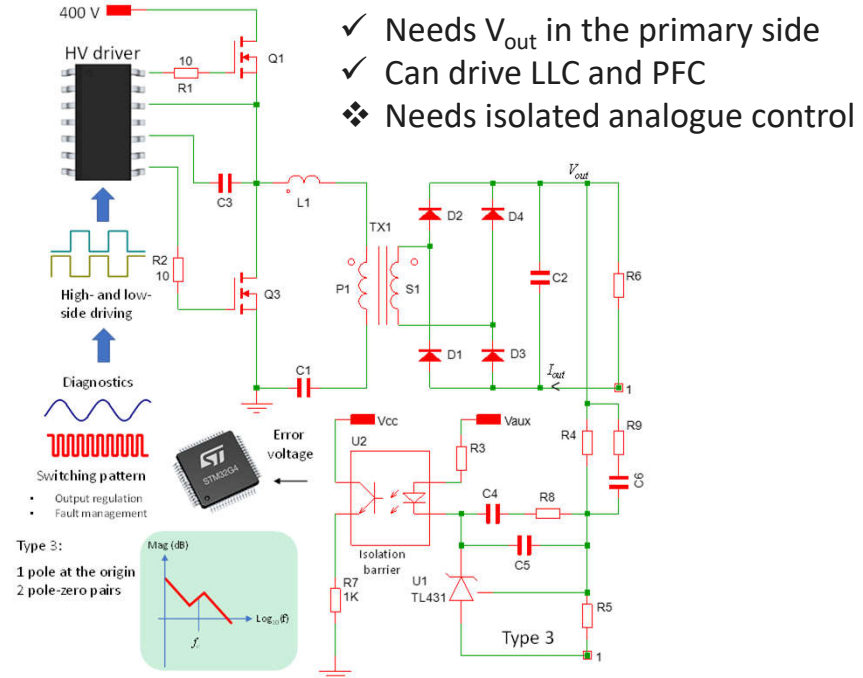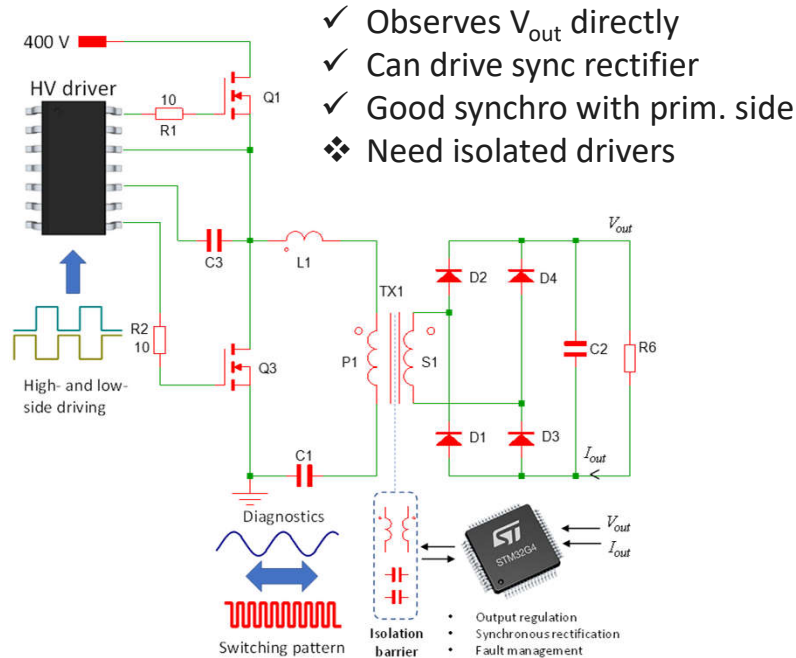- The component can be placed in the secondary- or primary-side of the converter
- ✓ *Secondary side* gives access to V_{out} and sync rect control – how to drive HV MOSFETs?
- ✓ *Primary side* drives and monitors MOSFETs directly but needs isolated access to V_{out}



A GaN-based 500-W LLC Converter



- The circuit will switch at 250 kHz and deliver 48 V/10 A from a 400-V dc source
- MasterGaN1 integrated half-bridge is used in the primary side
- A STM32G4 will control the operations and ensure regulation



MasterGaN1



STM32G4
512 kB flash
128 kB RAM

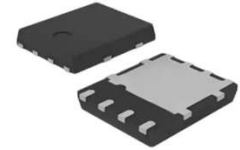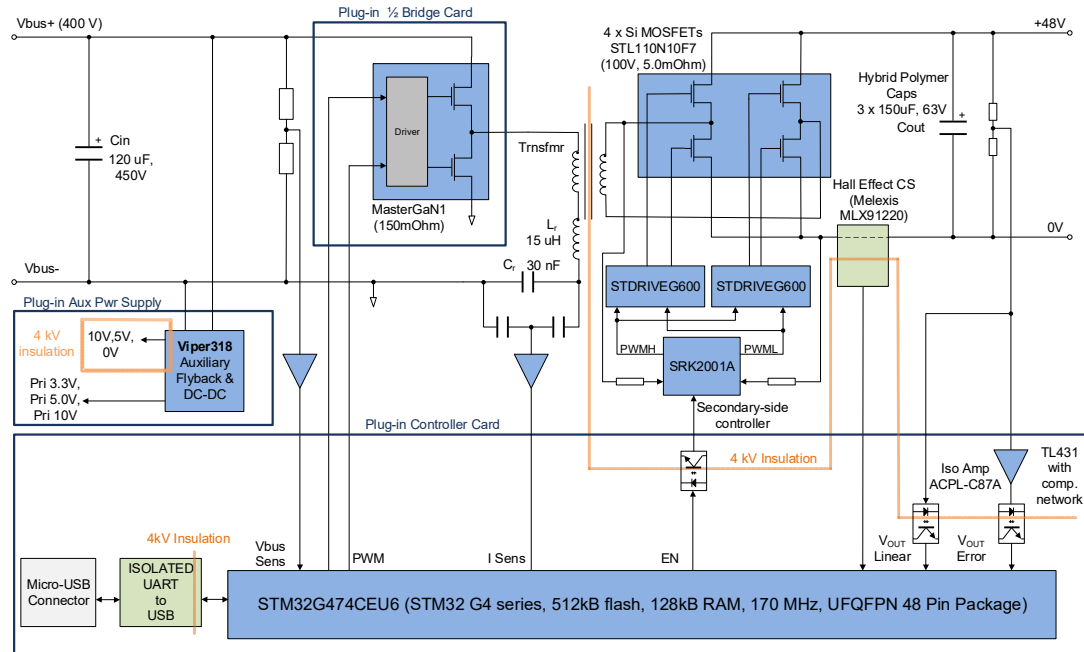




Secondary full-bridge synchronous rectification



Optocoupler-based hybrid configuration for the feedback


Isolating the Regulation Path

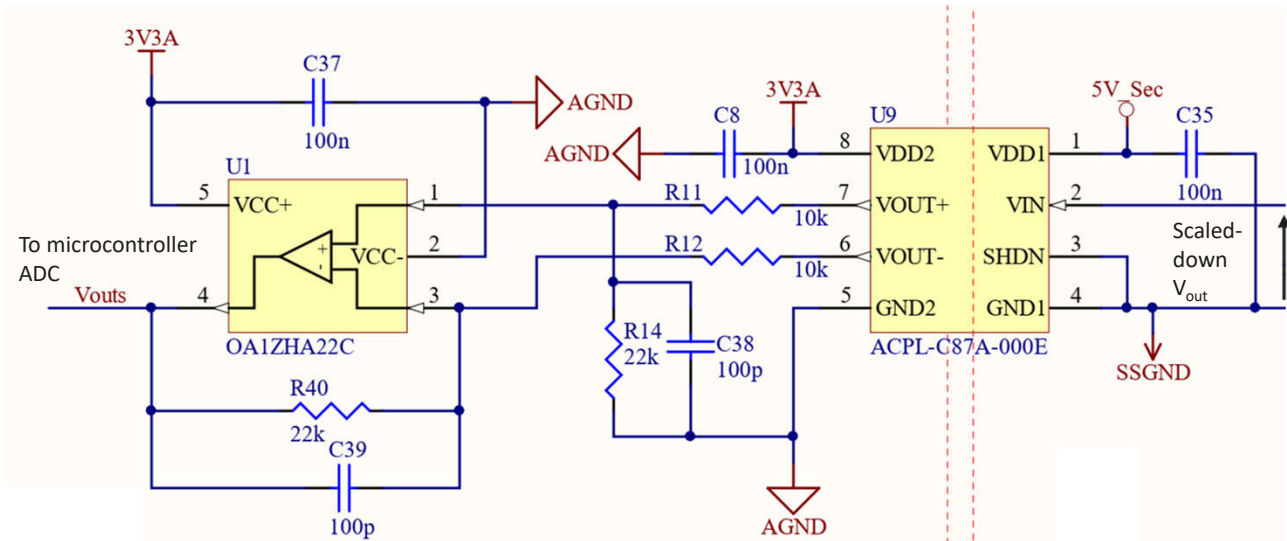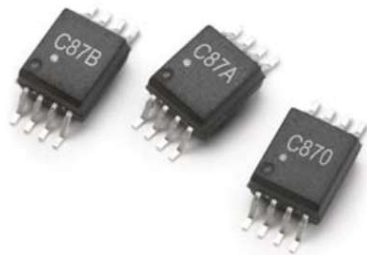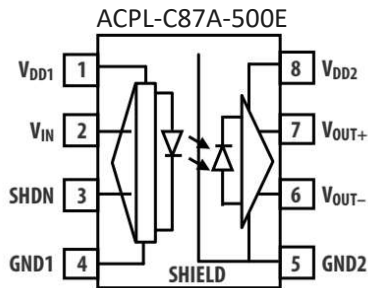- One easy solution consists of using a fully-isolated linear amplifier
- ✓ The part exhibits a 100-kHz bandwidth with 1 kV+ isolation voltage
- ✓ Compact 8-pin package
- ❖ Cost is high



The Control-to-Output Transfer Function

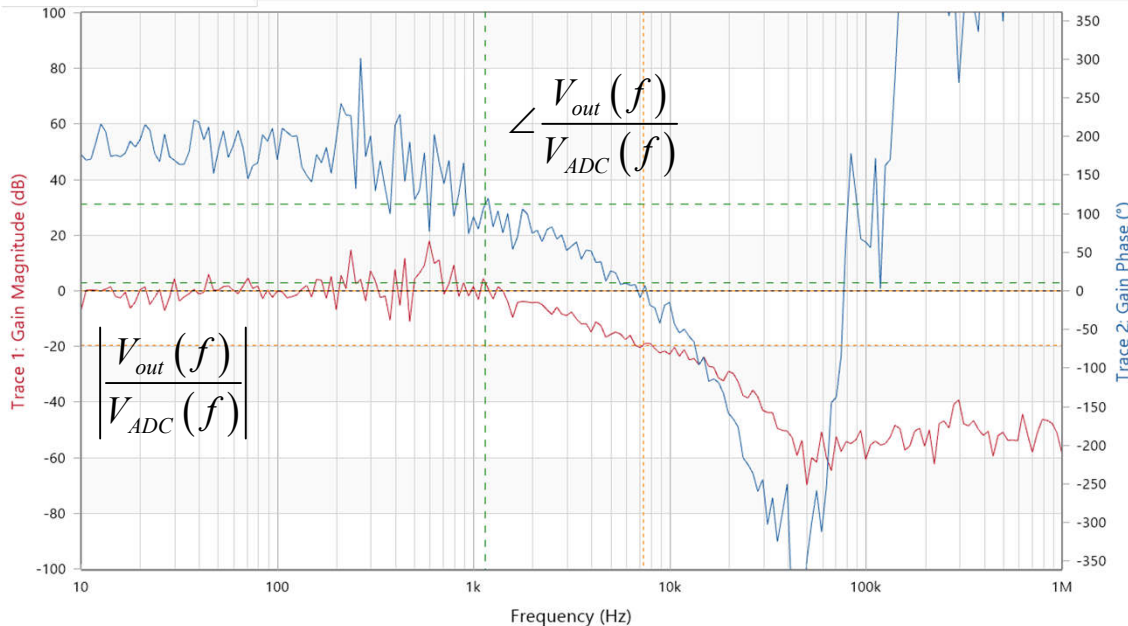- This is the starting point for the loop stabilization exercise
- A stimulus is applied to the microcontroller ADC input with $k_d = k_i = 0$
- Coefficient k_p is kept for transmitting the modulation pattern from the FRA




- A *stimulus* is applied at the ADC input
- This stimulus modulates the switching frequency to form a *response*

$$H(s) = \frac{V_{out}(s)}{V_{ADC}(s)} \leftarrow \begin{array}{l} \text{response} \\ \text{stimulus} \end{array}$$

Discrete Loop Compensation

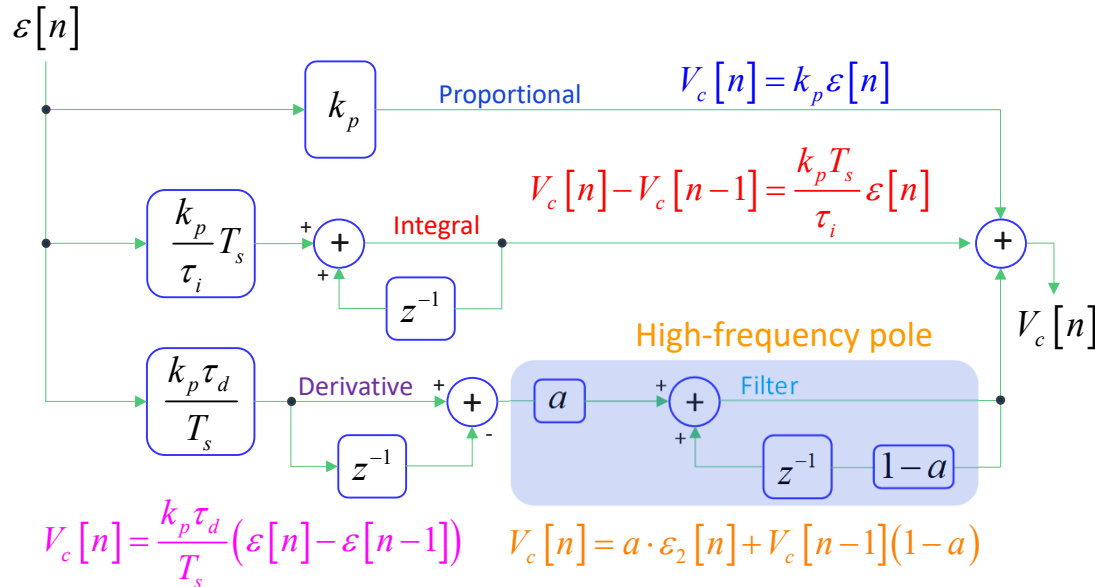- The microcontroller implements an unfiltered-PID routine used for the first experiments
- The sampling frequency is 50 kHz and the goal is to crossover at 1 kHz
- A PID is made of several blocks introducing a pole at the origin and two zeroes
- These parameters are set by coefficients k_i , k_d and k_p



Example of code, *PID_regulators.c*, STMicroelectronics

```
int16_t PID_Regulator(int16_t hReference, int16_t hPresentFeedback, PID_Struct_t *PID_Struct)
{
    int32_t wError, wProportional_Term, wIntegral_Term, wOutput_32, wIntegral_sum_temp;
    int32_t wDischarge = 0;
    int16_t hUpperOutputLimit = PID_Struct->hUpper_Limit_Output;
    int16_t hLowerOutputLimit = PID_Struct->hLower_Limit_Output;

#ifdef DIFFERENTIAL_TERM_ENABLED
    int32_t wDifferential_Term;
#endif
    // error computation
    wError = (int32_t)(hReference - hPresentFeedback);

    // Proportional term computation
    wProportional_Term = PID_Struct->hKp_Gain * wError;

    // Integral term computation
    if (PID_Struct->hKi_Gain == 0)
    {
        PID_Struct->wIntegral = 0;
    }
    else
    {
        wIntegral_Term = PID_Struct->hKi_Gain * wError;
        wIntegral_sum_temp = PID_Struct->wIntegral + wIntegral_Term;


        if (wIntegral_sum_temp < 0)
        {
            if (PID_Struct->wIntegral > 0)
            {

```

Convert Poles and Zeroes to Coefficients

- It is advantageous to convert the wanted poles and zeroes to PID coefficients
- Methods like Ziegler-Nichols are based on empirical approach

$$\tau_i = \frac{\omega_{z_1} + \omega_{z_2}}{\omega_{z_1} \omega_{z_2}} - \frac{1}{\omega_{p_1}} \quad N = \frac{\omega_{p_1}^2}{\omega_{p_1} \omega_{z_1} + \omega_{p_1} \omega_{z_2} - \omega_{z_1} \omega_{z_2}} - 1 \quad k_p = \frac{\omega_{p_0}}{\omega_{z_1}} - \frac{\omega_{p_0}}{\omega_{p_1}} + \frac{\omega_{p_0}}{\omega_{z_2}} \quad \tau_d = \frac{(\omega_{p_1} - \omega_{z_1})(\omega_{p_1} - \omega_{z_2})}{(\omega_{p_1} \omega_{z_1} + \omega_{p_1} \omega_{z_2} - \omega_{z_1} \omega_{z_2}) \omega_{p_1}}$$

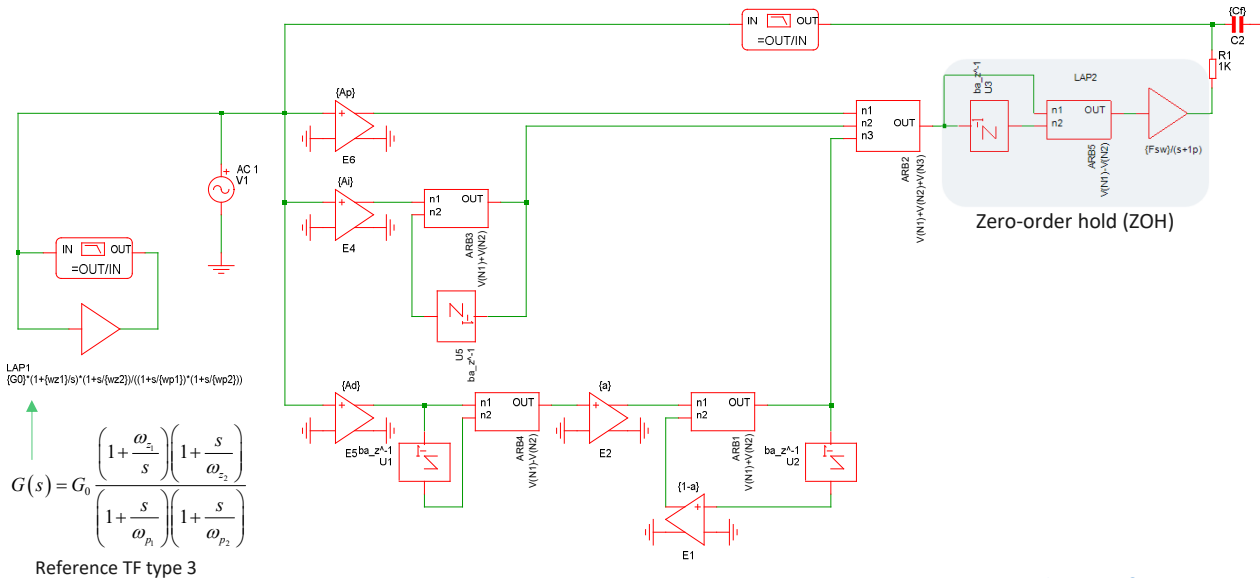


- Choose poles/zeroes position
- Compute PID coefficients

$f_c = 3 \text{ kHz}$	}	$\tau_d = 193 \mu\text{s}$
$G_{f_c} = 20 \text{ dB}$		$N = 26.43$
$f_{z_1} = 200 \text{ Hz}$		$\tau_i = 1.053 \text{ ms}$
$f_{z_2} = 600 \text{ Hz}$		$k_p = 2.64$
$f_{p_1} = 21 \text{ kHz}$		$A_i = 2.51 \text{ m}$
$f_{p_2} = 21 \text{ kHz}$		$A_d = 509.6$


Magnitude and Phase Response of the Discrete PID

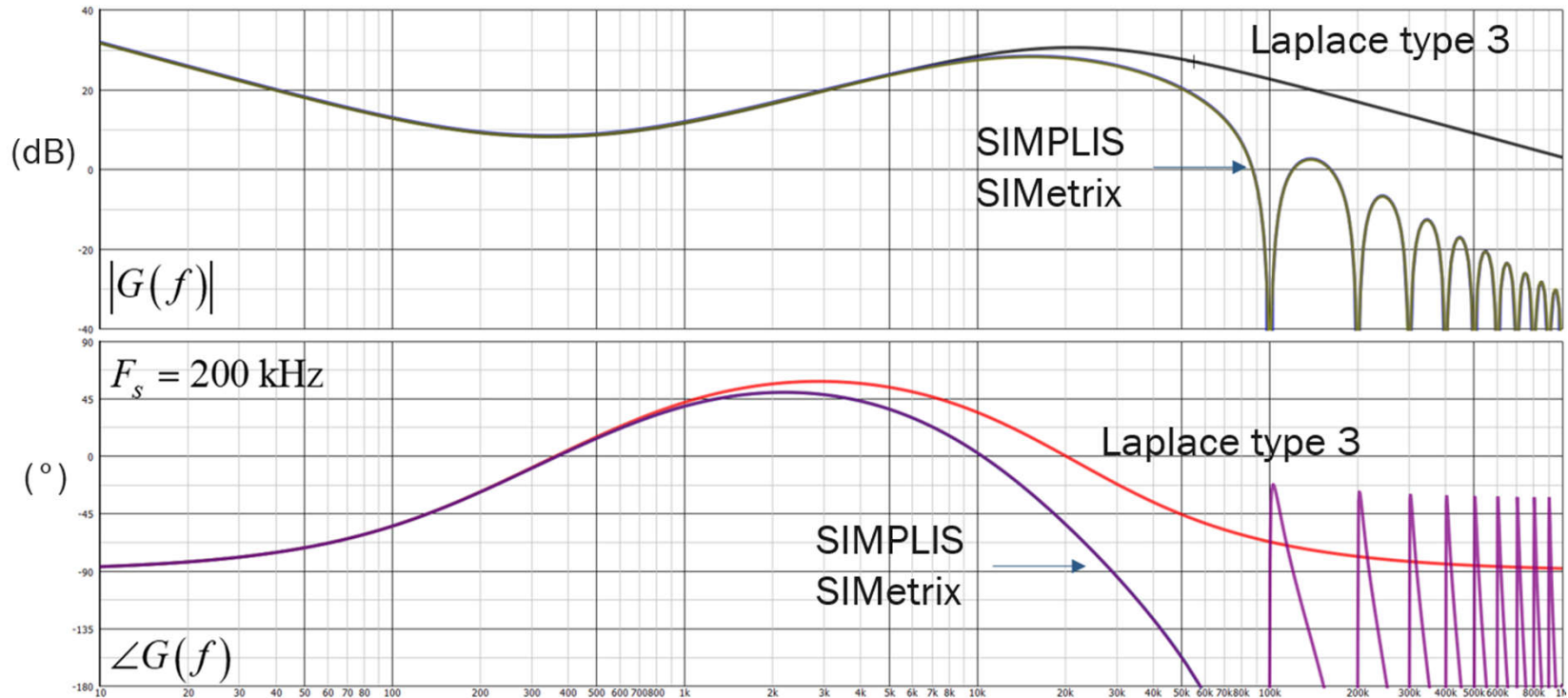- The PID with a second pole shows a response of a type 3 compensator
- The response deviates from the original time-continuous response past a few kHz



Compensated Loop Gain

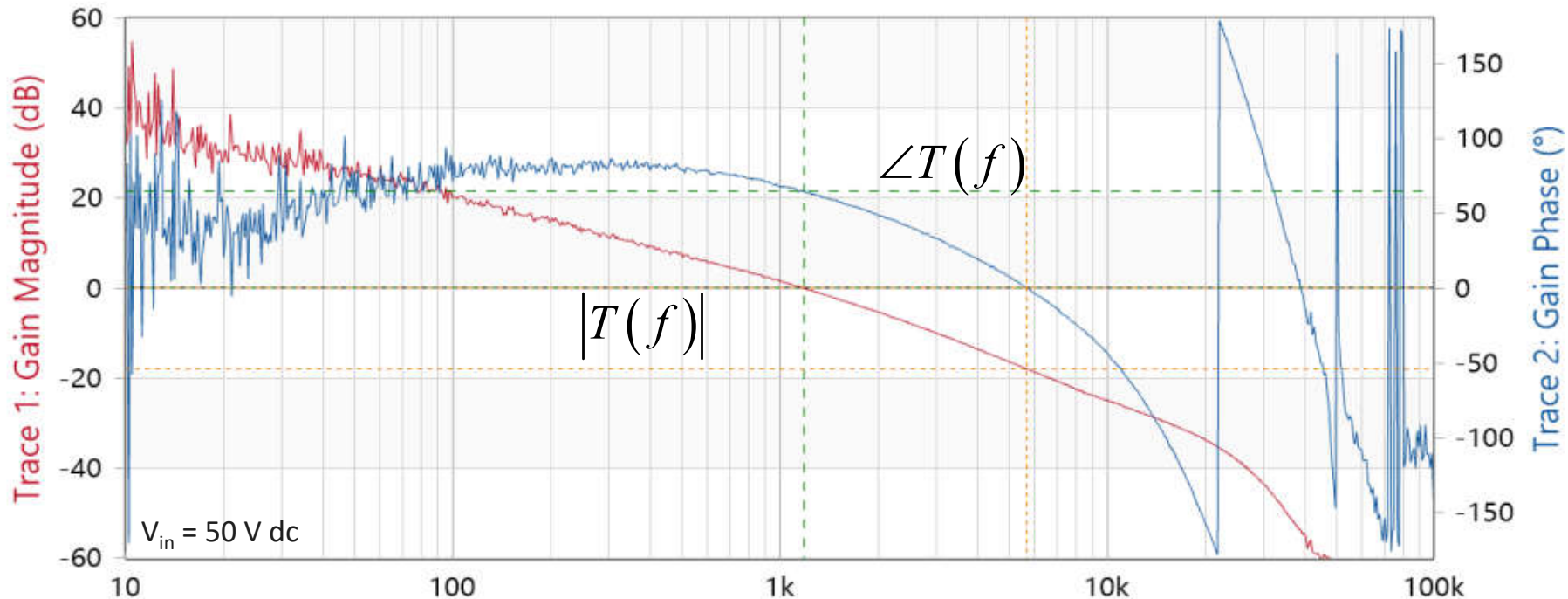
- Computed coefficients lead to a good frequency response for the low-voltage version
- The crossover frequency is slightly above 1 kHz with more than 50° of phase margin



Agenda

- The LLC Converter
- Controlling the Power Flow
- A Closed-Loop Control System
- Bringing a Microcontroller on Board
- **Combining Analogue and Digital**
- Practical Implementation
- Conclusion


Analogue and Digital Control

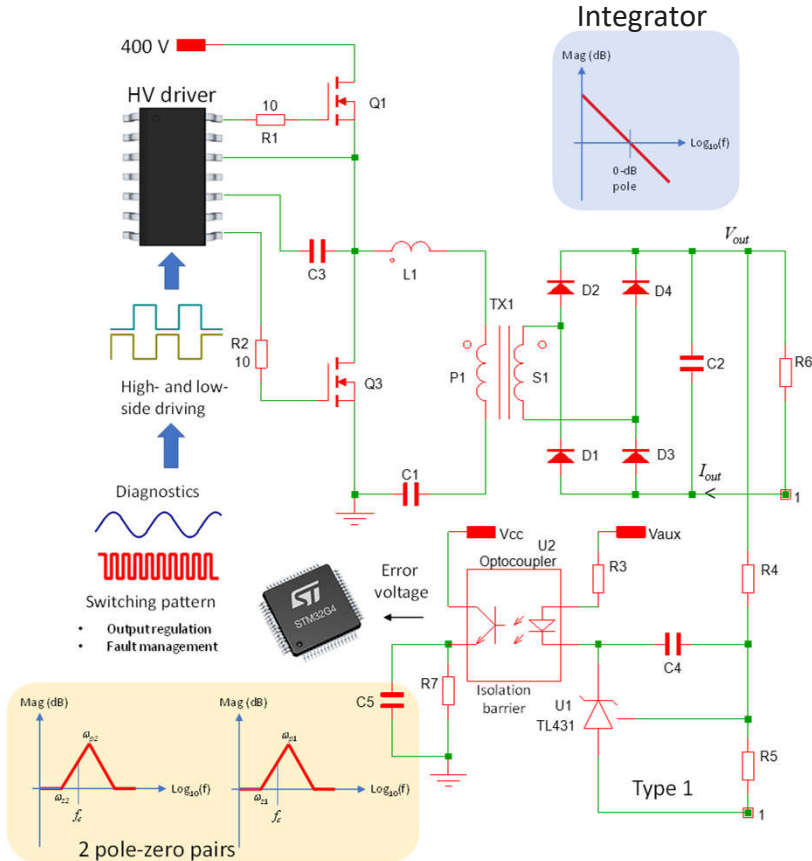

- The adopted solution combines an analogue front-end with a digital compensator
- ✓ The analogue section offers a high dc gain with a pole at the origin
- ✓ A low-cost TL431 coupled with an optocoupler transmits the control signal to the ADC
- ✓ The microcontroller implements a two-zero two-pole digital filter
- ✓ Adjusting the distance between the poles and zeroes sizes the phase boost amount

An Isolated Integrator with TL431

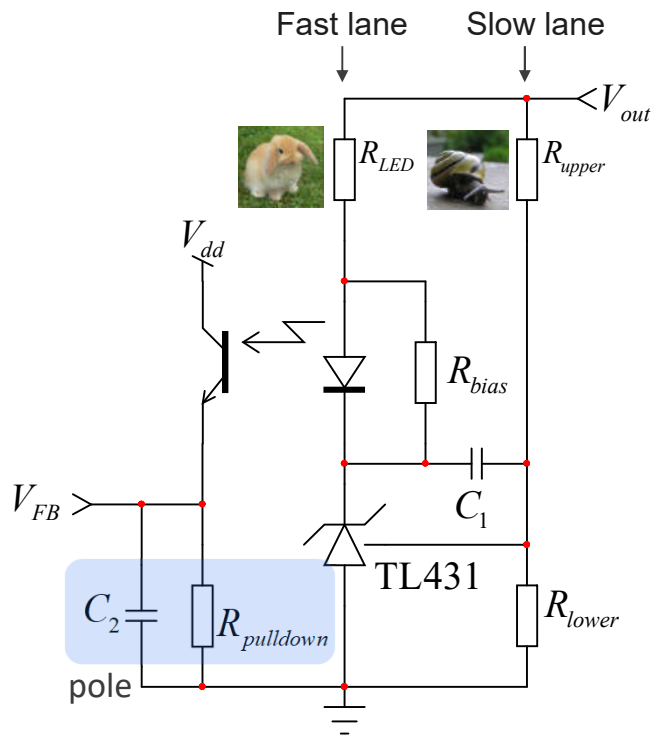- The TL431 configured with a fast lane introduces a zero in the transfer function
- By neutralizing this zero with a pole, an integrator is implemented



$$\frac{V_{FB}(s)}{V_{out}(s)} = -\frac{R_{pull-down} \text{CTR}}{R_{LED}} \left[\frac{1 + sR_{upper}C_1}{sR_{upper}C_1(1 + sR_{pull-down}C_2)} \right]$$

$$sR_{upper}C_1 = sR_{pull-down}C_2 \implies C_1 = \frac{R_{pull-down}}{R_{upper}}C_2$$



$$\omega_{po} = \frac{\text{CTR}}{C_2 R_{LED}} \implies C_2 = \frac{\text{CTR}}{2\pi f_{po} R_{LED}}$$

substitute

$$\implies \omega_{po} = \frac{1}{\frac{R_{upper}R_{LED}}{R_{pull-down} \text{CTR}} C_1}$$

Extending the Optocoupler Bandwidth

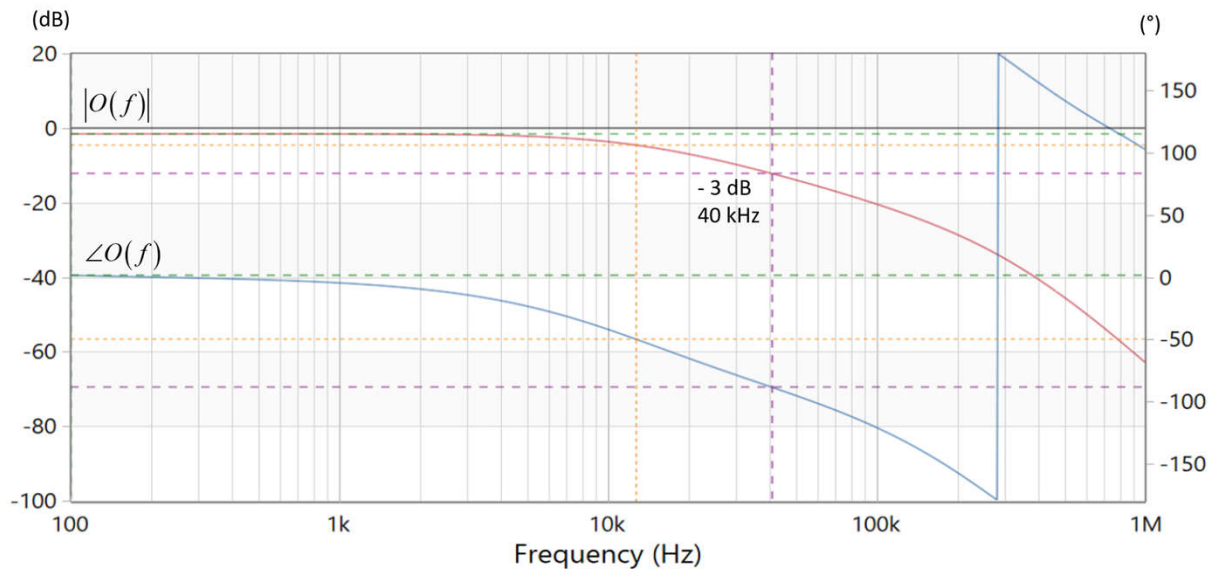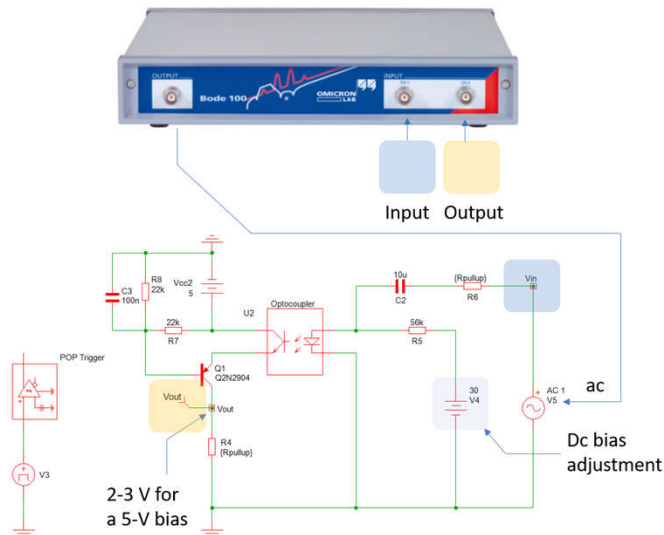- The optocoupler includes a low-frequency pole which hampers the compensation path
- The cascode configuration relegates this pole to higher frequencies





- The pole is located at 40 kHz and would be at ≈ 4 kHz in classic common-collector circuit

The Digital Filter – Two Pole-Zero Pairs


- A type 3 compensator is realized by cascading the integrator with two pole-zero pairs
- These elements are digitally coded and can later be easily modified
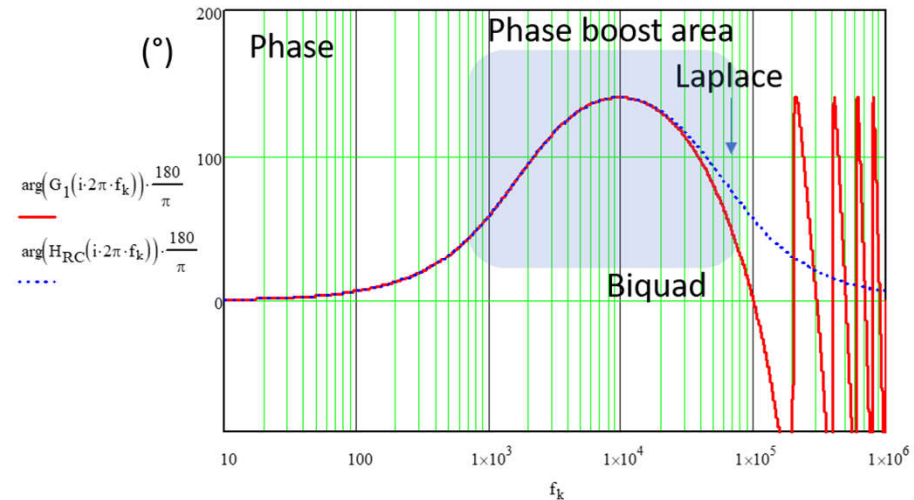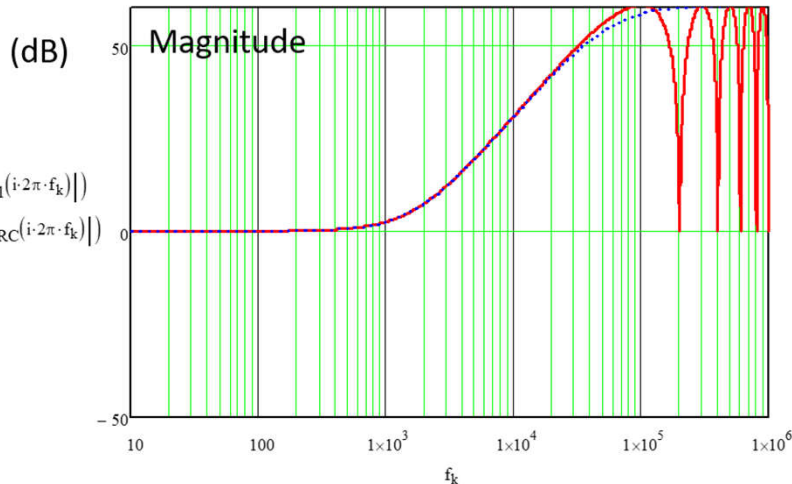
$$H(s) = \left(\frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \right)^2 \xrightarrow{\text{Bilinear transform}} H(z) = \frac{\omega_p^2 (2z + T_s \omega_z + T_s \omega_z z - 2)^2}{\omega_z^2 (2z + T_s \omega_p + T_s \omega_p z - 2)^2} \xrightarrow{\quad} H(z) = \frac{a_0 + a_1 z^{-1} + a_2 z^{-2}}{1 + b_1 z^{-1} + b_2 z^{-2}}$$



Simulating the Compensated Converter

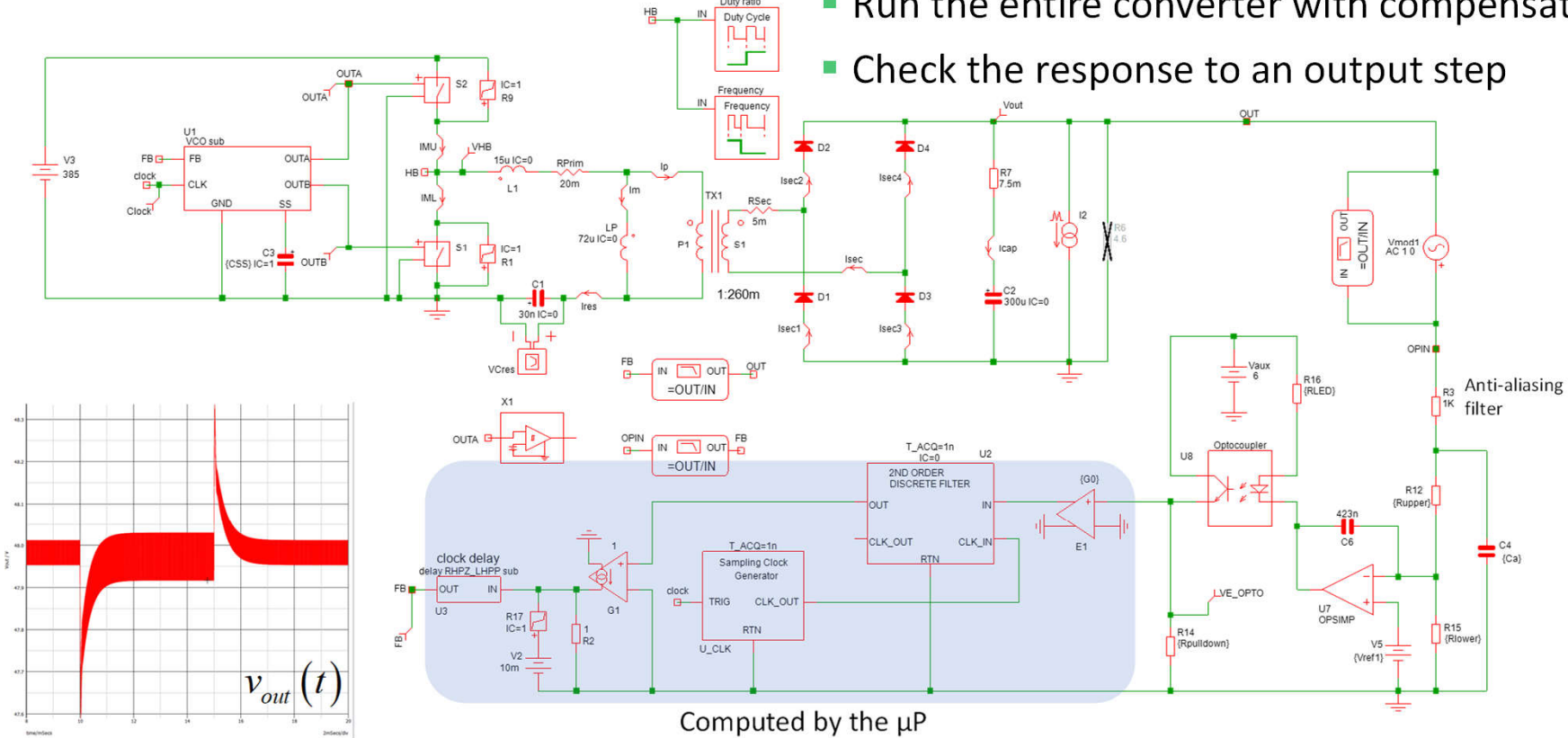- Run the entire converter with compensation
- Check the response to an output step






Output voltage response to the load step, $V_{in} = 385\text{ V}$

The Digital Filter – A modified PID

- It is also possible to adjust coefficients of an existing PID library
- The PID transfer function includes 1 pole at the origin and 2 zeroes
- ✓ Bring k_i to zero and you are left with a dc gain and a zero:

$$H_{PID}(s) = k_p \left(1 + \frac{1}{s\tau_i} + s\tau_d \right) \xrightarrow{\text{Set it to 0}} H_{PID}(s) = k_p (1 + s\tau_d) = H_0 \left(1 + \frac{s}{\omega_z} \right)$$

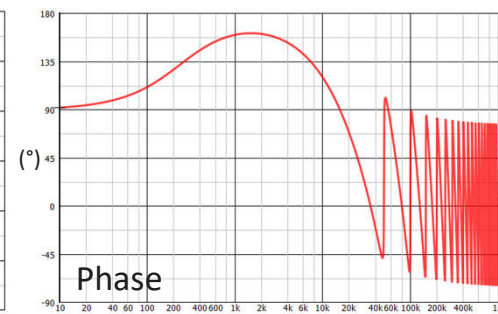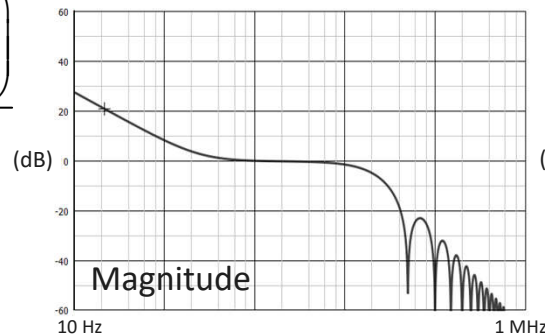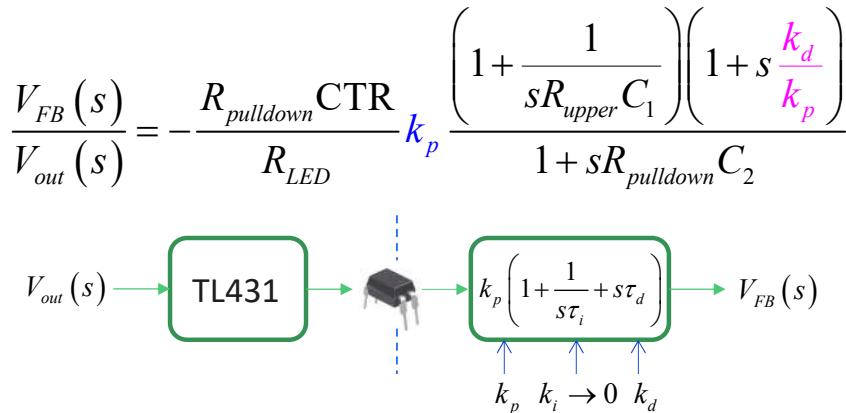
- Combined with the front-end analogue integrator, it breaks the -1-slope to 0:



This is a type 2 compensator

Final Implementation

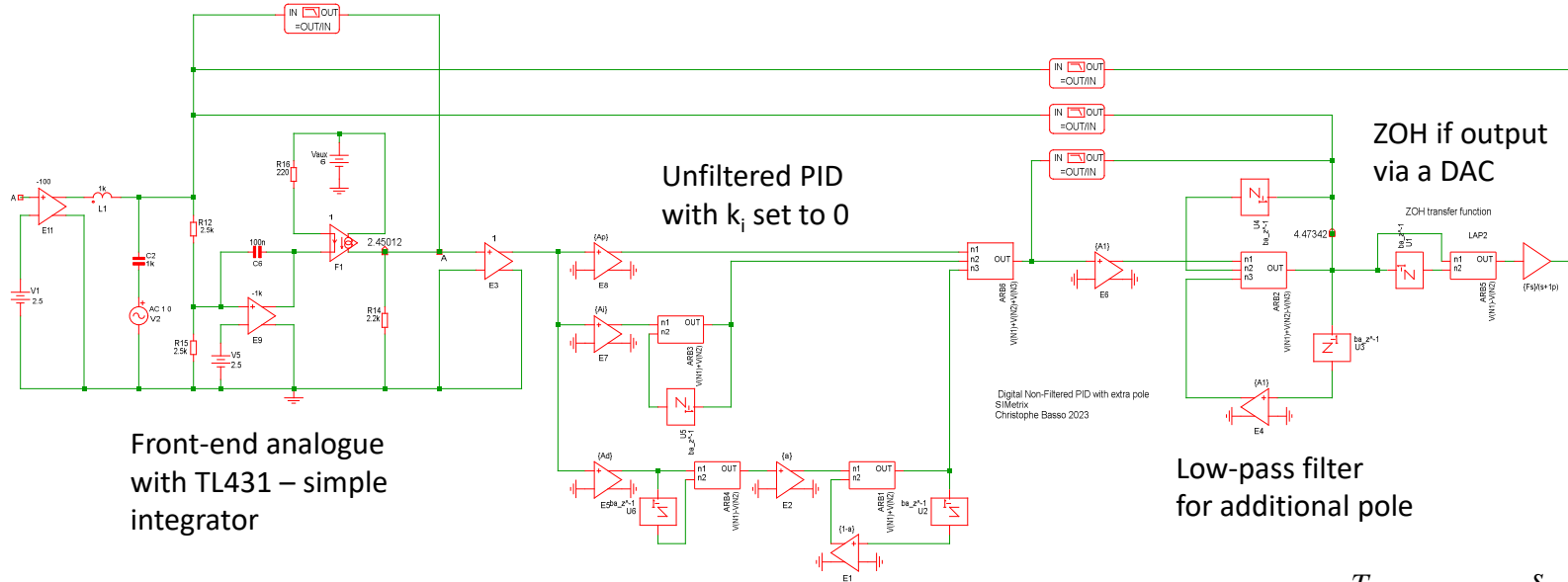- The original sampled PID is supplemented with a pole for filtering purpose
- The zero will be positioned before crossover for boosting the phase



Front-end analogue with TL431 – simple integrator

Unfiltered PID with k_i set to 0

ZOH if output via a DAC

Low-pass filter for additional pole


$$H_{TL431}(s) = \frac{CTR \cdot R_{pulldown}}{R_{LED}} \cdot \frac{1}{s} \cdot \frac{1}{\omega_{po}}$$

$$H_{PID}(s) = k_p \left(1 + \frac{1}{s\tau_i} + s\tau_d \right)$$

$$H_{LP}(s) = \frac{1 + s\frac{T_s}{2}}{1 + sT_s \left(2^n - \frac{1}{2} \right)} = \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$

Frequency Response

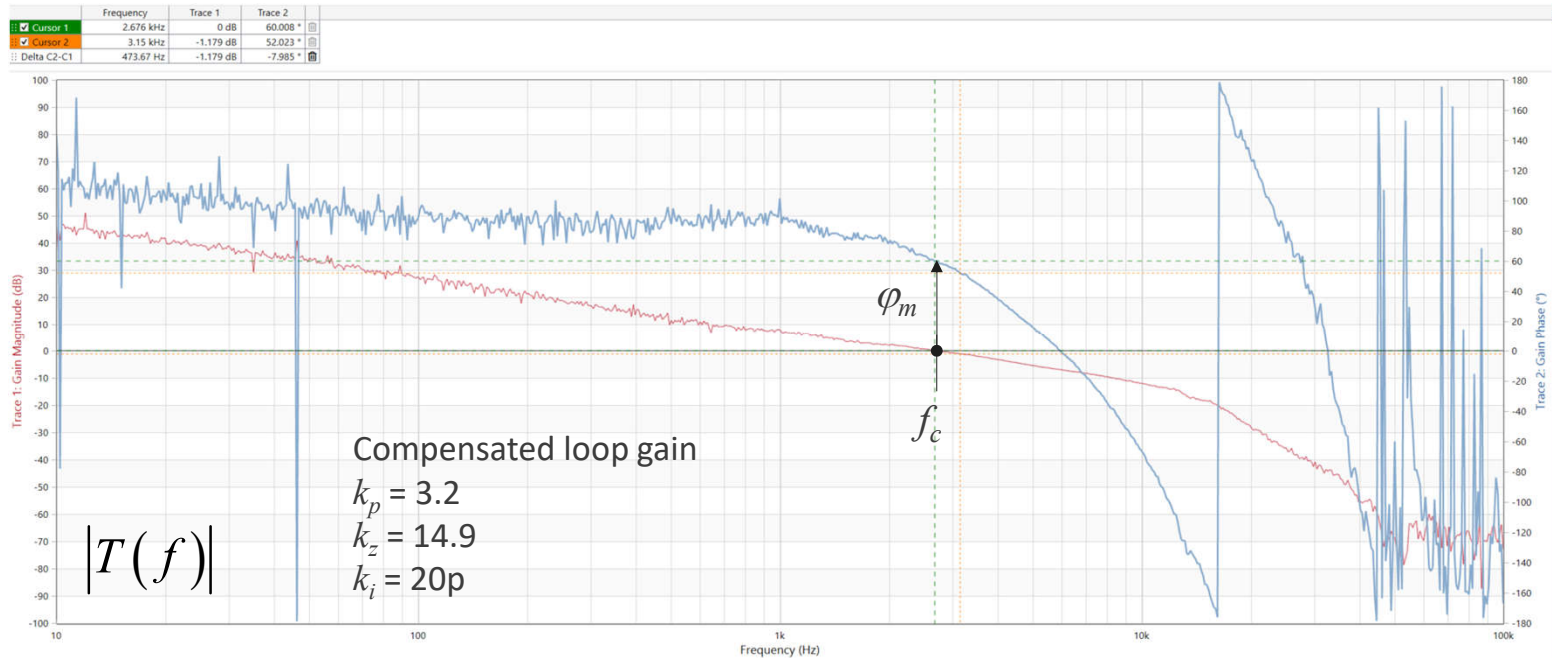- A frequency-response analyzer (FRA) is used to graph the control-to-output response
- Crossover is set to 2.8 kHz and leads to a phase margin of 60°




Agenda


- The LLC Converter
- Controlling the Power Flow
- A Closed-Loop Control System
- Bringing a Microcontroller on Board
- Combining Analogue and Digital
- Practical Implementation
- Conclusion

High-Voltage Stage

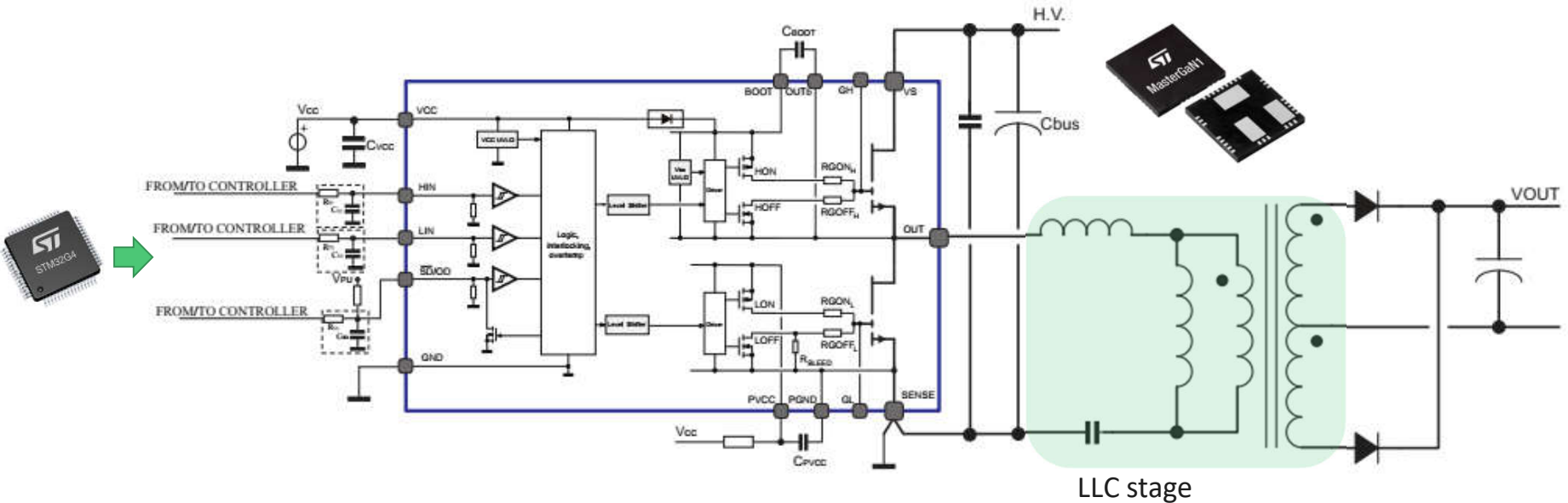- The half-bridge uses a MASTERGAN1 from ST which leads to a compact solution
- ✓ 600-V 150-mΩ $r_{DS(on)}$ GaN transistors with onboard bootstrap diode
- ✓ Least components count when used in an LLC converter




Auxiliary Power Supply

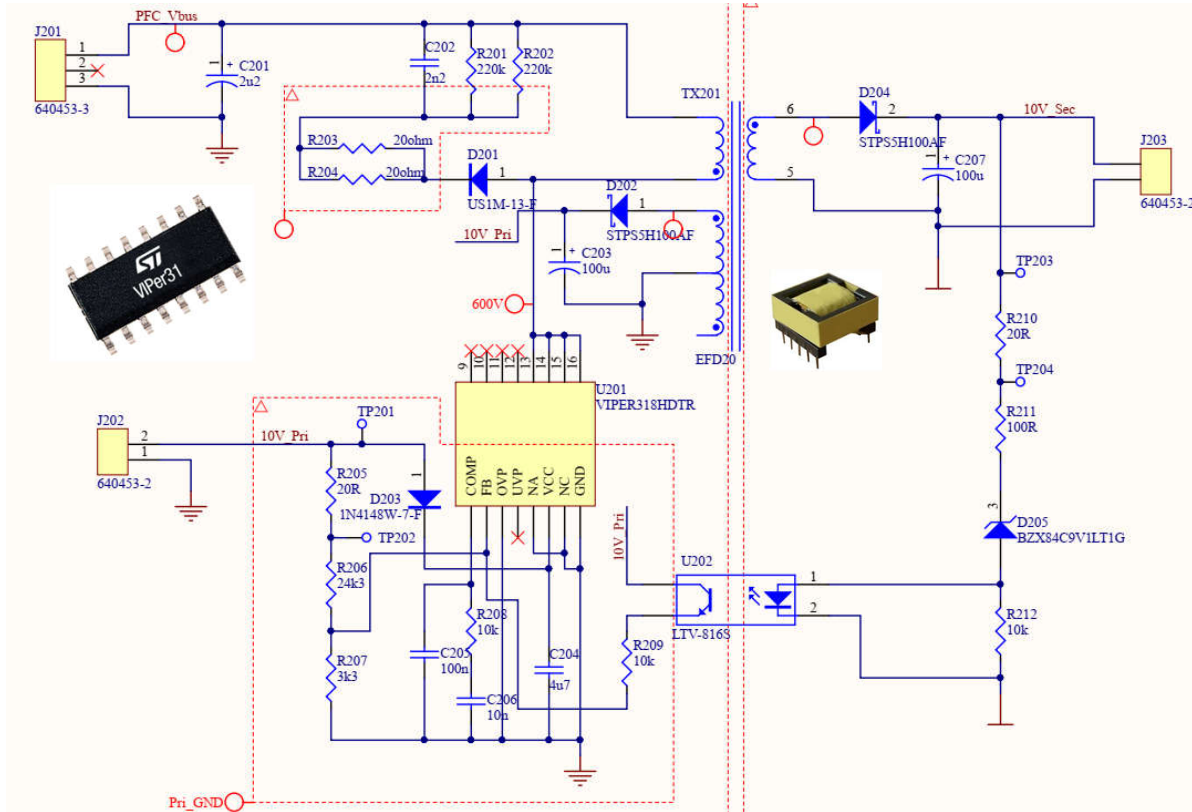

- The 10-V auxiliary power supply feeds the board and provides a voltage for:
 - ✓ Powering the STM32 micro-controller
 - ✓ Biasing the GaN drivers with a 5-V downstream dc-dc
- The flyback delivers a raw voltage whose value is set by a Zener-based loop.


Practical Implementation

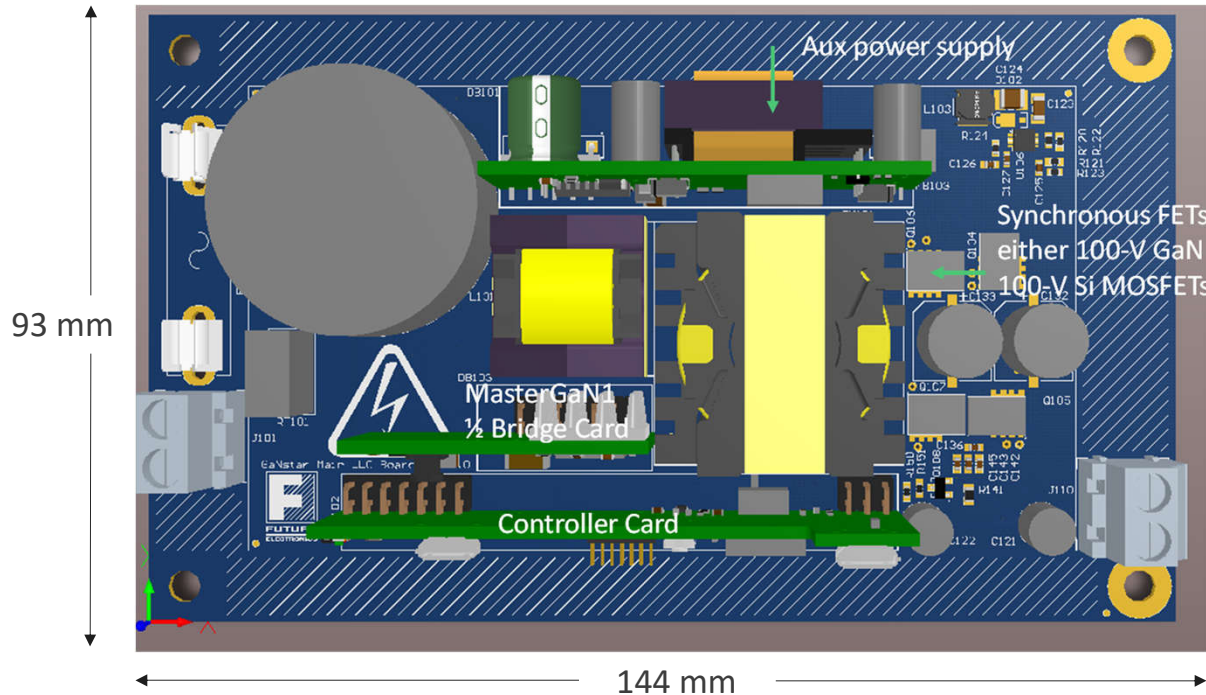- The converter has been assembled in a compact format owing to integrated components
- ✓ A miniature fan has been added for a permanent 500-W power delivery



Thermal Performance

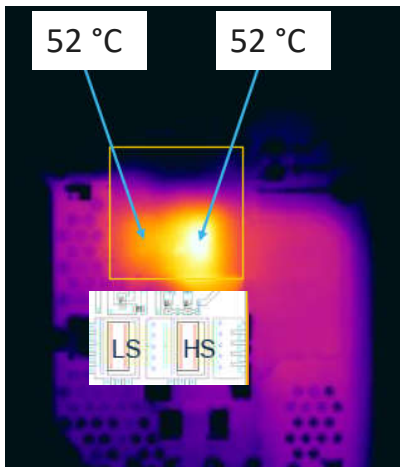- Temperature measurements have been carried on the board with and without fan
- The losses on the MasterGaN half-bridge are kept within safe limits




The dissipated power is very well balanced between the low- and high-side transistors




The power is dissipated through the PCB vias and proper routing is essential to maximize the heat flow to the heatsink on the other side.

With fan, $T_A = 25\text{ °C}$

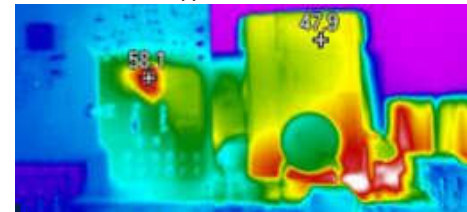

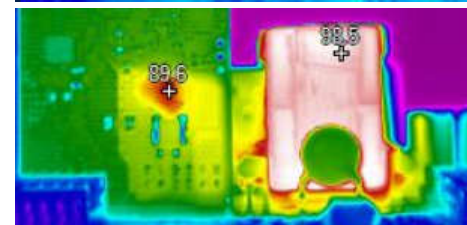$P_{out} = 500\text{ W}$
 $T_{GaN} = 58\text{ °C}$



$P_{out} = 400\text{ W}$
 $T_{GaN} = 90\text{ °C}$

Without fan, $T_A = 25\text{ °C}$

The operating temperature remains in safe limits for a continuous 500-W power with a fan.

Conclusion and Future Work

- A microcontroller placed in the primary side requires an isolated image of V_{out} for regulating
- A fully-isolated amplifier represents an option but is not an option for cost reasons
- The literature reports regulation with a microcontroller based on a type 2 or 3 in the sec. side
- It defeats the possibility to implement a digital control loop in the microcontroller
- We propose an analogue integrator which transmits an isolated error signal to the primary side
- This analogue integrator is supplemented by a digitally-implemented compensation strategy
- Combining both approaches brings the low cost of the analogue option and the flexibility of digital coding.
- The next step is to control a PFC front-end stage with the microcontroller