



ON Semiconductor®

Simulating power supplies with SPICE

presented by Christophe Basso
Product Applications Engineering Director

Pardon his
French!



Seth Bullock

Course agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering
- Conclusion



Course agenda

- Why simulating power supplies?**
 - Average modeling techniques
 - The PWM switch concept, CCM
 - The PWM switch concept, DCM
 - The voltage-mode model at work
 - Current-mode modeling
 - The current-mode model at work
 - Power factor correction
 - Switching models
 - EMI filtering
 - Conclusion



Why simulate Switch Mode Power Supplies?


- Simulation helps feeling how the product behaves before breadboard
- Experiment What If? at any level. Power libraries do not blow!
- Easily shows impact of parameter variations: ESR, Load etc.
- Draw Bode plots without using costly equipments
- Avoid trials and errors: compensate the loop on the PC first!
- Use SPICE to assess current amplitudes, voltage stresses etc.
- Go to the lab. and check if the assumptions were valid.

SPICE does **NOT** replace the breadboard!



Why average simulations?

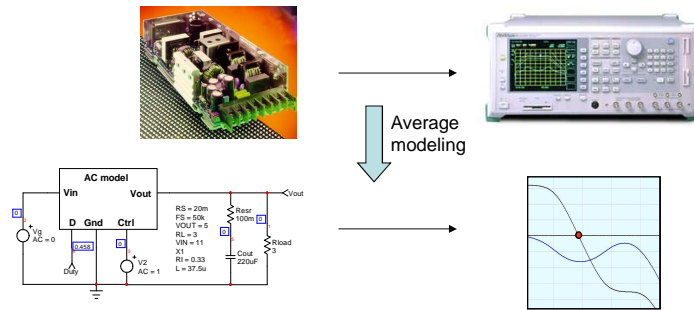- ❑ An average model is made of equations that are continuous in time
- ❑ The switching component has disappeared, leading to:
 - ❖ a simpler ac analysis of the power supply
 - ❖ the study of the stability margins in various conditions
 - ❖ the assessment of the ESRs contributions in the loop stability
 - ❖ a flashing simulation time!




5 • Chris Basso • October 08

ON Semiconductor®



Why switching simulations?

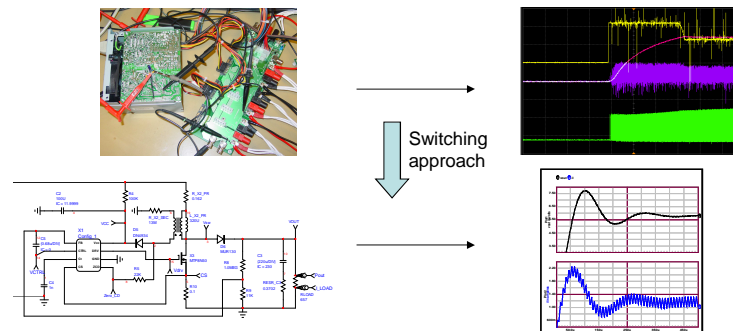- ❑ An switching model is like breadboarding on the PC
- ❑ The switching component is back in place, leading to:
 - ❖ the analysis of current and voltage stresses
 - ❖ the study of leakage and stray elements impacts
 - ❖ the analysis of the input current signature – EMI
 - ❖ a longer simulation time...



6 • Chris Basso • October 08

ON Semiconductor®




Course agenda

- Why simulating power supplies?
- Average modeling techniques**
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering
- Conclusion



Average modeling, the SSA

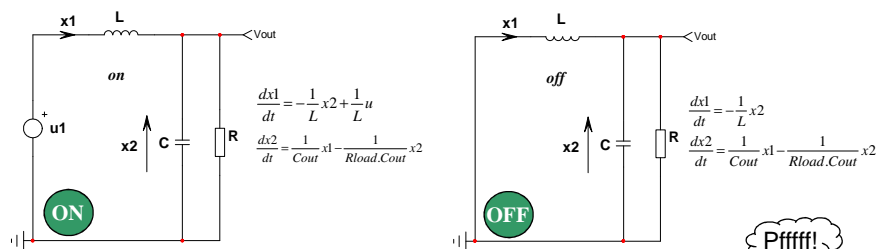- State-Space Averaging (SSA)
- Introduced by Slobodan Ćuk in the 80'
- Long and painful process
- Fails** to predict sub-harmonic oscillations




Apply smoothing process → Linearize ★



Average modeling, the PWM switch

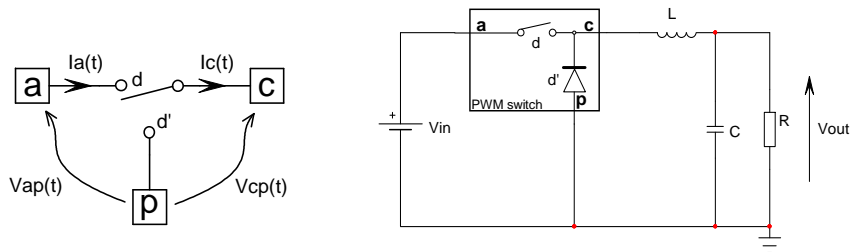- ❑ The PWM Switch
- ❑ Introduced by Vatché Vorperian in the mid-80'
- ❑ Easy to derive and fully invariant
- ❑ **No** auto-toggling mode models
- ❑ **Can** predict sub-harmonic oscillations in CCM
- ❑ DCM model in current-mode was never published!




9 • Chris Basso • October 08

ON Semiconductor®



The PWM switch concept

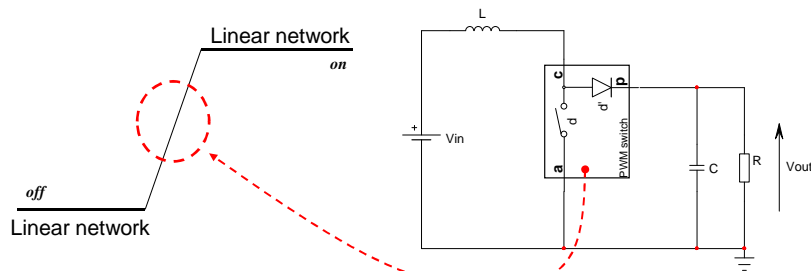- ❑ Identify the guilty network: the transistor and the diode
- ❖ Average their voltage and current waveforms: large-signal model
- ❖ Linearize the equations around a dc point: small-signal model



diode + transistor = guilty for non-linearity!

What do you plead?



10 • Chris Basso • October 08

ON Semiconductor®




Course agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM**
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering
- Conclusion



The PWM switch concept

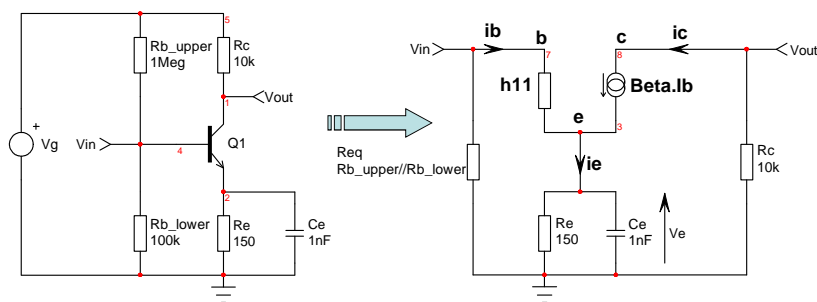- The transistor is a highly non-linear device:
 - ❖ Replace the transistor with its small-signal model
 - ❖ Solve a system of linear equations



Replace Q_1 by its small-signal model




Remember the *bipolars* Ebers-Moll model...



The PWM switch concept

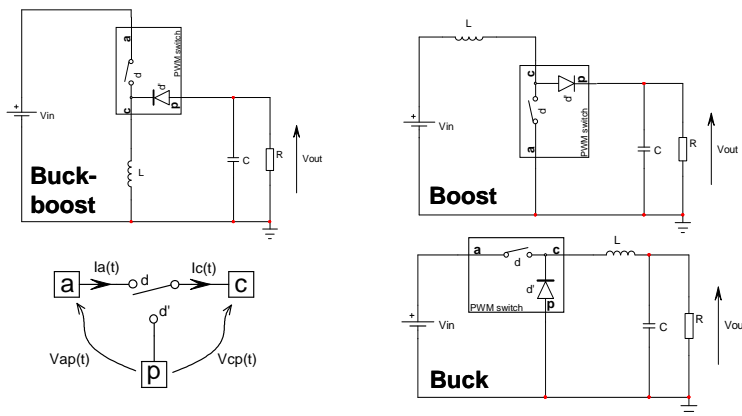- The PWM switch model works in all two switch converters:
- ❖ Rotate the model to match the switch and diode connections
- ❖ Solve a system of linear equations




13 • Chris Basso • October 08

ON Semiconductor



The PWM switch concept

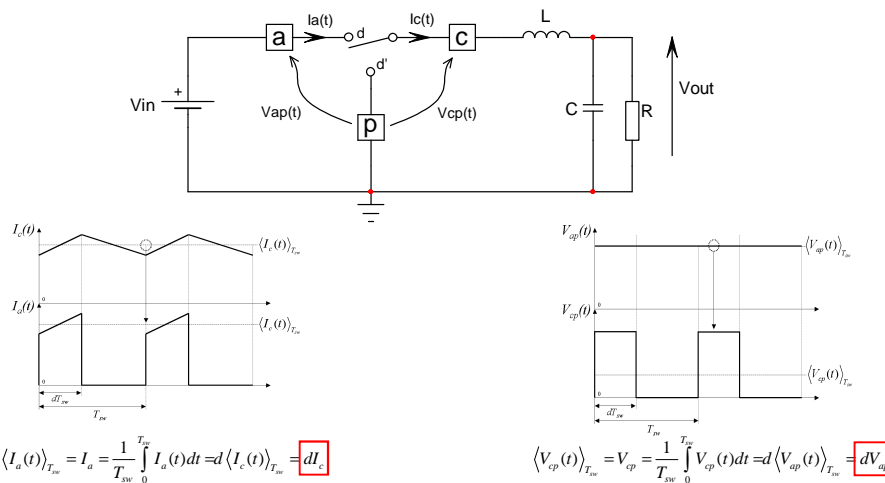- The keyword with average modeling: waveforms averaging




14 • Chris Basso • October 08

ON Semiconductor



The PWM switch concept

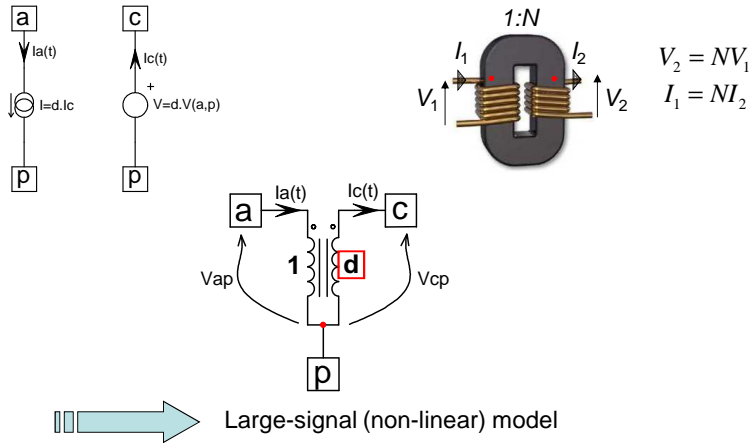- The obtained set of equations is that of a transformer
- A CCM two-switch dc-dc can be modeled like a $1:D$ transformer!




15 • Chris Basso • October 08

ON Semiconductor



The PWM switch concept

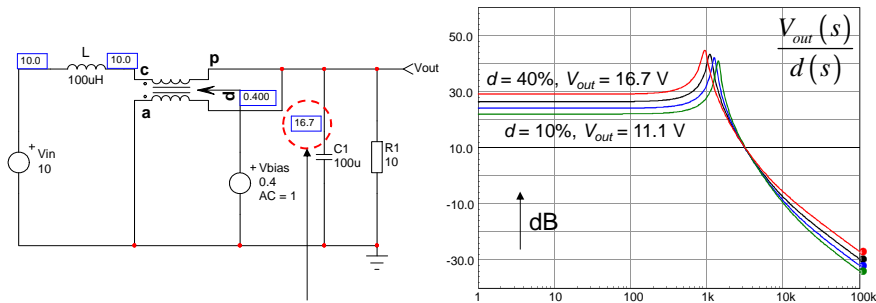- SPICE only deals with linear equations
- It first computes a bias point then it linearizes the network



- No equations, result appears in a second!
- Make sure the bias point is correct...

16 • Chris Basso • October 08

ON Semiconductor



The PWM switch concept

- We have a set of non-linear equations: can't derive transfer functions!
- We need a small-signal model: linearize the equations by hand
- ❖ two options: perturbation or partial derivatives...

Perturbation

$$\begin{aligned}
 I_a &= dI_c & V_{cp} &= dV_{ap} \\
 I_a &= I_{a0} + \hat{i}_a & V_{cp} &= V_{cp0} + \hat{v}_{cp} \\
 I_c &= I_{c0} + \hat{i}_c & d &= d_0 + \hat{d} \\
 d &= d_0 + \hat{d}
 \end{aligned}$$

same

$$I_{a0} + \hat{i}_a = (d_0 + \hat{d})(I_{c0} + \hat{i}_c)$$

$$\begin{aligned}
 I_{a0} &= d_0 I_{c0} & V_{cp0} &= d_0 V_{ap0} \\
 \hat{i}_a &= d_0 \hat{i}_c + \hat{d} I_{c0} & \hat{v}_{cp} &= d_0 \hat{v}_{ap} + \hat{d} V_{ap0}
 \end{aligned}$$

Partial derivatives

$$\begin{aligned}
 I_a &= dI_c & V_{cp} &= dV_{ap} \\
 \hat{i}_a &= \frac{\partial I_a}{\partial I_c} \hat{i}_c + \frac{\partial I_a}{\partial d} \hat{d} & \hat{v}_{cp} &= \frac{\partial V_{cp}}{\partial V_{ap}} \hat{v}_{ap} + \frac{\partial V_{cp}}{\partial d} \hat{d}
 \end{aligned}$$


$$\begin{aligned}
 \hat{i}_a &= d_0 \hat{i}_c + \hat{d} I_{c0} & \hat{v}_{cp} &= d_0 \hat{v}_{ap} + \hat{d} V_{ap0}
 \end{aligned}$$

ac and dc equations ac equations
No dc point



The PWM switch concept

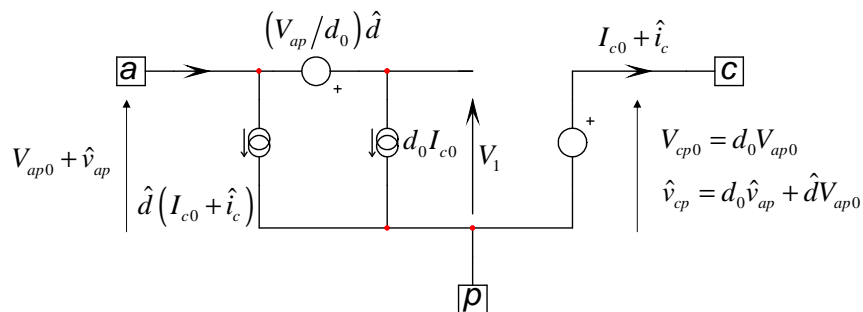- Put the small-signal sources in the large-signal model
- ❖ You obtain the small-signal model of the CCM PWM switch



- You can now analytically find the dc bias and the ac response!




Course agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM**
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering
- Conclusion




The PWM switch in DCM

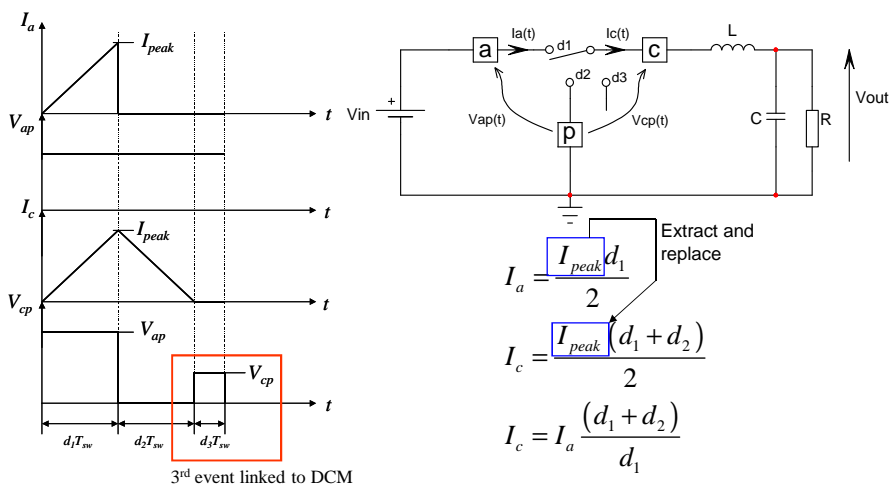- The original model could not be auto-toggling
- A new DCM-CCM model has been derived



The PWM switch in DCM

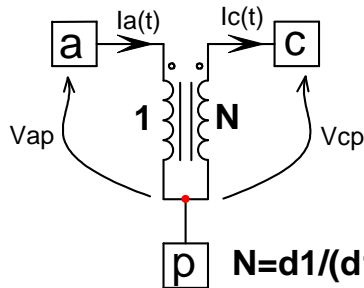- By clamping the d_2 equation, the circuit toggles between the modes



Clamp d_2 :

$$d_2 \text{ CCM} = 1 - d_1$$

$$d_2 \text{ DCM} = 1 - d_1 - d_3$$



$$d_2 < 1 - d_1$$

model is in DCM!

$$d_2 = \frac{2I_c L - V_{ac} d_1^2 T_{sw}}{V_{ac} d_1 T_{sw}} = \frac{2LF_{sw}}{d_1} \frac{I_c}{V_{ac}} d_1$$

Model input




Course agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work**
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering
- Conclusion



The PWM switch in DCM

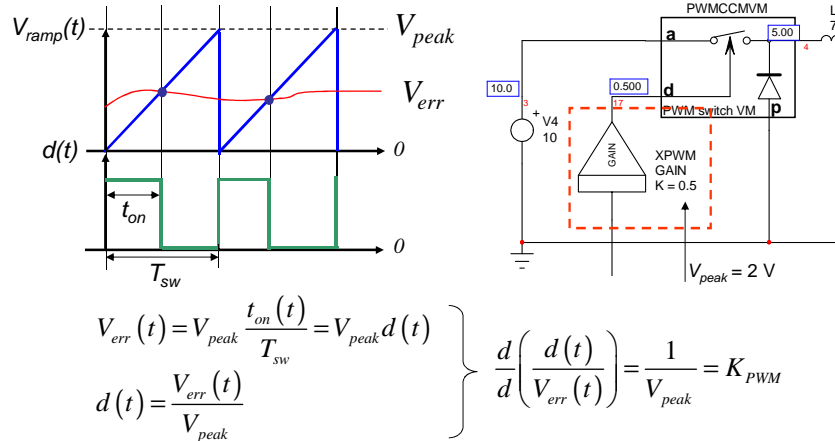- In voltage-mode, the duty-cycle is built with a ramp generator
- The transition occurs when the error voltage crosses the ramp




23 • Chris Basso • October 08

ON Semiconductor



The voltage-mode model at work

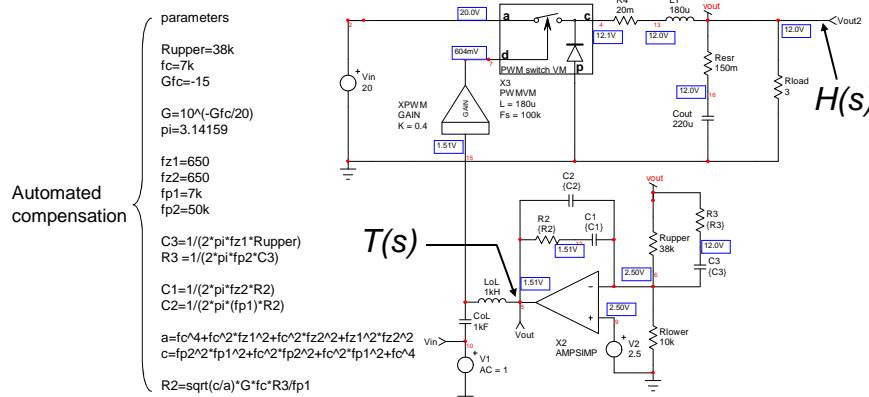- Let us compensate a buck converter operated in CCM and DCM
1. Run an open-loop Bode plot at full load, lowest input
 2. Identify the excess/deficiency of gain at the selected cross over
 3. Place a double zero at f_0 , a pole at the ESR zero and a pole at $F_{sw}/2$
 4. Check final loop gain and run a transient load test




24 • Chris Basso • October 08

ON Semiconductor



The voltage-mode model at work

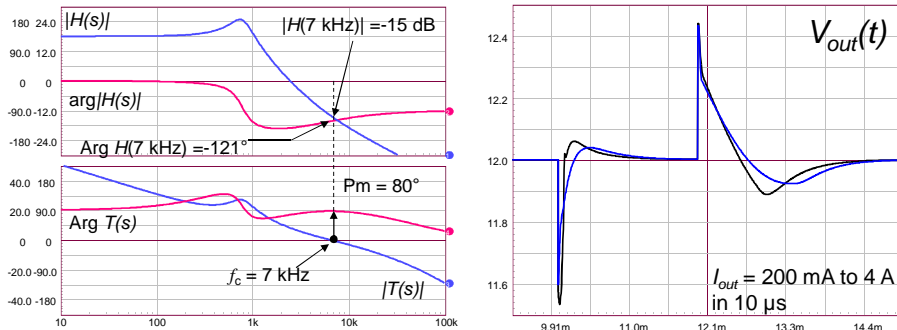- The Bode plot reveals a gain loss of -15 dB at 7 kHz
- The compensator provides a +15 dB gain increase plus phase boost



- The final loop gain shows a comfortable phase margin
- The transient response at both input levels shows a stable signal

25 • Chris Basso • October 08

ON Semiconductor



Course agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling**
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering
- Conclusion


26 • Chris Basso • October 08

ON Semiconductor



Current-mode operation

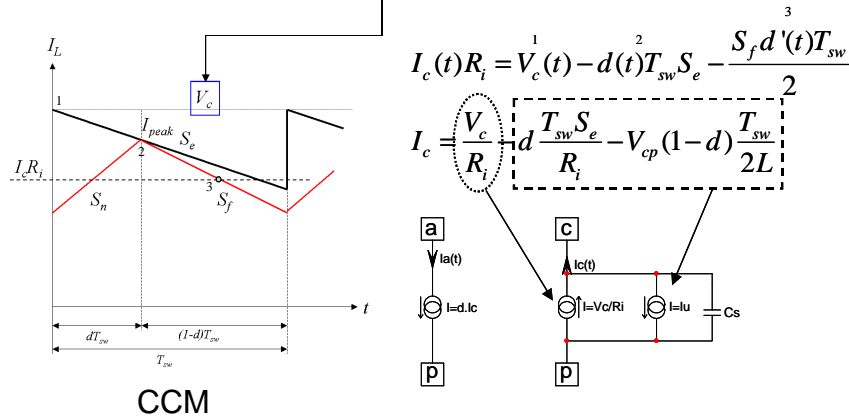- ❑ In voltage-mode, the error signal directly controls the duty cycle
- ❑ In current mode, the error voltage sets the inductor peak current
- ❑ To derive a model, observe the current signals and average them!




27 • Chris Basso • October 08

ON Semiconductor



Current-mode operation

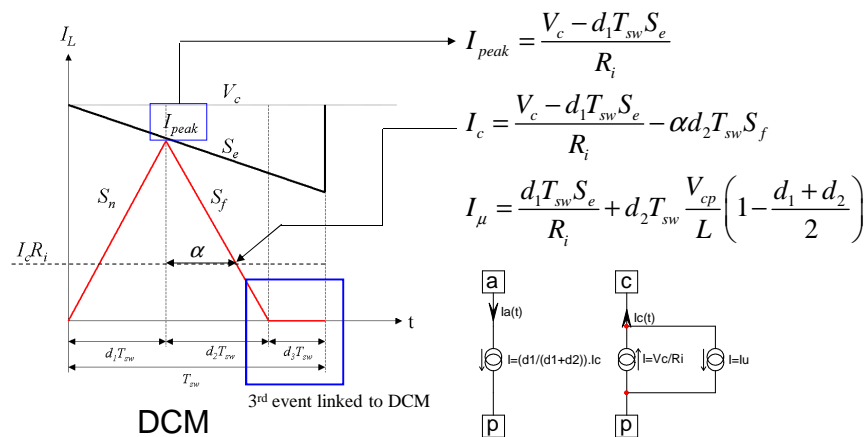- ❑ Do the same for DCM signals
- ❑ Match the previous structure to build a CCM/DCM model



28 • Chris Basso • October 08

ON Semiconductor



Course agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work**
- Power factor correction
- Switching models
- EMI filtering
- Conclusion



The current-mode model at work

- To study a converter, we can write down the equations
- Or use a SPICE simulation to get the Bode plot in a second
- Take the example of a current-mode flyback converter


$$|H(f)| = 20 \log_{10} \left[G_0 \frac{\sqrt{1 + \left(\frac{f}{f_{z1}}\right)^2} \sqrt{1 + \left(\frac{f}{f_{z2}}\right)^2} \sqrt{1 + \left(\frac{f}{f_{z3}}\right)^2}}{\sqrt{1 + \left(\frac{f}{f_p}\right)^2}} \frac{1}{\sqrt{\left(1 - \left(\frac{f}{f_n}\right)^2\right)^2 + \left(\frac{f}{f_n Q_p}\right)^2}} \right]$$

$$\arg H(f) = \tan^{-1}\left(\frac{f}{f_{z1}}\right) - \tan^{-1}\left(\frac{f}{f_{z2}}\right) + \tan^{-1}\left(\frac{f}{f_{z3}}\right) - \tan^{-1}\left(\frac{f}{f_p}\right) - \tan^{-1}\left(\frac{f}{f_n Q_p} \frac{1}{1 - \left(\frac{f}{f_n}\right)^2}\right)$$



Stabilizing a CCM flyback converter

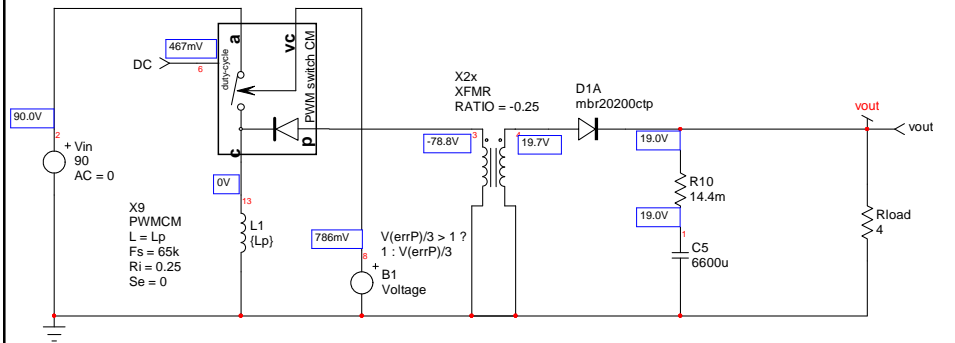- Capture a SPICE schematic with an averaged model



- Look for the bias points values: $V_{out} = 19\text{ V}$, ok
- $V_{setpoint} < 1\text{ V}$, enough margin on current sense


31 • Chris Basso • October 08

ON Semiconductor



Stabilizing a CCM flyback converter

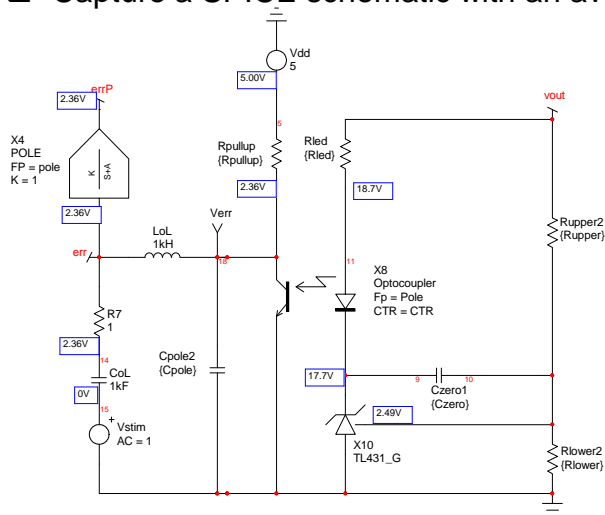- Capture a SPICE schematic with an averaged model



parameters

$V_{out}=19$
 $I_{bridge}=250u$
 $R_{lower}=2.5/I_{bridge}$
 $R_{upper}=(V_{out}-2.5)/I_{bridge}$
 $L_p=350u$
 $S_e=20k$
 $f_c=1k$
 $p_m=60$
 $G_{fc}=-22$
 $p_{fc}=-71$
 $G=10^{-(G_{fc}/20)}$
 $boost=p_m-(p_{fc}-90)$
 $\pi=3.14159$
 $K=\tan((boost/2+45)^{\circ})$
 $F_{zero}=f_c/k$
 $F_{pole}=k*f_c$
 $R_{pullup}=20k$
 $R_{LED}=CTR*R_{pullup}/G$
 $C_{zero}=1/(2^{\circ}\pi^{\circ}F_{zero}*R_{upper})$
 $C_{pole}=1/(2^{\circ}\pi^{\circ}F_{pole}*R_{pullup})$
 $CTR=1.5$
 $Pole=6k$

from Bode


32 • Chris Basso • October 08

ON Semiconductor



Stabilizing a CCM flyback converter

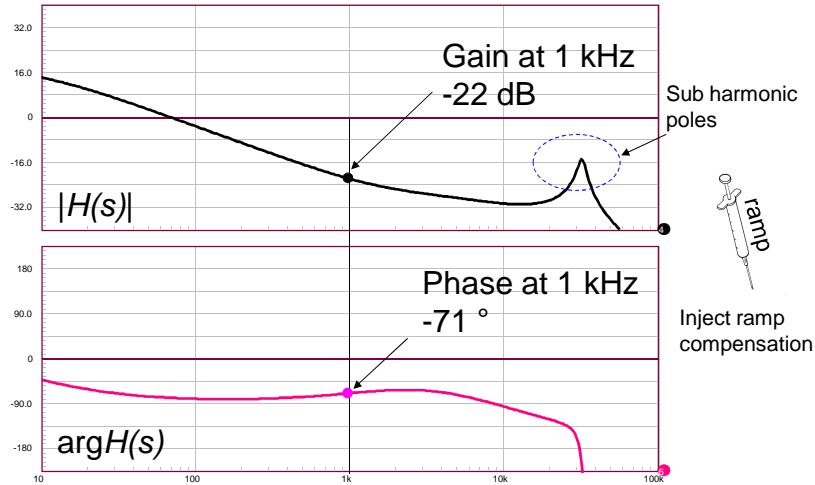- Capture a SPICE schematic with an averaged model



33 • Chris Basso • October 08

ON Semiconductor




Stabilizing a CCM flyback converter

- The easiest way to damp the poles:
 - Calculate the equivalent quality coefficient at $F_{SW}/2$
 - Calculate the external ramp to make Q less than 1

$$Q = \frac{1}{\pi \left(D \frac{S_e}{S_n} + \frac{1}{2} - D \right)} = \frac{1}{3.14 \times (0.5 - 0.46)} = 8$$
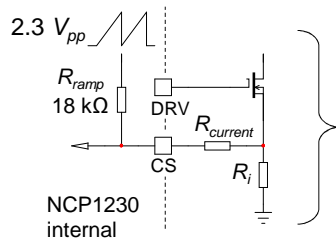
$$S_e = \frac{S_n}{D} \left(\frac{1}{\pi} - 0.5 + D \right) = \frac{V_m R_t}{L_p D} \left(\frac{1}{\pi} - 0.5 + D \right) = \frac{90 \times 0.25}{320 \mu \times (1 - 0.46)} \left(\frac{1}{3.14} - 0.5 + 0.46 \right) = 36 \text{ kV/s}$$



$$M_r = \frac{S_e}{S_n} = \frac{36k}{70k} = 51\% \quad \text{On-time slope } \frac{V_m R_t}{L_p}$$

$$S_{ramp} = \frac{2.3}{15 \mu} = 153 \text{ kV/s}$$

$$R_{current} = \frac{M_r S_n R_{ramp}}{S_{ramp}} = \frac{0.51 \times 70k \times 18k}{153k} = 4.1 \text{ k}\Omega$$


34 • Chris Basso • October 08

ON Semiconductor



Stabilizing a CCM flyback converter

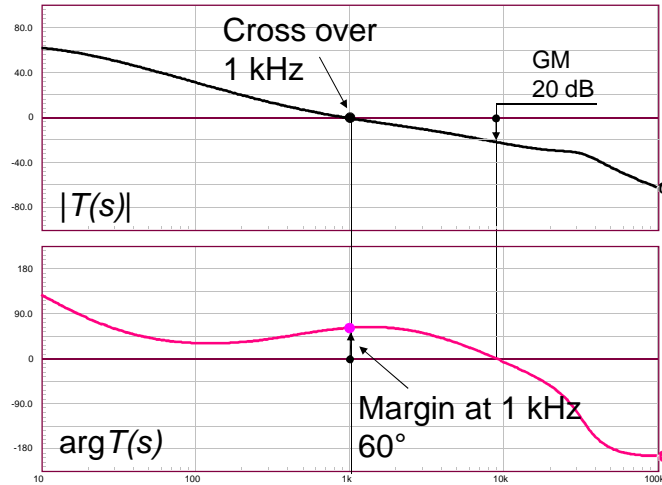- Boost the gain by +22 dB, boost the phase at f_c




35 • Chris Basso • October 08

ON Semiconductor®



Stabilizing a CCM flyback converter

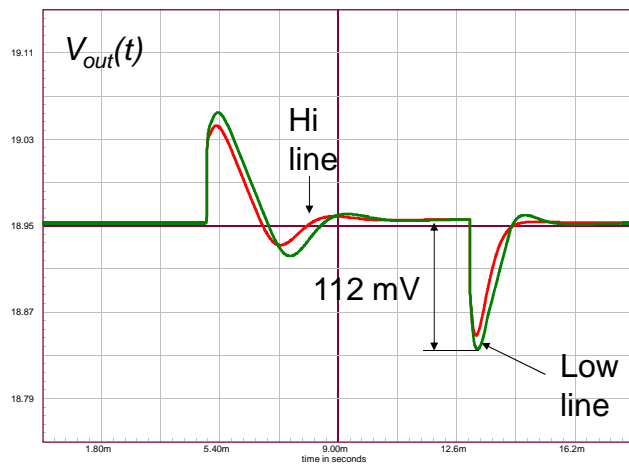- Test the response at both input levels, 90 and 265 Vrms
- Sweep ESR values and check margins again



Excellent!



36 • Chris Basso • October 08

ON Semiconductor®



Course agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- Power factor correction**
- Switching models
- EMI filtering
- Conclusion



37 • Chris Basso • October 08

ON Semiconductor



Power Factor Correction

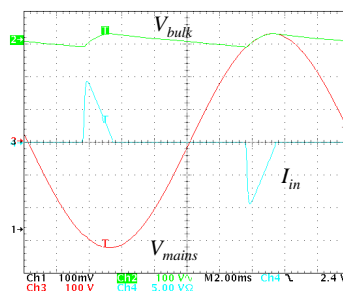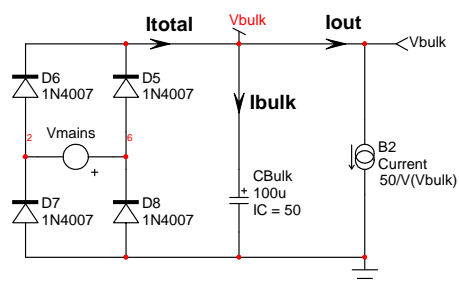- The bulk capacitor connects to a low-impedance source
- At the bulk capacitor refueling, a narrow peak current flows
- This peak conveys a large harmonic content




38 • Chris Basso • October 08

ON Semiconductor



Power Factor Correction

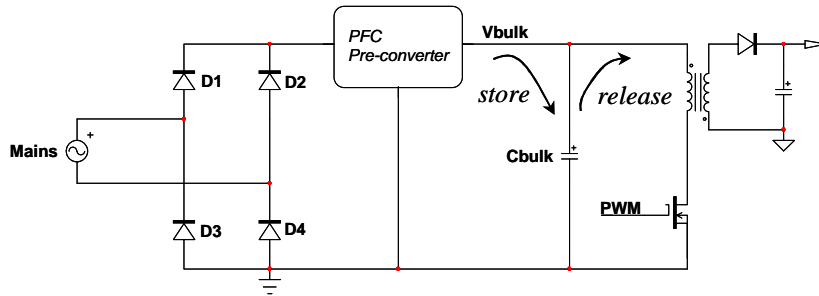- ❑ A pre-converter is installed as a front-end section
- ❑ The pre-converter draws a sinusoidal current
- ❑ The energy is stored and released in/by the bulk capacitor




39 • Chris Basso • October 08

ON Semiconductor®



Power Factor Correction

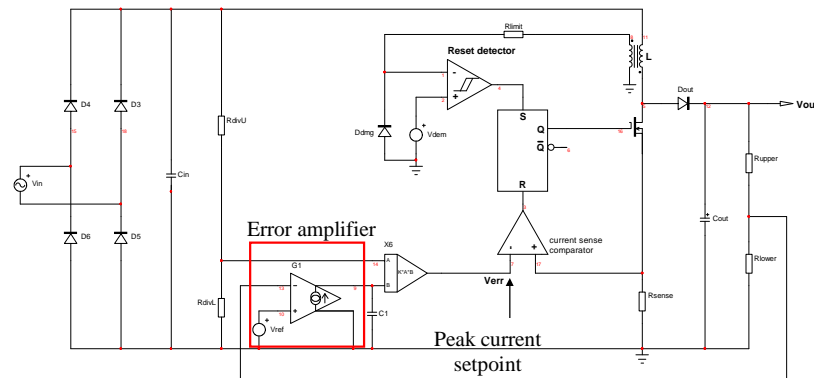- ❑ One of the most popular technique uses Borderline mode
- ❑ The MC33262 operates in peak current mode control



- ❑ The NCP1606 also operates in constant-on time


40 • Chris Basso • October 08

ON Semiconductor®



Power Factor Correction

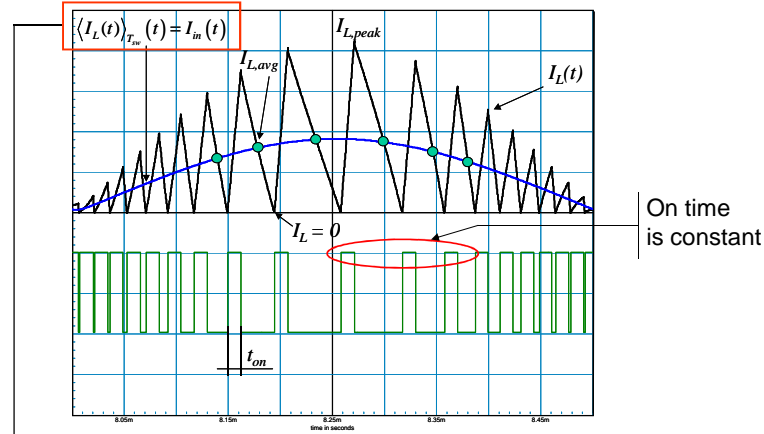
- ❑ The core is always reset from cycle to the other



- ❑ the average inductor current is half the inductor peak current value


Power Factor Correction

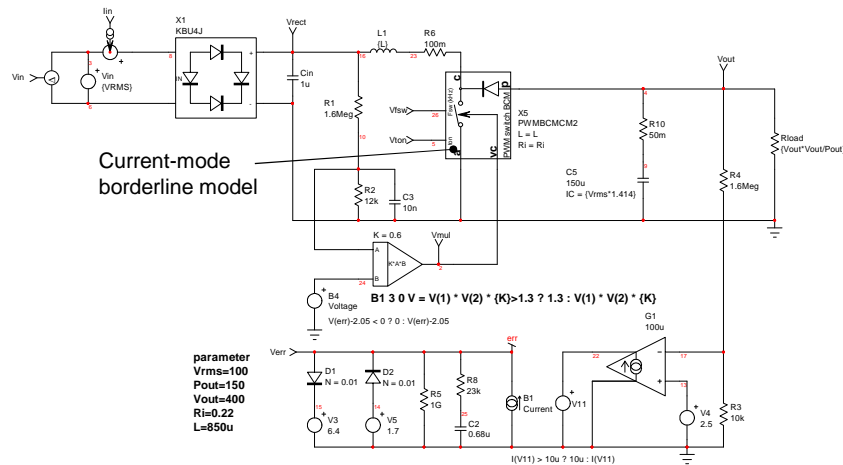- ❑ A 150-W BCM PFC average example with the MC33262



Power Factor Correction

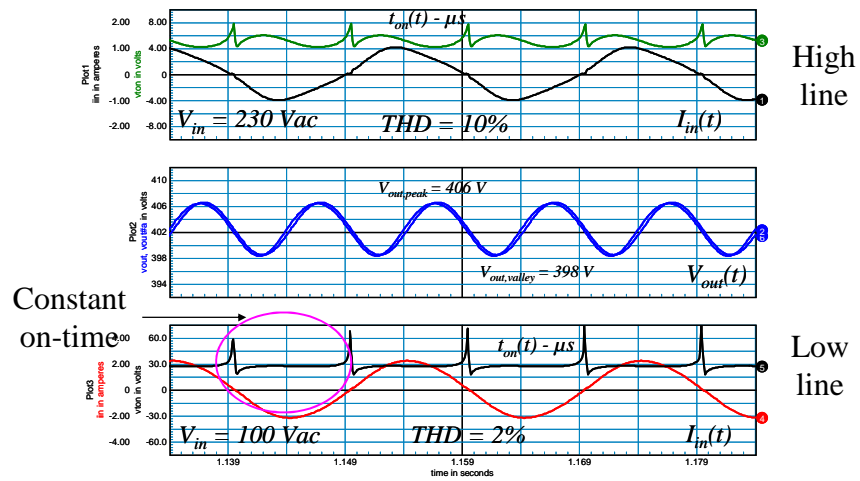- Average models can also work in transient conditions




43 • Chris Basso • October 08

ON Semiconductor



Power Factor Correction

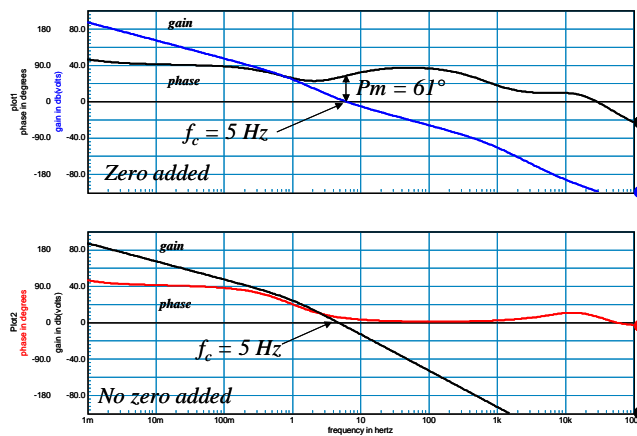- Use the model to boost the phase at the cross over point




44 • Chris Basso • October 08

ON Semiconductor



Power Factor Correction

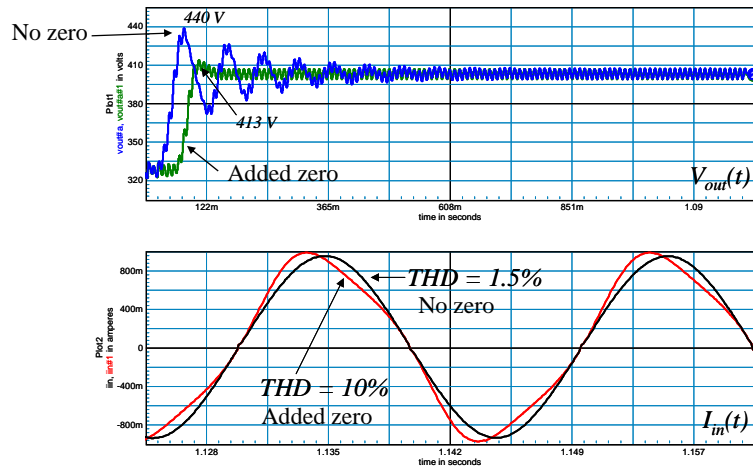- ❑ The zero improves the overshoot but degrades the THD...



45 • Chris Basso • October 08

ON Semiconductor



Course agenda

- ❑ Why simulating power supplies?
- ❑ Average modeling techniques
- ❑ The PWM switch concept, CCM
- ❑ The PWM switch concept, DCM
- ❑ The voltage-mode model at work
- ❑ Current-mode modeling
- ❑ The current-mode model at work
- ❑ Power factor correction
- ❑ **Switching models**
- ❑ EMI filtering
- ❑ Conclusion


46 • Chris Basso • October 08

ON Semiconductor



Switching models, the breadboard on PC

- Turn your PC into a virtual breadboard

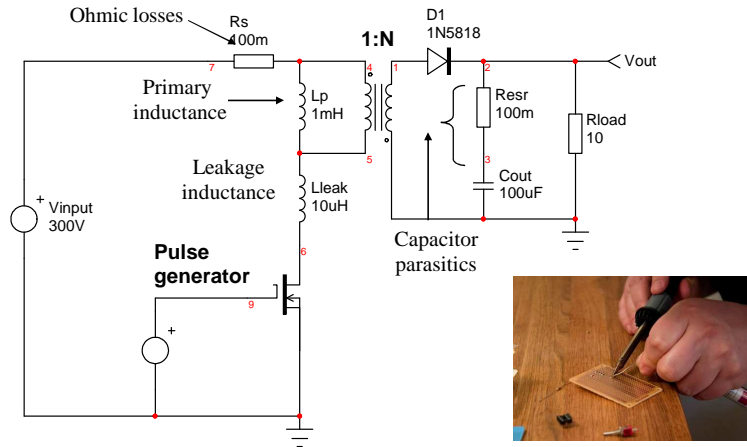


47 • Chris Basso • October 08

ON Semiconductor

Switching models, the breadboard on PC

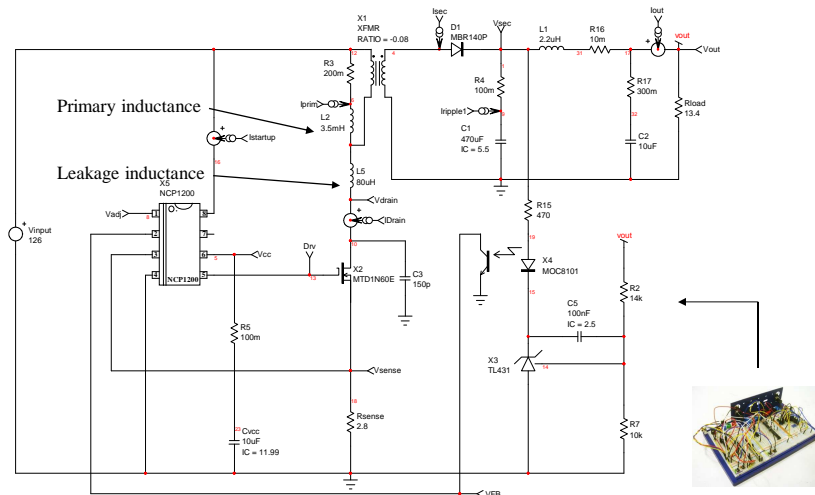- Wire your device as you would do in the lab.




48 • Chris Basso • October 08


ON Semiconductor

Simulations (really) work!!

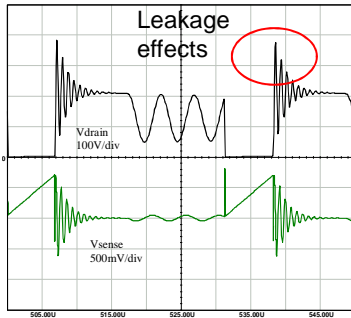- ❑ Assess the average, rms currents in your circuit
- ❑ Check if enough margins exist on your semiconductors



simulated

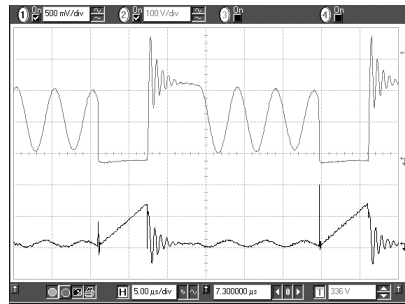

measured


49 • Chris Basso • October 08

ON Semiconductor




Simulations (really) work!!

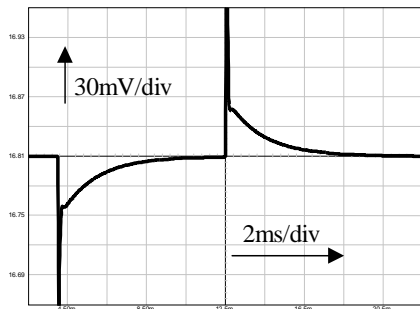- ❑ With accurate models, the simulation results are excellent
- ❑ You can then vary the parasitic terms and see their impact



simulated

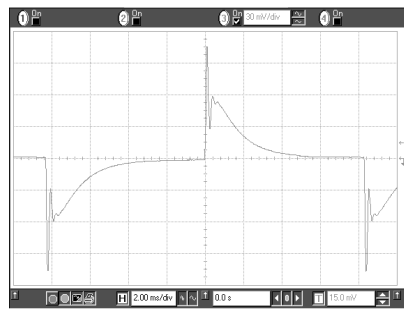

measured

50 • Chris Basso • October 08

ON Semiconductor




Course agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering**
- Conclusion




EMI filtering on a dc-dc

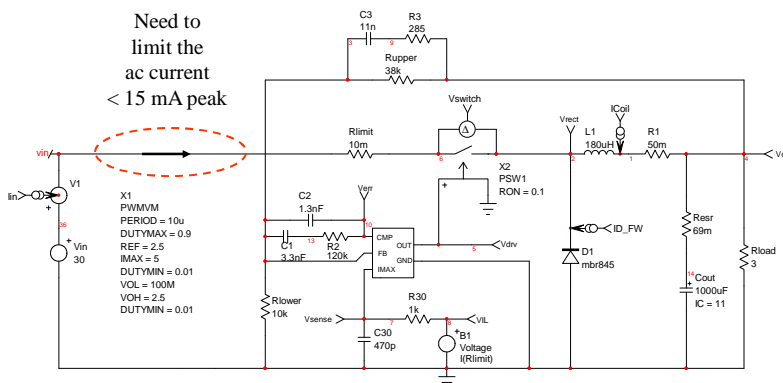- Dc-dc are highly EMI polluting systems
- A filter has to be installed to avoid noise in the source



EMI filtering on a dc-dc

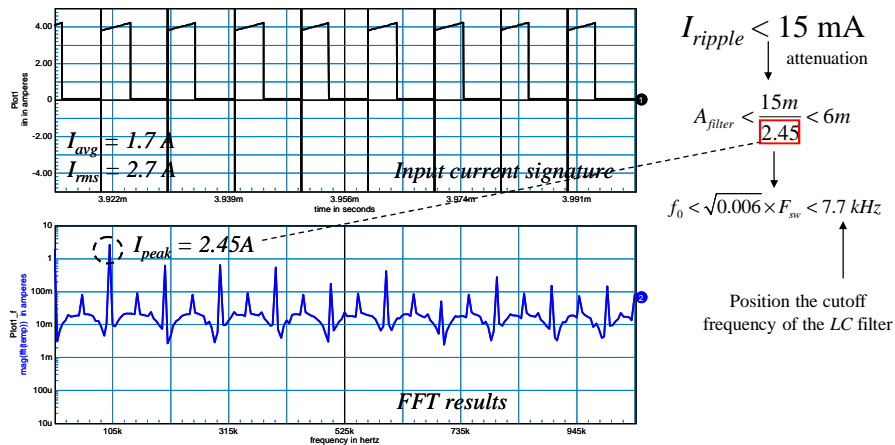- ❑ Use SPICE to extract the current signature
- ❑ Run Fourier analysis to look at the spectrum




53 • Chris Basso • October 08

ON Semiconductor



EMI filtering on a dc-dc

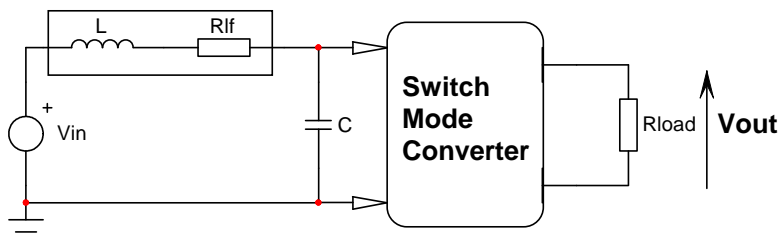- ❑ A LC configuration offers the best efficiency
- ❑ As any LC network, it is subject to resonances



$$L = 100 \mu\text{H}$$

$$C = \frac{1}{4\pi^2 f_0^2 L} = 5.2 \mu\text{F}$$

↑
7.7 kHz

→ Check
impedance
peaking

$$\|Z_{outFILTER}\|_{max} = \frac{Z_0^2}{R_1} \sqrt{1 + \left(\frac{R_1}{Z_0}\right)^2}$$


54 • Chris Basso • October 08

ON Semiconductor



EMI filtering on a dc-dc

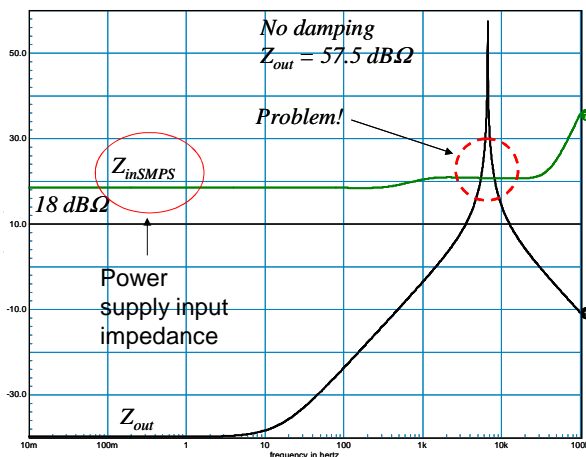- ❑ The incremental input resistance of a dc-dc in negative
- ❑ A LC filter loaded by a negative resistance can oscillate!




Need to damp this!



EMI filtering on a dc-dc

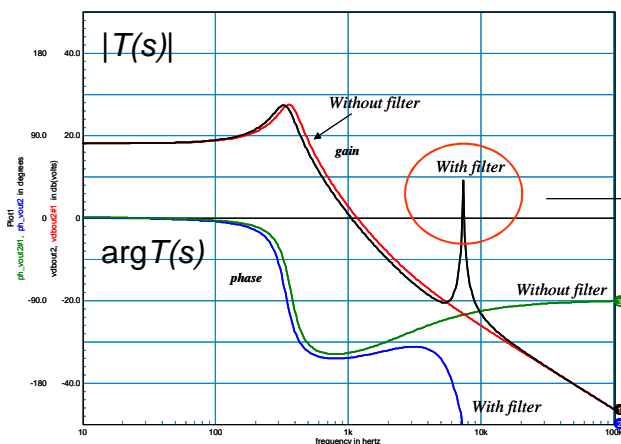- ❑ If the resonance is too peaky, problems can arise




Not stable!



EMI filtering on a dc-dc

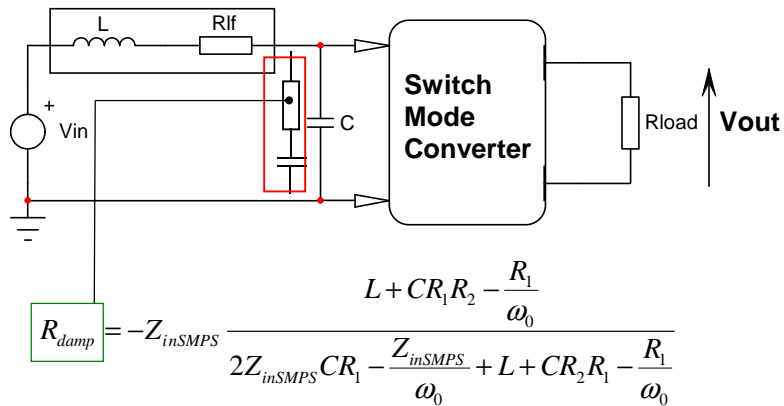- ❑ A resistor is damping the LC filter by creating losses
- ❑ A dc-block capacitor is installed to limit dissipation




57 • Chris Basso • October 08

ON Semiconductor®



EMI filtering on a dc-dc

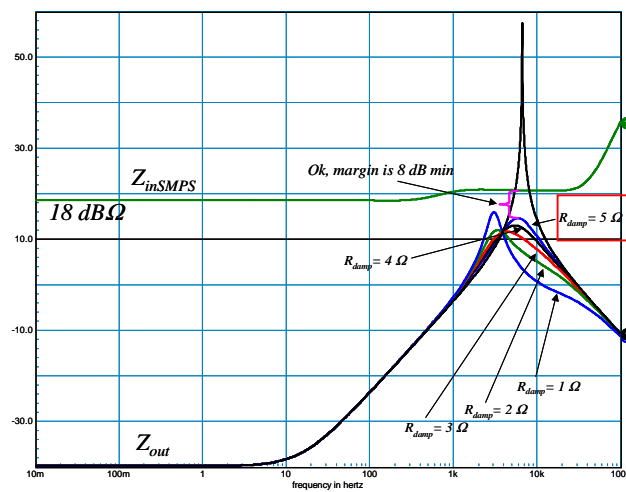- ❑ The right resistor prevents the overlaps between curves




58 • Chris Basso • October 08

ON Semiconductor®



EMI filtering on a dc-dc

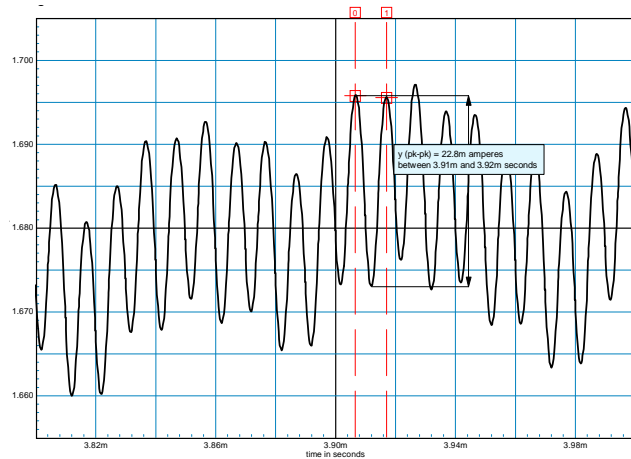- ❑ A final check shows a noise amplitude under control




59 • Chris Basso • October 08

ON Semiconductor

A book on power supply design

- ❑ To learn more about power supplies and simulations...

886 pages, 8 chapters

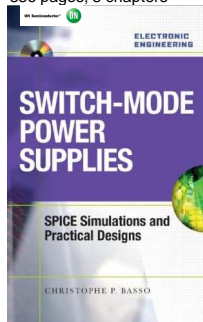

- ❑ Learn dc-dc converters theory
- ❑ Understand average modeling
- ❑ Feedback and loop control
- ❑ Design examples of dc-dc and ac-dc
- ❑ Power Factor Correction
- ❑ Chapters on flyback and forward converters
- ❑ Supplied CDROM with working examples

I already have ideas for the next edition!!



60 • Chris Basso • October 08

ON Semiconductor

Conclusion

- SPICE can be seen as a design companion
- It shields us from going through complex equations
- Simulation time is short and PC helps to run tests
- Use SPICE before going to the bench: NO trial and error!
- Once the simulation is stable, build the prototype
- Simulations and laboratory debug: the success recipe!

