



ON Semiconductor®


Small-Signal Analysis of the Constant Peak Current-Operated Flyback Converter in Frequency Foldback

Christophe Basso



Reducing the Switching Frequency

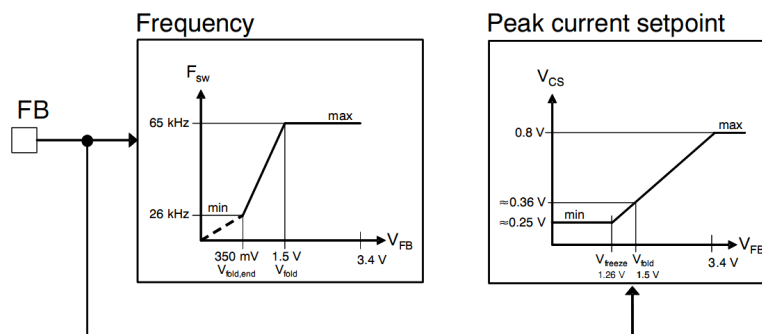- ❑ New generation controllers reduce frequency in light load
- ❑ The peak current is frozen and frequency is controlled




- ❑ The relationship between \hat{v}_{out} and \hat{i}_p is known at constant F_{sw}
- ❑ What about the relationship linking \hat{v}_{out} to \hat{F}_{sw} at I_{peak} constant?



Where do We Start From?

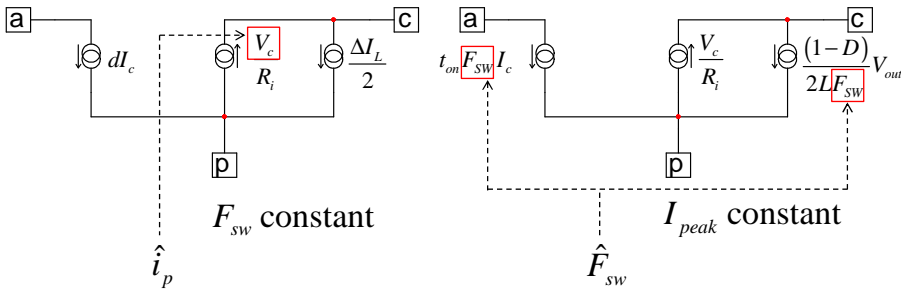- We have a DCM peak-current mode control large-signal model
- The PWM switch controls the peak current at a fixed F_{sw}
- Why not fixing the peak current and controlling F_{sw} ?




- The peak current is frozen and the frequency is controlled



A Transient Load Step Response First

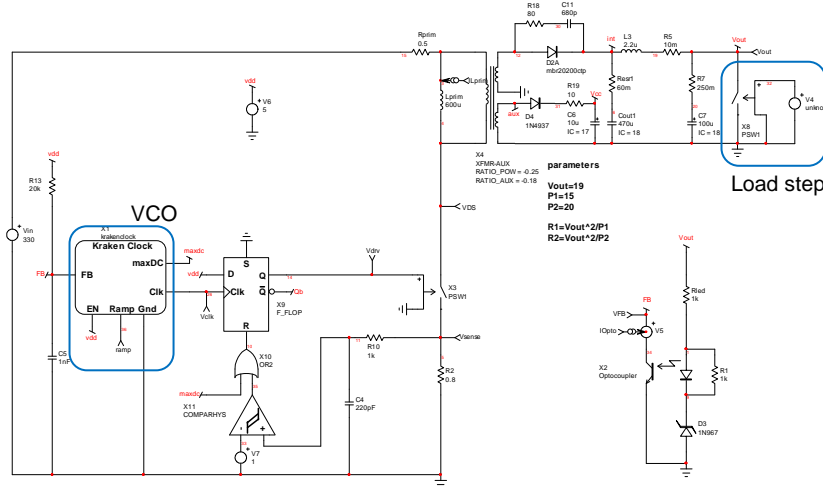- We can check the cycle-by-cycle response to a load step




Cycle by cycle model

$F_{sw} = 51$ kHz



A Transient Load Step Response First

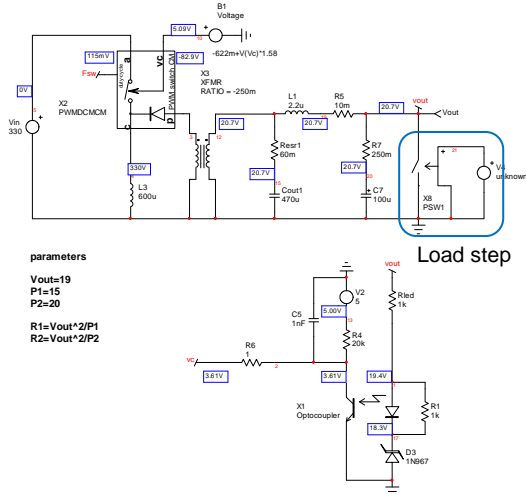- And compare it to that of a modified PWM switch model



`.param {Vc}=1` Current frozen to $1/R_{sense}$

```
Bdc dcx 0 V =
{Vc}*V(Fsw)*10k/((Se)+(abs(v(a,c))*(Ri))/(L)+1u)
Xdc dcx dc limit params: clampH=0.99
clampL=7m
BVcp 6 p V=(V(dc)/(V(dc)+V(d2)))^V(a,p)
Blap a p I=(V(dc)/(V(dc)+V(d2)))^I(VM)
Bd2 d2X 0 V=(2*(VM)*L)-
v(a,c)*V(dc)^2*1/(V(Fsw)*10k) / (
+v(a,c)*V(dc)*1/(V(Fsw)*10k)+1u)
Xd2 d2X dc d2 limit2
Rdum1 dc 0 1Meg
Rdum2 vc 0 1Meg
RS 7 c 1u
VM 6 7
.ENDS
```

Modified netlist of the PWM switch

$F_{sw} = 50.9 \text{ kHz}$

Averaged model


5 • Chris Basso

ON Semiconductor



You Need to Adjust the VCO Modulator

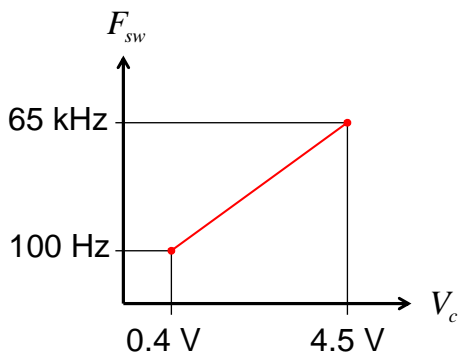- The control voltage to the switching frequency is the VCO gain



$$y = ax + b$$

$$y = \frac{\Delta F_{sw}}{\Delta V_c} = \frac{64.9k}{4.1} = 15.8 \text{ kHz/V}$$

$$100 = ax + b = 0.4 \times 15.8k + b$$

Scaling factor $\downarrow 1/10000$

$$b = 0.10 - 0.4 \times 15.8 = -622 \text{ mV}$$

$$V_{Fsw} \leftarrow \times 10k \leftarrow -0.622 + 15.8 \times V_{FB} \leftarrow V_{FB}$$

VCO gain G_{VCO} is 15.8 kHz/V


6 • Chris Basso

ON Semiconductor




Compare the Transient Responses

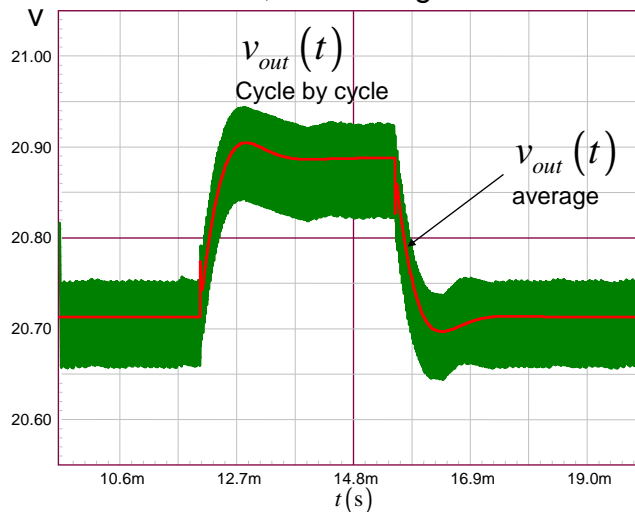- ☐ Responses are identical, the averaged version looks correct



Keys of Small-Signal Analysis

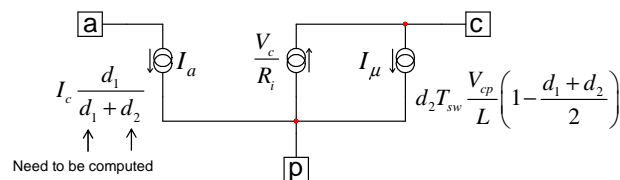- ☐ Rather than going full speed into small-signal analysis:
 - break down the system into smaller parts
 - run simplifications whenever you can
 - go step by step and verify the answer always fits the original



Start from here, DCM model

"Switch-mode Power Supplies: SPICE Simulations and Practical Designs", C. Basso, McGraw-Hill 2008, page 161

Simplifying and Compacting the Model

- Compact the DCM model to suppress variables computing

$$I_a = I_c \frac{d_1}{d_1 + d_2} \quad I_\mu = \frac{d_2 V_{cp}}{F_{sw} L_p} \left(1 - \frac{d_1 + d_2}{2} \right) \quad d_1 = \frac{L_p V_c F_{sw}}{V_{ac} R_i} \quad d_2 = \frac{2 I_c F_{sw} L_p}{d_1 V_{ac}} d_1$$

substitute



"Let the craziness begin"

$$I_a = I_c \frac{d_1}{d_1 + d_2}$$


$$I_a = \frac{F_{sw} L_p V_c^2}{2 R_i^2 V_{ac}}$$

$$I_\mu = - \frac{V_{cp} (V_c - I_c R_i) (F_{sw} L_p V_c^2 - 2 I_c R_i^2 V_{ac})}{F_{sw} L_p R_i V_c^2 V_{ac}}$$




The New Model Looks Simpler

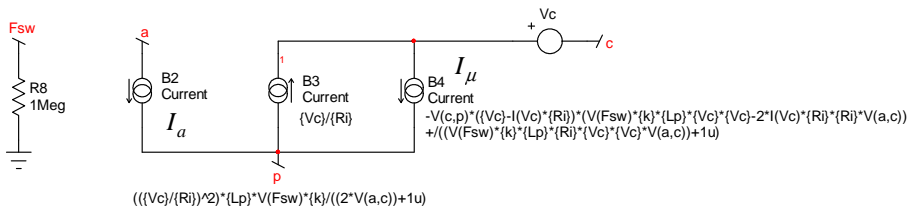- The equations no longer include a computed variable




Check against the complete model

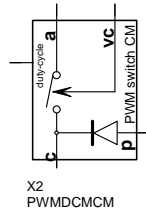

Ac Responses are Similar

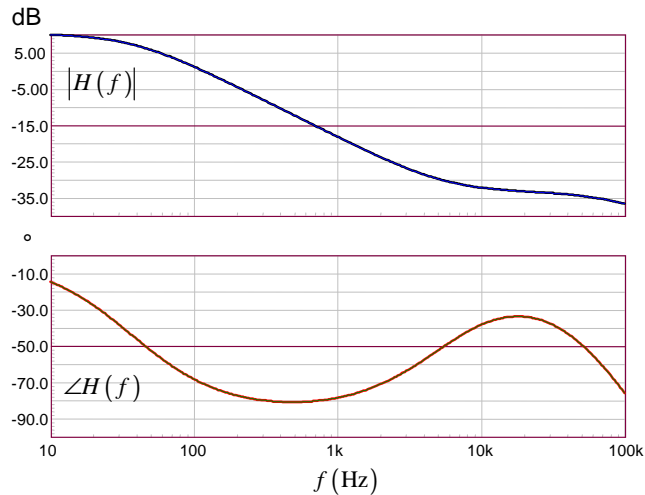- The curves perfectly superimpose, 1st step is ok



Second Step, Linearize the Sources

- To apply Laplace equations, we need linear elements
- Linearization can be done in different ways:
 - ✓ perturb all equations with a small quantity (the "hat" notation)
 - ✓ re-arrange the terms and collect dc and ac contributors
 - ❖ can be tedious to re-arrange, you neglect cross products

$$V_1 = R_1 I_1 + D V_3$$

$$V_1 + \hat{v}_1 = R_1 (I_1 + \hat{i}_1) + (\hat{d} + D)(V_3 + \hat{v}_3)$$

$$V_1 = R_1 I_1 + D V_3 \quad \text{dc equation (bias point)}$$

$$\hat{v}_1 = R_1 \hat{i}_1 + \hat{d} V_3 + \hat{d} \hat{v}_3 + D \hat{v}_3 \quad \text{ac equation}$$

$\hat{d} \hat{v}_3 \approx 0$

Second Step, Linearize the Sources

- A second option is to calculate partial derivative coefficients
- ✓ the process can be automated by Mathcad®
- ✓ you only have ac terms, no sort needed

$$V_1(I_1, D, V_3) = R_1 I_1 + D V_3$$

$$dV_1 = \left(\frac{\partial V_1(I_1, D, V)}{\partial I_1} \right) \Big|_{D, V_3} dI_1 + \frac{\partial V_1(I_1, D, V)}{\partial D} \Big|_{I_1, V_3} dD + \frac{\partial V_1(I_1, D, V)}{\partial V_3} \Big|_{D, I_1} dV_3$$

$$\hat{v}_1 = \frac{\partial V_1(I_1, D, V)}{\partial I_1} \Big|_{D, V_3} \hat{i}_1 + \frac{\partial V_1(I_1, D, V)}{\partial D} \Big|_{I_1, V_3} \hat{d} + \frac{\partial V_1(I_1, D, V)}{\partial V_3} \Big|_{D, I_1} \hat{v}_3$$

$$\hat{v}_1 = R_1 \hat{i}_1 + D \hat{v}_3 + \hat{d} V_3$$

ac equation, no cross products



Second Step, Linearize the Sources

- Now, identify the variables in each source

$$I_a = \frac{F_{sw} L_p V_c^2}{2R_i^2 V_{ac}} \longrightarrow \frac{F_{sw}}{V_{ac}}$$


$$I_\mu = - \frac{V_{cp} (V_c - I_c R_i) (F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw} L_p R_i V_c^2 V_{ac}} \longrightarrow \frac{V_{cp}}{V_{ac}}, \frac{F_{sw}}{I_c}$$

- 6 variables imply six partial derivatives, 6 coefficients
- You must identify these static variables first
- Look at the PWM switch configuration



Identify the Variables in the Schematic

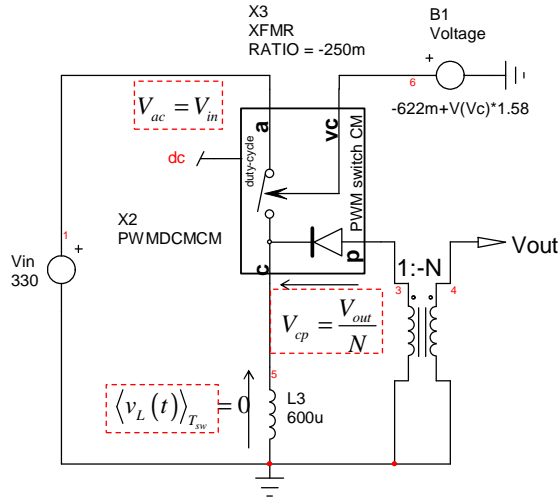- the average voltage across L_3 is 0: point c is grounded.



Sources Derivation

- We can now individually derive all these sources

$$I_a = \frac{F_{sw} L_p V_c^2}{2R_i^2 V_{ac}} \quad \hat{i}_a = \left(\frac{\partial I_a}{\partial F_{sw}} \right)_{V_{ac}} \hat{F}_{sw} + \left(\frac{\partial I_a}{\partial V_{ac}} \right)_{F_{sw}} \hat{v}_{ac}$$

$$k_1 = \frac{L_p V_c^2}{2R_i^2 V_{ac}} \quad k_2 = -\frac{F_{sw} L_p V_c^2}{2R_i^2 V_{ac}^2}$$

$$I_\mu = -\frac{V_{cp} (V_c - I_c R_i) (F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw} L_p R_i V_c^2 V_{ac}}$$

$$\hat{i}_\mu = \left(\frac{\partial I_\mu}{\partial V_{cp}} \right)_{I_c, F_{sw}, V_{ac}} \hat{v}_{cp} + \left(\frac{\partial I_\mu}{\partial I_c} \right)_{F_{sw}, V_{cp}, V_{ac}} \hat{i}_c + \left(\frac{\partial I_\mu}{\partial F_{sw}} \right)_{I_c, V_{cp}, V_{ac}} \hat{F}_{sw} + \left(\frac{\partial I_\mu}{\partial V_{ac}} \right)_{V_{cp}, I_c, F_{sw}} \hat{v}_{ac}$$

$$k_3 \quad k_4 \quad k_5 \quad k_6$$



Sources Derivation

Yes, Mathcad® or an equivalent software is of great help...

$$k_3 = -\frac{(V_c - I_c R_i)(F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw} L_p R_i V_c^2 V_{ac}}$$

$$k_4 = \frac{V_{cp}(F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw} L_p V_c^2 V_{ac}} + \frac{2R_i V_{cp}(V_c - I_c R_i)}{F_{sw} L_p V_c^2}$$

$$k_5 = \frac{V_{cp}(V_c - I_c R_i)(F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw}^2 L_p R_i V_c^2 V_{ac}} - \frac{V_{cp}(V_c - I_c R_i)}{F_{sw} R_i V_{ac}}$$

$$k_6 = \frac{V_{cp}(V_c - I_c R_i)(F_{sw} L_p V_c^2 - 2I_c R_i^2 V_{ac})}{F_{sw} L_p R_i V_c^2 V_{ac}^2} + \frac{2I_c R_i V_{cp}(V_c - I_c R_i)}{F_{sw} L_p V_c^2 V_{ac}}$$



Evaluate all These Coefficients

Select a converter at a certain operating point

$$V_{out} = 21.1 \text{ V}$$

$$R_{load} = 18 \ \Omega$$

$$R_i = 0.8 \ \Omega$$

$$V_c = 1 \text{ V}$$

$$V_{ac} = 330 \text{ V}$$

$$r_C = 0.06 \ \Omega$$

$$C_{out} = 470 \ \mu\text{F}$$

$$N_1 = 0.25$$

$$V_{cp} = \frac{V_{out}}{N_1} = 84.4 \text{ V}$$

$$L_p = 600 \ \mu\text{H}$$

$$k_F = 10000$$

$$F_{sw} = \frac{2I_{out} R_i^2 V_{out}}{L_p V_c^2} = 52.8 \text{ kHz}$$

$$I_c = \frac{F_{sw} L_p V_c^2 (V_{ac} + V_{cp})}{2R_i^2 V_{ac} V_{cp}} = 0.368 \text{ A}$$

$$I_a = \frac{F_{sw} L_p V_c^2}{2R_i^2 V_{ac}} = 0.075 \text{ A}$$

$$I_\mu = 0.882 \text{ A}$$




Test the Coefficient Values with the Sources

- Capture a new schematic with the linearized sources



Responses with Previous Models are Similar

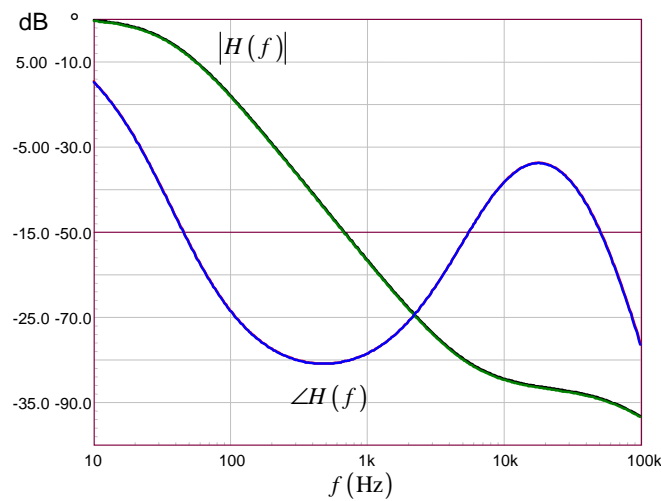
- The curves perfectly superimpose, 2nd step is ok



Combine and Arrange the Sources


Now, re-arrange the sources in a more convenient way

Ac response is ok!

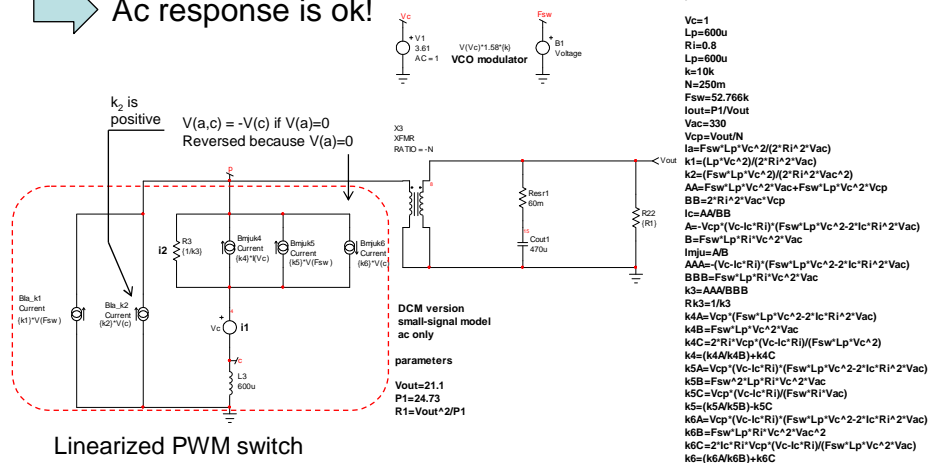

Go for Mesh and Node Analysis

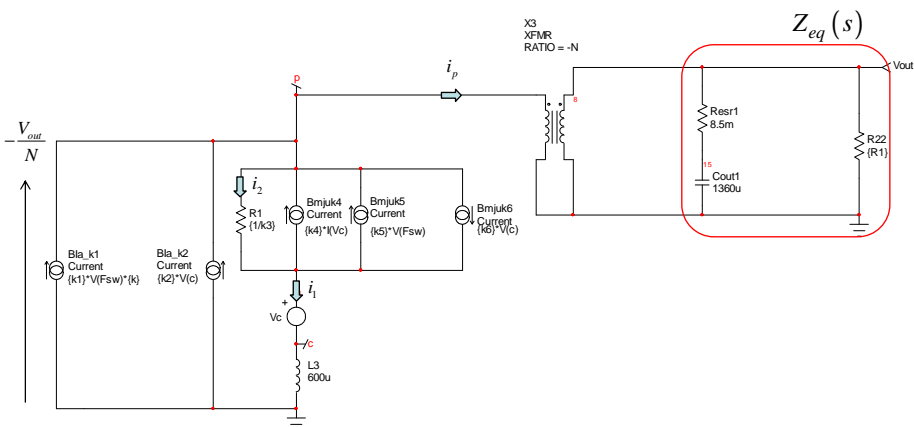Express the current and voltage in the primary side



Mesh and Node Analysis

□ KCL: the sum of currents arriving at a node equals the sum of currents leaving the node:

$$k_4 i_1 + k_5 V(F_{sw}) + i_1 = i_2 + s k_6 L_p i_1 \quad i_2 = i_1 + i_1 k_4 + k_5 V(F_{sw}) - s L_p i_1 k_6$$

$$i_1 = \frac{-\frac{V_{out}}{N_1} - R_1 i_2}{s L_p}$$

$$i_1(s) = -\frac{V_{out}(s) + N_1 R_1 i_1(s) + N_1 R_1 i_1(s) k_4 + N_1 R_1 k_5 V(F_{sw}) - s L_p R_1 i_1(s) k_6 N_1}{L_p N_1 s}$$

□ solve for i_1 :

$$i_1(s) = -\frac{V_{out}(s) + N_1 R_1 k_5 V(F_{sw})}{N_1 R_1 (1 + k_4) + s L_p N_1 (1 - k_6 R_1)}$$

Mesh and Node Analysis

□ Apply similar technique to get the primary current:

$$i_p(s) = k_1 V(F_{sw}) + k_2 i_1(s) s L_p - i_1(s)$$

$$i_p(s) = \frac{V_{out}(s) - L_p V_{out}(s) k_2 s + N_1 R_1 V(F_{sw})(k_1 + k_5 + k_1 k_4) + s L_p N_1 V(F_{sw})(k_1 - R_1 k_1 k_6 - R_1 k_2 k_5)}{N_1 (R_1 + R_1 k_4 + s L_p - s L_p R_1 k_6)}$$


$$i_{out} = -\frac{i_p}{N_1} \quad V_{out} = i_{out} Z_{eq}$$

$$V_{out}(s) = \frac{V_{out}(s) - L_p V_{out}(s) k_2 s + N_1 R_1 V(F_{sw})(k_1 + k_5 + k_1 k_4) + s L_p N_1 V(F_{sw})(k_1 - R_1 k_1 k_6 - R_1 k_2 k_5)}{N_1^2 (R_1 + R_1 k_4 + s L_p - s L_p R_1 k_6)} Z_{eq}(s)$$

$$\frac{V_{out}(s)}{V(F_{sw})} = \frac{(N_1 R_1 (k_1 + k_5 + k_1 k_4) + s L_p N_1 (k_1 - R_1 k_1 k_6 - R_1 k_2 k_5))}{N_1^2 (s R_1 L_p k_6 - s L_p - R_1 k_4 - R_1) - Z_{eq}(s) + s L_p k_2 Z_{eq}(s)} Z_{eq}(s)$$

Fast Analytical Techniques

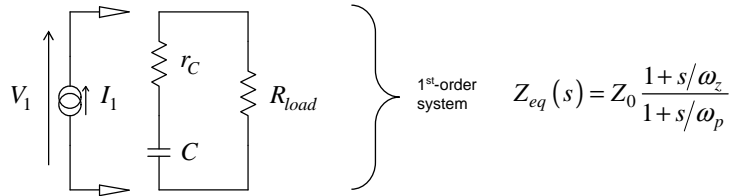- Fast analytical techniques unveil Z_{eq} in a second!




1. In dc, open the capacitor: $Z_0 = R_{load}$
2. What prevents the excitation I_1 from reaching the output V_1 ?
 - A short-circuit between r_C and C :

$$r_C + \frac{1}{sC} = \frac{sr_C C + 1}{sC} = 0 \quad \Rightarrow \quad \omega_z = \frac{1}{r_C C}$$

Fast Analytical Techniques

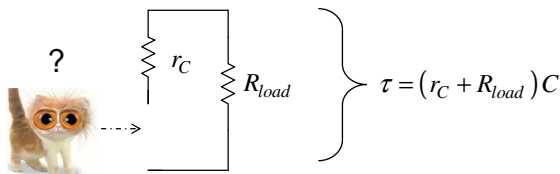- Get the time constant by putting the excitation to zero:
 - open the current source and look at the cap. driving R



- The equivalent impedance is therefore:

$$Z_{eq}(s) = R_{load} \frac{1 + sr_C C}{1 + sC(r_C + R_{load})}$$

You cannot beat equation-solving by inspection!

Almost There...

- Develop the expression with $Z_{eq}(s)$, cry and re-arrange:

$$H(s) = H_0 \frac{N(s)}{D(s)} \quad H_0 = -G_{VCO} \frac{N_1 R_{load} R_1 (k_1 + k_5 + k_1 k_4)}{R_{load} + N_1^2 R_1 (1 + k_4)} = \frac{V_{out}}{2F_{sw}} G_{VCO}$$

$$N(s) = \left(1 + sL_p \left(\frac{k_1 - R_1 k_1 k_6 - R_1 k_2 k_5}{R_1 (k_1 + k_5 + k_1 k_4)} \right) \right) (1 + sr_C C) \quad D(s) = 1 + as + bs^2$$

$$a = C_{out} \left(R_{load} + r_C - \frac{R_{load}^2}{R_{load} + N_1^2 R_1 (1 + k_4)} \right) + L_p \left(\frac{N_1^2 - R_{load} k_2 - N_1^2 R_1 k_6}{R_{load} + N_1^2 R_1 (1 + k_4)} \right)$$

$$b = L_p N_1^2 C_{out} \left(\frac{R_{load} + r_C - \frac{R_{load}}{N_1^2} k_2 r_C - R_1 R_{load} k_6 - R_1 k_6 r_C}{R_{load} + N_1^2 R_1 (1 + k_4)} \right)$$



A Few More Minutes, Keep the Faith...

- Put the denominator under a second-order form and identify

$$D(s) = 1 + as + bs^2 = 1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0} \right)^2$$

$$f_0 = \frac{1}{2\pi \sqrt{L_p C_{out}}} \sqrt{\frac{\frac{R_{load}}{N_1^2} + R_1 (1 + k_4)}{R_{load} + r_C - \frac{R_{load}}{N_1^2} k_2 r_C - R_1 k_6 (R_{load} + r_C)}} = 1.75 \text{ kHz}$$

$$Q = \frac{1}{\omega_0 \left(C_{out} \left(R_{load} + r_C - \frac{R_{load}^2}{R_{load} + N_1^2 R_1 (1 + k_4)} \right) + L_p \left(\frac{N_1^2 - R_{load} k_2 - N_1^2 R_1 k_6}{R_{load} + N_1^2 R_1 (1 + k_4)} \right) \right)} = 0.021$$



A Few More Minutes, Keep the Faith...

- Extract the zeros:

$$f_{z_1} = \frac{1}{2\pi L_p \left(\frac{k_1 - R_1(k_1 k_6 - k_2 k_5)}{R_1(k_1 + k_5 + k_1 k_4)} \right)} = \uparrow 487 \text{ kHz} \quad f_{z_2} = \frac{1}{2\pi r_C C_{out}} = 5.6 \text{ kHz}$$

RHPZ

- Extract the low-frequency poles:

$$f_{p_1} = \frac{1}{2\pi C_{out} \left(R_{load} + r_C - \frac{R_{load}^2}{R_{load} + N_1^2 R_1 (1 + k_4)} \right)} = \frac{1}{2\pi C_{out} \left(R_{load} + r_C - \frac{R_{load}}{2} \right)} \approx \frac{1}{\pi R_{load} C_{out}}$$

$r_C \ll R_{load}$


$$f_{p_1} = \frac{1}{\pi C_{out} (R_{load} + r_C)} = 37.73 \text{ Hz}$$

$$f_{p_2} = \frac{1}{2\pi L_p \left(\frac{N_1^2 - R_{load} k_2 - N_1^2 R_1 k_6}{R_{load} + N_1^2 R_1 (1 + k_4)} \right)} = 152 \text{ kHz}$$



Final Lap, Compare the ac Plots

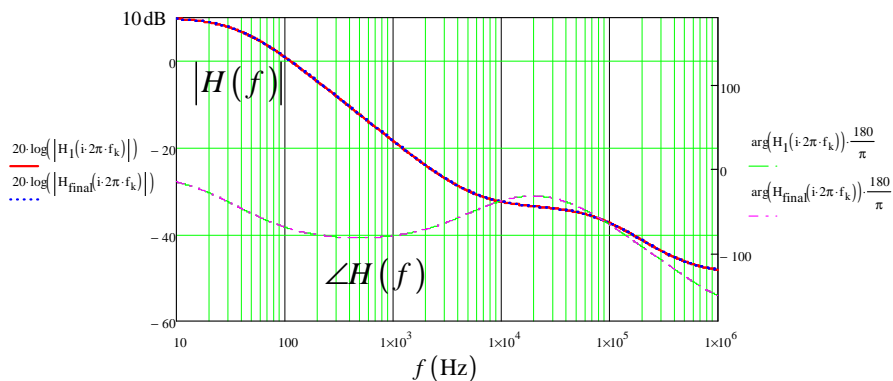- Compare the original equation and its re-arranged form:




- It confirms the derivation is correct!




The Final Test: SPICE vs Mathcad

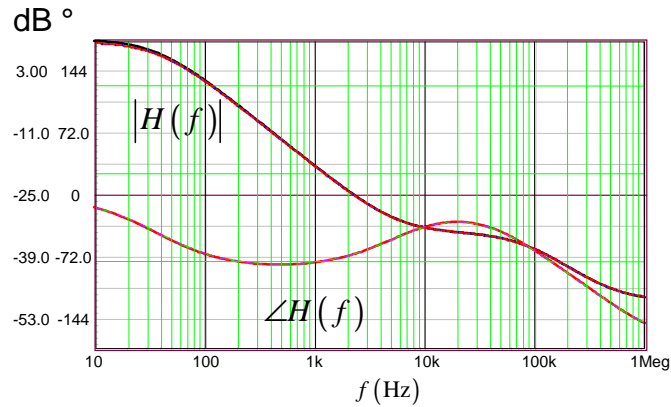- ❑ If all is well, the curves must perfectly superimpose




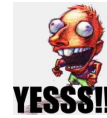- If not, there is a hidden mistake: chase it (good luck)



The Final Transfer Function

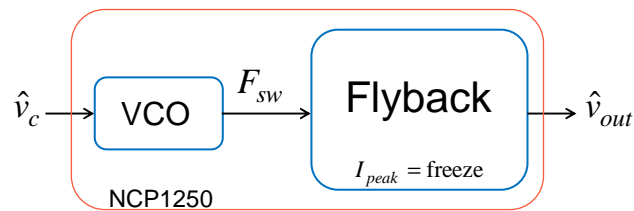
- ❑ The current-mode flyback converter is operated in DCM
- ❑ The peak current is fixed and F_{sw} is controlled
- ❑ What is the simplified transfer function?




$$H(s) = \frac{\hat{v}_{out}}{\hat{v}_c} = H_0 \frac{1 + s/\omega_z}{1 + s/\omega_p} = \frac{V_{out}}{2F_{sw}} G_{VCO} \frac{1 + s r_C C_{out}}{1 + s \frac{R_{load}}{2} C_{out}}$$

A Faster Way?

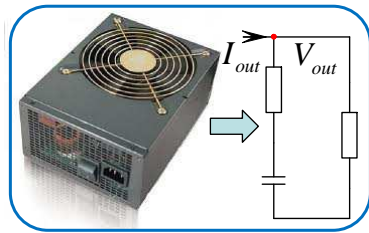- ❑ If you are in a hurry and looking for a faster way:
 - Formulate the output current expression
 - Differentiate the expression to its variables
 - Draw an equivalent schematic and solve the equations



A DCM/CCM
current-mode converter

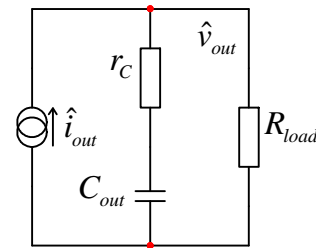

Simplified linearized model

The Founding Equation is Well Known

- ❑ A flyback converter running in DCM obeys:

$$P_{out} = I_{out} V_{out} = \frac{1}{2} L_p I_{peak}^2 F_{sw} \rightarrow I_{peak} = \frac{V_c}{R_i} \rightarrow I_{out} V_{out} = \frac{1}{2} L_p \left(\frac{V_c}{R_i} \right)^2 F_{sw}$$

$$I_{out} = \frac{L_p \left(\frac{V_c}{R_i} \right)^2 \boxed{F_{sw}}}{\boxed{2V_{out}}} \quad \text{Two variables}$$

$$\hat{i}_{out} = \left(\frac{\partial I_{out}(F_{sw}, V_{out})}{\partial V_{out}} \right)_{F_{sw}} \hat{v}_{out} + \left(\frac{\partial I_{out}(F_{sw}, V_{out})}{\partial F_{sw}} \right)_{V_{out}} \hat{F}_{sw}$$

First Expression Comes Easily


- Rework the individual coefficients to a simpler form

$$\left(\frac{\partial I_{out}(F_{sw}, V_{out})}{\partial V_{out}} \right)_{F_{sw}} \hat{v}_{out} = - \frac{F_{sw} L_p}{2 V_{out}^2} \left(\frac{V_c}{R_i} \right)^2 \hat{v}_{out} \Rightarrow g_m \cdot \hat{v}_{out} = \frac{1}{R} \hat{v}_{out}$$

$$\downarrow$$

$$[\Omega^{-1}]$$

$$-\frac{F_{sw} L_p}{2 V_{out}^2} \left(\frac{V_c}{R_i} \right)^2 = -\frac{\frac{1}{2} I_{peak}^2 F_{sw} L_p}{V_{out}^2}$$

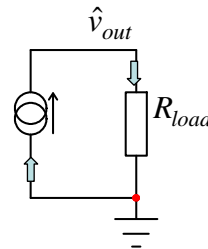
$$-\frac{P_{out}}{V_{out}^2} = -\frac{V_{out} I_{out}}{V_{out} V_{out}} = -\frac{1}{R_{load}}$$


Second Expression is Also Simple

- Identify the power in the equation, simplify...

$$\left(\frac{\partial I_{out}(F_{sw}, V_{out})}{\partial F_{sw}} \right)_{V_{out}} \hat{F}_{sw} = \frac{L_p}{2 V_{out}} \left(\frac{V_c}{R_i} \right)^2 \hat{F}_{sw}$$
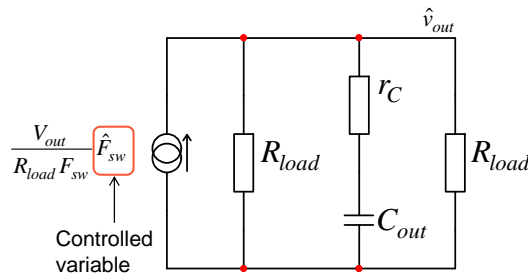
$$\frac{L_p}{2 V_{out}} \left(\frac{V_c}{R_i} \right)^2 \hat{F}_{sw} = \frac{P_{out}}{F_{sw} V_{out}} \hat{F}_{sw} = \frac{V_{out}}{R_{load}} \frac{V_{out}}{F_{sw} V_{out}} \hat{F}_{sw} = \frac{V_{out}}{R_{load} F_{sw}} \hat{F}_{sw}$$



Can't beat such a simple schematic!

The Transfer Function is Immediate

- The transfer function is now straightforward

$$\hat{v}_{out}(s) = \hat{F}_{sw}(s) \frac{V_{out}}{R_{load} F_{sw}} \boxed{R_{load} \parallel Z_{eq}(s)} \longrightarrow \approx \frac{R_{load}}{2} \frac{1 + sr_C C}{1 + sC \left(\frac{R_{load}}{2} \right)}$$

$$\hat{v}_{out}(s) = \hat{v}_c(s) k_F G_{VCO} \frac{V_{out}}{2F_{sw}} \frac{1 + sr_C C}{1 + sC \left(\frac{R_{load}}{2} \right)}$$

- Put it under the normalized form

$$H(s) = \frac{\hat{v}_{out}}{\hat{v}_c} = H_0 \frac{1 + s/\omega_z}{1 + s/\omega_p} = \frac{V_{out}}{2F_{sw}} k_F G_{VCO} \frac{1 + sr_C C_{out}}{1 + s \frac{R_{load}}{2} C_{out}}$$


- No RHPZ and no high-frequency pole prediction
- Good for low-frequency analysis only, but good enough for us!



Simulation Shows the Differences

- SPICE only manipulates linear equations

Large-signal equation

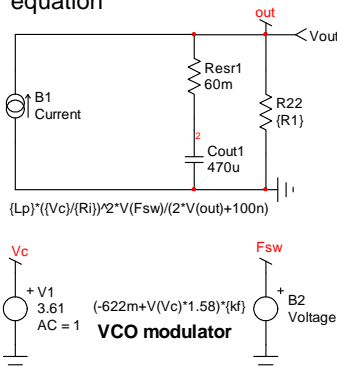


$\{Lp\} \cdot \{(Vc) / \{Ri\}\} \cdot 2 \cdot V(Fsw) / (2 \cdot V(out) + 100n)$

parameters

Vc=1
Lp=600u
Ri=0.8
Lp=600u
kf=10k

Vout=21.1
P1=24.73
R1=Vout^2/P1
Fsw=50.8k

Small-signal equation

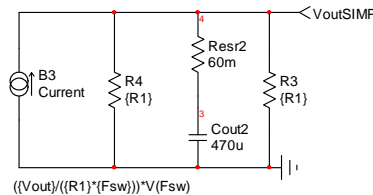


$\{(Vout) / \{(R1) \cdot \{Fsw\}\}\} \cdot V(Fsw)$

$$20 \log_{10} |H_0| = 20 \log_{10} \left(\frac{V_{out}}{2F_{sw}} k_F G_{VCO} \right) = 20 \log_{10} \left(\frac{21.1}{2 \times 50.8k} 10k \cdot 1.58 \right) = 10.3 \text{ dB}$$




Simulation Shows the Differences

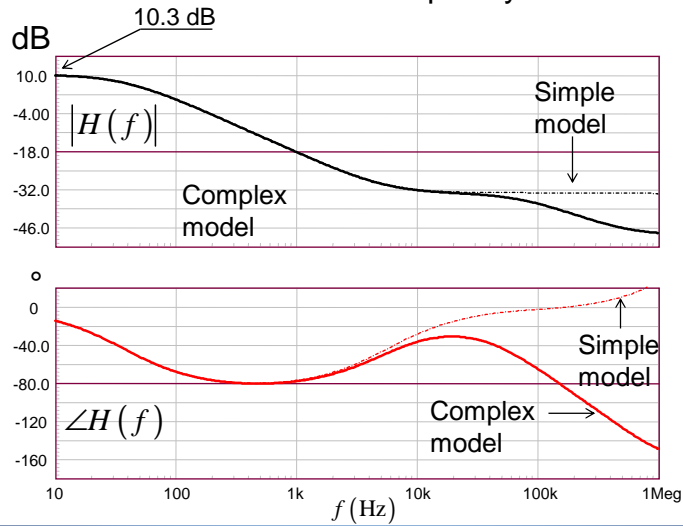- Ac results are identical at low frequency




Test Fixture

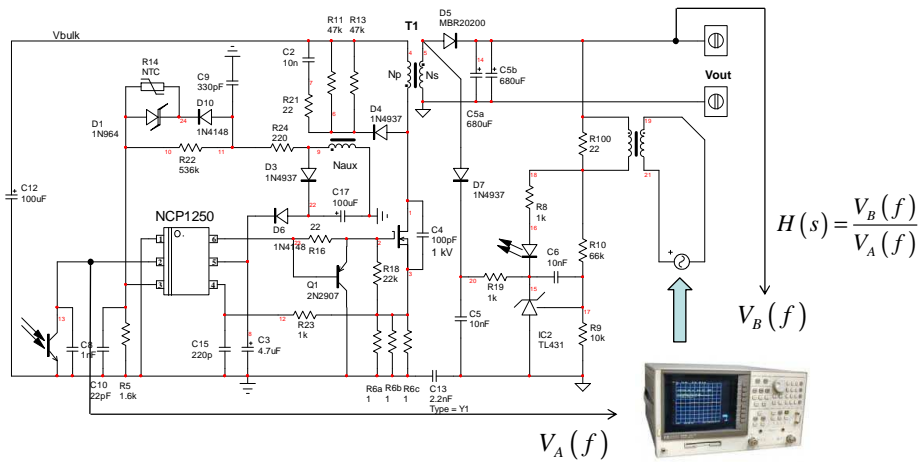- Plant frequency response with a NCP1250
- Load is reduced to force DCM where I_{peak} is frozen




Connections

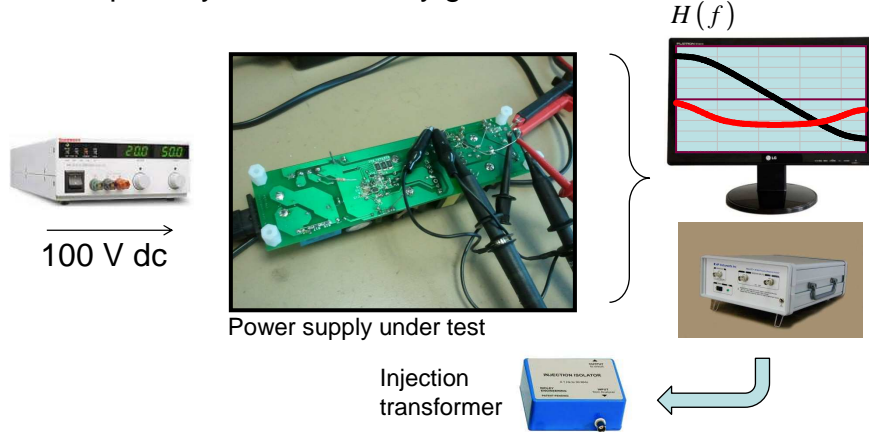- ❑ Connect probe grounds to a quiet point: opto emitter is ok
- ❑ Use an isolated current-limited dc-supply
- ❑ Short primary and secondary grounds



Run the SPICE Simulation

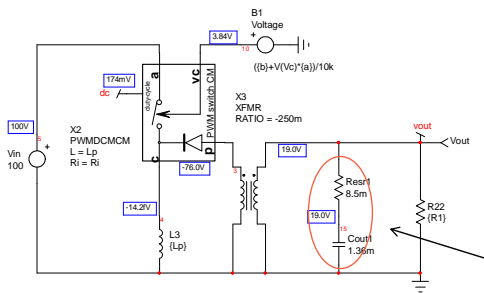

parameters

Vout=19
P1=6.6
R1=Vout*2/P1
Lp=600u
Rl=0.33

Fmax=65k
Fmin=26k
Vfold=1.5
Vmin=0.35
a2=(Fmax-Fmin)/(Vfold-Vmin)
a=27.75k
b=Fmin-Vmin*a

VCO slope measured to 27.8 kHz/V

- ❑ Check operating points:

$$F_{sw} = 38.6 \text{ kHz (bench)} \quad 38.4 \text{ kHz (SPICE)}$$

$$V_{FB} = 0.71 \text{ V (bench)} \quad 0.79 \text{ V (SPICE)}$$

Main contributor to errors is the capacitor ESR




ZL series Rubycon



Approximate ESR Extraction

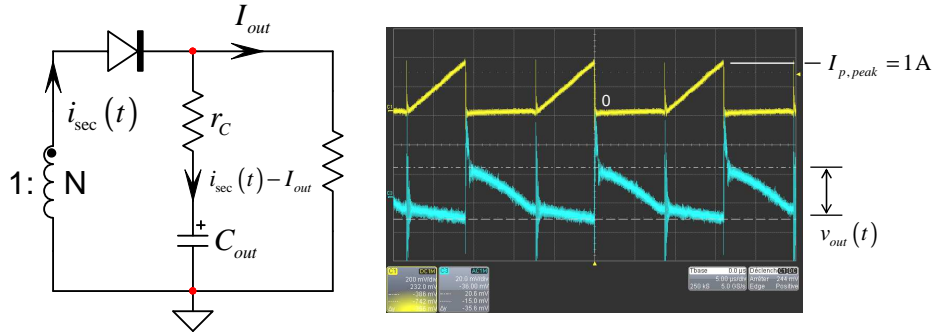- A triangular output shows that ESR is the main contributor




$$I_{sec,peak} = \frac{I_{p,peak}}{N} = \frac{1}{0.25} = 4A$$

$$V_{out,peak} \approx I_{sec,peak} r_C$$

$$r_C \approx \frac{V_{out,pp}}{I_{sec,peak}} = \frac{35m}{4} = 8.75m\Omega$$

DS says 11.5 mΩ

Plant Frequency Response

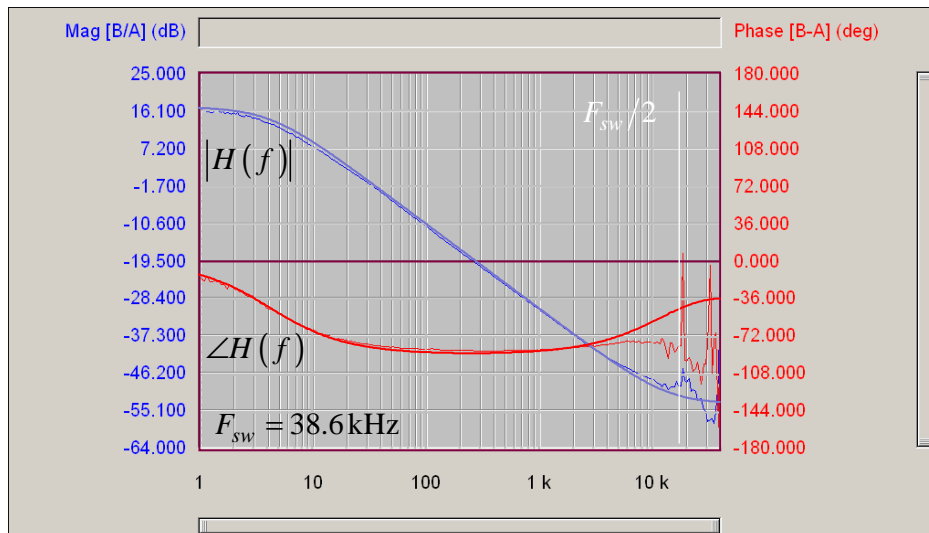

Conclusion

- ❑ The transfer function in DCM frequency foldback has been derived
- ❑ It can be approximated in low frequency as a 1st order system
- ❑ Stability in this mode is not at stake with current designs
- ❑ Besides the comprehensive PWM switch approach, the linearized output current gives good results too.
- ❑ Bench measurements confirm the low-frequency results, high-frequency points start to diverge as we approach the switching frequency.

