
Table of Contents

CHAPTER 1: TRANSFER FUNCTIONS	3
1.1 TRANSFER FUNCTIONS	3
1.1.1 <i>Different Types of Transfer Functions</i>	7
1.1.2 <i>Time Constants, Poles and Zeroes of a Transfer Function</i>	11
1.1.3 <i>Writing the Transfer Functions the Right Way</i>	21
1.1.4 <i>Determining an Impedance</i>	24
1.2 WHAT SHOULD I RETAIN FROM THIS CHAPTER?.....	29
1.3 REFERENCES	29
CHAPTER 2: FAST ANALYTICAL CIRCUITS TECHNIQUES	30
2.1 AN INTRODUCTION TO FAST ANALYTICAL CIRCUITS TECHNIQUES OR FACTS	30
2.1.1 <i>State of the Passive Element for First-Order Circuits</i>	34
2.1.2 <i>States of Passive Elements in Higher-Order Circuits</i>	37
2.2 WHAT SHOULD I RETAIN FROM THIS CHAPTER?.....	51
2.3 REFERENCES	52
CHAPTER 3: ZEROES OF A TRANSFER FUNCTION	53
3.1 DETERMINING THE ZEROES	53
3.2 THE NULL DOUBLE INJECTION.....	61
3.3 WHAT SHOULD I RETAIN FROM THIS CHAPTER?.....	83
3.4 REFERENCES	83
CHAPTER 4: GENERALIZED TRANSFER FUNCTIONS	84
4.1 THE GENERALIZED TRANSFER FUNCTION	84
4.2 WHAT SHOULD I RETAIN FROM THIS CHAPTER?.....	99
4.3 REFERENCES	99
CHAPTER 5: FIRST-ORDER TRANSFER FUNCTIONS	100
5.1 A SET OF THREE EXPRESSIONS	100
5.2 CIRCUITS WITH ONE ENERGY-STORING ELEMENT	101
5.3 LIST OF FIGURES AND TRANSFER FUNCTIONS	164
CHAPTER 6: SECOND-ORDER TRANSFER FUNCTIONS	166
6.1 ZEROED EXCITATION AND NULL DOUBLE INJECTION FOR 2 ND -ORDER SYSTEMS	166
6.2 CIRCUITS WITH TWO ENERGY-STORING ELEMENTS	169
6.3 LIST OF FIGURES AND TRANSFER FUNCTIONS	228
6.4 REFERENCES	229
CHAPTER 7: THIRD-ORDER TRANSFER FUNCTIONS	230
7.1 ZEROED EXCITATION AND NULL DOUBLE INJECTION FOR 3 RD -ORDER SYSTEMS	230

7.2	CIRCUITS WITH THREE ENERGY-STORING ELEMENTS.....	234
7.3	LIST OF FIGURES AND TRANSFER FUNCTIONS.....	259
7.4	REFERENCES	259
APPENDIX A – ILLUSTRATING THE PROCESS OF DETERMINING POLES AND ZEROES		260