
CONTENTS

Foreword	xiii
Preface	xv
Nomenclature	xvii

Chapter 1. Introduction to Power Conversion 1

1.1. “Do You Really Need to Simulate?”	/ 1
1.2. What You Will Find in the Following Pages	/ 2
1.3. What You Will Not Find in this Book	/ 3
1.4. Converting Power with Resistors	/ 3
1.4.1. Associating Resistors	/ 3
1.4.2. A Closed-Loop System	/ 5
1.4.3. Deriving Useful Equations with the Linear Regulator	/ 7
1.4.4. A Practical Working Example	/ 10
1.4.5. Building a Simple Generic Linear Regulator	/ 14
1.4.6. Conclusion on Linear Regulators	/ 17
1.5. Converting Power with Switches	/ 18
1.5.1. A Filter Is Needed	/ 19
1.5.2. Current in the Inductance, Continuous or Discontinuous?	/ 21
1.5.3. Charge and Flux Balance	/ 25
1.5.4. Energy Storage	/ 27
1.6. The Duty Cycle Factory	/ 27
1.6.1. Voltage-Mode Operation	/ 27
1.6.2. Current-Mode Operation	/ 29
1.7. The Buck Converter	/ 30
1.7.1. On-Time Event	/ 30
1.7.2. Off-Time Event	/ 31
1.7.3. Buck Waveforms—CCM	/ 31
1.7.4. Buck Waveforms—DCM	/ 34
1.7.5. Buck Transition Point DCM—CCM	/ 37
1.7.6. Buck CCM Output Ripple Voltage Calculation	/ 39
1.7.7. Now with the ESR	/ 41
1.7.8. Buck Ripple, the Numerical Application	/ 41
1.8. The Boost Converter	/ 42
1.8.1. On-Time Event	/ 43
1.8.2. Off-Time Event	/ 44
1.8.3. Boost Waveforms—CCM	/ 44
1.8.4. Boost Waveforms—DCM	/ 47
1.8.5. Boost Transition Point DCM—CCM	/ 50
1.8.6. Boost CCM Output Ripple Voltage Calculations	/ 51
1.8.7. Now with the ESR	/ 54
1.8.9. Boost Ripple, the Numerical Application	/ 54
1.9. The Buck-Boost Converter	/ 55
1.9.1. On-Time Event	/ 56
1.9.2. Off-Time Event	/ 56

vi CONTENTS

- 1.9.3. Buck-Boost Waveforms—CCM / 57
- 1.9.4. Buck-Boost Waveforms—DCM / 59
- 1.9.5. Buck-Boost Transition Point DCM—CCM / 63
- 1.9.6. Buck-Boost CCM Output Ripple Voltage Calculation / 64
- 1.9.7. Now with the ESR / 65
- 1.9.8. Buck-Boost Ripple, the Numerical Application / 65
- 1.10. Input Filtering / 66
 - 1.10.1. The RLC Filter / 67
 - 1.10.2. A More Comprehensive Representation / 70
 - 1.10.3. Creating a Simple Closed-Loop Current Source with SPICE / 71
 - 1.10.4. Understanding Overlapping Impedances / 72

Chapter 2. Small-Signal Modeling**95**

- 2.1. State-Space Averaging / 98
 - 2.1.1. SSA at Work for the Buck Converter—First Step / 100
 - 2.1.2. The DC Transformer / 102
 - 2.1.3. Large-Signal Simulations / 105
 - 2.1.4. SSA at Work for the Buck Converter, the Linearization—Second Step / 106
 - 2.1.5. SSA at Work for the Buck Converter, the Small-Signal Model—Final Step / 108
- 2.2. The PWM Switch Model—the Voltage-Mode Case / 111
 - 2.2.1. Back to the Good Old Bipolars / 112
 - 2.2.2. An Invariant Internal Architecture / 113
 - 2.2.3. Waveform Averaging / 114
 - 2.2.4. Terminal Currents / 116
 - 2.2.5. Terminal Voltages / 117
 - 2.2.6. A Transformer Representation / 117
 - 2.2.7. Large-Signal Simulations / 118
 - 2.2.8. A More Complex Representation / 121
 - 2.2.9. A Small-Signal Model / 123
 - 2.2.10. Helping with Simulation / 128
 - 2.2.11. Discontinuous Mode Model / 129
 - 2.2.12. Deriving the d_2 Variable / 132
 - 2.2.13. Clamping Sources / 132
 - 2.2.14. Encapsulating the Model / 134
 - 2.2.15. The PWM Modulator Gain / 138
 - 2.2.16. Testing the Model / 142
 - 2.2.17. Mode Transition / 143
- 2.3. The PWM Switch Model—the Current-Mode Case / 145
 - 2.3.1. Current-Mode Instabilities / 146
 - 2.3.2. Preventing Instabilities / 151
 - 2.3.3. The Current-Mode Model in CCM / 153
 - 2.3.4. Upgrading the Model / 158
 - 2.3.5. The Current-Mode Model in DCM / 161
 - 2.3.6. Deriving the Duty Cycles d_1 and d_2 / 163
 - 2.3.7. Building the DCM Model / 165
 - 2.3.8. Testing the Model / 168
 - 2.3.9. Buck DCM, Instability in DC / 172
 - 2.3.10. Checking the Model in CCM / 172
- 2.4. The PWM Switch Model—Parasitic Elements Effects / 175
 - 2.4.1. A Variable Resistor / 179
 - 2.4.2. Ohmic Losses, Voltage Drops: The VM Case / 180
 - 2.4.3. Ohmic Losses, Voltage Drops: The CM Case / 182
 - 2.4.4. Testing the Lossy Model in Current Mode / 183
 - 2.4.5. Convergence Issues with the CM Model / 186
- 2.5. PWM Switch Model in Borderline Conduction / 187
 - 2.5.1. Borderline Conduction—the Voltage-Mode Case / 187
 - 2.5.2. Testing the Voltage-Mode BCM Model / 191

2.5.3. Borderline Conduction—the Current-Mode Case	/ 194
2.5.4. Testing the Current-Mode BCM Model	/ 198
2.6. The PWM Switch Model—a Collection of Circuits	/ 202
2.6.1. The Buck	/ 203
2.6.2. The Tapped Buck	/ 204
2.6.3. The Forward	/ 205
2.6.4. The Buck-Boost	/ 206
2.6.5. The Flyback	/ 207
2.6.6. The Boost	/ 208
2.6.7. The Tapped Boost	/ 208
2.6.8. The Nonisolated SEPIC	/ 209
2.6.9. The Isolated SEPIC	/ 210
2.6.10. The Nonisolated Cuk Converter	/ 211
2.6.11. The Isolated Cuk Converter	/ 212
2.7. Other Averaged Models	/ 213
2.7.1. Ridley Models	/ 213
2.7.2. Small-Signal Current-Mode Models	/ 213
2.7.3. Ridley Models at Work	/ 214
2.7.4. CoPEC Models	/ 216
2.7.5. CoPEC Models at Work	/ 218
2.7.6. Ben-Yaakov Models	/ 220
What I Should Retain from Chap. 2	/ 224
References	/ 224
Appendix 2A Basic Transfer Functions for Converters	/ 225
2A.1. Buck	/ 226
2A.2. Boost	/ 229
2A.3. Buck-Boost	/ 231
References	/ 235
Appendix 2B Poles, Zeros, and Complex Plane—a Simple Introduction	/ 235
References	/ 240

Chapter 3. Feedback and Control Loops

241

3.1. Observation Points	/ 243
3.2. Stability Criteria	/ 247
3.3. Phase Margin and Transient Response	/ 248
3.4. Choosing the Crossover Frequency	/ 249
3.5. Shaping the Compensation Loop	/ 250
3.5.1. The Passive Pole	/ 250
3.5.2. The Passive Zero	/ 251
3.5.3. Right Half-Plane Zero	/ 253
3.5.4. Type 1 Amplifier—Active Integrator	/ 255
3.5.5. Type 2 Amplifier—Zero-Pole Pair	/ 256
3.5.6. Type 2A—Origin Pole Plus a Zero	/ 258
3.5.7. Type 2B—Proportional Plus a Pole	/ 259
3.5.8. Type 3—Origin Pole Plus Two Coincident Zero-Pole Pairs	/ 261
3.5.9. Selecting the Right Amplifier Type	/ 262
3.6. An Easy Stabilization Tool—the k Factor	/ 263
3.6.1. Type 1 Derivation	/ 264
3.6.2. Type 2 Derivation	/ 264
3.6.3. Type 3 Derivation	/ 266
3.6.4. Stabilizing a Voltage-Mode Buck Converter with the k Factor	/ 267
3.6.5. Conditional Stability	/ 270
3.6.6. Independent Pole-Zero Placement	/ 272
3.6.7. Crossing Over Right at the Selected Frequency	/ 273
3.6.8. The k Factor versus Manual Pole-Zero Placement	/ 275
3.6.9. Stabilizing a Current-Mode Buck Converter with the k Factor	/ 280
3.6.10. The Current-Mode Model and Transient Steps	/ 286

- 3.7. Feedback with the TL431 / 286
 - 3.7.1. A Type 2 Amplifier Design Example with the TL431 / 291
 - 3.7.2. A Type 3 Amplifier with the TL431 / 292
 - 3.7.3. Biasing the TL431 / 298
 - 3.7.4. The Resistive Divider / 303
- 3.8. The Optocoupler / 304
 - 3.8.1. A Simplified Model / 305
 - 3.8.2. Extracting the Pole / 306
 - 3.8.3. Accounting for the Pole / 308
- 3.9. Shunt Regulators / 312
 - 3.9.1. SPICE Model of the Shunt Regulator / 313
 - 3.9.2. Quickly Stabilizing a Converter Using the Shunt Regulator / 314
- 3.10. Small-Signal Responses with PSIM and SIMPLIS / 316
 - What I Should Retain from Chap. 3 / 322
 - References / 322
 - Appendix 3A Automated Pole-Zero Placement / 323
 - Appendix 3B A TL431 Spice Model / 326
 - 3B.1. A Behavioral TL431 Spice Model / 326
 - 3B.2. Cathode Current versus Cathode Voltage / 328
 - 3B.3. Output Impedance / 329
 - 3B.4. Open-Loop Gain / 330
 - 3B.5. Transient Test / 331
 - 3B.6. Model Netlist / 331
 - Appendix 3C Type 2 Manual Pole-Zero Placement / 332
 - Appendix 3D Understanding the Virtual Ground in Closed-Loop Systems / 335
 - 3D.1. Numerical Example / 336
 - 3D.2. Loop Gain Is Unchanged / 337

Chapter 4. Basic Blocks and Generic Switched Models

341

- 4.1. Generic Models for Faster Simulations / 341
 - 4.1.1. In-Line Equations / 341
- 4.2. Operational Amplifiers / 343
 - 4.2.1. A More Realistic Model / 344
 - 4.2.2. A UC384X Error Amplifier / 345
- 4.3. Sources with a Given Fan-Out / 348
- 4.4. Voltage-Adjustable Passive Elements / 349
 - 4.4.1. The Resistor / 350
 - 4.4.2. The Capacitor / 351
 - 4.4.3. The Inductor / 353
- 4.5. A Hysteresis Switch / 355
- 4.6. An Undervoltage Lockout Block / 358
- 4.7. Leading Edge Blanking / 359
- 4.8. Comparator with Hysteresis / 361
- 4.9. Logic Gates / 362
- 4.10. Transformers / 364
 - 4.10.1. A Simple Saturable Core Model / 366
 - 4.10.2. Multioutput Transformers / 372
- 4.11. Astable Generator / 372
 - 4.11.1. A Voltage-Controlled Oscillator / 374
 - 4.11.2. A Voltage-Controlled Oscillator Featuring Dead Time Control / 377
- 4.12. Generic Controllers / 377
 - 4.12.1. Current-Mode Controllers / 378
 - 4.12.2. Current-Mode Model with a Buck / 380
 - 4.12.3. Current-Mode Instabilities / 381
 - 4.12.4. The Voltage-Mode Model / 382
 - 4.12.5. The Duty Cycle Generation / 382
 - 4.12.6. A Quick Example with a Forward Converter / 384

- 4.13. Dead Time Generation / 387
- 4.14. List of Generic Models / 387
- 4.15. Convergence Options / 388
- What I Should Retain from Chap. 4 / 391
- References / 392
- Appendix 4A An Incomplete Review of the Terminology Used in Magnetic Designs / 392
 - 4A.1. Introduction / 392
 - 4A.2. Field Definition / 393
 - 4A.3. Permeability / 393
 - 4A.4. Founding Laws / 396
 - 4A.5. Inductance / 396
 - 4A.6. Avoiding Saturation / 397
 - References / 398
- Appendix 4B Feeding Transformer Models with Physical Values / 398
 - 4B.1. Understanding the Equivalent Inductor Model / 398
 - 4B.2. Determining the Physical Values of the Two-Winding T Model / 400
 - 4B.3. The Three-Winding T Model / 401
 - References / 405

Chapter 5. Simulations and Practical Designs of Nonisolated Converters 407

- 5.1. The Buck Converter / 407
 - 5.1.1. A 12 V, 4 A Voltage-Mode Buck from a 28 V Source / 407
 - 5.1.2. AC Analysis / 410
 - 5.1.3. Transient Analysis / 413
 - 5.1.4. The Power Switch / 417
 - 5.1.5. The Diode / 418
 - 5.1.6. Output Ripple and Transient Response / 419
 - 5.1.7. Input Ripple / 421
 - 5.1.8. A 5 V, 10 A Current-Mode Buck from a Car Battery / 425
 - 5.1.9. AC Analysis / 426
 - 5.1.10. Transient Analysis / 429
 - 5.1.11. A Synchronous Buck Converter / 433
 - 5.1.12. A Low-Cost Floating Buck Converter / 434
 - 5.1.13. Component Constraints for the Buck Converter / 439
- 5.2. The Boost Converter / 441
 - 5.2.1. A Voltage-Mode 48 V, 2 A Boost from a Car Battery / 441
 - 5.2.2. AC Analysis / 444
 - 5.2.3. Transient Analysis / 449
 - 5.2.4. A Current-Mode 5 V, 1 A Boost from a Li-Ion Battery / 452
 - 5.2.5. AC Analysis / 454
 - 5.2.6. Transient Analysis / 459
 - 5.2.7. Input Filter / 460
 - 5.2.8. Component Constraints for the Boost Converter / 465
- 5.3. The Buck-Boost Converter / 465
 - 5.3.1. A Voltage-Mode 12 V, 2 A Buck-Boost Converter Powered from a Car Battery / 465
 - 5.3.2. AC Analysis / 468
 - 5.3.3. Transient Analysis / 474
 - 5.3.4. A Discontinuous Current-Mode 12 V, 2 A Buck-Boost Converter Operating from a Car Battery / 476
 - 5.3.5. AC Analysis / 479
 - 5.3.6. Transient Analysis / 483
 - 5.3.7. Component Constraints for the Buck-Boost Converter / 486
 - References / 486
- Appendix 5A The Boost in Discontinuous Mode, Design Equations / 487
 - 5A.1. Input Current / 487
 - 5A.2. Output Ripple Voltage / 489

Chapter 6. Simulations and Practical Designs of Off-Line Converters—The Front End

491

- 6.1. The Rectifier Bridge / 491
 - 6.1.1. Capacitor Selection / 493
 - 6.1.2. Diode Conduction Time / 495
 - 6.1.3. RMS Current in the Capacitor / 496
 - 6.1.4. Current in the Diodes / 498
 - 6.1.5. Input Power Factor / 498
 - 6.1.6. A 100-W Rectifier Operated on Universal Mains / 499
 - 6.1.7. Hold-Up Time / 501
 - 6.1.8. Waveforms and Line Impedance / 502
 - 6.1.9. In-Rush Current / 506
 - 6.1.10. Voltage Doubler / 508
- 6.2. Power Factor Correction / 510
 - 6.2.1. Definition of Power Factor / 512
 - 6.2.2. Nonsinusoidal Signals / 512
 - 6.2.3. A Link to the Distortion / 514
 - 6.2.4. Why Power Factor Correction? / 515
 - 6.2.5. Harmonic Limits / 517
 - 6.2.6. A Need for Storage / 518
 - 6.2.7. Passive PFC / 520
 - 6.2.8. Improving the Harmonic Content / 524
 - 6.2.9. The Valley-Fill Passive Corrector / 526
 - 6.2.10. Active Power Factor Correction / 527
 - 6.2.11. Different Techniques / 528
 - 6.2.12. Constant On-Time Borderline Operation / 529
 - 6.2.13. Frequency Variations in BCM / 531
 - 6.2.14. Averaged Modeling of the BCM Boost / 532
 - 6.2.15. Fixed-Frequency Average Current-Mode Control / 535
 - 6.2.16. Shaping the Current / 540
 - 6.2.17. Fixed-Frequency Peak Current-Mode Control / 543
 - 6.2.18. Compensating the Peak Current-Mode Control PFC / 544
 - 6.2.19. Average Modeling of the Peak Current-Mode PFC / 546
 - 6.2.20. Hysteretic Power Factor Correction / 549
 - 6.2.21. Fixed-Frequency DCM Boost / 550
 - 6.2.22. Flyback Converter / 555
 - 6.2.23. Testing the Flyback PFC / 559
- 6.3. Designing a BCM Boost PFC / 559
 - 6.3.1. Average Simulations / 567
 - 6.3.2. Reducing the Simulation Time / 570
 - 6.3.3. Cycle-by-Cycle Simulation / 571
 - 6.3.4. The Follow-Boost Technique / 574
- What I Should Retain from Chap. 6 / 575
- References / 576

Chapter 7. Simulations and Practical Designs of Flyback Converters

579

- 7.1. An Isolated Buck-Boost / 579
- 7.2. Flyback Waveforms, No Parasitic Elements / 583
- 7.3. Flyback Waveforms with Parasitic Elements / 586
- 7.4. Observing the Drain Signal, No Clamping Action / 588
- 7.5. Clamping the Drain Excursion / 591
- 7.6. DCM, Looking for Valleys / 597
- 7.7. Designing the Clamping Network / 599
 - 7.7.1. The RCD Configuration / 601
 - 7.7.2. Selecting k_c / 604
 - 7.7.3. Curing the Leakage Ringing / 605

CONTENTS

xi

7.7.4.	Which Diode to Select?	/ 609
7.7.5.	Beware of Voltage Variations	/ 610
7.7.6.	TVS Clamp	/ 612
7.8.	Two-Switch Flyback	/ 614
7.9.	Active Clamp	/ 616
7.9.1.	Design Example	/ 622
7.9.2.	Simulation Circuit	/ 625
7.10.	Small-Signal Response of the Flyback Topology	/ 628
7.10.1.	DCM Voltage Mode	/ 628
7.10.2.	CCM Voltage Mode	/ 635
7.10.3.	DCM Current Mode	/ 636
7.10.4.	CCM Current Mode	/ 638
7.11.	Practical Considerations about the Flyback	/ 642
7.11.1.	Start-Up of the Controller	/ 642
7.11.2.	Start-Up Resistor Design Example	/ 644
7.11.3.	Half-Wave Connection	/ 646
7.11.4.	Good Riddance, Start-up Resistor!	/ 648
7.11.5.	High-Voltage Current Source	/ 649
7.11.6.	The Auxiliary Winding	/ 651
7.11.7.	Short-Circuit Protection	/ 653
7.11.8.	Observing the Feedback Pin	/ 654
7.11.9.	Compensating the Propagation Delay	/ 655
7.11.10.	Sensing the Secondary Side Current	/ 660
7.11.11.	Improving the Drive Capability	/ 662
7.11.12.	Overvoltage Protection	/ 663
7.12.	Standby Power of Converters	/ 665
7.12.1.	What Is Standby Power?	/ 666
7.12.2.	The Origins of Losses	/ 666
7.12.3.	Skipping Unwanted Cycles	/ 667
7.12.4.	Skipping Cycles with a UC384X	/ 669
7.12.5.	Frequency Foldback	/ 670
7.13.	A 20-W, Single-Output Power Supply	/ 670
7.14.	A 90-W, Single-Output Power Supply	/ 687
7.15.	A 35-W, Multioutput Power Supply	/ 706
7.16.	Component Constraints for the Flyback Converter	/ 725
	What I Should Retain from Chap. 7	/ 726
	References	/ 727
	Appendix 7A Reading the Waveforms to Extract the Transformer Parameters	/ 727
	Appendix 7B The Stress	/ 729
	7B.1. Voltage	/ 730
	7B.2. Current	/ 731
	Appendix 7C Transformer Design for the 90 W Adapter	/ 732
	7C.1. Core Selection	/ 732
	7C.2. Determining the Primary and Secondary Turns	/ 733
	7C.3. Choosing the Primary and Secondary Wire Sizes	/ 734
	7C.4. Choosing the Material, Based on the Desired Inductance, or Gapping the Core If Necessary	/ 735
	7C.5. Designs Using Intusoft Magnetic Designer	/ 735

Chapter 8. Simulations and Practical Designs of Forward Converters **739**

8.1.	An Isolated Buck Converter	/ 739
8.1.1.	Need for a Complete Core Reset	/ 742
8.2.	Reset Solution 1, a Third Winding	/ 746
8.2.1.	Leakage Inductance and Overlap	/ 752
8.3.	Reset Solution 2, a Two-Switch Configuration	/ 756
8.3.1.	Two-Switch Forward and Half-Bridge Driver	/ 760
8.4.	Reset Solution 3, the Resonant Demagnetization	/ 762

xii CONTENTS

8.5. Reset Solution 4, the RCD Clamp	/ 767
8.6. Reset Solution 5, the Active Clamp	/ 778
8.7. Synchronous Rectification	/ 796
8.8. Multioutput Forward Converters	/ 799
8.8.1. Magnetic Amplifiers	/ 799
8.8.2. Synchronous Postregulation	/ 804
8.8.3. Coupled Inductors	/ 806
8.9. Small-Signal Response of the Forward Converter	/ 817
8.9.1. Voltage Mode	/ 817
8.9.2. Current Mode	/ 821
8.9.3. Multioutput Forward	/ 825
8.10. A Single-Output 12-V, 250-W Forward Design Example	/ 828
8.10.1. MOSFET Selection	/ 833
8.10.2. Installing a Snubber	/ 835
8.10.3. Diode Selection	/ 838
8.10.4. Small-Signal Analysis	/ 839
8.10.5. Transient Results	/ 841
8.10.6. Short-Circuit Protection	/ 846
8.11. Component Constraints for the Forward Converter	/ 849
What I Should Retain from Chap. 8	/ 849
References	/ 850
Appendix 8A Half-Bridge Drivers Using the Bootstrap Technique	/ 851
Appendix 8B Impedance Reflections	/ 855
Appendix 8C Transformer and Inductor Designs for the 250-W Adapter	/ 859
8C.1. Transformer Variables	/ 859
8C.2. Transformer Core Selection	/ 859
8C.3. Determining the Primary and Secondary Turns	/ 860
8C.4. Choosing the Primary and Secondary Wire Sizes	/ 861
8C.5. Gapping the Core	/ 861
8C.6. Designs Using Intusoft Magnetic Designer	/ 862
8C.7. Inductor Design	/ 865
8C.8. Core Selection	/ 866
8C.9. Choosing the Wire Size and Checking the DC Resistive Loss	/ 867
8C.10. Checking the Core Loss	/ 867
8C.11. Estimating the Temperature Rise	/ 867
Appendix 8D CD-ROM Content	/ 868

Conclusion 869**Index 871**